



FACULTY OF INFORMATION TECHNOLOGY

COMPUTER SYSTEMS ENGINEERING DEPARTMENT

DIGITAL ELECTRONICS AND COMPUTER ORGANIZATION LAB (ENCS 211)

Prelab - Experiment III

Encoders, Decoders, Multiplexers and Demultiplexers

**Prepared for:
Ms. Bayan Nimer**

**Assistant:
Mus'ab B'airat**

**Student Name: Baibers Qasem
Student Number: 1082092**

Due to: 28-10-2013

a) $Y=f(A, B, C) = AB'+B'C$

$$F(A,B,C) = AB'(C+C') + (A+A')B'C$$

$$= AB'C + AB'C' + AB'C + A'B'C$$

$$= \sum(1,4,5)$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

b) The input connections necessary to implement the function in part (a) is shown in figure (1).

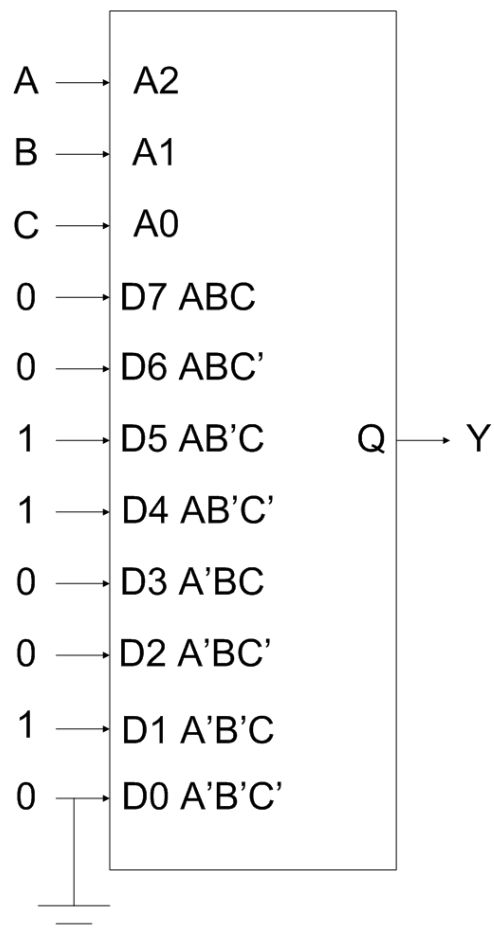


Figure (1): 8-to-1 MUX.

c) Refer to function in (a) to fill the table below.

A	B	C	Y	Y'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

3-

a) Convert the following expression into summation form:

$$Y = A'BC + BC'$$

$$Y = A'BC + BC' = A'BC + (A+A') BC'$$

$$Y = A'BC + ABC' + A'BC'$$

$$Y = \sum (2, 3, 6)$$

b) The demultiplexer output is selected, and will go low, by the address of inputs A, B, C when the IC is enabled .therefore, we can create the output function Y by summing together the outputs indicated by the summation form above. Since the outputs of the demultiplexers are active–low, this is done with a NAND gate. Connect each of the true minterms output of the demultiplexer to an input of the NAND gate, connect all unused NAND inputs to logic 1.

 


Figure (2): 3-to-8 DeMUX.