

[Dashboard](#) / [My courses](#) / [DIGITAL SYSTEMS-Lecture-1203 - ENCS2340 - Meta](#) / [General](#) / [Second Exam](#)

**Started on** Sunday, 15 August 2021, 3:00 PM

**State** Finished

**Completed on** Sunday, 15 August 2021, 4:02 PM

**Time taken** 1 hour 2 mins


**Grade** 21.88 out of 25.00 (88%)

### Question 1

Complete

Mark 1.25 out of 1.25

 What is the output for the following circuit:



- a. 000101
- b. 001001
- c. 100101
- d. 110101
- e. 101001

The correct answer is:


100101

**Question 2**

Complete

Mark 1.25 out of 1.25

 Assume that I0 has the lowest priority, show the output Y1Y0 for X2X1X0= 111



- a. None is correct
- b. 10
- c. 11
- d. 00
- e. 01

The correct answer is:


11

**Question 3**

Complete

Mark 1.25 out of 1.25

 The circuit has two inputs X and Y each is a 2-bit unsigned number. It has an output number Z such that



the minimum number of bits required for the output number Z is

Select one:

- a. 4
- b. 5
- c. 3
- d. 2

The correct answer is: 5

## Question 4

Complete

Mark 0.63 out of 1.25

A demultiplexer is used to ...

- a. None is correct
- b. Perform serial to parallel conversion
- c. Route the data from single input to one of many outputs
- d. All is correct
- e. Select data from several inputs and route it to single output

The correct answers are:

Route the data from single input to one of many outputs,

Perform serial to parallel conversion

## Question 5

Complete

Mark 1.25 out of 1.25

You asked to design a combinational logic circuit which takes a 4-bit unsigned number  $X$  ( $X_3 X_2 X_1 X_0$ ) as input and produces an output  $F$  which equals the result of integer division of  $X$  by 3 (e.g., if  $X=7$ ,  $F=2$ ). How many bits does the output  $F$  have?

Select one:

- a. 4 bits
- b. 3 bits
- c. 1 bit
- d. 2 bits

The correct answer is: 3 bits

## Question 6

Complete

Mark 1.25 out of 1.25

The size of the smallest multiplexer that can be used to implement any function of the form  $F(A,B,C,D)$  without any other logic gates (not even inverter) is:

- a. 8x1
- b. 32x1
- c. 2x1
- d. 16x1
- e. 4x1

The correct answer is:


16x1

## Question 7

Complete

Mark 1.25 out of 1.25

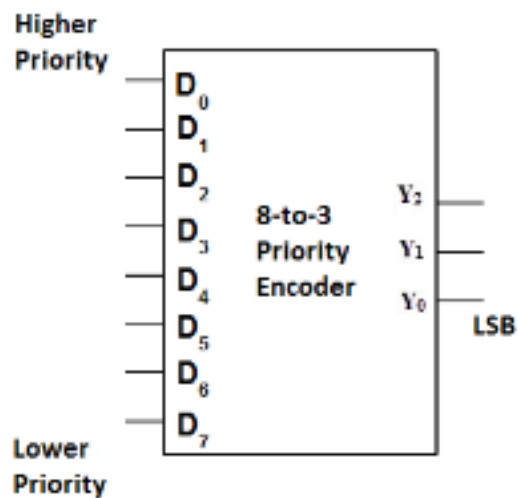In the priority encoder shown below.  $D_0$  is highest priority and  $D_7$  is the lowest priority, the output  $Y_2Y_1Y_0 = 101$  when the status at inputs  $D_0$ - $D_7$  is as described in \_\_\_\_\_ with all other inputs being in a don't care condition.



Select one:

- a.  $D_1 = 1$  and  $D_2 = 1$ .
- b.  $D_3 = 1$  and  $D_5 = 1$ .
- c.  $D_0 = 1$  and  $D_2 = 1$ .
- d.  $D_6 = 1$  and  $D_5 = 1$ .


The correct answer is:  $D_6 = 1$  and  $D_5 = 1$ .

## Question 8

Complete

Mark 1.25 out of 1.25

 Having the following diagram, represent the function  $G$  in terms of  $F_1(a,b,c)$ ,  $F_2(a,b,c)$  and  $X$ .



Select one:

- a.  $X' F_1 + X F_2$
- b.  $X' F_1 + X F_2'$
- c.  $X' F_1 + F_2$
- d.  $X F_1 + X' F_2$
- e.  $X' F_1' + X F_2$


The correct answer is:  $X' F_1 + X F_2$

## Question 9

Complete

Mark 1.25 out of 1.25

 Consider the following diagram of a 3-bit adder:



What is the value of  $s_2$ ,  $s_1$ ,  $s_0$  and  $C_{out}$ , if  $a_2a_1a_0 = 101$  and  $b_2b_1b_0 = 110$  and  $C_{in} = 0$  ?

Select one:

- a.  $s_2 s_1 s_0 = 011$  and  $C_{out} = 1$
- b.  $s_2 s_1 s_0 = 001$  and  $C_{out} = 1$
- c.  $s_2 s_1 s_0 = 011$  and  $C_{out} = 0$
- d.  $s_2 s_1 s_0 = 0110$  and  $C_{out} = 1$
- e.  $s_2 s_1 s_0 = 010$  and  $C_{out} = 1$


The correct answer is:  $s_2 s_1 s_0 = 011$  and  $C_{out} = 1$

## Question 10

Complete

Mark 0.00 out of 1.25

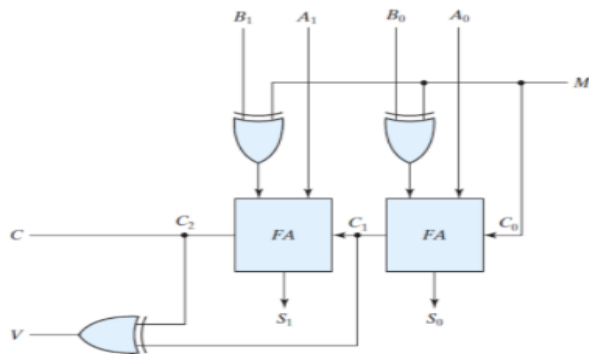For the following two-bit adder/subtractor with overflow detection. If inputs  $M=0$ , two unsigned numbers  $A_1A_0=01$ ,  $B_1B_0=01$ , what's the value of  $S_1$ ,  $S_0$ ,  $C$ , and  $V$ ?



السؤال غير مكتمل

- a.  $S_1 S_0 = 11, C = 1, V = 0$
- b.  $S_1 S_0 = 10, C = 1, V = 1$
- c.  $S_1 S_0 = 10, C = 1, V = 0$
- d.  $S_1 S_0 = 10, C = 0, V = 0$
- e.  $S_1 S_0 = 01, C = 1, V = 0$

The correct answer is:

$S_1 S_0 = 10, C = 1, V = 0$




## Question 11

Complete

Mark 0.00 out of 1.25

The circuit below implements the following function using a MUX, what should be the input labeled (#) connected to?
 
$$F(A,B,C,D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$



- a. 1
- b. 0
- c. D
- d. D'

The correct answer is:



D

Question 12



Complete

Mark 1.25 out of 1.25

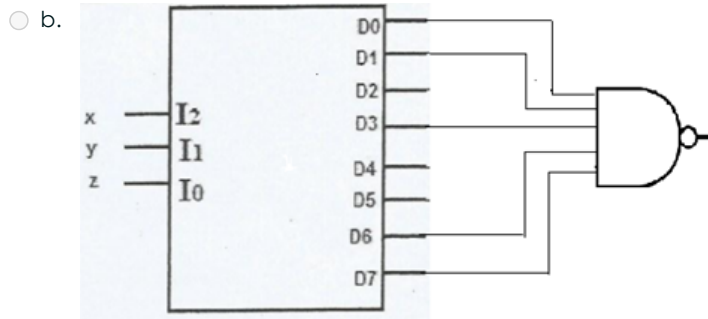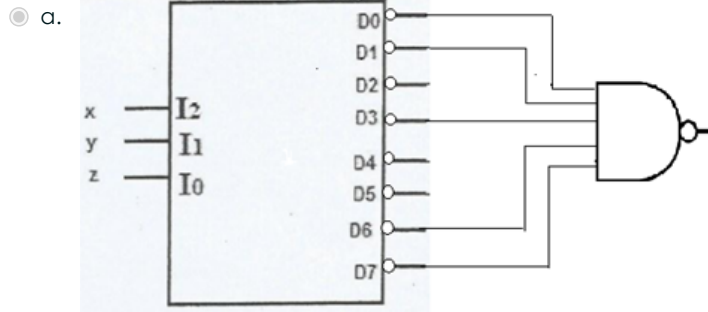
The correct Implementation of  $f(x,y,z) = \prod (2,4,5)$  using 3x8 Decoder and one NAND gate



c. None is correct

  

The correct answer is:

 


**Question 13**

Complete

Mark 1.25 out of 1.25

 Write the reduced Boolean expression for  $F1(X,Y,Z)$ . Given that  $F2(X,Y,Z) = X'YZ$



- a.  $YZ$
- b.  $Y'Z'$
- c.  $Y'+Z'$
- d.  $XY$
- e.  $Y+Z$

The correct answer is:

$YZ$


## Question 14

Complete


Mark 1.25 out of 1.25

Implement  $F(x,y,z) = \Sigma(2,3,4,6,7)$  using Decoder and one NOR gate


a.

 


b.

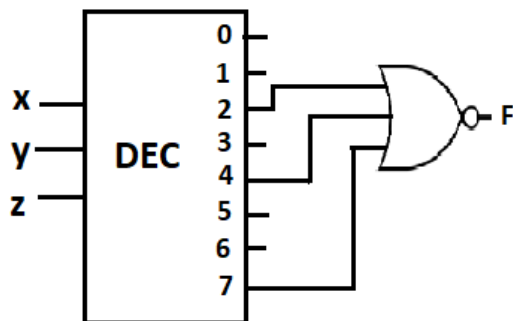


c.

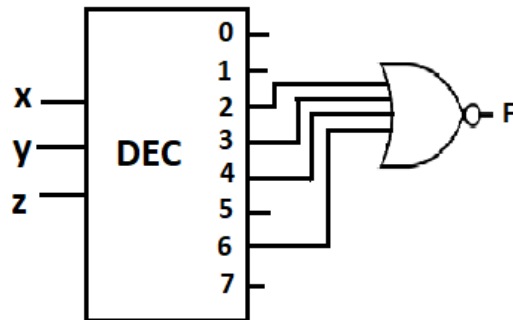

d.

 

The correct answer is:

 

## Question 15

Complete

Mark 1.25 out of 1.25

The following is a Verilog behavioral description for the module *CKT*.

The *CKT* is a \_\_\_\_\_.

```
module CKT(I, Y, X);
```

```
  input [1:0] I;
```

```
  input X;
```

```
  output [0:3] Y;
```

```
  reg [0:3] Y;
```

```
  always @(I or X)
```

```
    case ({X, I})
```

```
      3'b000: Y = 4'b1000;
```

```
      3'b001: Y = 4'b0100;
```

```
      3'b010: Y = 4'b0010;
```

```
      3'b011: Y = 4'b0001;
```

```
      default: Y = 4'b1000;
```

```
    endcase
```

```
endmodule
```

Select one:

- a. 2-to-4 decoder with enable active high enable
- b. 2-to-4 decoder with enable active low enable
- c. 4-to-16 decoder with enable active high enable
- d. 4-to-16 decoder with enable active low enable
- e. 4-to-1 Mux with enable active high enable


The correct answer is: 2-to-4 decoder with enable active low enable

## Question 16

Complete

Mark 1.25 out of 1.25

 Consider the following diagram of a 4-bit adder/ subtractor:



**Configure the value of M, A3, A2, A1, A0** the above circuit to implement 4-bit 2's complement, such that the input is B3 B2 B1 B0, and the output S3 S2 S1 S0= (2's of (B3 B2 B1 B0))

- a. M=1, A3=1, A2=1, A1=1, A0=1
- b. M=0, A3=0, A2=0, A1=0, A0=0
- c. M=1, A3=0, A2=0, A1=0, A0=0
- d. M=0, A3=1, A2=1, A1=1, A0=1

The correct answer is:

**M=1, A3=0, A2=0, A1=0, A0=0**

## Question 17

 
 
 
 
Complete


Mark 1.25 out of 1.25

Implement the following function using **only one 4-to-1 MUX without enable**, no other gates allowed (But invertors are allowed).


$$f(x,y,z) = x \oplus y \oplus z$$

Select one:

 a. b. c. d. e.

 

The correct answer is:

 


**Question 18**

Complete

Mark 1.25 out of 1.25

 The circuit represents the Boolean function



- a.  $F(A, B, C) = A'C + A'B'$
- b.  $F(A, B, C) = ABC + A'B'$
- c.  $F(A, B, C) = AB + A'C + A'B'$
- d. None
- e.  $F(A, B, C) = AB + A'C$

The correct answer is:

$F(A, B, C) = AB + A'C + A'B'$




## Question 19

Complete

Mark 1.25 out of 1.25

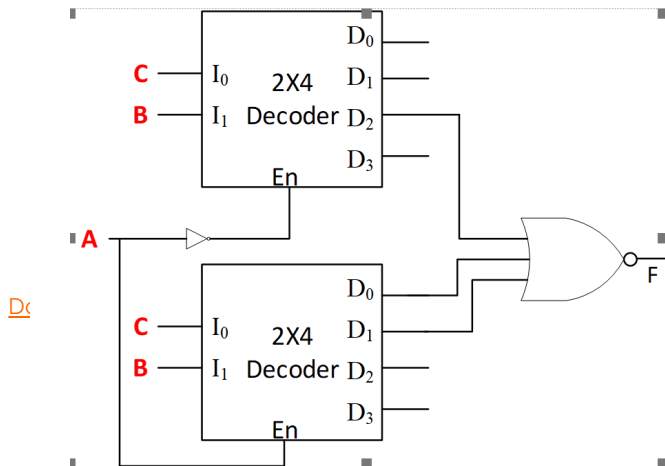The function  $F(A,B,C)$  of this implemented circuit is:



- a. None
- b.  $F = \sum(1, 3, 6, 7)$
- c.  $F = \sum(0, 1, 3, 6, 7)$
- d.  $F = \sum(0, 1, 6, 7)$
- e.  $F = \sum(0, 1, 3, 6)$

The correct answer is:

$$F = \sum(0, 1, 3, 6, 7)$$

## Question 20

Complete

Mark 1.25 out of 1.25

The largest decoder we can build using five 2-to-4 decoders with Enable *without* any additional components is a

Select one:

- a. 4-to-16 decoder
- b. 3-to-8 decoder
- c. 6-to-64 decoder
- d. 5-to-32 decoder

The correct answer is: 4-to-16 decoder

◀ First Exam

Final Exam (All Sections) ▶