

Chapter 3


Gate level Minimization

- How to make cost Reduction for any digital circuit.
- The complexity of digital logic gates is directly proportional to the boolean expression from which the Function implemented.

ex $F = x \cdot y + x \cdot y'$

$F = x(y + y')$

More simplify $F = X$

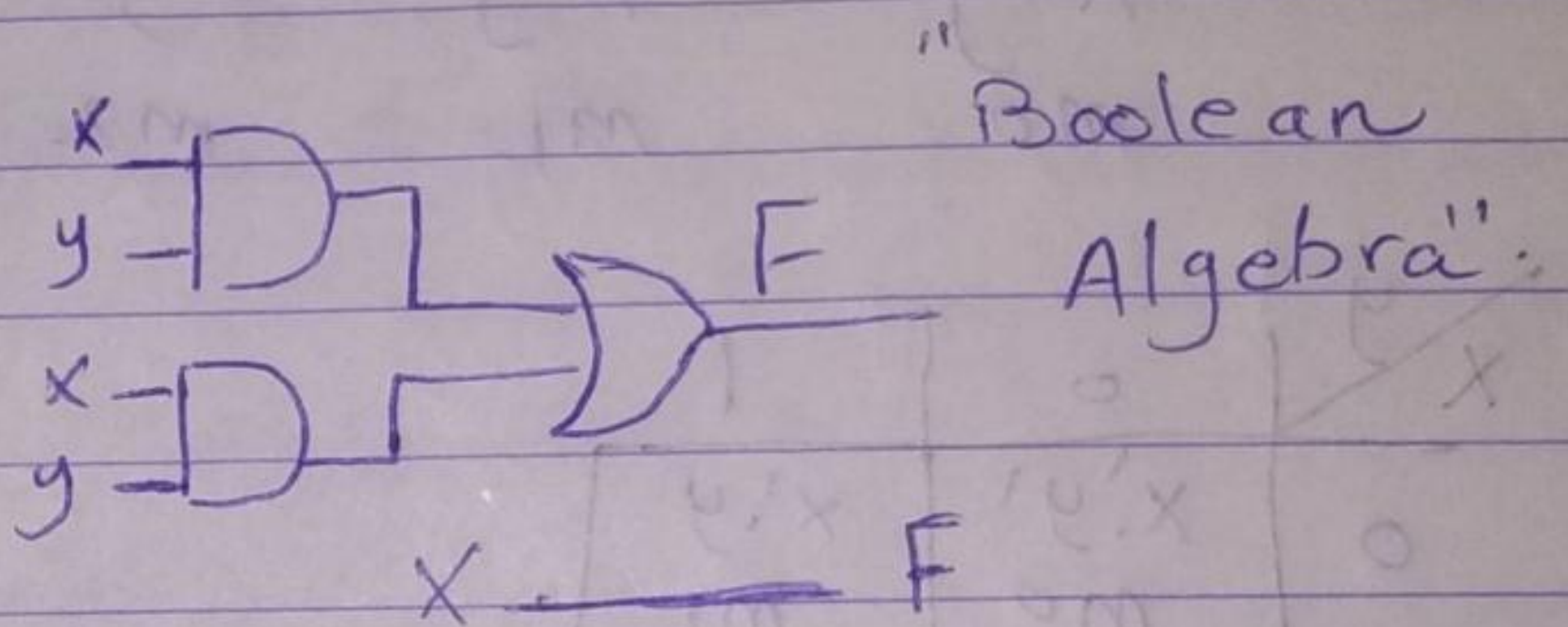

ch2. غير مباشر

* Minimize the Function using algebra is awkward approach, so we need another way for minimization.

is a straight forward approach for minimization.

* Map Method for Minimization.

Note :- Truth table is unique.

$F = x \cdot y + x \cdot y' \equiv F = X$

$X = 0$

$F = 0$

$X = 1$

$F = 1$

Mathematical expression

is not unique.

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

K-map method for minimization.

Diagram made of squares, each square represent one minterm.

ex Two variables maps.

2 variables $\Rightarrow 2^2 = 4$ minterms.

$x'y'$ $x'y$ xy' xy
 m_0 m_1 m_2 m_3

$x \backslash y$	0	1
0	$x'y'$ m_0	$x'y$ m_1
1	$x.y'$ m_2	$x.y$ m_3

ex Minimize the following function.

$$F(x, y) = x'y + x.y' + x.y$$

Sum of minterms.

$$= m_1 + m_2 + m_3 = [1, 2, 3]$$

$$F(x, y) = x'y + x(y + y')$$

$$= x'y + x = (x + x') \cdot (x + y)$$

$x \backslash y$	0	1
0	0	1
1	1	1

one variable


ex $F(x, y) = x' \cdot y' + x' \cdot y + x \cdot y$ Algebra.

$$= x' (y' + y) + x \cdot y$$

$$= x' + x \cdot y$$

$$= (x' + x) \cdot (x' + y) = x' + y$$


K-map :-

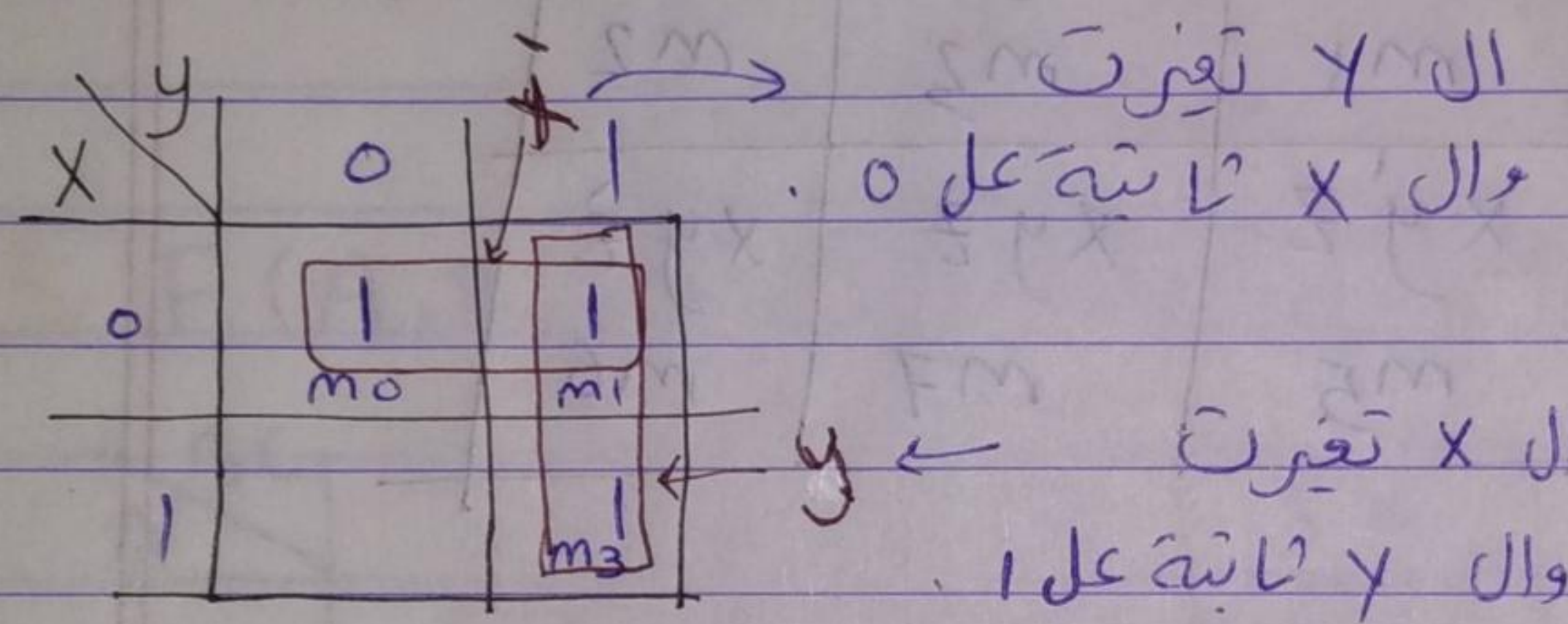

ex $F = x' \cdot y' + x \cdot y$

$$= m_0 + m_3$$

$$F = x' \cdot y' + x \cdot y$$

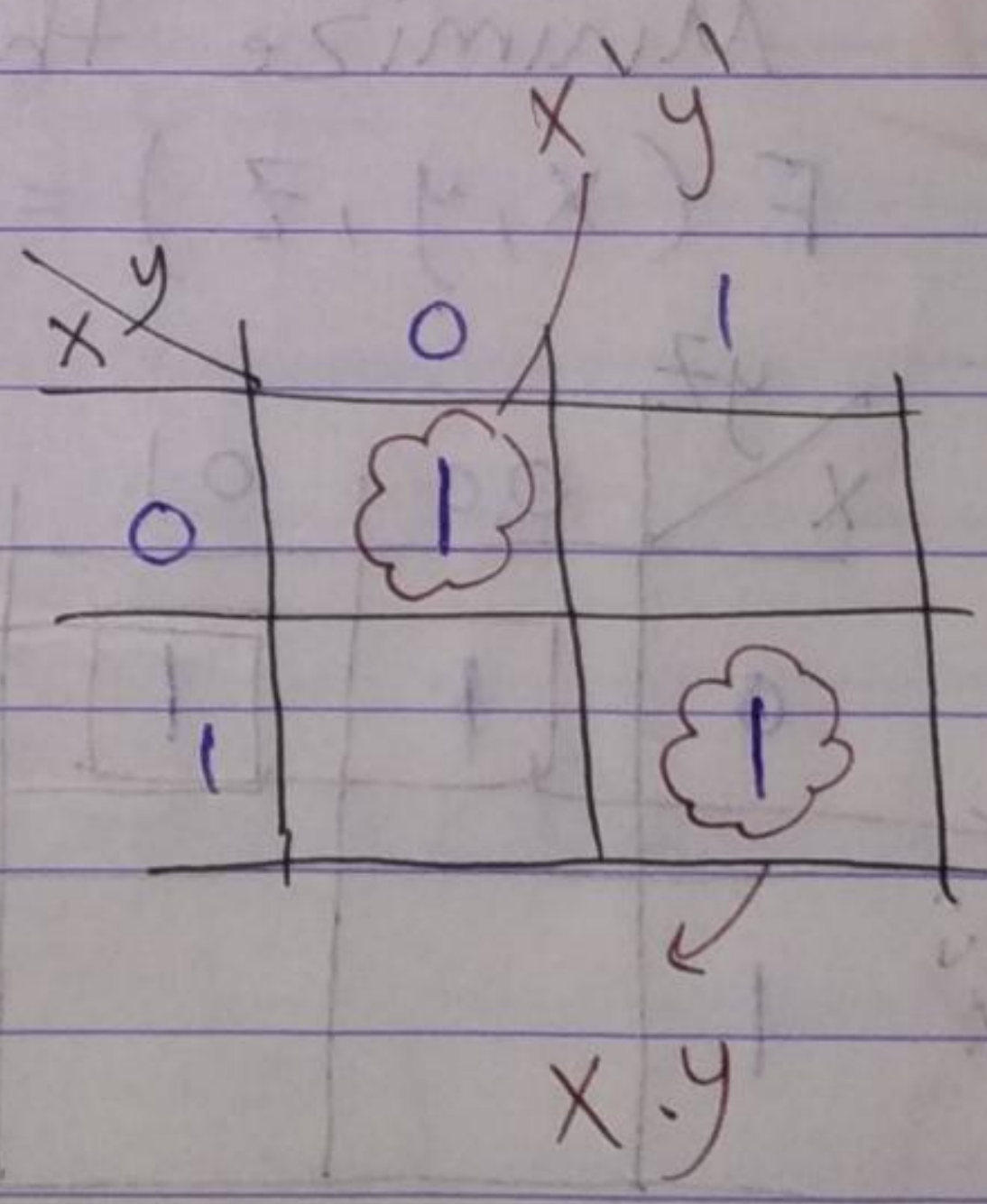

* Three variable maps:

3 variable \Rightarrow max & minterm.
 $=$ 8 squares.

		yz			
	x	00	01	11	10
	0	$x'y'z'$ m0	$x'y'z$ m1	$x'yz$ m3	$x'y'z'$ m2
	1	$xy'z'$ m4	$xy'z$ m5	xyz m7	xyz m6

ex Minimize the following function using k-maps
 $F(x, y, z) = \sum (0, 1, 3, 7)$

		yz			
	x	00	01	11	10
	0	1	1	1	
	1			1	

\downarrow y.z

$$x \cdot y' + y \cdot z$$

ex $F(A, B, C) = \sum (0, 1, 2, 3)$

A \ BC	00	01	11	10
0	1	1	1	1
1	0	0	0	0

← A'

ex $F(A, B, C) = \sum (0, 1, 2, 3, 4, 6)$

A \ BC	00	01	11	10
0	1	1	1	1
1	1	0	0	1

← A'

← C'

← A' + C'

ex $F(A, B, C) = \sum (0, 2, 4, 5, 6, 7)$

A \ BC	00	01	11	10
0	1	0	0	1
1	1	1	1	1

← A

← A + C'

ex $F(A, B, C) = \sum 3, 5, 6, 7$

	BC	00	01	11	10
A	0	0	1	1	0
1	1	1	1	1	0

AC (points to the 1s in row A=1, column BC=01 and 11)
A.B (points to the 1s in row A=1, column BC=11 and 10)
B.C (points to the 1s in column BC=11, row A=0 and 1)

$AC + BC + AB$

* Four variables maps :-

$F(A, B, C, D) = 4$ variables.

16 minterms = 16 squares.

	CD	00	01	11	10
AB	00	$ABCD'$ m ₀	$A'B'CD'$ m ₁	$A'BCD'$ m ₃	$A'B'CD$ m ₂
	01	$A'BCD'$ m ₄	$AB'CD'$ m ₅	$A'BCD$ m ₇	$ABCD'$ m ₆
	11	$ABCD'$ m ₁₂	$AB'CD$ m ₁₃	$ABCD$ m ₁₅	$ABCD'$ m ₁₄
	10	$AB'CD$ m ₈	$AB'CD'$ m ₉	$AB'CD$ m ₁₁	$A'BCD'$ m ₁₀

ex Minimize using K-map.

$$F(A, B, C, D) = \sum (0, 1, 4, 5, 7)$$

AB \ CD	00	01	11	10
00	1	1		
01	1	1	1	
11				
10				

$$\bar{A}\bar{C} + \bar{A}BD$$

ex Minimize using K-map.


$$F(A, B, C, D) = \sum (0, 2, 4, 6, 8, 10)$$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11				
10	1			1

$$\bar{A}\bar{D} + \bar{B}\bar{D}$$


ex $F(A, B, C, D) = \sum(0, 1, 2, 3, 5, 7, 13, 15, 9, 11)$.

AB \ CD	00	01	11	10
00	1	1	1	1
01		1	1	
11		1	1	
10		1	1	

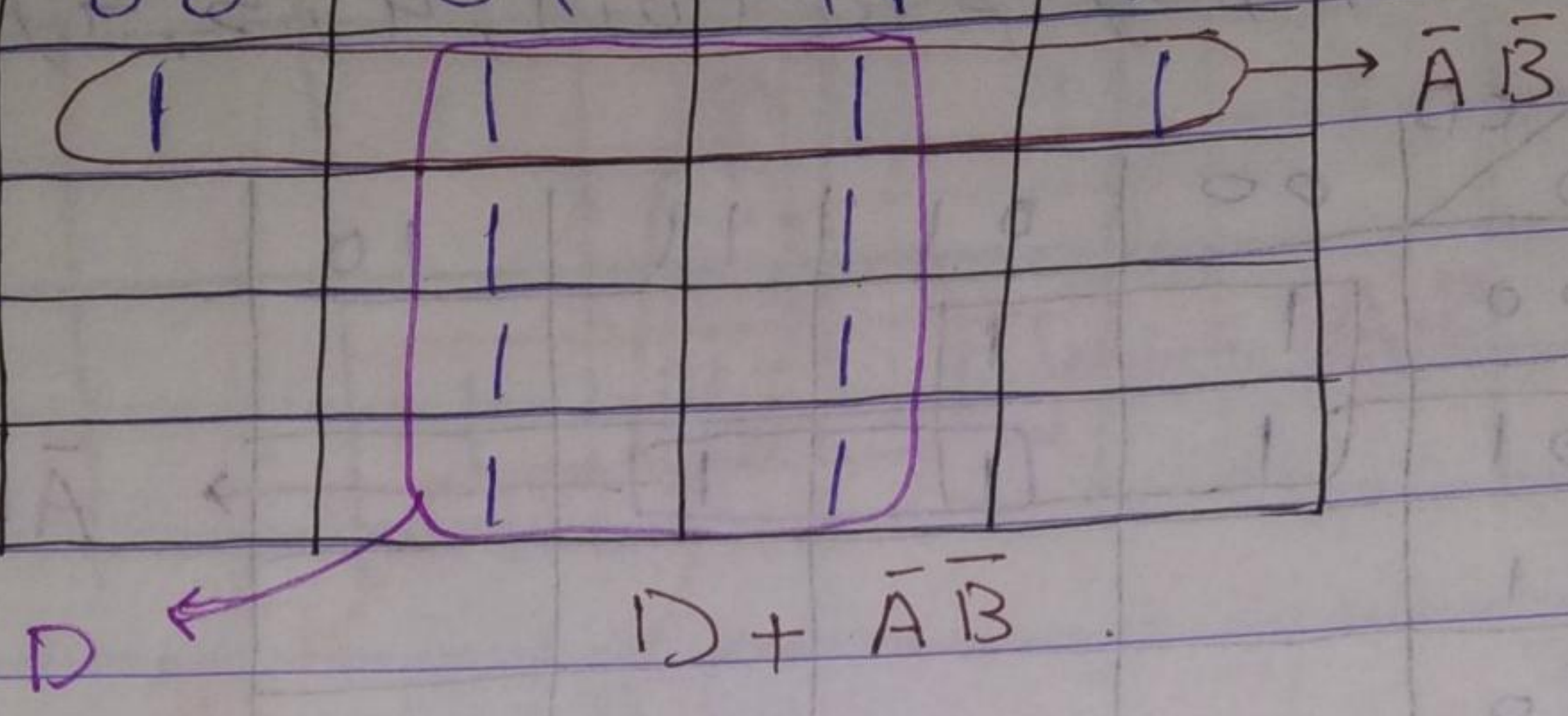

ex $F(A, B, C, D) = \sum(0, 2, 4, 6, 8, 10, 12, 14)$.

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	1			1
10	1			1

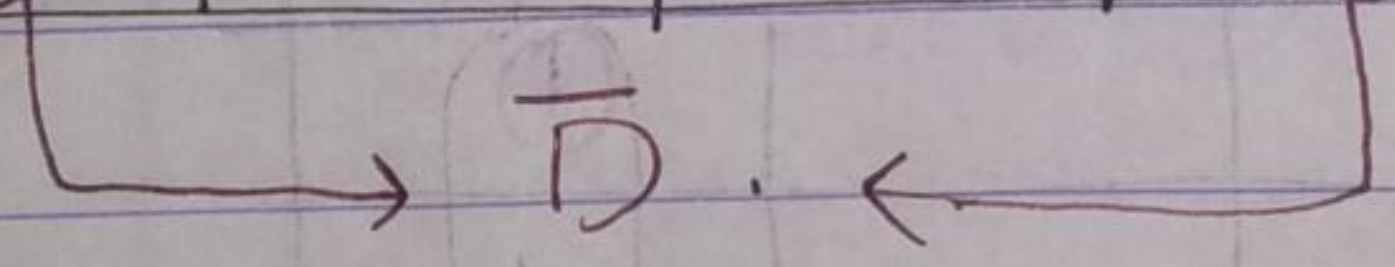

* Five variables maps = 32 minterms.

Note :- $F(A, B, C) = \sum 0, 2, 4, 6$.

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Handwritten notes: $n=0$ (circled around rows 1-4), $n=1$ (circled around rows 5-8).

A	B
0	0

C	F
0	1
1	0

AB = 01
C F
0 1
1 0

AB = 10
C F
0 1
1 0

AB = 11
C F
0 1
1 0

ex Minimize $F(A, B, C, D, E) = \{0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31\}$

A = 0


A = 1

BC \ DE	00	01	11	10
00	ABCDE m0	m1	m3	ABCDE m2
01	m4	m5	m7	m6
11	m12	m13	ABCDE m5	m14
10	m8	m9	m11	m10

BC \ DE	00	01	11	10
00	m16	m17	m19	m18
01	m20	m21	m23	m22
11	m28	m29	m31	m30
10	m24	m25	m27	m26

BC \ DE	00	01	11	10
00	1			1
01	1			1
11		1		
10		1		

BC \ DE	00	01	11	10
00				
01		1	1	
11		1	1	
10			1	

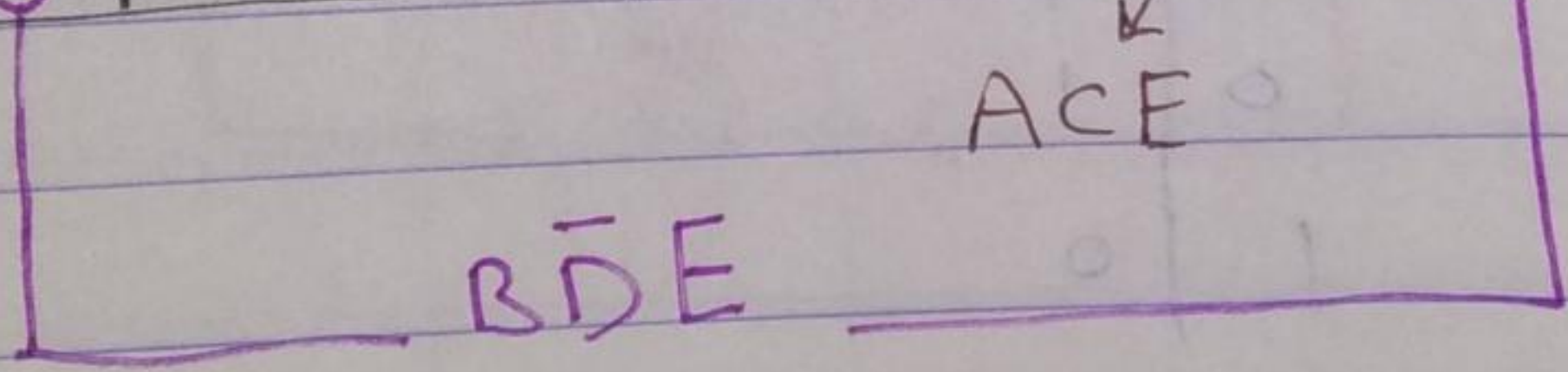

$$\bar{A}\bar{B}\bar{E} + A\bar{D}\bar{E} + ACE$$

* 6 variable maps. (algebra)


$$F(A, B, C, D, E, G) = \sum$$

$$\underline{AB = 00}$$

$$\underline{AB = 01}$$

$$\underline{AB = 11}$$

$$\underline{AB = 10}$$

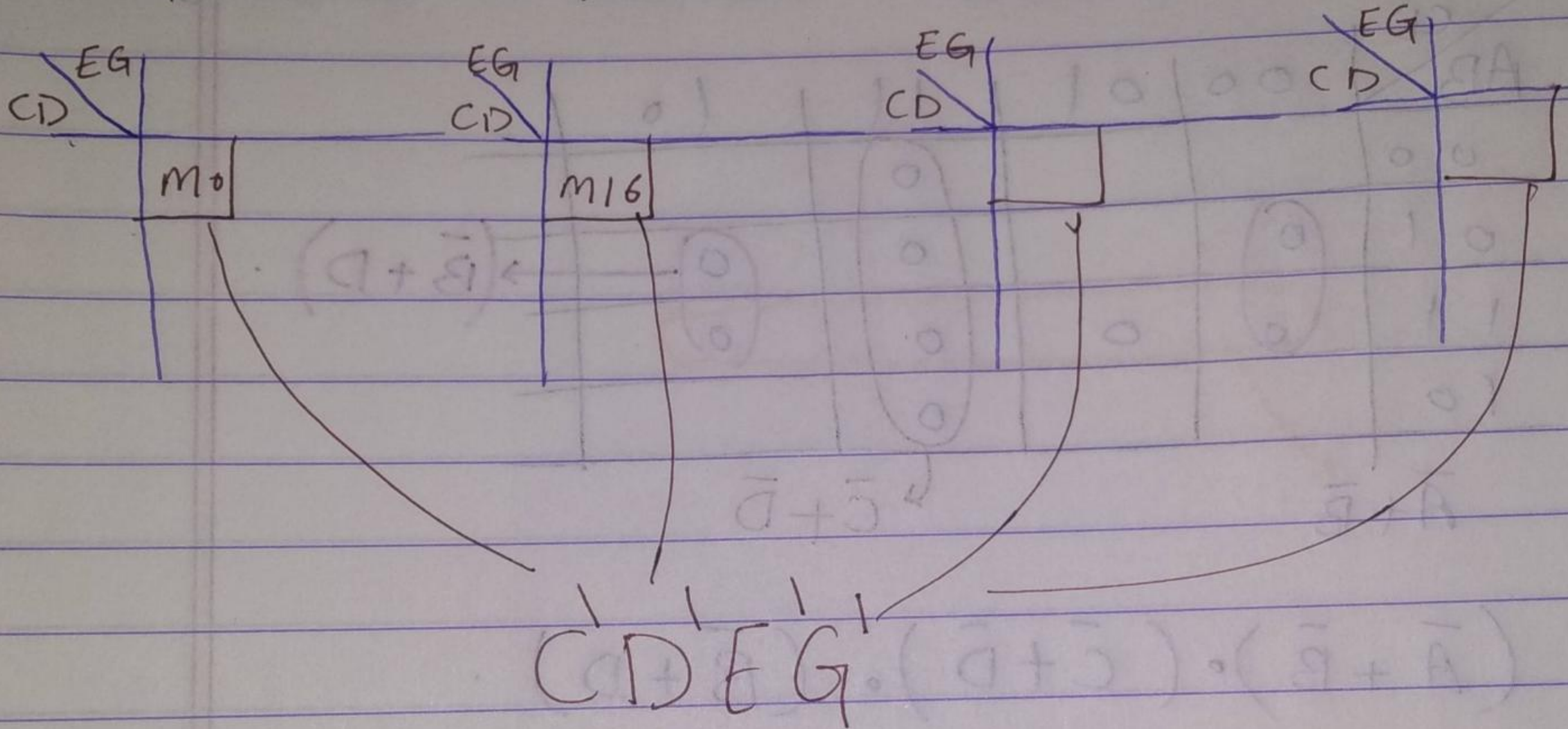

* product of maxterm :-

Simplify the following function.

$$F(A, B, C, D) = \Pi(3, 4, 6, 7, 11, 12, 13, 14, 15)$$

AB \ CD	00	01	11	10
00			0	
01	0		0	0
11	0	0	0	0
10			0	

$\bar{A} + \bar{B}$ $\bar{C} + \bar{D}$ $(\bar{B} + D)$

$$(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \cdot (\bar{B} + D)$$

* Don't Care Condition *

Function that have unspecified outputs for some inputs.

The unspecified minterm of a function are don't care condition denoted by X.

ex Simplify the boolean function.

$$F(w, x, y, z) = \sum (1, 3, 7, 11, 15)$$

that has don't care condition.

$$d(w, x, y, z) = \sum (0, 2, 5)$$

w	x	y	z	F
0	0	0	0	X
0	0	0	1	1
0	0	1	0	X
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	1

w \ x \ yz	00	01	11	10
00	X	1	1	X
01	1	X	1	
11			1	
10			1	

$$w'z + yz$$

* أو بتقدير نعمل الصف الأول والحدان

ونفخذ الصف الأول بتفسير

$$yz + w'x'$$

* Prime Implicant (PI)

ex $F(A, B, C, D) = \sum (0, 2, 5, 7, 8, 10, 13, 15)$

CD \ AB	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1

$B'D'$ [essential PI] \rightarrow 0, 2, 8, 10
 [= term]
 BD [term essential] \rightarrow 5, 7, 13, 15
 [essential PI]

$F(A, B, C, D) = \sum (0, 2, 5, 7, 8, 10, 13, 14, 15)$

CD \ AB	00	01	11	10
00	1			1
01		1	1	1
11	x	1	1	1
10	1			1

$B'D'$ [EPI]
 BC [PI] ①
 CD' [PI] ②
 BD [EPI]

not essential
 (لا يوجد، نه لو بطريقتين)

① - $BD + B'D' + CD'$

② - $BD + B'D' + BC$

ex $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 9, 10, 11, 13, 15)$

AB \ CD	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1	1	1	1

AB' (green box around row 10)
AD (orange box around columns 01, 11, 10)

$B'D'$ [EPI] . لأن ال 0, 2
 ما بتقدر تكتبها إلا بطريقة واحدة .

BD [EPI]

$$F = B'D' + BD + AD$$

$$= BD' + BD + AB'$$

ex $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 9, 10, 11, 13, 14, 15, 6)$


AB \ CD	00	01	11	10
00	1			1
01		1	1	1
11		1	1	1
10	1	1	1	1

AD (green box around columns 01, 11, 10)
BC (purple box around rows 01, 11)

$B'D'$ (EPI) . $A = 7$

BC (PT) . $B'A = 0$



AD (PI)

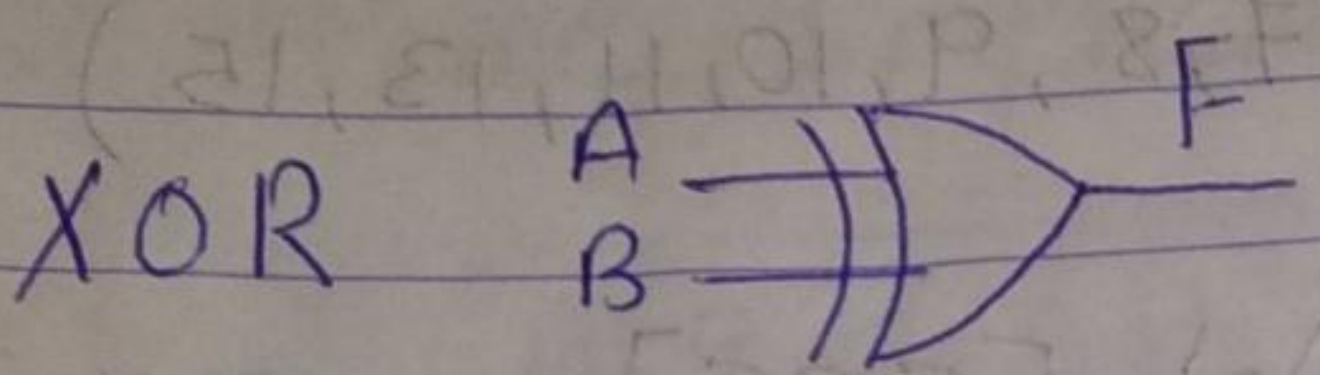

A	B	F
0	0	0
0	1	1 ← A'B
1	0	1 ← AB'
1	1	0

$$F = m_1 + m_2$$

$$= A'B + AB'$$

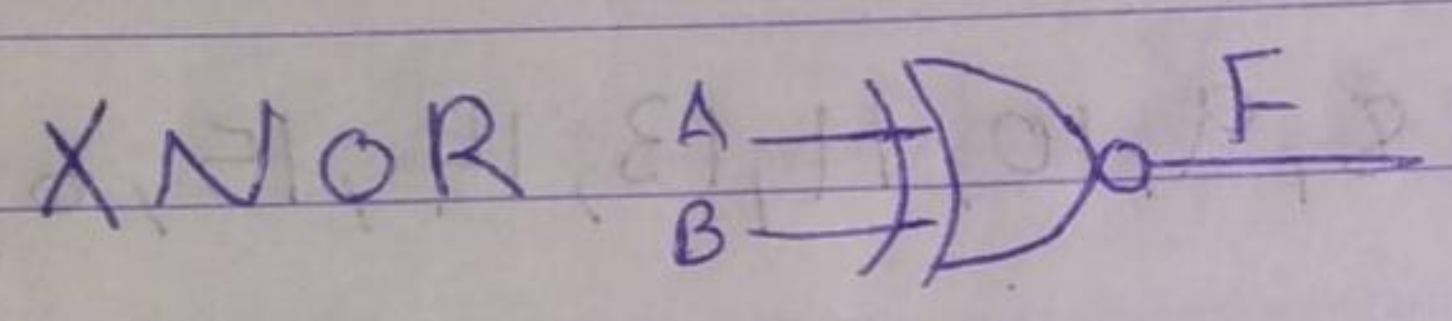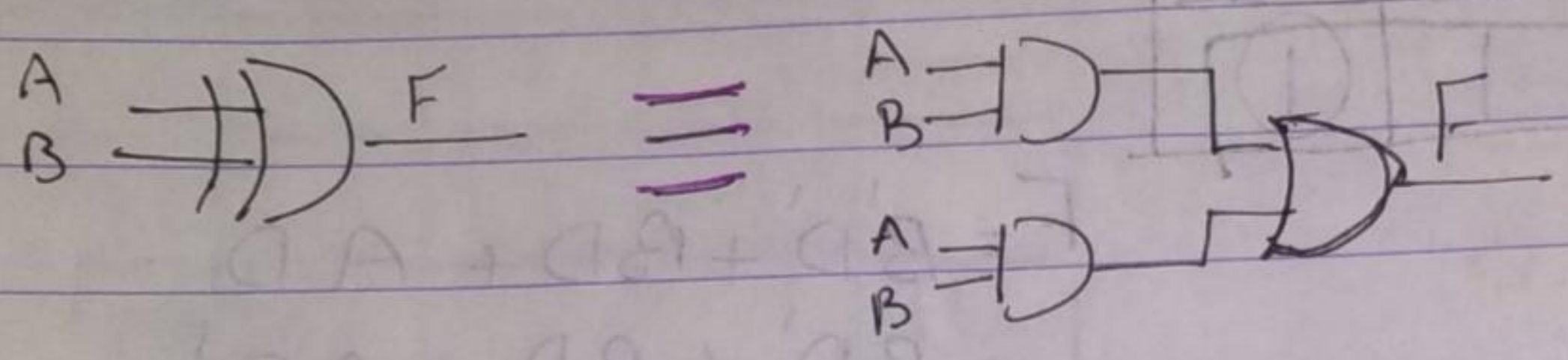

A	B	F
0	0	1 ← A'B'
0	1	0
1	0	0
1	1	1 ← AB

$$F = \overline{A \oplus B}$$

$$F = m_0 + m_3$$

$$= A'B' + AB$$

$$(A'B + AB')' \equiv A'B + AB$$

$$XNOR = (A \oplus B)' = [A'B + AB']'$$

$$= (A'B)' \cdot (AB')'$$

$$= (A + B') \cdot (A' + B)$$

$$= \cancel{AA'} + AB + A'B' + \cancel{B'B}$$



$$= AB + A'B'$$

Note All gates are associated except


NAND

NOR


$$(A + B + C) \oplus R = (A + B) + C$$

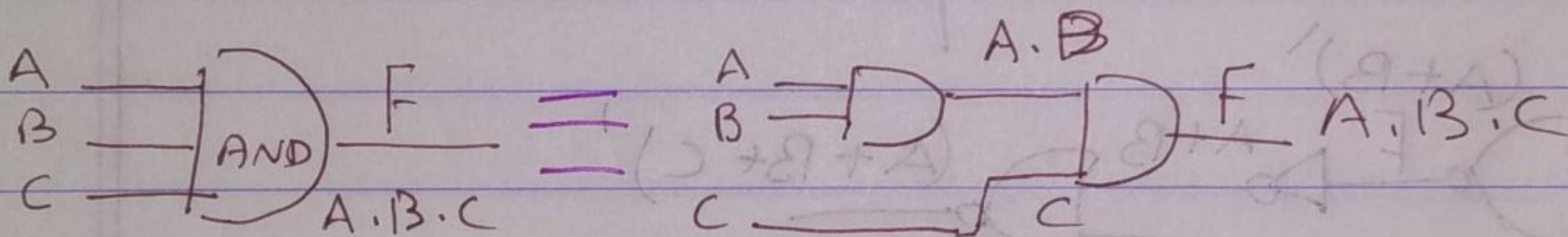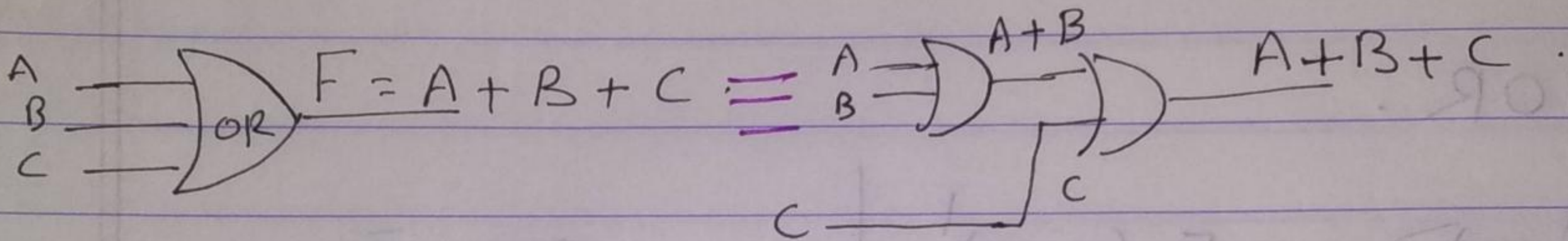



NAND

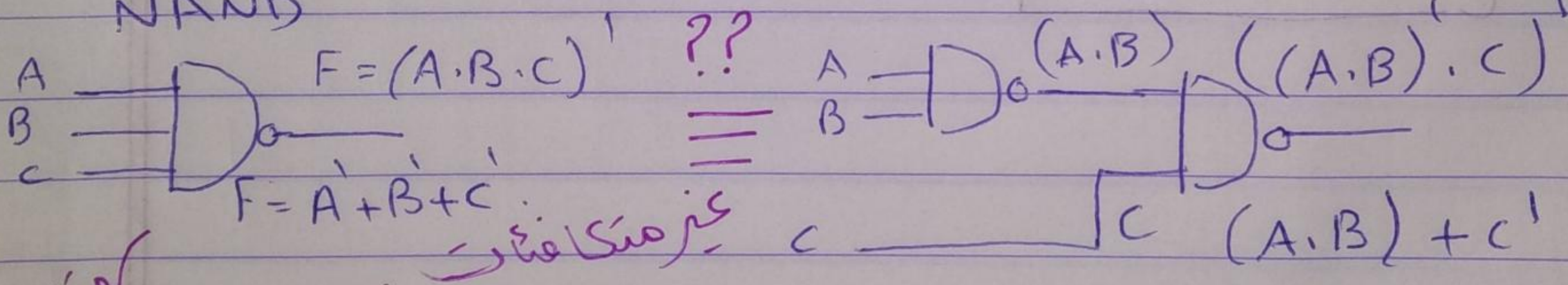

سكا افتار


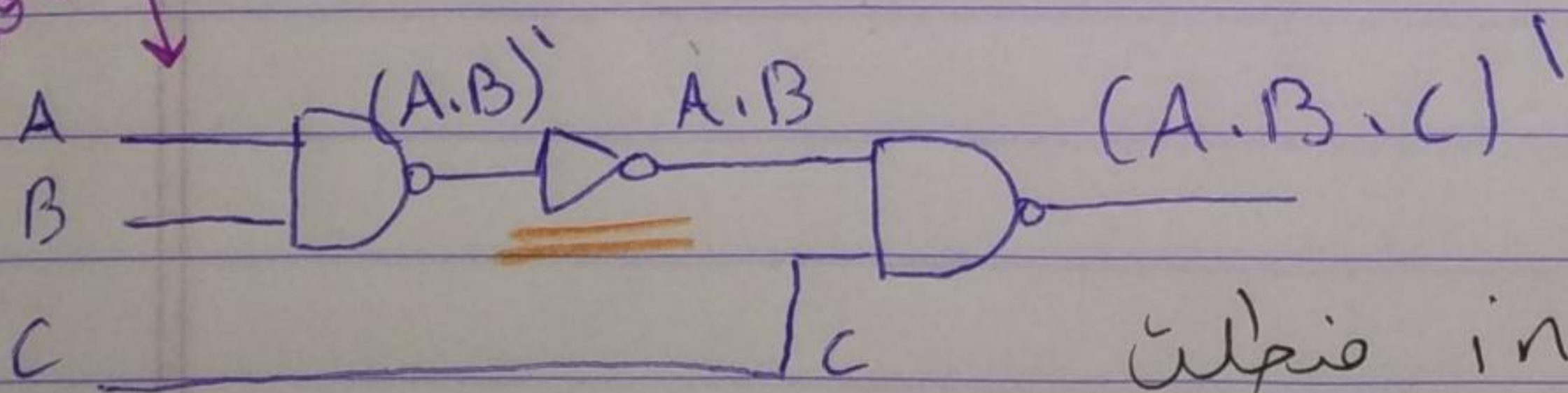


inverter liep associated.

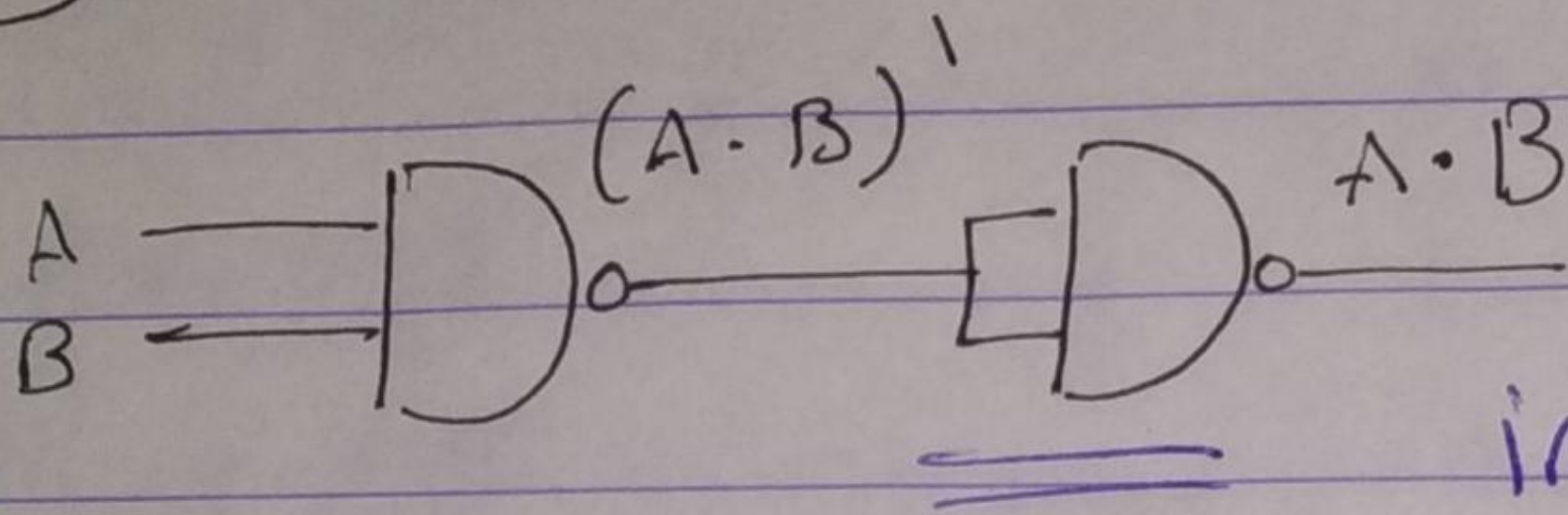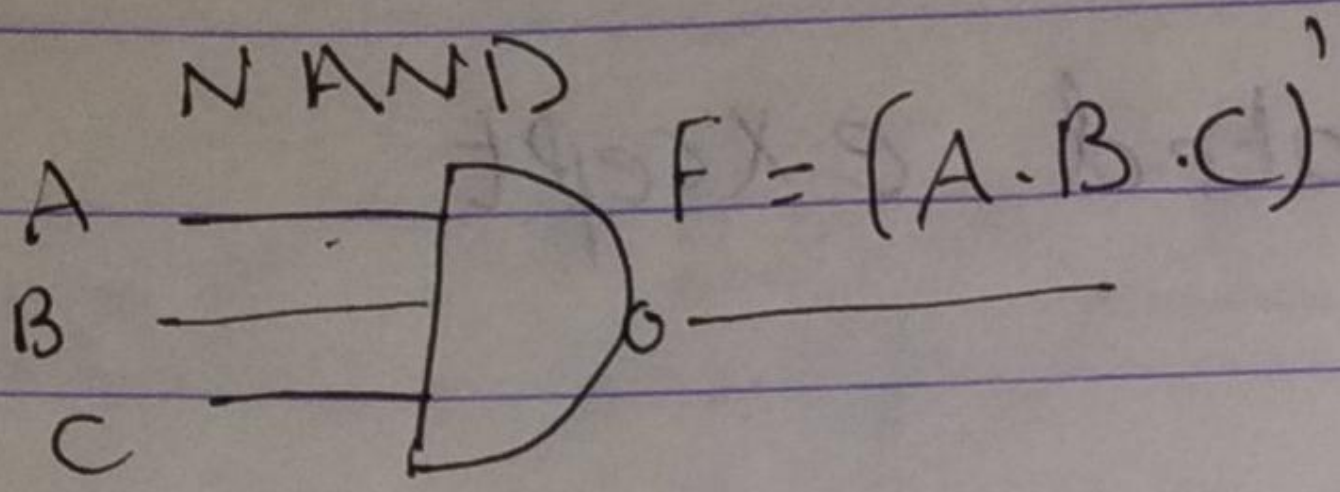

inverter *

NOR

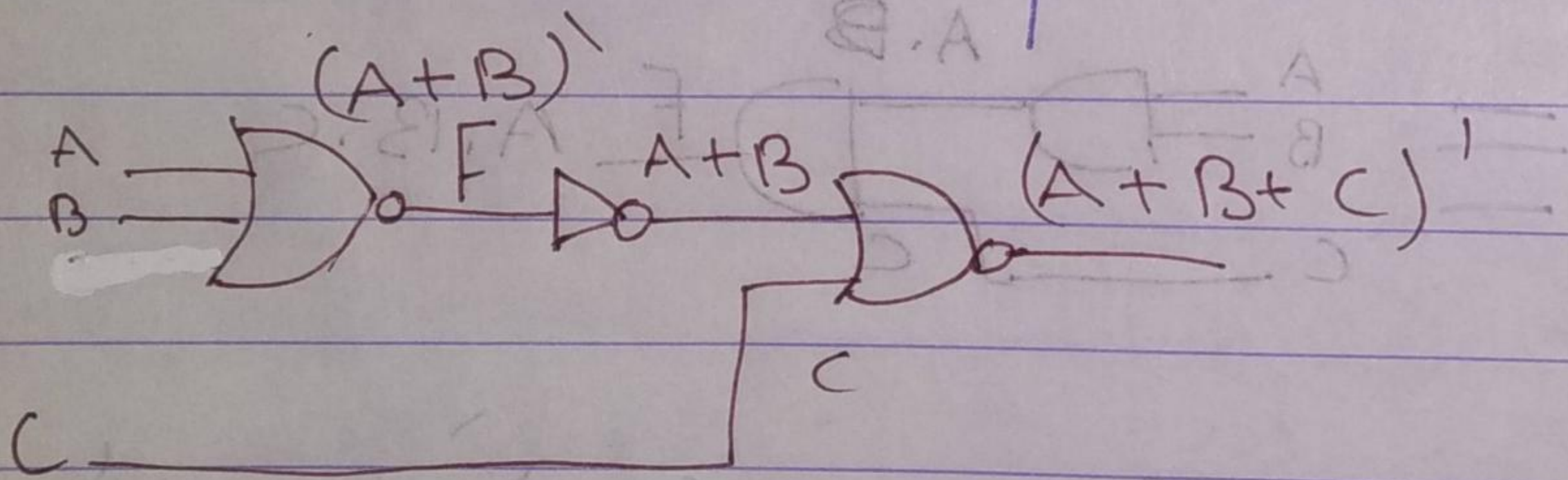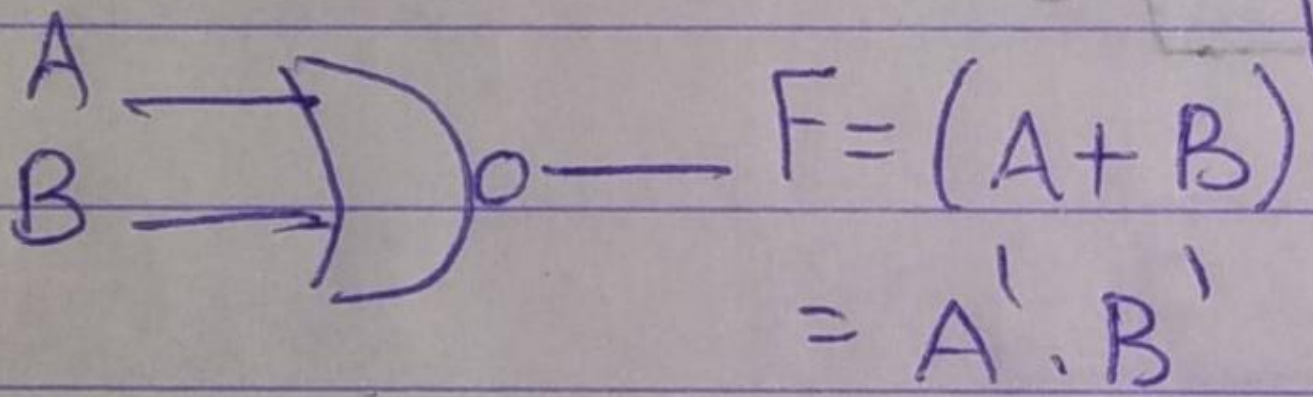


NAND & NOR Implementation.

Digital circuits are more frequently constructed with NAND/NOR than and/or.

① NAND/NOR use fewer number of transistors.



so ① it's cheaper. ② less delay.

③ NAND/NOR universal gates.

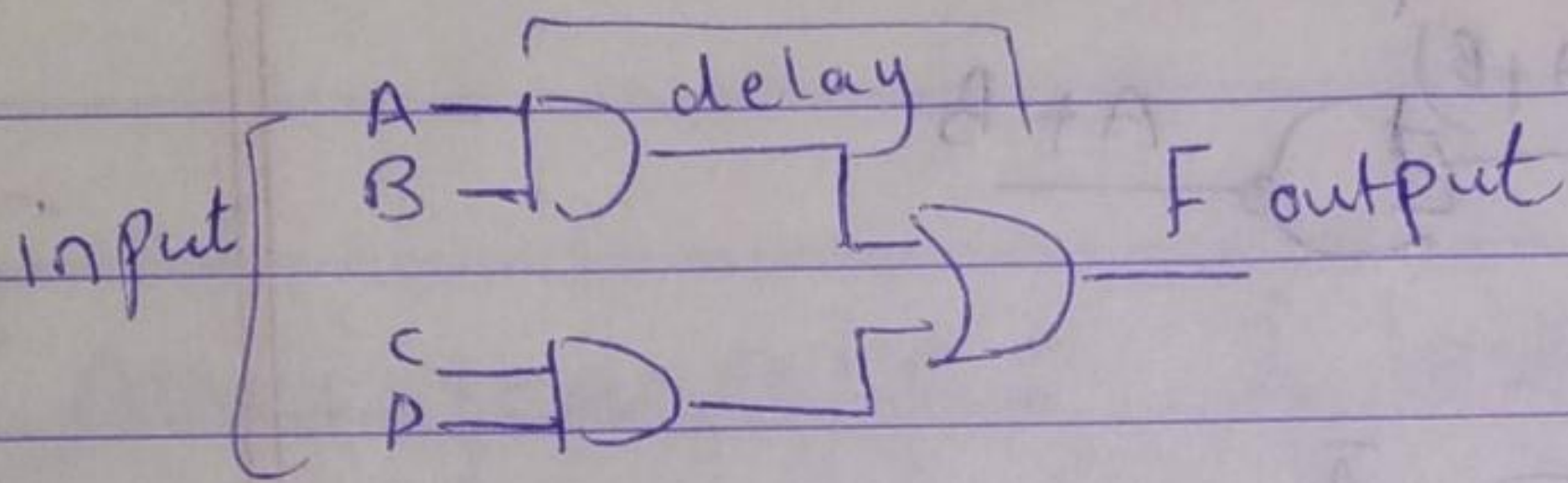


$$A \quad B \quad \left| \quad F = (A \cdot B)' = \bar{A} + \bar{B}$$


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

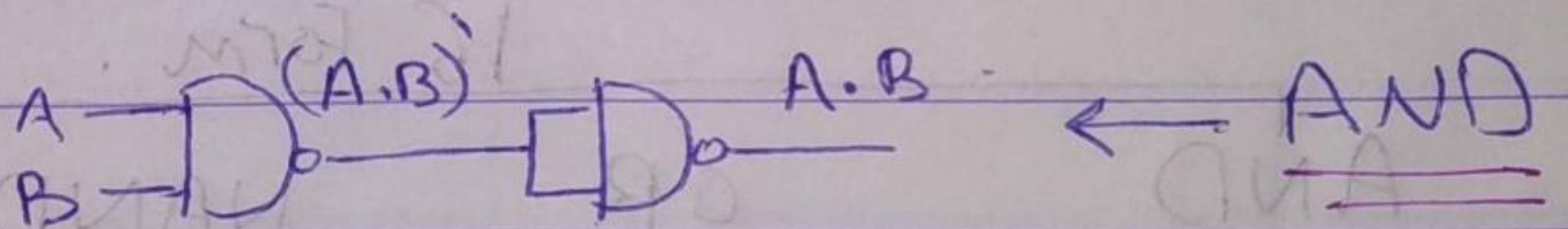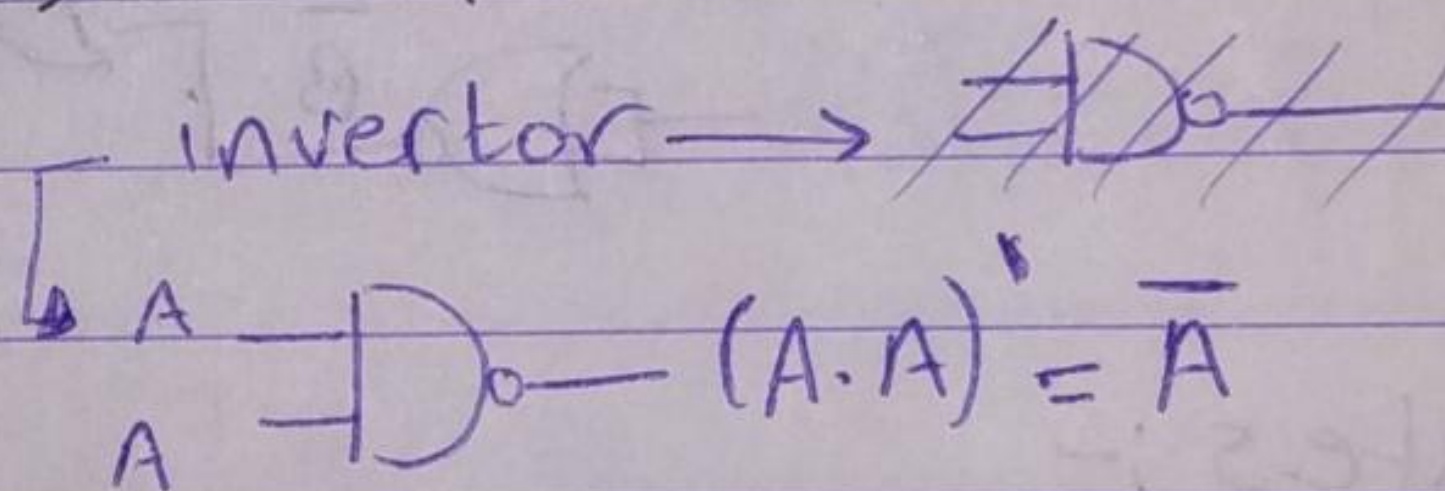

③ OR

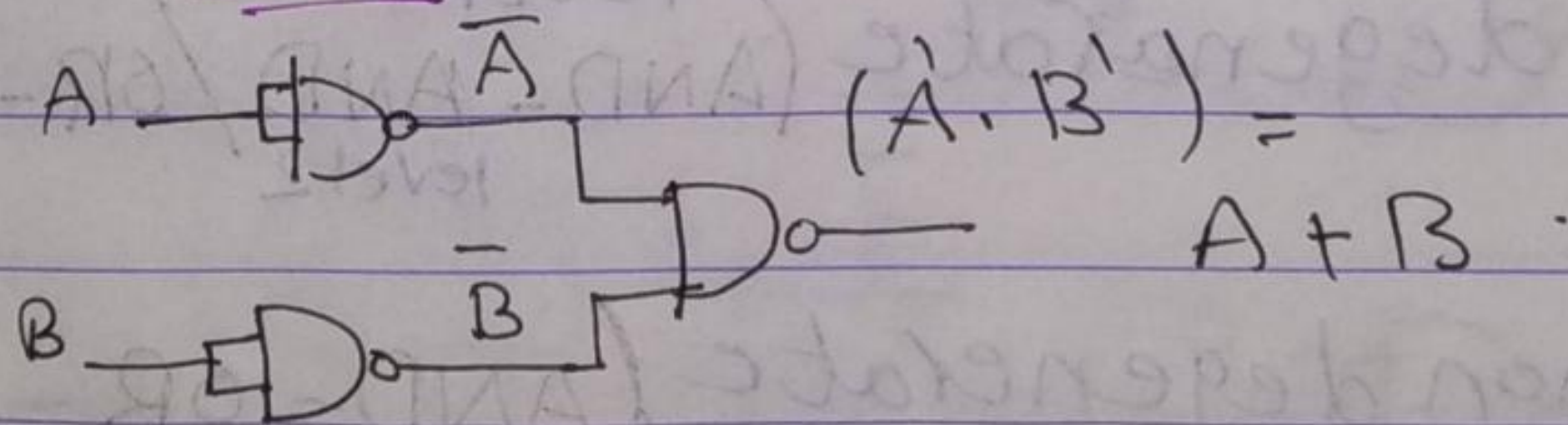


Transistor is an Electronic Device

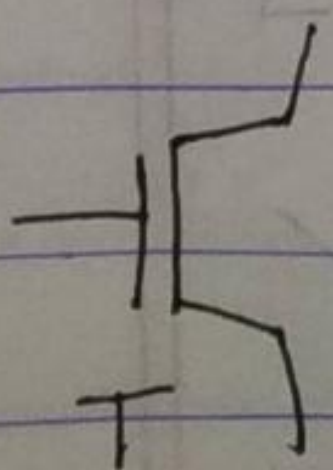




لا يوصل (لا يوصل) ، ولا يوصل
open circuit

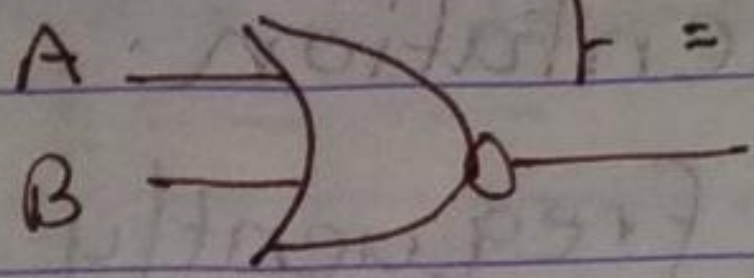NOR. $F = (A+B)'$ $= \bar{A} \cdot \bar{B}$



A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

(1) Inverter

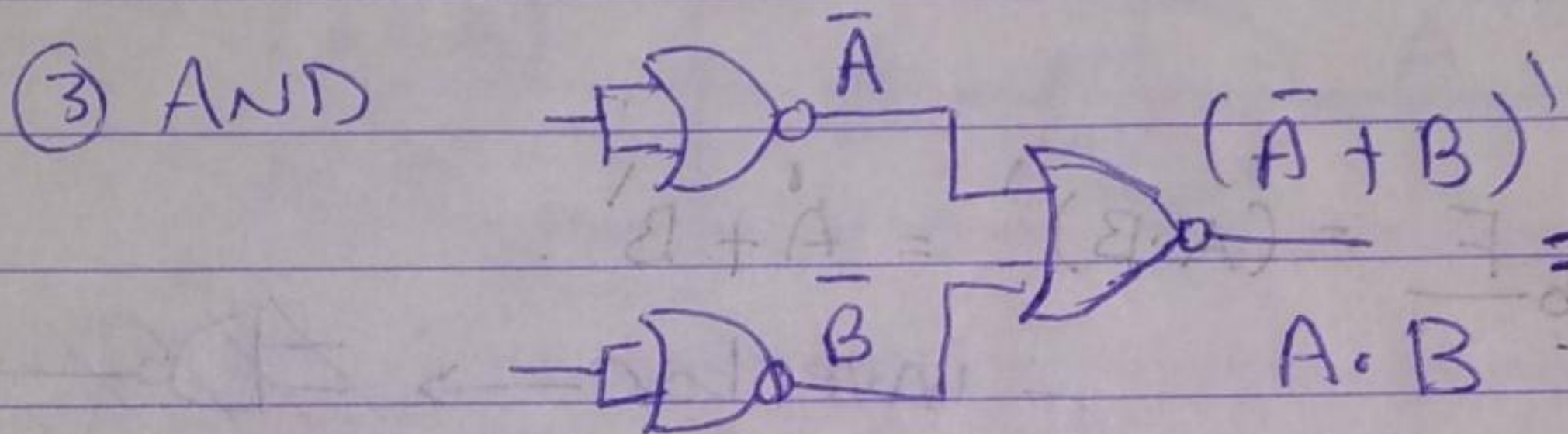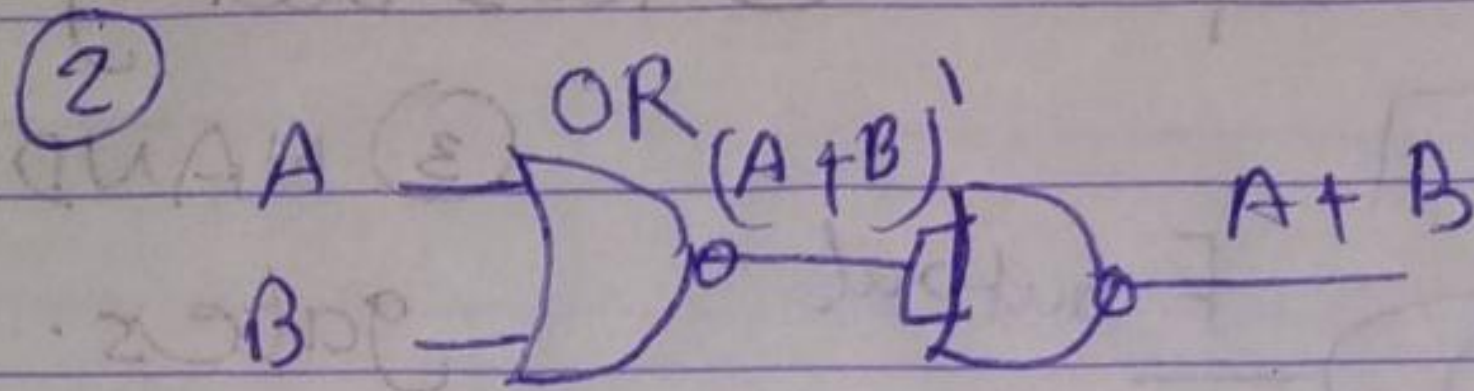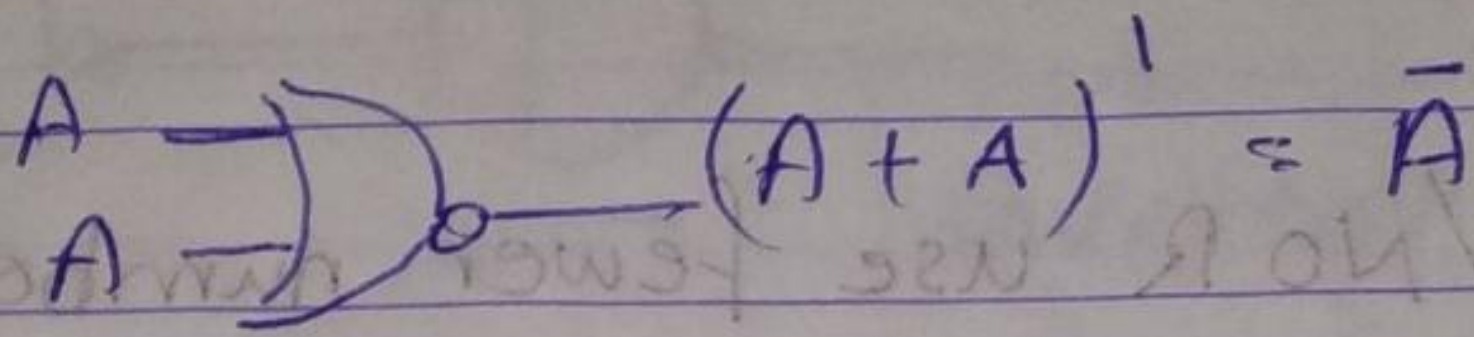

Basic Gates :-

16 Form.


AND OR NAND NOR.

8 Form / degenerate (AND-AND / OR-OR)
 level 1
 level 2

8 Form / non degenerate (AND-OR, NAND-NAND, NOR-OR, OR-NAND)
 minterms ←
] ✓
] x

maxterms ← (OR-AND, NOR-NOR, NAND-AND, AND-NOR)
] ✓
] x

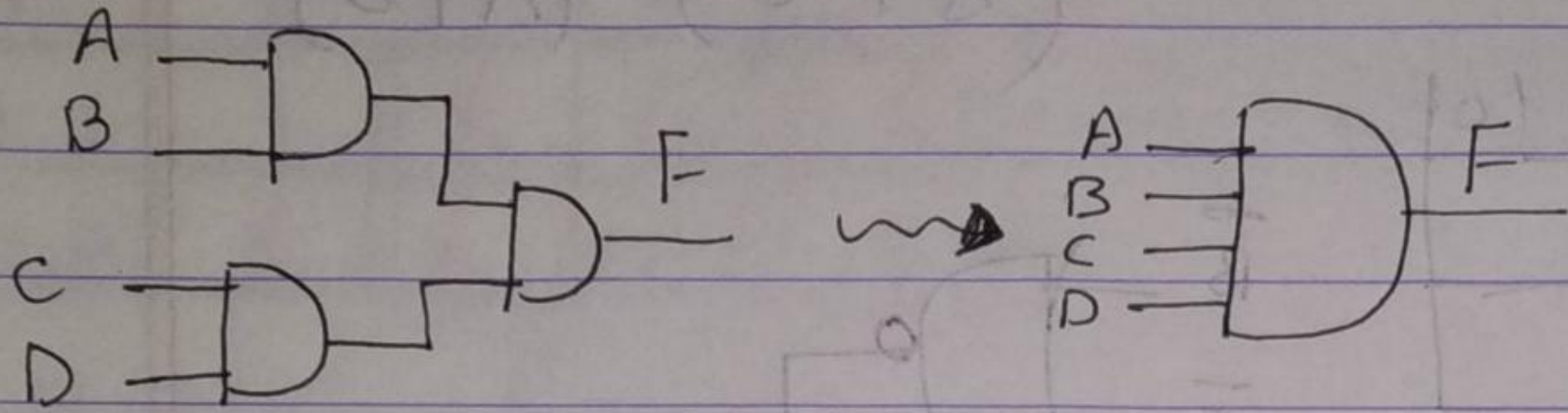انہو بنیاد پر انہو کے ال 2 level و 1 level Degenerate :-



مثال :-


ما بنیاد پر انہو کے ال 1 level Nondegenerate :-

ex $F(A, B, C) = \sum 0, 1, 2, 6$ ← minterm.



	BC	00	01	11	10
A		1	1		1

Annotations: $\bar{A}\bar{B}$ (circled around 00), $B\bar{C}$ (circled around 10)

$$= \bar{A}\bar{B} + B\bar{C}$$


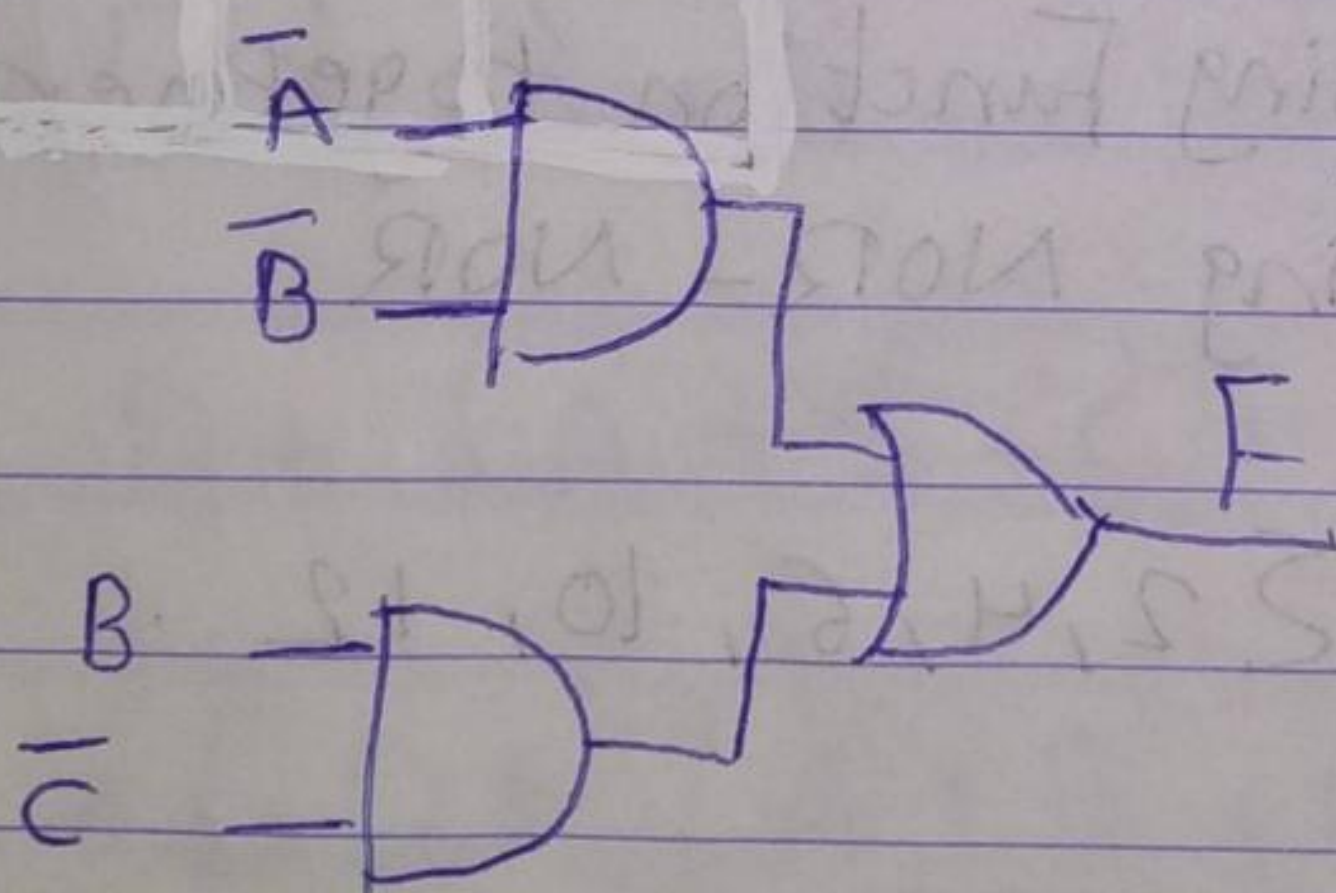


AND-OR = (NAND-NAND)

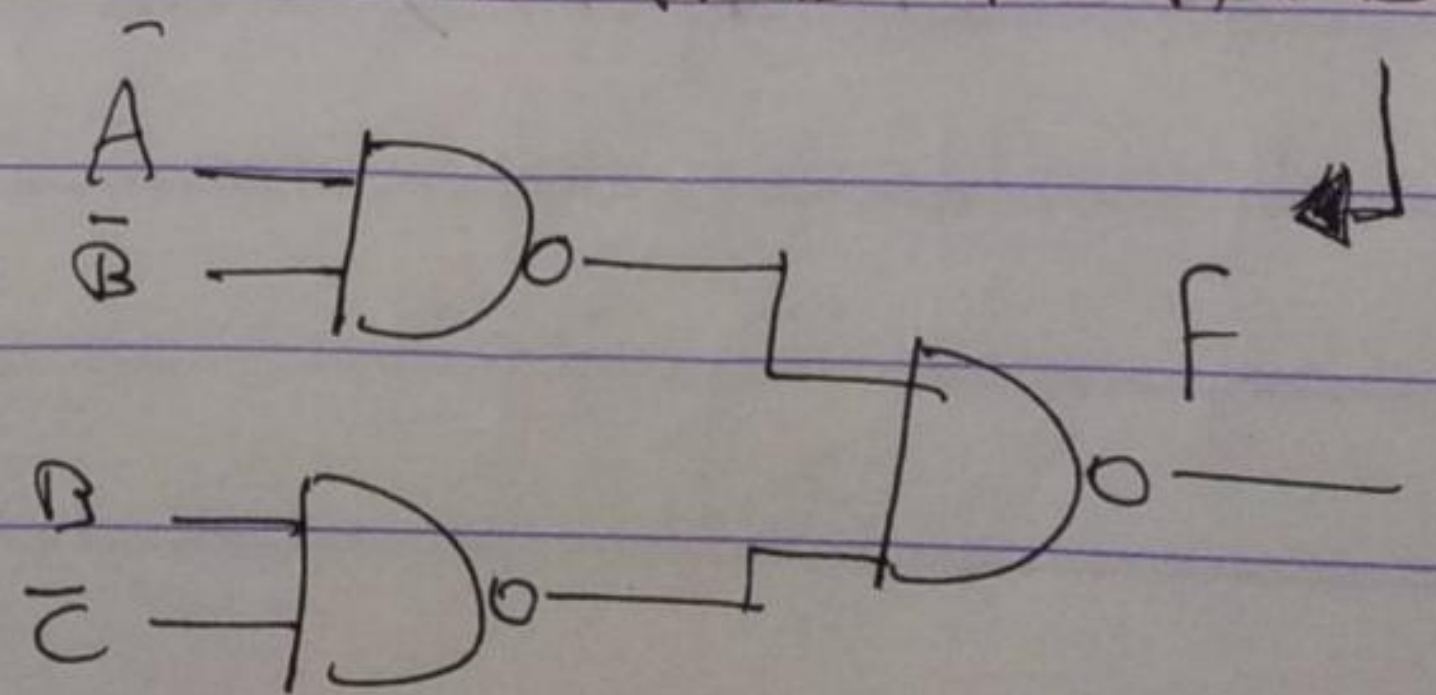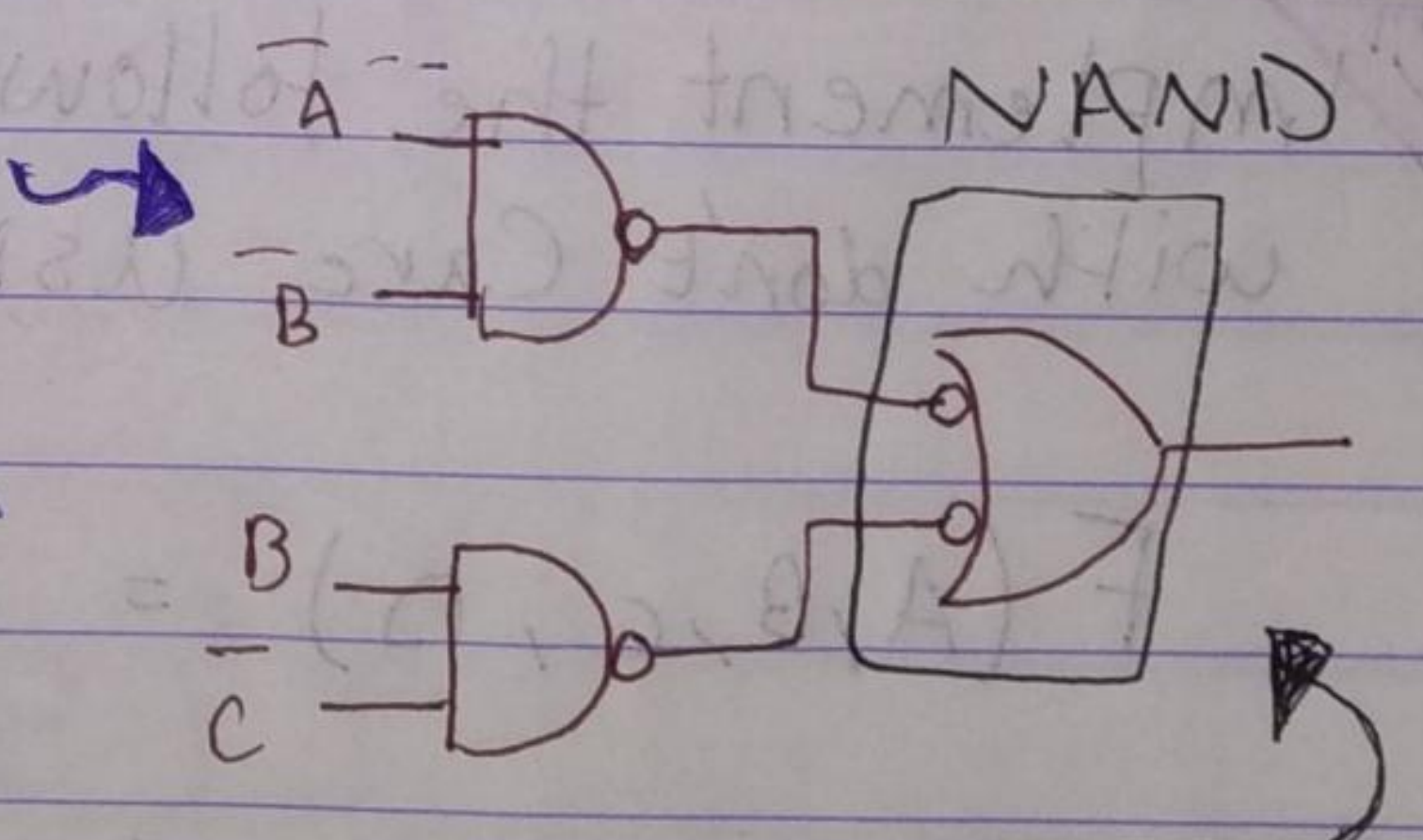

ex $F(A, B, C) = \prod(3, 4, 5, 7)$

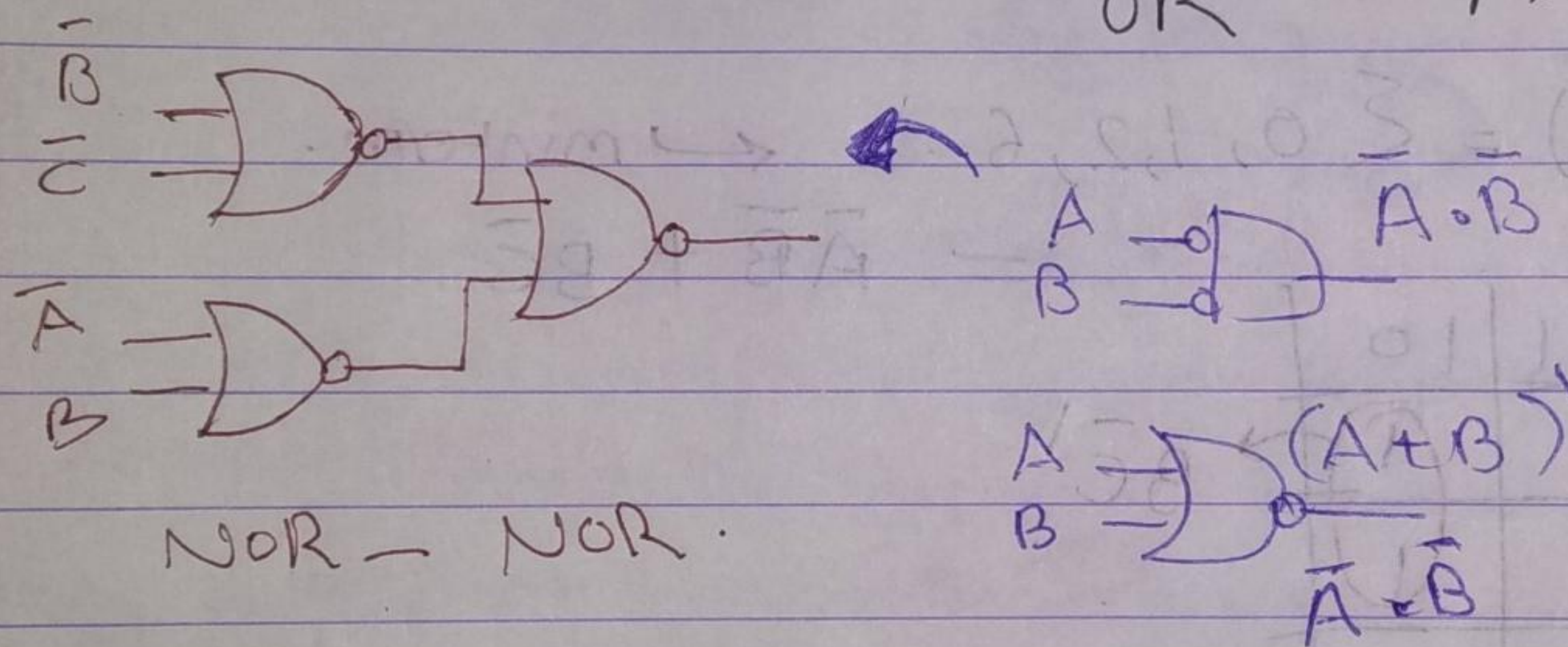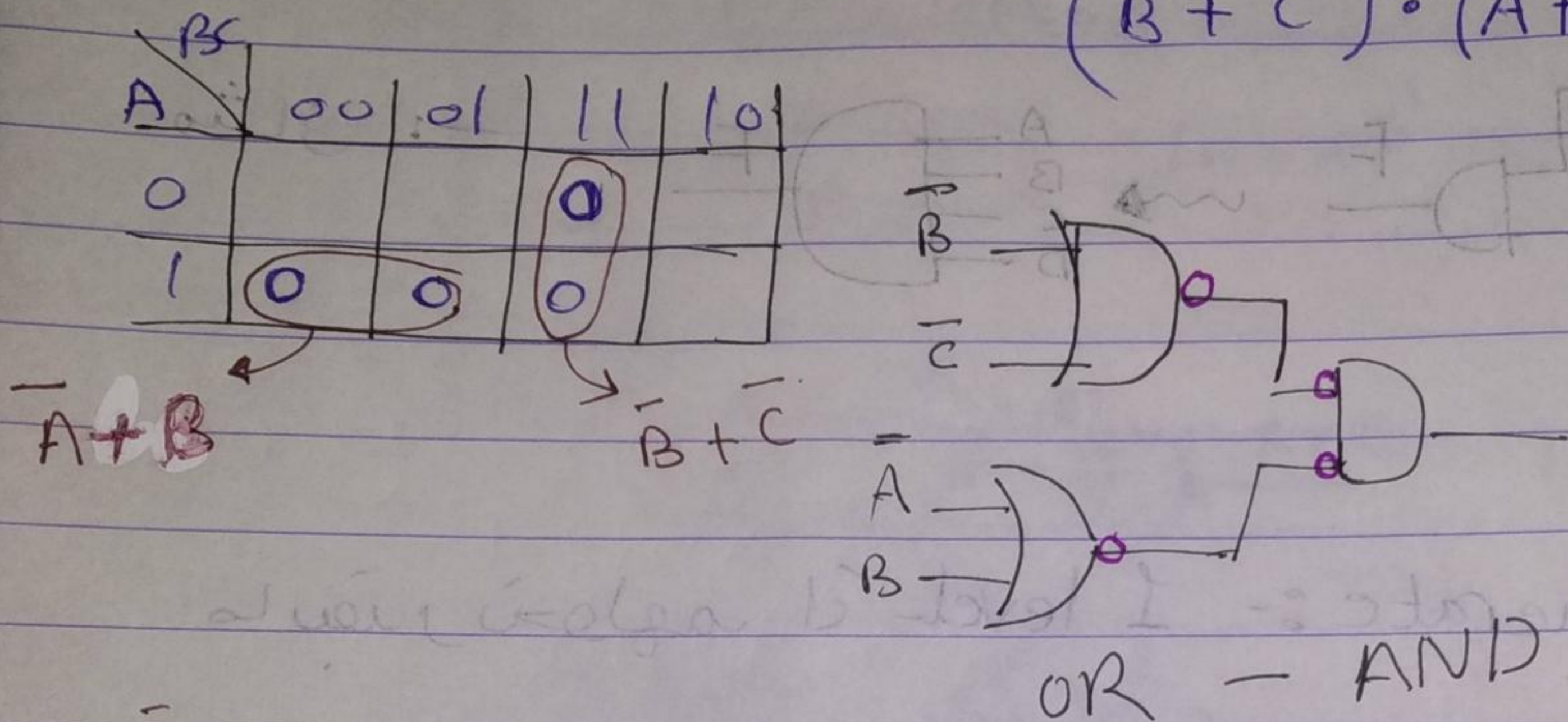
NOR - NOR = $(\bar{B} + \bar{C}) \cdot (\bar{A} + B)$



ex Implement the following Function together with don't Care using NOR - NOR.



$F(A, B, C, D) = \sum 2, 4, 6, 10, 12$

$d(A, B, C, D) = \sum 0, 8, 9, 13$

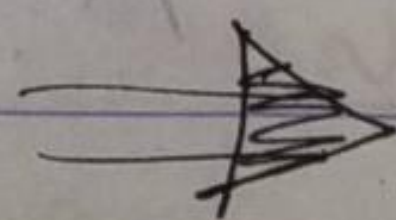

	CD				
AB	00	01	11	10	
00	X	0	0	1	
01	1	0	0	1	
11	1	X	0	0	$(\bar{A} + \bar{B} + \bar{C})$
10	X	X	0	1	
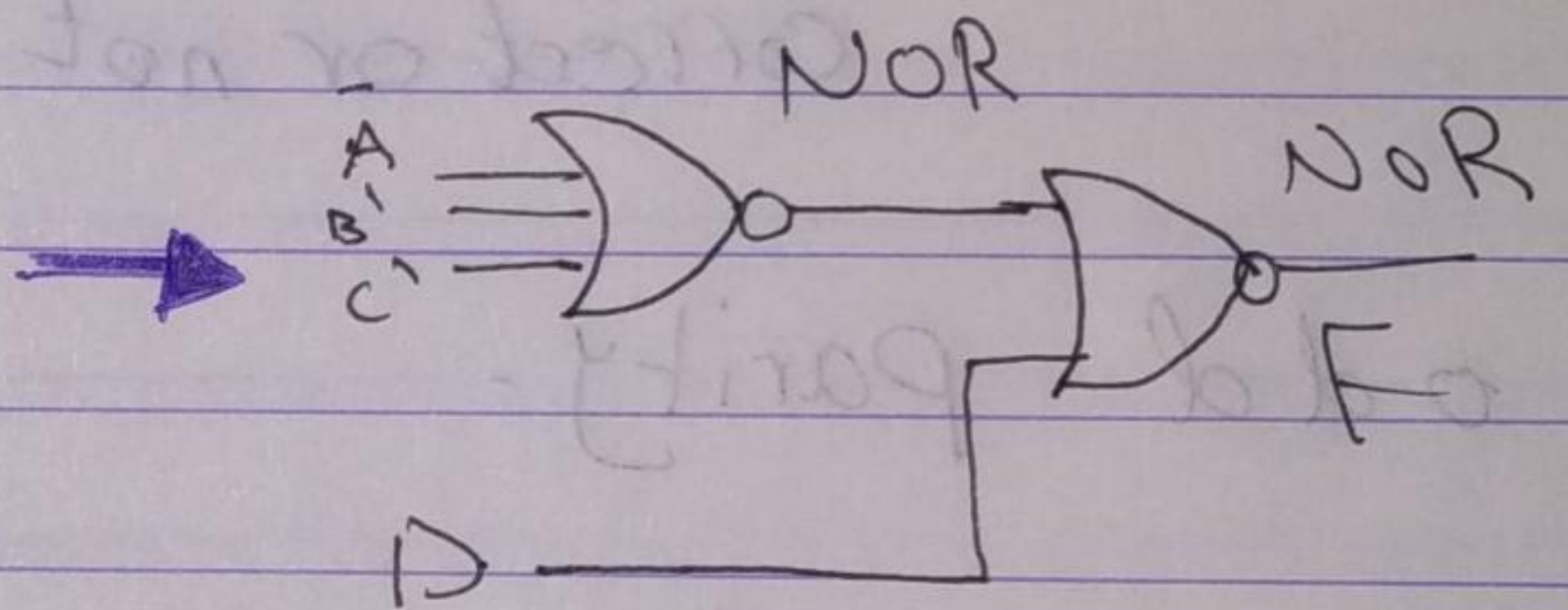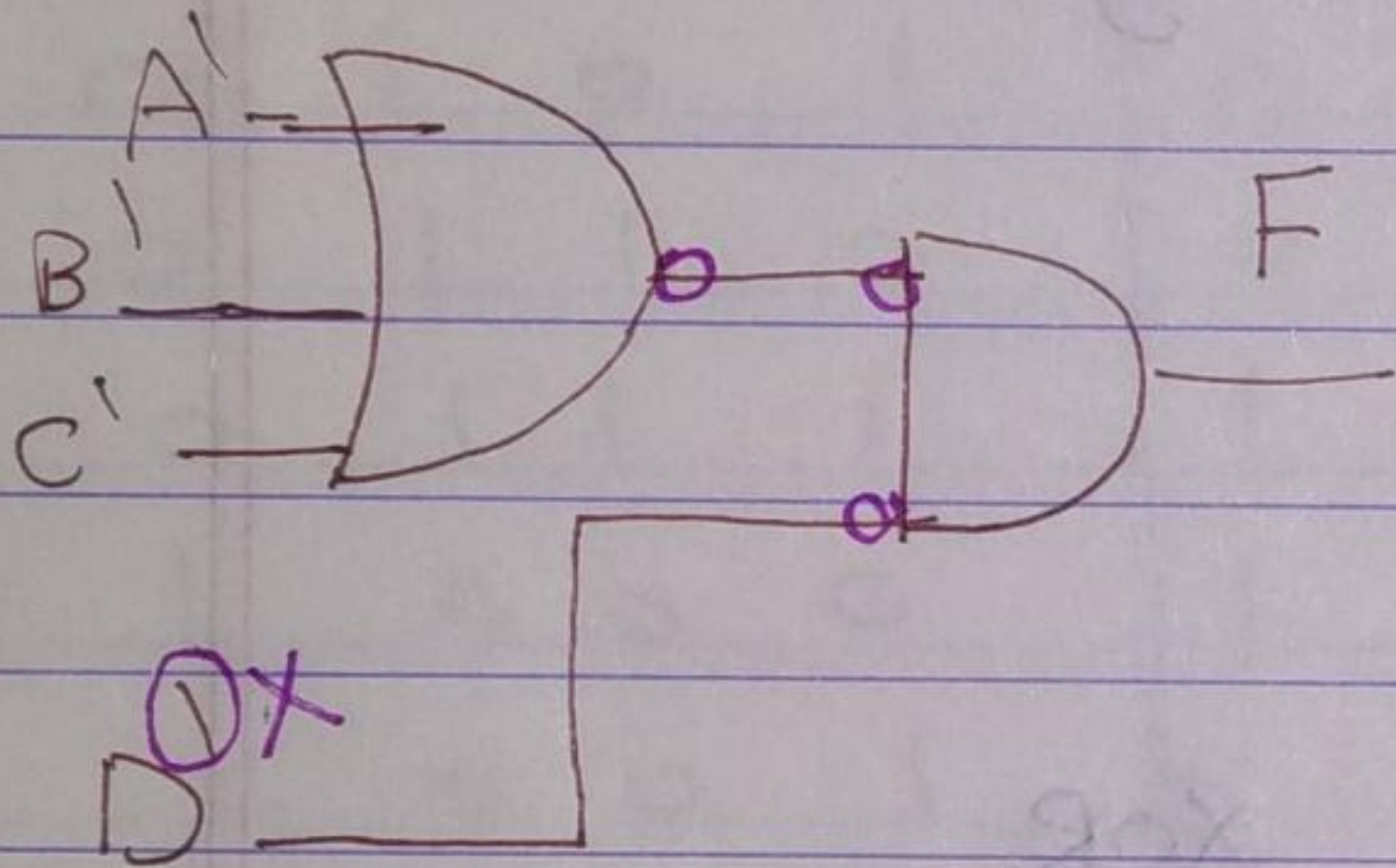
$$F = \bar{D} \cdot (\bar{A} + \bar{B} + \bar{C})$$



$$F = \bar{D} \cdot (\bar{A} + \bar{B} + \bar{C})$$

$$F' = [\bar{D} \cdot (\bar{A} + \bar{B} + \bar{C})]'$$


$$F' = D + (\bar{A} + \bar{B} + \bar{C})'$$

$$F'' = F = [D + (\bar{A} + \bar{B} + \bar{C})']'$$

NOR

Parity Generator :-

Sender

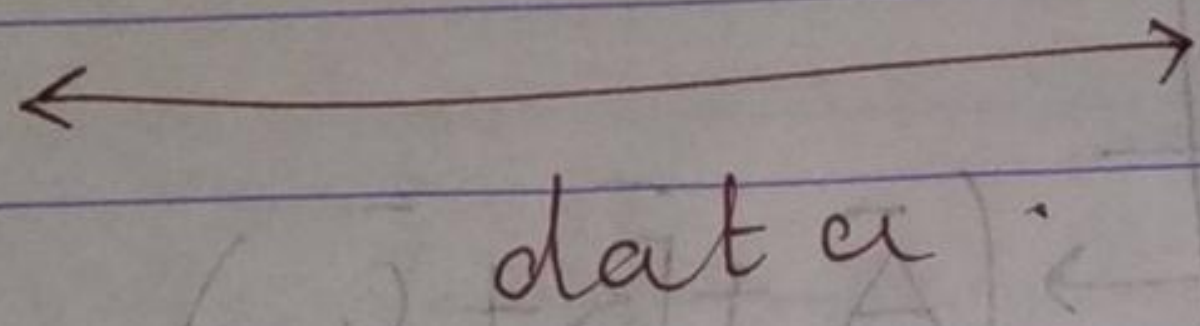

Receiver

Parity :- Extra bit added by sender
To check if the message is correct or not.

① odd parity.

② even parity.

ex Sender

A	B	C	P (even)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


عشان نفهم
عدد الواحدات زوجي

إذا كان odd

XNOR

Receiver

A	B	C	D	Check
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0

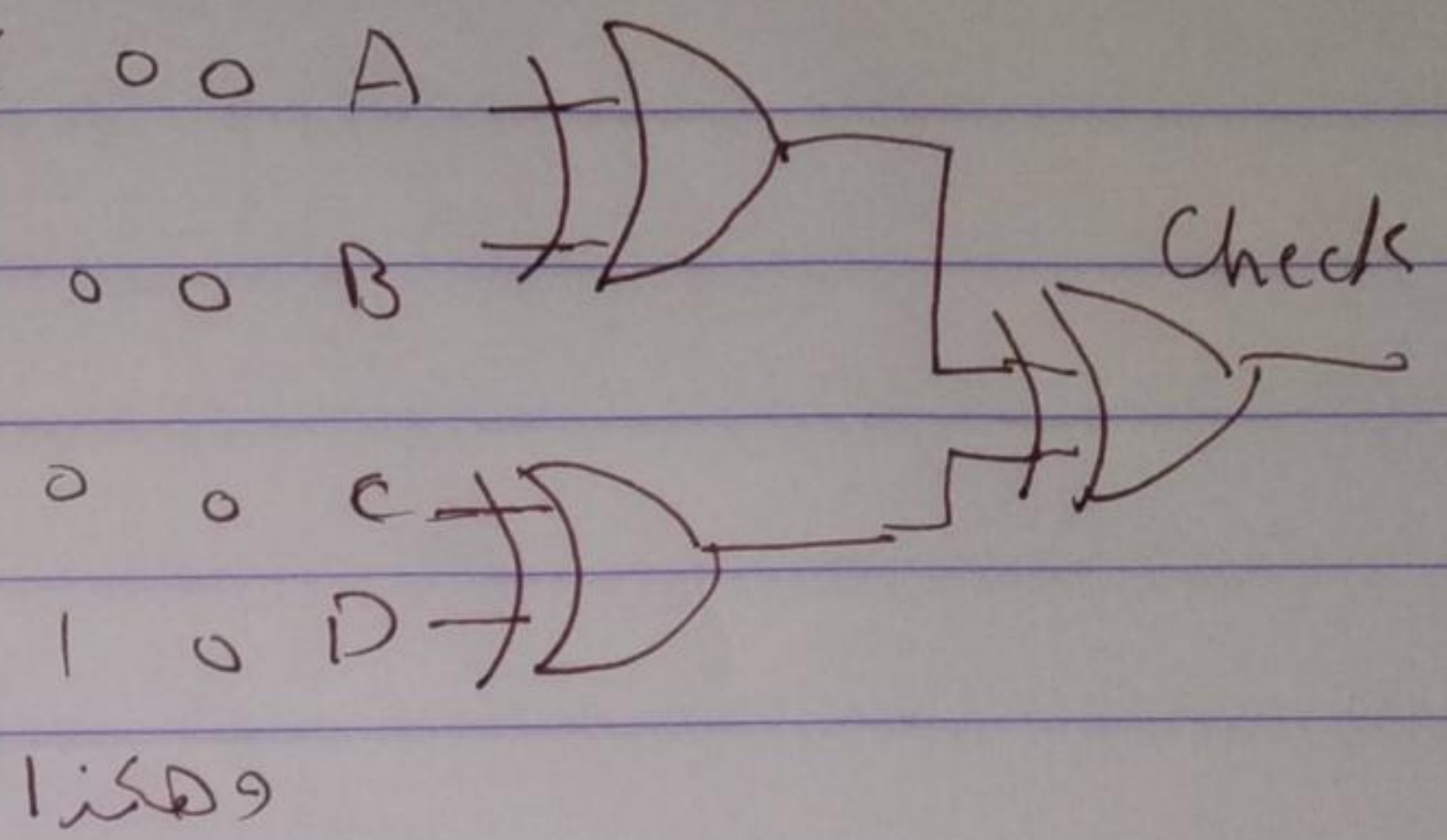

parity (odd).

x	y	z	p
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

x \ yz	00	01	11	10
0	1		1	
1		1		1

$$\begin{aligned}
 P &= x'y'z' + x'yz' + xy'z + xyz' \\
 P &= x'(y'z' + yz) + x(y'z + yz') \\
 &= x'(y \oplus z)' + x(y \oplus z) \\
 &= x'w' + xw \\
 &= (x \oplus w)' = (x \oplus y \oplus z)'
 \end{aligned}$$

