

10

Name: Sajeda Murra ID: 1166724 sec:1

- A. Write a behavioral description for the MUX4x1.
- B. Write a testbench for the MUX4x1.

```

A. Entity mux4-1 IS
  PORT ( a,b,c,d, s1,s2: IN STD-LOGIC;
        out1: OUT STD-LOGIC);
  End entity mux4-1;
  
```

s2	s1
0	0
0	1
1	0
1	1


architecture simple of mux4-1 is

Begin

```

out1 <= a when s1='0' and s2='0'
Else b when s1='1' and s2='0'
Else c when s1='0' and s2='1'
Else d when s1='1' and s2='1';
  
```

End architecture simple;

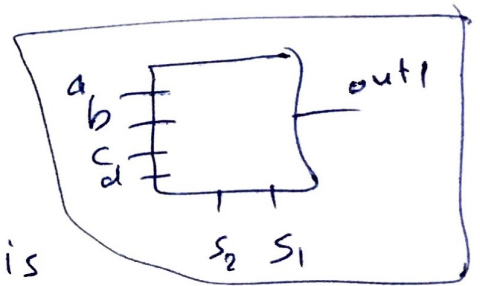

```

B. Entity test_mux is
  End Entity test_mux;
  
```

architecture test of test\_mux is

```

signal a,b,c,d,s1,s2,out1: STD-LOGIC;
  
```

Begin

Entity work\_mux4-1  
(simple) port map  
(a,b,c,d,s1,s2,out1);

```

s1 <= '0';
after 20 ns,
s1 <= '1';
after 40 ns,
s2 <= '0';
after 30 ns,
s2 <= '1';
after 60 ns,
a <= '0';
after 50 ns,
a <= '1';
after 70 ns,
a <= '0';
  
```


b ← '0' ,  
'1' after 10 ns;

c ← '0' ,  
'1' after 30 ns;

d ← '0' ,  
'1' after 60 ns;

End architecture test;

Name: Sajeda Murra sec: 1  
 id: 1160724

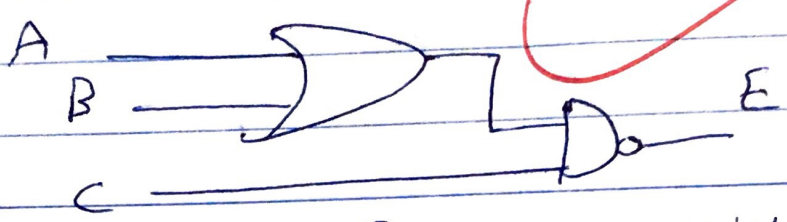

find when E is sensitive to B.

$$E = f(A, B, C) = ((A+B), C)$$

$$= (A+B)' + C'$$

$$= A'B' + C'$$

$$\frac{dE}{dB} = f(B=0) \oplus f(B=1)$$

$$= (A' + C') \oplus C' = 1$$

$A' + C' = 1$  or  $C' = 1$

but not both

A	C	A'	C'	A' + C'	(A' + C') ⊕ C'
0	0	1	1	1	0
0	1	1	0	1	1
1	0	0	1	1	0
1	1	0	0	0	0

E is sensitive to B when ~~AC = 00~~  $\overline{AC} = 01$

~~AC = 00~~  
~~AC = 01~~  
~~AC = 10~~  
~~AC = 11~~



Name: Sajeda Nurra  
 ID: 1160724

	00	01	11	10
a	a, 0, b, -	-	-	d, -
b	a, -	b, !	b, !	c, -
c	b, -	-	b, -	a, 0
d	c, -	a, !	c, -	a, !

	00	01	11	10
a	0	X	X	X
b	<del>X</del>	1	1	X
c	<del>X</del>	X	1	0
d	X	1	<del>1</del>	1

9