



DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333

2nd SEMESTER (2015-2016)

Dr. Khader Mohammad

Lecture #6

Introduction

Layout of an Inverter and basic gates

Digital Integrated Circuits


Course topics and Schedule	
	Subject
1	Introduction to Digital Integrated Circuits Design
2	Semiconductor material: pn-junction, NMOS, PMOS
3	IC Manufacturing and Design Metrics CMOS
4	Transistor Devices and Logic Design The CMOS inverter
5	Combinational logic structures
7	Sequential logic gates; Latches and Flip-Flops
6	Layout of an Inverter and basic gates
8	Parasitic Capacitance Estimation
9	Device modeling parameterization from I-V curves. Short Test
10	Arithmetic building blocks
11	Interconnect: R, L and C - Wire modeling
12	Timing Power dissipation;
13	SPICE Simulation Techniques (Project)
14	Memories and array structures Midterm
15	Clock Distribution
16	Supply and Threshold Voltage Scaling
17	Reliability and IC qualification process
18	Advanced Voltage Scaling Techniques
19	Power Reduction Through Switching Activity Reduction
20	CAD tools and algorithms
21	Final & Project discussion

DIGITAL GATES


Fundamental Parameters

- Functionality
- Reliability, Robustness
- Area
- Performance
 - Speed (delay)
 - Power Consumption
 - Energy


Layout

 


Layout

 

Real silicon

 


 

Process (μ)		0.25	0.18	0.13	0.10	0.07	0.05
V_{DD} (V)		2	1.8	1.5	1.2	0.9	0.7
L_{eff} (nm)		160	100	70	50	35	25
t_{ox} (Å)		50	45	30	25	20	15
Levels		6	6	7	8	9	9
Poly	H (μ)	0.2	0.15	0.13	0.1	0.07	0.07
	W (μ)	0.25	0.18	0.13	0.1	0.07	0.05
	space (μ)	0.25	0.18	0.13	0.1	0.07	0.05
	sheet ρ (Ω/\square)	4	5.3	6.2	8	11.4	11.4
M1-2	H (μ)	0.5	0.46	0.34	0.26	0.2	0.14
	W (μ)	0.30	0.23	0.17	0.13	0.1	0.07
	space (μ)	0.30	0.23	0.17	0.13	0.1	0.07
	sheet ρ (Ω/\square)	0.044	0.048	0.065	0.085	0.11	0.16
	t_{ins} (nm)	650	500	360	320	270	210
M3-4	H (μ)	0.9	0.8	0.7	0.55	0.4	0.28
	W (μ)	0.6	0.5	0.4	0.3	0.2	0.14
	space (μ)	0.6	0.5	0.4	0.3	0.2	0.14
	sheet ρ (Ω/\square)	0.024	0.028	0.031	0.04	0.055	0.079
	t_{ins} (nm)	900	800	700	600	500	400
M5-6	H (μ)	2.5	2.5	1.5	1.2	1.0	0.8
	W (μ)	2.0	2.0	1.0	1.0	0.6	0.5
	space (μ)	2.0	2.0	1.0	1.0	0.6	0.5
	sheet ρ (Ω/\square)	0.009	0.009	0.015	0.018	0.022	0.028
	t_{ins} (nm)	1400	1400	900	800	700	600
M7-8	H (μ)	-	-	2.5	2.5	1.5	1.4
	W (μ)	-	-	2.0	2.0	1.0	0.9
	space (μ)	-	-	2.0	2.0	1.0	0.9
	sheet ρ (Ω/\square)	-	-	0.009	0.009	0.015	0.016
	t_{ins} (nm)	-	-	1400	1400	900	800
M9	H (μ)	-	-	-	-	2.5	2.5
	W (μ)	-	-	-	-	2.0	2.0
	space (μ)	-	-	-	-	2.0	2.0
	sheet ρ (Ω/\square)	-	-	-	-	0.009	0.009
	t_{ins} (nm)	-	-	-	-	1400	1400
Via (M1-M2)	size (μ)	0.55	0.26	0.2	0.16	0.12	0.09
	R (Ω)	0.95	1.32	1.61	2.23	3.35	4.63
κ		3.3	2.7	2.3	2	1.8	1.5

Design Rules



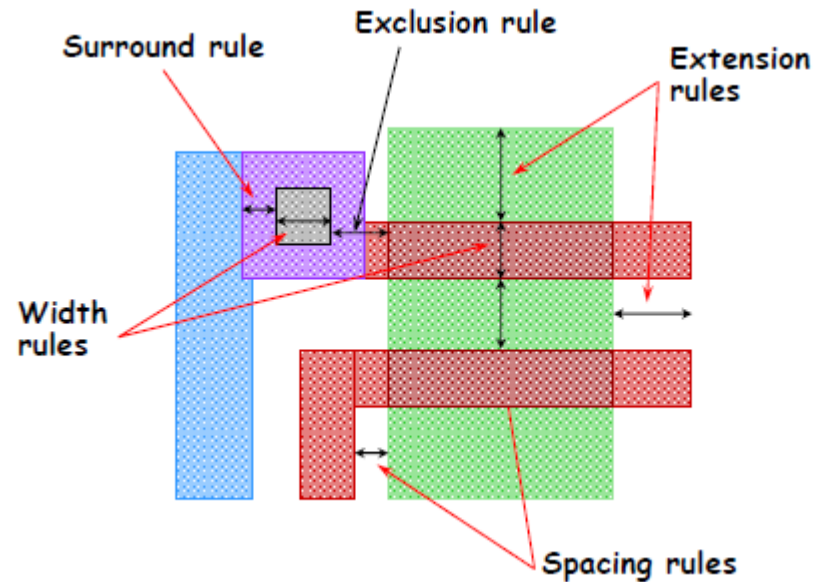






- Design rules are an abstraction of the fabrication process that specify **various geometric constraints on how different masks can be drawn.**
- Design rules can be **absolute measurements (e.g. in nm) or scaled to an abstract unit, the lambda.** Lambda-based designs are scaled to the appropriate absolute units depending on the manufacturing process finally used.





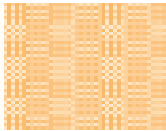
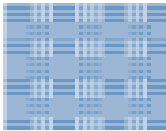

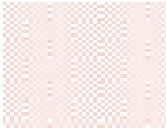

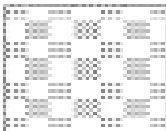







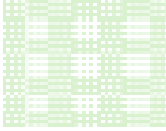
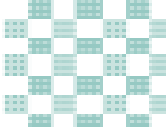

Design Rules

- Interface between designer and process engineer
- Guidelines for constructing process masks
- Unit dimension: Minimum line width
 - scalable design rules: lambda parameter
 - absolute dimensions (micron rules)


CMOS Process Layers

Layer	Color	Representation
Well (p,n)	Yellow	
Active Area (n+,p+)	Green	
Select (p+,n+)	Green	
Polysilicon	Red	
Metal1	Blue	
Metal2	Magenta	
Contact To Poly	Black	
Contact To Diffusion	Black	
Via	Black	


Layers in 0.25 μm CMOS process

Layer Description	Representation				
metal	 m1	 m2	 m3	 m4	 m5
well	 nw				
polysilicon	 poly				
contacts & vias	 ct	 v12, v23, v34, v45	 nwc	 pwc	
active area and FETs	 ndif	 pdif	 nfet	 pfet	
select	 nplus	 pplus	 prb		


Intra-Layer Design Rules

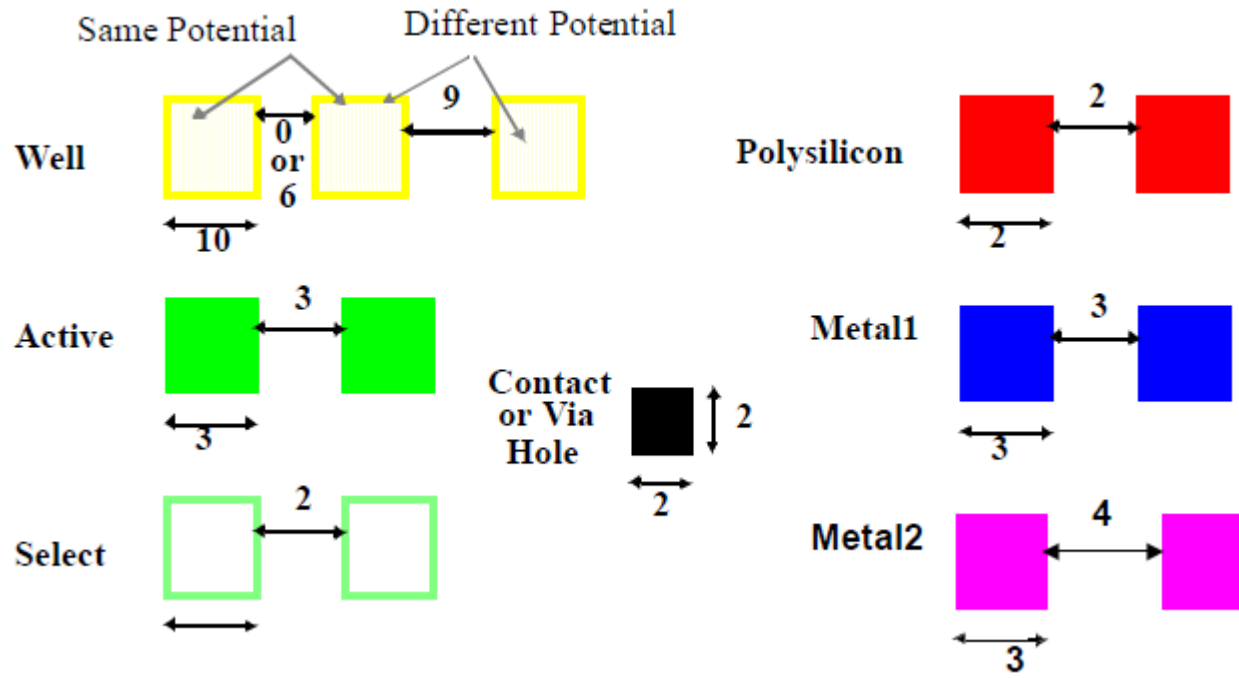


Transistor Layout

 


Vias and Contacts

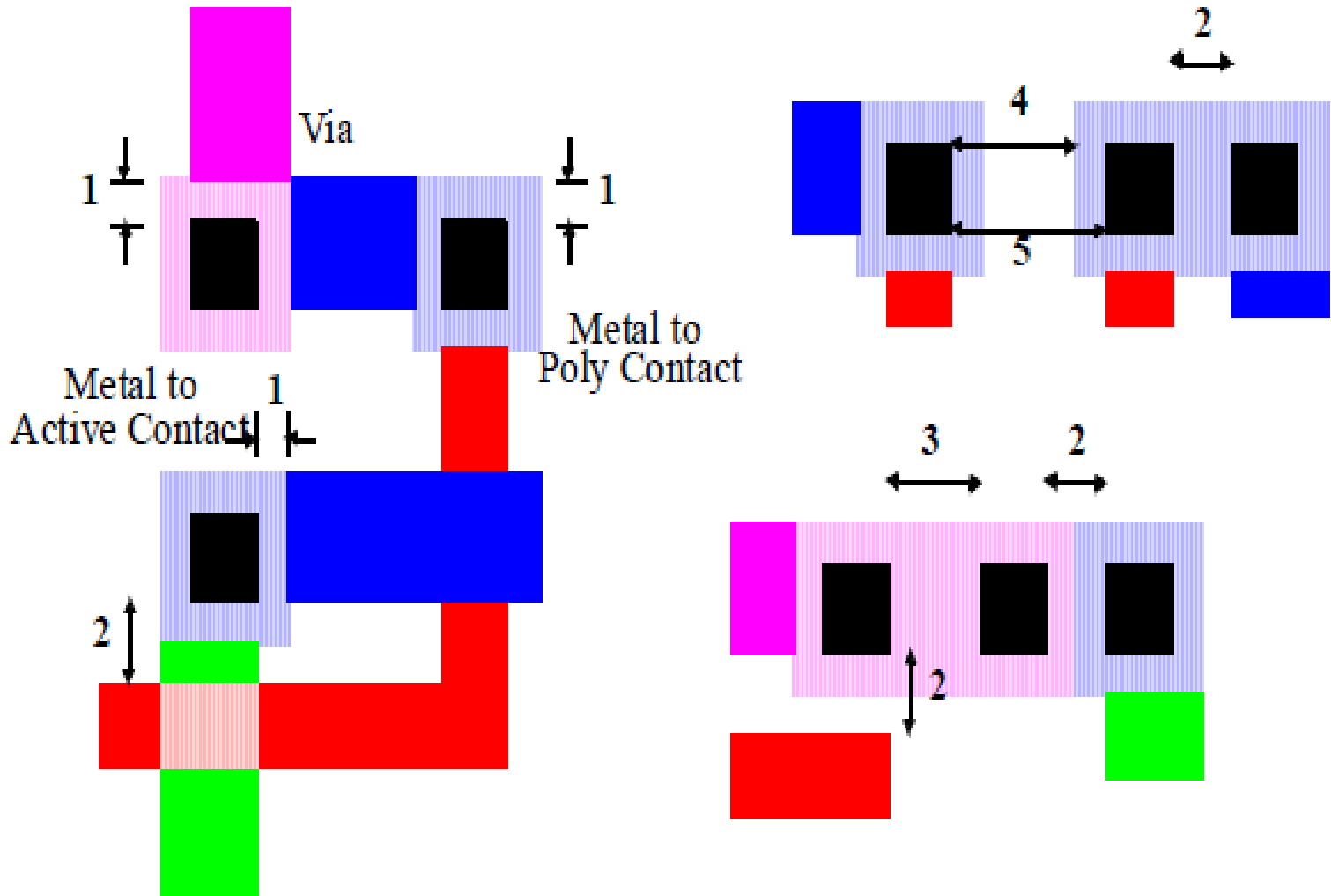


Select Layer

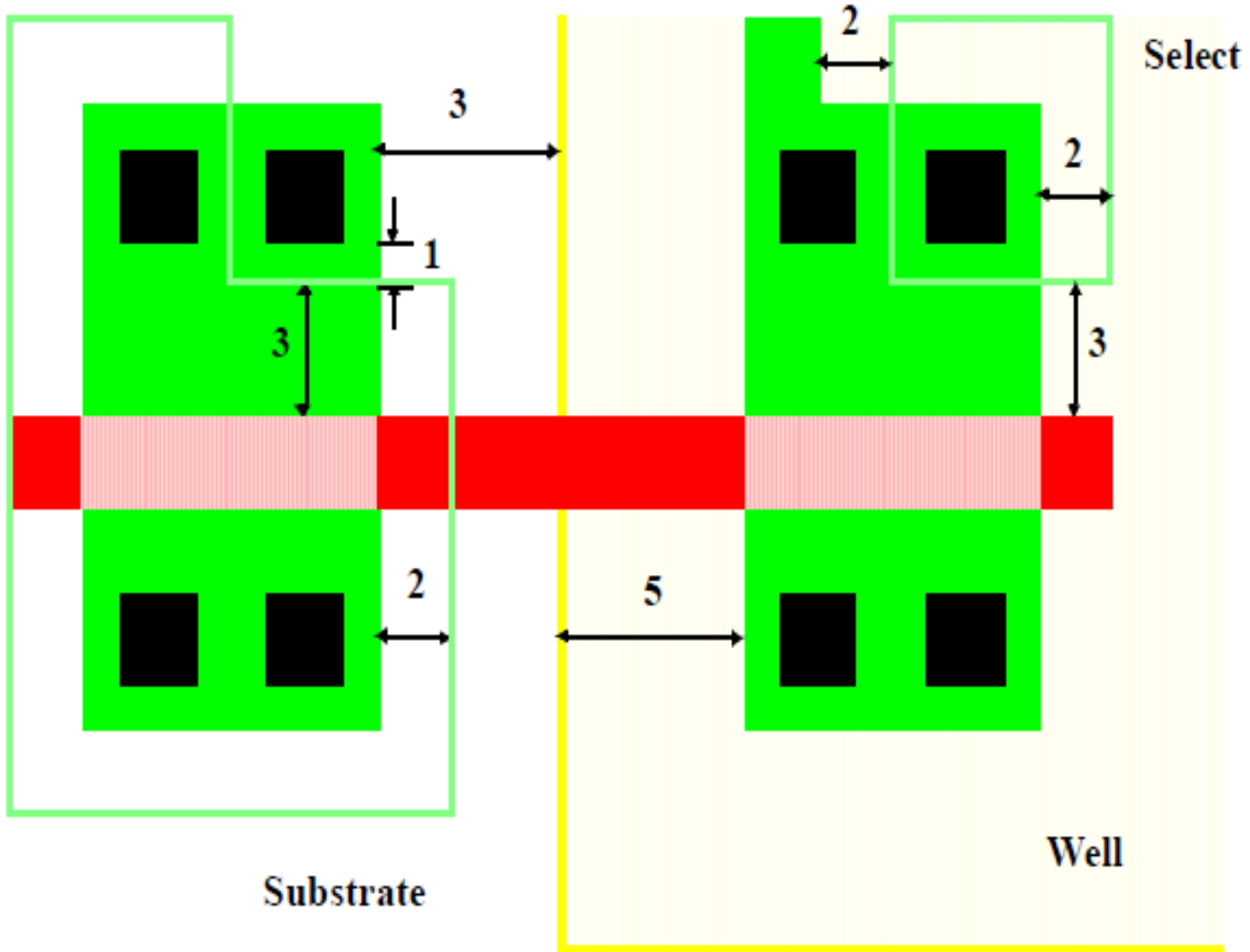

CMOS Inverter Layout

 


(a) Layout

 

 
(b) Cross-Section along A-A'

Lambda-based Design Rules

- One lambda (λ)= one half of the “minimum” mask dimension.
- Typically the length of a transistor channel is 2λ .
- Usually all edges must be “on grid”, e.g., in the MOSIS scalable rules, all edges must be on a lambda grid.



Layout Editor

 


Design Rules


- Intra-layer
 - Widths, spacing, area
- Inter-layer
 - Enclosures, distances, extensions, overlaps
- Special rules (sub-0.25 μm)
 - Antenna rules, density rules, (area)

Transistor Layout

Cross-Sectional View

 

Layout View

 


Why Have Design Rules?




- To be able to tolerate some level of fabrication errors such as

1. Mask misalignment

 


2. Dust

 3. Process parameters
(e.g., lateral diffusion)




4. Rough surfaces

max Layer Representation

 


- Metals (five) and vias/contacts between the interconnect levels
 - Note that **m5** connects only to **m4**, **m4** only to **m3**, etc., and **m1** only to poly, ndif, and pdif
 - Some technologies support “stacked vias”
- Active – active areas on/in substrate (poly gates, transistor channels (**nfet**, **pfet**), source and drain diffusions (**ndif**, **pdif**), and well contacts (nwc, pwc))
- Wells (nw) and other select areas (pplus, nplus, prb)

CMOS Inverter *max* Layout

 

Intra-Layer Design Rule Origins

 
- Minimum dimensions (e.g., widths) of objects on each layer to maintain that object after fab
 - minimum line width is set by the resolution of the patterning process (photolithography)
- Minimum spaces between objects (that are *not* related) on the same layer to ensure they will not short after fab




Inter-Layer Design Rule Origins


1. Transistor rules – transistor formed by overlap of active and poly layers

Transistors

 


Unrelated Poly & Diffusion

 


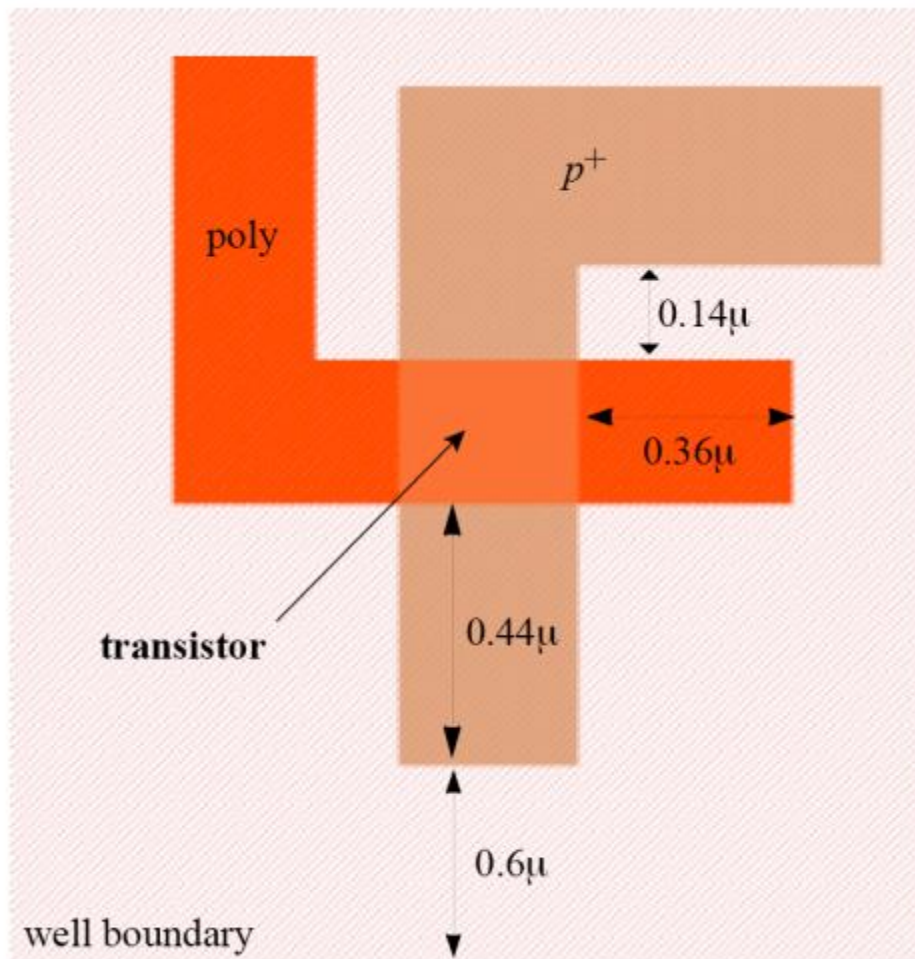


Inter-Layer: Well and Substrate

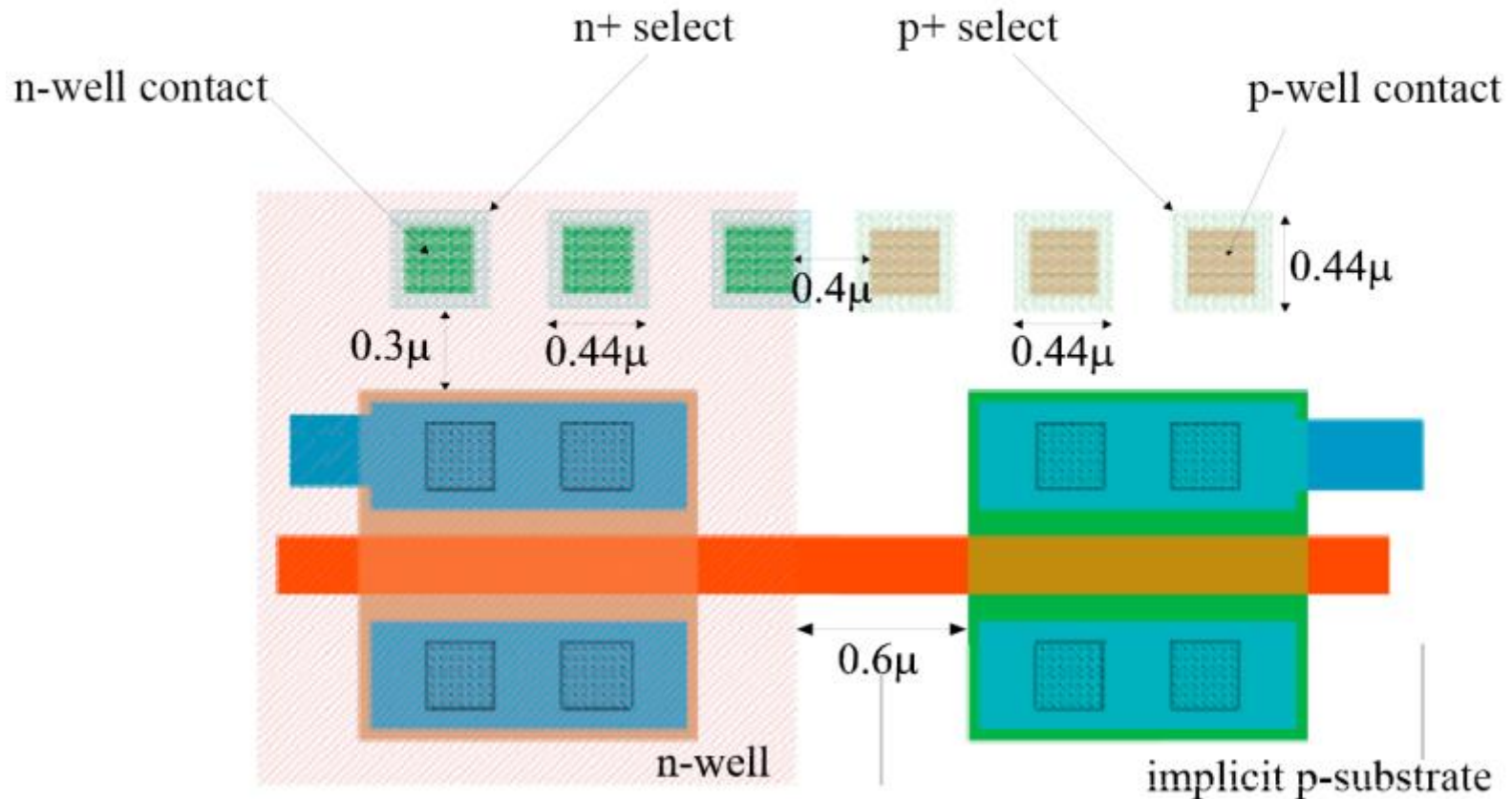



Design Rule Checker

 

Circuit Under Design

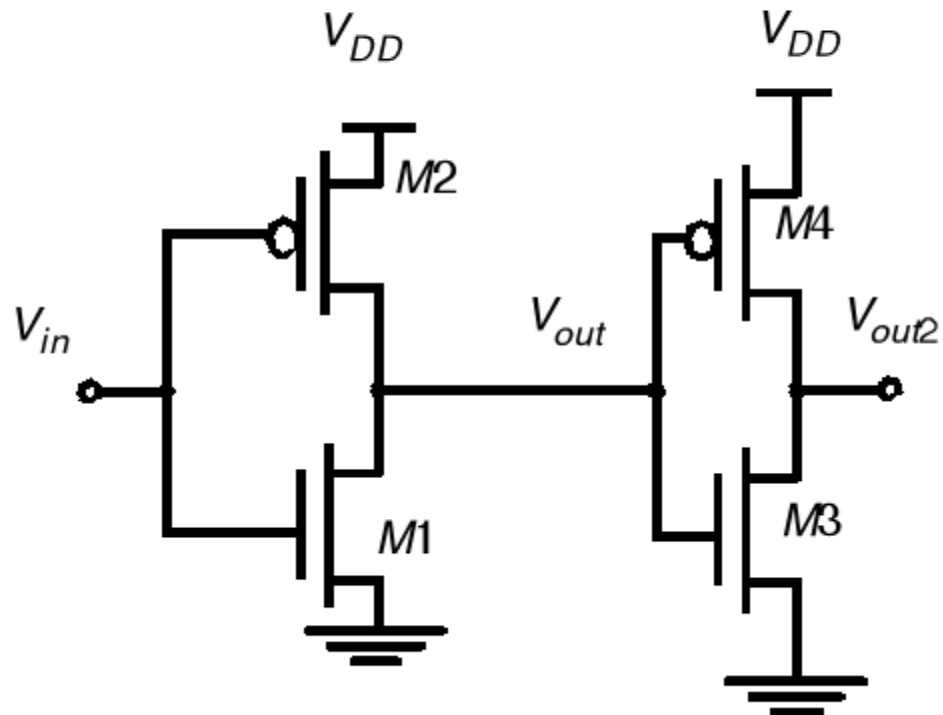



CMOS Inverter

  

Two Inverters

Share power and ground


Abut cells

  


Gate Layout

- Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
- Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules
 - nMOS at bottom and pMOS at top
 - All gates include well and substrate contacts

Example: Inverter

 

 Layout Design Rules *Conservative rules to get started!*



Design Rules Summary

- Metal and diffusion have minimum width and spacing of 4λ
- Contacts are $2\lambda \times 2\lambda$ and must be surrounded by 1λ on the layers above and below
- Polysilicon uses a width of 2λ
- Polysilicon overlaps diffusions by 2λ where a transistor is desired and has spacing of 1λ away where no transistor is desired
- Polysilicon and contacts have a spacing of 3λ from other polysilicon or contacts
- N-well surrounds pMOS transistors by 6λ and avoid nMOS transistors by 6λ

The power and ground lines are called supply rails

Inverter Layout

- Transistor dimensions specified as W / L ratio
- Minimum size is $4\lambda / 2\lambda$, sometimes called 1 unit



 
 
 



FIG 1.40 Inverter with dimensions labeled

Inverter Standard Cell Area (1/2)

 


 

2-input NAND gate

 


3-input Standard Cell NAND

 


Wiring Tracks

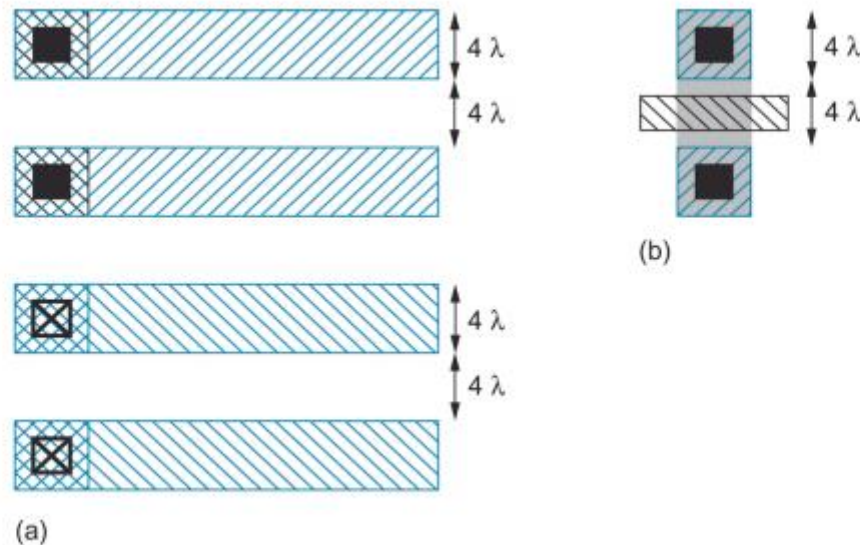- A **wiring track** is the space required for a wire
 - 4λ width, 4λ spacing from neighbor = 8λ pitch
 - Transistors also consume one wiring track



Well Spacing

 - Wells must surround transistors by 6λ
 - Implies 12λ between opposite transistor flavors
 - Leaves room for one wire track




Area Estimation

Horizontal
 $4 \times 8 = 32$


Vertical
 $5 \times 8 = 40$

 - Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ






Stick Diagrams

 - **Stick diagrams** help plan layout quickly
 - Need not be to scale
 - Draw with color pencils or dry-erase markers




CMOS Inverter Stick Diagrams

   - **CMOS** inverter described in other way.





Sticks Diagram

 


Stick diagram of inverter

- Dimensionless layout entities
- Only topology is important
- Final layout generated by “compaction” program

CMOS Inverter

  


Two Inverters

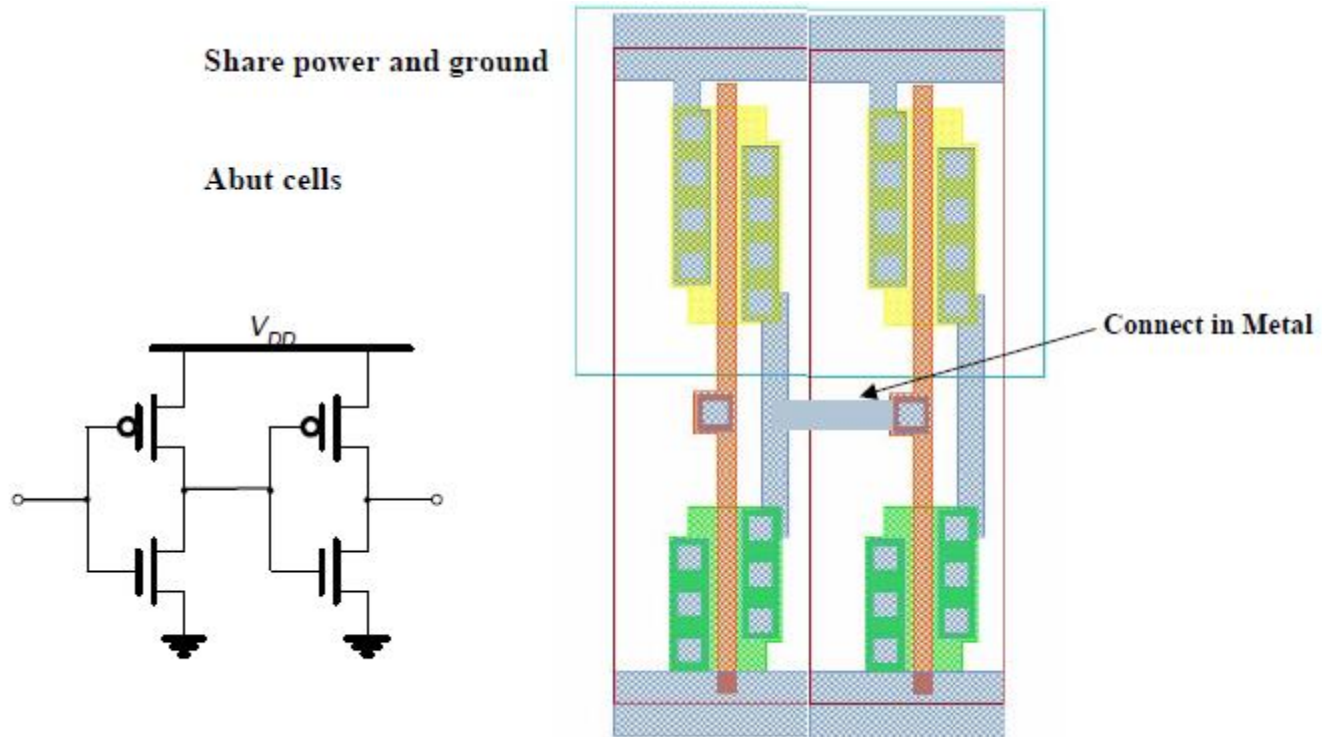

Stick Diagram

$$F = (AB)+E+(CD)$$

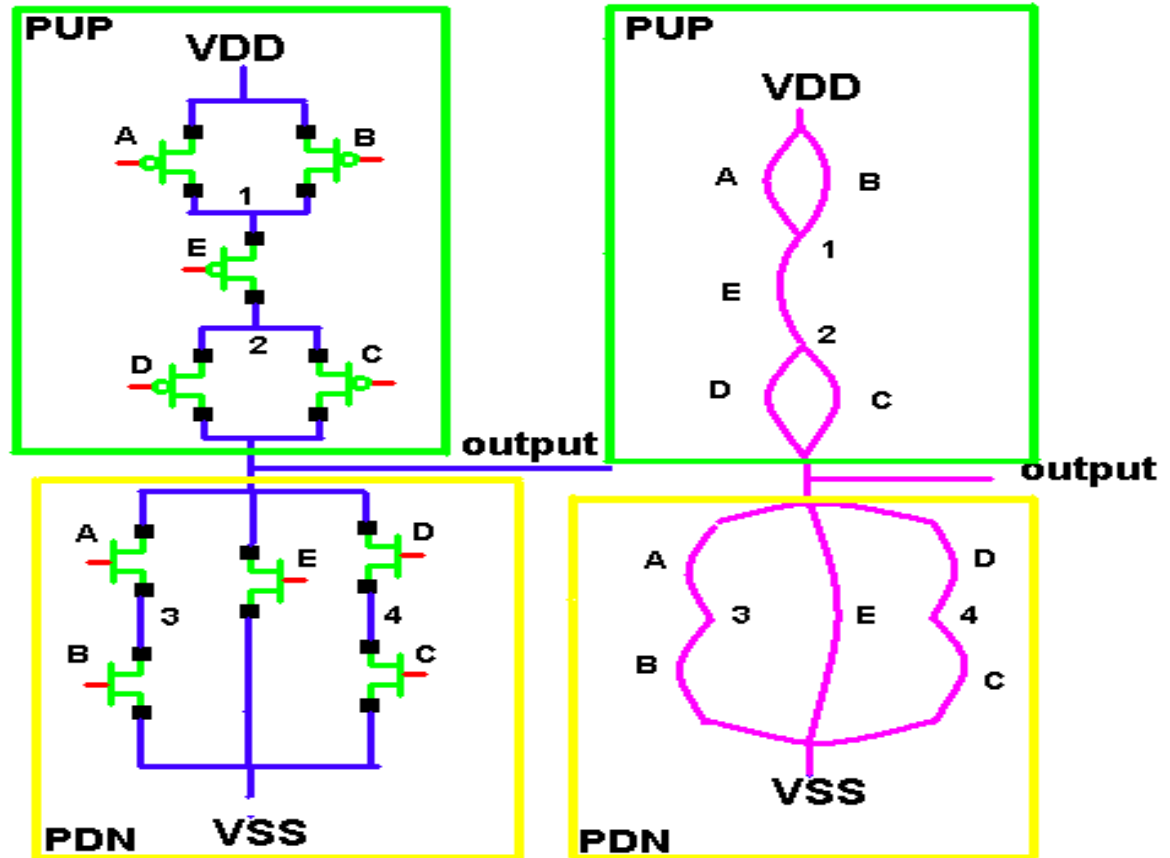


Identify each transistor and connection to the transistor by a unique name

construct a logic graph

$$F = (AB)+E+(CD)$$

See the tutorial for further details.

 


EULER PATH = {A,B,E,D,C}


- construct one Euler path for both the Pull up and Pull down network

EULER PATH = {A,B,E,D,C}

— METAL 1
— POLY
— ACTIVE

 


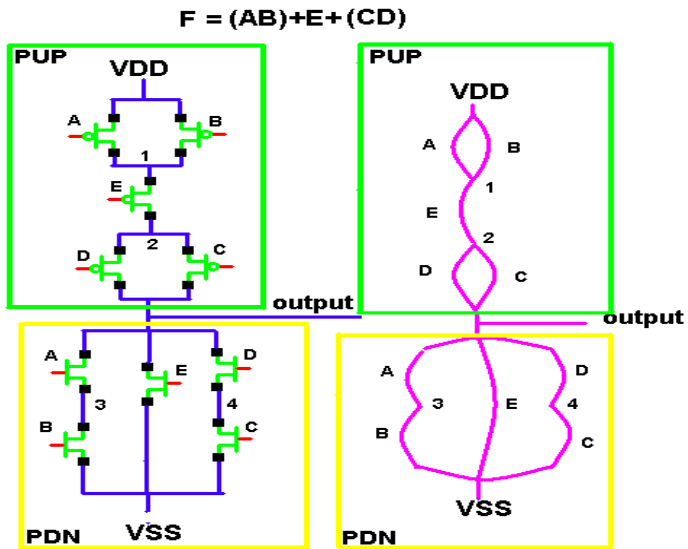- Trace two green lines horizontally to represent the NMOS and PMOS devices and surround them by n and p-wells
- Trace the number of inputs (5 in this example) vertically across each green strip and label them in order.
- Trace blue lines to represent VDD and VSS
- Place the connection labels upon the NMOS and PMOS devices




EULER PATH = {A,B,E,D,C}

ME
PO
AC

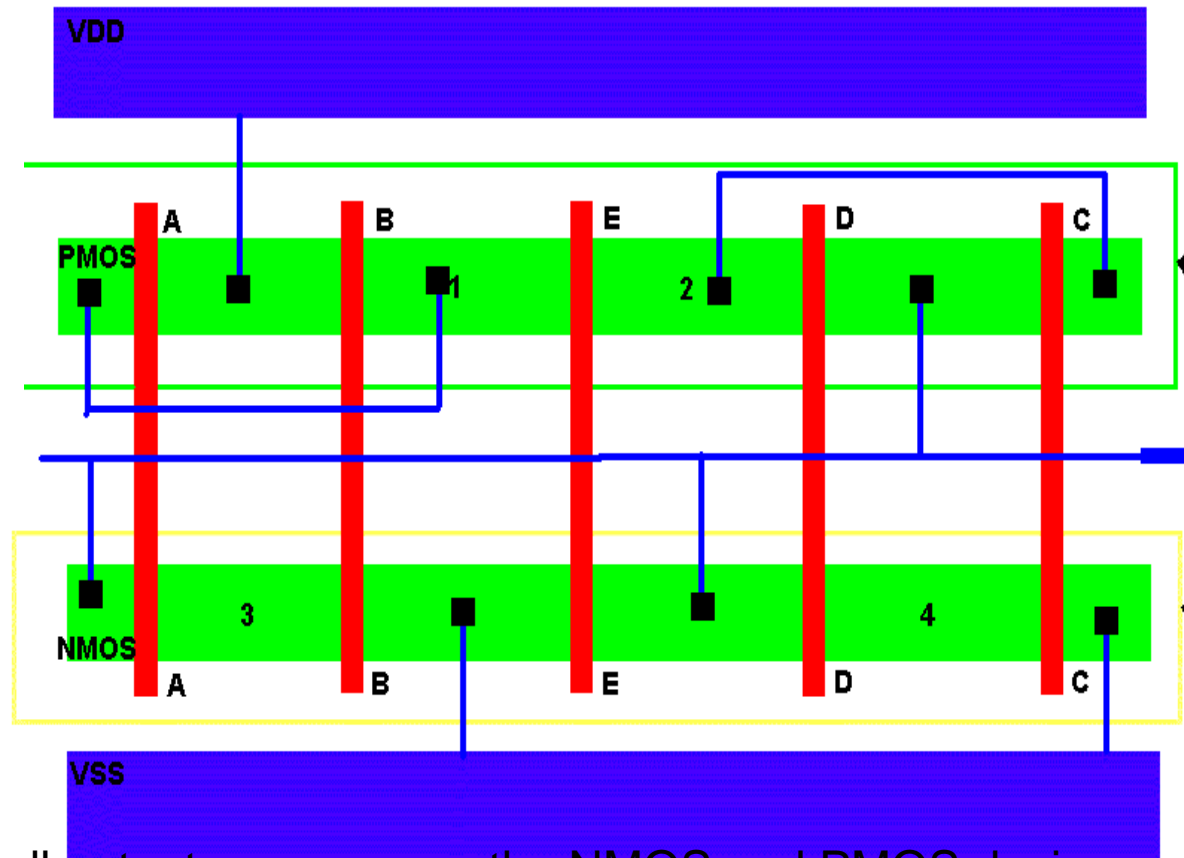


- Place the VDD, VSS and all output names upon the NMOS and PMOS devices
- interconnect the devices based on Euler path.

One finger

 


Two fingers (folded)

 



Less diffusion capacitance

Future device


 


25 nm MOS transistor (Folded Channel)

Layout vs. Schematic

  

Gate Layout Tricks

  

Gate Layout Tricks

