



Faculty of Engineering and Technology  
Department of Electrical and Computer Engineering

ENEE 2103

CIRCUITS AND ELECTRONICS LABORATORY

Experiment #10, Pre-Lab #6

“Multistage Amplifiers and Frequency Response”

---

Prepared by:

Nour Naji-1190270

Section: 1

Supervised by:

Dr. Alhareth Zyoud

Teaching assistant:

Eng. Esmail Abualia


Date: 1/11/202

---


# Table of Contents

- 1.Adding Application:..... 1
  - 1.1Calculated voltage .....3
- 2.Voltage Follower application:.....5
- 3.Comparator Application: .....7
- 4.Integrator and Differentiator: ..... 10
  - 4.1. Integrator: ..... 10
  - 4.2 Differentiator:..... 11
- 5. To investigate the effect of adding hysteresis..... 12


### 1. Adding Application:

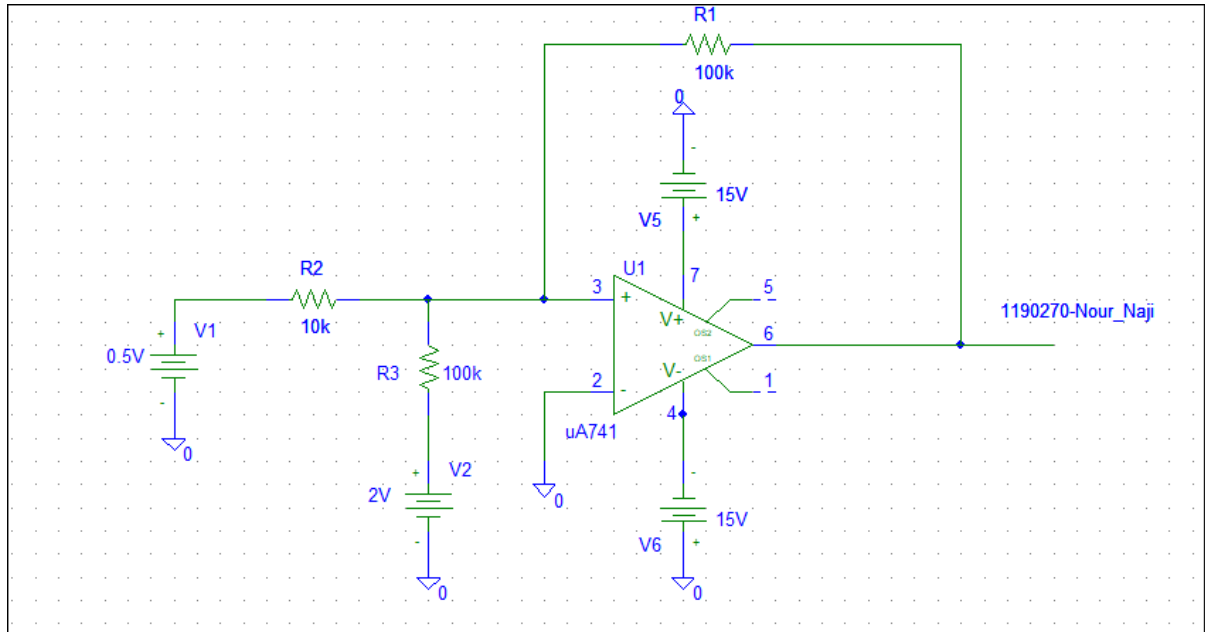

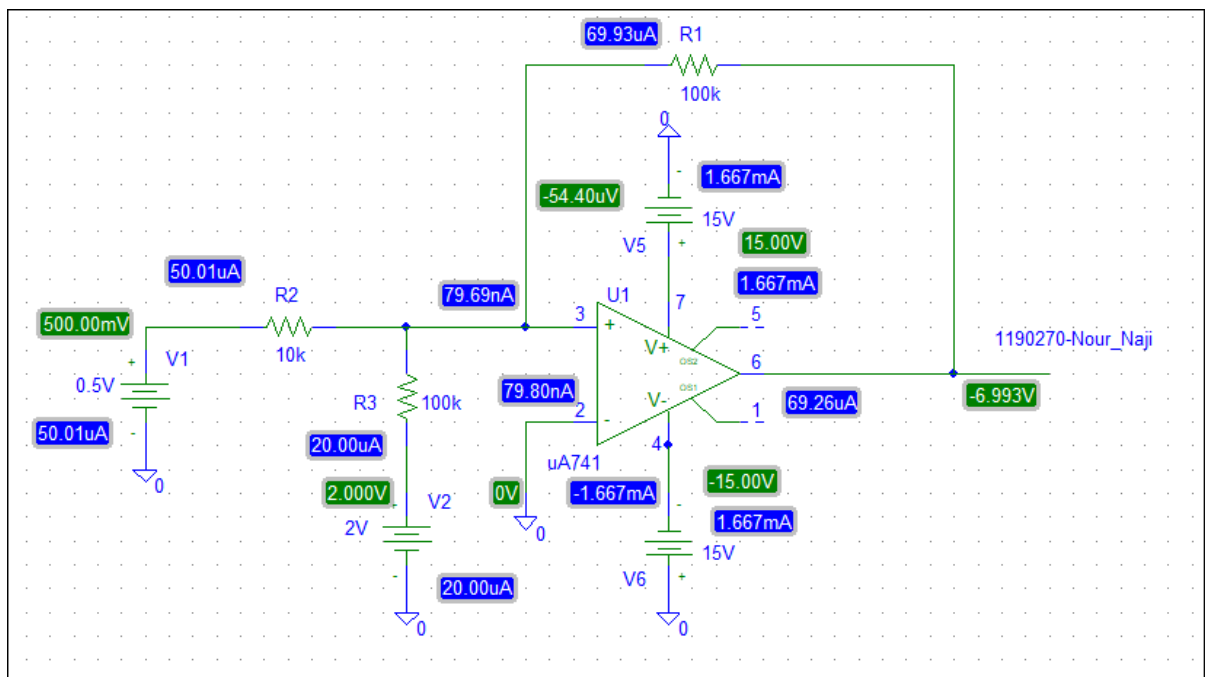
- If  $V_1 = 0.5v$  and  $V_2 = 2v$ , then  $V_0 =$ :



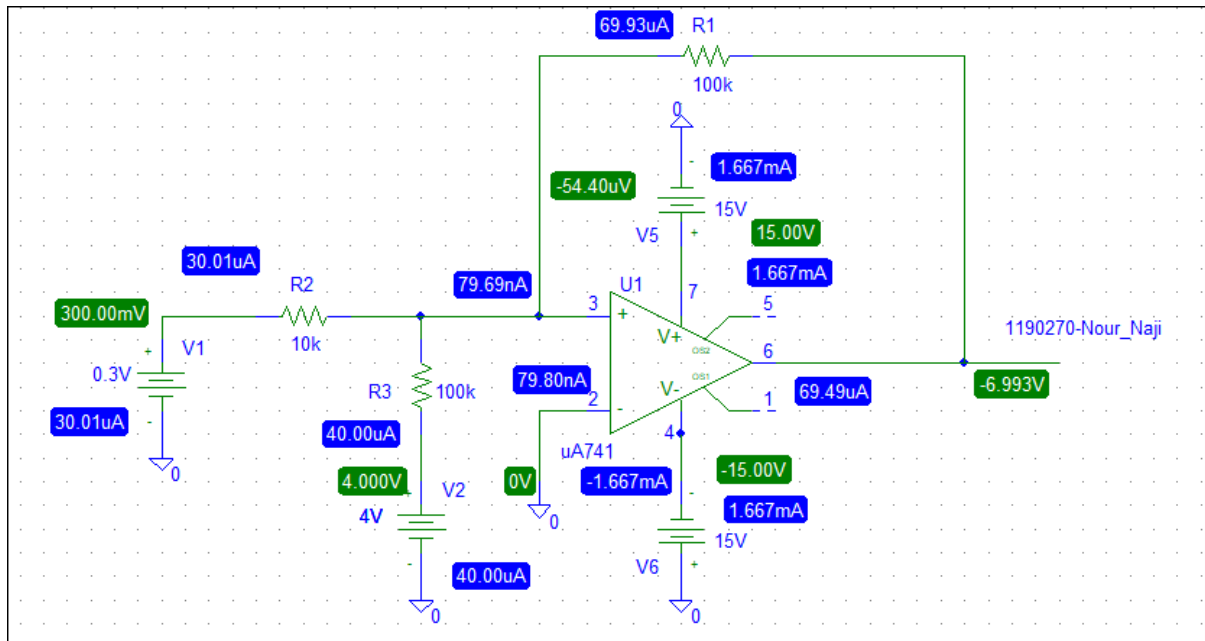- If  $V_1 = 0.3v$  and  $V_2 = 4v$ , then  $V_0 =$ :



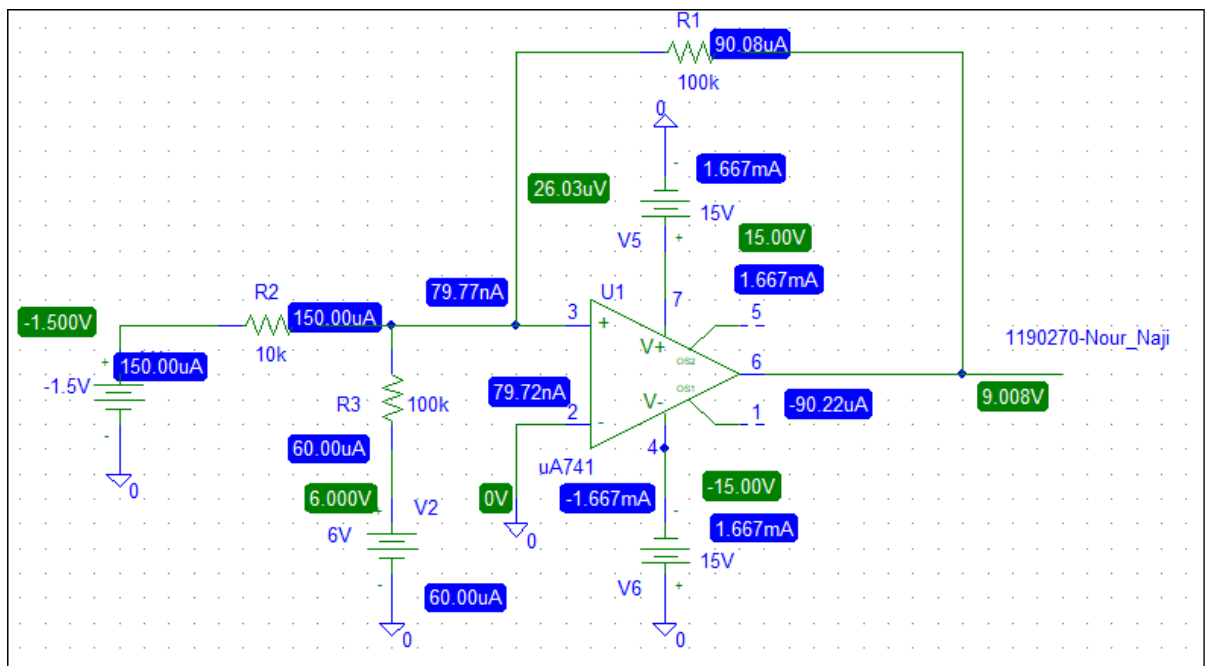- If  $V_1 = -1.5v$  and  $V_2 = 6v$ , then  $V_0 =$ :



### 1.1 Calculated voltage

**Calculated voltage  $\Rightarrow$**

$$V_o = - \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \cdot R\text{-feedback.}$$

**If  $V_1 = 0.5V$  and  $V_2 = 2V \Rightarrow$**

$$V_o = - \left( \frac{0.5}{10k} + \frac{2}{100k} \right) \cdot 100k$$

$$\boxed{V_o = -7V}$$

**If  $V_1 = 0.3V$  and  $V_2 = 4V \Rightarrow$**

$$V_o = - \left( \frac{0.3}{10k} + \frac{4}{100k} \right) \cdot 100k$$

$$\boxed{V_o = -7V}$$

**If  $V_1 = -1.5V$  and  $V_2 = 6V \Rightarrow$**

$$V_o = - \left( \frac{-1.5}{10k} + \frac{6}{100k} \right) \cdot 100k$$

$$\boxed{V_o = 9V}$$

- By comparing the values obtained from the simulation with the calculated ones we notice that they are approximately equal

Input voltage		Output voltage	
$V_1$	$V_2$	$V_o$	Calculated voltage
0.5	2	-6.993	-7
0.3	4	-6.993	-7
-1.5	6	9.008	9

- Write The expression relating  $V_o$  to  $V_1$  and  $V_2$ : i.e.  $V_o = XV_1 + YV_2$   
(Find X, Y)

$$V_o = - \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \cdot R_{fb}$$

$$V_o = - \left[ \frac{R_{fb}}{R_1} \cdot V_1 + \frac{R_{fb}}{R_2} \cdot V_2 \right]$$

$$V_o = - \frac{R_{fb}}{R_1} \cdot V_1 - \frac{R_{fb}}{R_2} \cdot V_2$$


$$\boxed{V_o = X V_1 + Y V_2}$$

$$\Rightarrow X = - \frac{R_{fb}}{R_1} = - \frac{100K}{10K} = -10K$$


$$Y = - \frac{R_{fb}}{R_2} = - \frac{100K}{100K} = -1K$$

$$\hookrightarrow \boxed{V_o = -10V_1 - V_2}$$


## 2. Voltage Follower application:

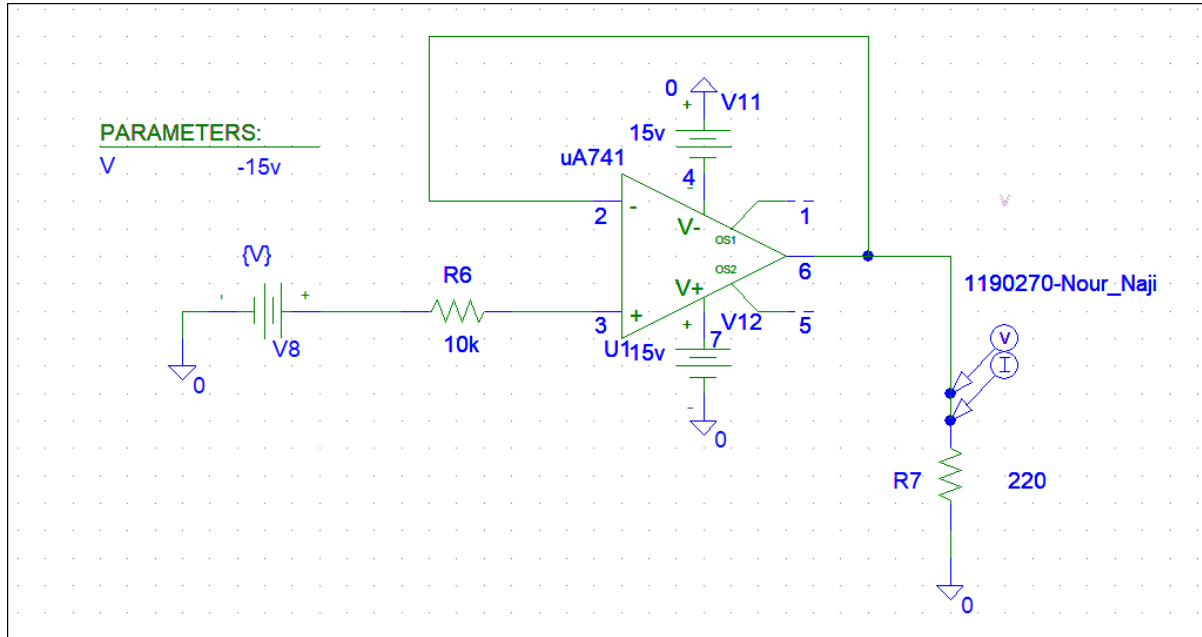

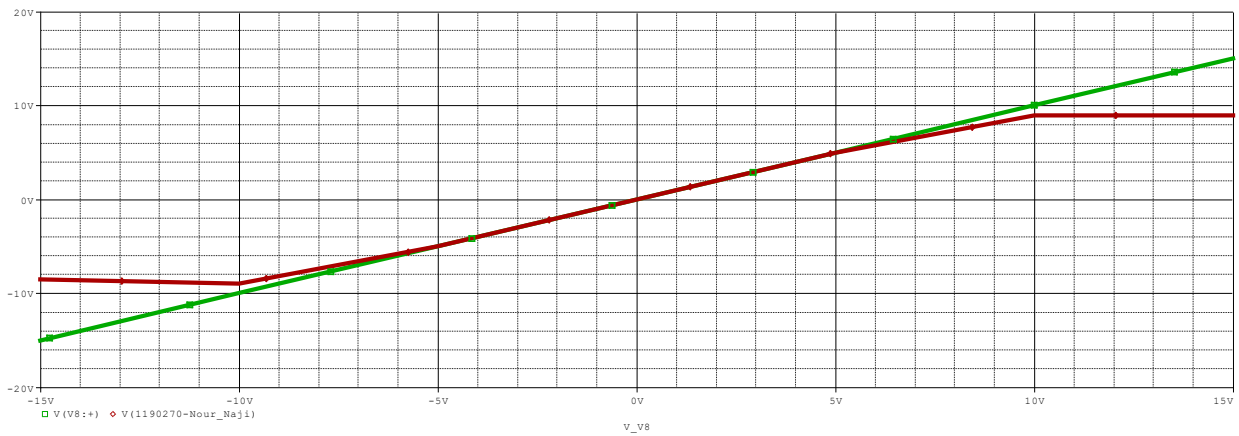- Transient Plot  $V_o$  and observe the relationship between  $V_o$  and  $V_i$ :



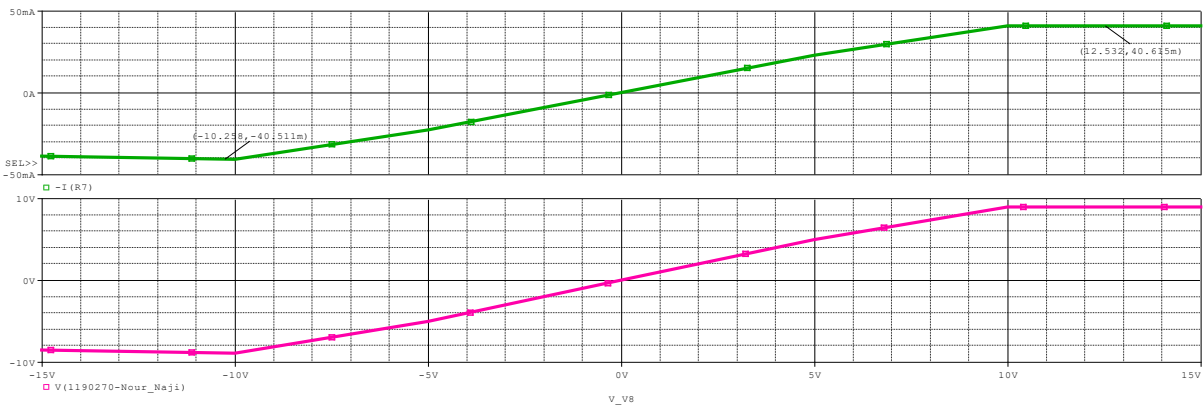
- Transient Plot  $I_o$  and observe its behavior?




In this part we have current limit at 40mA this leads to voltage limit at approximately 8.935V

- Transient Repeat 2,3,4 but with the 220-ohm resistor replaced by 10 k

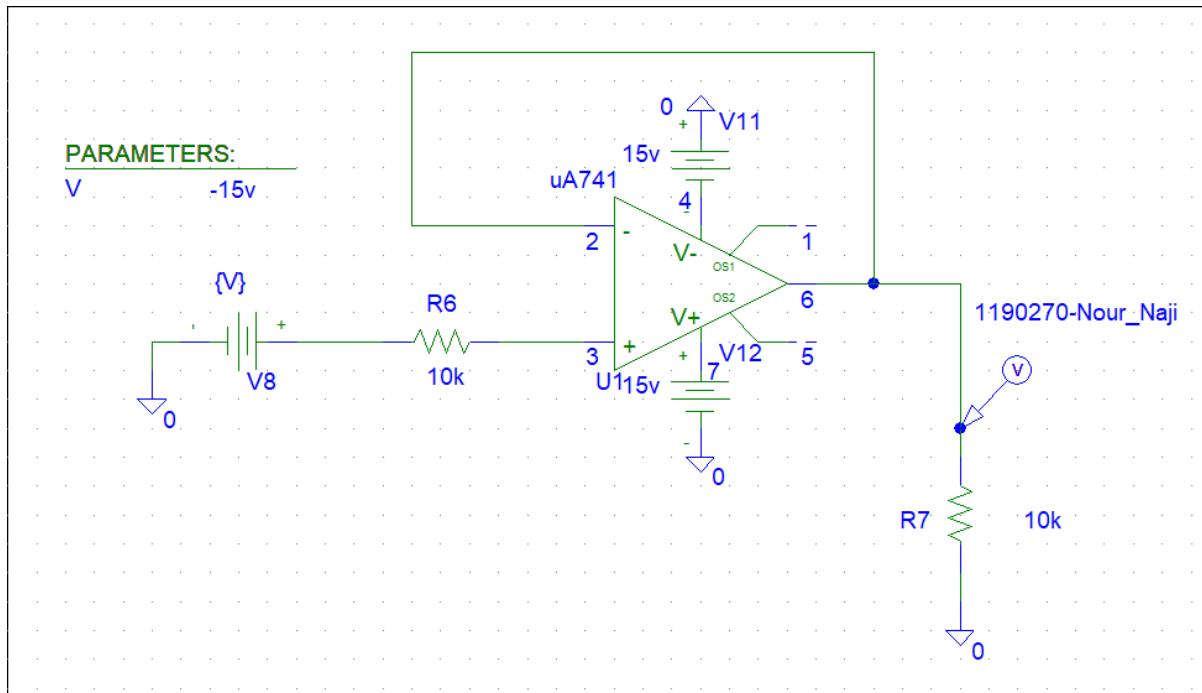
When the resistor is replaced by 10k ohm the results become as follows:



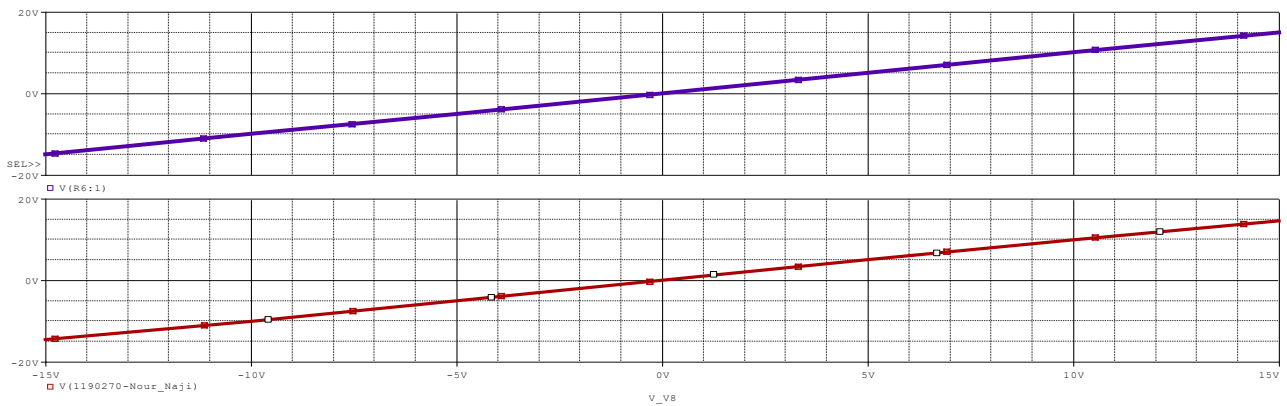- Transient Plot  $V_o$  and observe the relationship between  $V_o$  and  $V_i$ :



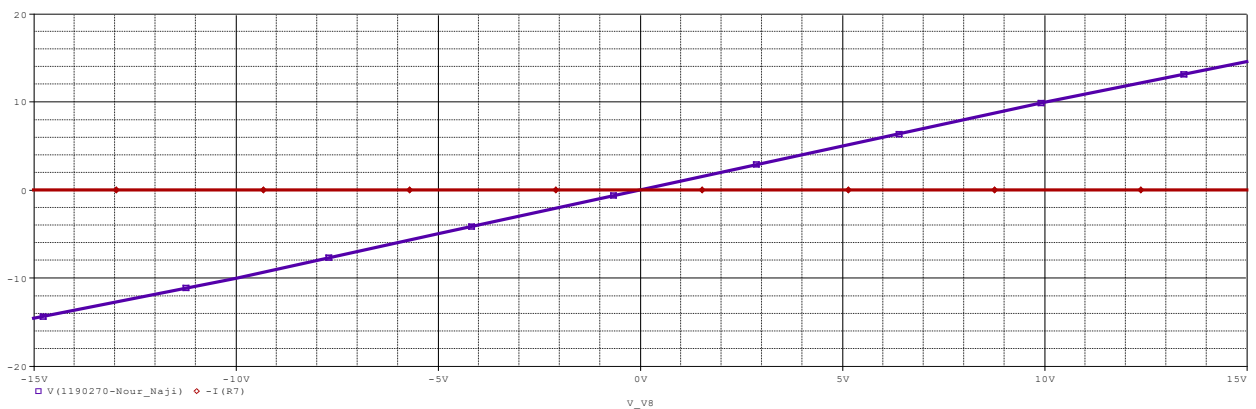- Transient Plot  $I_o$  and observe its behavior?



⇒ In this part there is no current limit.





### 3. Comparator Application:



⇒ In Opamp comparator

- If  $V (+) > V (-) \rightarrow V_o = +V_{sat}$
- If  $V (+) < V (-) \rightarrow V_o = -V_{sat}$



➤  $V_1 = 0V$

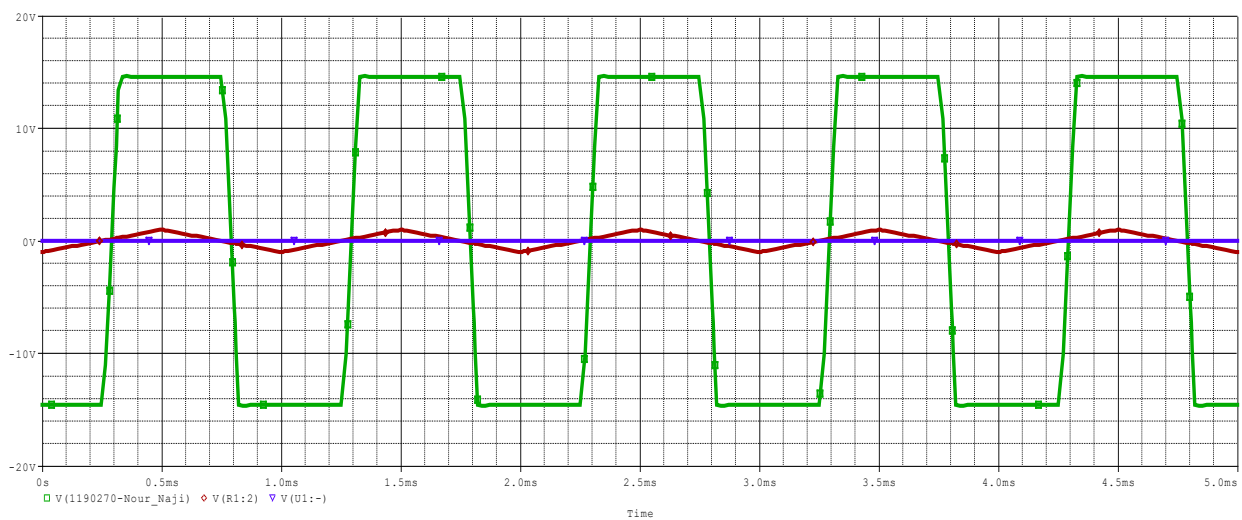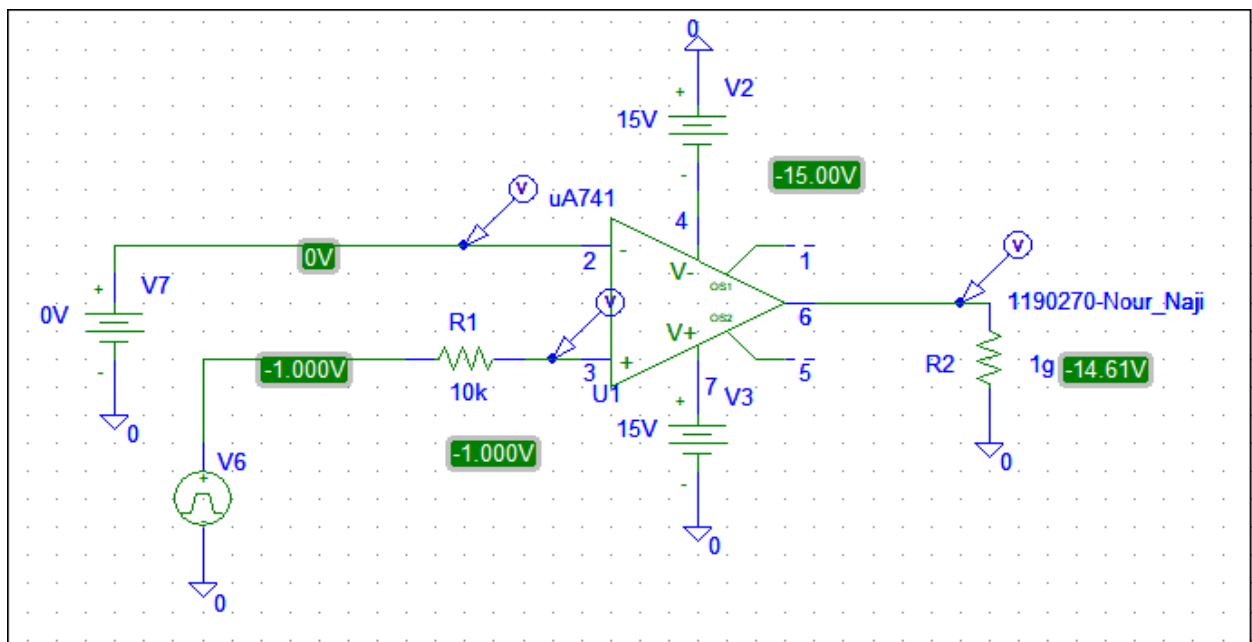

➤ **V1 = 0.98V**

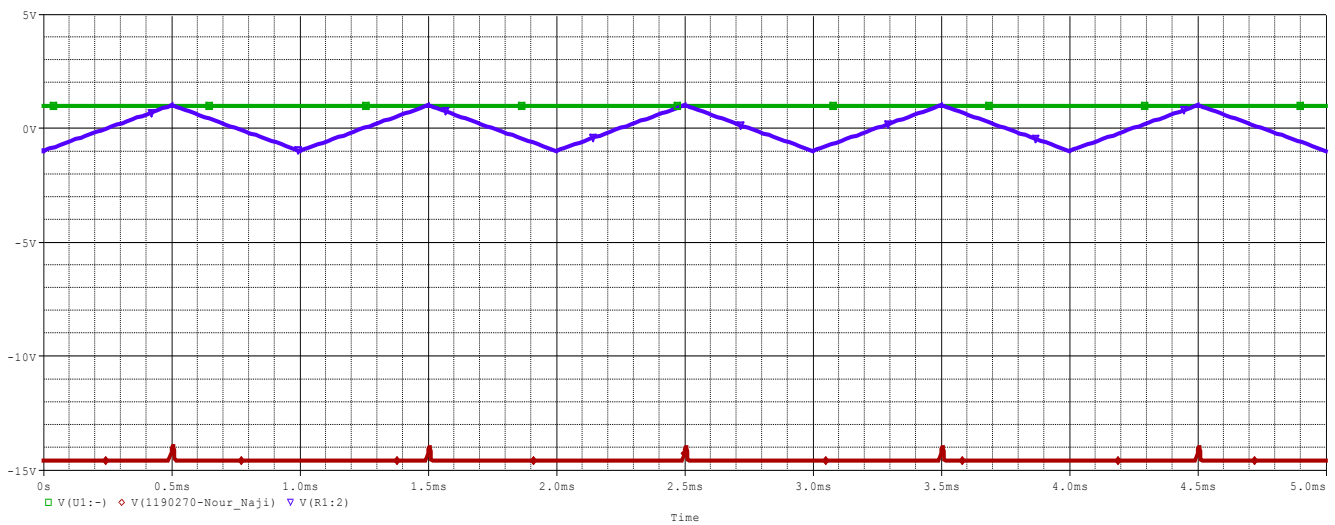
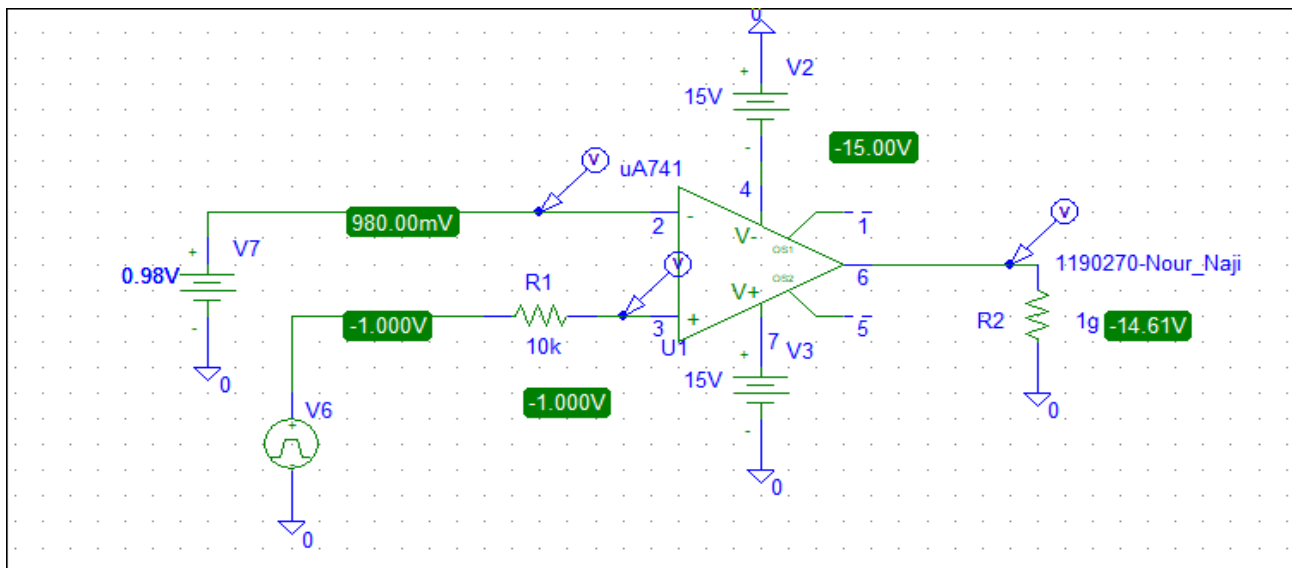


➤ **V1 = -0.98V**

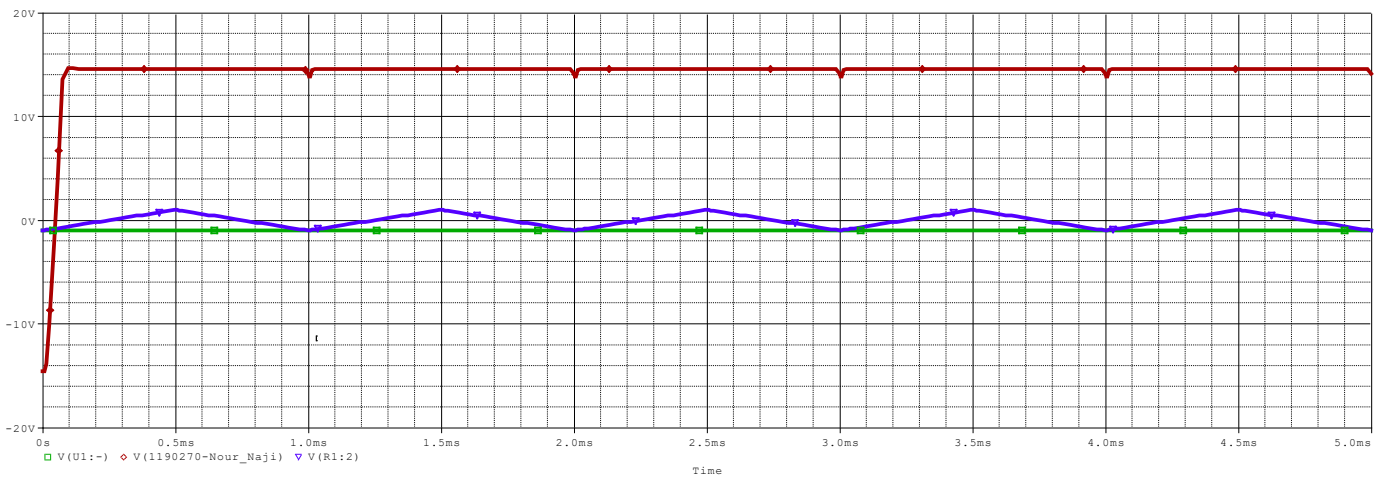
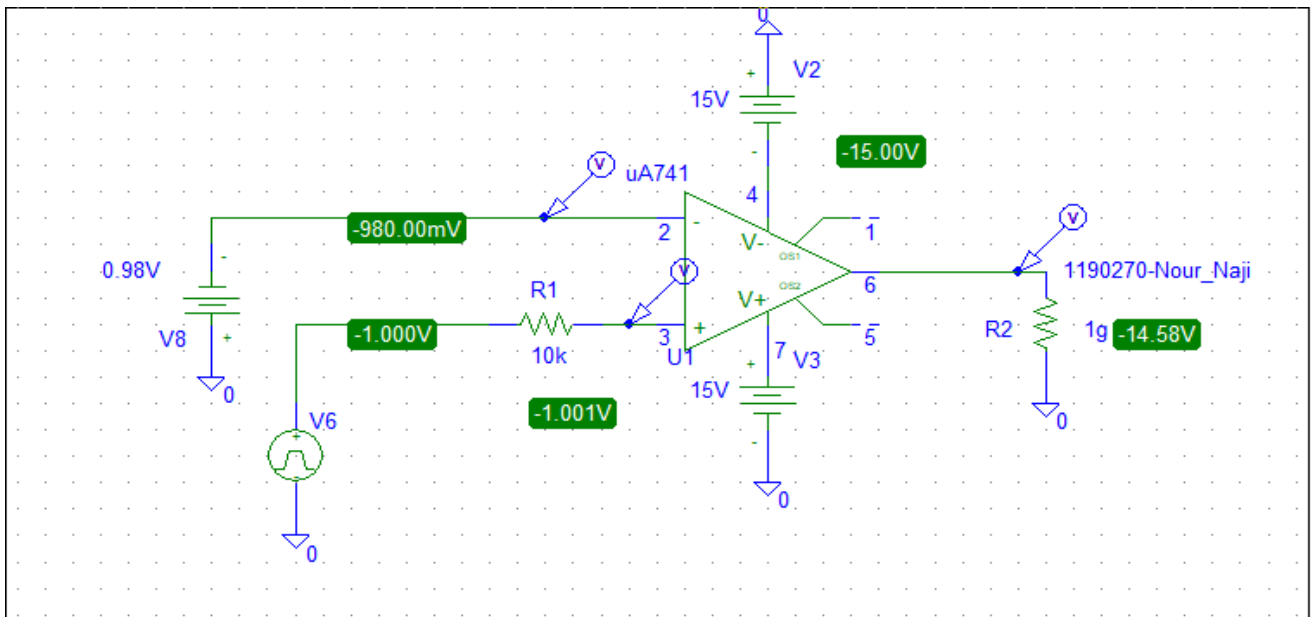


## 4. Integrator and Differentiator:



### 4.1. Integrator:

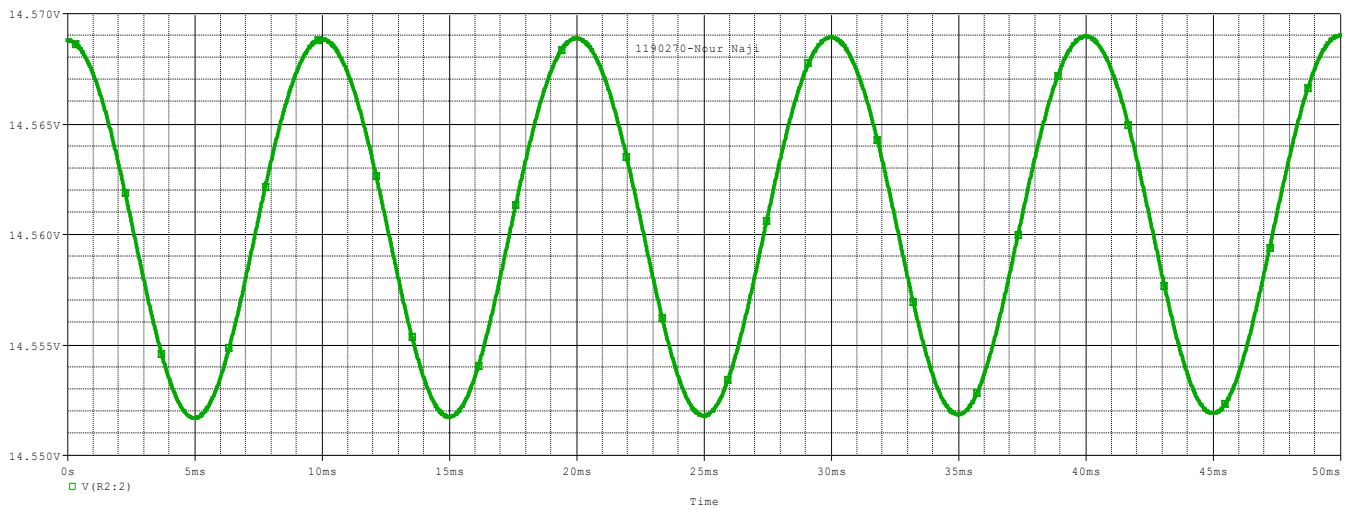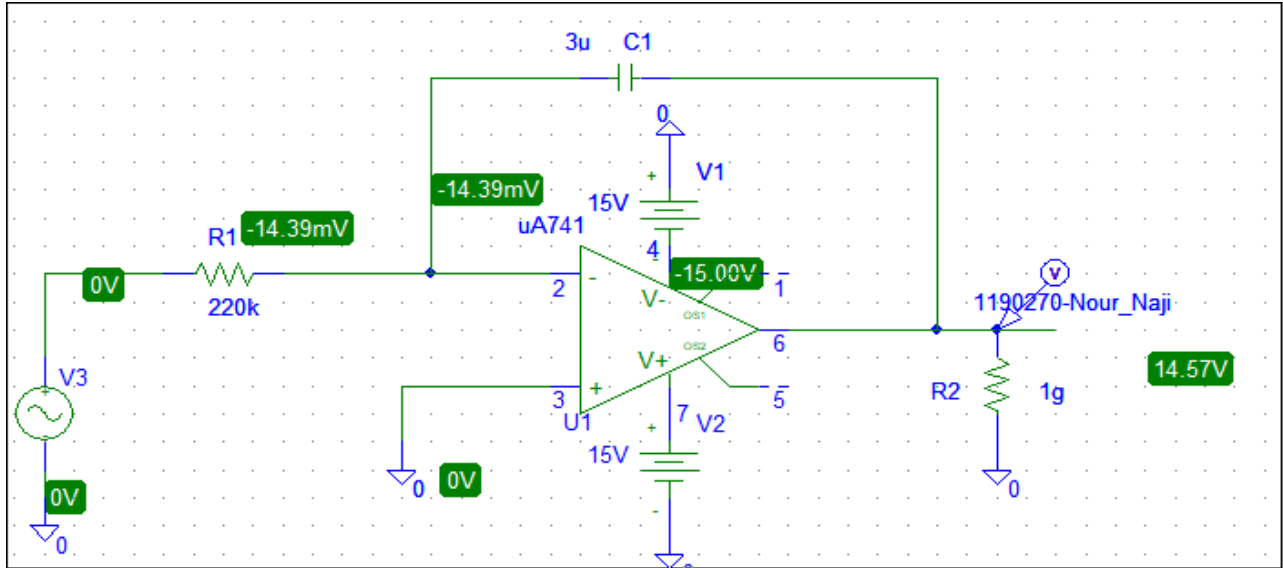

### 4.2 Differentiator:

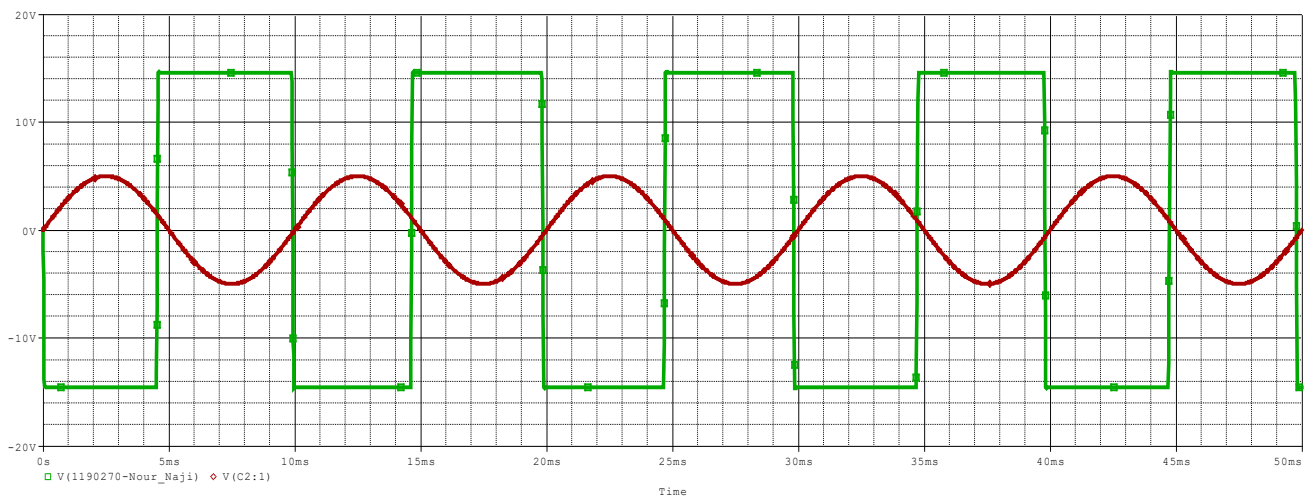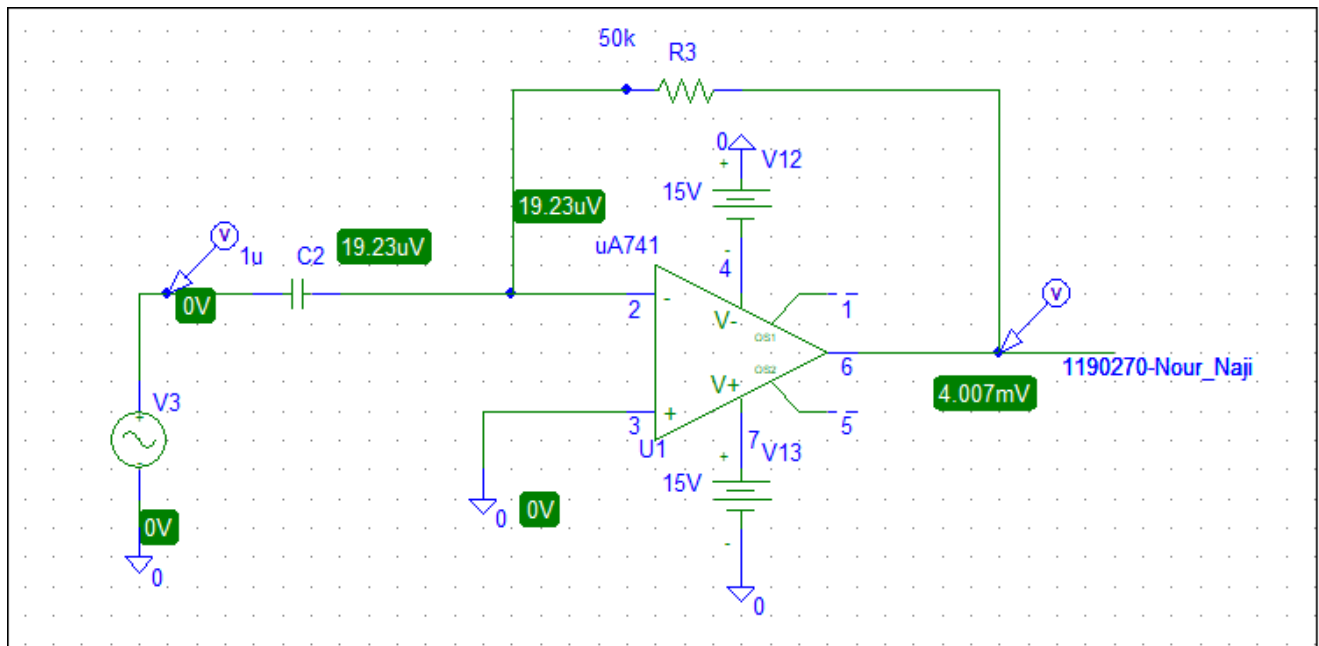
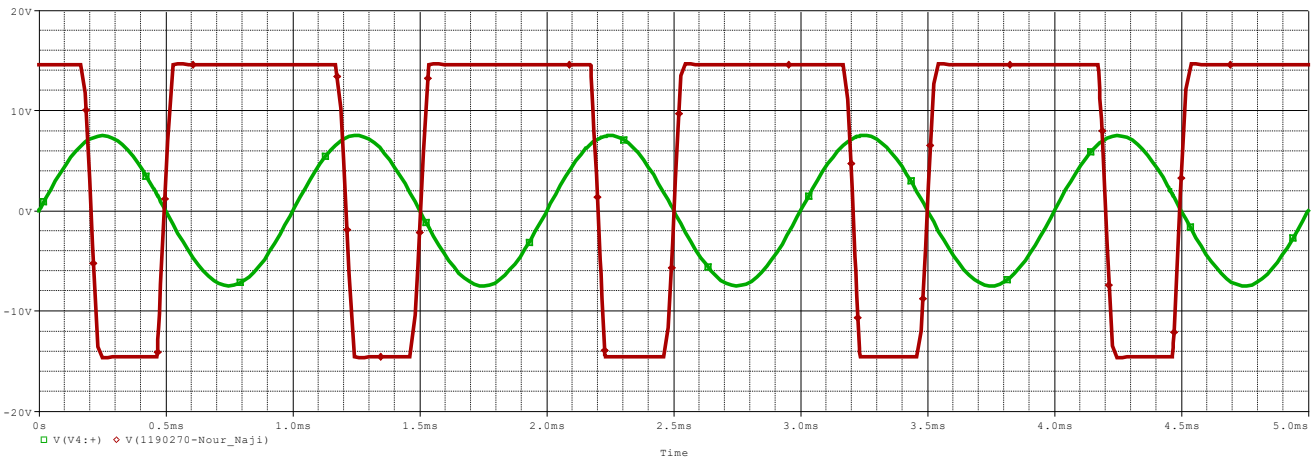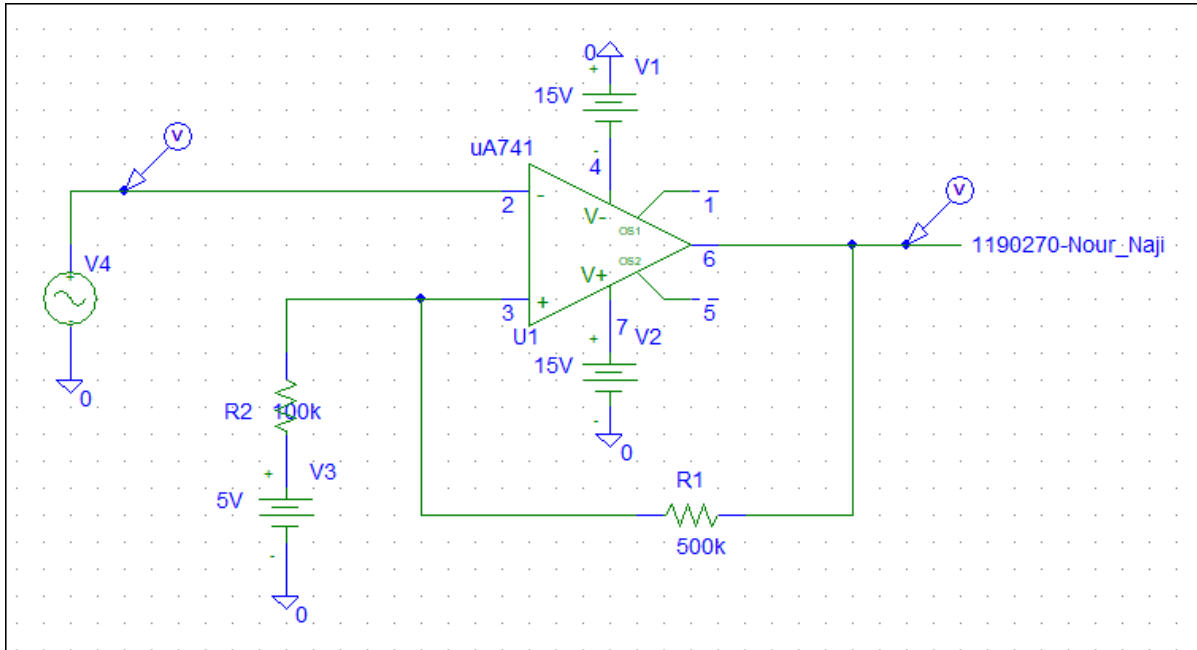
### 5. To investigate the effect of adding hysteresis



The reference voltage at the non-inverting input changes creating two different reference voltage values and two different switching points. One point being called the Upper Trip Point (UTP), while the other is called the Lower Trip Point (LTP). The difference between these two trip points is known as Hysteresis.