



Faculty of Engineering and Technology
Department of Electrical and Computer Engineering

ENEE 2103

CIRCUITS AND ELECTRONICS LABORATORY

Experiment #11, Pre-Lab #7

Zener Diodes and Voltage Regulators

Prepared by:

Nour Naji-1190270

Section: 1

Supervised by:

Dr. Alhareth Zyoud

Teaching assistant:

Eng. Esmail Abu alia

Date: 1/11/2020


Table of Contents

1.ZENER DIODE	1
1.1 Zener diode with 1 k Ω resistor	1
1.2 Zener diode with 100 Ω resistor	2
1.3 Zener diode with load resistor.....	3
2.THE VOLTAGE REGULATED POWER SUPPLY	4
2.1 Opamp series voltage regulator.....	4
2.2Opamp series voltage regulator with current limit.....	9


1. ZENER DIODE.

1.1 Zener diode with 1 k Ω resistor


→ Circuit using PSpice:

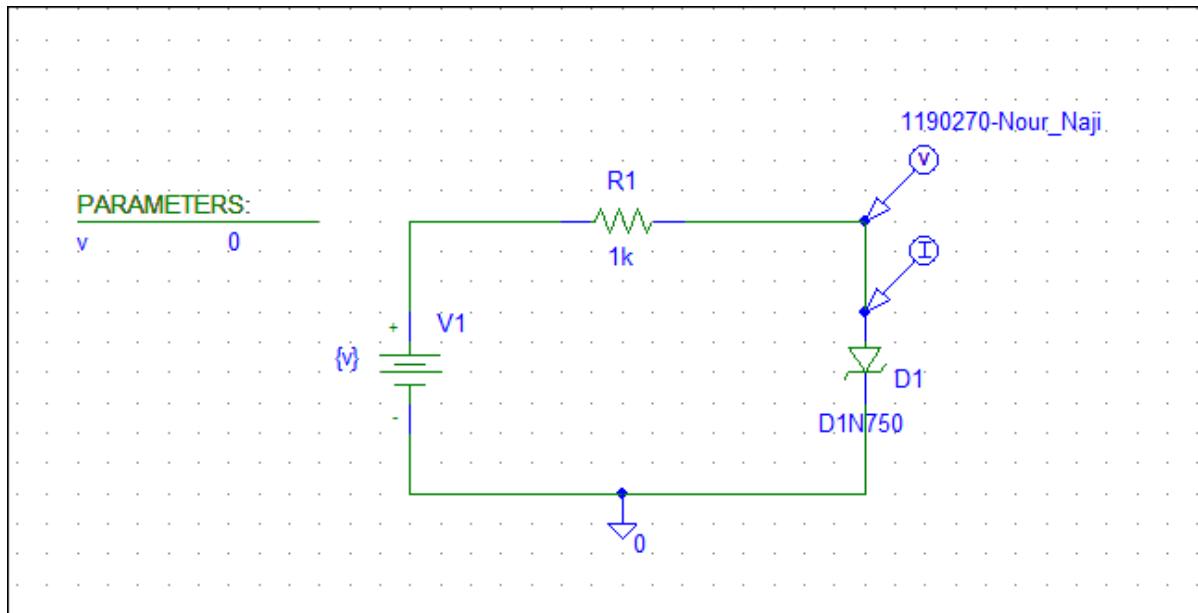

- Zener voltage (V_o) :

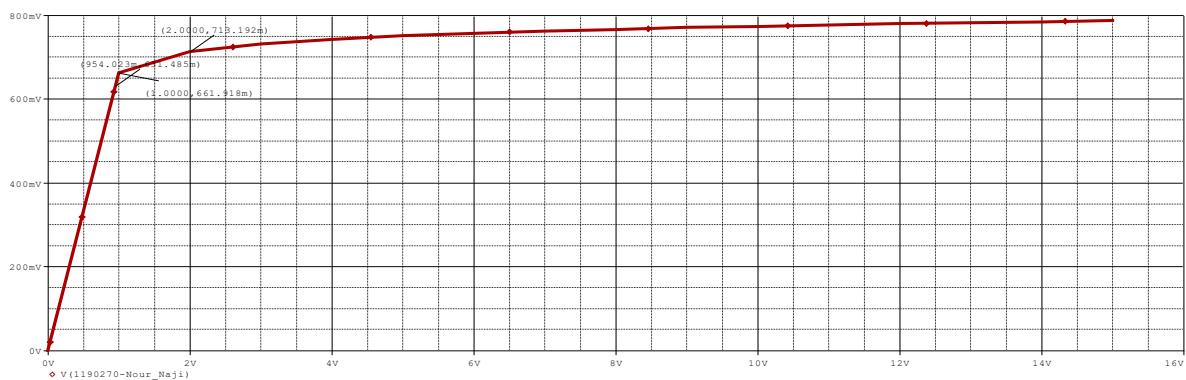


- Current in the circuit: (I_z) :

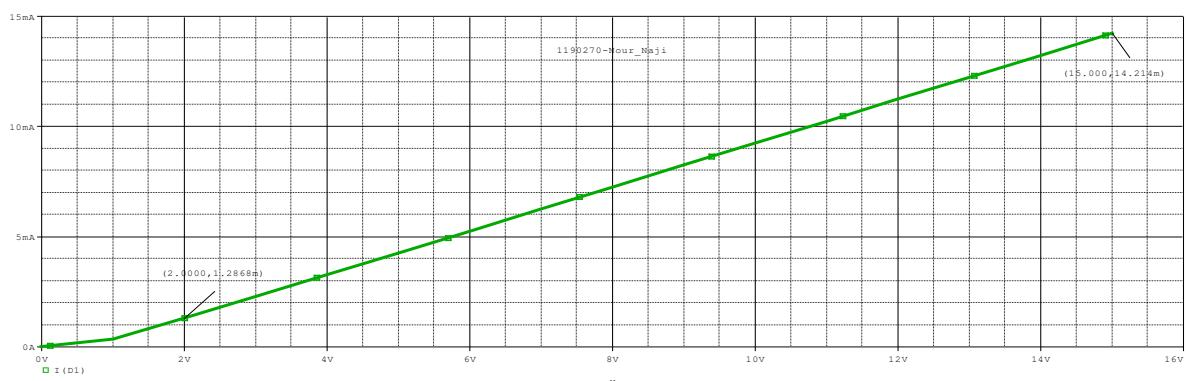


1.2 Zener diode with $100\ \Omega$ resistor


→ Circuit using PSpice:

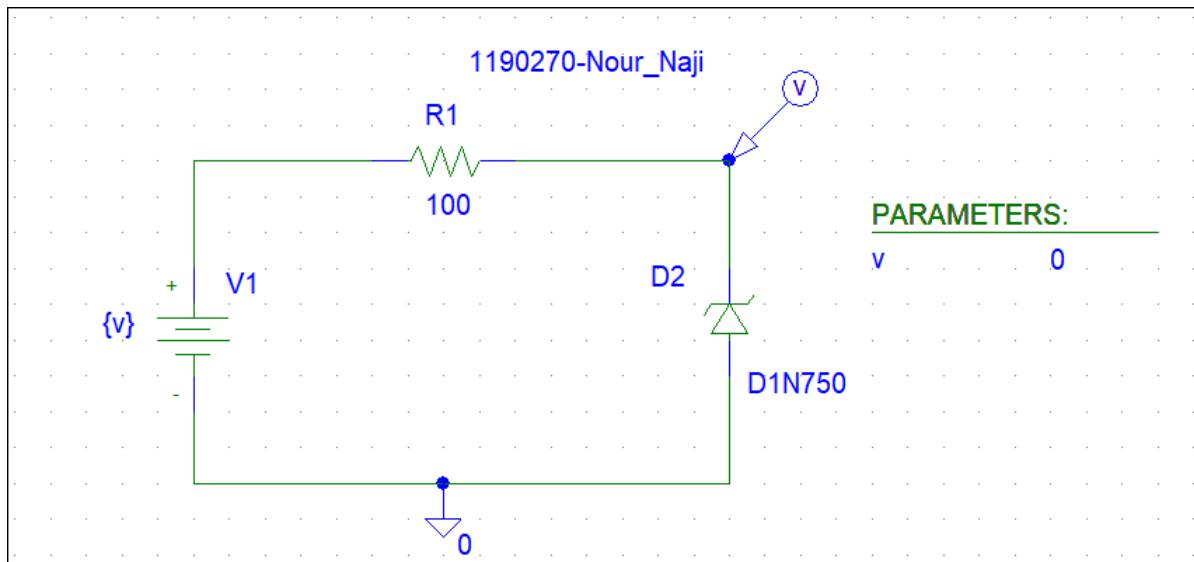

- Zener voltage (V_o) :

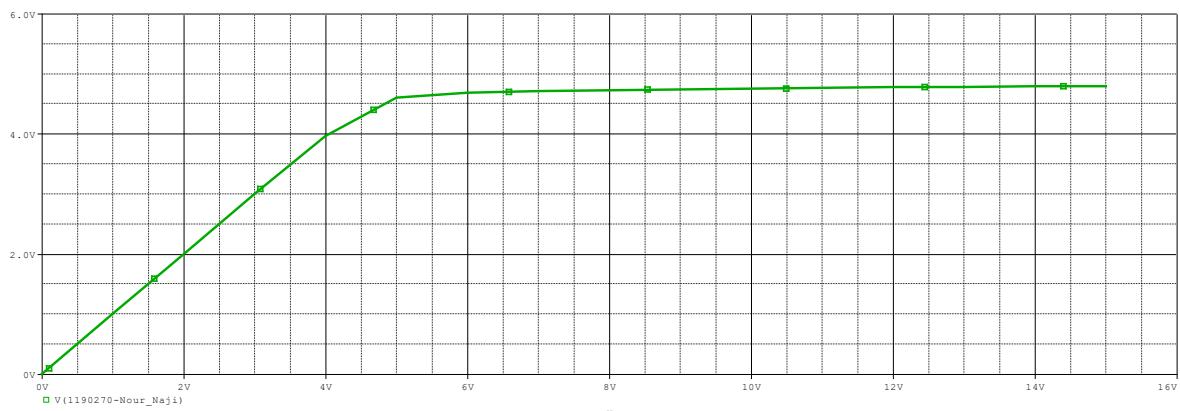


- Current in the circuit: (I_z) :

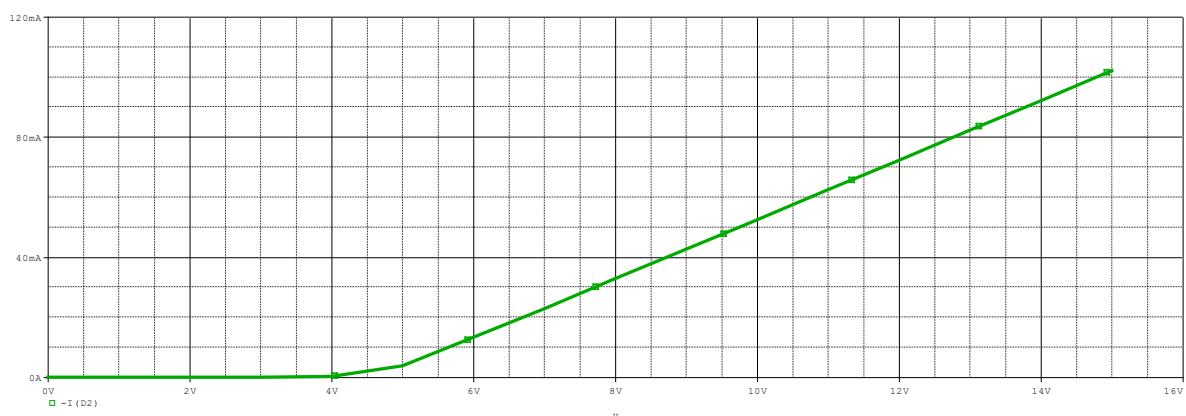


1.3 Zener diode with load resistor

→ Circuit using PSpice:

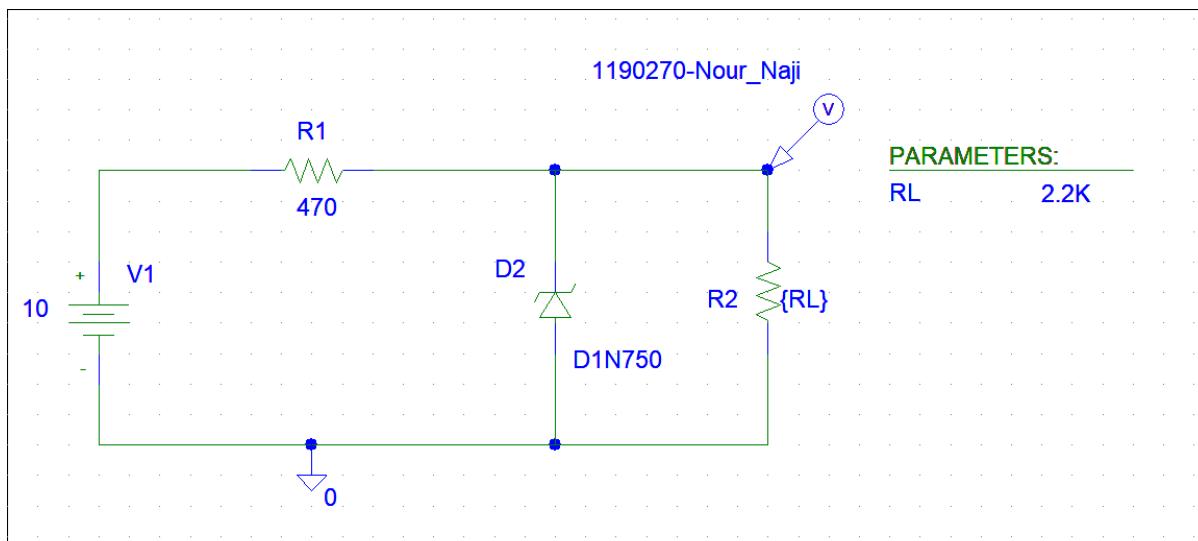

- Voltage across the load resistor:

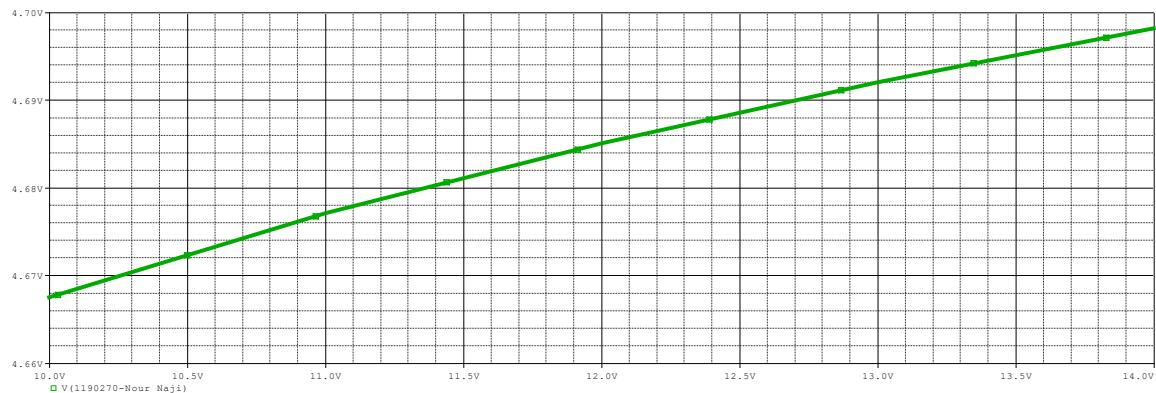


- Voltage across RL after applying DC sweep for it, and the input voltage is 10 V:



2. THE VOLTAGE REGULATED POWER SUPPLY.

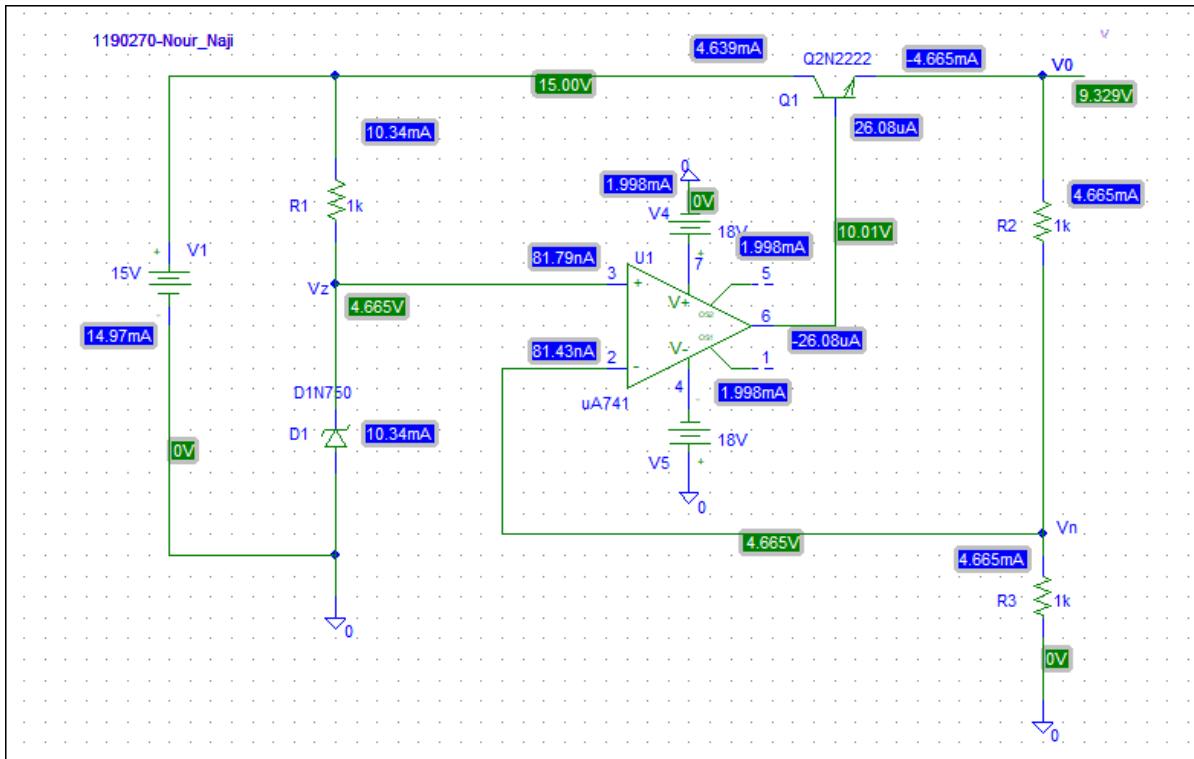2.1 Opamp series voltage regulator


- Circuit using PSpice and Bias point analysis



From the bias point analysis of the circuit:

- $V_o = 9.329\text{V}$
- $V_z = 4.665\text{V}$

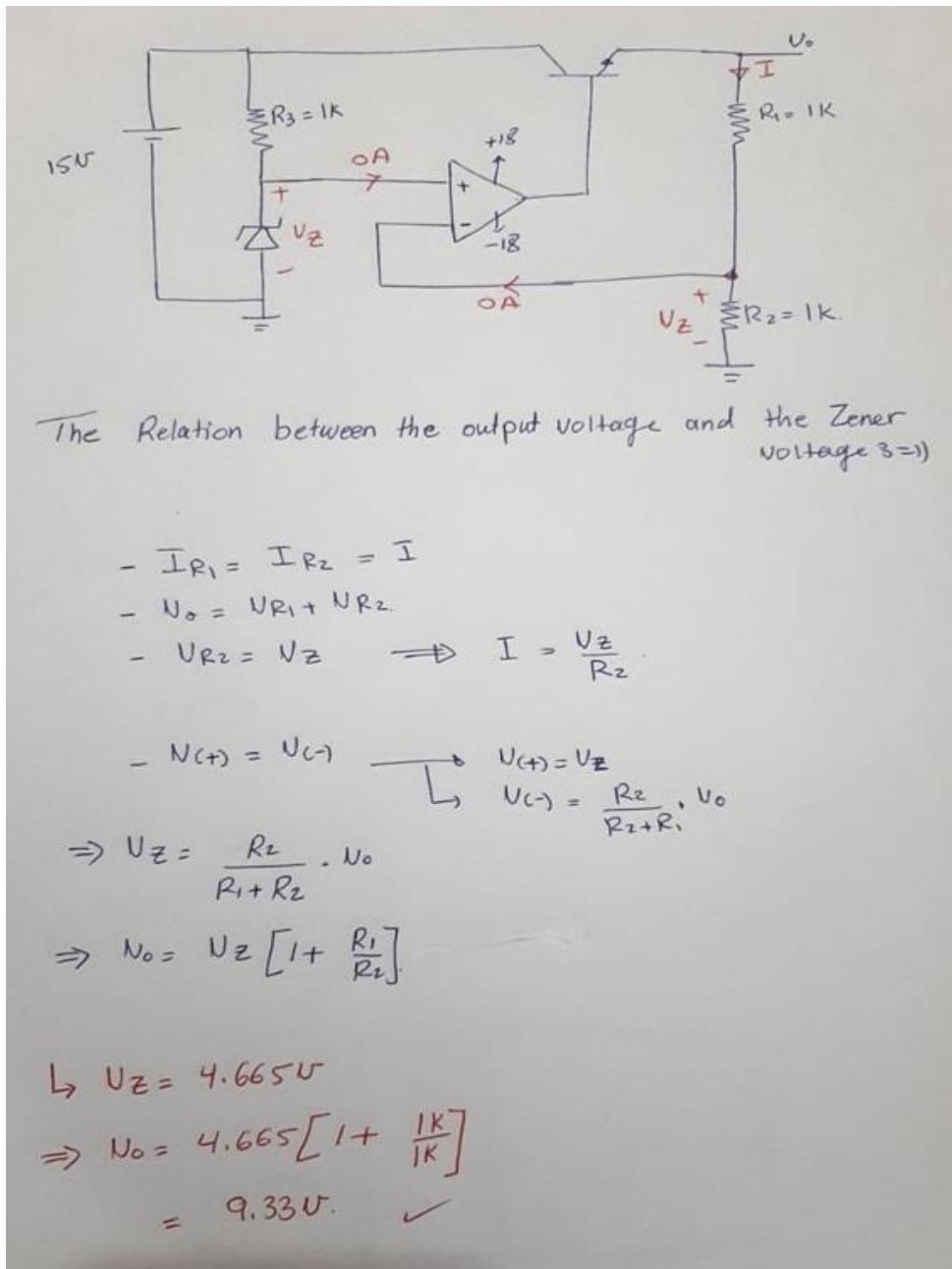
How V_o and V_z are related to each other?



- ❖ From this equation $V_o = V_z [1 + \frac{R_2}{R_3}]$, we conclude that V_o voltage is directly proportional to the Zener voltage. As far as the Zener voltage remains stable, V_o also remains stable.
 - ❖ V_o is not possible to exceed V_1 . It can be almost as much high as V_1 when T_1 saturates, but no more than this. V_o could not also be lower than V_z . That's why $V_z < V_o < V_1$.

Attach a 1k load resistor to the output


⇒ Circuit using PSpice :

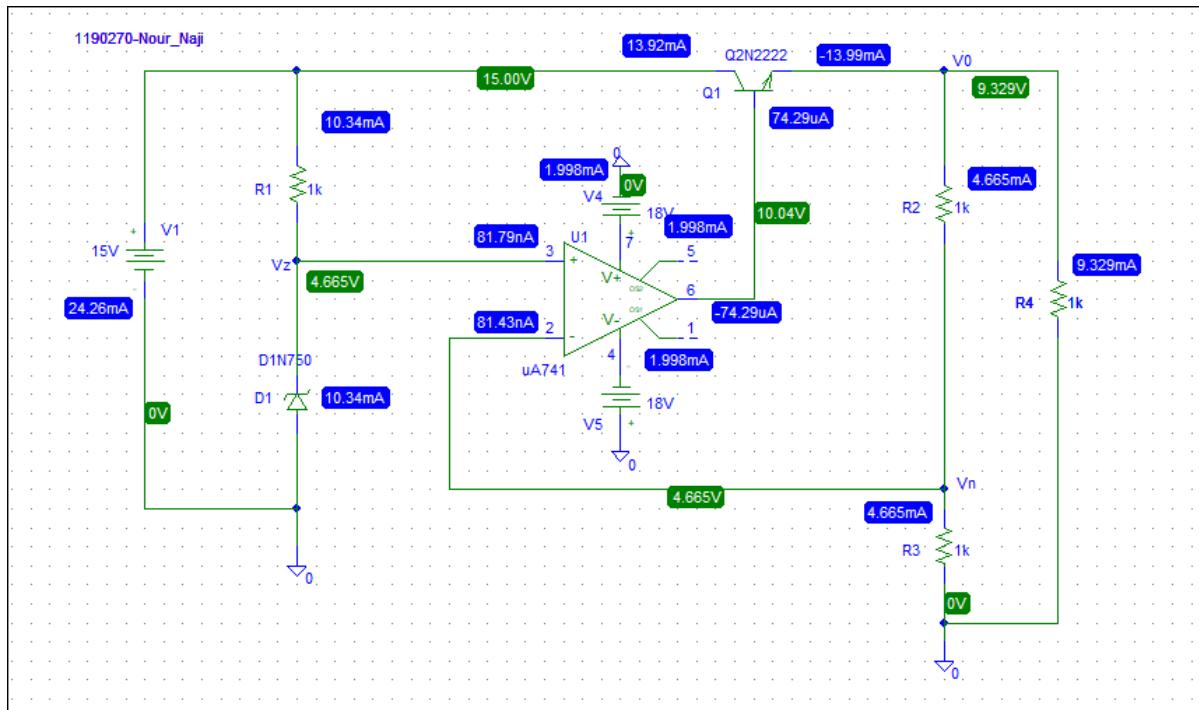


- $V_o = 9.329 \text{ v}$
- $I_o = 9.329 \text{ mA} \rightarrow$ which is obtained from the relation $I_o = \frac{V_o}{R_4} = \frac{9.329}{1K}$

➤ Applying DC sweep for the Load Resistor (RL):

V_o :

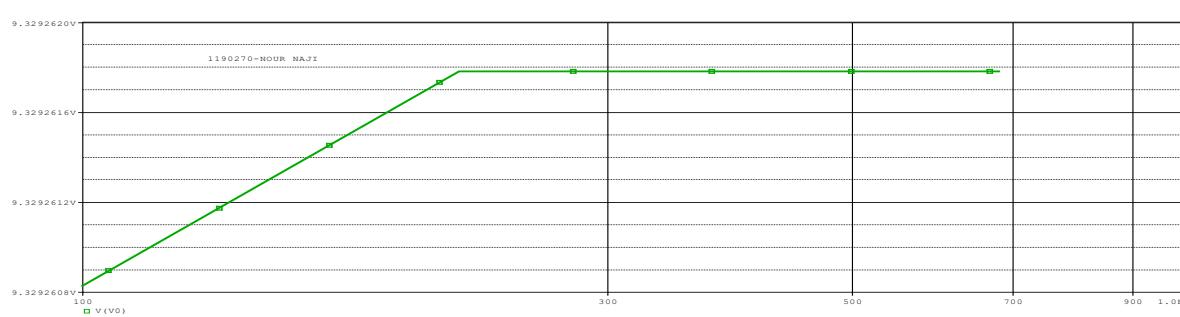


I_o :

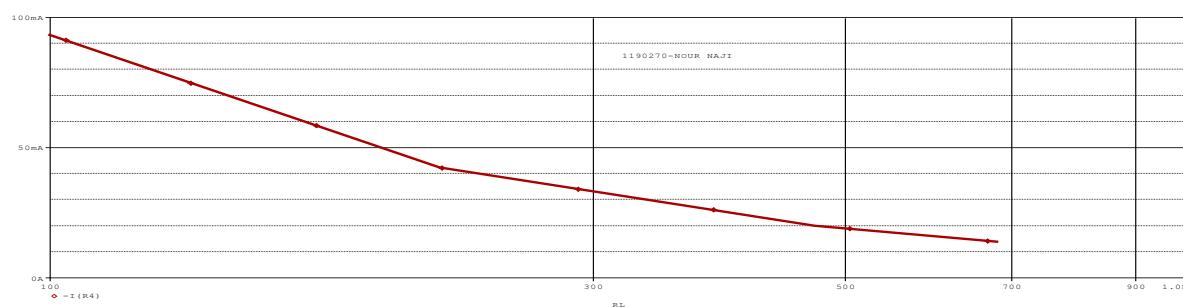


- $RL = 1 \text{ k}\Omega$, $R3 = 470 \Omega$:

⇒ Circuit using PSpice

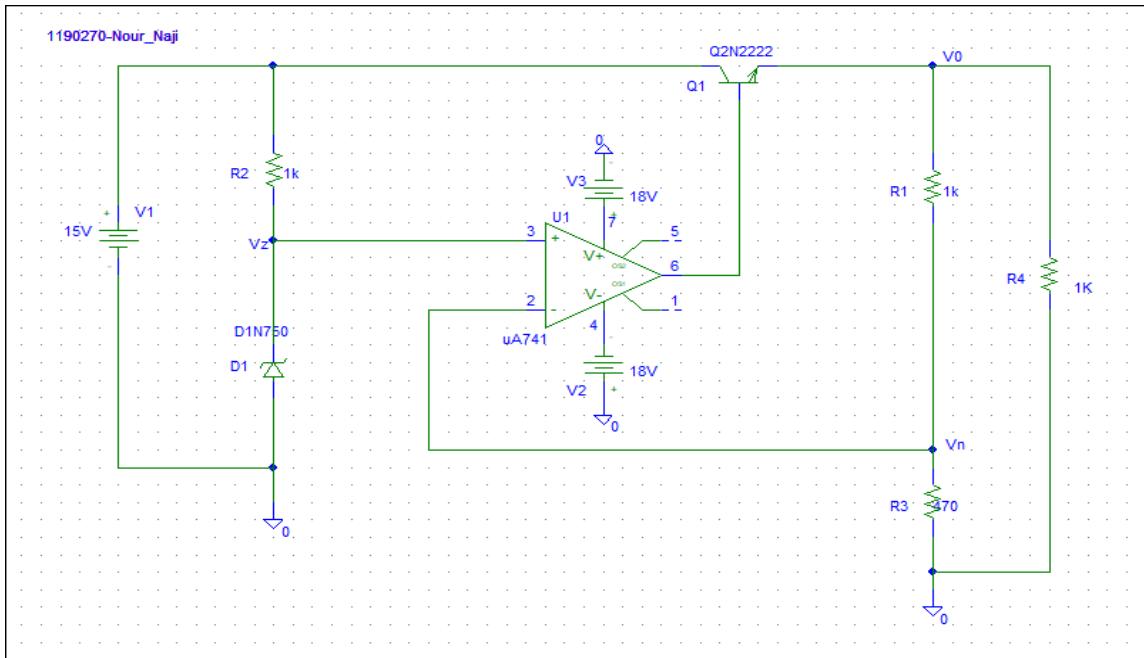

- Bias point analysis:

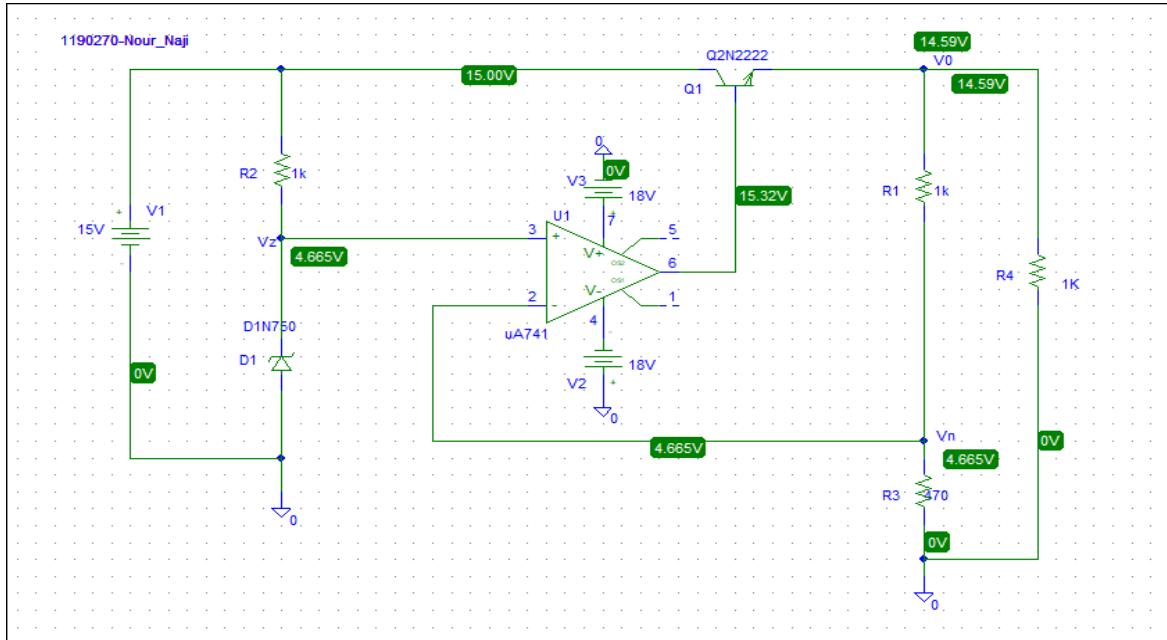


⇒ The output voltage (V_o) = 14.59 V, and the voltage across the Zener (V_z) = 4.665 V.


$$\Rightarrow V_o = V_z [1 + \frac{R_2}{R_3}] = V_o = 4.665 [1 + \frac{1K\Omega}{470\Omega}] = 14.59V.$$

- $RL = 1 \text{ k}\Omega$, $R3 = 2.2 \text{ k}\Omega$:

⇒ Circuit using PSpice

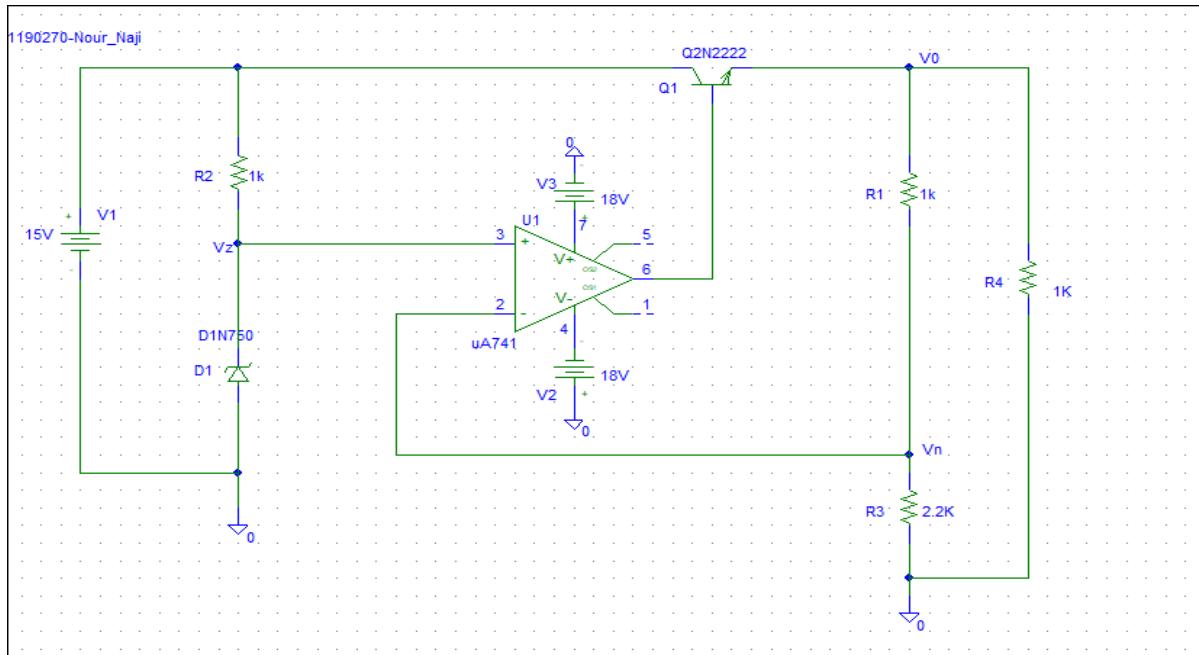

- Bias point analysis:

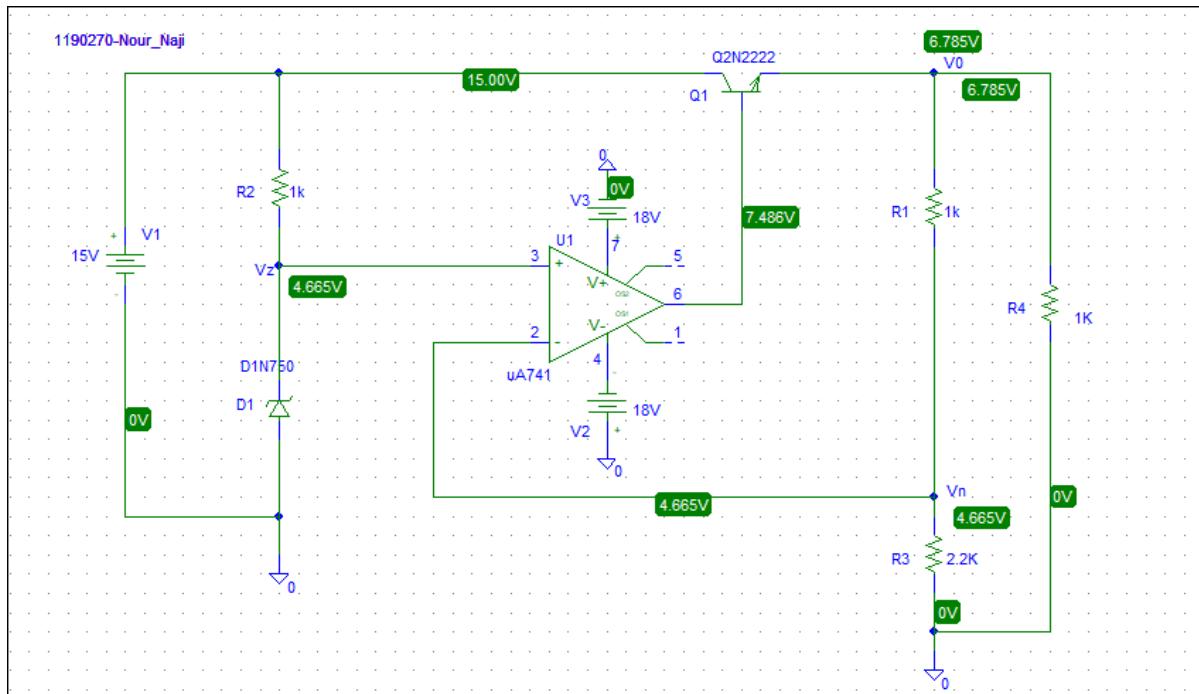


⇒ The output voltage (V_o) = 6.785V, and the voltage across the Zener (V_z) = 4.665 V.


$$\Rightarrow V_o = V_z [1 + \frac{R_2}{R_3}] = V_o = 4.665 [1 + \frac{1K\Omega}{2.2K\Omega}] = 6.7854.$$

2.2 Opamp series voltage regulator with current limit

- Circuit using PSpice:

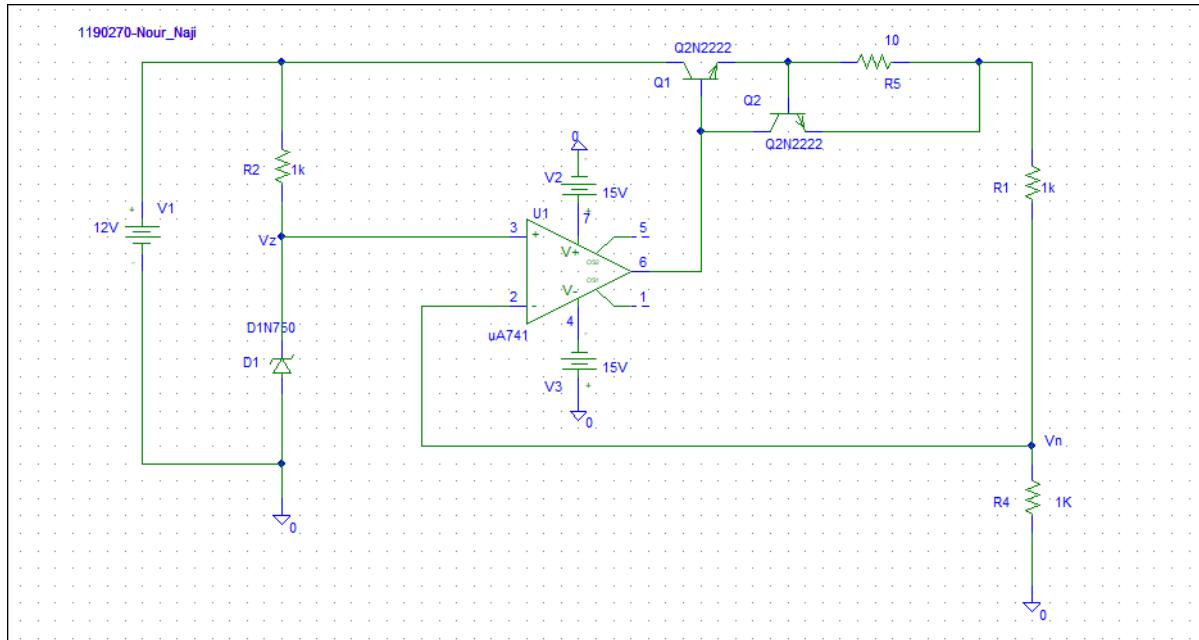


- Bias point analysis:

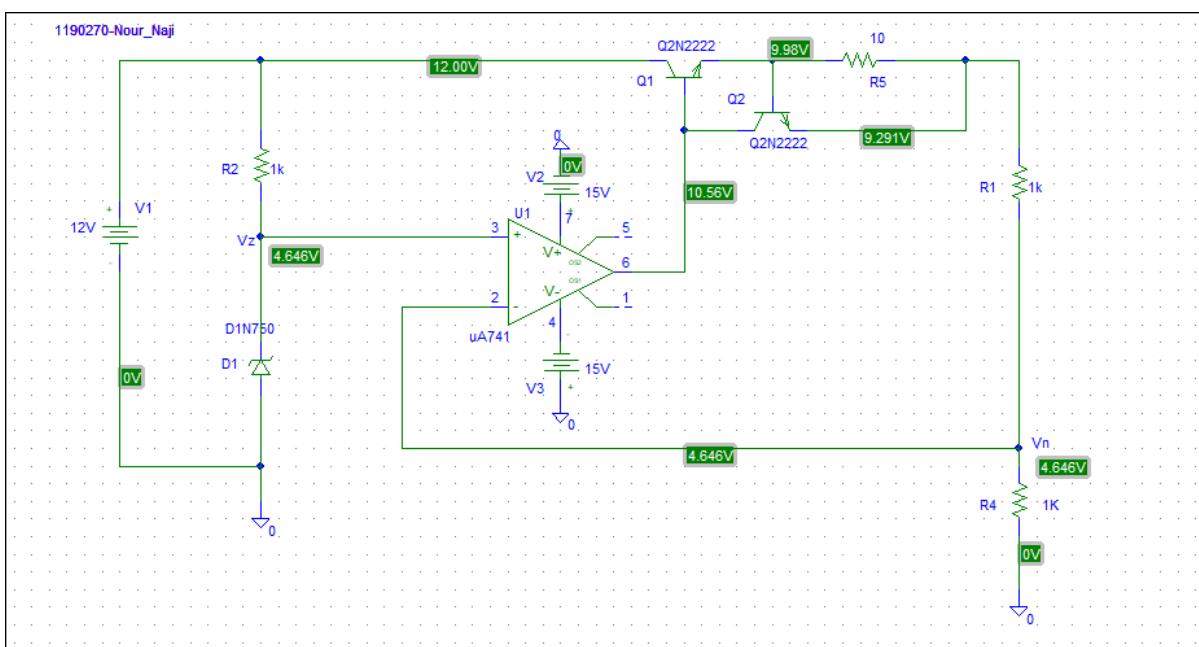


⇒ The output voltage (V_o) = 9.291 V

- Applying DC sweep for Load Resistor (RL):

V_o :

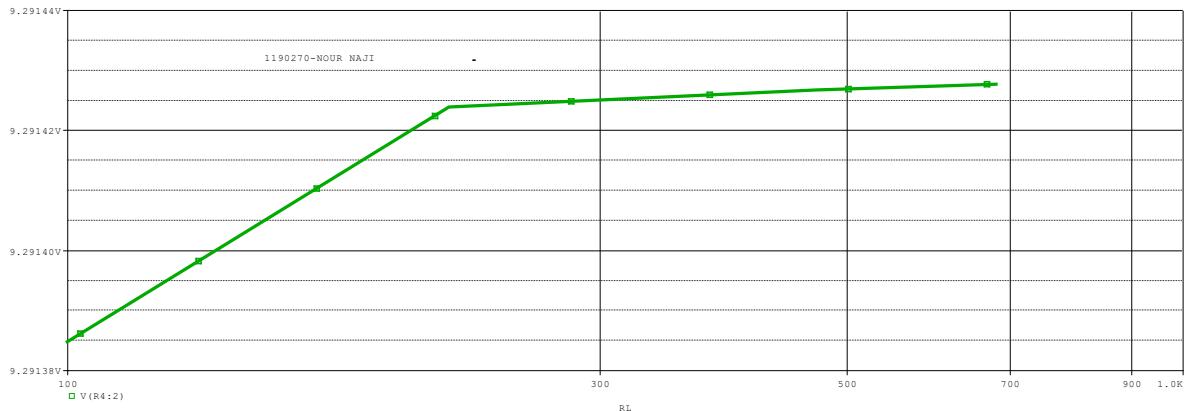


I_o :

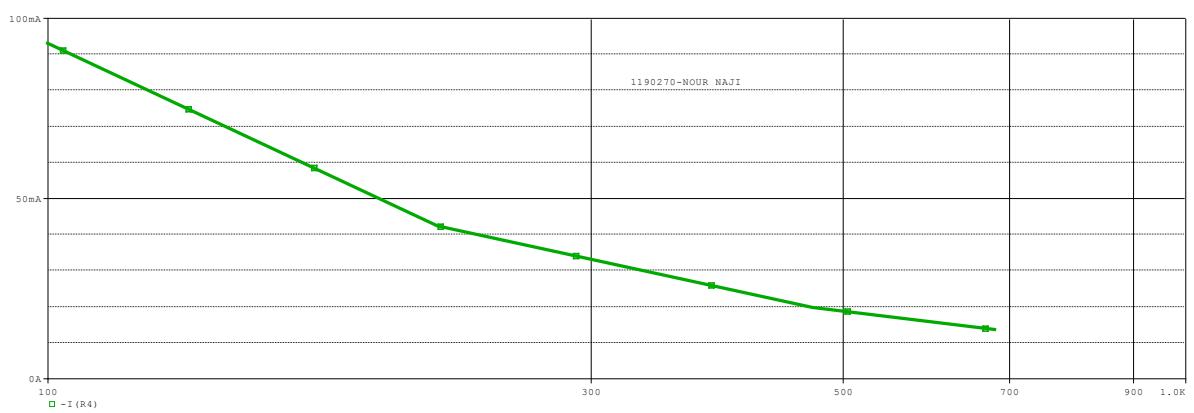


- $RL = 1 \text{ k}\Omega$, $R3 = 470 \Omega$:

- Circuit using PSpice:

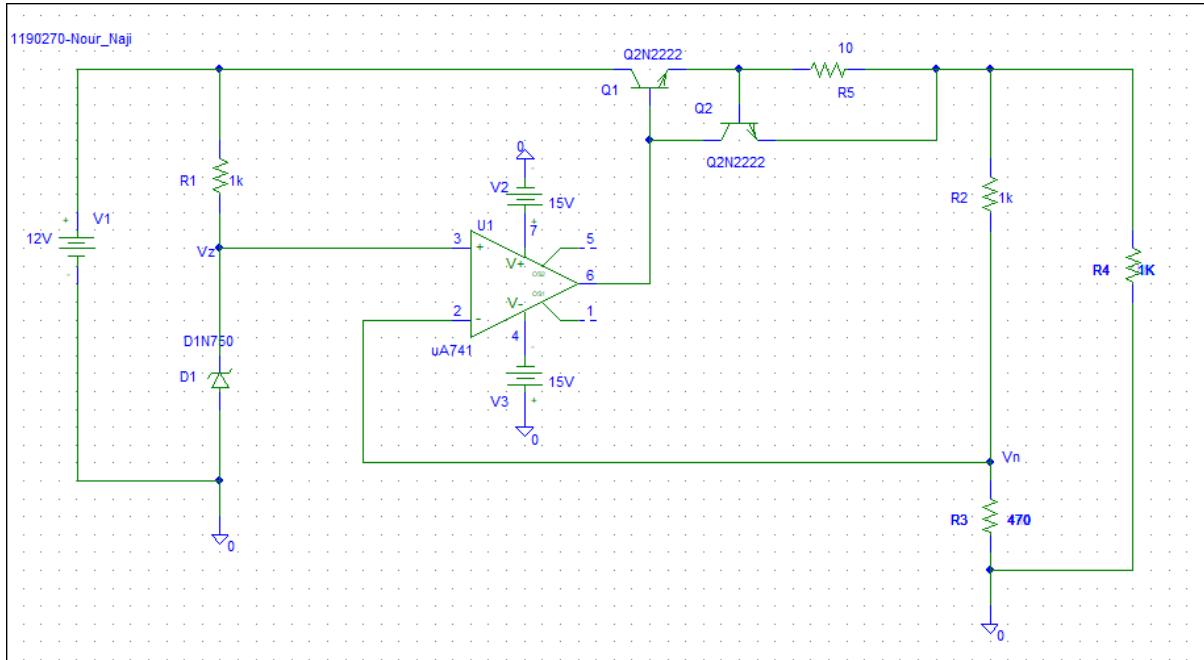

- Bias point analysis:

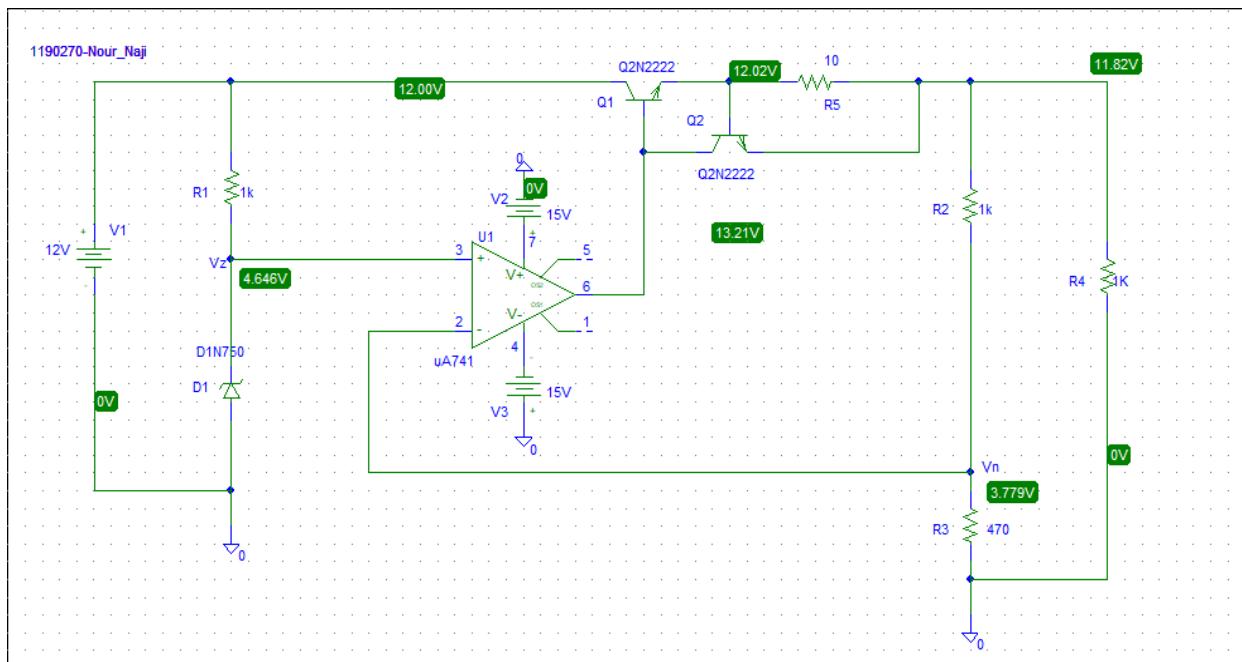

⇒ The output voltage (V_o) = 11.82 V