



Faculty of Engineering and Technology  
Department of Electrical and Computer Engineering  
CIRCUITS AND ELECTRONICS LABORATORY  
ENEE 2103

Experiment \_ 2  
Pre-Lab \_ 1  
“ Circuit Laws and Theorems ”

---

Student's Name: Nour Naji

Student ID: 1190270

Section: 1

Instructor: Dr. Alhareth Zyoud

Teaching assistant: Eng. Esmail

Date: 20/9/2021

## Part A : KVL, KCL

- $R_x = 1\text{ k}\Omega$

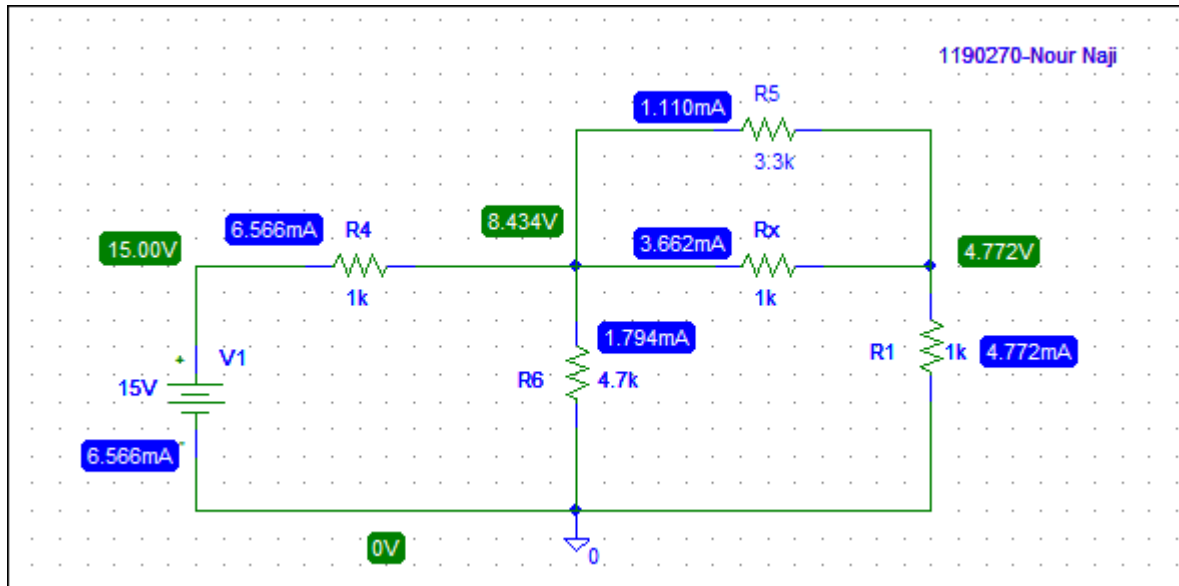


Fig 1 :  $R_x = 1\text{ k}\Omega$

- $R_x = 0.5\text{ k}\Omega$

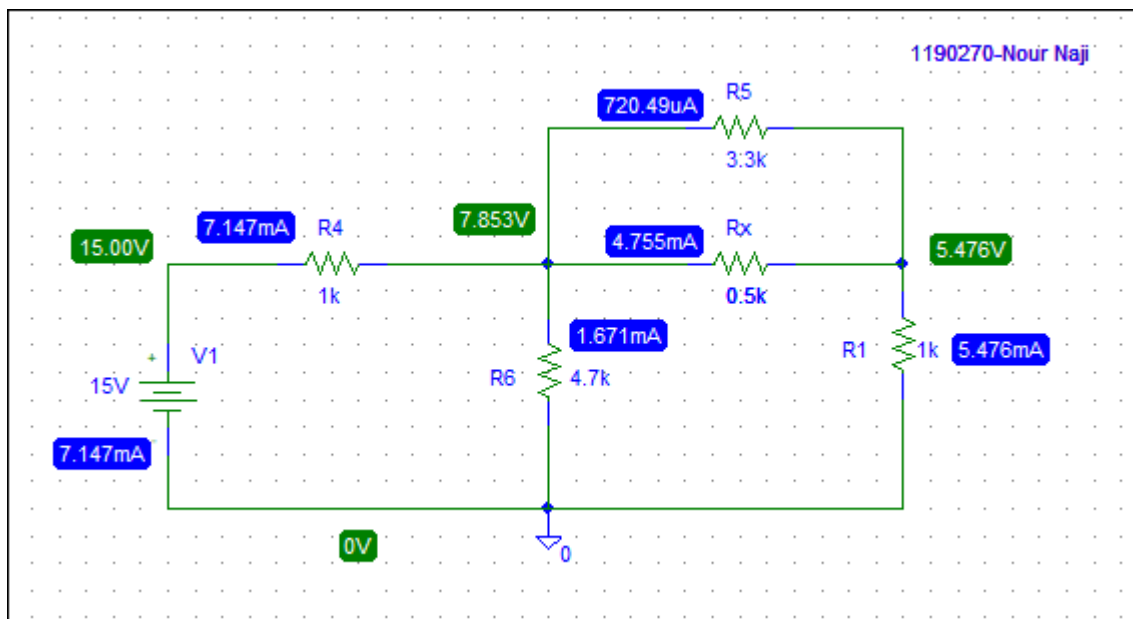


Fig 2 :  $R_x = 0.5\text{ k}\Omega$

VS	POT	R1		R4	
		V1(v)	I1(mA)	V4	I4
15v	Rx	4.772	4.722	6.566	6.566
15v	0.5Rx	5.476	5.476	7.147	7.147

R5		R6		Rx	
V5	I5	V6	I6	Vx	Ix
1.109	1.110	8.434	1.794	3.662	3.662
0.72	0.72	7.853	1.671	4.754	4.775

### Part B: Voltage & Current Division:

- Voltage division

- $R_x = 1\text{ k}\Omega$

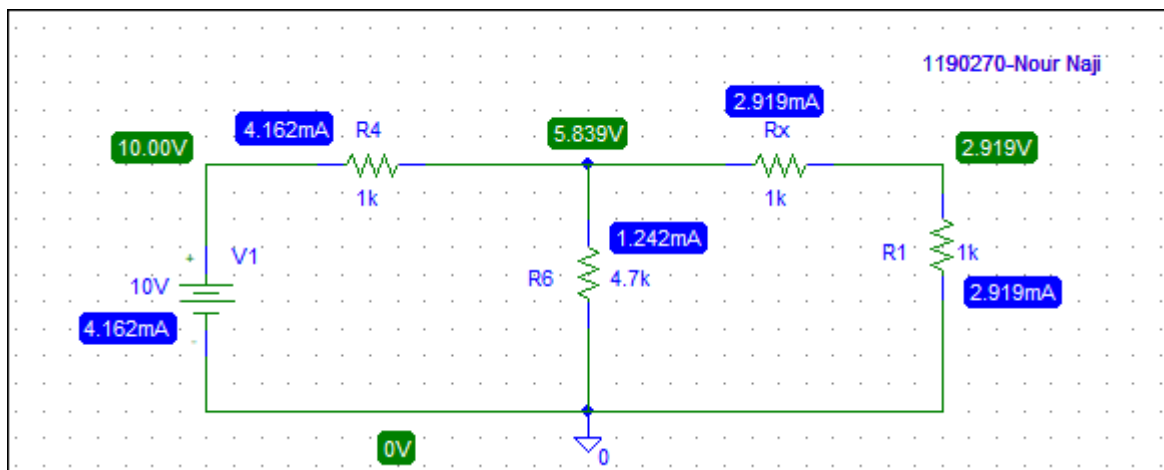


Fig 3 :  $R_x = 1\text{ k}\Omega$

- $R_x = 0.5$

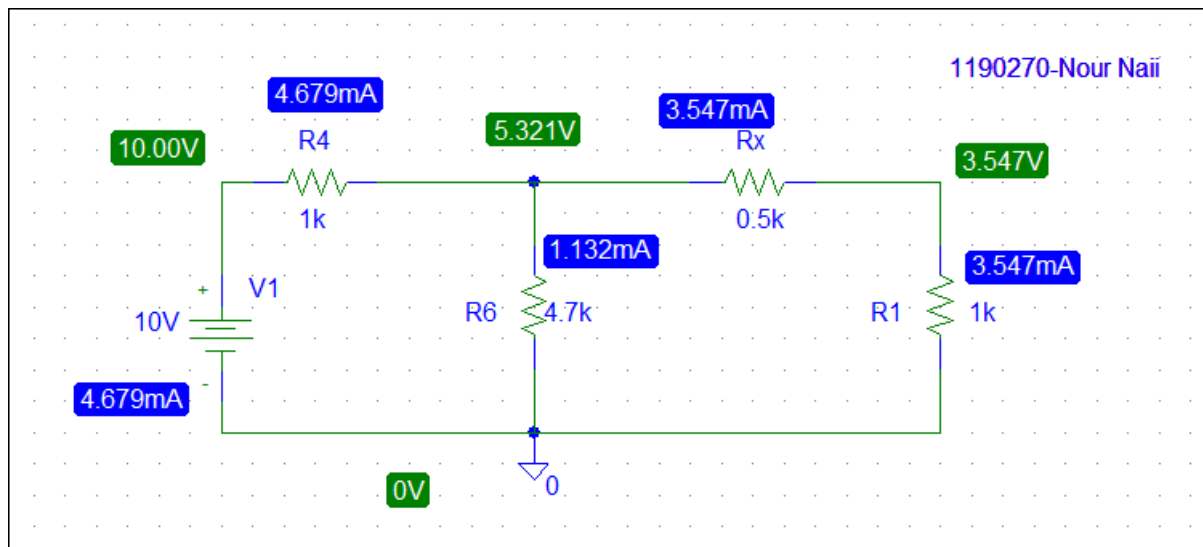


Fig 4 :  $R_X = 0.5 \text{ k}\Omega$

VS (VOLT)	POT	V1	V4	V6	VX
10 V	$R_x$	2.919	4.161	5.839	5.84
10 V	$0.5R_x$	3.547	4.679	5.321	1.774

- II. Current division

- $R_x = 1 \text{ k}\Omega$

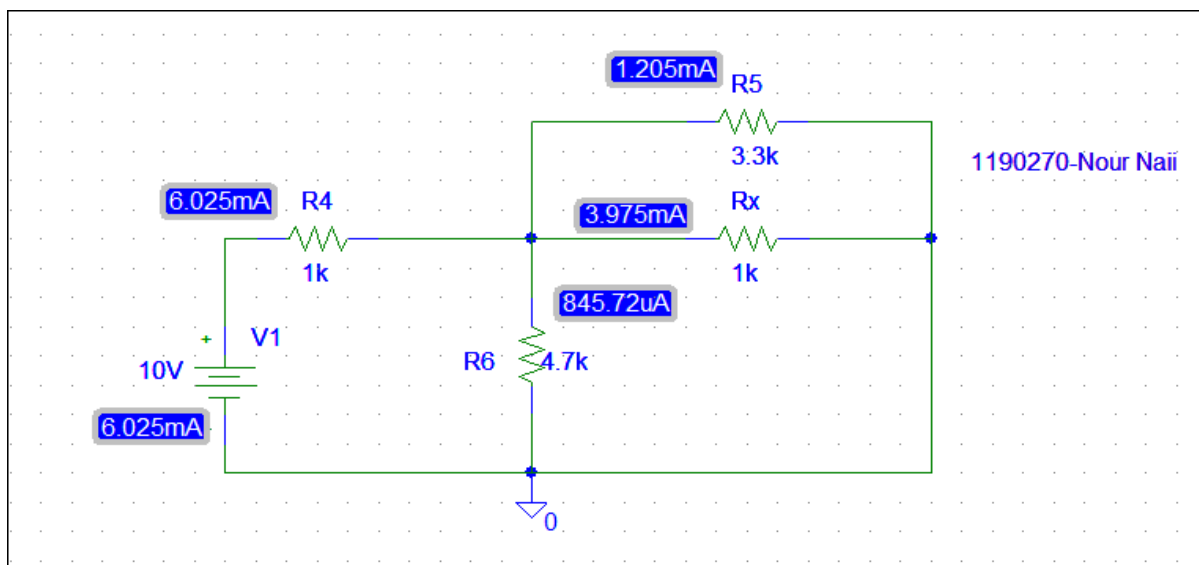


Fig 5 :  $R_X = 1 \text{ k}\Omega$

- $R_x = 0.5 \text{ k}\Omega$

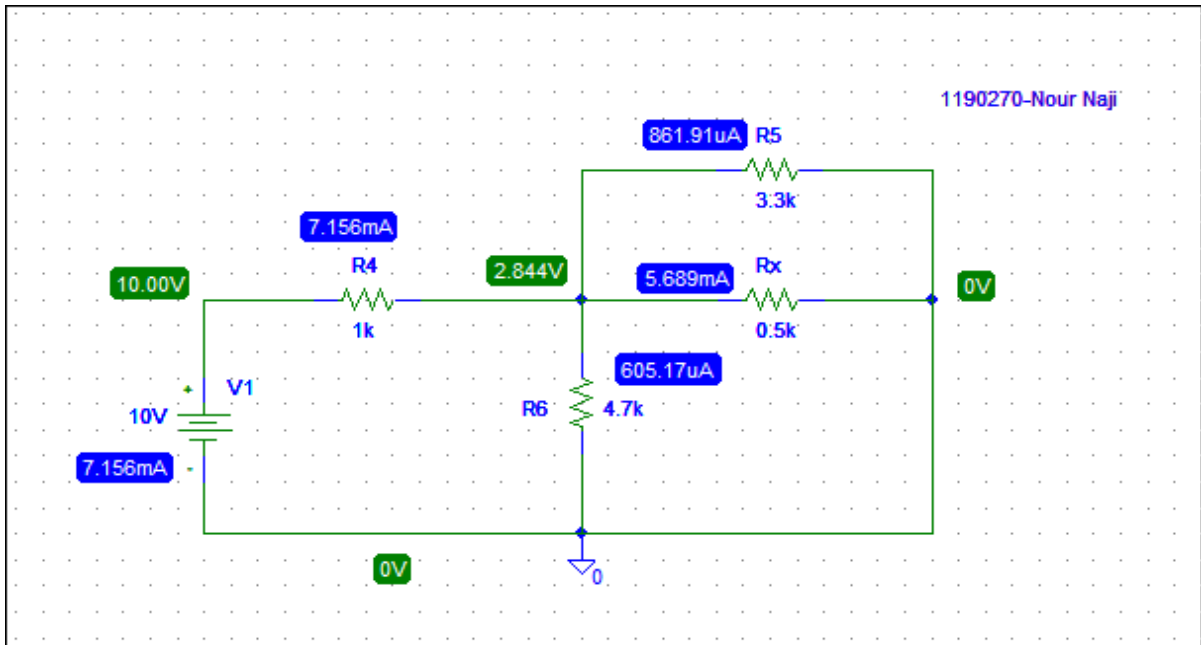


Fig 6 :  $R_x = 0.5 \text{ k}\Omega$

VS (VOLT)	POT	I4	I5	I6	IX
10 V	$R_x$	6.025	1.205	0.845	3.975
10 V	$0.5R_x$	7.156	0.8619	0.60517	5.689

## Part C : Superposition:

- $V_{s1} = 5v, V_{s2} = 10v$

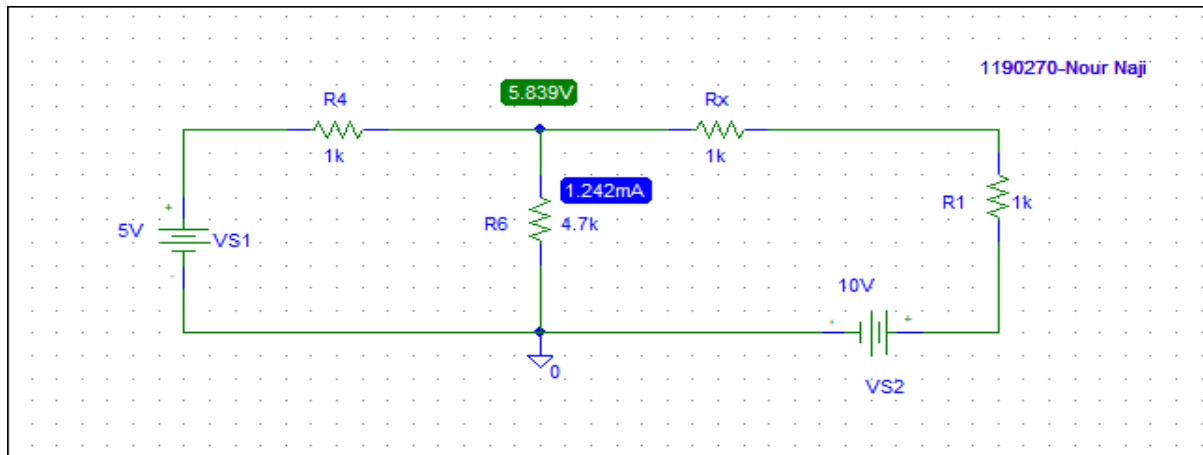


Fig 7 :  $V_{s1} = 5v, V_{s2} = 10v$

- $V_{s1} = 0v, V_{s2} = 10v$

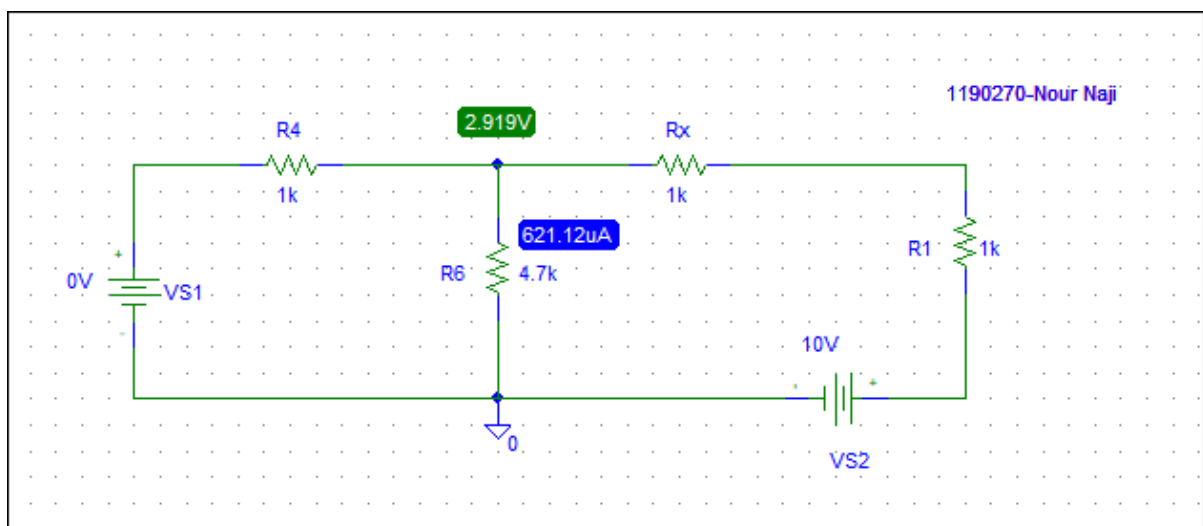


Fig 8 :  $V_{s1} = 0v, V_{s2} = 10v$

- $V_{s1} = 5v, V_{s2} = 0v$

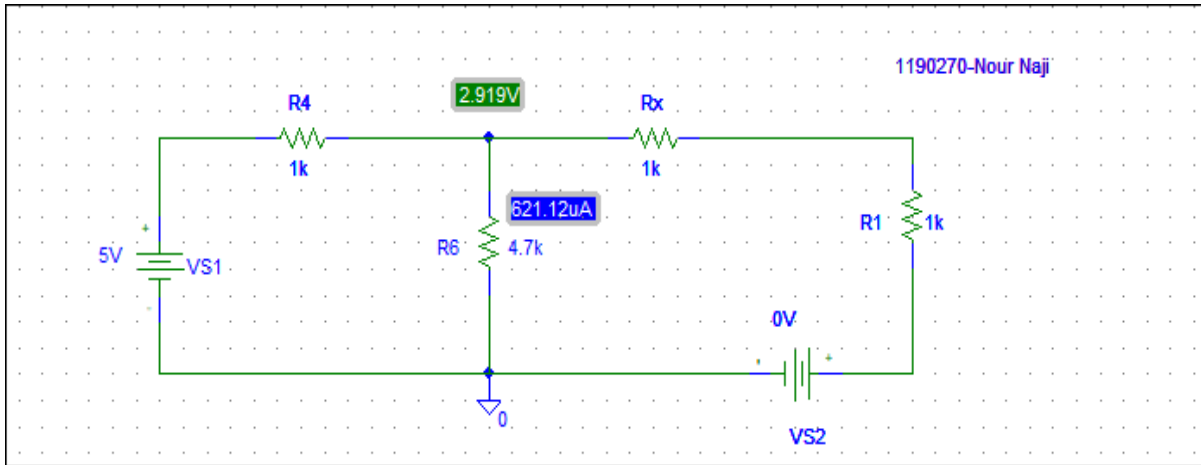


Fig 9 :  $V_{s1} = 5v, V_{s2} = 0v$

$V_{S1}$ (VOLT)	$V_{S2}$ (VOLT)	$V_6$ (VOLT)	$I_6$ (MA)
5	10	8.839	1.242
0	10	2.919	0.62112
5	0	2.919	0.62112

## Part D: Thevenin and Norton equivalent circuits:

2-

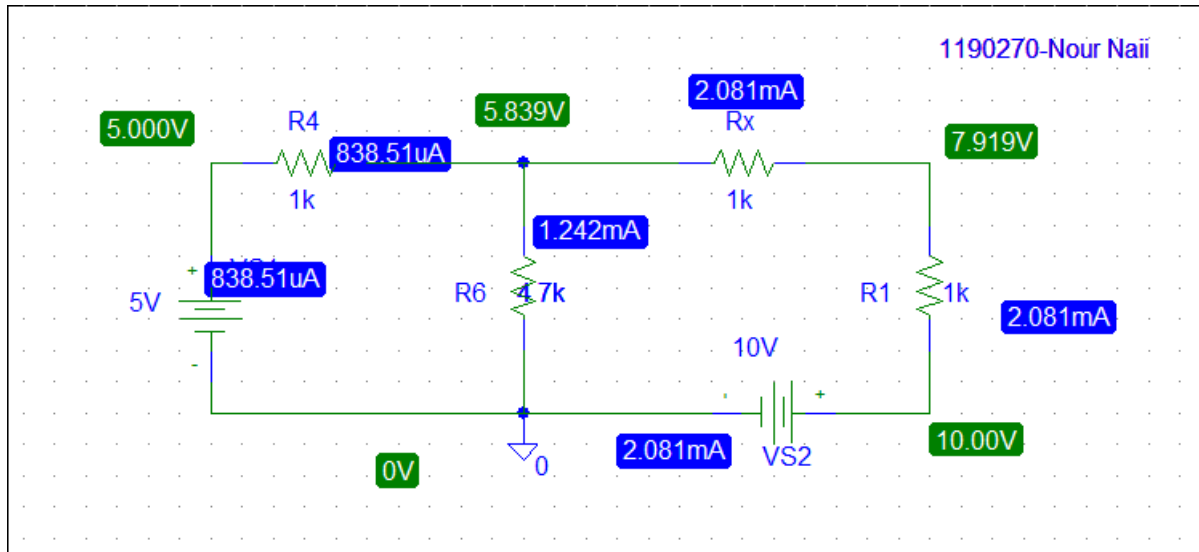


Fig 10

✓  $I_{R_x} = 2.081 \text{ mA}$  ,  $V_{R_x} = (10 - 7.919) / 1 = 2.081 \text{ v}$

3-

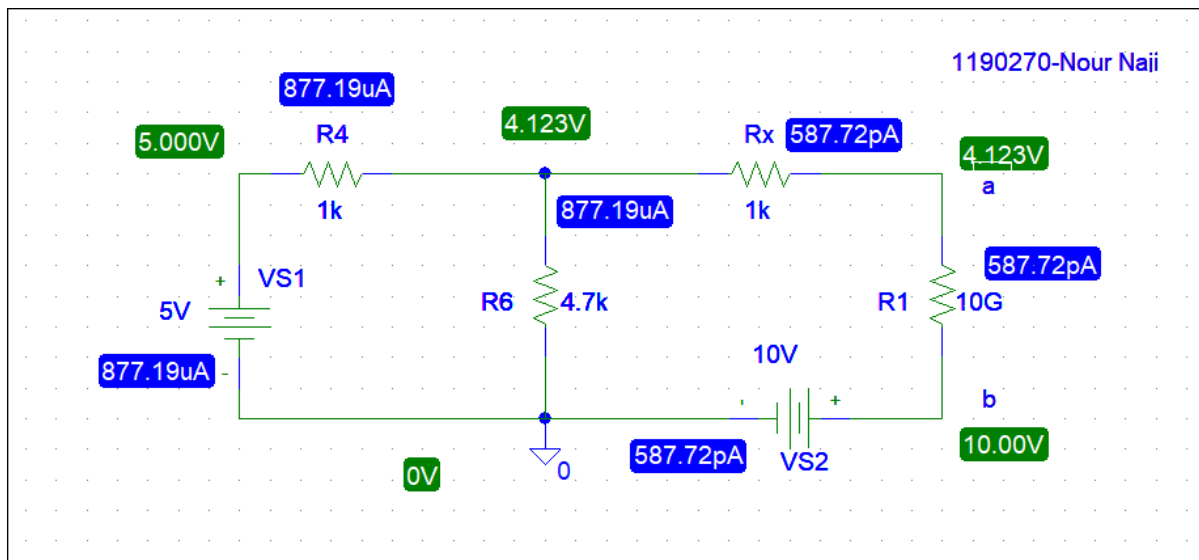


Fig 11

✓  $V_{open} = V(ab) = 4.123 - 10 = -5.877 \text{ v}$



4-

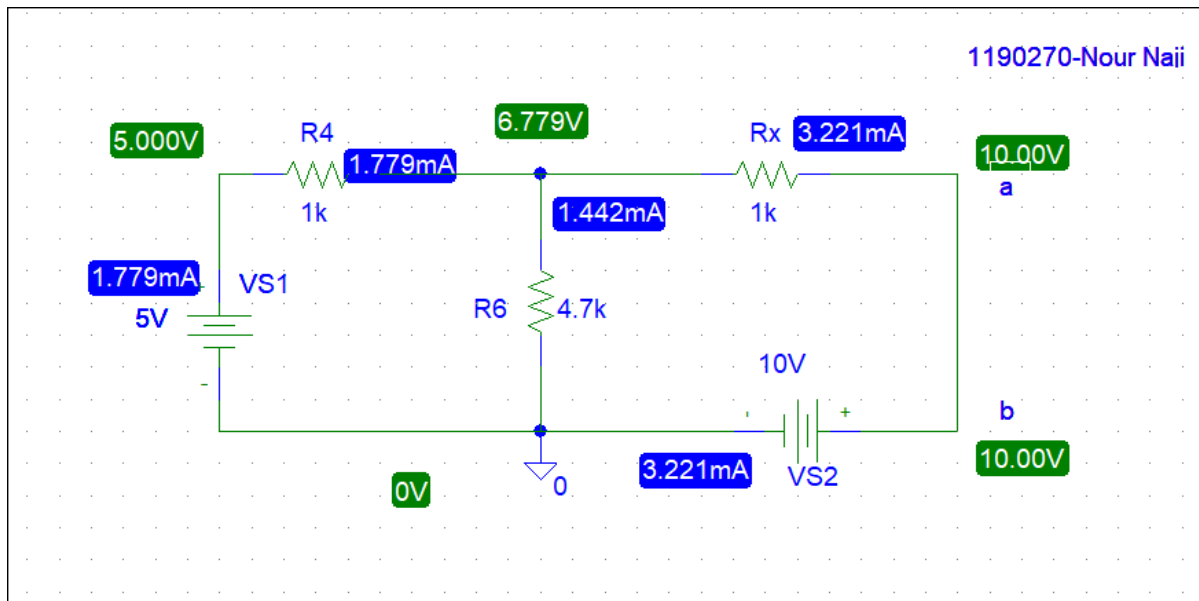


Fig 12

✓  $I_{sc} = 3.221 \text{ mA}$

5-

$$R_{th} = (4.7 // 1) + 1 = 1.824 \text{ k}\Omega$$

7-

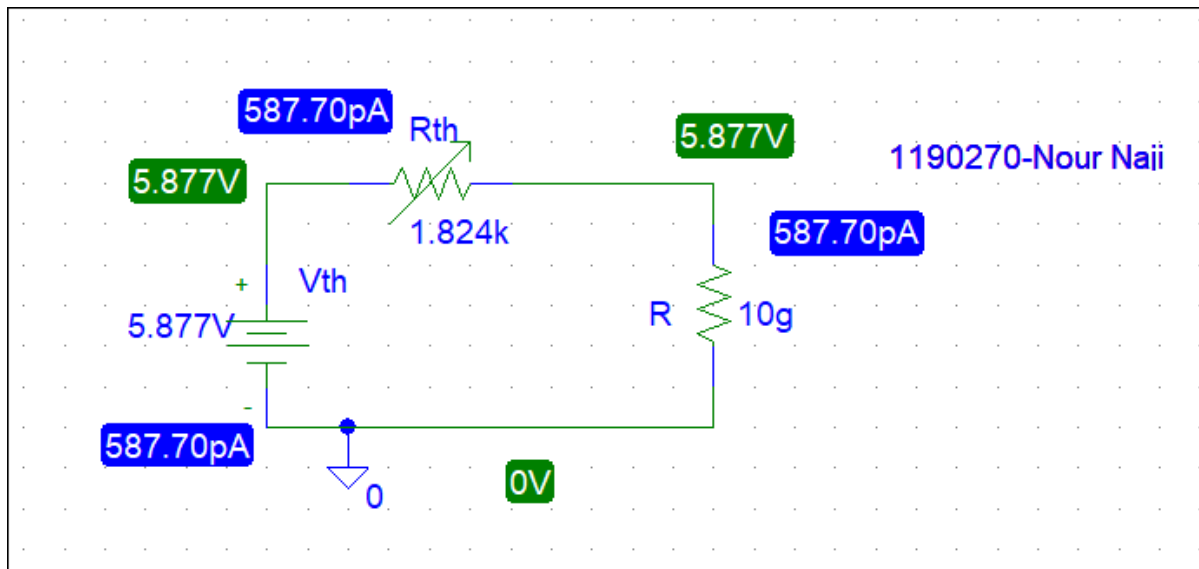


Fig 13

10-

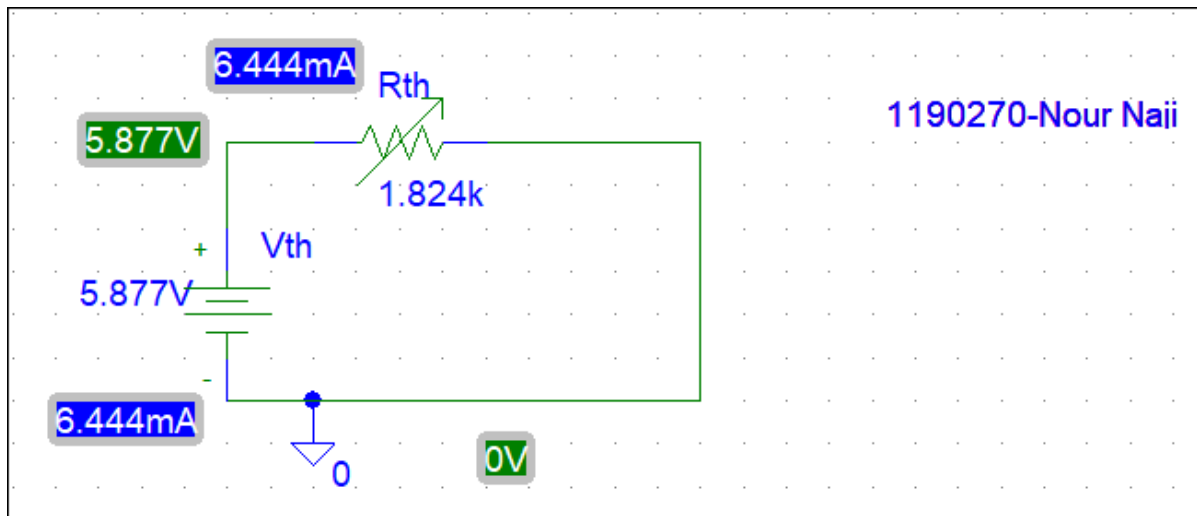


Fig 14

15-

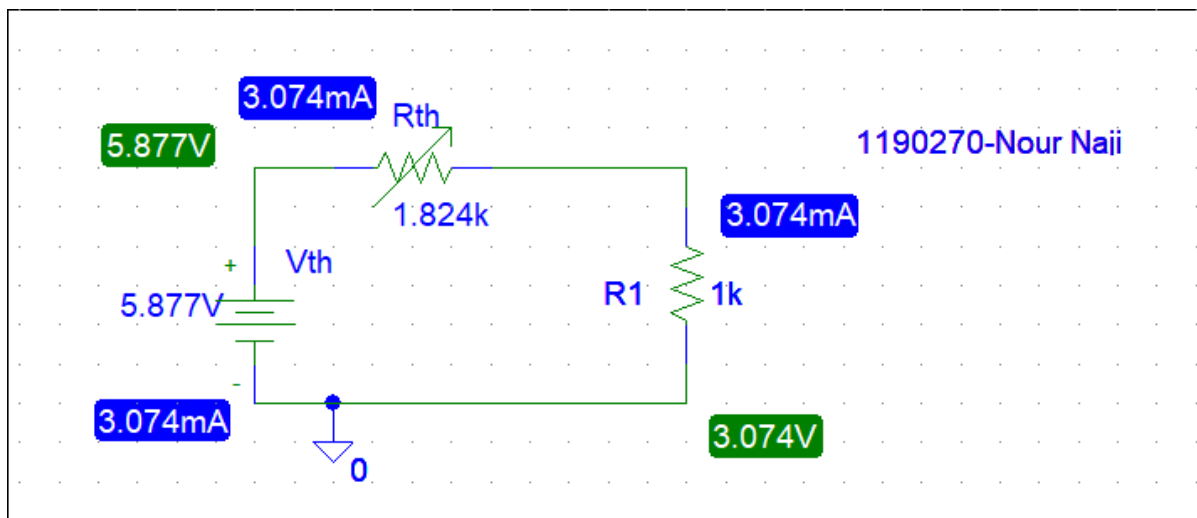


Fig 15