



Faculty of Engineering and Technology  
Department of Electrical and Computer Engineering

ENEE 2103

CIRCUITS AND ELECTRONICS LABORATORY

Experiment #4, Pre-Lab #8

---

Prepared by:

Nour Naji-1190270

Section: 1

Supervised by:

Dr. Alhareth Zyoud

Teaching assistant:

Eng. Ismail Abualia

Date: 29/11/2021

# 1. Part A (Impedance)

## 1.1 Resistive circuit

→ Circuit using PSpice:

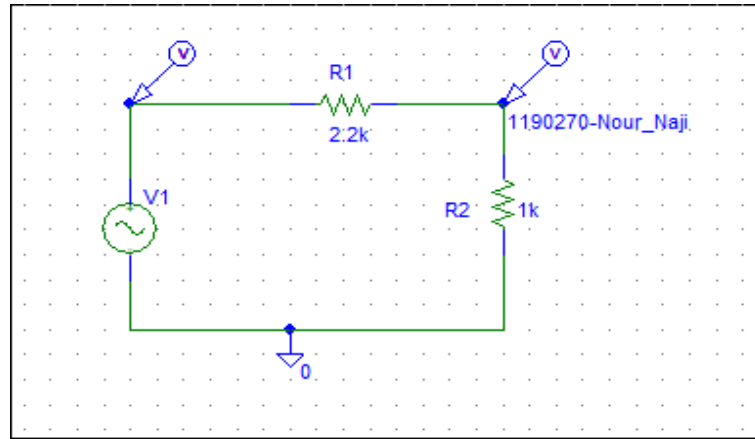


Figure 1. 1

### 1.1.1 Frequency = 1 kHz

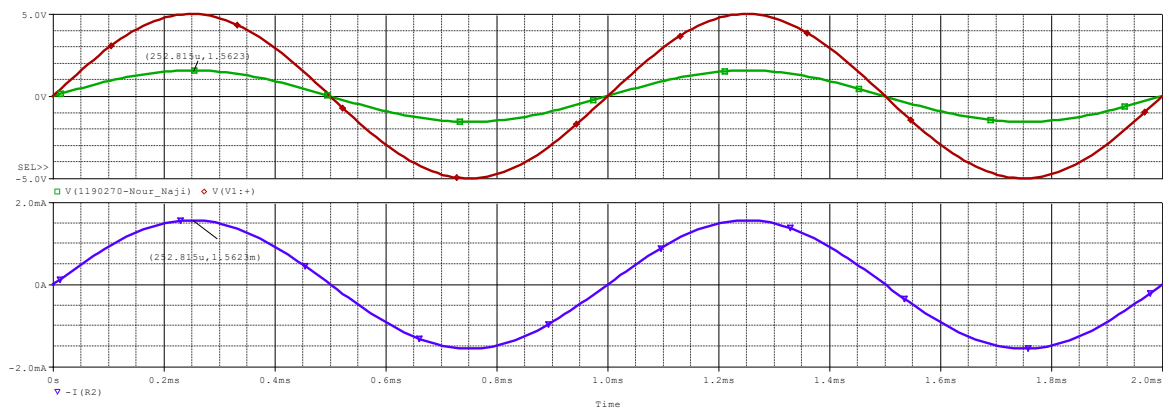


Figure 1. 1.1.1

### 1.1.2 Frequency = 500 Hz

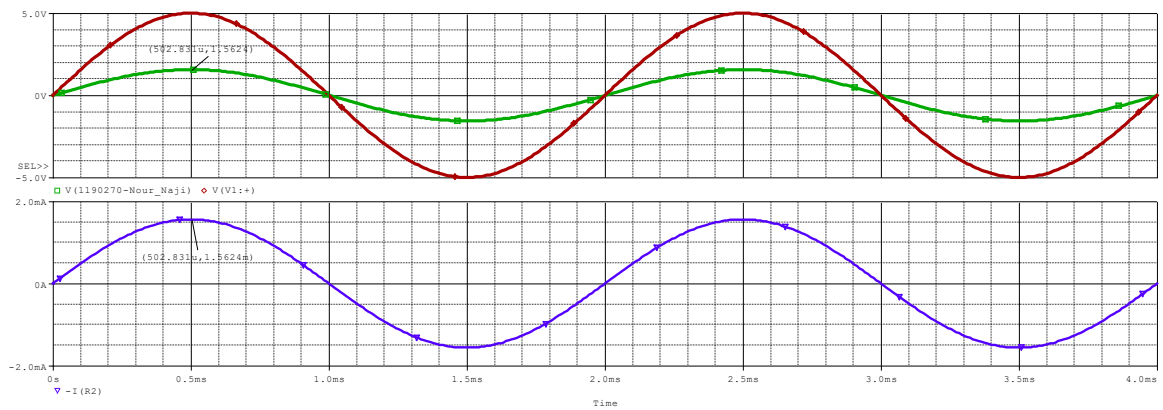


Figure 1. 1.2.1

### 1.1.3 Frequency = 1500 Hz

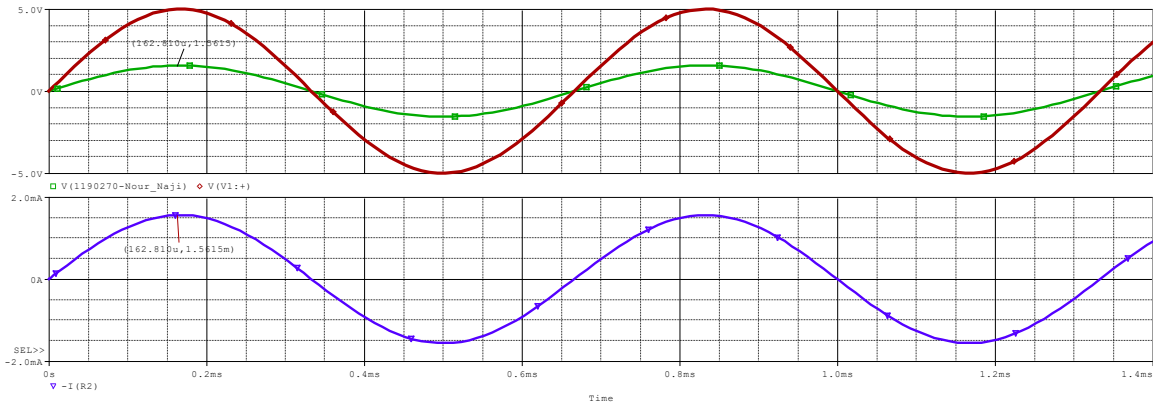


Figure 1. 1.3.1

### 1.1.4 All Frequencies

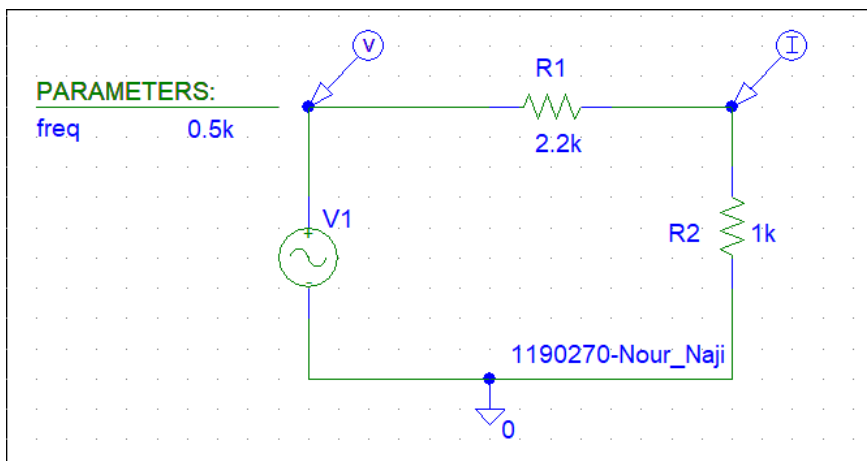


Figure 1. 1.4.1

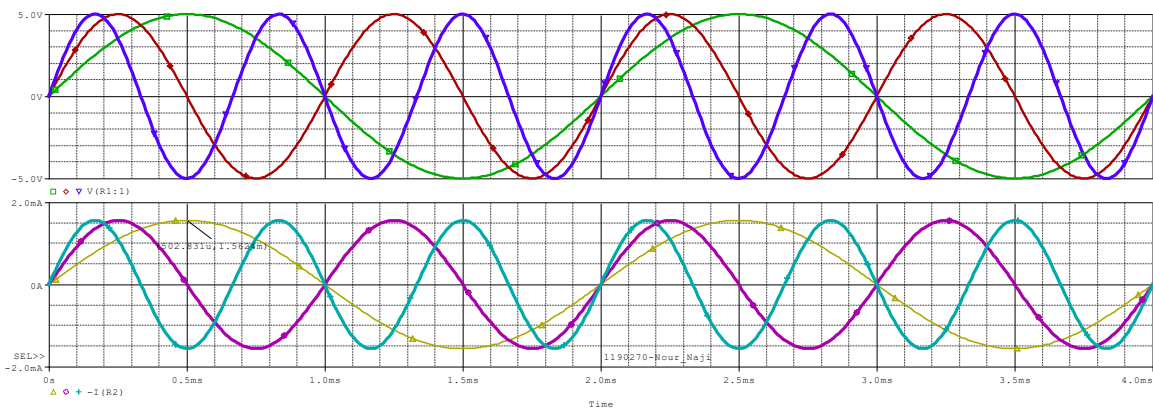


Figure 1. 1.4.2

## 1.2 RC circuit

→ Circuit using PSpice:

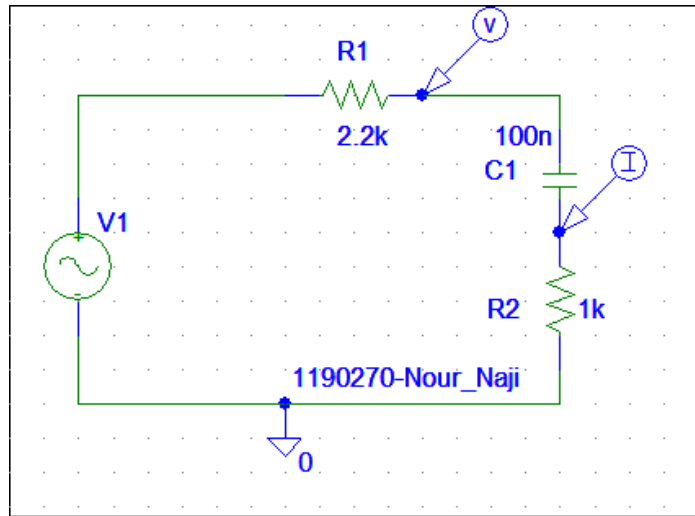


Figure 1. 2.1

### 1.2.1 Frequency = 1000 Hz

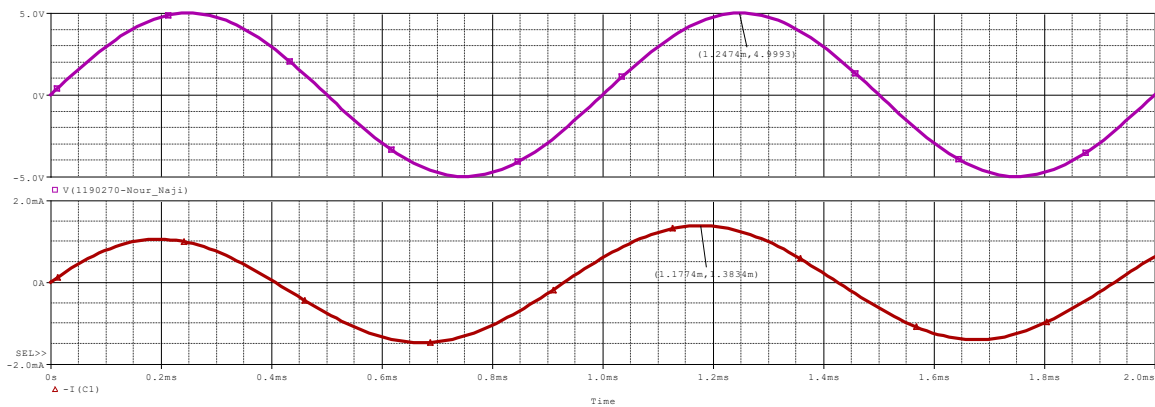


Figure 1. 2.1.1

### 1.2.2 Frequency = 500 Hz

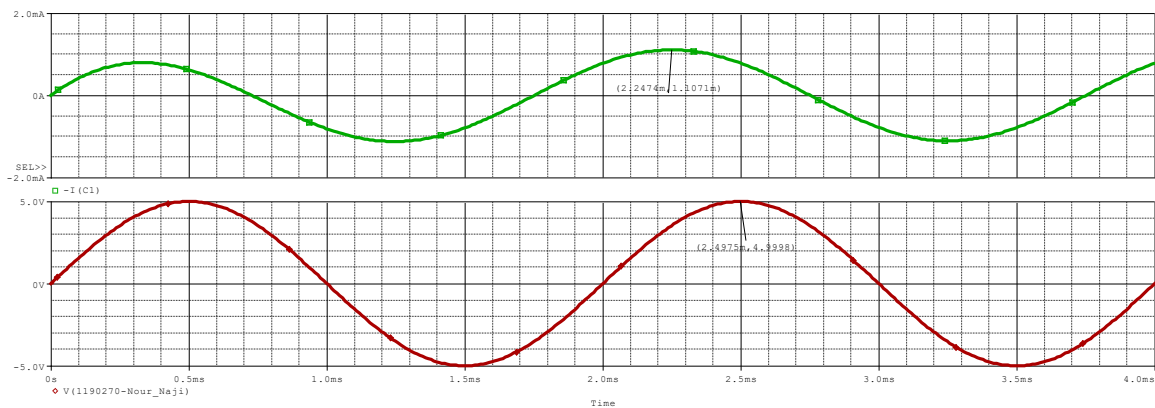


Figure 1. 2.2.1

### 1.2.3 Frequency = 1500 Hz

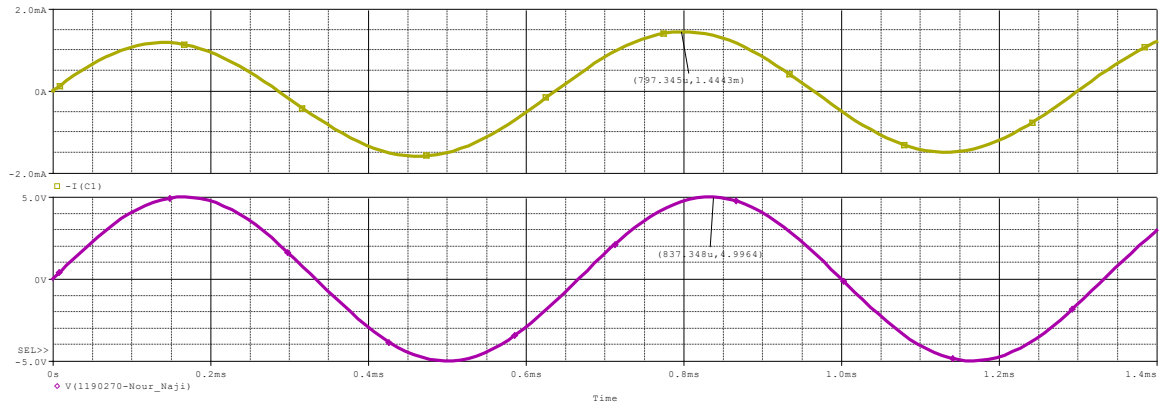


Figure 1. 2.3.1

### 1.2.4 All Frequencies

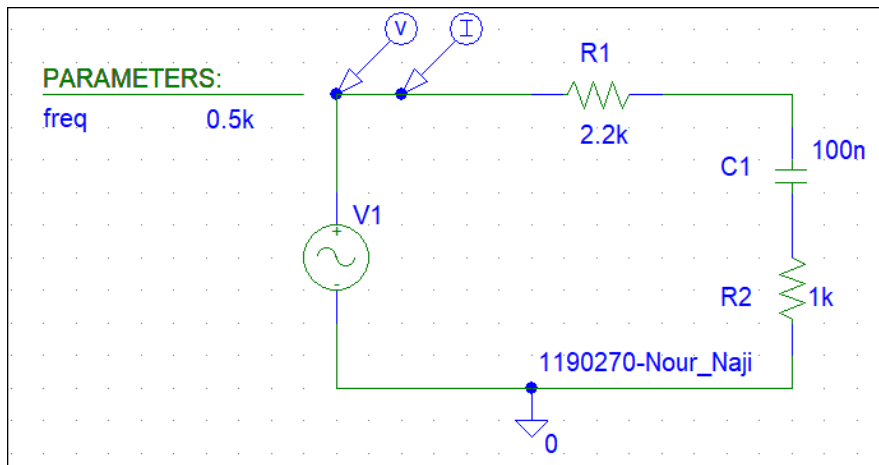


Figure 1. 2.4.1

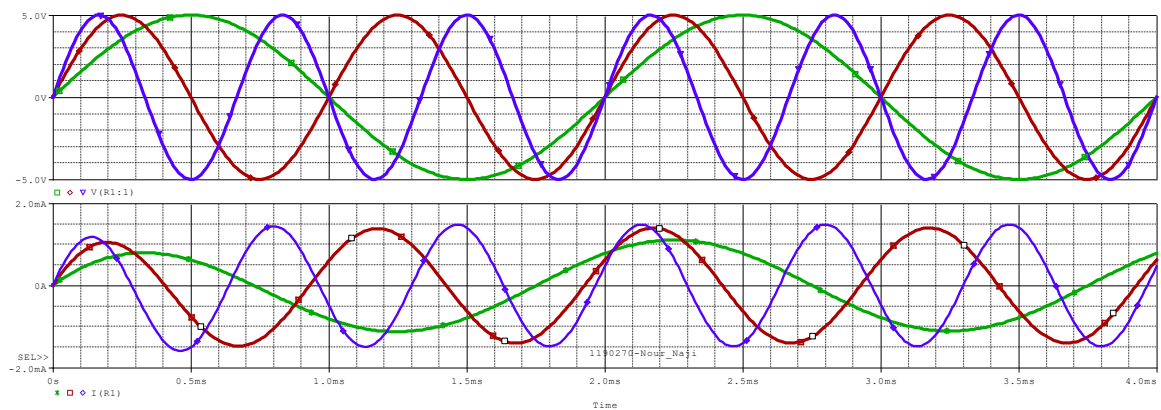


Figure 1. 2.4.2

### 1.3 RL circuit

→ Circuit using PSpice:

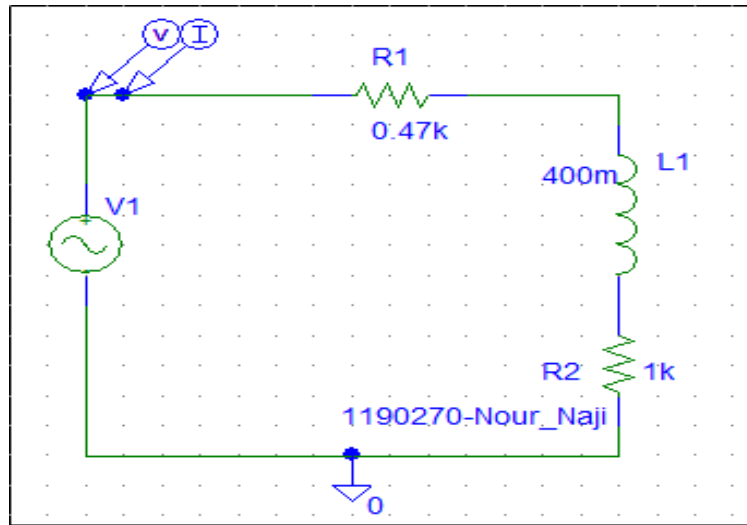


Figure 1. 3.1

#### 1.3.1 Frequency = 1000 Hz

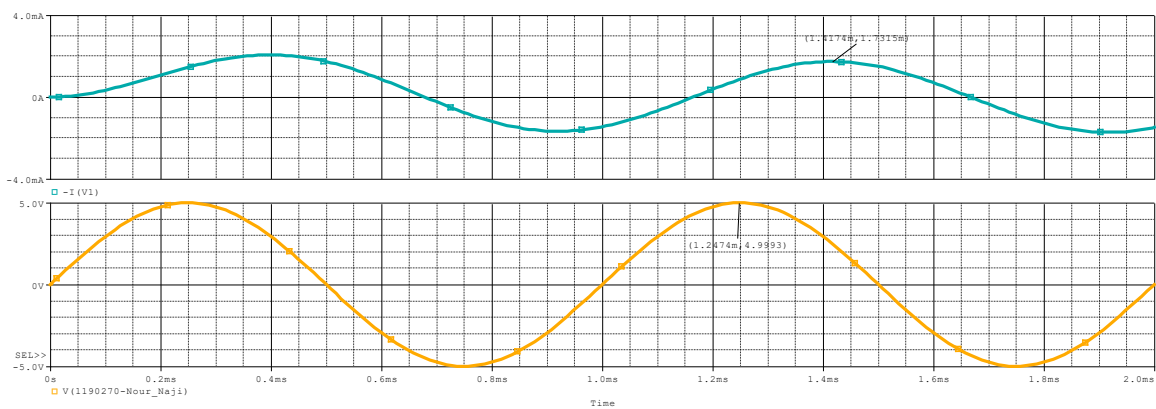


Figure 1. 3.1.1

#### 1.3.2 Frequency = 500 Hz

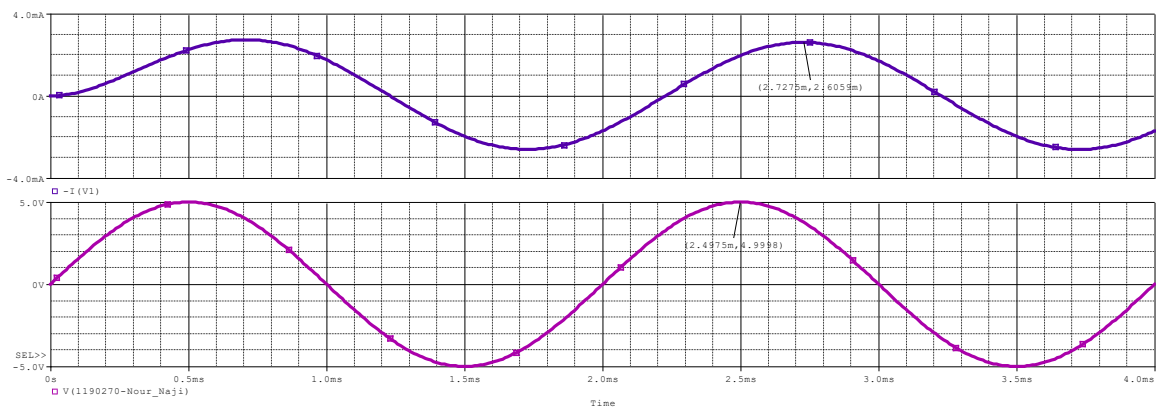


Figure 1. 3.2.1

### 1.3.3 Frequency = 1500 Hz

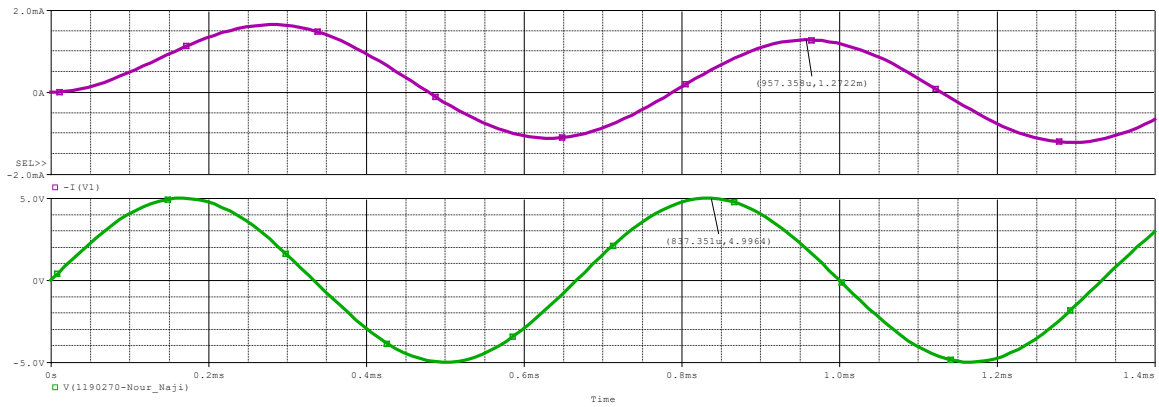


Figure 1. 3.3.1

### 1.3.4 All Frequencies

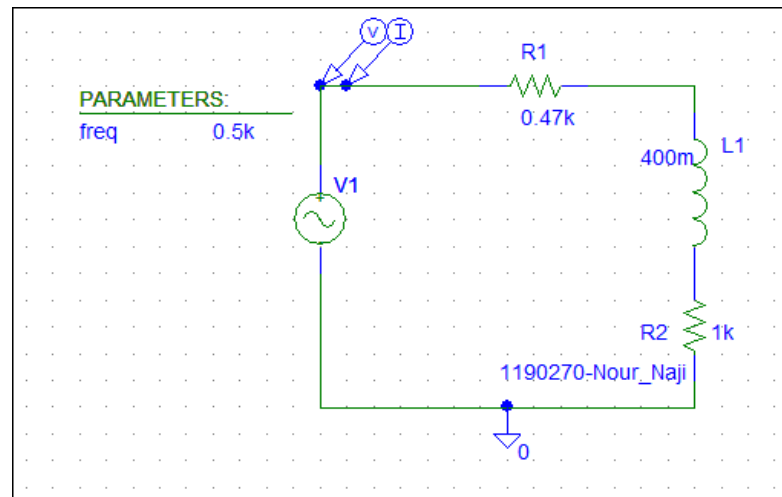


Figure 1. 3.4.1

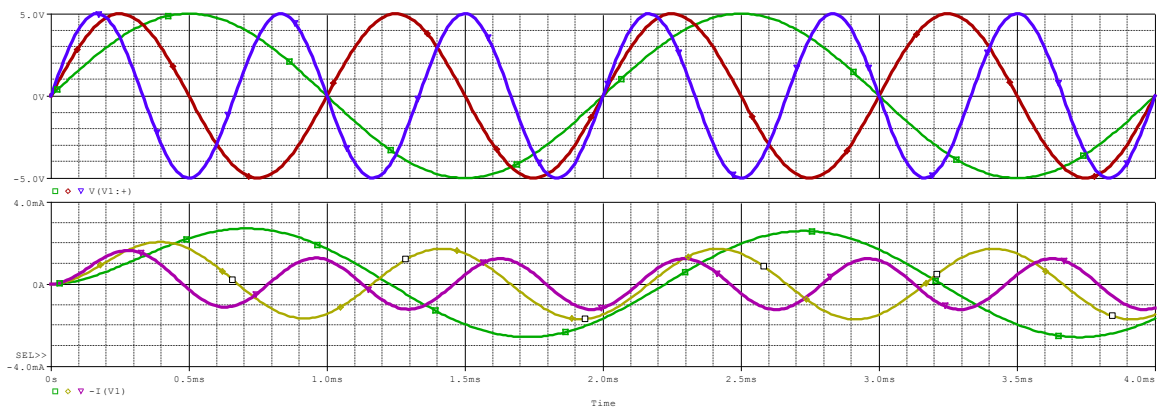


Figure 1. 3.4.2

## 1.4 Capacitive and inductive behavior

➔ Circuit using PSpice:

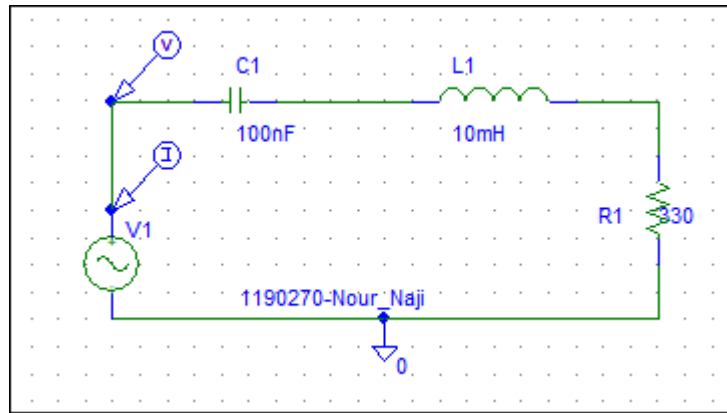


Figure 1. 4.1

➤ F=1KHZ

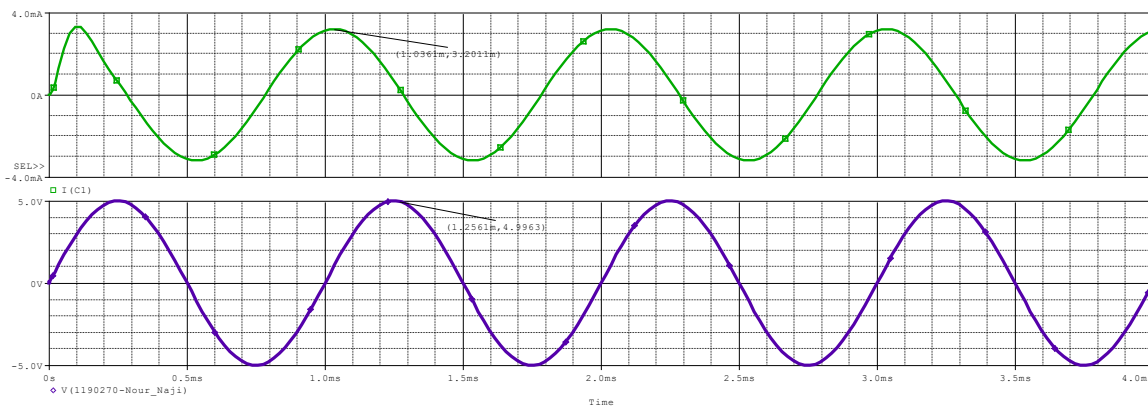


Figure 1. 4.2

➤ F = Fo (Resonance Frequency):

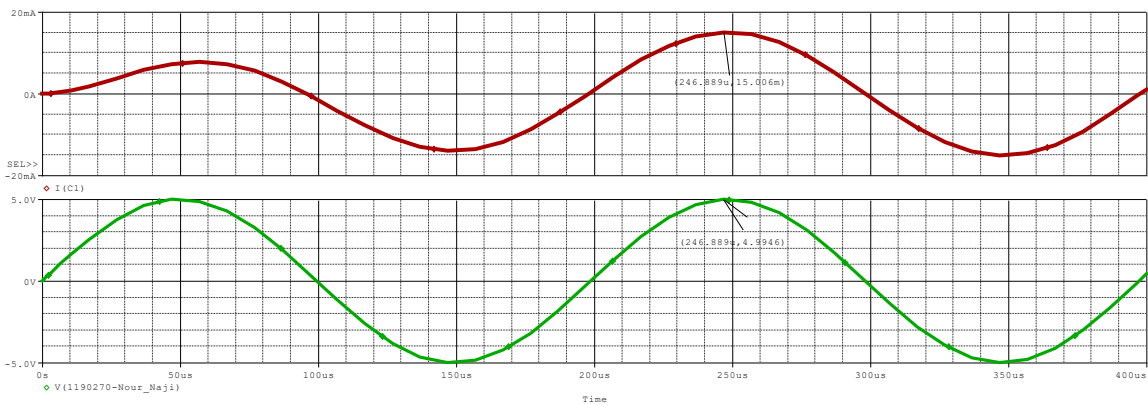


Figure 1. 4.3



$F = 2F_0$

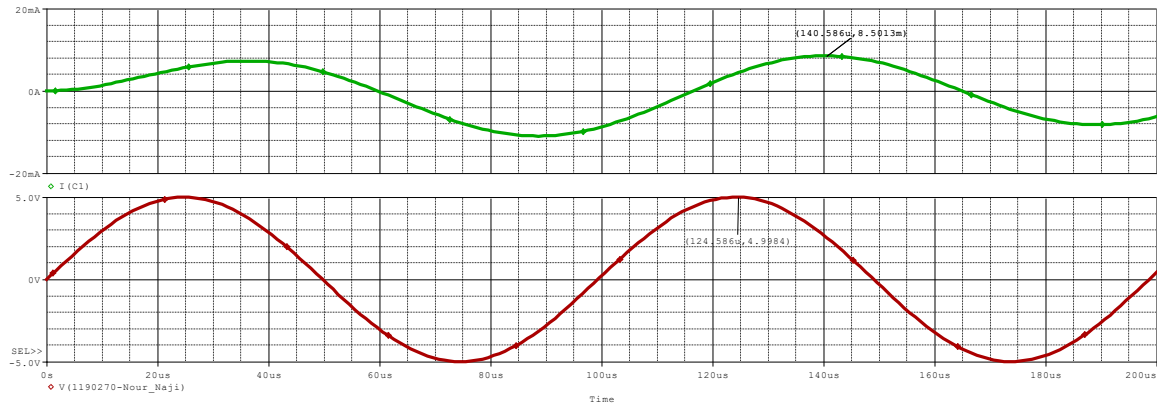


Figure 1. 4..4

1.4.1 Double the value of the capacitor:

→ Circuit using PSpice:

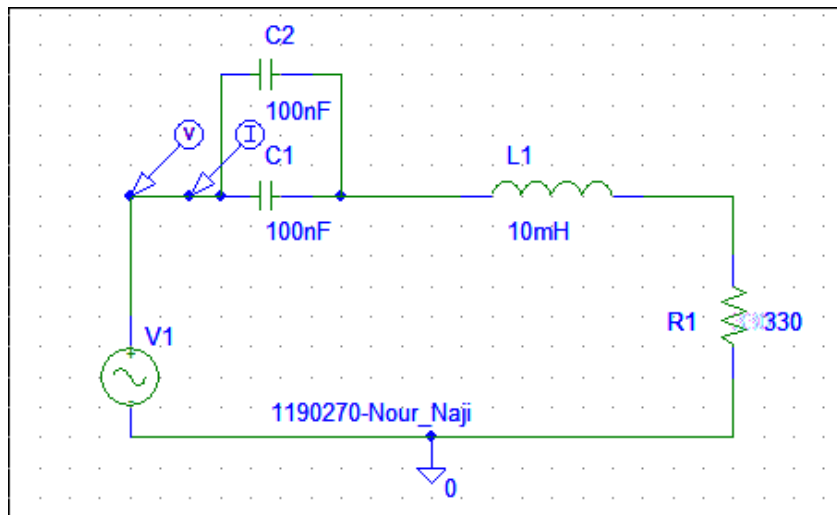


Figure 1. 4.1.1

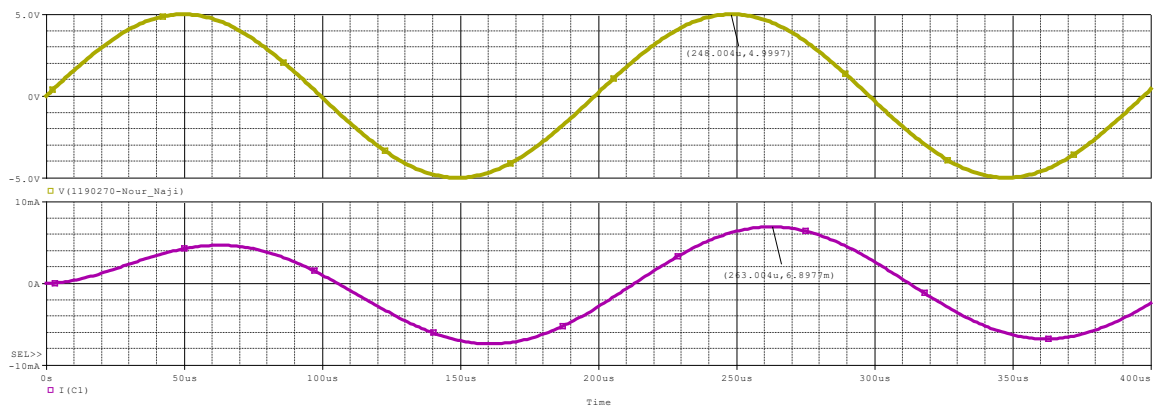


Figure 1. 4.1.2

### 1.4.2 Double the value of the inductor

→ Circuit using PSpice:

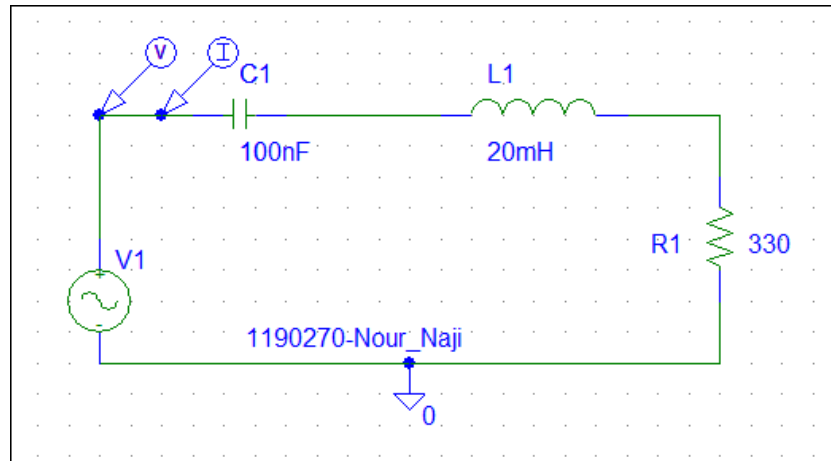


Figure 1. 4.2.1

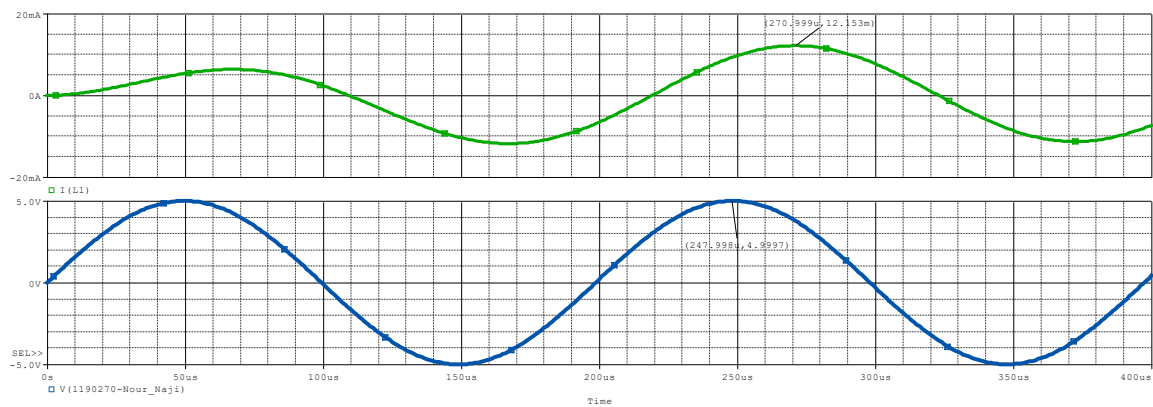


Figure 1. 4.2.2

### 1.5 Sinusoidal steady state power

→ Circuit using PSpice:

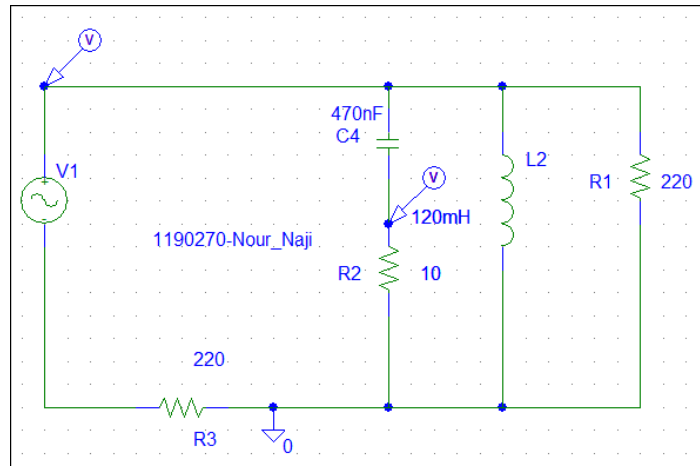


Figure 1. 5.1

Plot the voltage and current across R2

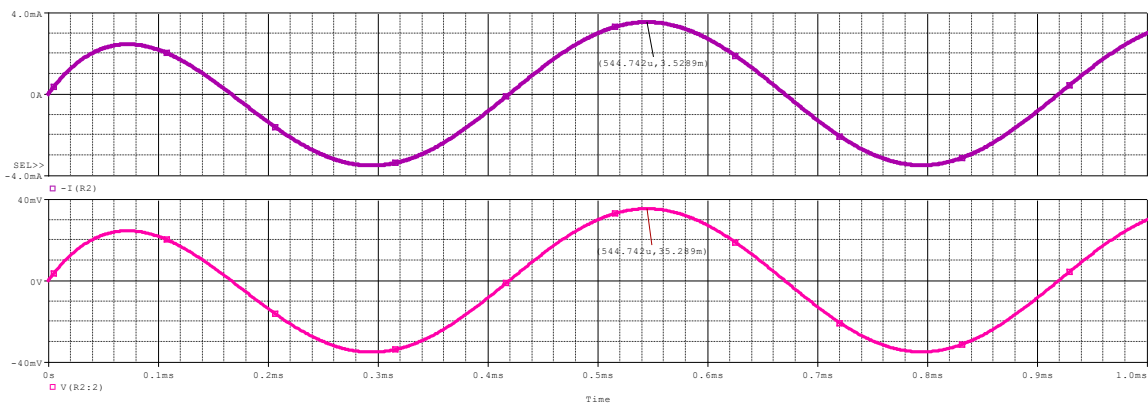


Figure 1. 5.2

Plot Vs and Is and measure phase shift

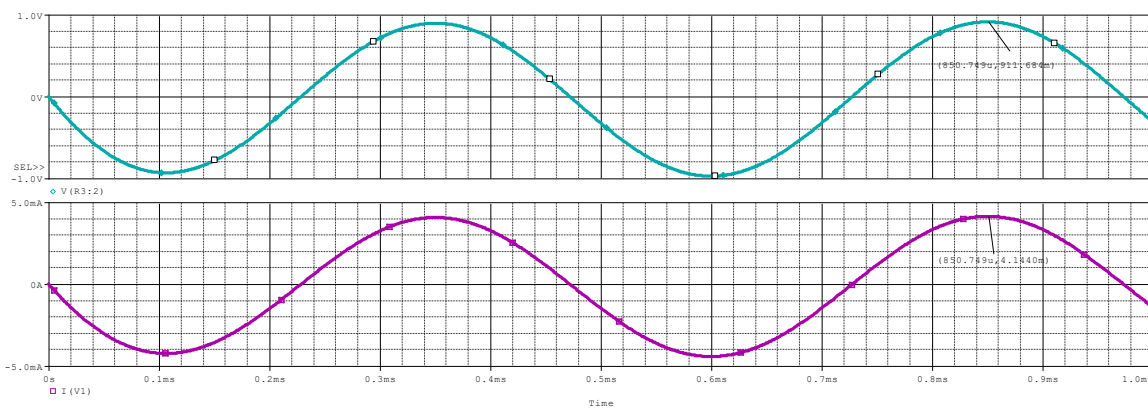


Figure 1. 5.3

Plot  $V_c$  and  $I_c$  and measure phase shift

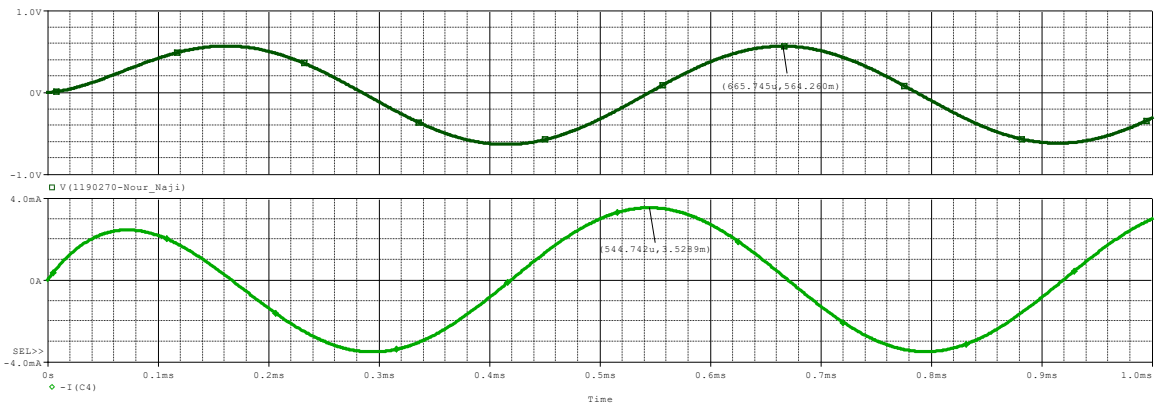


Figure 1. 5.4

Plot  $V_L$  and  $I_L$  and measure phase shift

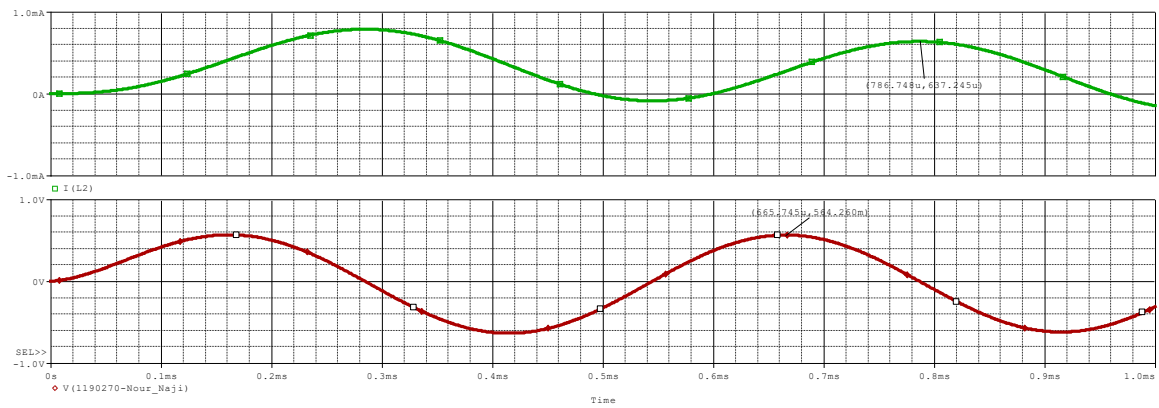


Figure 1. 5.5

Plot voltage across  $R_1$  and  $I_s$  and measure phase shift

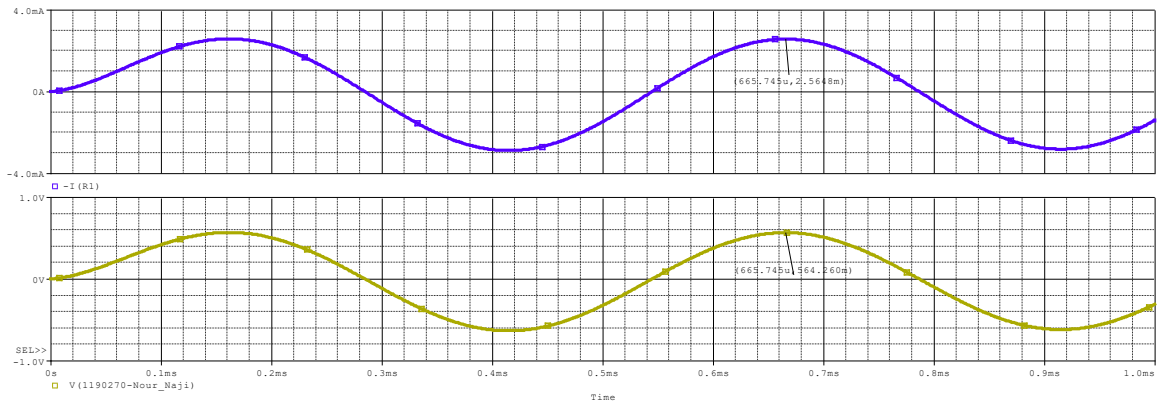


Figure 1. 5.6