

Calculation: =>

part A [Impedance] : =>

- from figure [1.0.1.0.1 → 1.0.3.0.1] ⇒ there are in phase and the impedance are almost the same.

* from graph:

$$- Z = \frac{V_{max}}{I_{max}} = \frac{4.99V}{1.5624mA} = \boxed{3.194k\Omega}$$

$$- \text{phase shift} = \frac{\Delta t}{T} (360) = \boxed{\text{Zero}} \quad \text{since } \Delta t = 0 \text{ in all cases.}$$

* from theory:

$$- Z = R = (2.2k + 1k) = \boxed{3.2k\Omega}$$

$$- I = \frac{V_P}{Z_{in}} = \frac{5}{3.2k} = \boxed{1.5625mA}$$

$$- \text{phase shift} = \tan^{-1} \left(\frac{\text{Imaginary part}}{\text{Real part} = 3.2k} \right) = \boxed{\text{Zero}}$$

RC circuit s=>

from figure (1.2.2.0.1) when $F = 500Hz$

$$- Z = \frac{V_{max}}{I_{max}} = \frac{4.99}{1.1071} = \boxed{4.507k\Omega}$$

$$- \text{phase shift} = \frac{\Delta t}{\text{periodic}} \cdot 360 = \frac{2.2474 - 2.4975}{2m} \cdot 360 = \boxed{-45^\circ}$$

from Theory s=>

$$Z = R_1 + R_2 + \frac{1}{j\pi f_c} = 2.2k + 1k + \frac{1}{j(2\pi)(0.5k)(100n)} \approx 3.2 - j(3.18)k\Omega$$

$$- |Z| = \sqrt{(3.2)^2 + (3.18)^2} = \boxed{4.5113k\Omega}$$

$$- \text{phase shift} = \tan^{-1} \left(\frac{-3.18}{3.2} \right) = \boxed{-44.92 \text{ degree}}$$

- from figure (1.2.1.1) when $F = 1000 \text{ Hz}$

$$Z = \frac{V_{\max}}{I_{\max}} = \frac{4.99 \text{ V}}{1.3834 \text{ mA}} = \boxed{3.604 \text{ k}\Omega}$$

$$\text{phase shift} = \frac{\Delta t}{\text{period}} \cdot 360 = \frac{(1.01774 - 1.2474) \text{ ms} \times 360}{1 \text{ ms}} = \boxed{25.2 \text{ degrees}}$$

* from theory:

$$Z = R_1 + R_2 + \frac{1}{j\pi f C} = 2.2 \text{ k} + 1 \text{ k} + \frac{1}{j(2\pi)(1\text{k})(100\text{n})}$$

$$Z = 3.2 \text{ k} - j(1.592)$$

$$|Z| = \sqrt{(3.2)^2 + (1.592)^2} = \boxed{3.574 \text{ k}\Omega}$$

$$\text{phase shift} = \tan^{-1}\left(\frac{-1.592}{3.2}\right) = \boxed{-26.45 \text{ degrees}}$$

from figure (1.2.3.1) when $F = 1500 \text{ Hz}$

$$Z = \frac{V_{\max}}{I_{\max}} = \frac{4.99}{1.4443} = \boxed{3.454 \text{ k}\Omega}$$

$$\text{phase shift} = \frac{(-837.348 \mu + 797.345 \mu)}{0.6667 \text{ ms}} \times 360 = \boxed{-21.6 \text{ degrees}}$$

* from theory:

$$Z = R_1 + R_2 + \frac{1}{j2\pi f C} = 2.2 + 1 + \frac{1}{j(2\pi)(1.5)(100\text{n})} = 3.2 - j(1.06) \text{ k}\Omega$$

$$|Z| = \sqrt{(3.2)^2 + (1.06)^2} = \boxed{3.37 \text{ k}\Omega}$$

$$\text{phase shift} = \tan^{-1}\left(\frac{-1.06}{3.2}\right) = \boxed{-18.32 \text{ degrees}}$$

- RL Circuit $\beta = 11$

from Figure [1.3.1.1] / $F = 1000 \text{ Hz}$.

$$- Z = \frac{V_{\max}}{I_{\max}} = \frac{4.49 \text{ V}}{1.7315 \text{ m}} = \boxed{2.88 \text{ k}\Omega}$$

$$- \text{phase shift} = \frac{(1.4174 - 1.2474)}{1 \text{ m}} \cdot 360 = \boxed{60.22 \text{ degrees}}$$

from theory:

$$Z = R_1 + R_2 + j2\pi fL$$
$$= 0.47 + 1 + j(2\pi)(1\text{k})(400\text{m}) \approx 1.47 + j(2.514) \text{ k}\Omega$$

$$- |Z| = \sqrt{(1.47)^2 + (2.514)^2} = \boxed{2.912 \text{ k}\Omega}$$

$$- \text{phase shift} = \tan^{-1}\left(\frac{2.514}{1.47}\right) = \boxed{59.68 \text{ degrees}}$$

from Figure [1.3.2.1] / $F = 500 \text{ Hz}$.

$$- Z = \frac{V_{\max}}{I_{\max}} = \frac{4.99}{2.6059} = \boxed{2.3841 \text{ k}\Omega}$$

$$- \text{phase shift} = \frac{(2.7275 - 2.4975)}{2 \text{ m}} \cdot 360 = \boxed{41.4 \text{ degrees}}$$

from theory:

$$Z = R_1 + R_2 + j2\pi fL = 0.47 + 1 + j2\pi(0.5)(400) \approx 1.4 + j(1.257) \text{ k}\Omega$$

$$- |Z| = \sqrt{(1.4)^2 + (1.257)^2} = \boxed{1.934 \text{ k}\Omega}$$

$$- \text{phase shift} = \tan^{-1}\left(\frac{1.257}{1.4}\right) = \boxed{40.5 \text{ degrees}}$$

from figure [1.3.3.1] / $F = 1500 \text{ Hz}$

$$- Z = \frac{V_{\max}}{I_{\max}} = \frac{4.99}{1.2722} = 3.92 \text{ k}\Omega$$

$$- \text{phase shift} = \frac{(957.358 \mu - 837.351 \mu)}{0.6667} \cdot 360 \approx \boxed{64.8 \text{ degrees}}$$

* from theory:

$$Z = 0.47 + 1 + j2\pi(1.5)(400) \approx 1.47 + j(3.77) \text{ k}\Omega$$

$$- |Z| = \sqrt{(1.47)^2 + (3.77)^2} = \boxed{4.046 \text{ k}\Omega}$$

$$- \text{phase shift} = \tan^{-1}\left(\frac{3.77}{1.47}\right) \approx \boxed{68.69 \text{ degrees}}$$

* Capacitive and Inductive behavior! = 1)

from figure [1.4.2] $\phi = 1)$

$$- \text{phase shift} = \frac{(1.0361 - 1.2561)}{1.1} \cdot 360 = \boxed{-79.2 \text{ degrees}}$$

* from theory:

$$X = j2\pi fL + \frac{1}{j2\pi fc} = j(2\pi)(1\text{k})(10\text{m}) + \frac{1}{(2\pi)(1\text{k})(100\text{n})}$$
$$\approx \boxed{-j1528.7}$$

$$\text{phase shift} = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{-1528.7}{330}\right) = \boxed{-77.82}$$

* the current leads voltage by 77.82, so it's capacitive circuit.

from Figure [1.4.3] when $F = F_0$

$$\rightarrow F_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(10m)(100n)}} \approx \boxed{5033 \text{ Hz}}$$

$$\text{phase shift} = \frac{(246.889\mu - 246.889\mu)}{0.1987m} \cdot 360 = \boxed{\text{Zero}}$$

from Theory:

$$X = j2\pi fL + \frac{1}{j2\pi fc} = j2\pi(5.033k)(10m) + \frac{1}{j(2\pi)(5.033)(100n)}$$
$$= \text{Zero}$$

$$\text{phase shift} = \tan^{-1}\left(\frac{0}{330}\right) = \boxed{0 \text{ degree}}$$

* The current and voltage signal are in phase.

when $F = 2f_0$

- From Figure [1.4.4] \Rightarrow

$$\text{phase shift} = \frac{(-124.586\mu + 140.586\mu)}{99.344\mu} \cdot 360 = \boxed{57.98 \text{ degrees}}$$

from theory \Rightarrow

$$X = j2\pi fL + \frac{1}{j2\pi fc} \approx j(474.354)$$

$$\text{phase shift} = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{474.354}{330}\right) = \boxed{55.17 \text{ degrees}}$$

* voltage leads current by 55.17° , So it's an inductive circuit.

Double the value of capacitor $\epsilon=1$

from figure [1.4.1.2] $\epsilon=1$

$$\text{phase shift} = \frac{(263.004\mu - 248.004\mu)}{198.689\mu} \cdot 360 = \boxed{27.178 \text{ degree}}$$

from theory:

$$X = j2\pi fL + \frac{1}{j2\pi fc} = j2\pi(5.033k) + \frac{1}{j2\pi(5.033)(200\mu)}$$

$$= j(158.122)$$

$$\text{phase shift} = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{158.122}{330}\right) = \boxed{25.6 \text{ degree}}$$

Double the value of inductor $\epsilon=1$

from figure [1.4.2.2] $\epsilon=1$

$$\text{phase shift} = \frac{(270.999\mu - 247.998\mu)}{198.689\mu} \cdot 360 = \boxed{41.67 \text{ degree}}$$

from theory $\epsilon=1$

$$X = j2\pi fL + \frac{1}{j2\pi fc} = j2\pi(5.033k) + \frac{1}{j(2\pi)(5.033)(100\mu)}$$

$$= j(316.233)$$

$$\text{phase shift} = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{316.233}{330}\right) = \boxed{43.78^\circ}$$

* Voltage leads the current by 43.78° , so it's an inductive circuit.

Sinusoidal Steady State power 3=1)

$$* V_{RMS} = \frac{V_P}{\sqrt{2}} \Rightarrow \boxed{V_P = 1.412V}$$

from figure 1.5.4 3=1)

$$V_C = 564.260m$$

$$I_C = 3.5289m$$

$$\text{phase shift} = \frac{(544.742 - 665.745)\mu}{0.5m} \cdot 360$$
$$= \boxed{-87.122 \text{ degrees}}$$

$$X = \frac{V_C}{I_C} = \frac{564.260m}{3.5289m} = \frac{1}{2\pi fC} + RI$$

$$\Rightarrow \boxed{C = 6.255\mu F} \quad !$$

from figure 1.5.3 3=1)

$$V_S = 911.68m$$

$$I_S = 4.1440m$$

$$\text{- phase shift} = \frac{(850.749\mu - 850.749\mu)}{0.5m} \cdot 360 = \boxed{\text{Zero}}$$

from figure 1.5.5 \Rightarrow

$$V_L = 564.260 \text{ mV}$$

$$\bar{I}_L = 637.245 \mu$$

$$\text{phase shift} = \frac{(786.748 \mu - 665.745 \mu) \cdot 360}{0.5 \text{ m}} = \boxed{87.122}$$

$$X = \frac{V_L}{\bar{I}_L} = 2\pi L$$

$$\frac{564.260 \text{ m}}{637.245 \mu} = 2\pi L f \Rightarrow \boxed{L = 70.49 \text{ mH}}$$

from figure 1.5.6 \Rightarrow

$$V_{R1} = 564.260 \text{ mV}$$

$$\bar{I}_{R1} = 2.5648 \text{ mA}$$

$$\text{phase shift} = \frac{665.745 - 665.745}{0.5 \text{ m}} \cdot 360 = \text{Zero}$$

$$R = \frac{V_{220\Omega}}{\bar{I}_{R1}} \cong 220 \Omega$$