


Part A (passive filters)

First order Circuit $\epsilon=1$

* from theory $\epsilon=1$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2(3.14)(2.2\text{K})(220\text{n})} = 328.999 \text{ Hz.}$$
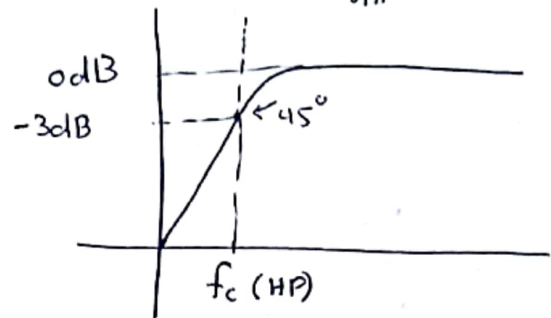
$$\text{Gain} = 20 \log \frac{V_{out}}{V_{in}}$$



* from figure 10.2 $\epsilon=1$


$$f_c = 324.07 \text{ Hz.}$$

\Rightarrow [High pass filter].

* from figure 10.3 $\epsilon=1$

$$f_c = 330.483 \text{ Hz}$$

\Rightarrow [low pass filter].

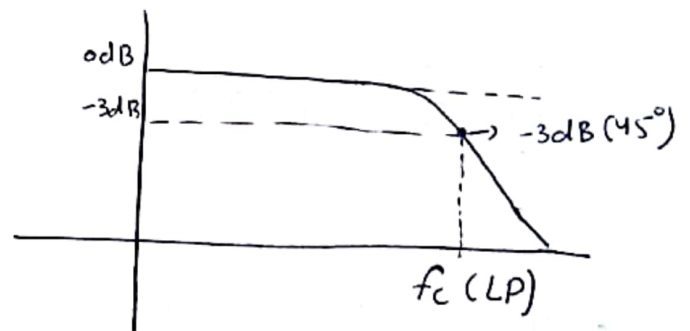

* phase shift from theory $\epsilon=1$

$$f_c = \frac{1}{2\pi RC}$$

$$\Phi_c = -\tan^{-1}(2\pi R C f)$$

$$= -\tan^{-1}(2(3.14)(2.2\text{K})(220\text{n})(328.999))$$

$$= -44.99997 \approx -45^\circ$$

- from figure 10.4 $\epsilon=1$

$$\hookrightarrow \Phi_r \text{ when } f \approx f_c \Rightarrow \Phi = 44.846^\circ$$

$$\hookrightarrow \Phi_c \text{ when } f \approx f_c \Rightarrow \Phi = -45.154^\circ$$

Second Order Circuit $\zeta=1$

- from theory $\zeta=1$

$$f_c = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2(3.14)\sqrt{(100\text{mH})(470\text{n})}} = 734.499\text{ Hz}$$

$$\hookrightarrow 2\pi f_c = \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \pm \frac{R}{2L}$$

$$\Rightarrow \boxed{f = \frac{1}{2\pi} \left(\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \mp \frac{R}{2L} \right)}$$

$$\hookrightarrow f_L = \frac{1}{2\pi} \left(\sqrt{\left(\frac{1\text{K}}{2(100\text{m})}\right)^2 + \frac{1}{(100\text{m})(470\text{n})}} - \frac{1\text{K}}{2(100\text{m})} \right) = 287.05\text{ Hz}$$

$$\hookrightarrow f_H = 1879.4\text{ Hz}$$

- from figure 1.6 $\zeta=1$

from Green graph:

$$\hookrightarrow f_c = 726.752\text{ Hz}$$

$$\hookrightarrow f_L = 288.121\text{ Hz}$$


$$\hookrightarrow f_H = 1.909\text{ KHz}$$

from Red graph $\zeta=1$

$$\hookrightarrow f_L = 288.121\text{ Hz}$$

$$\hookrightarrow f_H = 1.909\text{ KHz}$$

\Rightarrow Band Pass filter.

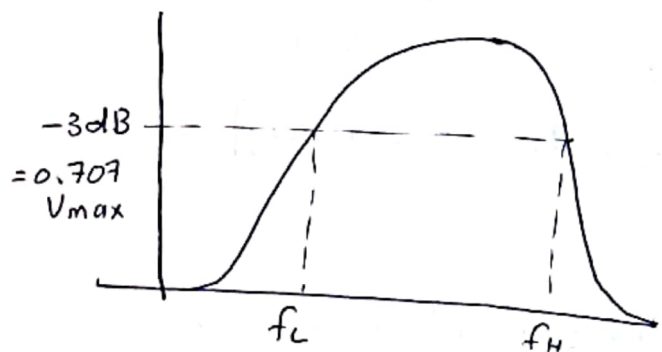

* phase shift from theory $\delta=1$.

$$\Phi_c = -\tan^{-1} \left[\frac{\frac{1}{LC} - (2\pi f_c)^2}{2\pi f_c R/L} \right]$$

$$\Phi_c \text{ [when } f = f_c = 734.499] \cong 0 \text{ degree}$$

$$\Phi_c \text{ [when } f_c = 288.121] \cong -45 \text{ degree}$$

$$\Phi_c \text{ [when } f_c = 1.909 \text{ K}] = 45 \text{ degree}$$

from figure 107 $\delta=1$

* from Green graph $\delta=1$

$$\Phi \text{ when } f = f_c = 533.691 \cong 0 \text{ degree}$$

$$\Phi \text{ when } f = f_L = 44.865 \text{ degree}$$

$$\Phi \text{ when } f = f_H = -45.842 \text{ degree}$$

* from Red graph $\delta=1$

$$\Phi \text{ when } f = f_L = -45.522 \text{ degree}$$

$$\Phi \text{ when } f = f_H = 45.693 \text{ degree}$$

Part B (Active filters) $\delta=1$

- from theory $\delta=1$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2(3.14)(2.2k)(220n)} = 328.99 \text{ Hz.}$$

$$\Phi_c = -\tan^{-1}(2\pi f_c RC) \cong -45 \text{ degree.}$$

- from figure 1.11 $\delta=1$

$$f_c = 329.405 \text{ Hz [low pass filter]}$$

$$\Phi_{\text{when } f=f_c} = 135^\circ = -45^\circ \text{ in } \tan \Phi.$$

