



Faculty of Engineering and Technology  
Department of Electrical and Computer Engineering

ENEE 2103

CIRCUITS AND ELECTRONICS LABORATORY

Experiment #7, Pre-Lab #3

“ BJT Transistor As An Amplifier, CE, CC, CB Connection”

---

Prepared by:

Nour Naji-1190270

Section: 1

Supervised by:

Dr. Alhareth Zyoud

Teaching assistant:

Eng. Esmail Abualia

Date: 4/10/2021

---

# Table of Contents

- 1. COMMON EMITTER TRANSISTOR AMPLIFIER ..... 1
- 2. COMMON COLLECTER TRANSISTOR AMPLIFIER) ..... 4

# 1. COMMON EMITTER TRANSISTOR AMPLIFIER

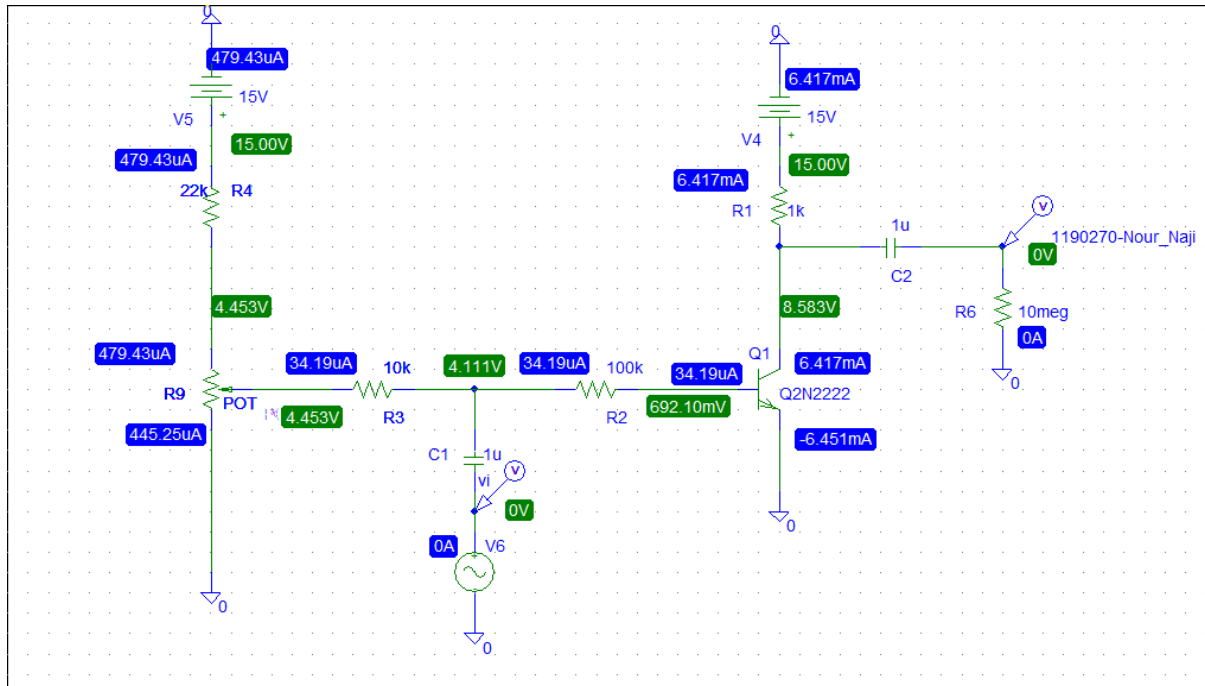



Figure 1-1:COMMON EMITTER TRANSISTOR AMPLIFIER

❖ Dc values:

- $V_C = 8.583 \text{ v}$
- $V_{BE} = 692.10 \text{ mv}$
- $V_{CE} = V_C - V_E = 8.583 - 0 = 8.583 \text{ v}$
- $I_C = 6.417 \text{ mA}$
- $I_B = 34.19 \text{ mA}$


❖ Adjust amplitude of  $V_i(t)$  to 1 V and measure  $V_o(t)$

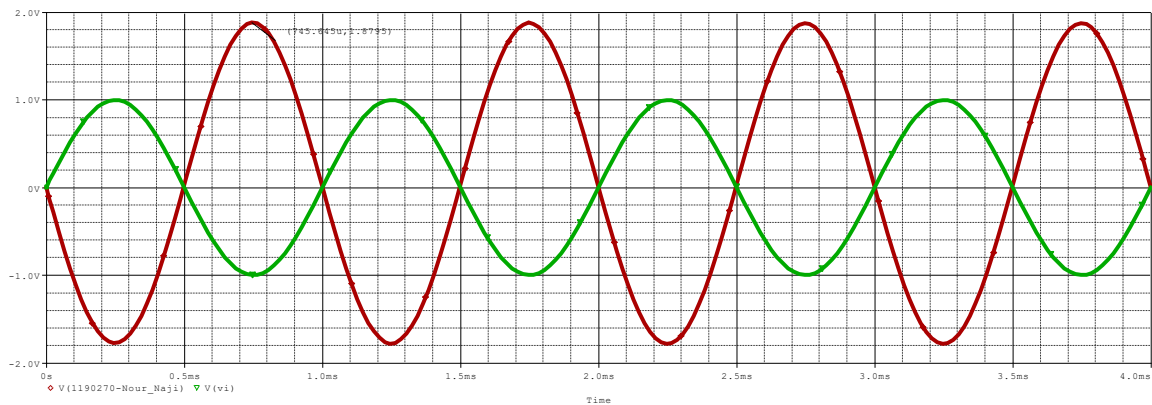Peak value of  $V_o(t) = 1.8795 \text{ v}$




❖ Change peak of  $V_i(t)$  such that  $V_o(t) = 4V$  peak and perform Transient analysis.

- Peak value of  $V_i(t) = 2.1492$  v.

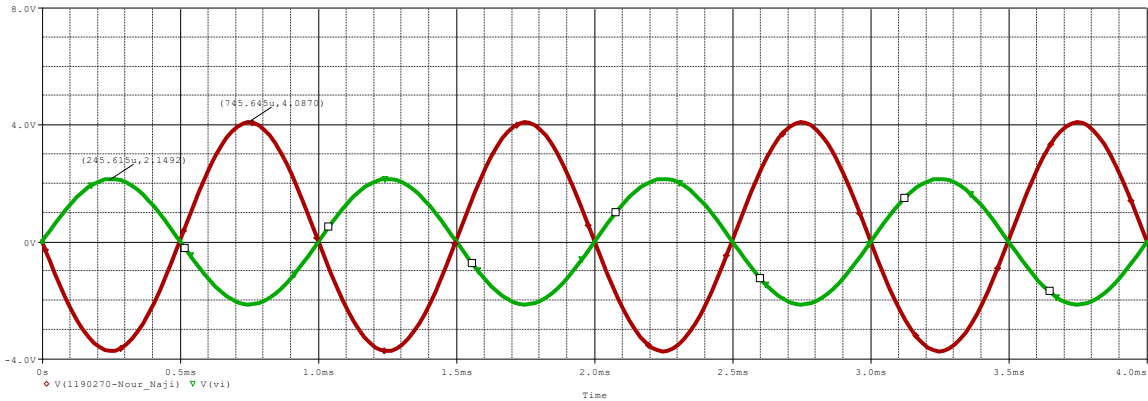


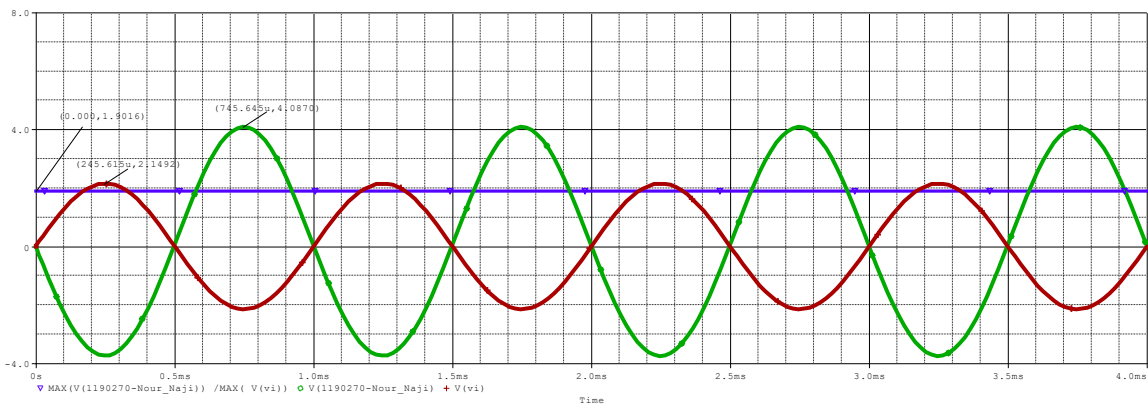❖ Calculate the voltage gain of the transistor  $A_v = \frac{v_o(t)}{v_i(t)}$




- $A_v$  (experimentally)  $= \frac{v_o(t)}{v_i(t)} = 1.9$
- $A_v$  (theoretically)  $= \frac{v_o(t)}{v_i(t)} = \frac{4}{2.15} = 1.86$

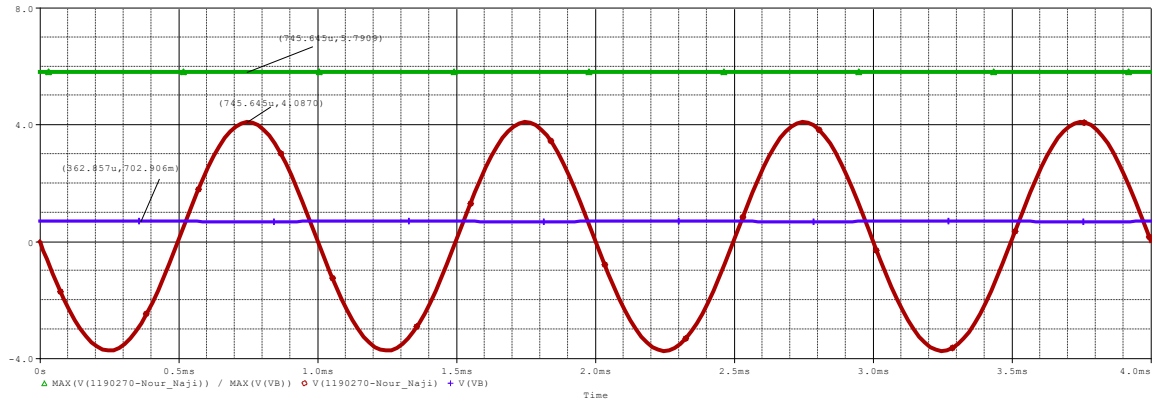❖ Calculate the voltage gain of the transistor  $A_{v1} = \frac{v_o(t)}{v_B(t)}$




- $A_v$  (experimentally) =  $\frac{v_o(t)}{v_B(t)} = 5.7909$
- $A_v$  (theoretically) =  $\frac{v_o(t)}{v_B(t)} = \frac{4}{692.10 \text{ mV}} = 5.779$

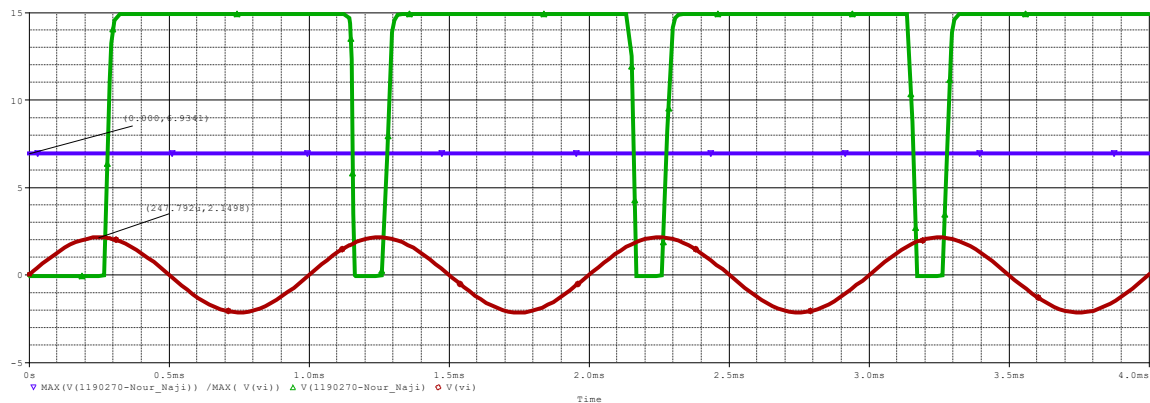❖ Remove the 100k resistor and see what happens to voltage gain?



✓ We can see from the figure above that the voltage gain will increase dramatically  
 ⇒  $A_v = 6.9341$
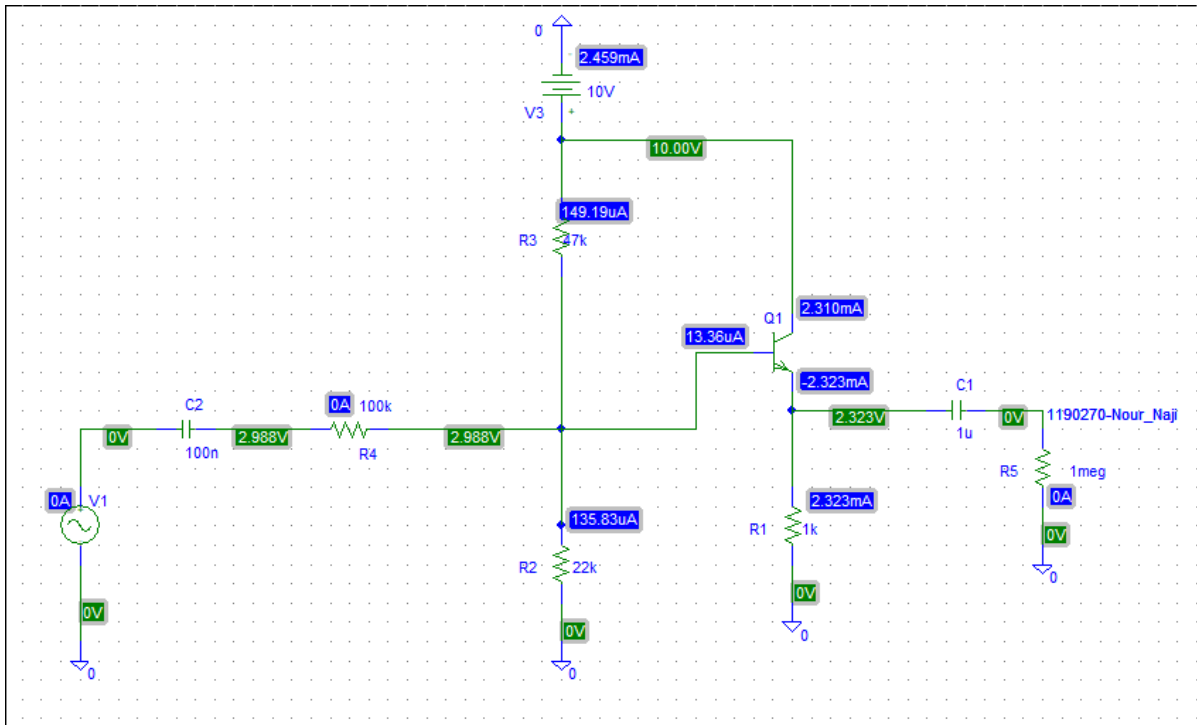
## 2. COMMON COLLECTER TRANSISTOR AMPLIFIER)




❖ Dc values:


- $V_B = 2.988 \text{ v}$
- $V_C = 10 \text{ v}$
- $I_B = 13.36 \mu\text{A}$
- $I_C = 2.310 \text{ mA}$

❖ Adjust the amplitude of the sine wave generator until an output amplitude from the amplifier is about 2 volts peak-to-peak. (Make sure the waveform is undistorted).

- Amplitude of  $V_i(t) = 8.3\text{v}$

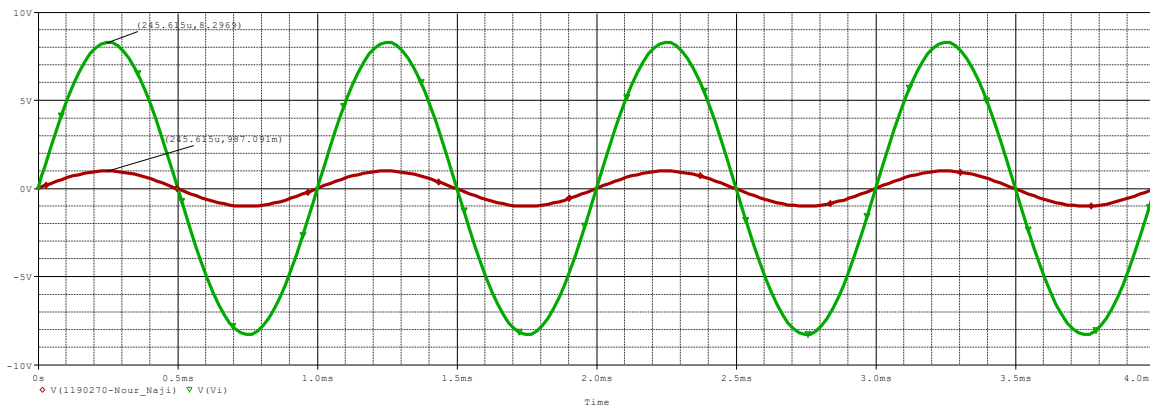


### ❖ Calculate the voltage gain $A_v$

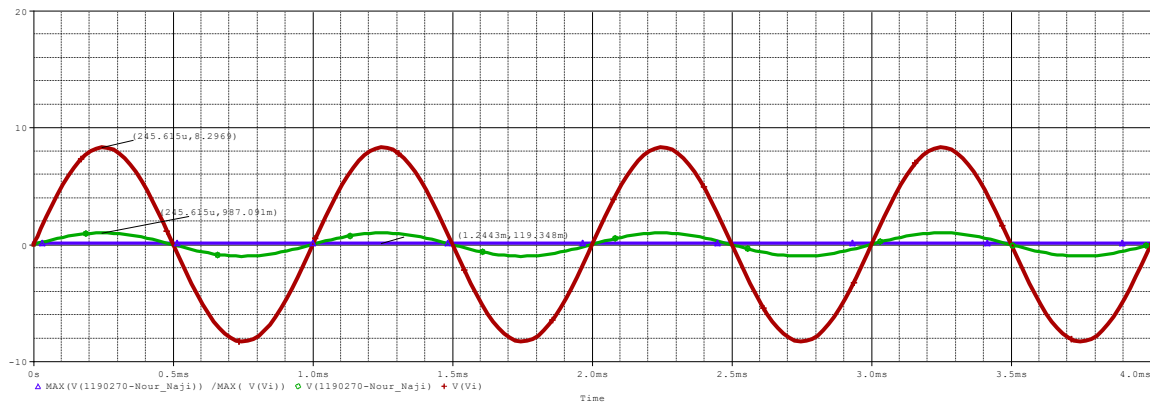

$$\blacksquare A_v = \frac{v_o(t)}{v_i(t)} = 0.119348$$
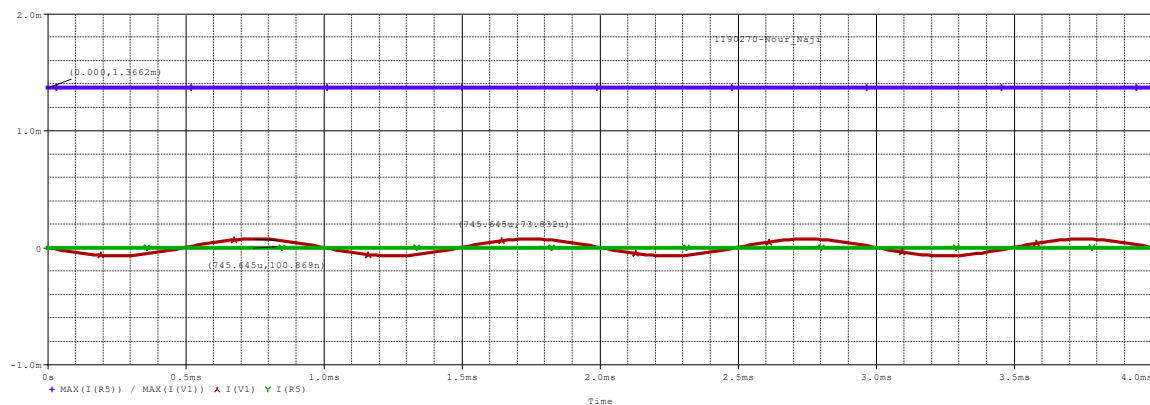
### ❖ Measure the input and output currents and calculate $A_i$




$$\blacksquare A_i = \frac{I_o(t)}{I_i(t)} = \frac{100.869n}{73.832u} = 1.3662m$$

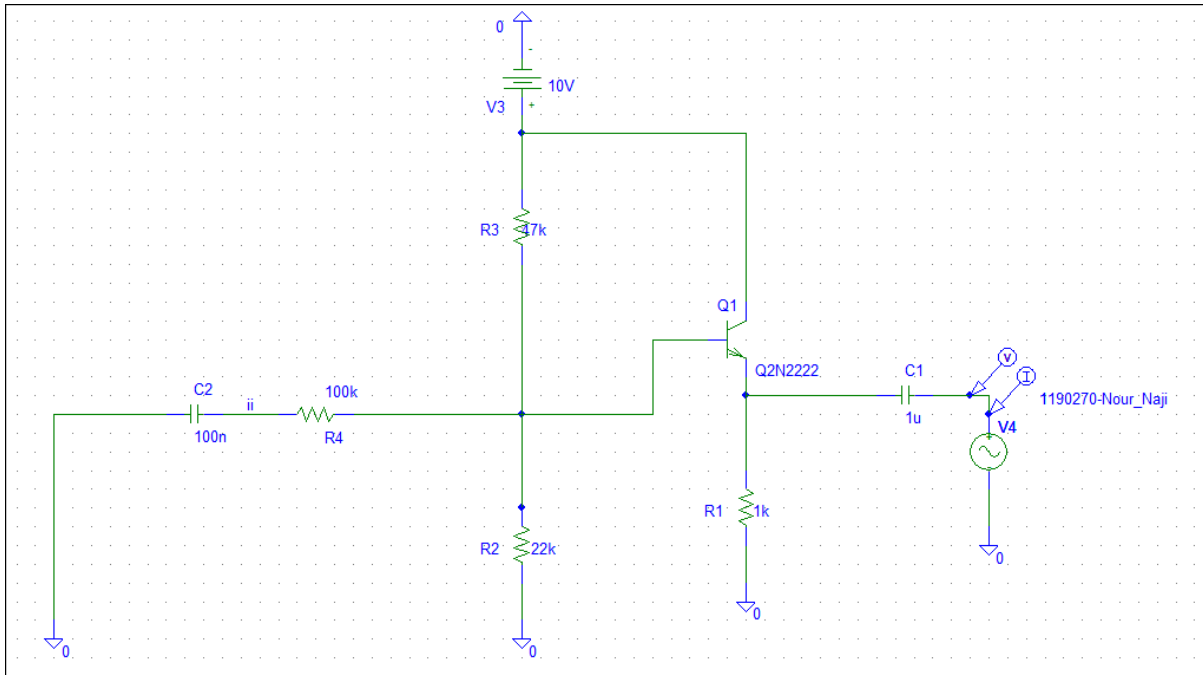
### ❖ Estimate $Z_i$ from $I_i$ and $V_i$ values

$$\blacksquare Z_i = \frac{V_i}{I_i} = \frac{8.3}{73.832 u} = 112417.38 \Omega$$

- ❖ To find the output impedance of the amplifier, you should take off the input sine wave generator and replace it with a short circuit, then you have to connect the generator to the output (emitter) via a capacitor, and measure its output voltage and current.



❖ Iout & Vout

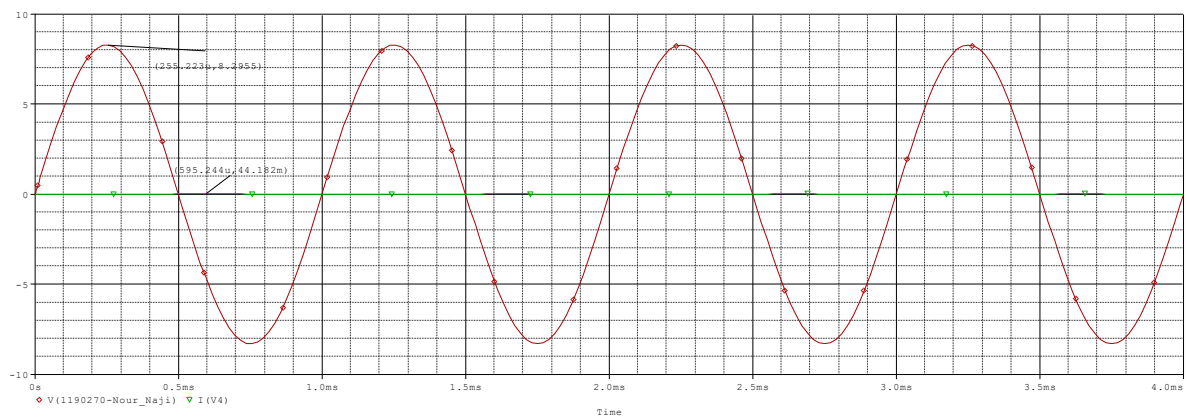

▪  $Z_{out} = \frac{V_{out}}{I_{out}} = \frac{8.2955}{44.182m} = 187.757\Omega$



QUANTITY	MEASURED VALUES
$V_{IN}$	8.3 v
$V_{OUT}$	987.091
$I_{IN}$	73.832u
$I_{OUT}$	100.869n
	<b>Calculated values</b>
$A_V = V_{OUT}/V_{IN}$	0.119348
$A_I = I_{OUT}/I_{IN}$	1.3662m
$Z_{IN} = V_{IN}/I_{IN}$	112417.38 $\Omega$
$Z_{OUT}$	187.757 $\Omega$