



Faculty of Engineering and Technology
Department of Electrical and Computer Engineering

ENEE 2103

CIRCUITS AND ELECTRONICS LABORATORY

Experiment #9, Pre-Lab #5

"Multistage Amplifier and Frequency Response"

Prepared by:

Nour Naji-1190270

Section: 1

Supervised by:

Dr. Alhareth Zyoud

Teaching assistant:


Eng. Esmail Abualia

Date: 25/10/20


Table of Contents

1.First Amplifier stage	1
2.Second Amplifier stage.....	3
3.Connect the two stages together:	5
4.Compare the dc bias voltages and currents obtained in 1,2 and 3:	7
5.Compare A_v (obtained in 3) with product $A_{v1} * A_{v2}$ (obtained in 1 and 2):	8
6.For the two stage Amplifier, perform ac sweep and show the frequency response in dB for frequency range 10Hz-10MHz	9
7.Based on F , estimate f_L and f_H (the cutoff frequencies at low and high frequencies)	10

1. First Amplifier stage

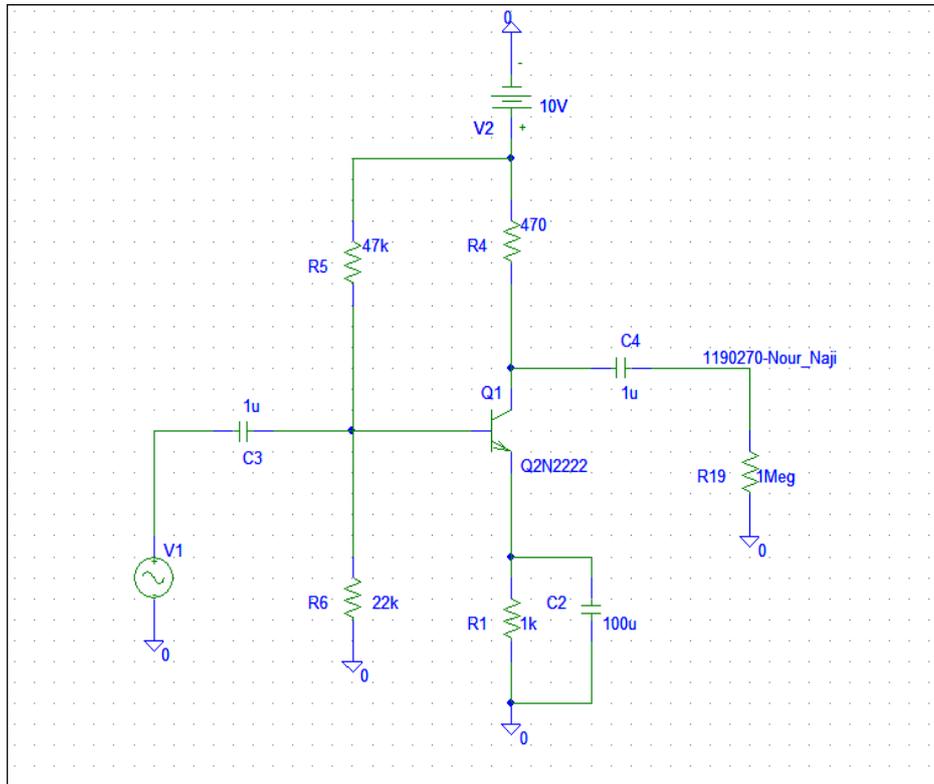


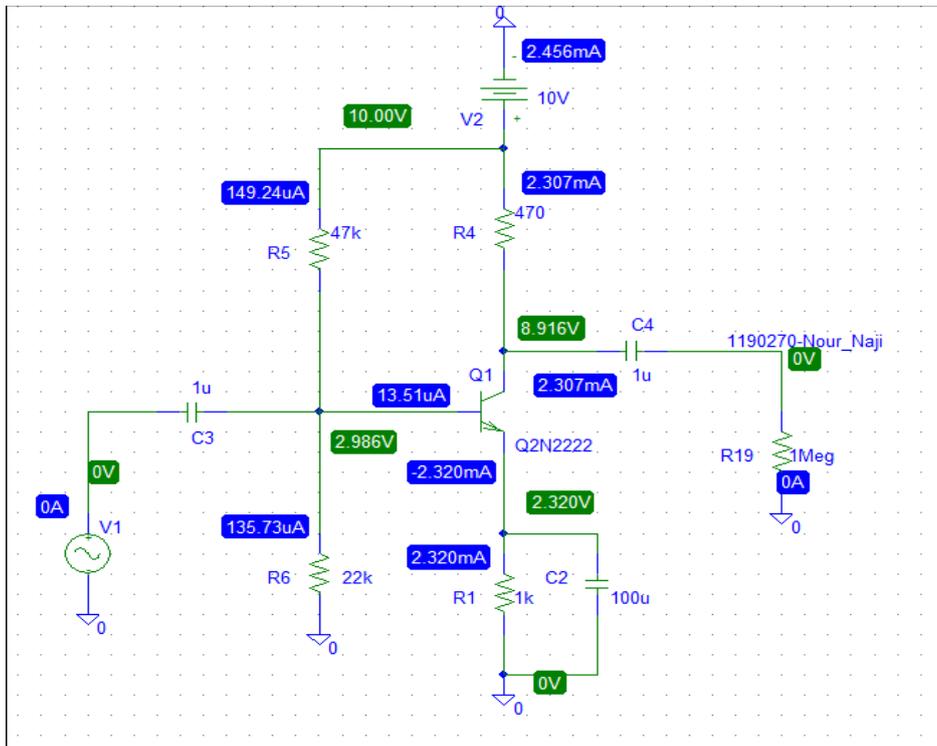❖ DC bias and measure V_B , V_C , V_E , I_C and I_B :



- $V_B = 2.986 \text{ v}$
- $V_C = 8.916 \text{ v}$
- $V_E = 2.32 \text{ v}$
- $I_C = 2.307 \text{ mA}$
- $I_B = 13.51 \mu\text{A}$

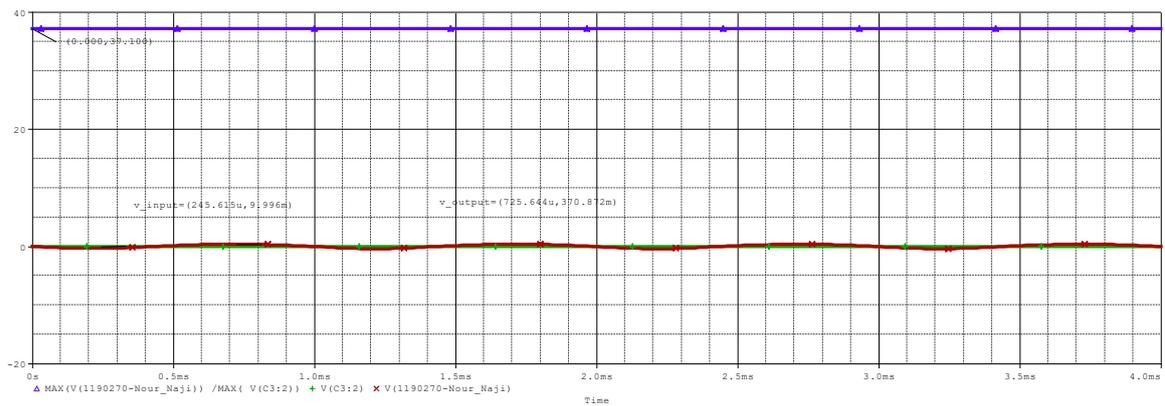❖ Transient analysis with a sine wave with frequency = 1 kHz and peak = 10 mV:




❖ Question:


What is the gain of the amplifier first stage?

➤ Voltage Gain $A_v = \frac{V_{out}}{V_{in}} = 37.100$

2. Second Amplifier stage

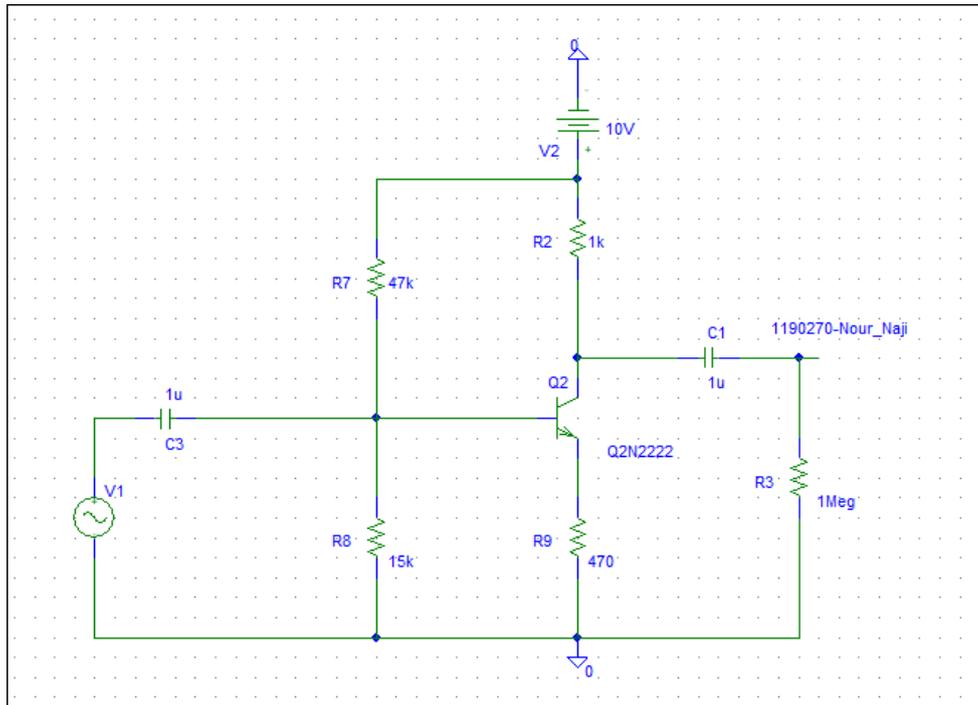


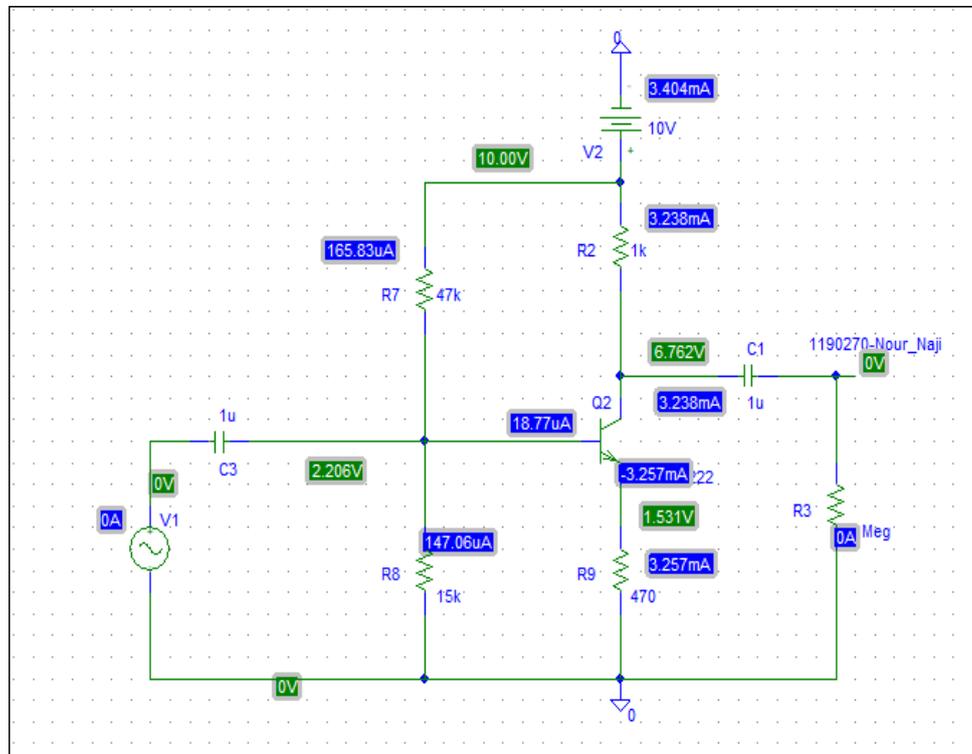❖ DC bias and measure V_B , V_C , V_E , I_C and I_B :



- $V_B = 2.206 \text{ v}$
- $V_C = 6.762 \text{ v}$
- $V_E = 1.531 \text{ v}$
- $I_C = 3.238 \text{ mA}$
- $I_B = 18.77 \mu\text{A}$

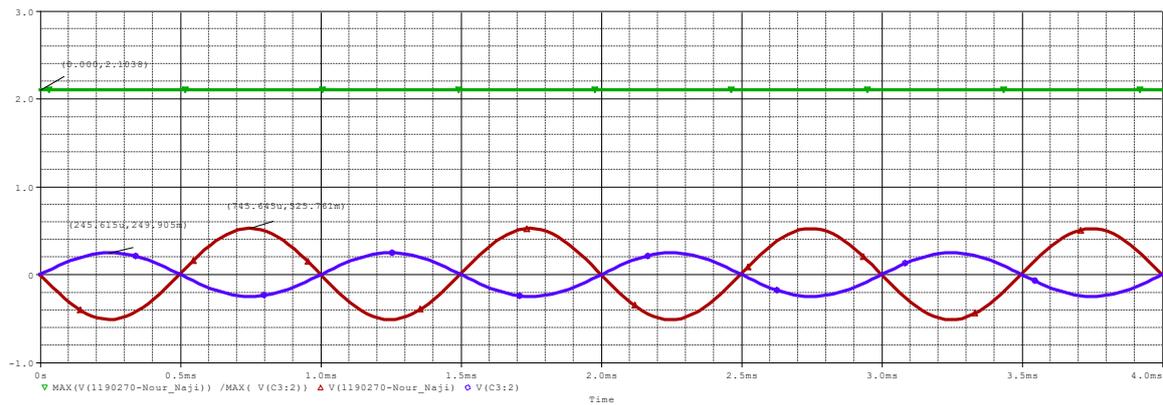❖ Transient analysis with a sine wave with frequency = 1 kHz and peak = 250 mV:




❖ Question:


What is the gain of the amplifier first stage?

➤ Voltage Gain $A_v = \frac{V_{out}}{V_{in}} = 2.1038$

3. Connect the two stages together:

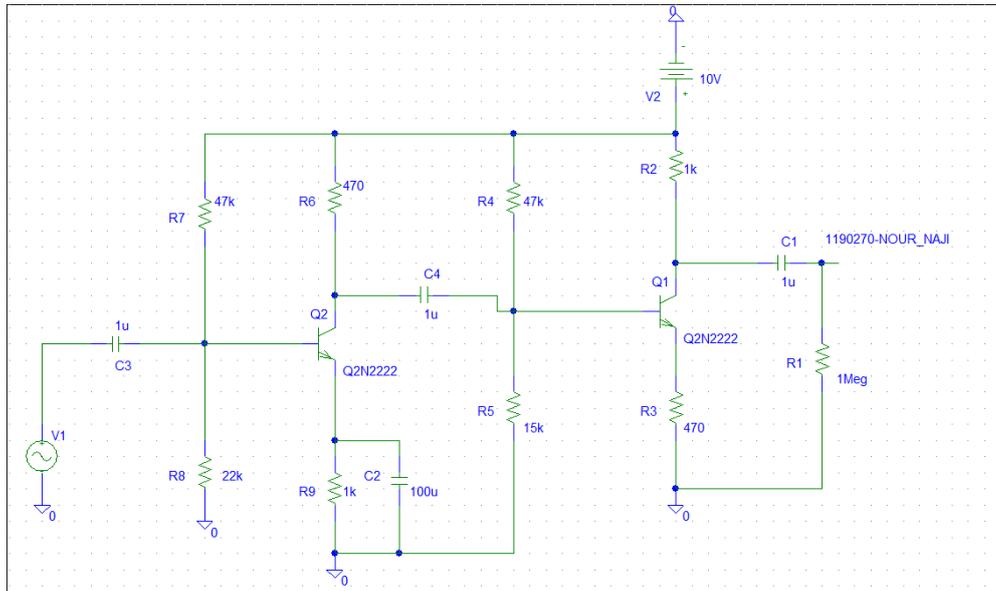


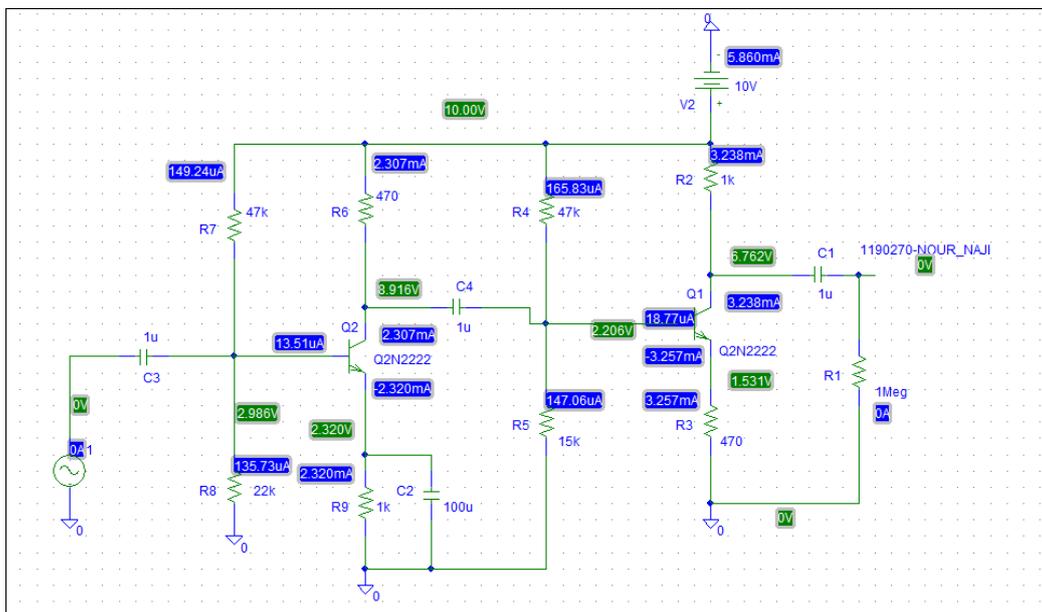❖ DC bias and measure $V_{B1}, V_{C1}, V_{E1}, I_{C1}$ and I_{B1} for first amplifier stage, $V_{B2}, V_{C2}, V_{E2}, I_{C2}$ and I_{B2} for second amplifier stage:



- $V_{B2} = 2.986 \text{ v}$
- $V_{C2} = 8.916 \text{ v}$
- $V_{E2} = 2.320 \text{ v}$
- $I_{C2} = 2.307 \text{ mA}$
- $I_{B2} = 13.51 \text{ }\mu\text{A}$
- $V_{B1} = 2.206 \text{ v}$
- $V_{C1} = 6.762 \text{ v}$
- $V_{E1} = 1.531 \text{ v}$
- $I_{C1} = 3.238 \text{ mA}$
- $I_{B1} = 18.77 \text{ }\mu\text{A}$

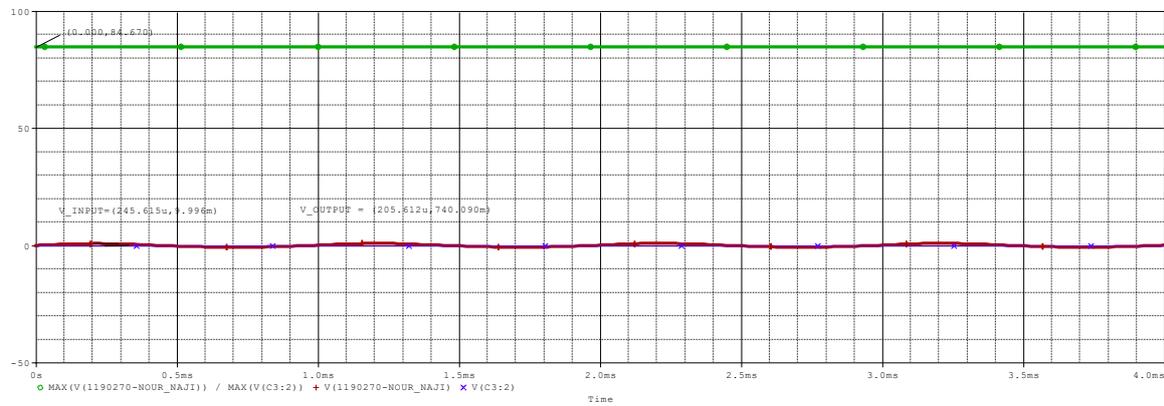- ❖ Transient analysis with $V_i(t)$ replaced by a sine wave with frequency = 1kHz and peak = 10 mV:



- ❖ Question:

What is the gain of the amplifier first stage?

➤ Voltage Gain $A_v = \frac{V_{out}}{V_{in}} = 84.670$

4. Compare the dc bias voltages and currents obtained in 1,2 and 3:

❖ DC bias and V_B , V_C , V_E , I_C and I_B obtained in A:

- $V_B = 2.986 \text{ v}$
- $V_C = 8.916 \text{ v}$
- $V_E = 2.32 \text{ v}$
- $I_C = 2.307 \text{ mA}$
- $I_B = 13.51 \mu\text{A}$

❖ DC bias and measure V_B , V_C , V_E , I_C and I_B obtained in B:

- $V_B = 2.206 \text{ v}$
- $V_C = 6.762 \text{ v}$
- $V_E = 1.531 \text{ v}$
- $I_C = 3.238 \text{ mA}$
- $I_B = 18.77 \mu\text{A}$

❖ DC bias and measure V_{B1} , V_{C1} , V_{E1} , I_{C1} and I_{B1} for first amplifier stage, V_{B2} , V_{C2} , V_{E2} , I_{C2} and I_{B2} for second amplifier stage:


- | | |
|--------------------------------|------------------------------|
| ▪ $V_{B1} = 2.986 \text{ v}$ | $V_{B2} = 2.206 \text{ v}$ |
| ▪ $V_{C1} = 8.916 \text{ v}$ | $V_{C2} = 6.762 \text{ v}$ |
| ▪ $V_{E1} = 2.32 \text{ v}$ | $V_{E2} = 1.531 \text{ v}$ |
| ▪ $I_{C1} = 2.307 \text{ Ma}$ | $I_{C2} = 3.238 \text{ mA}$ |
| ▪ $I_{B1} = 13.51 \mu\text{A}$ | $I_{B2} = 18.77 \mu\text{A}$ |

5. Compare A_v (obtained in 3) with product $A_{v1} * A_{v2}$ (obtained in 1 and 2):

- Voltage Gain $A_{v1} = \frac{V_{out}}{V_{in}} = 37.100$
- Voltage Gain $A_{v2} = \frac{V_{out}}{V_{in}} = 2.1038$
- Voltage Gain $A_v = \frac{V_{out}}{V_{in}} = 84.670$
- $A_{v1} * A_{v2} = 37.100 * 2.1038 = 78.05 \text{ v}$

- ✓ As can be shown, $A_v = \frac{V_{out}}{V_{in}}$ is the same as the result of the product of A_{v1} and A_{v2} , but with simple loading effect.

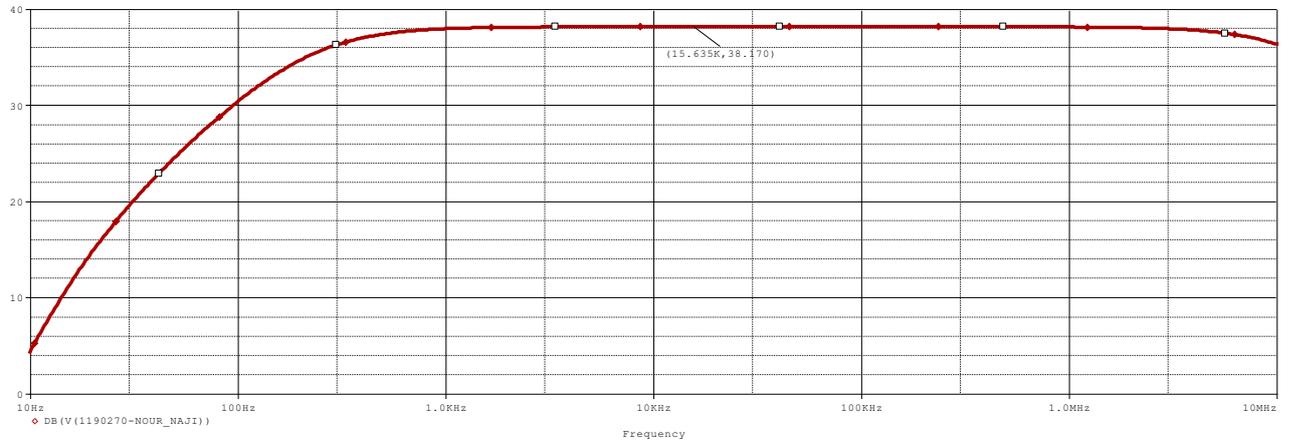
6. For the two stage Amplifier, perform ac sweep and show the frequency response in dB for frequency range 10Hz-10MHz



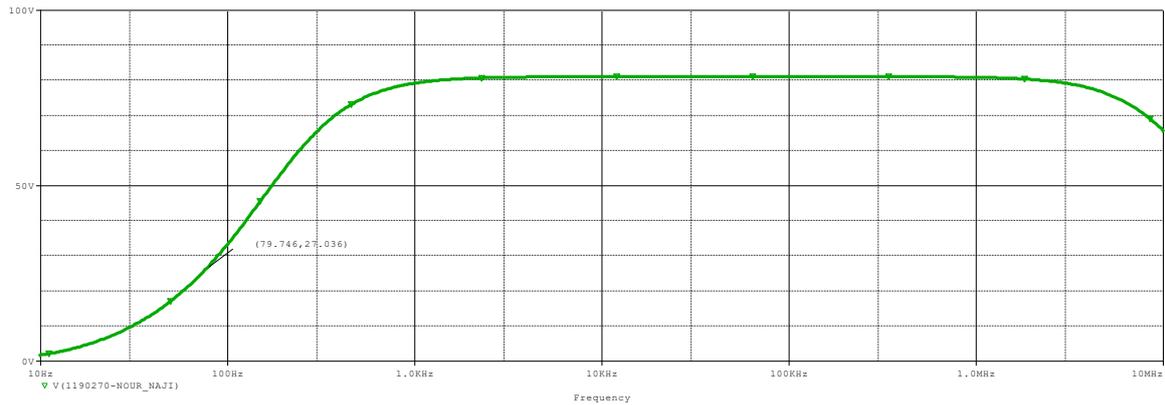7. Based on F, estimate F_L and f_H (the cutoff frequencies at low and high frequencies)

➤ $\text{Log } 38.170 = 1.5817 \text{ v}$

➤ $\frac{A_v}{\sqrt{2}} = \frac{38.170}{\sqrt{2}} = 27$



➤ So the cut-off frequency = 79.746