

L19 - part 2

# ENEE2360 Analog Electronics

T10:  
FET Amplifiers  
ac small signal analysis

Instructor : Nasser Ismail

1

$g_m = \frac{\partial I_D}{\partial V_{GS}} \rightarrow \frac{A}{V} = \frac{1}{\Omega} \times$   
 $= \Omega^{-1} \times$   
 $= \text{mho} \times$        $0 \text{ km}$   
 $= \underline{\underline{\text{Siemens}}}$  ✓✓

JFET  
 DMOSFET  $\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$   
 EMOSFET  $\rightarrow I_D = K_n (V_{GS} - V_T)^2$

## Definition: Transconductance $g_m$

For JFETs and DMOSFETs

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P}\right]$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P}\right] = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$



$g_m$   
always positive

$$g_{m0} = \frac{2I_{DSS}}{|V_P|} = g_m |_{V_{GS}=0}$$

For EMOSFET

$$I_D = K (V_{GS} - V_{GS(TH)})^2$$


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = 2K (V_{GS} - V_{GS(TH)})$$

$$(V_{GS} - V_{GS(TH)}) = \sqrt{\frac{I_D}{K}}$$

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(TH)})^2}$$

$$\therefore g_m = 2K \sqrt{\frac{I_D}{K}} = 2\sqrt{I_D K} = 2\sqrt{I_D} K$$


operating point

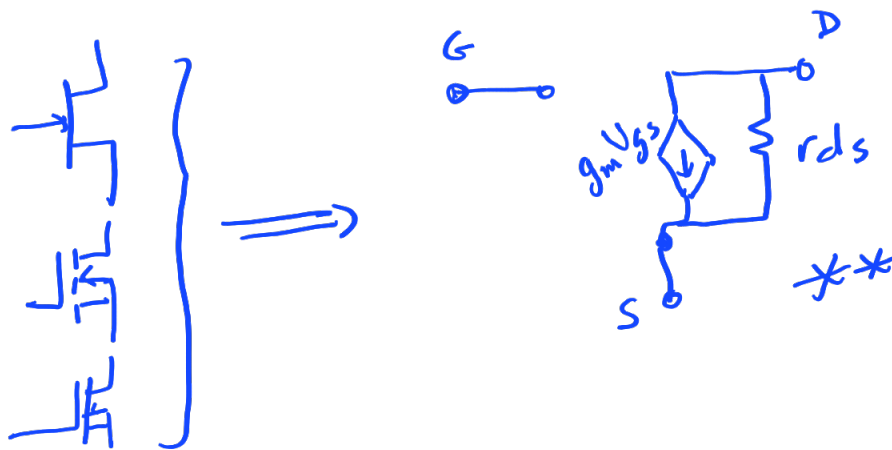
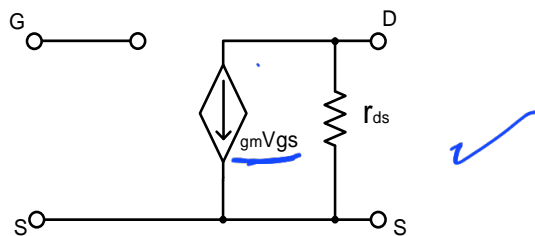
## AC Small Signal Equivalent Circuit (MODEL Valid for all FET Types)

- In ac

$$g_m = \frac{i_d}{v_{gs}} \Rightarrow i_d = g_m v_{gs}$$




Source Transformation

- Or

$$\mu = g_m r_{ds} \text{ - amplification factor}$$

unitless

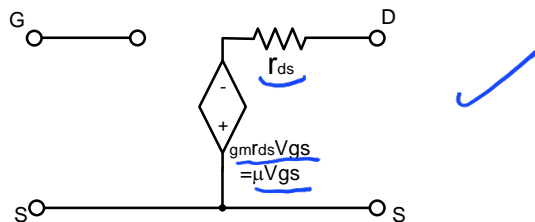

$$g_m V_{gs} r_{ds} = \frac{g_m r_{ds} V_{gs}}{1 V_{gs}} = \mu V_{gs}$$

# FET amplifiers

same ac eq. circuit {

1. Common Source (CS)	⇒	CE
2. " Drain (CD)	⇒	CC
3. " Gate (CG)	⇒	CB

BJT




## Common-Source (CS) Fixed-Bias

The input is applied to the gate and the output is taken from the drain

There is a 180° phase shift between the circuit input and output

**To construct ac ss equivalent circuit**

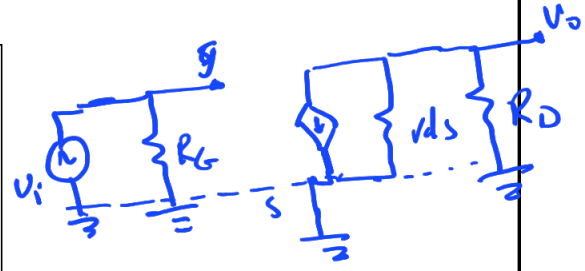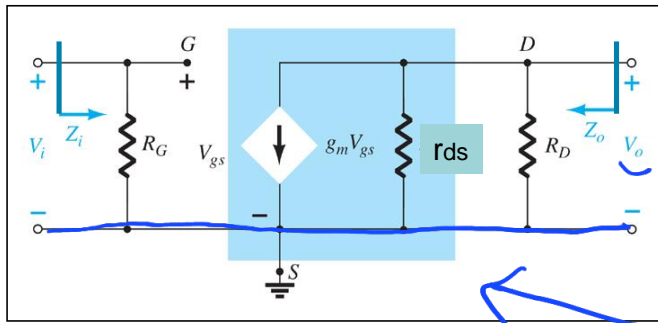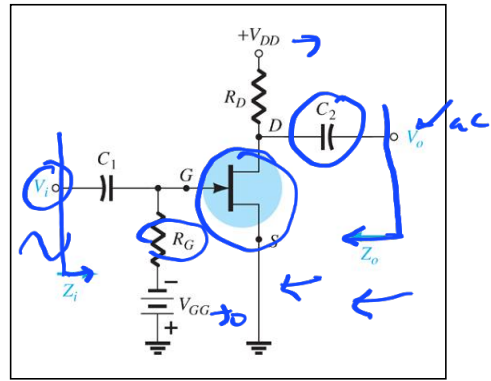- 1)  $C_1$  &  $C_2$  are replaced by short
- 2)  $V_{DD}=0$  V (short),  $V_{GG}=0 \rightarrow$  short
- 3) FET ac ss MODEL



# Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:

$$Z_o \Big|_{V_i=0} = R_D // r_{ds}$$

$$Z_o \Big|_{V_i=0} \cong R_D \quad r_{ds} \geq 10R_D$$

Voltage gain:


$$V_i = V_{gs}$$

$$V_o = V_{ds}$$

$$A_v = \frac{V_o}{V_i} = \frac{V_{ds}}{V_{gs}}$$

$$V_{ds} = -g_m V_{gs} (r_{ds} // R_D)$$


$$, V_{gs} = V_i$$

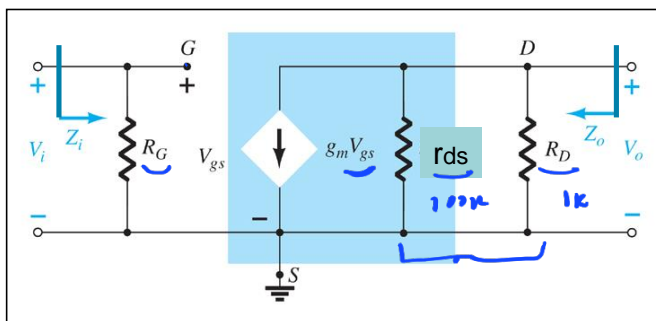

$$A_v = \frac{V_o}{V_i}; \quad V_o = (R_D // r_{ds}) - g_m V_{gs}$$

$$A_v = \frac{V_{ds}}{V_{gs}} = -g_m (r_{ds} // R_D)$$


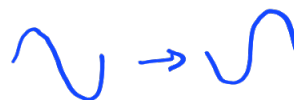
$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad r_{ds} \geq 10R_D$$



180° shift  $\rightarrow$   $o_v \times -1$
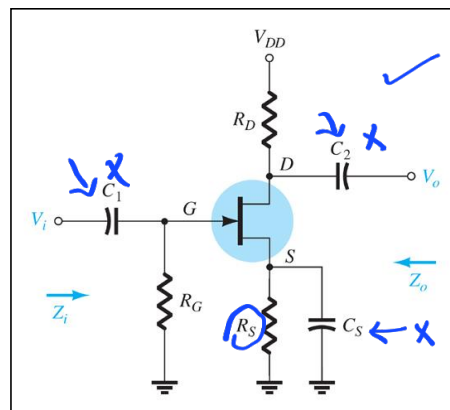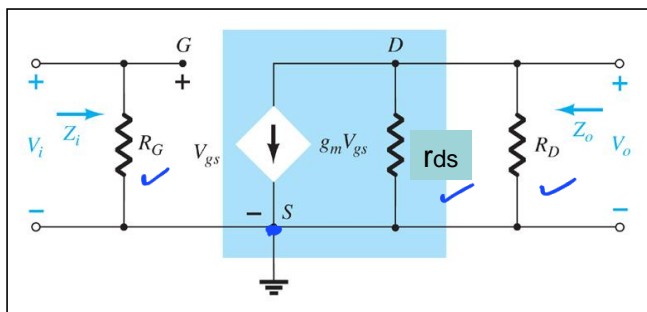
## Common-Source (CS) Self-Bias

This is a common-source amplifier configuration, so the input is applied to the gate and the output is taken from the drain.



There is a 180° phase shift between input and output.

# Calculations

**Input impedance:**

$$Z_i = R_G$$

**Output impedance:**


$$Z_o = r_{ds} // R_D$$

$$Z_o \cong R_D \quad \left| \quad r_{ds} \geq 10 R_D \right.$$

**Voltage gain:**

$$A_v = -g_m (r_{ds} // R_D)$$

$$A_v \cong -g_m R_D \quad \left| \quad r_{ds} \geq 10 R_D \right.$$

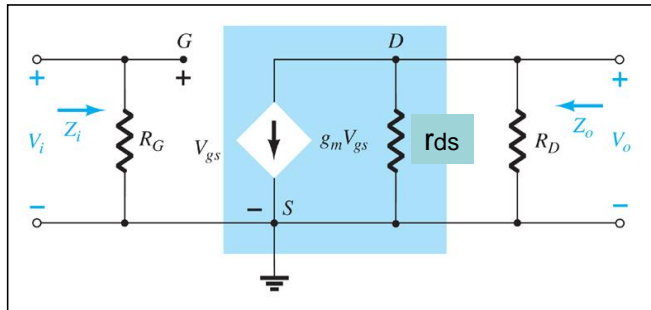

*Same as previous circuit*



$$V_o = -g_m V_{gs} R_D \dots (1) \rightarrow \frac{V_o}{V_{gs}} = -g_m R_D$$

$$V_{gs} = V_g - V_s ; V_g = V_i ; V_s = g_m V_{gs} R_s$$

$$V_{gs} = V_i - g_m V_{gs} R_s \Rightarrow V_i = V_{gs} (1 + g_m R_s) \dots (2)$$

$$\frac{V_{gs}}{V_i} = \frac{1}{1 + g_m R_s}$$
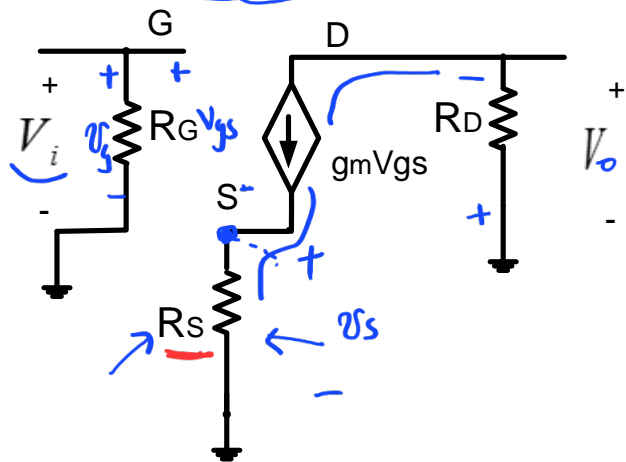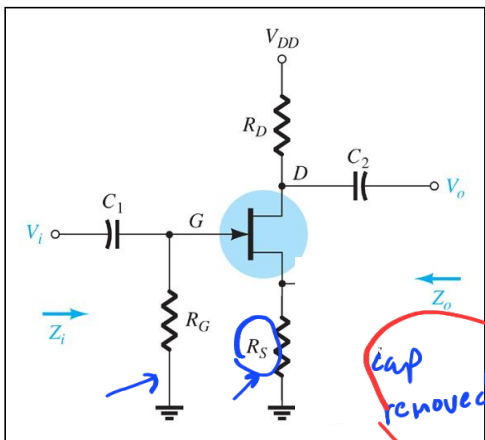
## Common-Source (CS) Self-Bias Effect of $R_s$ (ignore rds) $\rightarrow r_{ds} = \infty$



$$A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{gs} (R_D)$$

$$V_s = g_m V_{gs} (R_s)$$

$$V_g = V_i$$

$$V_{gs} = V_g - V_s = V_i - g_m V_{gs} R_s$$


$$\Rightarrow V_i = V_{gs} + g_m V_{gs} R_s$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} R_D}{V_{gs} + g_m V_{gs} R_s}$$


$$A_v = \frac{-g_m R_D}{1 + g_m R_s}$$

Gain is reduced due to  $R_s$

previous circuit without  $R_s$

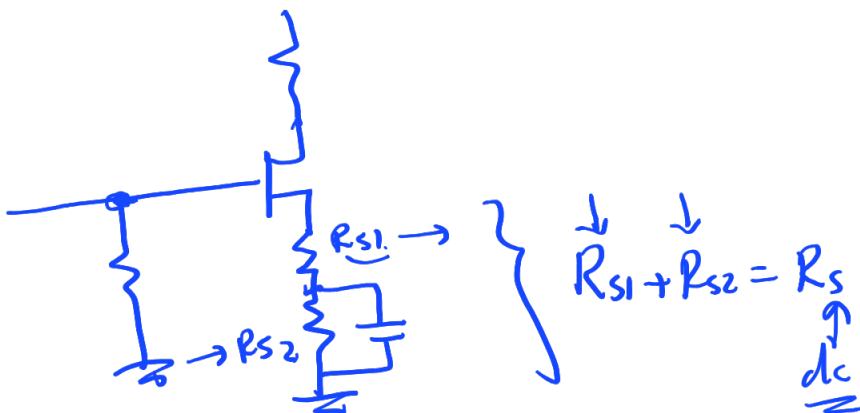




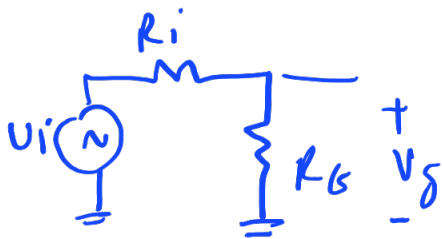

$V_i = V_g \rightarrow$  without  $R_i$   
 $V_g = V_i \frac{R_G}{R_G + R_i}$  \*
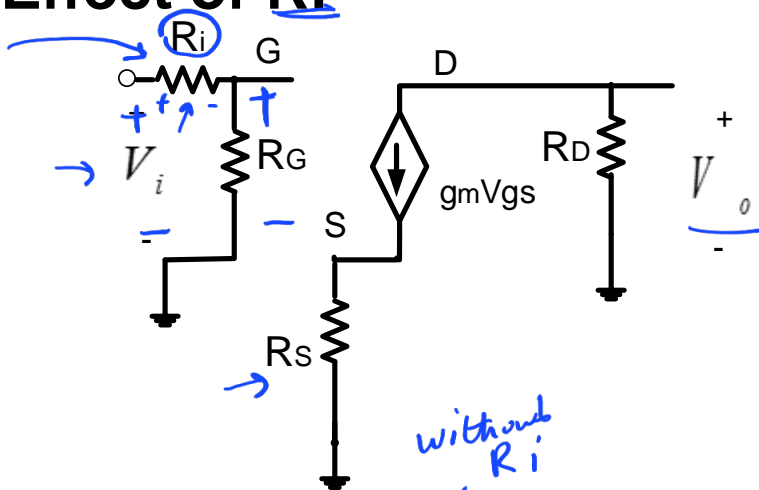
## Common-Source (CS) Self-Bias Effect of $R_i$



$$A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{gs} (R_D)$$

$$V_s = g_m V_{gs} (R_S)$$

$$V_g = \frac{R_G}{R_G + R_i} V_i$$

$$V_{gs} = V_g - V_s = \frac{R_G}{R_G + R_i} V_i - g_m V_{gs} R_S$$


$$\Rightarrow V_i = V_{gs} (1 + g_m R_S) \frac{R_G + R_i}{R_G}$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} \frac{R_G}{R_G + R_i}$$

Gain is reduced more due to  $R_i$


End of L19  
12/8/2021

FET's → ss equivalent circuit →

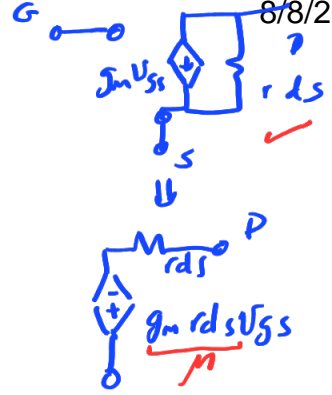
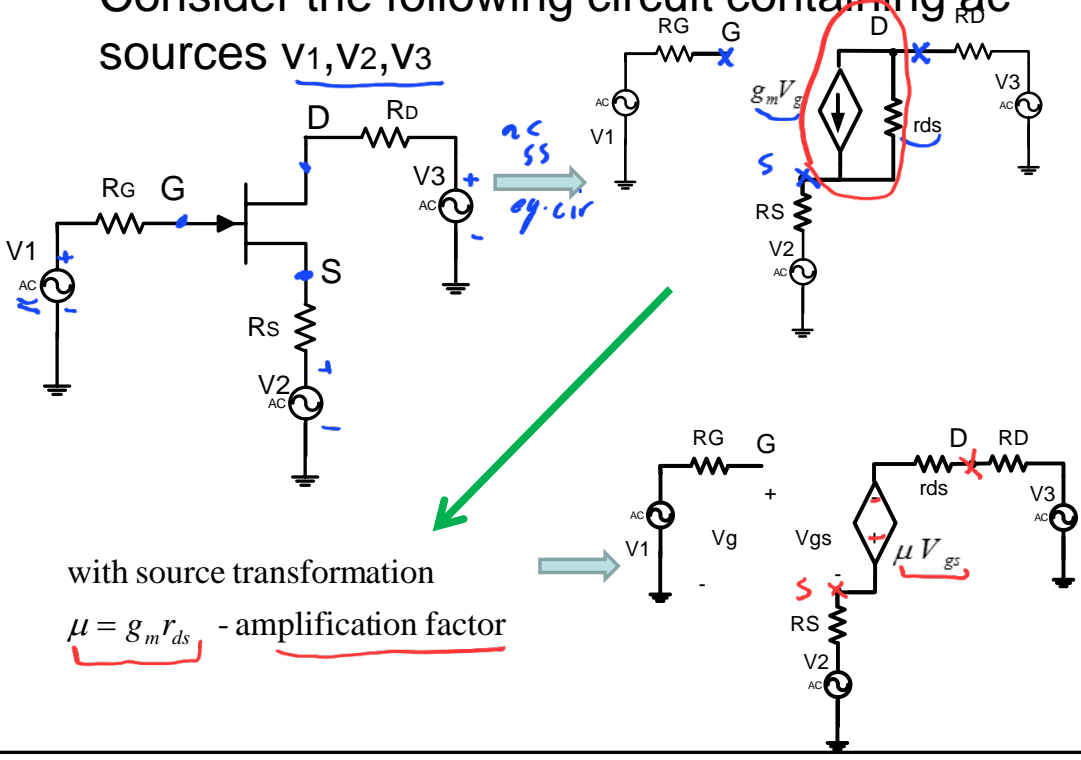
## Impedance Reflection

- Consider the following circuit containing ac sources  $V_1, V_2, V_3$



# Impedance Reflection

KVL for the drain - source loop

$$V_3 - i_D R_D - i_D r_{ds} - i_D R_S + \mu V_{gs} - V_2 = 0 \dots \dots \dots (1)$$

but

$$V_{gs} = V_g - V_S = V_g - (i_D R_S + V_2) \dots \dots \dots (2)$$

substituting (2) in (1) yields :

$$V_3 - i_D R_D - i_D r_{ds} - i_D R_S + \mu (V_g - (i_D R_S + V_2)) - V_2 = 0$$

$$V_3 - i_D R_D - i_D r_{ds} - i_D R_S + \mu V_g - \mu i_D R_S - \mu V_2 - V_2 = 0$$



$$V_3 - i_D R_D - i_D r_{ds} - i_D R_S (\mu + 1) + \mu V_g - V_2 (\mu + 1) = 0$$

$$i_D R_D + i_D r_{ds} + i_D R_S (\mu + 1) = V_3 + \mu V_g - V_2 (\mu + 1)$$

$$V_3 - i_D R_D - i_D r_{ds} - i_D R_S + \mu (V_g - (i_D R_S + V_2)) - V_2 = 0$$

$$i_D = \frac{V_3 + \mu V_g - V_2 (\mu + 1)}{R_D + r_{ds} + R_S (\mu + 1)} \dots \dots \dots (3) *$$

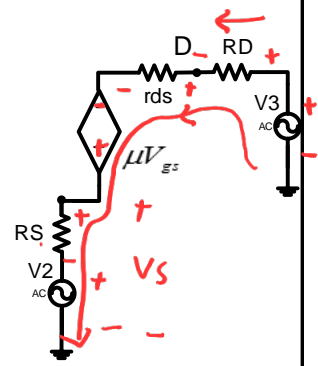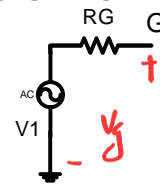(3) is the drain Equivalent circuit equation



→  $i_D$  ?

original circuit

$$i_D = \frac{V_3 + \mu V_g - V_2(\mu + 1)}{R_D + r_{ds} + R_s(\mu + 1)} \dots \dots \dots (3)$$

(3) is the drain Equivalent circuit equation

Reflection from Source to Drain

$$\mu V_{gs} \Rightarrow \mu V_g$$

$$R_s \Rightarrow R_s(\mu + 1)$$

$$V_2 \Rightarrow V_2(\mu + 1)$$

divide eq. (3) by  $(\mu + 1)$

$$i_D = \frac{\frac{V_3}{(\mu + 1)} + \frac{\mu V_g}{(\mu + 1)} - \underline{V_2}}{\frac{R_D}{(\mu + 1)} + \frac{r_{ds}}{(\mu + 1)} + \underline{R_S}} \dots \dots \dots (4)$$

(4) is the source equivalent circuit equation

Reflection Drain to Source

$$\mu V_{gs} \Rightarrow \frac{\mu V_g}{(\mu + 1)}$$

$$R_D \Rightarrow \frac{R_D}{(\mu + 1)}$$

$$r_{ds} \Rightarrow \frac{r_{ds}}{(\mu + 1)}$$

$$v_3 \Rightarrow \frac{v_3}{(\mu + 1)}$$

## Example: Phase Splitting circuit



- Two outputs:

- Vo1 from drain
- Vo2 from source

$r_{ds} = 100\text{ k}\Omega$   
 $g_m = 1\text{ mS}$


two outputs

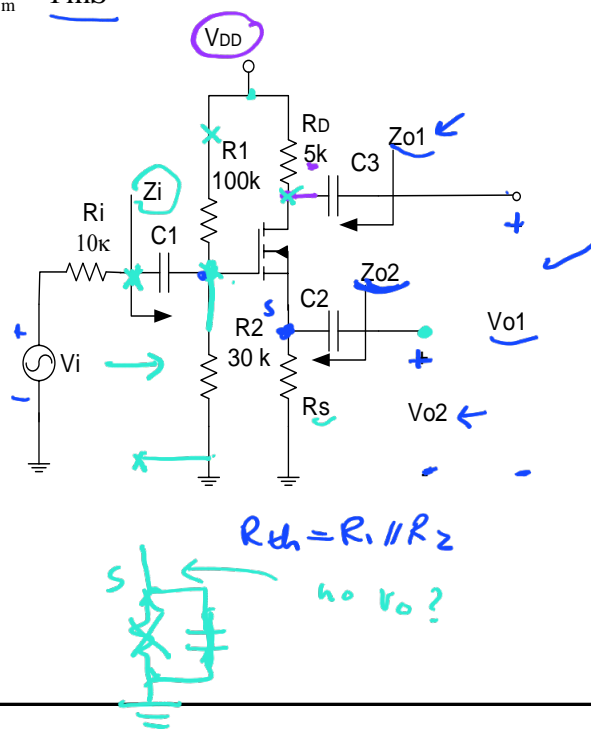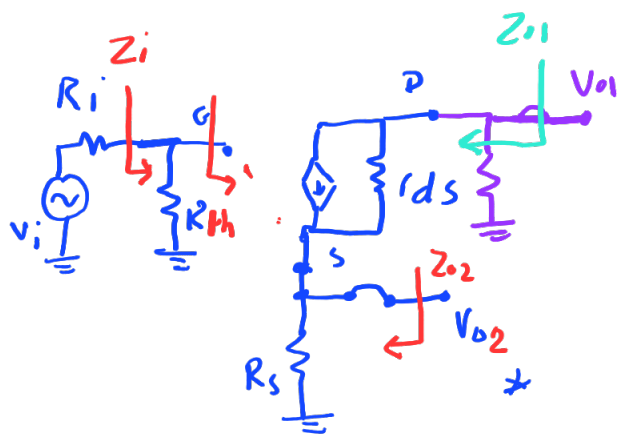Find  $A_v, A_i, Z_{O1}, Z_{O2}$  and  $Z_i$




$Z_{in} = R_{th}$

## Solution: ac ss equivalent circuit

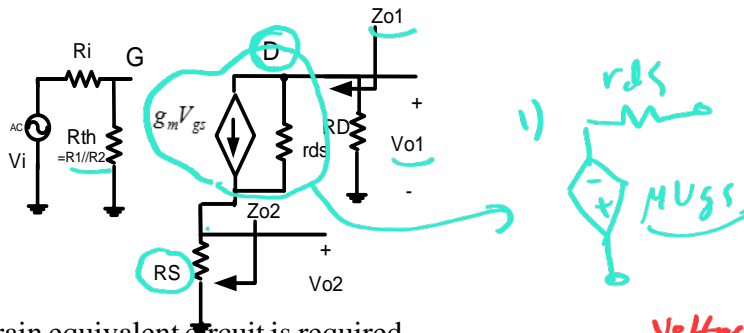

1) To Find  $Z_{o1}$ ,  $V_{o1}$  Drain equivalent circuit is required since both of these quantities are seen from the drain

Voltage Divider

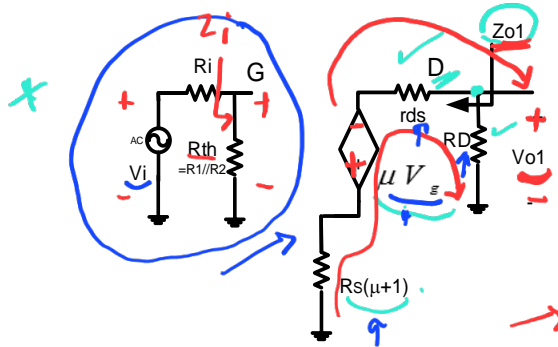


$$V_{o1} = \frac{R_D}{R_D + r_{ds} + R_S(\mu + 1)} (-\mu V_g) \rightarrow \frac{V_{o1}}{V_g}$$

$$V_g = V_i \frac{R_{th}}{R_{th} + R_i} \rightarrow \frac{V_g}{V_i}$$

$$A_v = \frac{V_{o1}}{V_i} = (-\mu) \frac{R_D}{R_D + r_{ds} + R_S(\mu + 1)} \times \frac{R_{th}}{R_{th} + R_i}$$


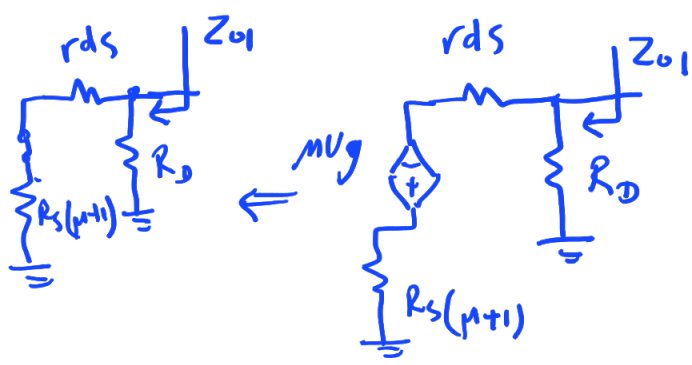
$$A_v = \frac{\mu}{R_S} \times \frac{V_g}{V_i}$$



$$Z_{o1} = R_D \parallel (r_{ds} + R_S(\mu + 1))$$

$V_i = 0$   
 $V_g = 0$   
 $\mu V_g = 0$   
(Short)

2) To Find  $Z_{O1}|_{V_i=0, V_g=0}$

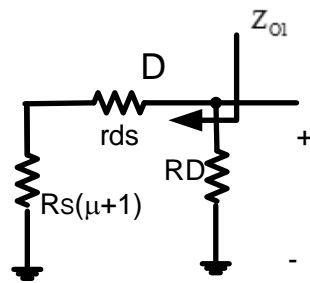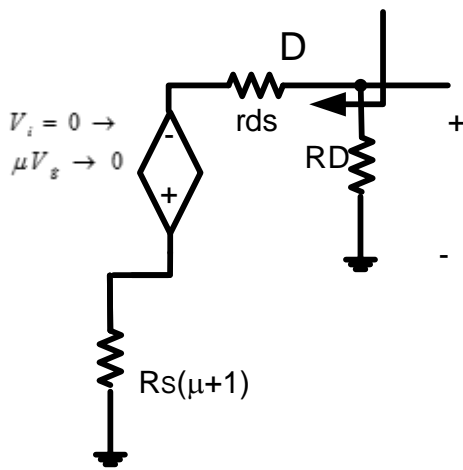

$$Z_{O1}|_{V_i=0, V_g=0} = R_D // [r_{ds} + R_s(\mu + 1)]$$



## Solution: continued

3) To Find  $Z_{O2}$ ,  $V_{O2}$  Source equivalent circuit is required since both of these quantities are seen from the source

Reflection Drain to Source


$$\mu V_{gs} \Rightarrow \frac{\mu V_g}{(\mu + 1)}$$

$$R_D \Rightarrow \frac{R_D}{(\mu + 1)}$$

$$r_{ds} \Rightarrow \frac{r_{ds}}{(\mu + 1)}$$

$$V_{o2} = \frac{R_{DS}}{R_D + r_{ds} + R_S} \left( \frac{\mu V_g}{(\mu + 1)} \right)$$

$$V_g = V_i \frac{R_{th}}{R_{th} + R_i}$$
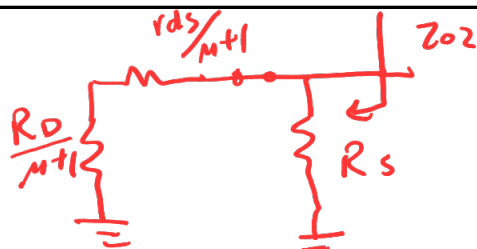
$$\rightarrow A_{v2} = \frac{V_{o2}}{V_i} = \frac{\mu}{(\mu + 1)} \frac{R_{DS}}{R_D + r_{ds} + R_S} \frac{R_{th}}{R_{th} + R_i}$$


$$Z_{O2} = R_S \parallel \left( \frac{r_{ds} + R_D}{\mu + 1} \right)$$

$V_i = 0$   
 $V_S = 0$   
 $\frac{\mu V_S}{\mu + 1} = 0$

if  $r_{ds} \rightarrow \infty$

$$Z_{O2} \Big|_{r_{ds} \rightarrow \infty} = R_S \parallel \frac{1}{g_m}$$


\*\*\*

$$Z_{O2} = R_S \parallel \frac{r_{ds} + R_D}{\mu + 1}$$

$$\lim_{r_{ds} \rightarrow \infty} \frac{r_{ds} + R_D}{\mu + 1} = \lim_{r_{ds} \rightarrow \infty} \frac{r_{ds} + R_D}{g_m r_{ds} + 1} = \lim_{r_{ds} \rightarrow \infty} \frac{1 + \frac{R_D}{r_{ds}}}{g_m + \frac{1}{r_{ds}}} = \frac{1}{g_m}$$

### Solution: continued

4) To Find  $Z_{O2} \Big|_{V_i=0, V_g=0}$

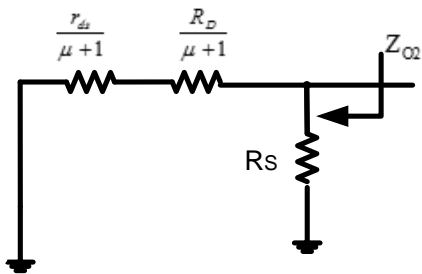

$$Z_{O2} \Big|_{V_i=0, V_g=0} = R_S \parallel \left[ \frac{r_{ds} + R_D}{(\mu + 1)} \right]$$







$$Z_{O2} \Big|_{V_i=0, V_g=0, r_{ds} \rightarrow \infty} = R_S \parallel \frac{1}{g_m}$$

since  $\lim_{r_{ds} \rightarrow \infty} \frac{r_{ds} + R_D}{\mu + 1} = \lim_{r_{ds} \rightarrow \infty} \frac{\frac{r_{ds}}{r_{ds}} + \frac{R_D}{r_{ds}}}{\frac{g_m r_{ds}}{r_{ds}} + \frac{1}{r_{ds}}} = \lim_{r_{ds} \rightarrow \infty} \frac{1 + \frac{R_D}{r_{ds}}}{g_m + \frac{1}{r_{ds}}} = \frac{1}{g_m}$  ✓


$$Z_i = R_{th} = R_1 \parallel R_2$$

# Common Gate Amplifier

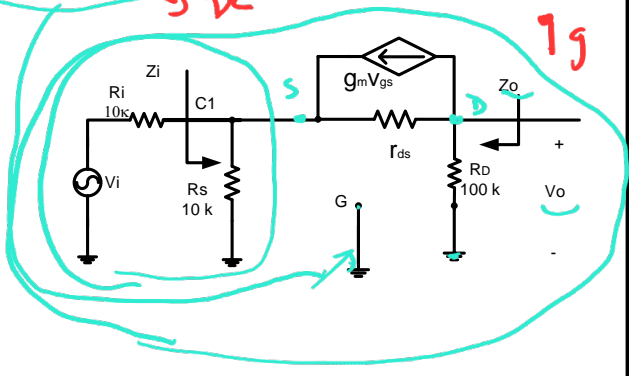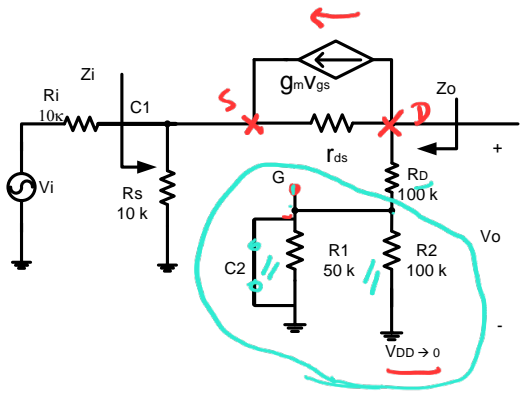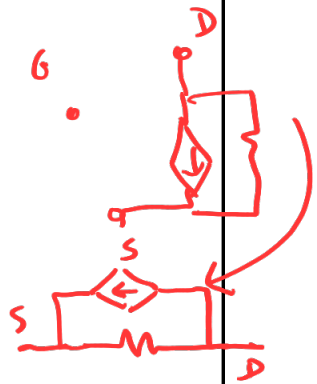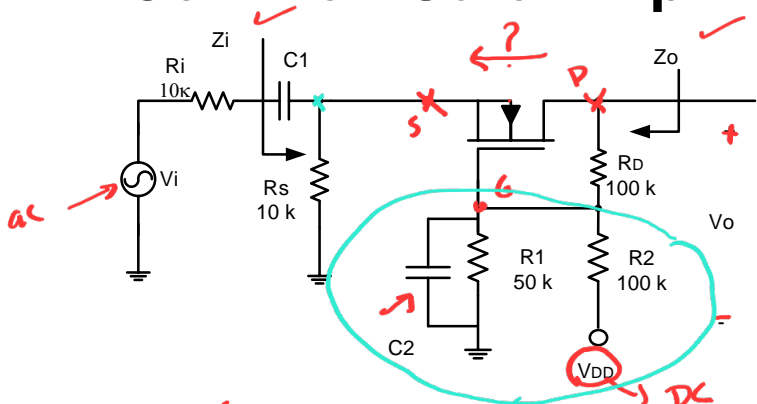

$\mu V_{gs} \rightarrow \mu V_g \rightarrow$   
 $R_i = R_s \leftarrow$  in this example

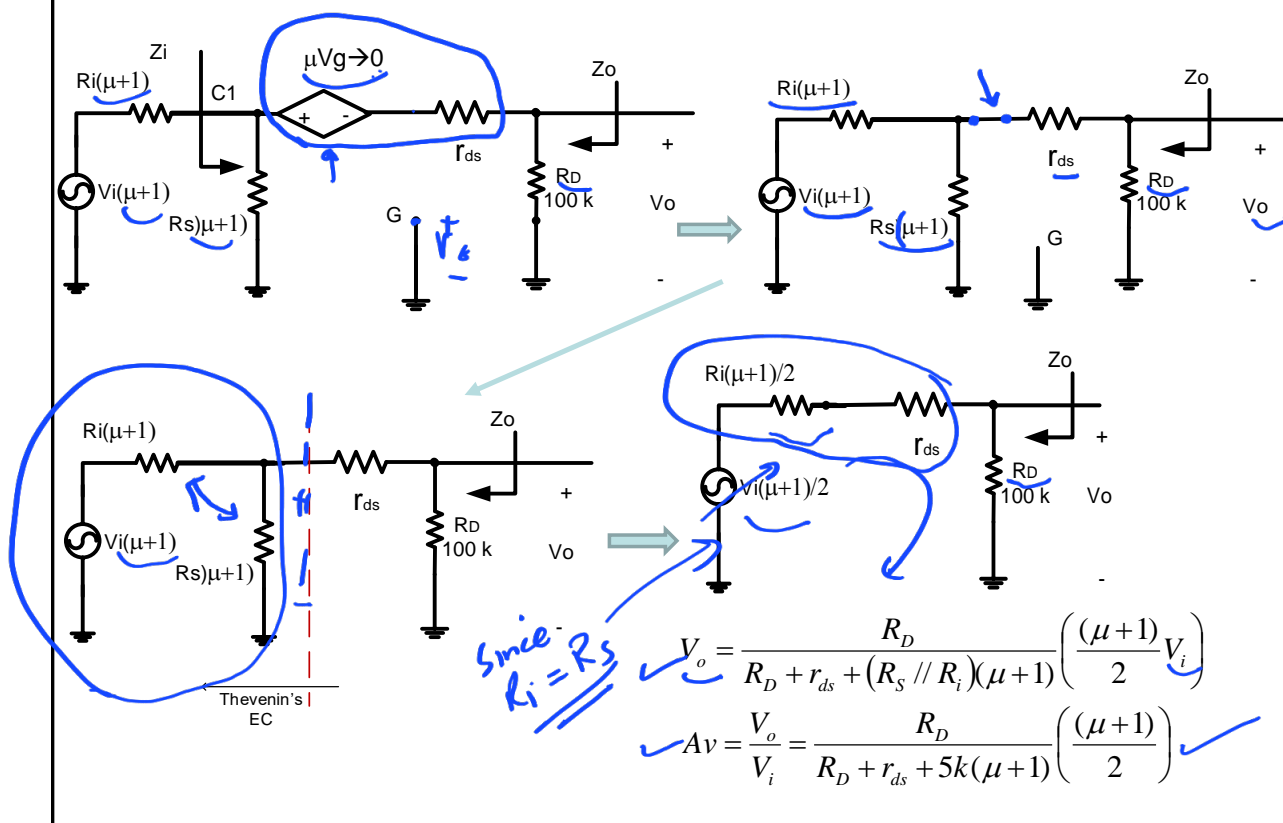
### Drain Equivalent circuit to find $V_o$ and $Z_o$



$$V_o = \frac{R_D}{R_D + r_{ds} + (R_s // R_i)(\mu+1)} \left( \frac{(\mu+1)}{2} V_i \right)$$

$$A_v = \frac{V_o}{V_i} = \frac{R_D}{R_D + r_{ds} + 5k(\mu+1)} \left( \frac{(\mu+1)}{2} \right)$$

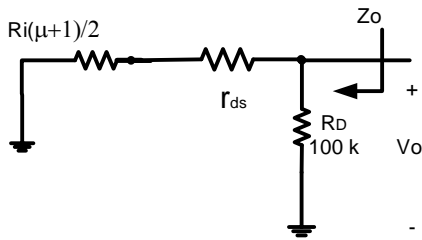
- Drain Equivalent circuit to find  $V_o$  and  $Z_o$



$$Z_O|_{V_i=0} = R_D // \left( r_{ds} + \frac{R_i(\mu+1)}{2} \right)$$

ENEE236

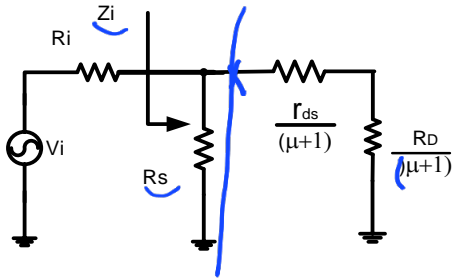
- To find  $Z_i$  source equivalent circuit is needed



$$Z_i = R_S \parallel \left[ \frac{r_{ds} + R_D}{(\mu + 1)} \right]$$

$$Z_i \Big|_{r_{ds} \rightarrow \infty} = R_S \parallel \frac{1}{g_m}$$

End of L20

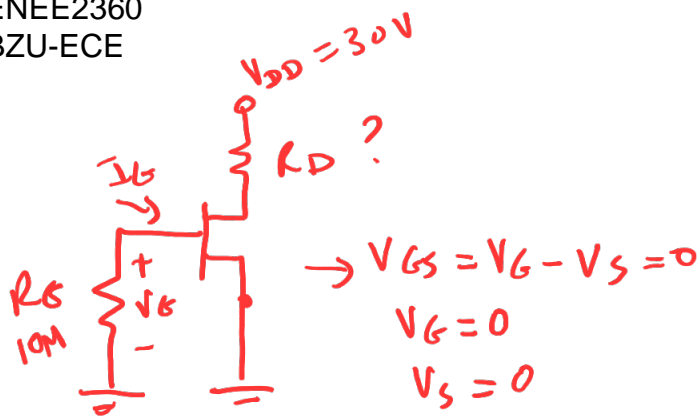

L21

16-8-2021

$$g_m = \frac{2 I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$= \frac{2 \times 10mA}{4} = 5 mS$$

## FET Amplifier Design (Important)

- Design a fixed bias network such that the ac voltage gain  $|A_v| = 10$ , i.e. find value of  $R_D$ .

$V_P = -4V$


$I_{DSS} = 10mA$

$r_{ds} = 50k\Omega$

→ DC analysis



→ AC analysis

$A_v = f(g_m, r_{ds})$

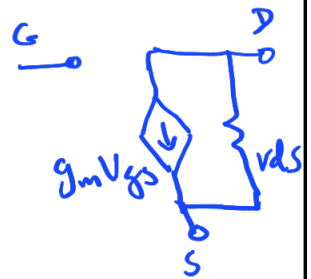

$g_m = \frac{\partial I_D}{\partial V_{GS}}$

$$= \frac{2 I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

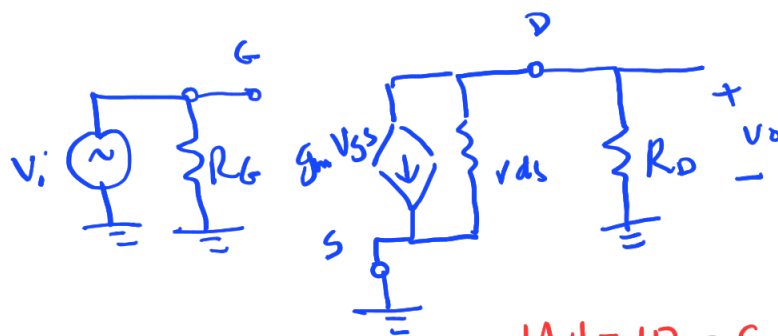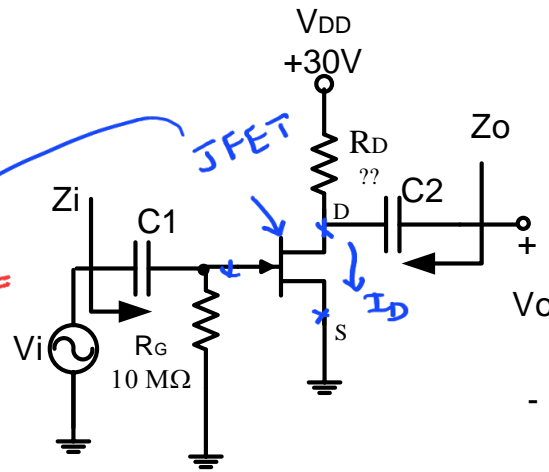

$A_v = \frac{V_o}{V_i}$

$V_o = -g_m V_{GS} (r_{ds} || R_D)$

$V_{GS} = V_i$

$A_v = -g_m (r_{ds} || R_D)$

$|A_v| = 10 = g_m \frac{r_{ds} \cdot R_D}{r_{ds} + R_D}$

$\therefore R_D =$

# Solution

ac ss equivalent circuit

$$V_{GS} = V_G - V_S = 0V$$

$$I_D = I_{DSS} \left( 1 - \frac{0}{-4} \right)^2 = I_{DSS} = 10mA$$

For JFETs

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

$$= \frac{2(10mA)}{|-4|} \left[ 1 - \frac{0}{-4} \right] = 5 \text{ mS}$$


$$V_{gs} = V_i$$

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{gs} (r_{ds} // R_D)$$

$$V_o = -g_m V_i (r_{ds} // R_D)$$

$$|A_v| = \left| \frac{V_o}{V_i} \right| = | -g_m (r_{ds} // R_D) |$$

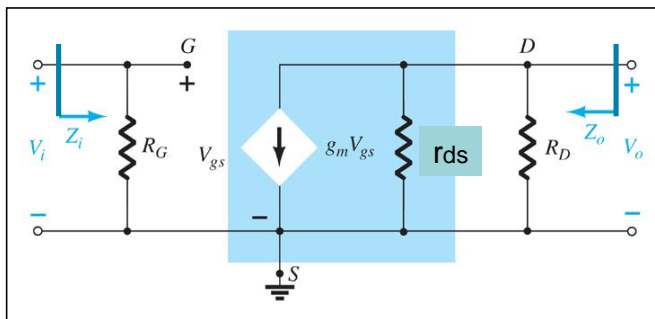

Since  $A_v$  &  $g_m$  are known, then

$$|A_v| = \left| \frac{V_o}{V_i} \right| = | -g_m (r_{ds} // R_D) | = 10$$

$$\therefore (r_{ds} // R_D) = \frac{10}{g_m} = \frac{10}{5 \text{ mS}} = 2 \text{ k}\Omega$$

Substitute  $r_{ds} = 50 \text{ k}\Omega$

$$(r_{ds} // R_D) = \frac{r_{ds} \cdot R_D}{r_{ds} + R_D} = \frac{50 \text{ k}\Omega \cdot R_D}{50 \text{ k}\Omega + R_D} = 2 \text{ k}\Omega$$

$$\rightarrow R_D = \frac{2 \text{ k}\Omega \cdot 50 \text{ k}\Omega}{48 \text{ k}\Omega} = 2.08 \text{ k}\Omega$$




## Design Example 2 (Important)

Choose the values of  $R_D$  and  $R_S$  that will result in

voltage gain  $|A_v| = 8$  using the value of  $g_m$  defined at  $V_{GSQ} = \frac{1}{4} V_p$
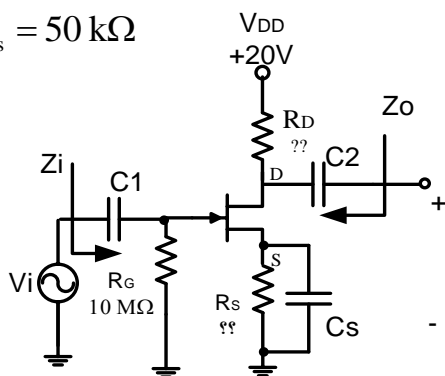
$$\left\{ \begin{array}{l} V_p = -4 \text{ V} \\ I_{DSS} = 10 \text{ mA} \\ r_{ds} = 50 \text{ k}\Omega \end{array} \right.$$



$$g_m = \frac{2I_{DSS}}{|V_p|} \left( 1 - \frac{V_{GS}}{V_p} \right)$$

$$g_{m1} = \frac{2I_{DSS}}{4} \left( 1 - \frac{-1}{-4} \right)$$

$$V_{GS} = \frac{1}{4} V_p$$

$$= \frac{2 \times 10 \text{ mA}}{4} \left( 1 - \frac{1}{4} \right)$$

$$= 3.75 \text{ mS}$$

## Solution (value of $R_D$ ?)

ac ss equivalent circuit

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

$$= \frac{2(10\text{mA})}{|-4|} \left[ 1 - \frac{-1}{-4} \right] = 3.75 \text{ mS}$$


$$V_{gs} = V_i$$

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{gs} (r_{ds} // R_D)$$

$$V_o = -g_m V_i (r_{ds} // R_D)$$

$$|A_v| = \left| \frac{V_o}{V_i} \right| = | -g_m (r_{ds} // R_D) |$$

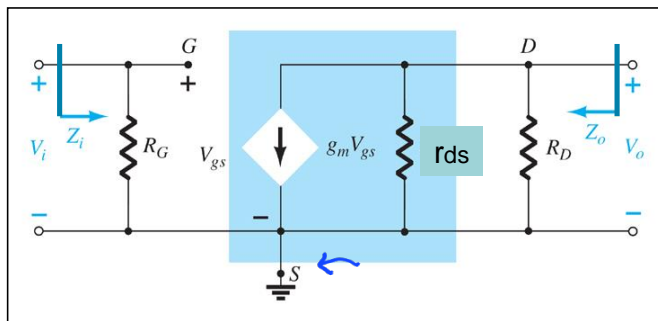

Since  $A_v$  &  $g_m$  are known, then

$$|A_v| = \left| \frac{V_o}{V_i} \right| = | -g_m (r_{ds} // R_D) | = 8$$

$$\therefore (r_{ds} // R_D) = \frac{8}{g_m} = \frac{8}{3.75 \text{ mS}} = 2.133 \text{ k}\Omega$$

Substitute  $r_{ds} = 50 \text{ k}\Omega$

$$(r_{ds} // R_D) = \frac{r_{ds} \cdot R_D}{r_{ds} + R_D} = \frac{50 \text{ k}\Omega \cdot R_D}{50 \text{ k}\Omega + R_D} = 2.133 \text{ k}\Omega$$

$$\rightarrow R_D = \frac{2.133 \text{ k}\Omega \cdot 50 \text{ k}\Omega}{47.867 \text{ k}\Omega} = 2.22 \text{ k}\Omega$$

## Value of Rs?

The value of  $R_s$  is determined from DC analysis

Given

$$V_{GS} = V_G - V_S = \frac{1}{4} V_P = -1$$


$$V_G = 0$$

$$V_S = I_D R_s = 1$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\text{but } I_D = I_{DSS} \left(1 - \frac{-1}{-4}\right)^2 = I_{DSS} \cdot 0.5625 = 5.625 \text{ mA}$$
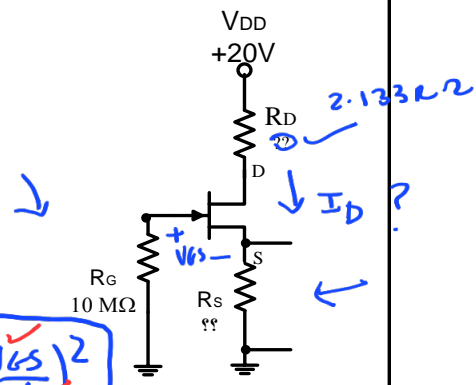
$$\therefore R_s = \frac{V_S}{I_D} = \frac{1 \text{ V}}{5.625 \text{ mA}} = 177.8 \Omega$$



Resistor  
standard values  
160  
→ 180  
200 } ±5%

## Design Example 3

Choose the values of  $R_D$  and  $R_S$  that will result in


voltage gain  $|Av| = 8$  using the value of  $g_m$  defined at  $V_{GSQ} = \frac{1}{4} V_p = -1V$

$V_p = -4V$

$I_{DSS} = 10mA$

$r_{ds} = \infty$

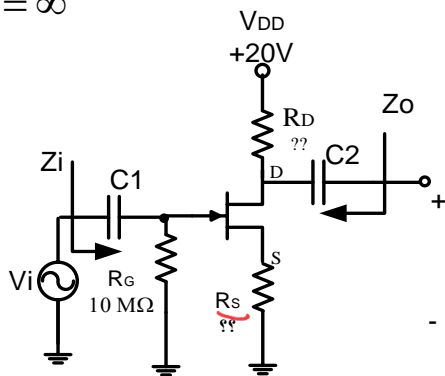Note: This is the same previous example except that no  $C_s$  (source capacitor)



# Solution

ac ss equivalent circuit

$$V_{GS} = -1 \text{ V}$$

$$I_D = 5.625 \text{ mA}$$

$$g_m = 3.75 \text{ mS} \text{ (from previous example)}$$

$$A_v = \frac{V_o}{V_i}$$


$$V_o = -g_m V_{gs} (r_{ds} // R_D) \leftarrow R_D$$

$$V_{gs} = V_g - g_m V_{gs} R_S$$

$$V_g = V_i$$

$$V_{gs} = V_i - g_m V_{gs} R_S$$

$$V_i = V_{gs} + g_m V_{gs} R_S$$

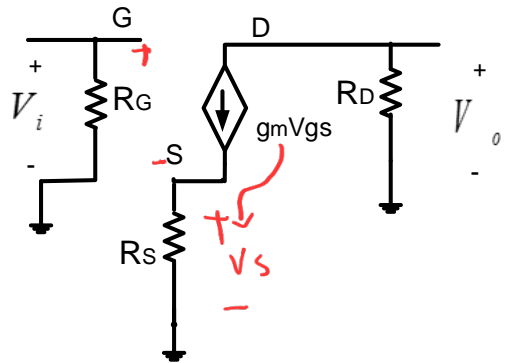

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} (R_D)}{V_{gs} + g_m V_{gs} R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$


$$|A_v| = \left| \frac{V_o}{V_i} \right| = \left| \frac{-g_m R_D}{1 + g_m R_S} \right| = 8$$

Since  $A_v$  &  $g_m$  and  $R_S$  are known, then

$$R_S = 180 \Omega \text{ (based on DC analysis)}$$

$$\therefore R_D = 3.573 \text{ k}\Omega$$

if  $r_{ds} \neq \infty$

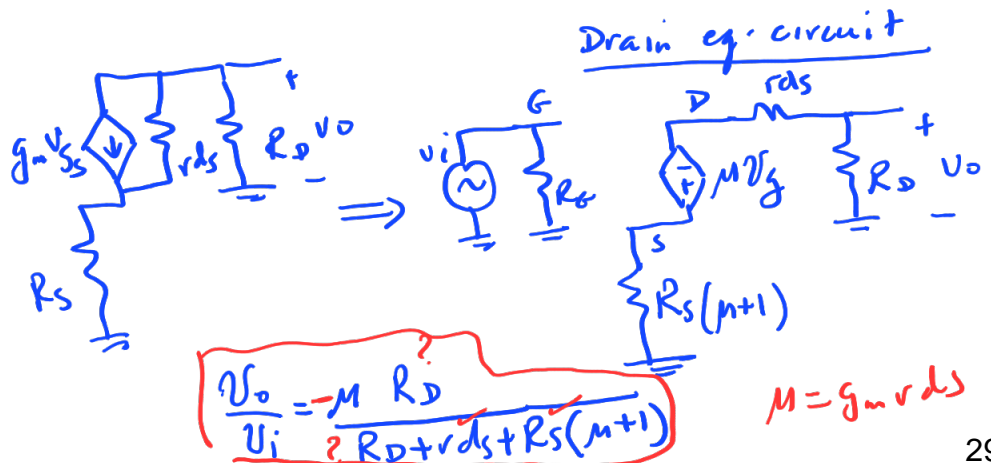

## Value of $R_S$ ?

The value of  $R_S$  is determined from DC analysis

*Given*

$$V_{GS} = V_G - V_S = \frac{1}{4} V_P = -1$$


$$V_G = 0$$


$$V_S = I_D R_S = -1$$

$$\text{but } I_D = I_{DSS} \left( 1 - \frac{-1}{-4} \right)^2 = I_{DSS} \cdot 0.5625 = 5.625 \text{ mA}$$

$$\therefore R_S = \frac{V_S}{I_D} = \frac{1 \text{ V}}{5.625 \text{ mA}} = 177.8 \text{ } \Omega$$

choose standard value  $180 \Omega$

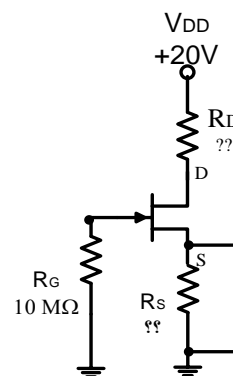

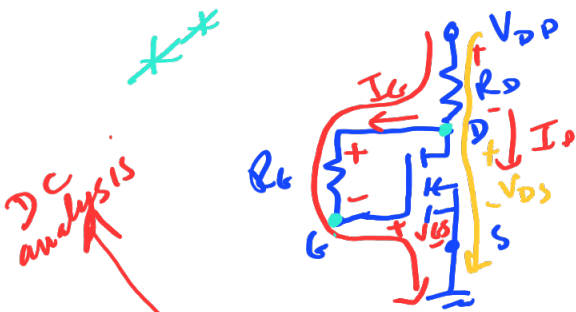

$$V_{GS} = V_G - V_S = V_{DD} - I_D R_D$$

$$V_S = 0$$

$$V_G =$$



$$V_{DD} - I_D R_D - I_G R_G - V_{GS} = 0$$

$$V_{DD} - I_D R_D - V_{DS} = 0 \Rightarrow$$

$$V_{DS} = V_{DD} - I_D R_S$$

$V_{GS} = V_{DS}$   
OR  
 $V_G = V_D$
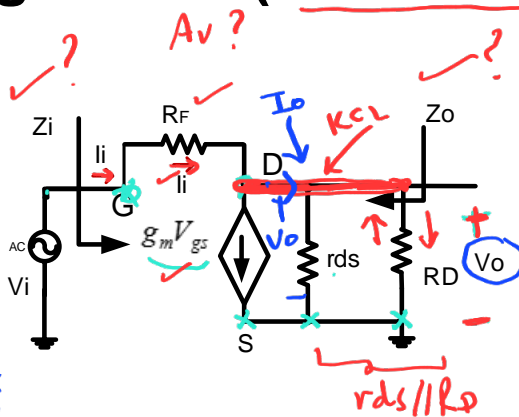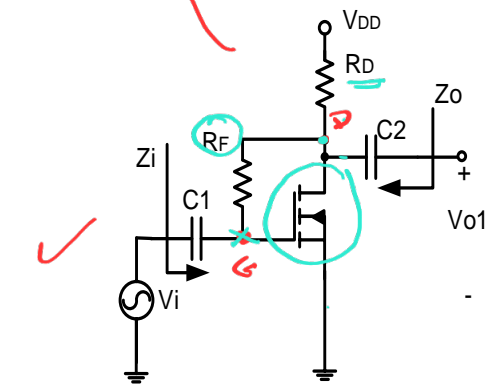
## Drain Feedback Configuration (self study)



$$A_v = \frac{V_o}{V_i}$$


KCL

$$I_i = g_m V_{gs} + \frac{V_o}{R_D // r_{ds}}$$

$V_{gs} = V_i$

$$I_i = g_m V_i + \frac{V_o}{R_D // r_{ds}}$$
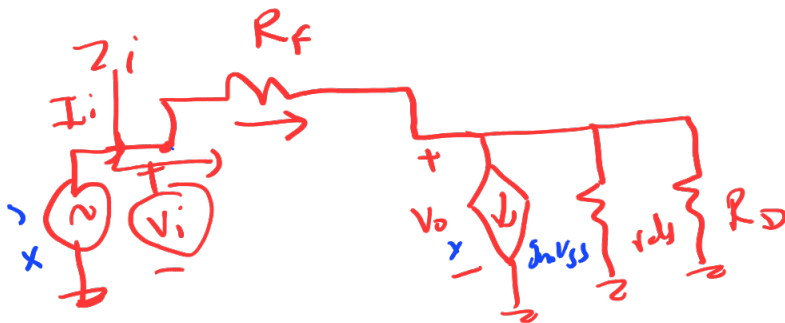
$$I_i - g_m V_i = \frac{V_o}{R_D // r_{ds}}$$



$$V_o = (I_i - g_m V_i)(R_D // r_{ds}) \quad \dots (1)$$

also

$$I_i = \frac{V_i - V_o}{R_F} \quad \dots (2)$$

$$I_i = \frac{V_i - ((I_i - g_m V_i)(R_D // r_{ds}))}{R_F}$$


$$I_i R_F = V_i - ((I_i - g_m V_i)(R_D // r_{ds}))$$

$$V_i [1 + g_m (R_D // r_{ds})] = I_i [R_F + (R_D // r_{ds})]$$

∴


$$Z_i = \frac{V_i}{I_i} = \frac{[R_F + (R_D // r_{ds})]}{[1 + g_m (R_D // r_{ds})]}$$

$$Z_i = \frac{V_i}{I_i}$$

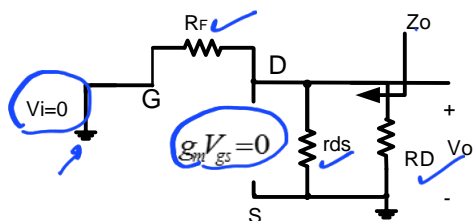

$$Z_o|_{V_i=0} = R_D // r_{ds} // R_F$$




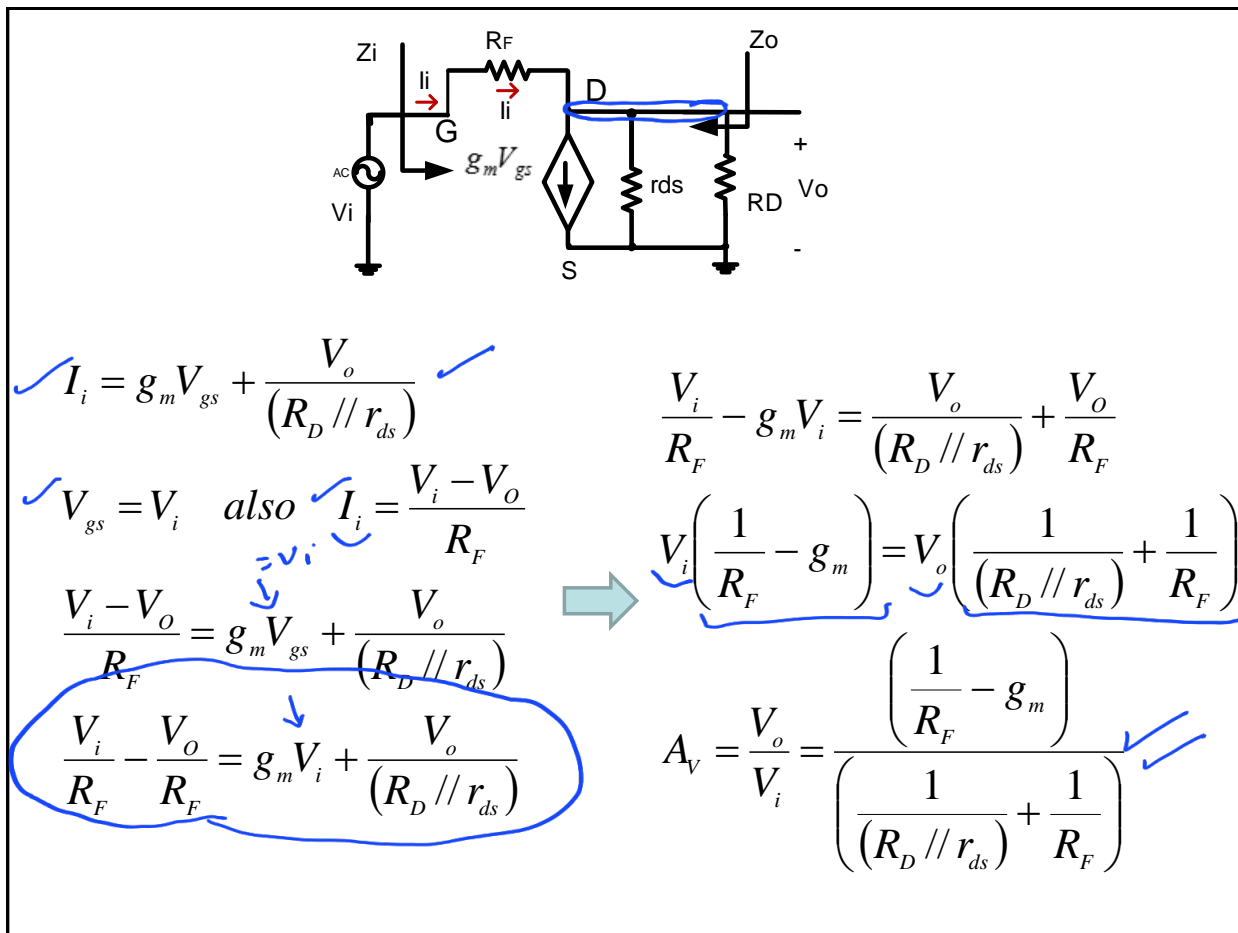

Best 3 of 4 quizzes will be counted

End of T10 FET TOPIC  
Monday 23/8  
Quiz #4  
T9 + T10

From Simulation

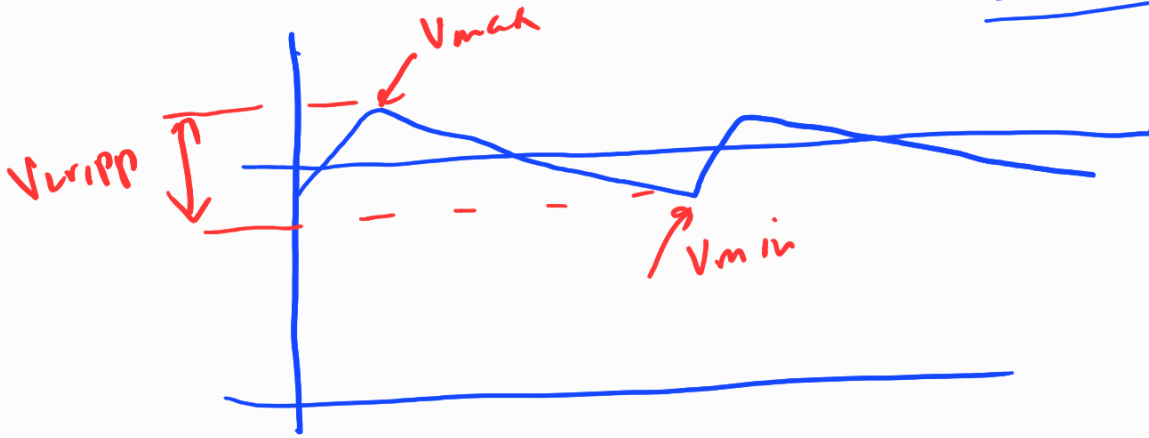

70 V ←  $V_{avg}$

80 V ? (V<sub>max</sub>)

$V_{avg} =$

$V_{Lripp} =$

✓  
5V → 4V

$$V_{rms} = \frac{V_{Lripp}}{2\sqrt{3}}$$

r % = 9

10% → 7% ✓

error 80-70=10

% error  $\frac{10}{70} \times 100\% \leq 2\%$

تقریب  
C?  
N<sub>1</sub>/N<sub>2</sub>