

L3
part 2
sec 2
8/7/2021

ENEE2360

Analog Electronics

T2:

Semiconductor Diodes and Diode Models

Instructor: Nasser Ismail

Diode Operating Conditions/Modes

A diode has three operating Modes:


- 1) No bias
- 2) Reverse bias
- 3) Forward bias

→ external
voltage
source

Diode Operating Modes

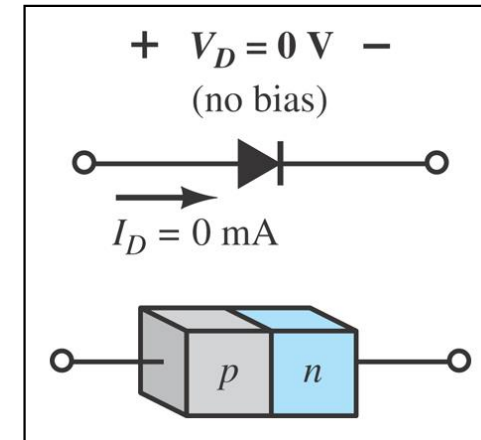
1) No Bias Condition

- No external voltage is applied: $V_D = 0 \text{ V}$
- There is no diode current: $I_D = 0 \text{ A}$
- Only a modest depletion region exists



2) Reverse Bias Condition

- External voltage is applied across the p - n junction in the opposite polarity of the p - and n -type materials.

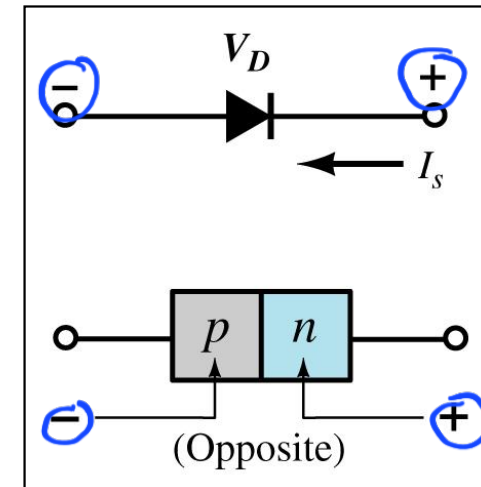


ENEE236 – Analog Electronics

Diode Operating Modes

Reverse Bias

- The reverse voltage causes the depletion region to widen.
- The electrons in the n -type material are attracted toward the positive terminal of the voltage source.
- The holes in the p -type material are attracted toward the negative terminal of the voltage source.


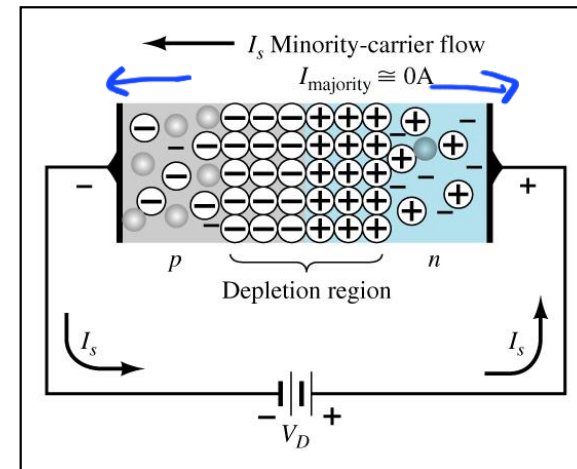


ENEE236 – Analog Electronics

Diode Operating Modes

3) Forward Bias Condition

- External voltage is applied across the p - n junction in the same polarity as the p - and n -type materials.
- The forward voltage causes the depletion region to narrow.
- The electrons and holes are pushed toward the p - n junction.
- The electrons and holes have sufficient energy to cross the p - n junction.

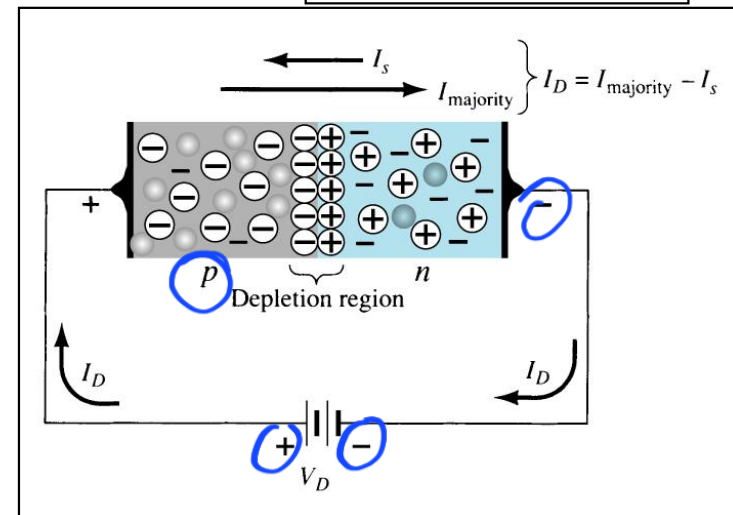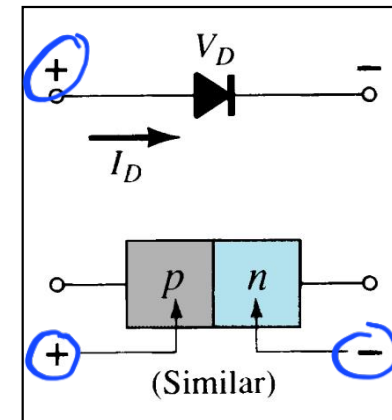


ENEE236 – Analog Electronics

Actual Diode Characteristics

Note the regions for no bias, reverse bias, and forward bias conditions.

Carefully note the scale for each of these conditions.

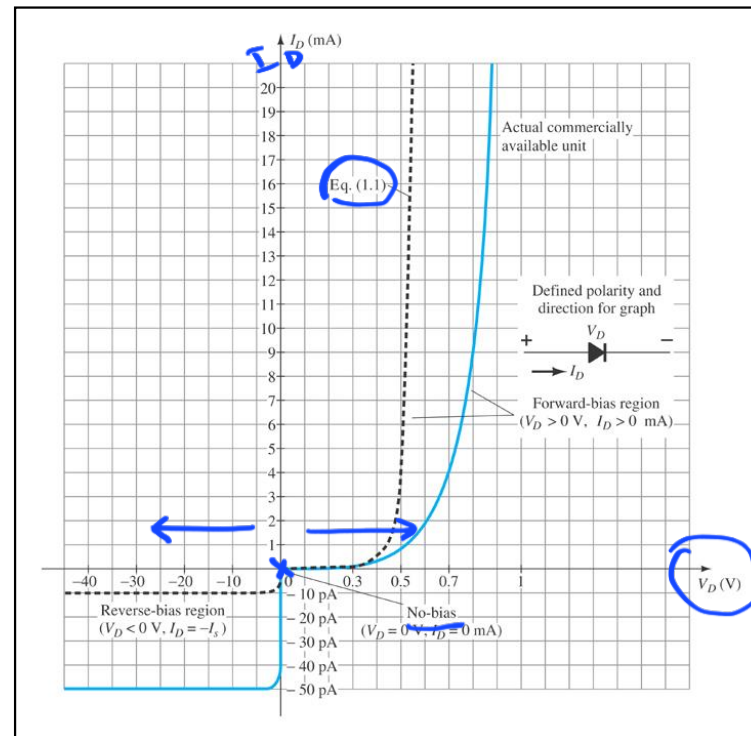

ENEE236 – Analog Electronics


Zener Region (Breakdown Region)

The Zener region is in the diode's reverse-bias region.

At some point the reverse bias voltage is so large the diode breaks down and the reverse current increases dramatically.

The maximum reverse voltage that won't take a diode into the zener region is called the **peak inverse voltage** or **peak reverse voltage**.

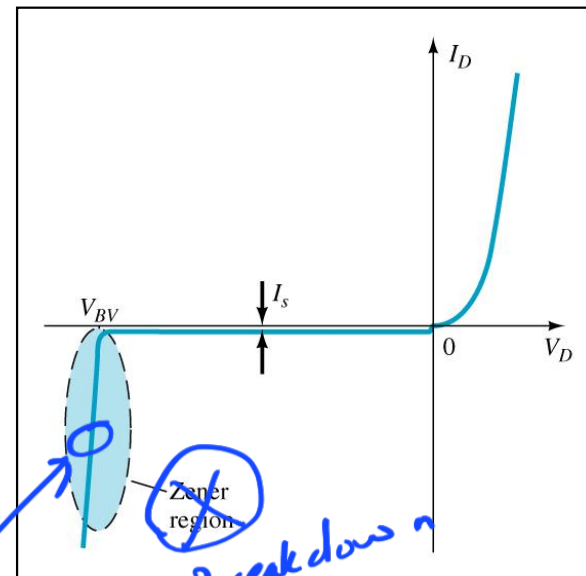The voltage that causes a diode to enter the zener region of operation is called the **zener voltage (V_Z)** or **reverse breakdown voltage (V_{BV})**.



$I \uparrow$

$I^2 R \uparrow$, heat, damage of Diode

Forward Bias Voltage

The point at which the diode changes from no-bias condition to forward-bias condition occurs when the electrons and holes are given sufficient energy to cross the p-n junction. This energy comes from the external voltage applied across the diode.

The forward bias voltage required for a:

gallium arsenide diode $\cong 1.2$ V

* \rightarrow **silicon diode $\cong 0.7$ V**

germanium diode $\cong 0.3$ V




ENEE236 – Analog Electronics

Temperature Effects

As temperature increases it adds energy to the diode.

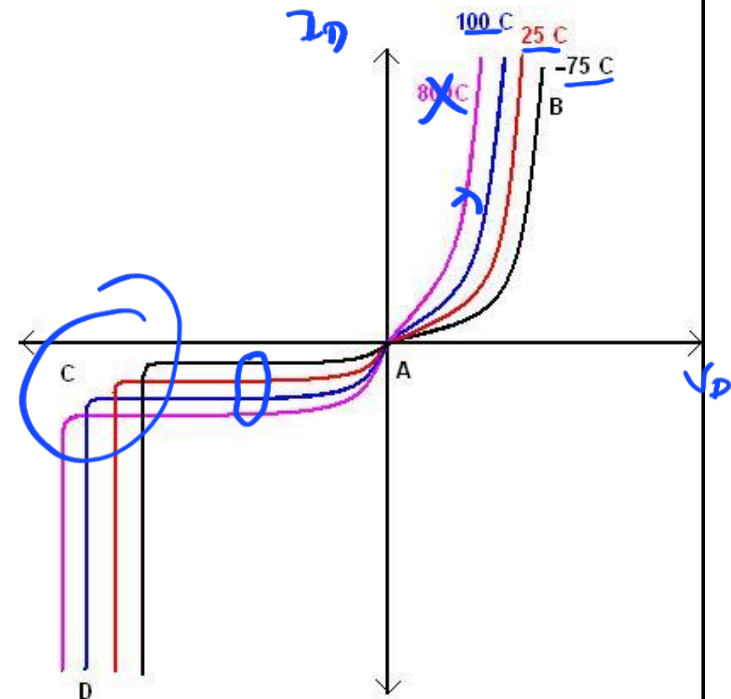- It reduces the required forward bias voltage for forward-bias conduction.
- It increases the amount of reverse current in the reverse-bias condition.
- It increases maximum reverse bias avalanche voltage.



$$P = I^2 R$$

Germanium diodes are more sensitive to temperature variations than silicon or gallium arsenide diodes.

Diode Internal Resistance

Semiconductors react differently to DC and AC currents.

There are three types of resistance:


DC (static) resistance

AC (dynamic) resistance ✓✓

Average AC resistance

| Resistance Levels | | | |
|-------------------|---|---|-------------------------|
| Type | Equation | Special Characteristics | Graphical Determination |
| DC or static | $R_D = \frac{V_D}{I_D}$ | Defined as a point on the characteristics | |
| * AC or dynamic | $r_d = \frac{\Delta V_d}{\Delta I_d} = \frac{26 \text{ mV}}{I_D} = V_T$ | Defined by a tangent line at the <u>Q-point</u> | |
| Average ac | $r_{av} = \frac{\Delta V_d}{\Delta I_d} \Big _{\text{pt. to pt.}}$ | Defined by a <u>straight</u> line between limits of operation | |

semiconductor physics

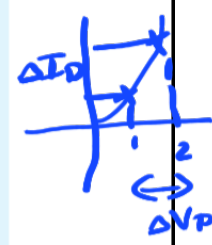

Diode Equation

$$i_D(t) = I_S \left(e^{\frac{V_D(t)}{\eta V_T}} - 1 \right)$$

I_S : Reverse saturation current



$$I_S = 10^{-12}, 10^{-14} \text{ A}$$

η : eta

$$1 \leq \eta \leq 2$$

for example
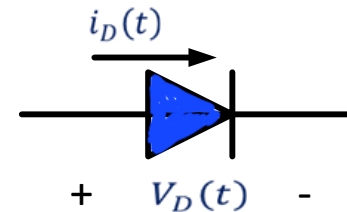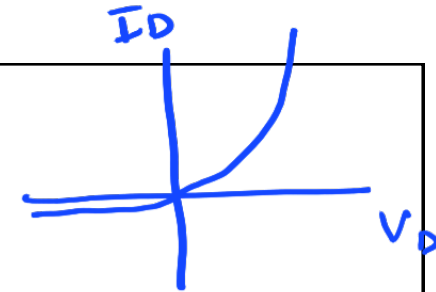
$$\eta = \begin{cases} 1 & \text{for Ge} \\ 2 & \text{for Si (small current)} \\ 1 & \text{for Si (large current)} \end{cases}$$



V_T = Thermal Voltage

$$V_T = \frac{T}{11600} \quad ; T \text{ in kelvin}$$

At Room Temp. $T = 298$ k
25°C

$\therefore V_T = 25.69 \text{ mv at Room Temp.}$

- The equation is a non linear equation
- \therefore The Diode is non linear Device

► For positive $V_D(t)$,

$$i_D(t) = I_S (e^{\frac{V_D(t)}{\eta V_T}})$$

► For negative $V_D(t)$

$$i_D(t) = -I_S$$


Handwritten:
 $0^\circ C \rightarrow 273 K$
 $25^\circ C \rightarrow 298 K$
 $V_T = \frac{298}{11600} \approx 25.69 \text{ mV}$

$$i_D(t) = I_S (e^{\frac{V_D(t)}{\eta V_T}} - 1)$$


Handwritten: $\ll 1$




Diode V-I Characteristic curve

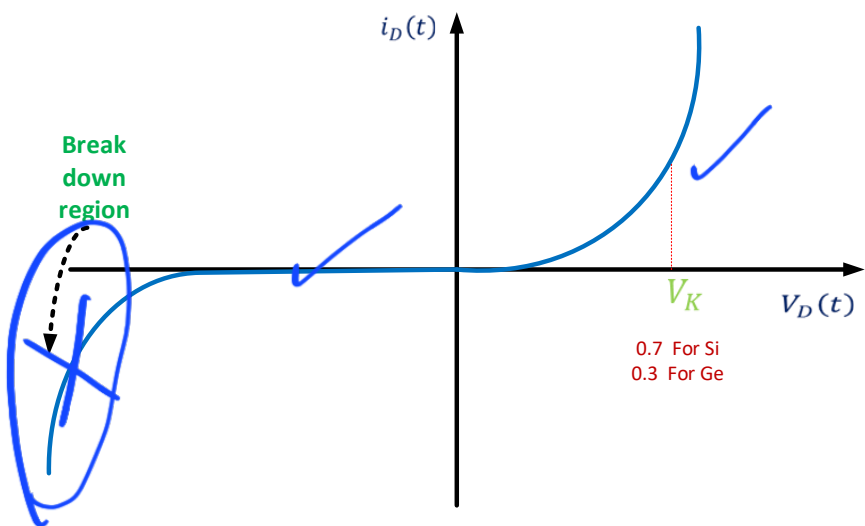

0.7 For Si
0.3 For Ge

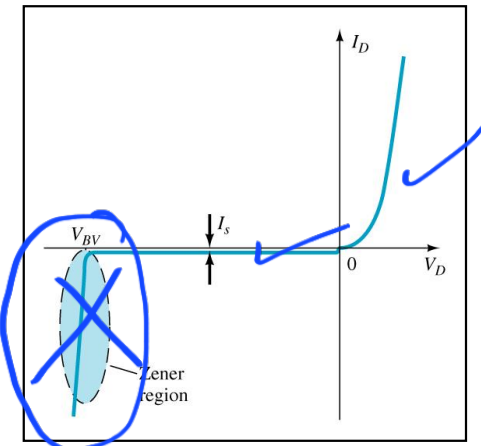

Practical circuit to measure diode curve

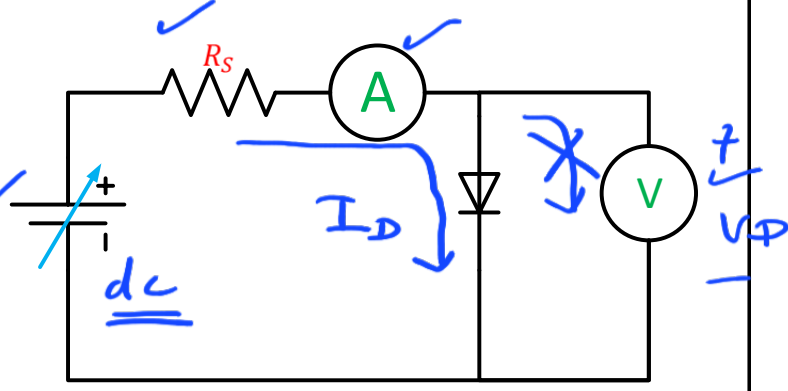

Approaches to Diode Circuit Analysis

The rectifier diode is a non linear device .


Find I_D
 V_D ?

There are essentially **three** basic approaches to the solution of such problem :

- 1- The use of non linear mathematics ✗
- 2- The use of graphical techniques ✓
- 3- The use of equivalent circuit (models) ≡ *

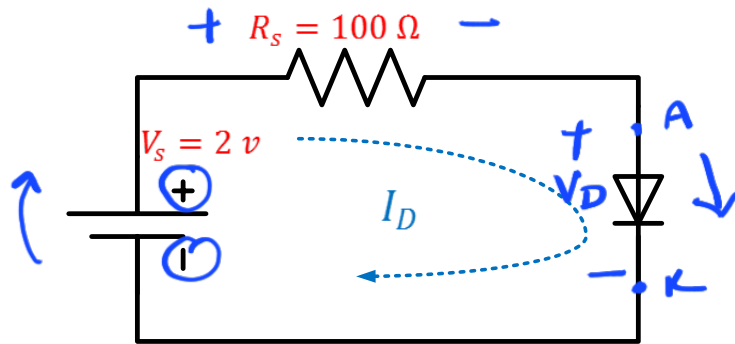1) The use of non linear mathematic (shown , but not required)

► For the circuit shown, find I_D and V_D



Silicon:
 $\eta = 1.1$
 $I_S = 10^{-14} \text{ A}$

► KVL : $V_S = R_S I_D + V_D$... (1)
 $I_D = I_S (e^{\frac{V_D}{\eta V_T}} - 1)$... (2)

► Since the diode is **forward biased** , we could approximate

$$I_D = I_S (e^{\frac{V_D}{\eta V_T}}) \rightarrow \frac{I_D}{I_S} = e^{\frac{V_D}{\eta V_T}}$$

► Solving for $V_D = \eta V_T \ln \frac{I_D}{I_S}$...

$$\ln \frac{I_D}{I_S} = \frac{V_D}{\eta V_T}$$

∴ We have two equations and two unknowns

$$V_S = R_S I_D + V_D \dots\dots\dots 1 \leftarrow$$

$$V_D = \eta V_T \ln \frac{I_D}{I_S} \dots\dots\dots 2$$

$$\therefore V_S = R_S I_D + \eta V_T \ln \frac{I_D}{I_S} \quad \checkmark$$

- **non linear equation**

Iterative Analysis

1) Let $V_D = 0.7\text{V}$

$$I_D = \frac{2 - 0.7}{0.1k} = 13\text{ mA}$$

$V_D = 0.7882392\text{V}$ The error is large

→ 2) Let $V_D = 0.7882392\text{V}$

$$I_D = 12.117608\text{ mA}$$

$V_D = 0.7862529\text{V}$ The error is small

2) $I_D = \frac{V_S - V_D}{R_S}$

3) $V_D = \eta V_T \ln \frac{I_D}{I_S}$

$$\frac{0.088}{0.7}$$

$$\frac{0.0020}{0.788}$$

3) Let $V_D = 0.7862529\text{v}$

$$I_D = 12.137471 \text{ mA}$$

$V_D = 0.7862991 \text{ V}$ The error getting smaller

4) Let $V_D = \underline{0.7862991 \text{ V}}$

$$V_D = \underline{0.786298066 \text{ V}}$$

$$I_D = \underline{12.137009\text{mA}}$$


$$I_D = 12.137 \text{ mA}$$

$$V_D = 0.7863\text{v}$$

للعلم فقط

2) The use of graphical techniques

(Requires the V-I exact plot)

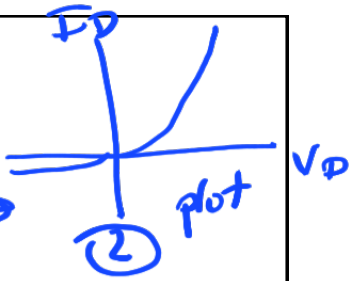


✓ ✓ ? ?

$$V_S = R_S I_D + V_D$$

$$I_D = I_S \left(e^{\frac{V_D}{\eta V_T}} - 1 \right)$$

- Using equation 1
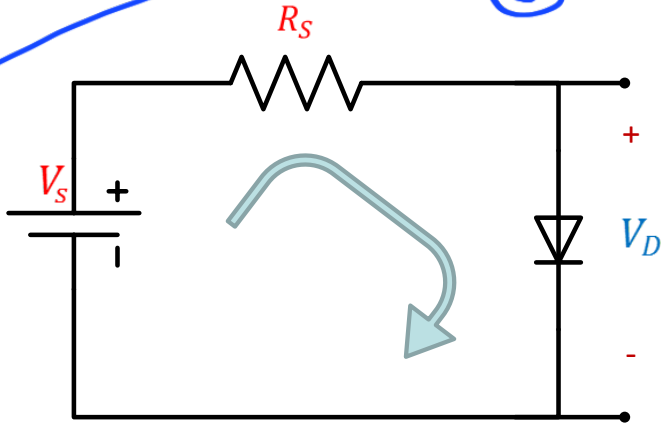
$$I_D = -\frac{1}{R_S} V_D + \frac{V_S}{R_S}$$



$I_D = f(V_D)$.. plot


$$I_D = \frac{V_S - V_D}{R_S}$$

$$= \frac{V_S}{R_S} - \frac{V_D}{R_S}$$

$I_D = f(V_D)$


$$I_D = -\frac{1}{R_S} V_D + \frac{V_S}{R_S}$$

Drawing the two equations

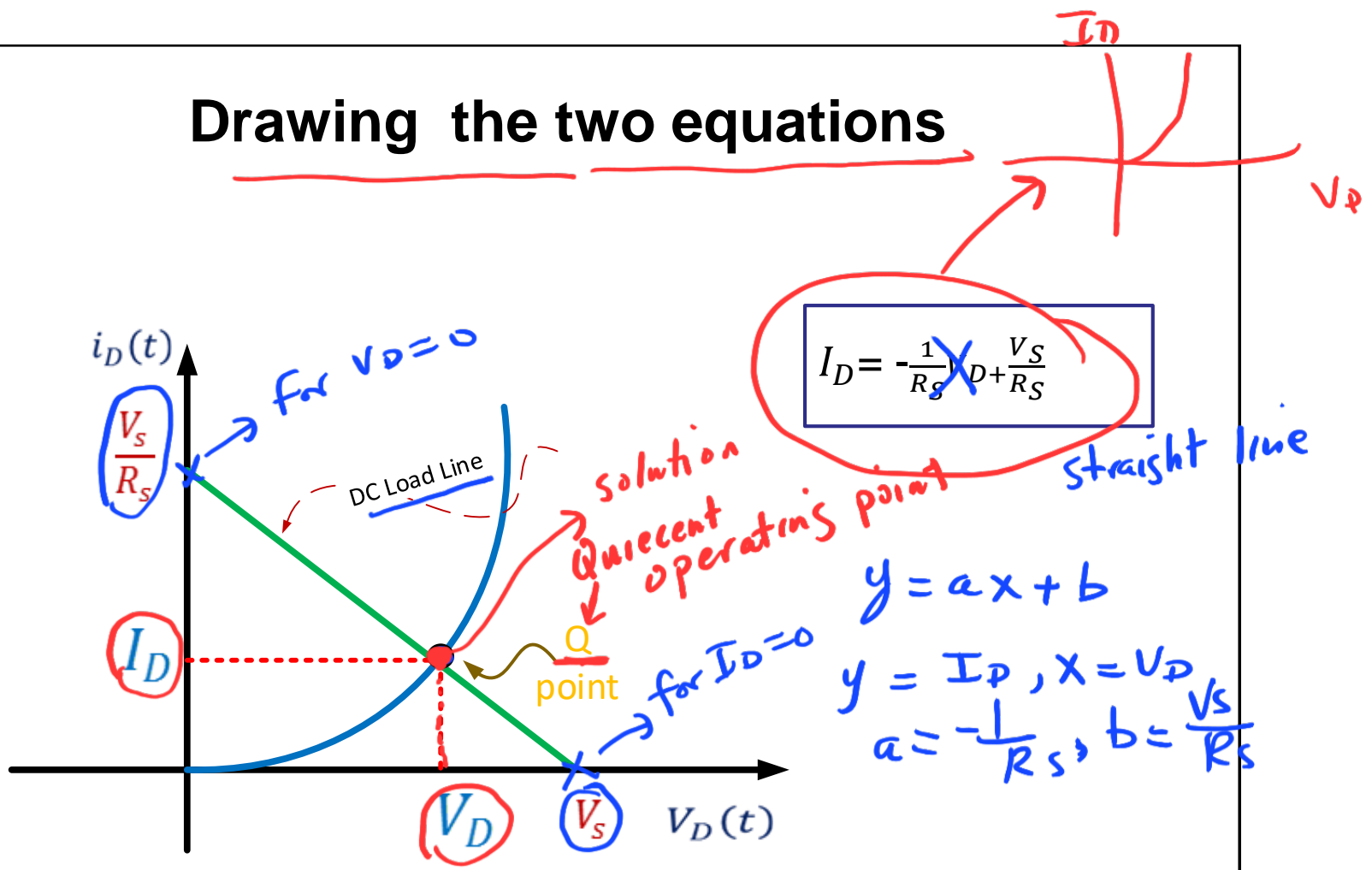


- $Q_{\text{point}} = (V_{DQ}, I_{DQ}) = Q_{\text{quiescent point}}$

The effect of R_s on the Qpoint

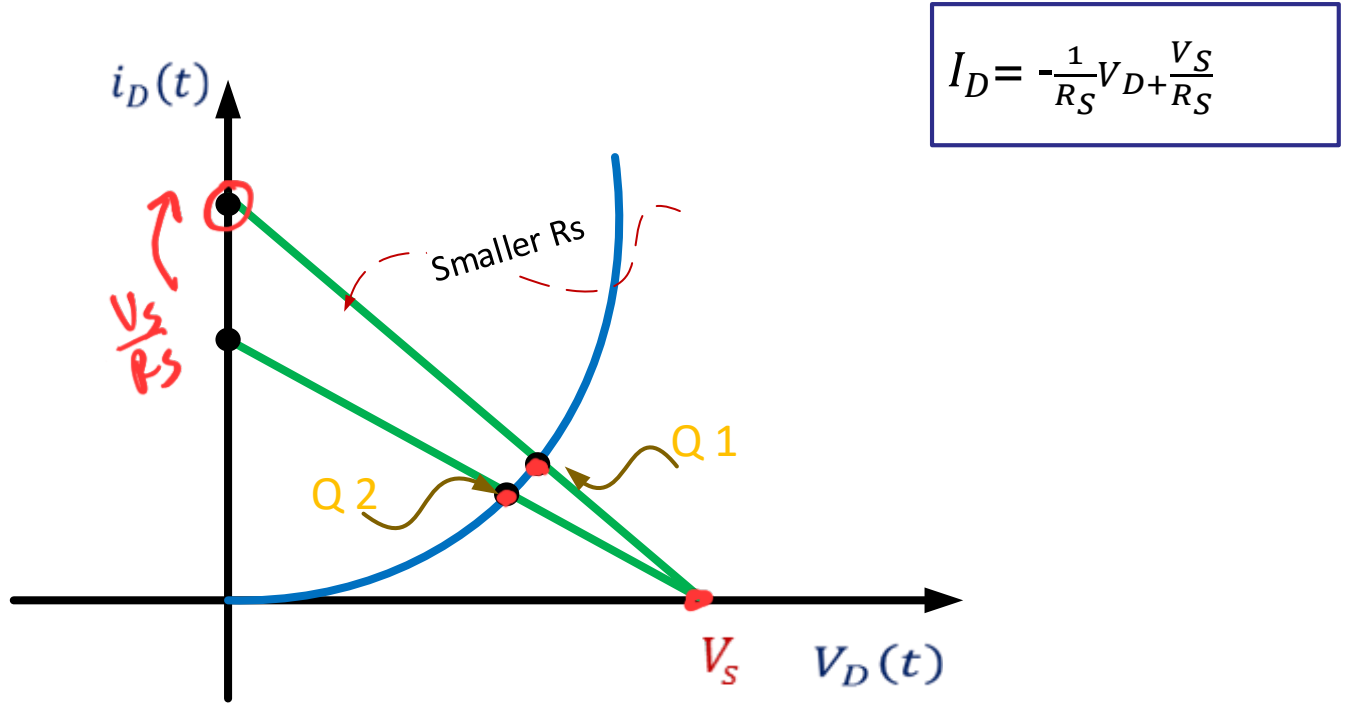



The effect of V_s on Qpoint

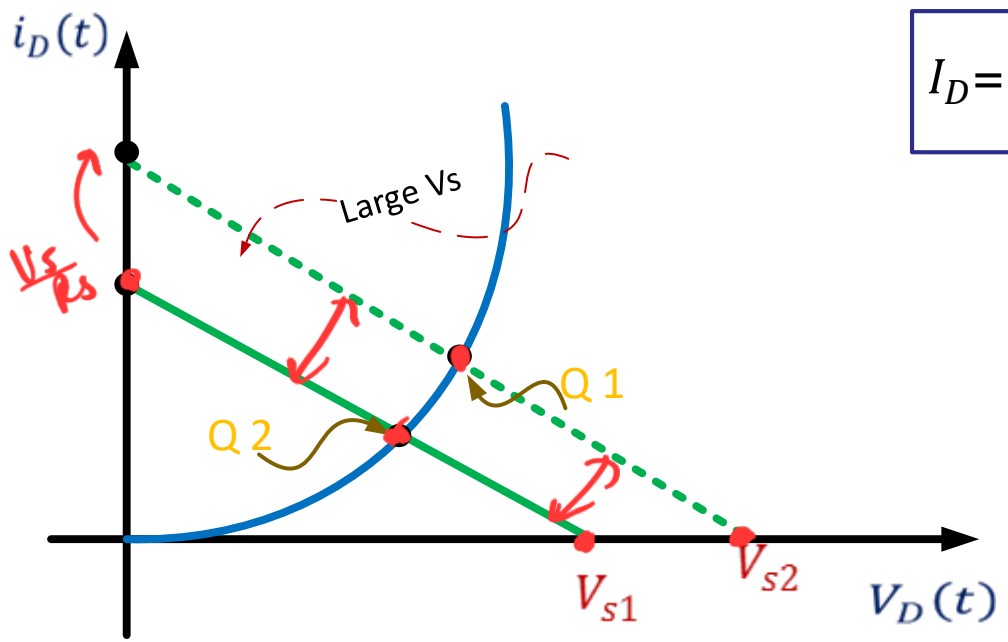

$$I_D = -\frac{1}{R_S}V_D + \frac{V_S}{R_S} \quad \checkmark$$

Diode (Models) ***

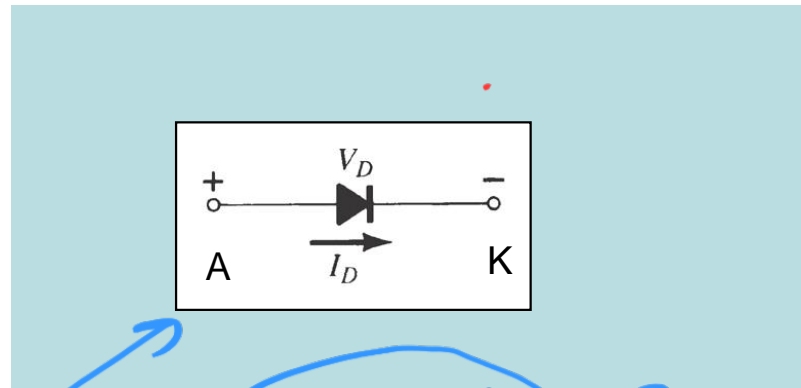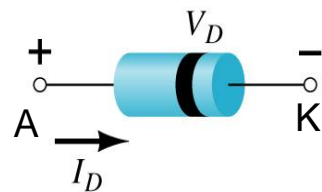- 1) Ideal Diode Model ✓✓
- 2) Simplified/piecewise/ knee model ✓✓
Linear
- 3) Complete diode model ✗ *Practical Model*




- Forward
- Reverse ?

ENEE236 – Analog Electronics

Ideal Diode Model



- 1) if the diode is forward biased ==> diode is replaced by short circuit

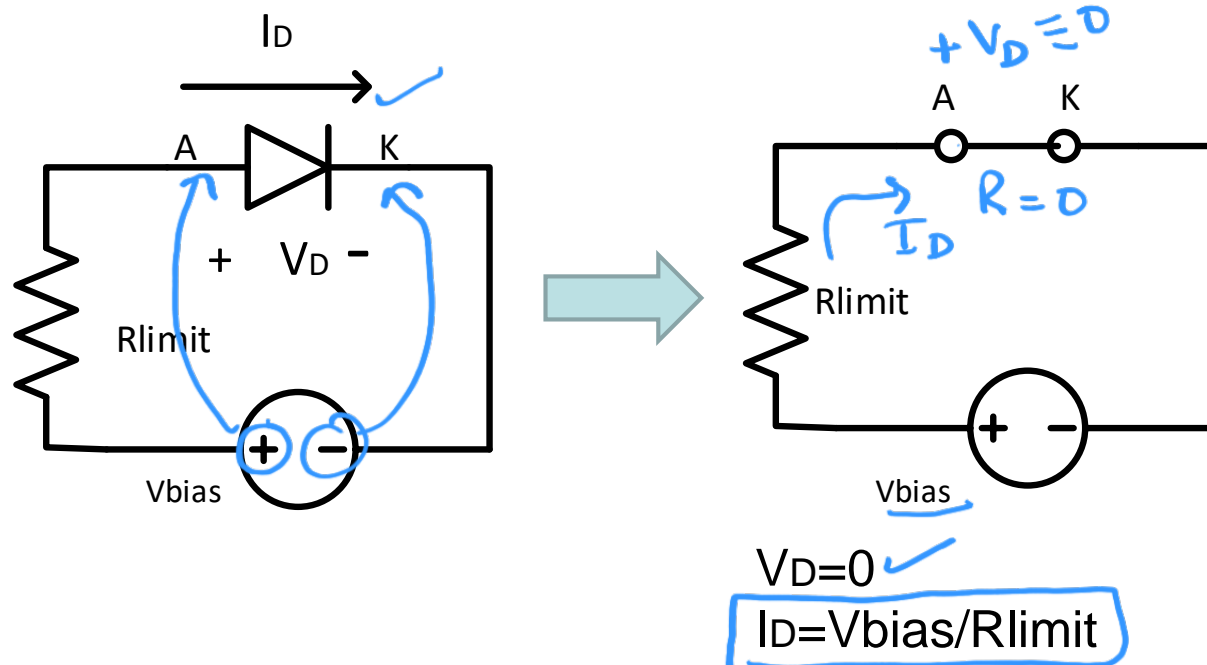

ENEE236 – Analog Electronics

Ideal Diode Model

- 2) if the diode is Reverse biased ==> diode is replaced by open circuit

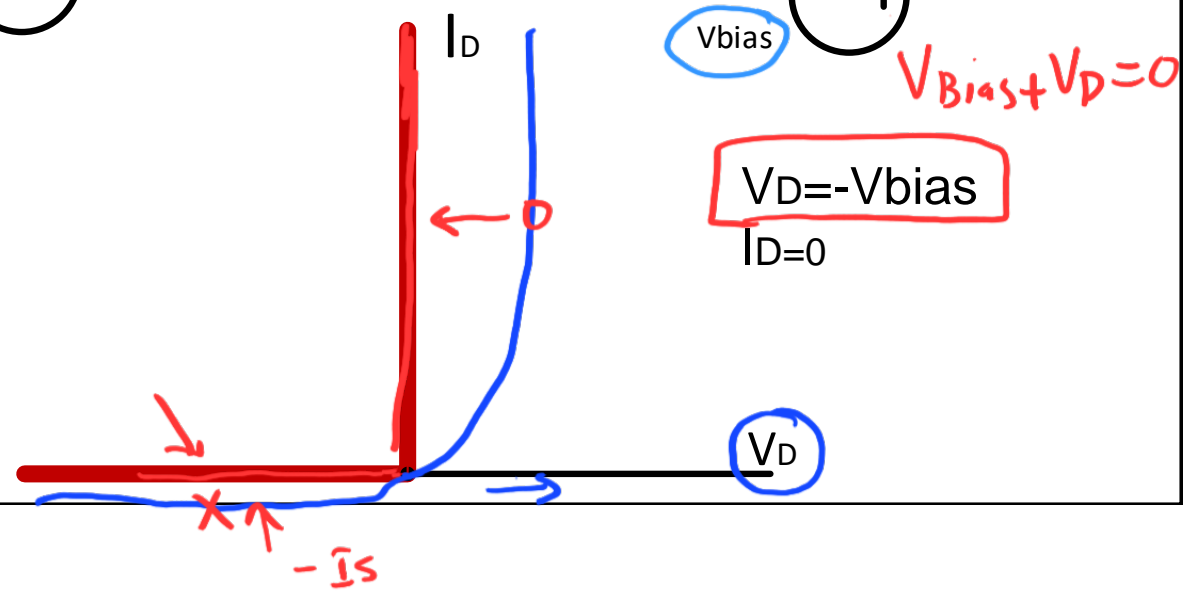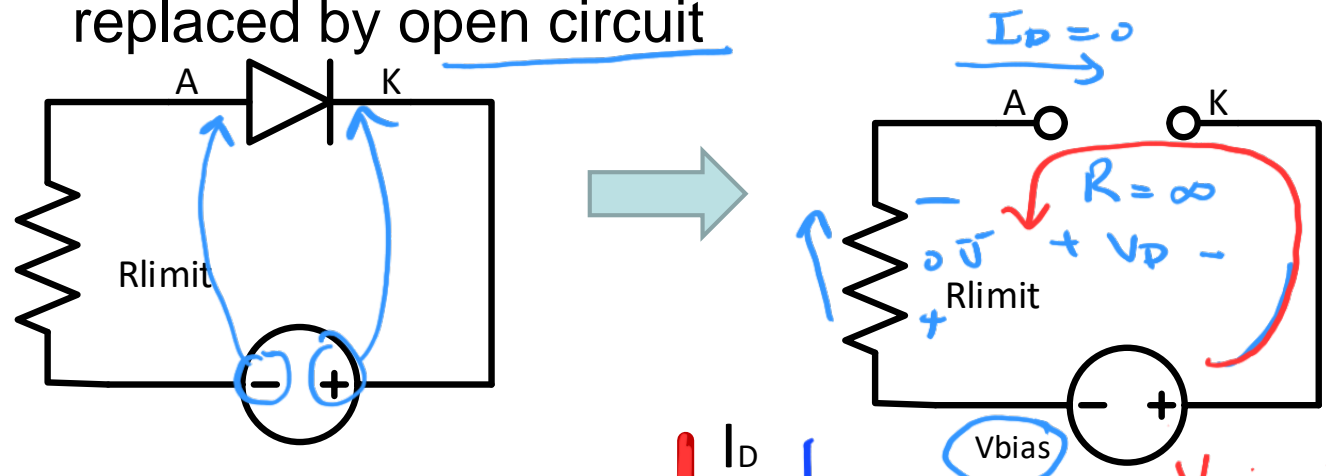


ENEE236 – Analog Electronics

Simplified / knee model

Practical

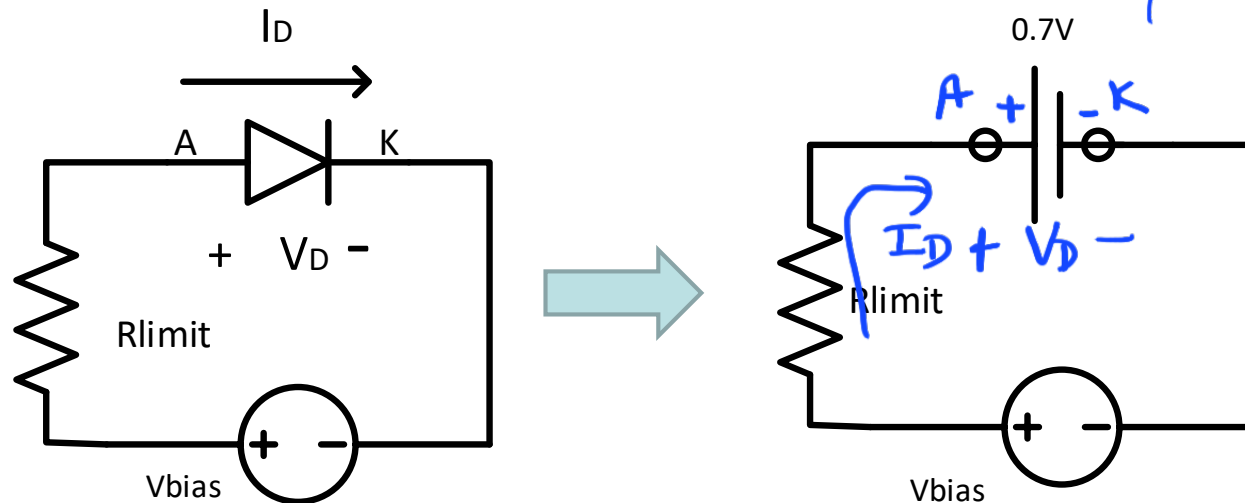- 1) if the diode is forward biased ==> diode is replaced by a 0.7V battery (for Si)




$$V_D = 0.7 \text{ V}$$

$$I_D = (V_{bias} - 0.7) / R_{limit}$$

ENEE236 – Analog Electronics

Simplified/ knee model


- 2) if the diode is Reverse biased ==> diode is replaced by open circuit (same as ideal model)

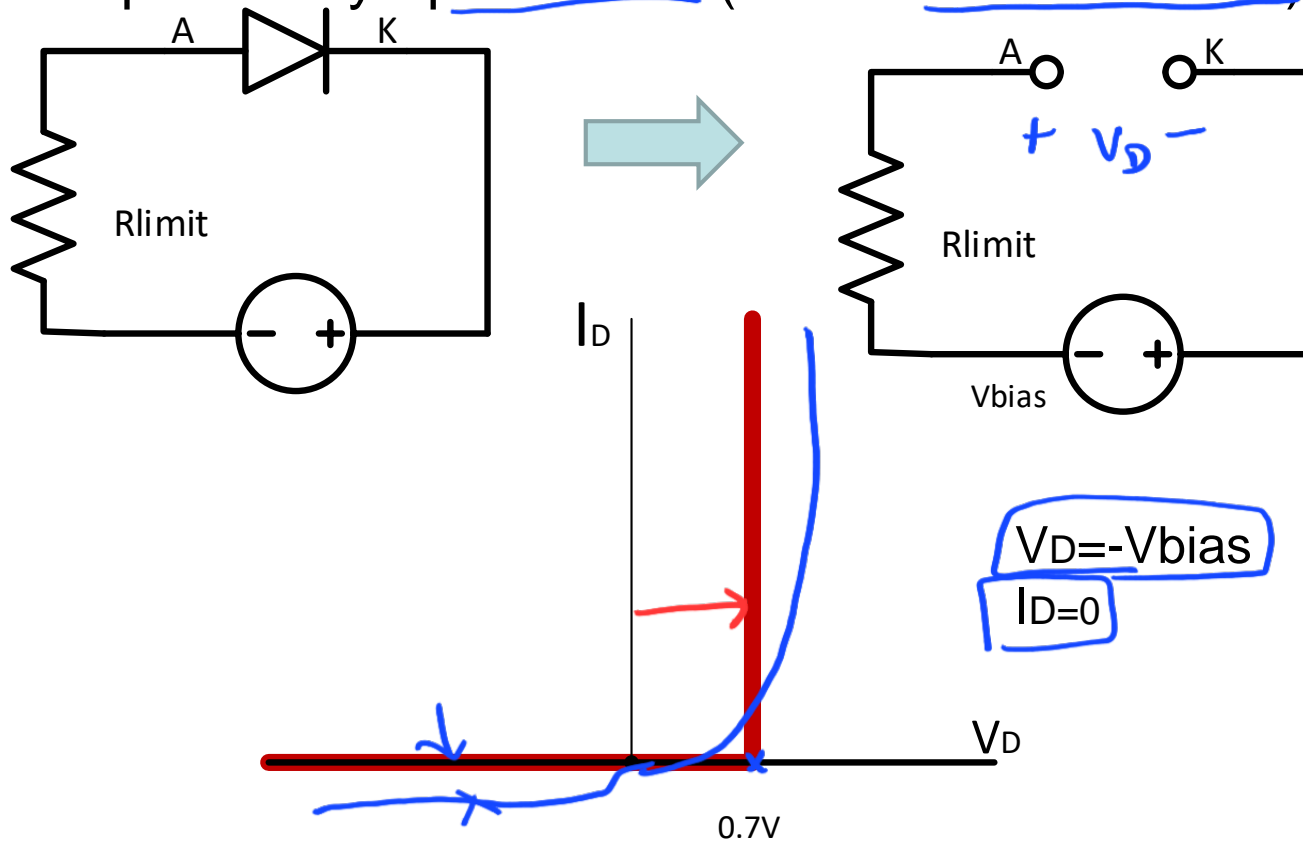

ENEE236 – Analog Electronics

Complete Diode model

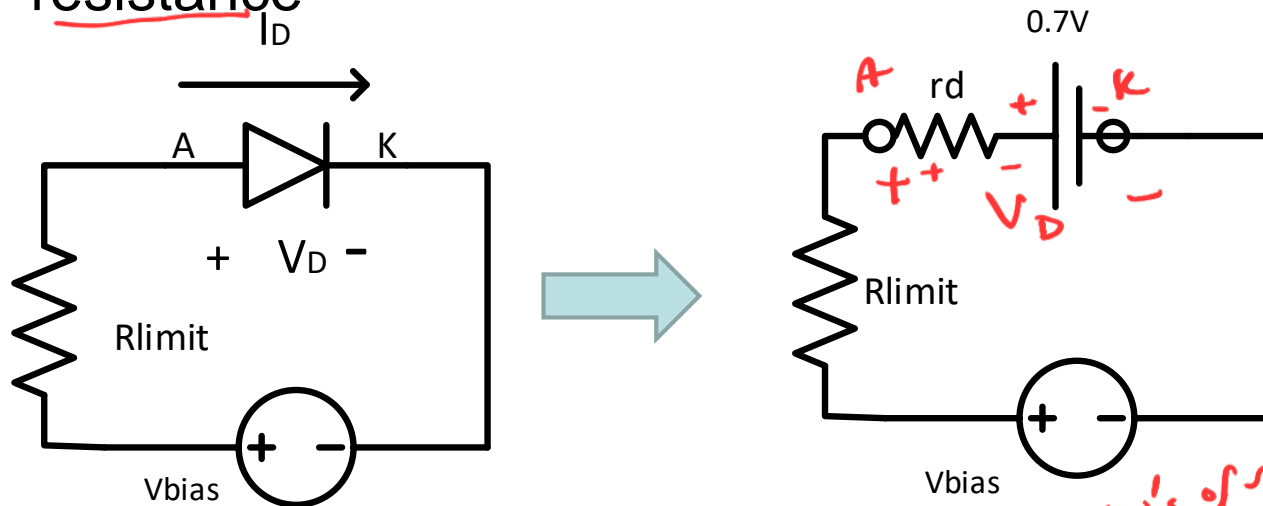- 1) if the diode is forward biased ==> diode is replaced by a 0.7V battery and forward dynamic resistance






$V_D = 0.7 + I_D \cdot r_d$
 $I_D = (V_{bias} - 0.7) / (R_{limit} + r_d)$

100's of \$\Omega\$'s
small \$\Omega\$'s

ENEE236 - Analog Electronics

Complete Diode model

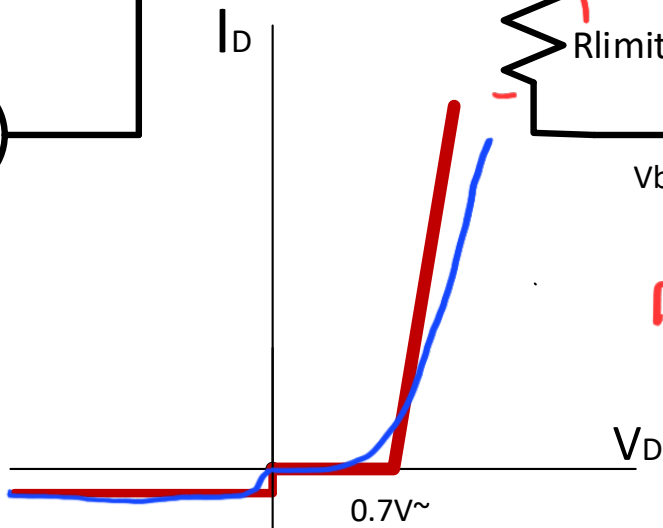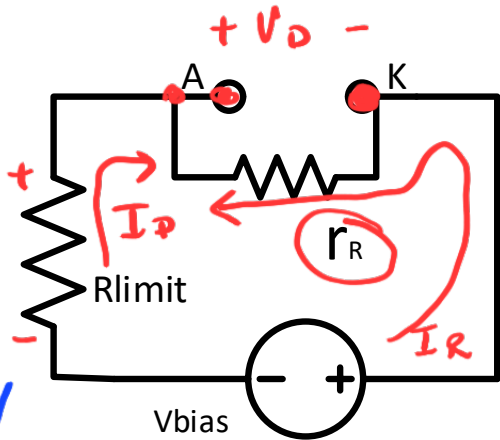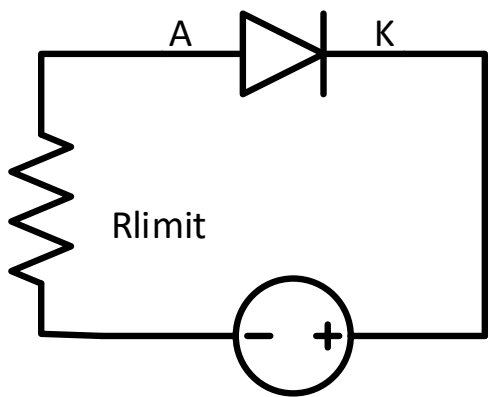- 2) if the diode is Reverse biased ==> diode is replaced by open circuit // to reverse resistance r_R



$V_D \approx -V_{bias}$
 $I_D = -I_R$
 $r_R \gg R_{limit}$
 \uparrow
 M's
 $V_{bias} + V_D - I_R \cdot R_{limit} = 0$

r_R
 not r_d

End of L3 8/7/2021

Diode Model

Ideal Practical Complete

Start of LY
13/7/2021



ENEE236 - Analog Electronics

Example:

Find the Q-point (I_{DQ} and V_{DQ})

- a) Use ideal diode model
- b) Use practical diode model
- c) Use exact model

Forward?
Reverse?

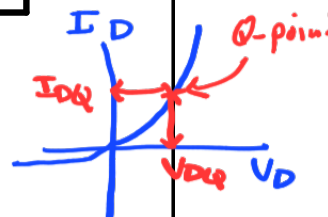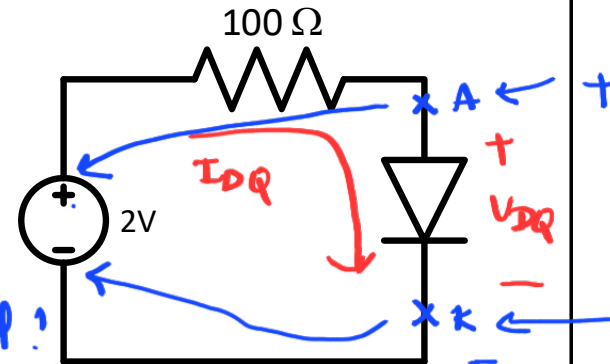


Forward Biased \equiv ON
Reverse " \equiv off

Solution

a) Since $V_A > V_K$, diode is forward biased (ON) \implies it can be replaced by a short circuit

$V_{DQ} = V_{AK} = 0 \text{ V}$ ✓

$I_{DQ} = 2\text{V} / 100 \Omega = 20 \text{ mA}$ ✓

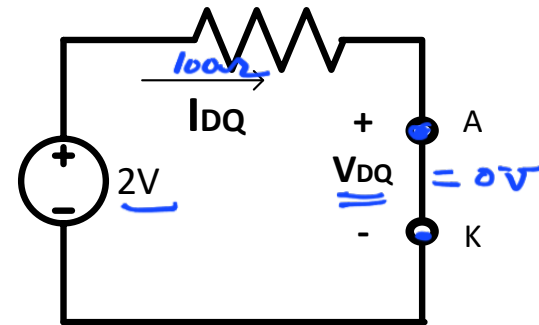


ENEE236 – Analog Electronics

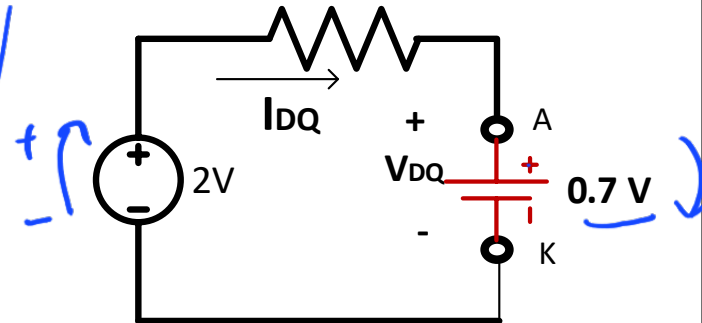b) When using practical model, diode is replaced by a 0.7 V battery

$$V_{DQ} = V_{AK} = 0.7 \text{ V}$$

$$I_{DQ} = (2 - 0.7) / 100 = 13 \text{ mA}$$



c) Exact solution yields

$$V_{DQ} = V_{AK} = 0.786 \text{ V}$$

$$I_{DQ} = 12.14 \text{ mA}$$

~ 0.7 V

Note: If applied voltage is much higher than V_{AK} (at least 10 times), then ideal diode model is recommended


ENEE236 – Analog Electronics

Example:

Find the Q-point

(I_{DQ} and V_{DQ})

Solution

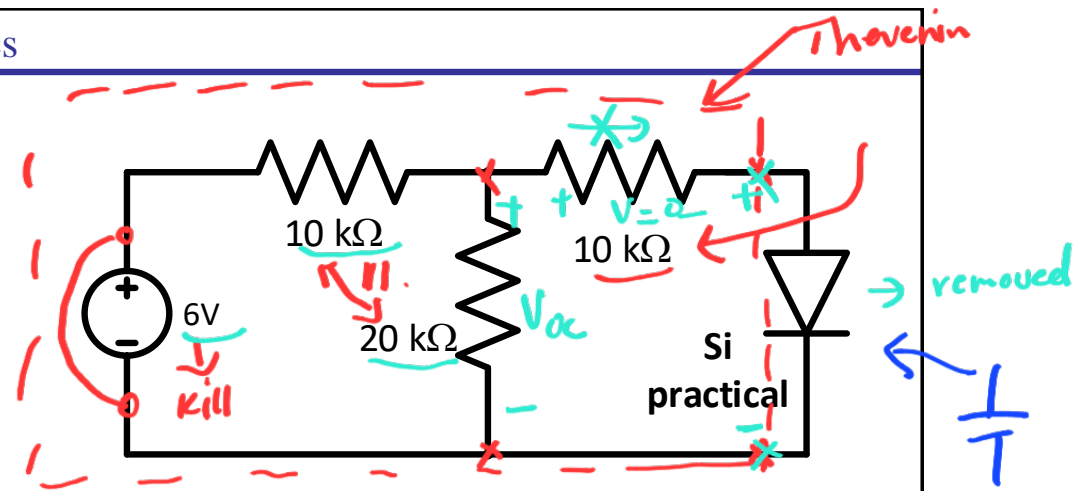


It is better to convert the two loop circuit to a single loop circuit by finding Thevenin's equivalent circuit

$V_{TH} = 6V \cdot \frac{20k}{20k+10k} = 4V$

$R_{TH} = (10k + (20k // 10k)) = 16.67k\Omega$


$V_{DQ} = V_{AK} = 0.7V$

$I_{DQ} = (4 - 0.7) / 16.67k\Omega = 0.198mA$

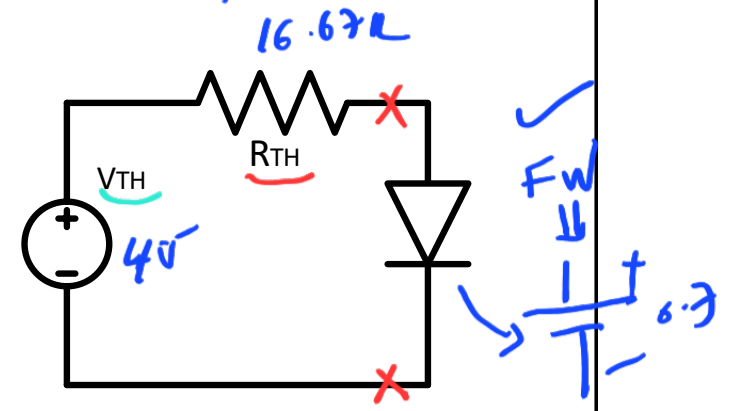

ENEE236 - Analog Electronics

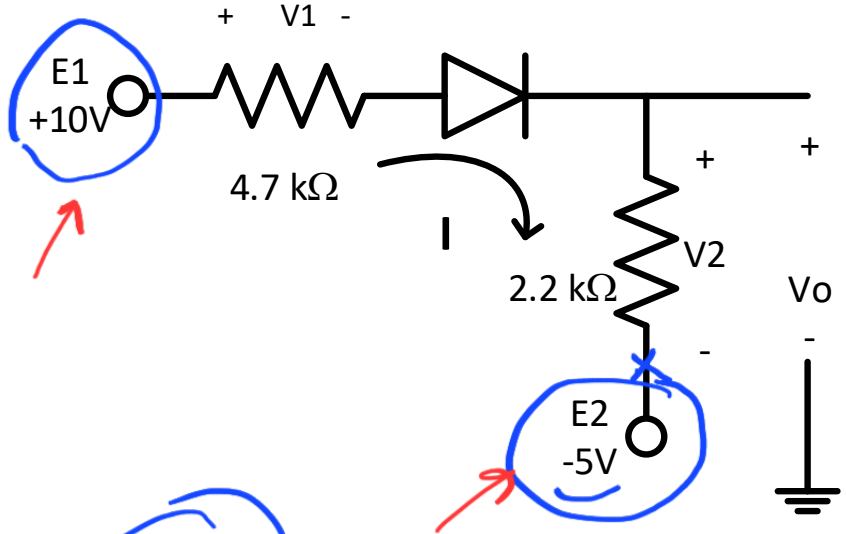Example: Find I, V_1, V and V_o (use simplified model)







E_1
+10V



+10V

?

Solution:

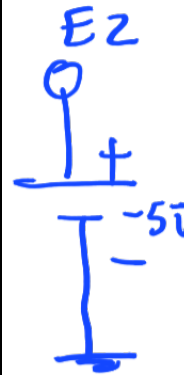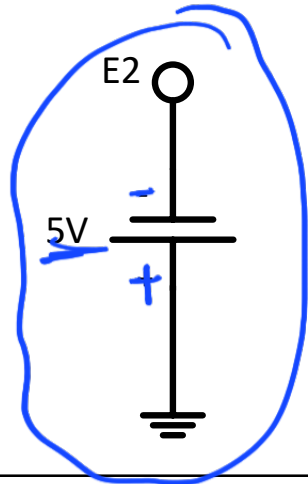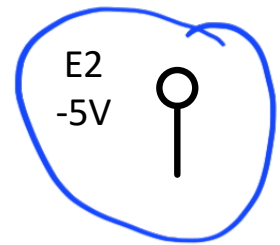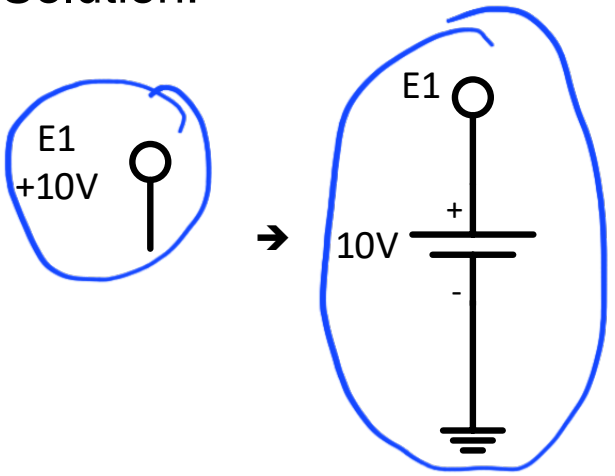

ENEE236 - Analog Electronics

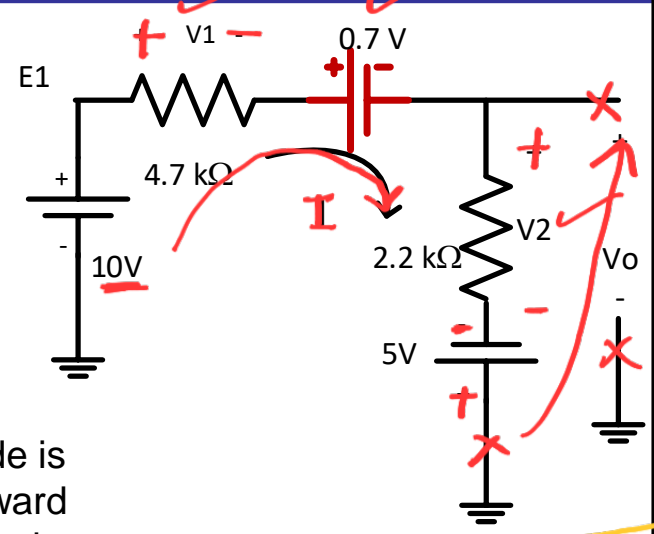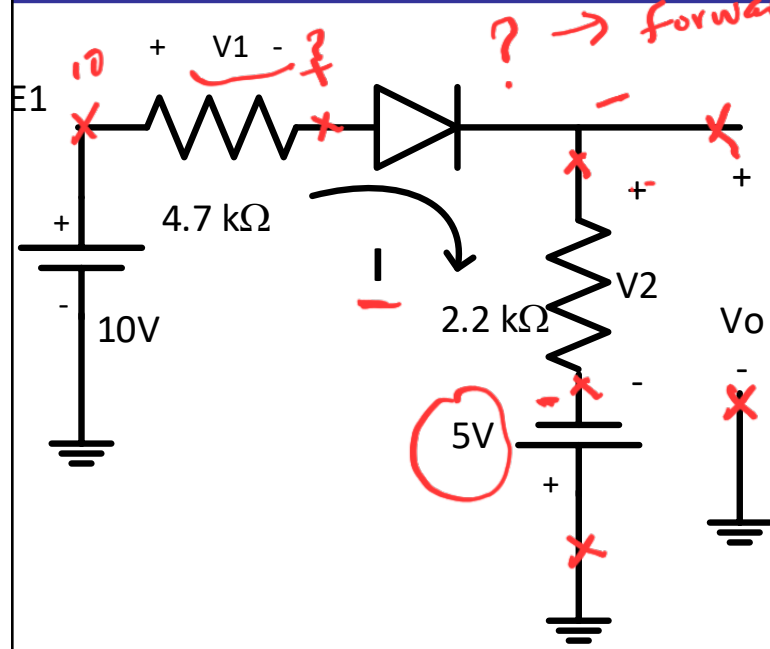

==>
Diode is
Forward
biased

Since $V_A > V_K$

$$10 + 5 = I \cdot 4.7k + 0.7 + I \cdot 2.2k$$

$$I = \frac{15 - 0.7}{6.9k} = 2.07mA$$

$$I = (10 + 5 - 0.7)V / (4.7 + 2.2) k\Omega = 2.07 mA$$

$$V1 = I \cdot R1 = 9.73 V = 2.07mA \times 4.7k$$

$$V2 = I \cdot R2 = 4.55 V = 2.07mA \times 2.2k$$

$$V_o = V2 - 5 = -0.45 V$$

ENEE236 – Analog Electronics

Find I_1 , I_2 , I_{D2} (use practical diode model)

Solution:



Applied voltage is suitable for forward biasing both diodes

$I_1 = 0.7 \text{ V} / 3.3 \text{ k}\Omega$
 $= 0.212 \text{ mA}$

$I_2 = (20 - 0.7 - 0.7) / 5.6 \text{ k}\Omega$
 $= 3.32 \text{ mA}$


$I_2 = I_1 + I_{D2}$

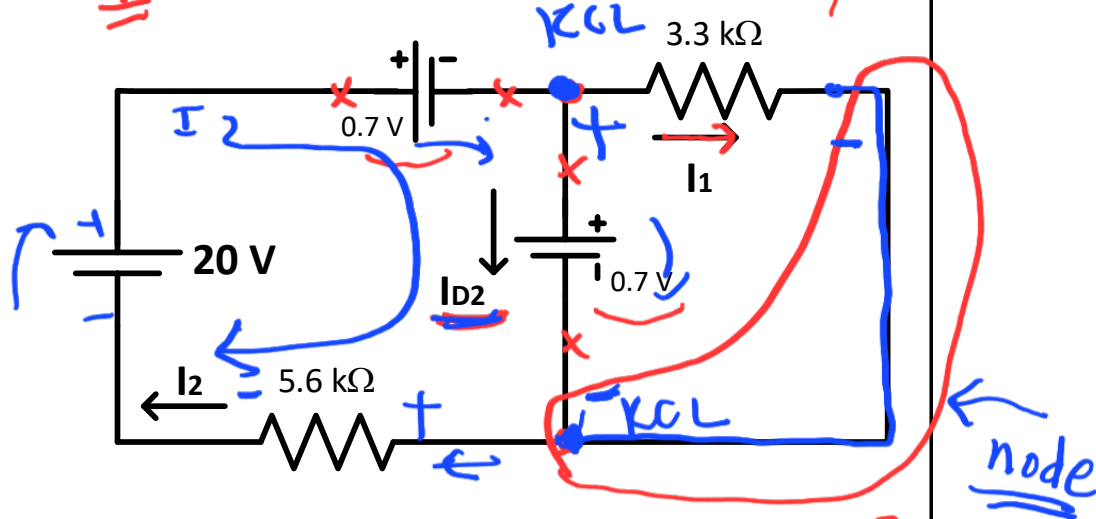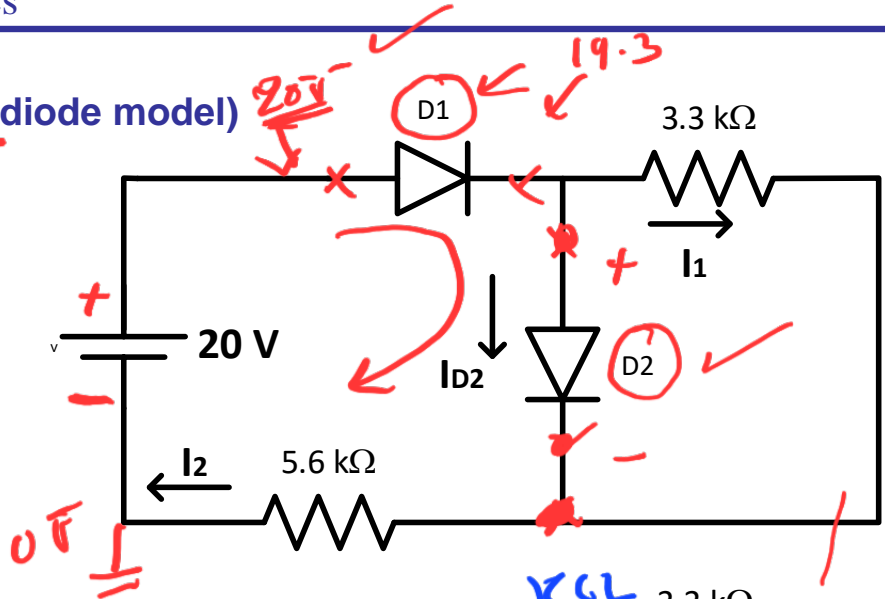$I_{D2} = I_2 - I_1 = 3.32 - 0.212$
 $= 3.11 \text{ mA}$



$I_1 = \frac{0.7}{3.3 \text{ k}}$

Diode Specification Sheets

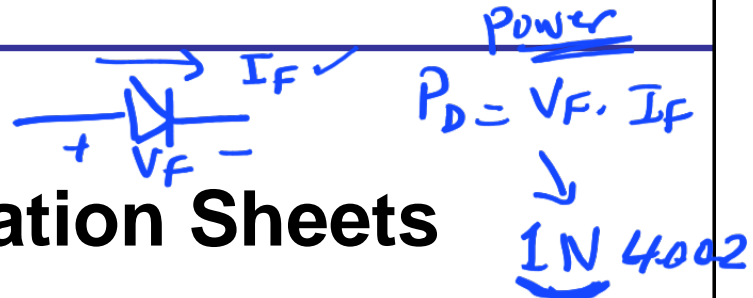


Diode data sheets contain standard information, making cross-matching of diodes for replacement or design easier.

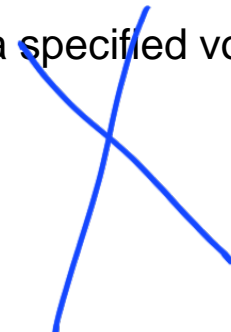1. Forward Voltage (V_F) at a specified current and temperature
2. Maximum forward current (I_F) at a specified temperature
3. Reverse voltage rating, PIV or PRV or $V_{(BR)}$, at a specified temperature
4. Maximum power dissipation, at a specified temperature
5. Reverse saturation current (I_R) at a specified voltage and temperature
6. Capacitance levels
7. Reverse recovery time, t_{rr}
8. Operating temperature range



Handwritten notes: "peak in reverse voltage" with an arrow pointing to item 3, and "reverse" with an arrow pointing to item 4.



Other Types of Diodes

There are several types of diodes besides the standard $p-n$ junction diode. Three of the more common are:

Zener diodes


Light-emitting diodes

Zener Diode (explained in ~~46~~ T5)

A **Zener diode** is one that is designed to safely operate in its zener region; i.e., biased at the Zener voltage (V_Z).


Common zener diode voltage ratings are between 1.8 V and 200 V

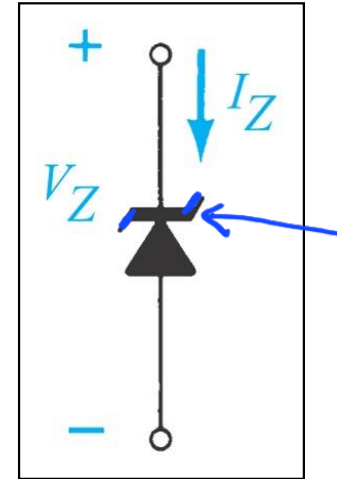The **Zener diode** is used mainly for voltage regulation, details will be discussed later



Light-Emitting Diode (LED)

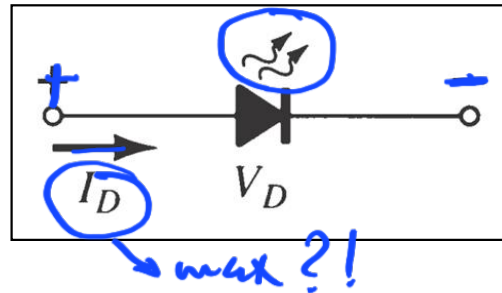An **LED** emits light when it is forward biased,
which can be in the infrared or visible spectrum.



The forward bias voltage is usually
in the range of 2 V to 3 V. ←

End of T3

L4 - part 1

13/7/2021
