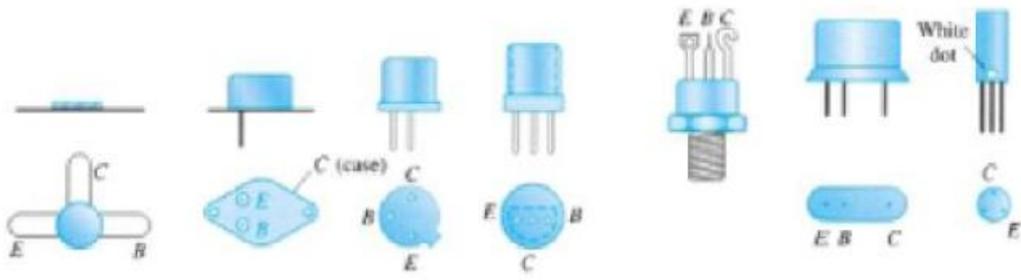


L12 - part 2  
sec 1  
31/7/2021



## ENEE2360 Analog Electronics

T8:

### BJT AC Models and Analysis

Instructor : Nasser Ismail

we will deal with small signal amplifiers in this course (not power amplifiers) X


## Small Signal ac Equivalent Circuit

- In order to simplify the analysis, we replace the Transistor by an equivalent circuit (model)
- An AC model represents the AC characteristics of the transistor.
- A model uses circuit elements that approximate the behavior of the transistor.
- There are two models commonly used in small signal AC analysis of a transistor:
  - $r_e$  model X
  - Hybrid equivalent model \*\* (h-parameter)

ENEE236
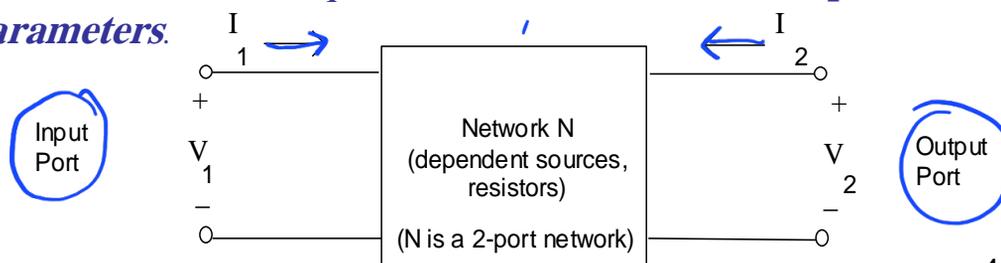
## Two-port networks


- Suppose that a network N has two ports as shown below. How could it be represented or modeled?
- A common way to represent such a network is to use one of 6 possible *two-port networks*.
- These networks are circuits that are based on one of 6 possible sets of *two-port equations*. These equations are simply different combinations of two equations that relate the variables  $V_1$ ,  $V_2$ ,  $I_1$ , and  $I_2$  to one another. The coefficients in these equations are referred to as *two-port parameters*.



4

ENEE234 – Circuit Analysis

Note that  $I_1$ ,  $I_2$ ,  $V_1$ , and  $V_2$  are labeled as shown by convention. Often there is a common negative terminal between the input and the output so the figure above could be redrawn as:

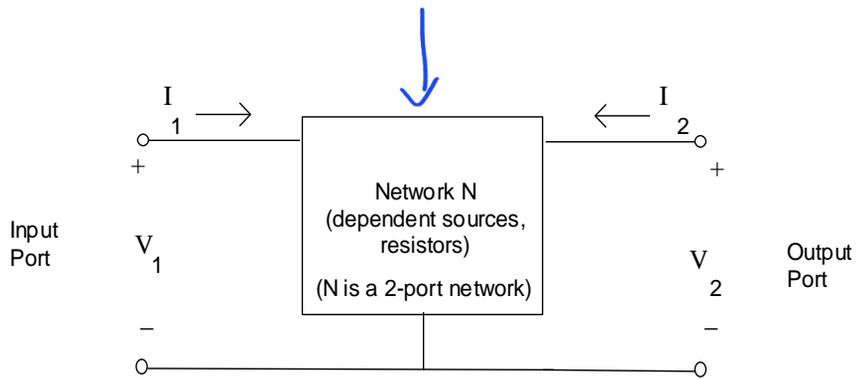


ENEE236

**Development of the h-parameter model of BJT:**

For A BJT the equivalent h parameter model can be described by the following equations:

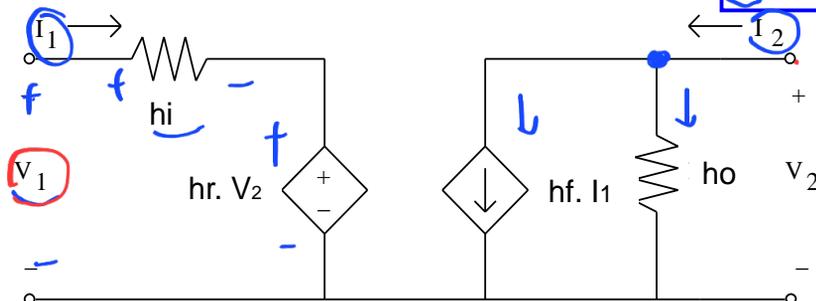**h - parameter equations :**

$$\begin{aligned} V_1 &= h_i \cdot I_1 + h_r \cdot V_2 \quad \leftarrow \text{KVL} \\ I_2 &= h_f \cdot I_1 + h_o \cdot V_2 \quad \leftarrow \text{KCL} \end{aligned}$$



$$h_i = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_r = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_f = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_o = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

*test  $V_2=0$*

$$V_1 = h_i I_1 + h_r V_2$$

$$h_i = \frac{V_1}{I_1} \quad V_2=0$$

$$h_f = \frac{I_2}{I_1} \quad V_2=0$$


$$I_2 = h_f I_1 + h_o V_2$$

7

ENEE236

Summary:


Note: This page is for information only

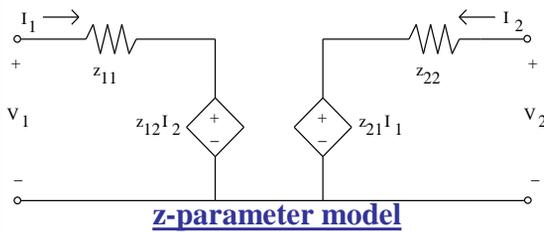

z - parameter equations :

$$V_1 = z_{11} \cdot I_1 + z_{12} \cdot I_2$$

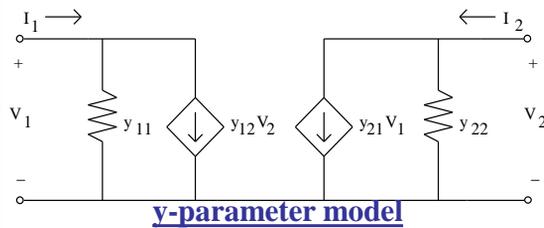
$$V_2 = z_{21} \cdot I_1 + z_{22} \cdot I_2$$



y - parameter equations :

$$I_1 = y_{11} \cdot V_1 + y_{12} \cdot V_2$$
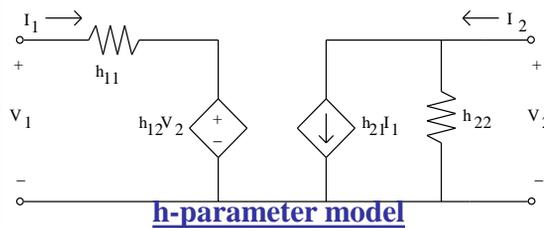
$$I_2 = y_{21} \cdot V_1 + y_{22} \cdot V_2$$



h - parameter equations :



$$V_1 = h_{11} \cdot I_1 + h_{12} \cdot V_2$$

$$I_2 = h_{21} \cdot I_1 + h_{22} \cdot V_2$$
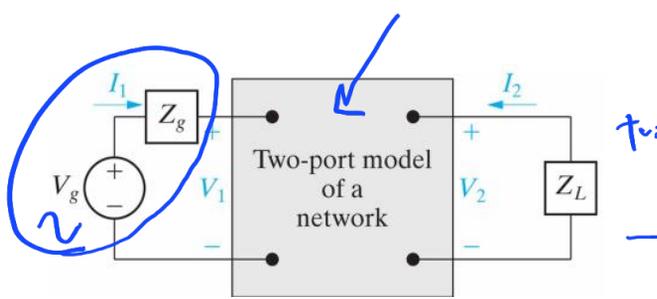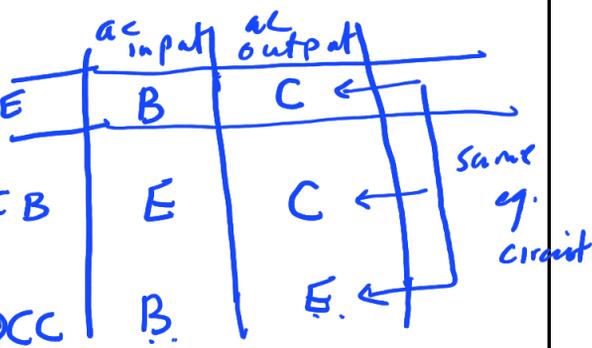
## BJT Configurations

Amplifiers


- Common Emitter → CE
- Common Base → CB
- Common Collector → CC



Terminated Two port network  
 Includes source and load


End of L12 - part 2  
 31/7/2021

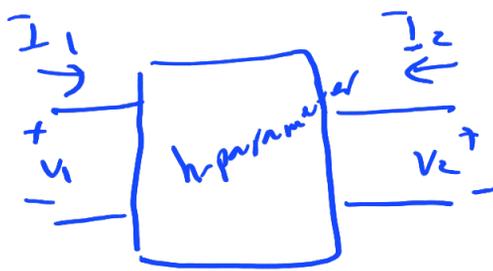L13 1/8/2021  
CE & CC  
 $h_i \rightarrow h_{ie}$   
 $h_r \rightarrow h_{re}$   
 $h_f \rightarrow h_{fe}$   
 $h_o \rightarrow h_{oe}$


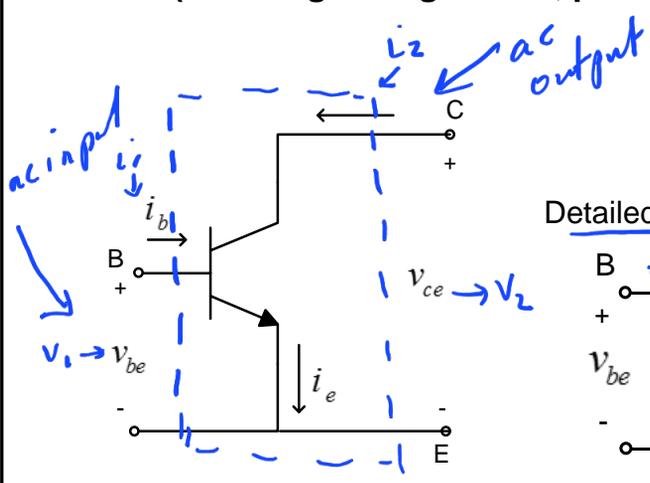
## Common Emitter Configuration

(inverting configuration, provides voltage and current gain)




h - parameter equations:


$$V_{be} = h_{ie} \cdot I_b + h_{re} \cdot V_{ce}$$

$$I_c = h_{fe} \cdot I_b + h_{oe} \cdot V_{ce}$$

Detailed Model

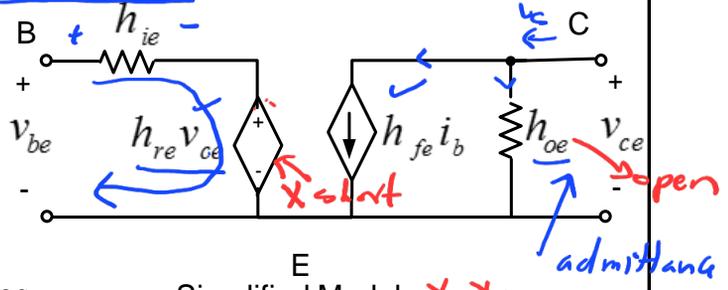

Simplified Model \*\*

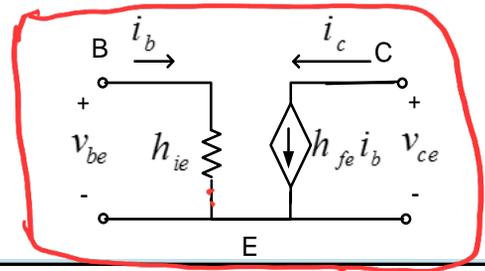

Typical Data sheet parameter values


- $h_{ie} \approx 1600 \Omega$
- $h_{re} \approx 0.0002$
- $h_{fe} \approx 80$
- $h_{oe} \approx 20 \cdot 10^{-6} \text{ Siemens}$


$\frac{1}{\Omega}$

ac equivalent circuit

KVL  
KCL  
admittance  
open  
1 h<sub>oe</sub>  
mS
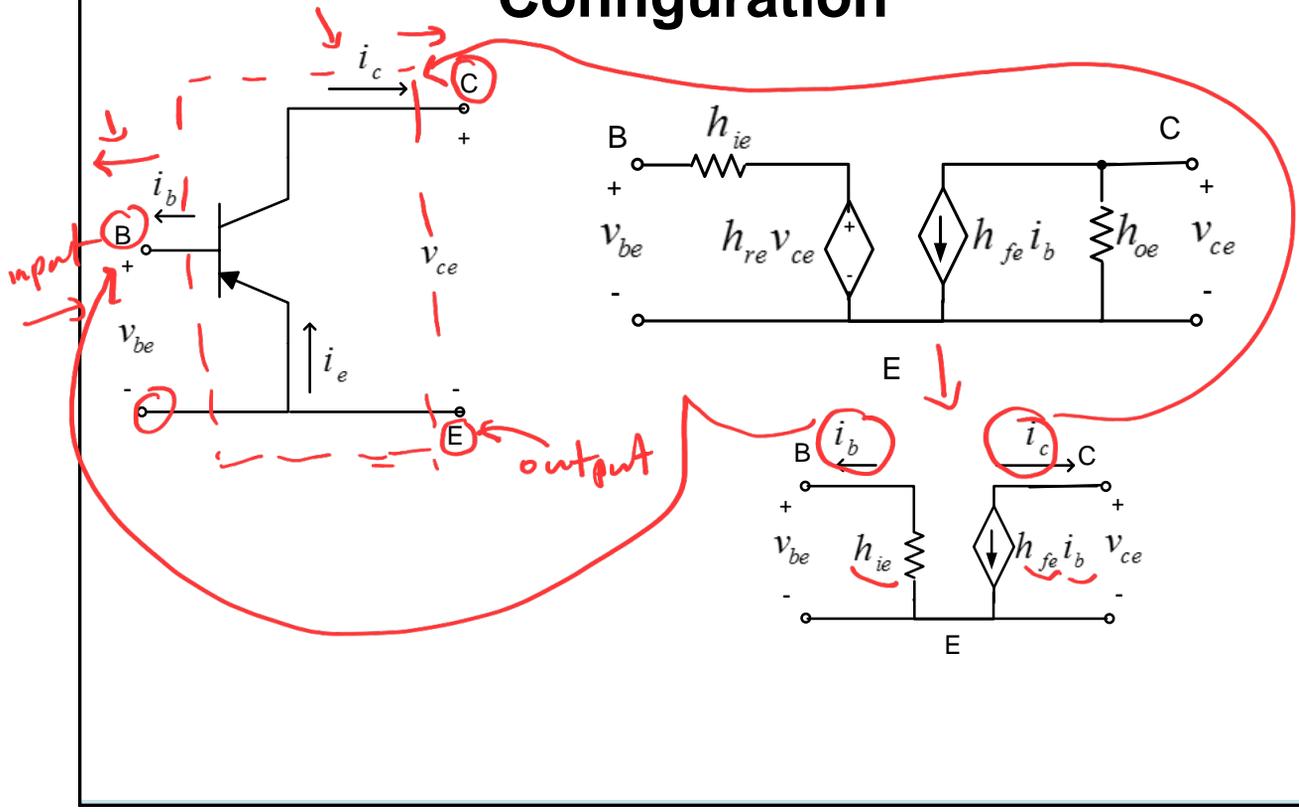
# Common Emitter and Common Collector Configuration



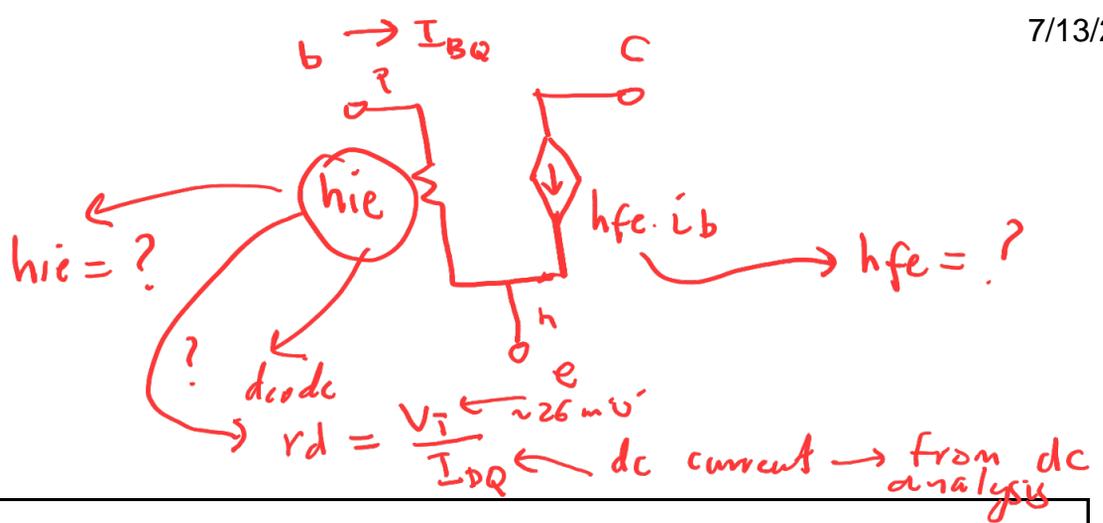

## Value of $h_{ie}$ → found from dc analysis

Base Emitter is a pn junction similar to a diode  
 $h_{ie}$  is the dynamic resistance of the pn junction

In a diode:

$$h_{fe} = \frac{i_c}{i_b} = \beta$$

$$r_d = \frac{V_T}{I_{DQ}} \Rightarrow$$

$$h_{ie} = \frac{V_T}{I_{BQ}} = \frac{V_T}{\frac{I_{CQ}}{h_{fe}}} = \frac{h_{fe} V_T}{I_{CQ}}$$

$I_{BQ}$  dc value of base current  
 $I_{CQ}$  dc value of collector current


$$h_{fe} = \beta$$

$$V_T = 25.69 \text{ mV @ } 25^\circ\text{C}$$
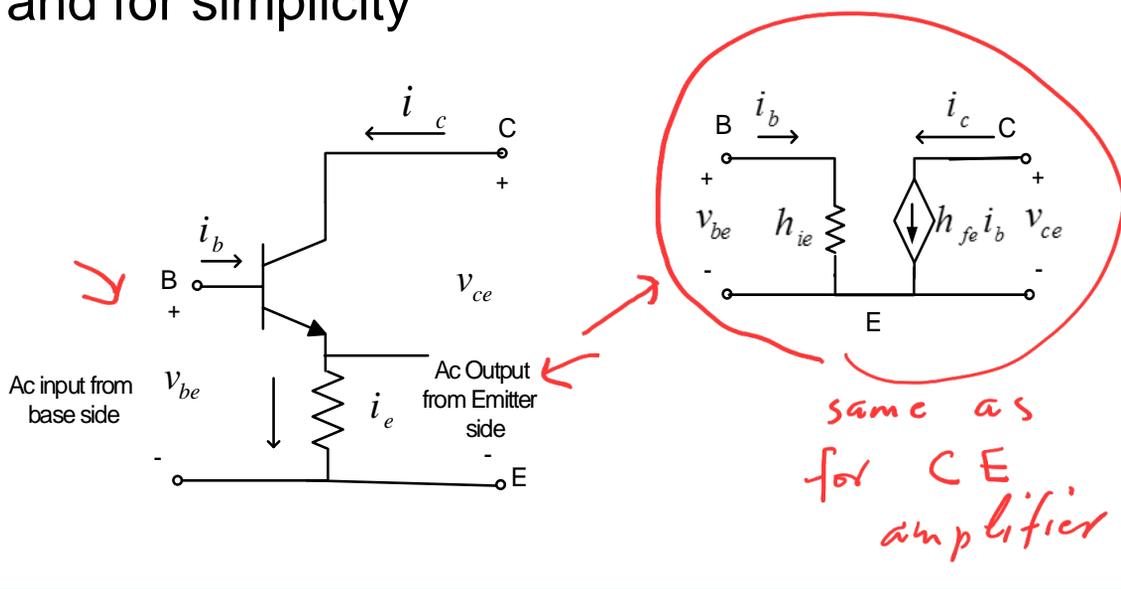
## Common Collector

(provides current gain and no voltage gain)

Same Model of Common Emitter will be used due to the similarities between them and for simplicity



**Common-Base Configuration**

*CB* →

Input →  $v_{eb}$   $i_e$   $i_b$   $i_c$   $v_{cb}$  → Output

$h$ -parameter equations:

$$V_{eb} = h_{ib} \cdot I_e + h_{rb} \cdot V_{cb}$$

$$I_c = h_{fb} \cdot I_e + h_{ob} \cdot V_{cb}$$


$$h_{ib} = \left. \frac{V_{EB}}{I_E} \right|_{V_{CB}=0}$$

$$h_{fb} = \alpha = \left. \frac{I_C}{I_E} \right|_{V_{CB}=0}$$

$$h_{rb} = \left. \frac{V_{EB}}{V_{CB}} \right|_{I_E=0}$$

$$h_{ob} = \left. \frac{I_C}{V_{CB}} \right|_{I_E=0}$$

*X* } to be ignored

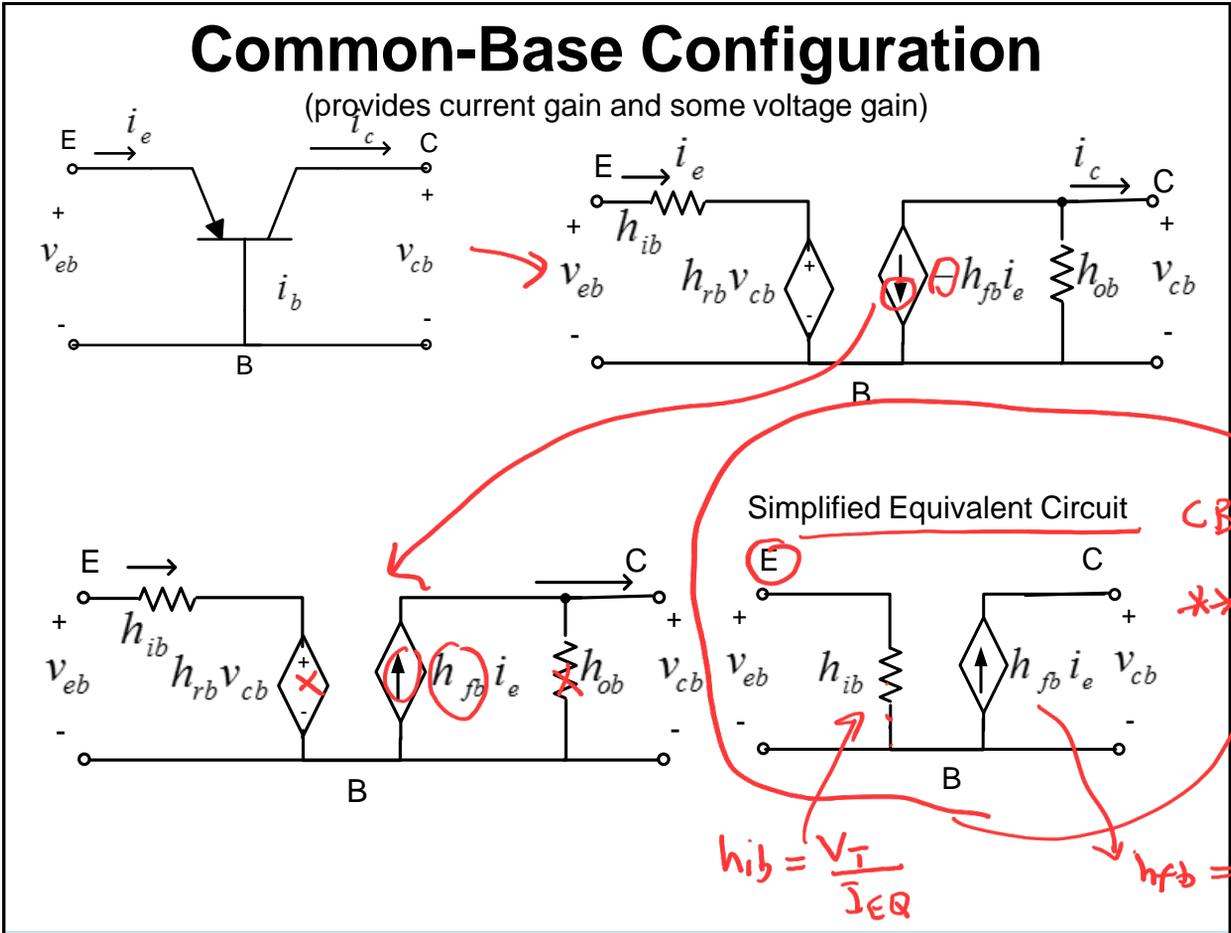

## Common-Base Configuration

$$h_{ib} = \frac{V_T}{I_{EQ}} \quad \checkmark$$

$$h_{fb} = \alpha \quad \checkmark$$

$$V_T = 25.69 \text{ mV @ } 25^\circ\text{C}$$

$$h_{ie} > h_{ib}$$

$$h_{ie} = \frac{V_T}{I_{BQ}}$$

$$h_{ie} = \frac{V_T}{\frac{I_E}{\beta+1}}$$

$$h_{ie} = \frac{V_T (\beta+1)}{I_E}$$

$$h_{ie} = h_{ib} (\beta+1)$$

*ac small-signal analysis*

## BJT Amplifier Analysis

When Analyzing Amplifier Circuits, we usually want to find some or all of the following quantities with and without  $R_s$ :

- 1)  $A_v = V_o/V_i$ , small signal voltage gain
- 2)  $A_i = i_o/i_i$ , small signal current gain
- 3)  $Z_i$  Input Impedance
- 4)  $Z_o$  Output Impedance



$A_v = \frac{V_o}{V_i}$   
*( $V_o$  and  $V_i$  are labeled as ac)*

*ac small signal (SS) quantities*

*analysis*

*to be given*

*to be given*

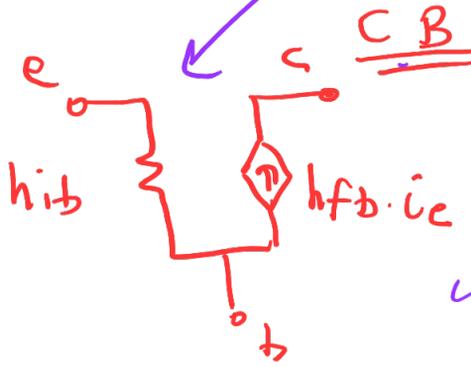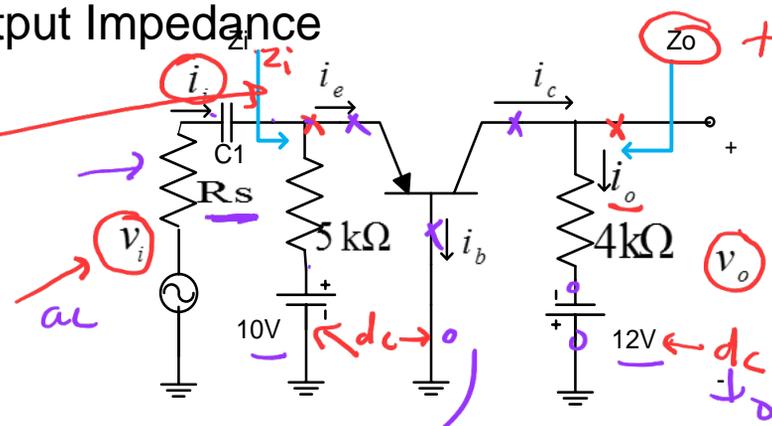

- ac analysis  $\rightarrow f \uparrow \uparrow$  large
- all dc sources are killed (deactivated)
    - $V \rightarrow 0 \rightarrow$  short
    - $I \rightarrow 0 \rightarrow$  open
  - Caps  $\rightarrow X_c = \frac{1}{2\pi f C}$   
 $X_c \cong 0 \rightarrow$  are replaced by short circuit


## BJT Amplifier Analysis

Solution: (with  $R_s=0$ )

We draw the ac small signal equivalent circuit

Capacitors  $\Rightarrow$  replaced by short circuit

DC sources are killed ,

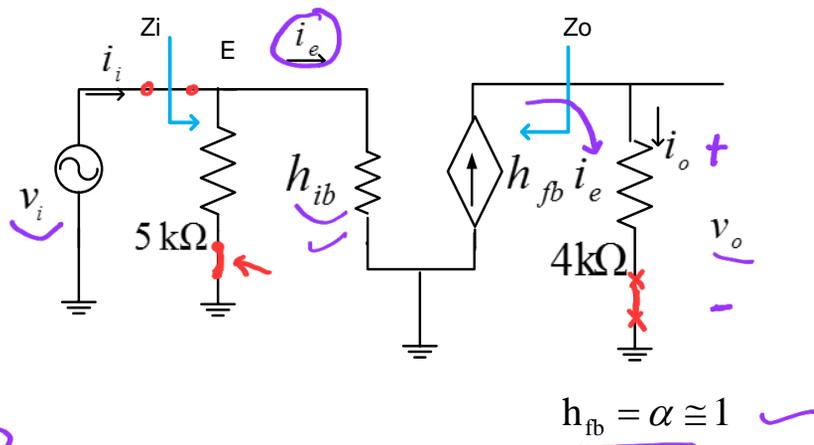

$$h_{ib} = \frac{V_T}{I_{EQ}}$$

$I_{EQ}$  must be calculated from DC analysis

$\underline{A_v} = \frac{v_o}{v_i}$

$v_o = i_o \cdot 4k \rightarrow \frac{v_o}{i_o} = 4k$  ①  
 $i_o = h_{fb} \cdot i_e \rightarrow \frac{i_o}{i_e} = h_{fb}$  ②  
 $i_e = \frac{v_i}{h_{ib}} \rightarrow \frac{i_e}{v_i} = \frac{1}{h_{ib}}$  ③

$\boxed{I_e = I_b(h_{fe} + 1)}$


$\textcircled{1} \times \textcircled{2} \times \textcircled{3} = \frac{v_o}{i_o} \times \frac{i_o}{i_e} \times \frac{i_e}{v_i} = \frac{v_o}{v_i} = A_v$   
 $A_v = 4k \times h_{fb} \times \frac{1}{h_{ib}}$

$$A_v = 4k \cdot h_{fb} \cdot \frac{1}{h_{ib}}$$

$h_{ib} = \frac{V_T}{I_{EQ}}$   
 dc current  $\rightarrow$  dc analysis
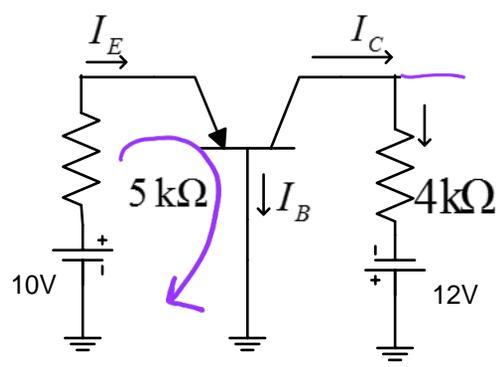
## DC Analysis

DC Equivalent Circuit:  
 -Cap ==> open  
 -Kill ac sources ==>



$$10 = 5 \text{ k}\Omega \cdot I_{EQ} + V_{EB}$$

$$I_{EQ} = \frac{10 - 0.7}{5 \text{ k}\Omega} = 1.86 \text{ mA}$$

$$h_{ib} = \frac{V_T}{I_{EQ}} = \frac{25.69 \text{ mV}}{1.86 \text{ mA}} = 13.98 \Omega$$


## Ac ss equivalent circuit

$$1) A_V = \frac{v_o}{v_i}$$

$$v_o = i_o \cdot 4 \text{ k}\Omega$$

$$i_o = h_{fb} \cdot i_e$$

$$i_e = \frac{v_i}{h_{ib}}$$

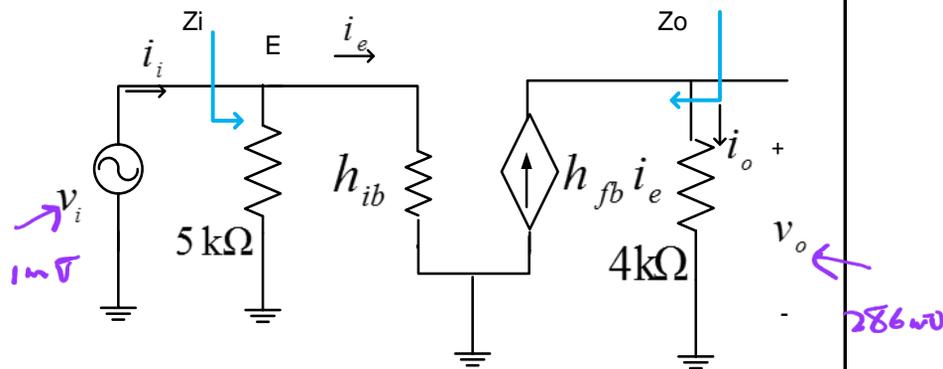

$$A_V = \frac{v_o}{v_i} = \frac{v_o}{i_o} \cdot \frac{i_o}{i_e} \cdot \frac{i_e}{v_i}$$



$$A_V = (4 \text{ k}\Omega) \cdot (h_{fb}) \cdot \left( \frac{1}{h_{ib}} \right)$$

$$= (4 \text{ k}\Omega) \cdot (1) \cdot \left( \frac{1}{13.98} \right) = 286 > 1$$


↑  
voltage gain

## Current Gain Ai

$$2) A_i = \frac{i_o}{i_i}$$

$$i_o = h_{fb} \cdot i_e$$
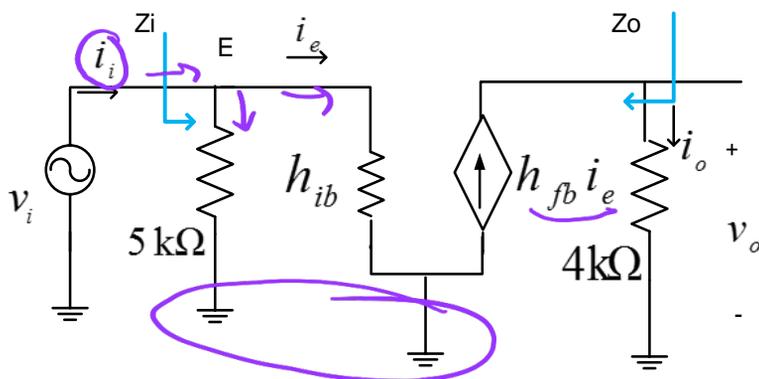
$$i_e = i_i \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + h_{ib}}$$



$$\Rightarrow A_i = \frac{i_o}{i_i} = \frac{i_o}{i_e} \cdot \frac{i_e}{i_i}$$


$$\Rightarrow A_i = (h_{fb}) \left( \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + h_{ib}} \right)$$

$$= (1) \left( \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + 13.98} \right) < 1$$

End of L13  
2/8/2021


# BJT Amplifier Configurations

L14 1sec  
4-8-2021

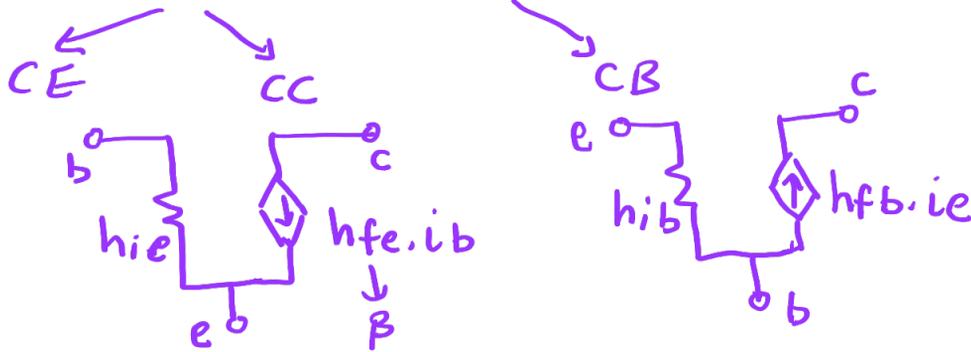

ac ss eq. circuit

## Zi & Zo

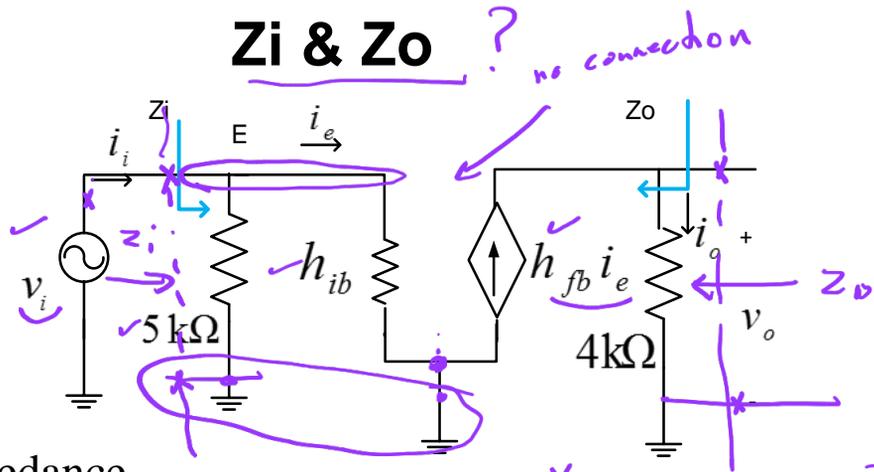




### 3) Input Impedance

$$Z_i = (h_{ib} // 5 \text{ k}\Omega) = \left( \frac{h_{ib} \cdot 5 \text{ k}\Omega}{5 \text{ k}\Omega + h_{ib}} \right)$$

### 4) Output Impedance

$$Z_o \Big|_{\text{all independent sources killed (i.e. } V_i=0 \text{ or short)}} = \underline{\underline{4 \text{ k}\Omega}}$$

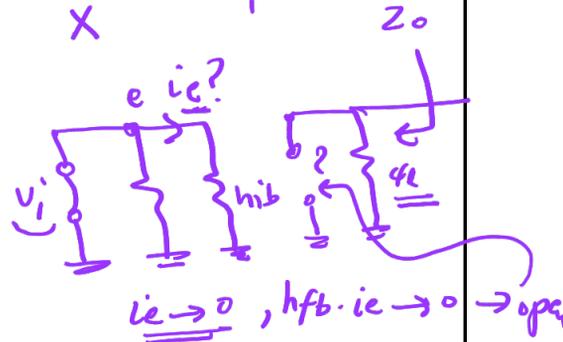

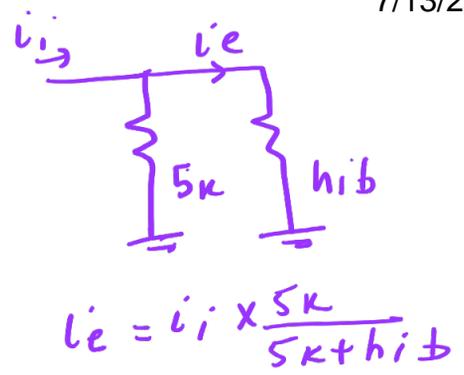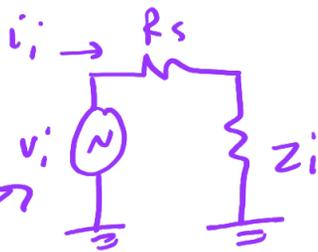


$$i_e = i_i \times \frac{5k}{5k + h_{ib}}$$

### With Presence of $R_s$

with  $R_s$

$$i_i = \frac{v_i}{Z_i + R_s}$$

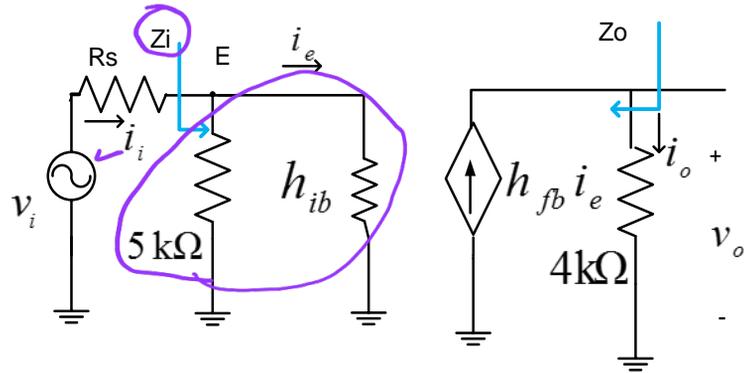

For  $R_s = 50 \Omega$

$A_v = 62.5$  ←

For  $R_s = 10 k\Omega$

$A_v = 0.4$  ←

$R_s = 0 \rightarrow A_v = 286$

↑  $R_s \rightarrow A_v ?$  ↓



$\frac{V_o}{V_i} \leftarrow A_v$        $Z_i$  ✓  
 $\frac{I_o}{I_i} \leftarrow A_i$        $Z_o$  ✓

## Example: Common Emitter (CE)

1) From DC Analysis, we find Q - point and value of




$$h_{ie} = \frac{V_T}{I_{BQ}}$$

*Handwritten notes:*  $h_{ie}$  is a small signal parameter,  $I_{BQ}$  is DC current.

Thevenin's equivalent circuit as seen from the base

$$V_{TH} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 50 \text{ k}\Omega} \cdot 24 \text{ V} = 4 \text{ V}$$
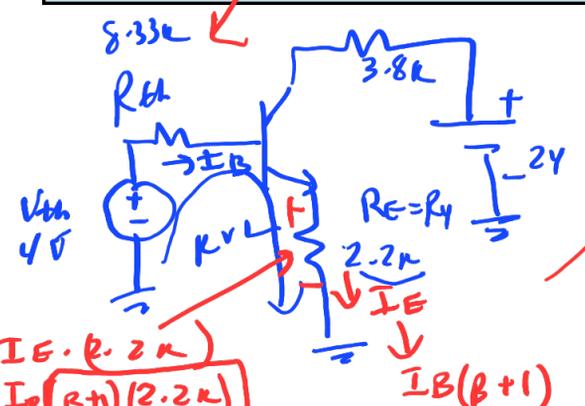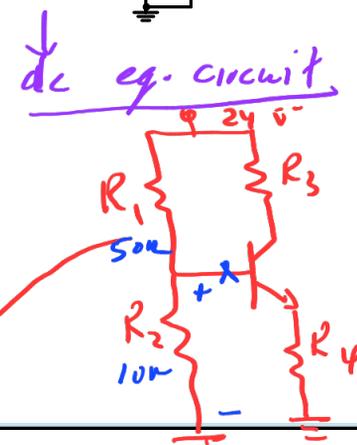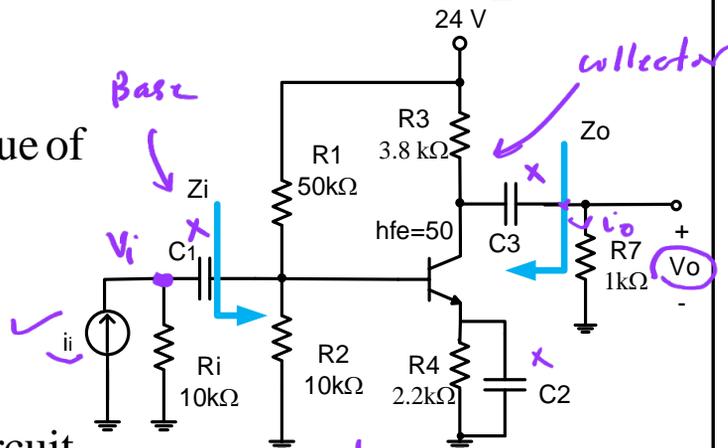
$$R_{TH} = 10 \text{ k}\Omega // 50 \text{ k}\Omega = 8.33 \text{ k}\Omega$$



$$I_B = \frac{V_{th} - 0.7}{R_{th} + R_E(\beta + 1)}$$


$$= \frac{4 - 0.7}{8.33 \text{ k}\Omega + 2.2 \text{ k}\Omega(50 + 1)}$$

\* Base equivalent circuit

$$I_E \cdot (2.2 \text{ k}\Omega)$$


$$I_B(\beta + 1)(2.2 \text{ k}\Omega)$$

$$I_B(\beta + 1)$$

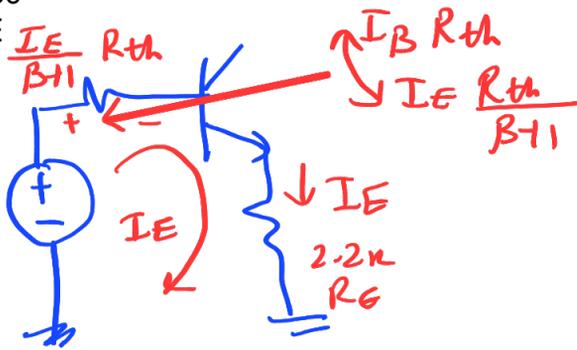

$$I_E = \frac{V_{th} - 0.7}{R_E + \frac{R_{th}}{\beta + 1}}$$

\* Emitter equivalent circuit

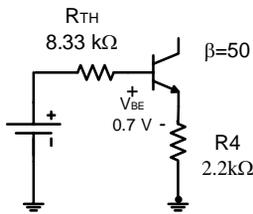


$$4 = 8.33 \text{ k}\Omega \cdot I_B + V_{BE} + 2.2 \text{ k}\Omega \cdot I_E$$

But,  $I_E = (1 + \beta)I_B$

$$\text{Solve for } I_E = \frac{4 - 0.7}{\frac{8.33 \text{ k}\Omega}{(1 + 50)} + 2.2 \text{ k}\Omega} = 1.4 \text{ mA}$$


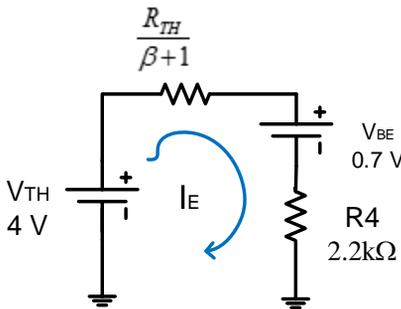
$$h_{ie} = \frac{V_T}{I_{BQ}} = \frac{25.69 \text{ mV}}{\frac{1.4 \text{ mA}}{51}} = 928 \Omega$$




Here we have base reflected to emitter


$$I_B \Rightarrow I_E = (\beta + 1)I_B$$
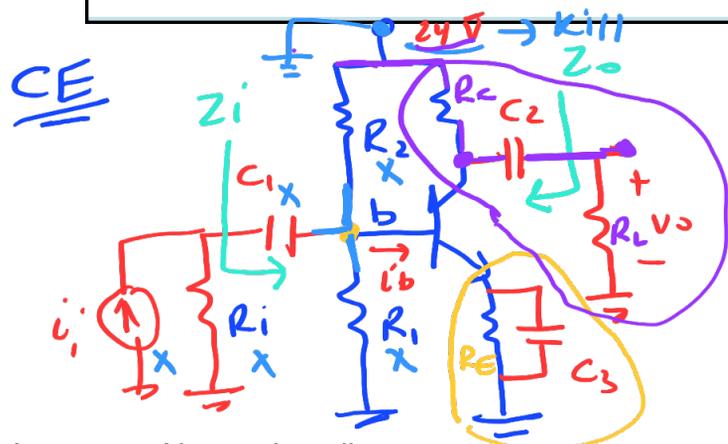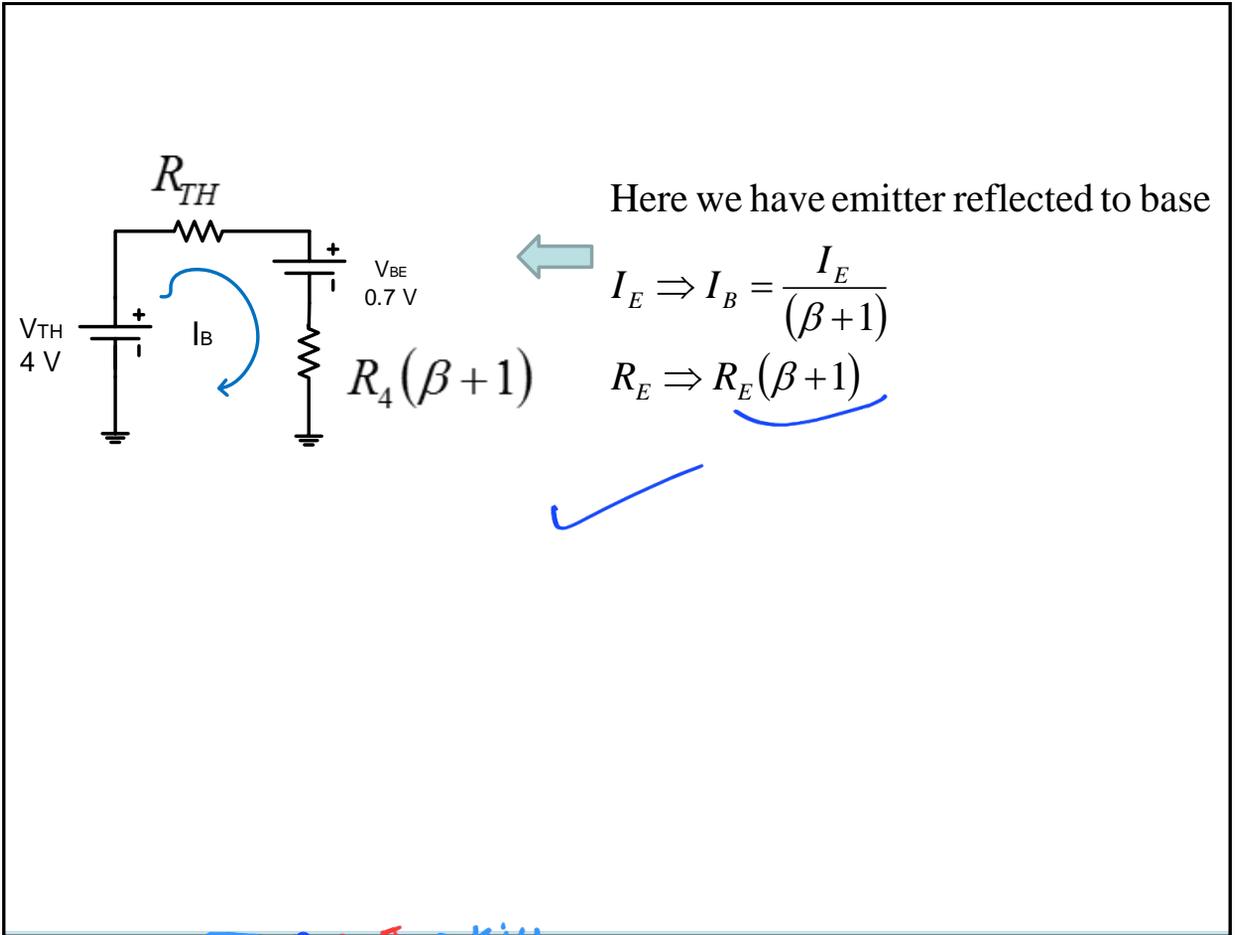
$$R_B \Rightarrow \frac{R_B}{\beta + 1}$$




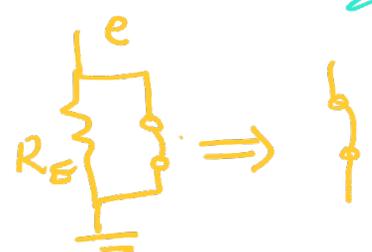ac ss eq. circuit  
to find  $A_v, A_i, Z_i, Z_o$



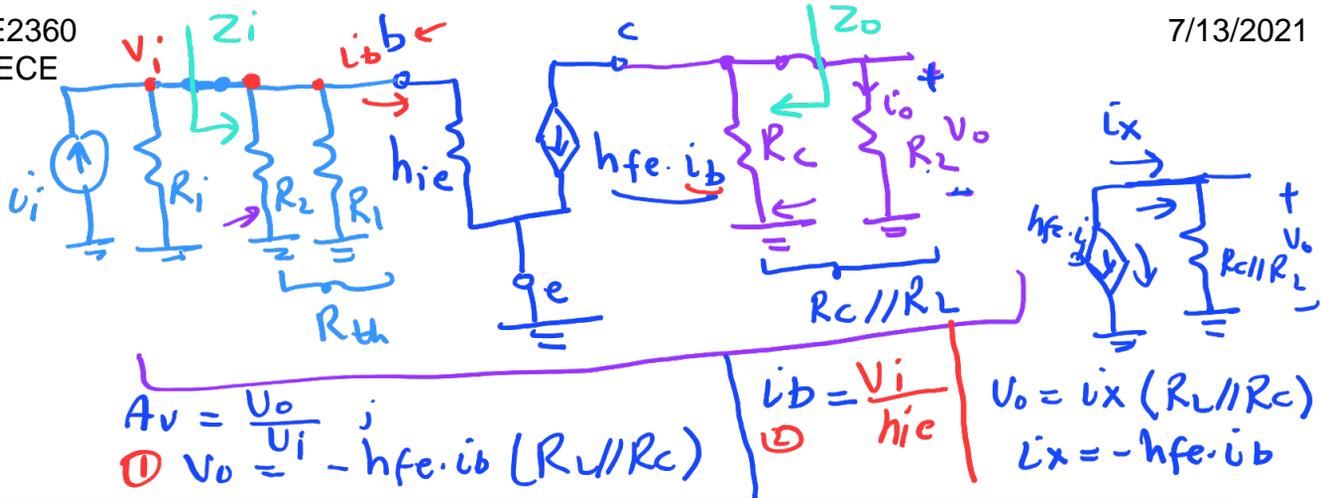

## AC small signal Equivalent Circuit

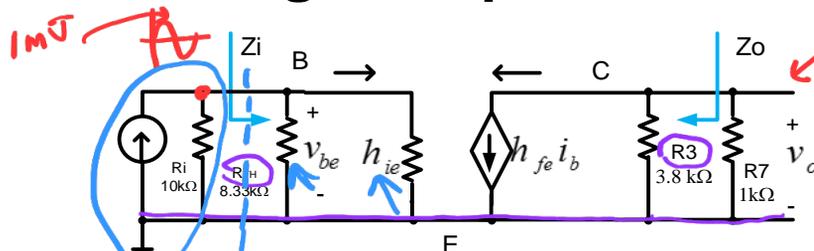

1)  $A_v = \frac{v_o}{v_i}$


$A_v = \frac{v_o}{v_i} = \frac{v_o}{i_b} \cdot \frac{i_b}{v_i}$

①  $v_o = -h_{fe} \cdot i_b \cdot (R_3 // R_7) \Rightarrow -h_{fe} \cdot (R_3 // R_7) \cdot \left( \frac{1}{h_{ie}} \right)$

②  $i_b = \frac{v_i}{h_{ie}} \Rightarrow -50 \cdot (3.8 \text{ k}\Omega // 1 \text{ k}\Omega) \cdot \left( \frac{1}{928 \Omega} \right) = -42.7$

$R_c // R_L$   
Phase shift 180°

## AC small signal Equivalent Circuit

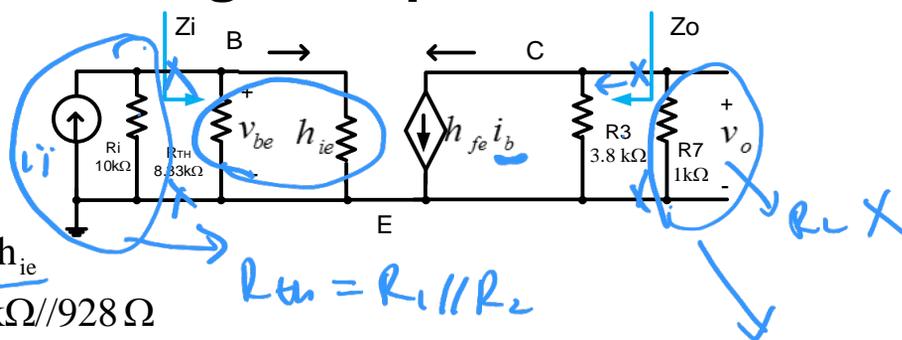


2)  $Z_I = R_{TH} // h_{ie}$   
 $= 8.33 \text{ k}\Omega // 928 \Omega$


only elements to the right of arrow are considered according to the given direction of the arrow

3)  $Z_o |_{\text{all independent sources killed (i.e. } V_i=0 \text{ or short)}} = 3.8 \text{ k}\Omega$

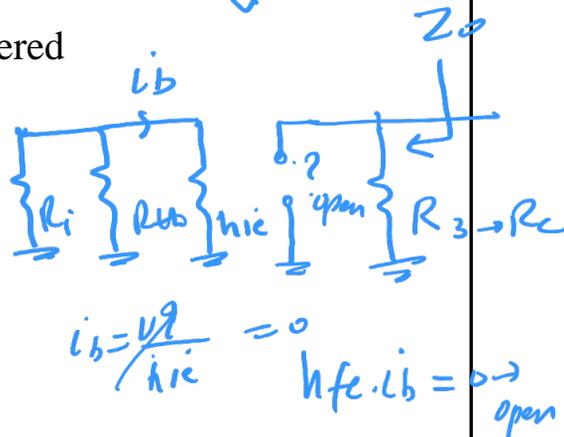here  $h_{fe} \cdot i_b = 0$  since  $i_b = 0$  ( $v_i = 0$  - killed)



# AC small signal Equivalent Circuit

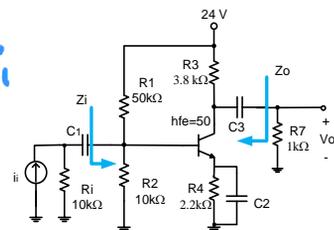


ac ss  
current gain

$$\frac{v_b}{i_i} \times \frac{i_o}{v_b} = \frac{i_o}{i_i} = A_i$$

4)  $A_i = \frac{i_o}{i_i}$

1)  $i_b = (i_i) \left( \frac{R_1 // R_{TH}}{(R_1 // R_{TH}) + h_{ie}} \right)$

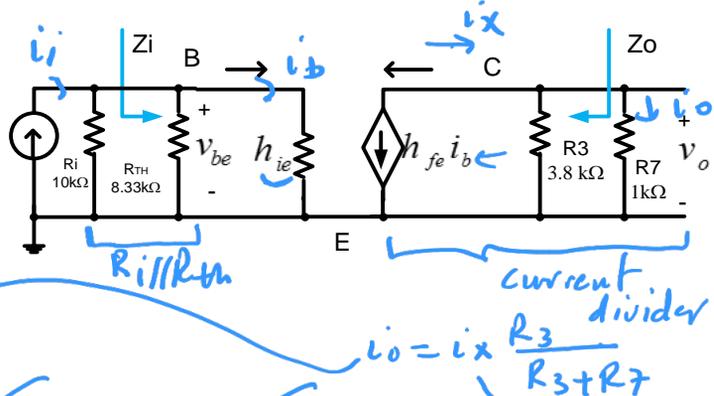2)  $i_o = -h_{fe} i_b \left( \frac{R_3}{R_3 + R_7} \right)$



$i_o = i_x \frac{R_3}{R_3 + R_7}$

$A_i = \frac{i_o}{i_i} = \frac{i_o}{i_b} \cdot \frac{i_b}{i_i} = -h_{fe} \left( \frac{R_3}{R_3 + R_7} \right) \left( \frac{R_1 // R_{TH}}{(R_1 // R_{TH}) + h_{ie}} \right) = \underline{\underline{-33}}$   $i_x = -h_{fe} \cdot i_b$

$i_b \Rightarrow i_e ?$


$i_e = (\beta + 1) i_b$

$i_b = \frac{i_e}{\beta + 1}$

Reflection  $\rightarrow$  simplification technique  
 From Emitter to base  
 Base to Emitter  
 or "

## Impedance Reflection Concept

v1, v2, v3 are all ac sources

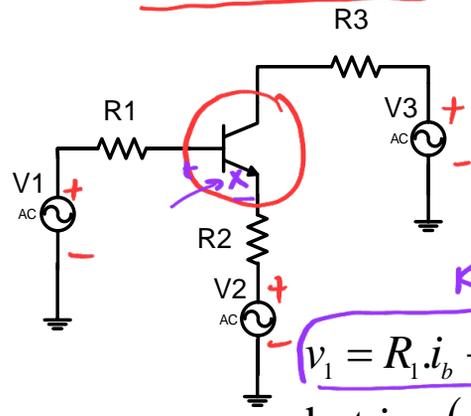


KVL

$v_1 = R_1 i_b + h_{ie} i_b + R_2 i_e + v_2$

but  $i_e = (\beta + 1) i_b$


$v_1 = R_1 i_b + h_{ie} i_b + R_2 (\beta + 1) i_b + v_2$

ac ss equivalent circuit

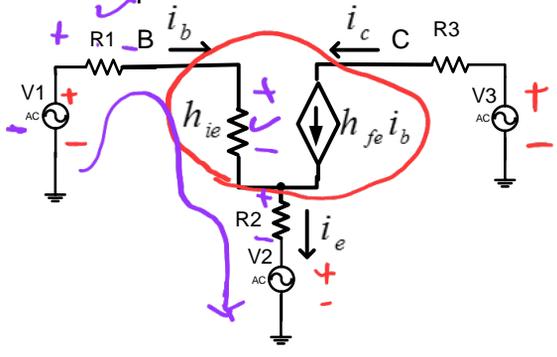


$i_b = \frac{v_1 - v_2}{R_1 + h_{ie} + R_2 (\beta + 1)}$   $\leftarrow$  base loop equivalent circuit equation


$\beta = h_{fe}$

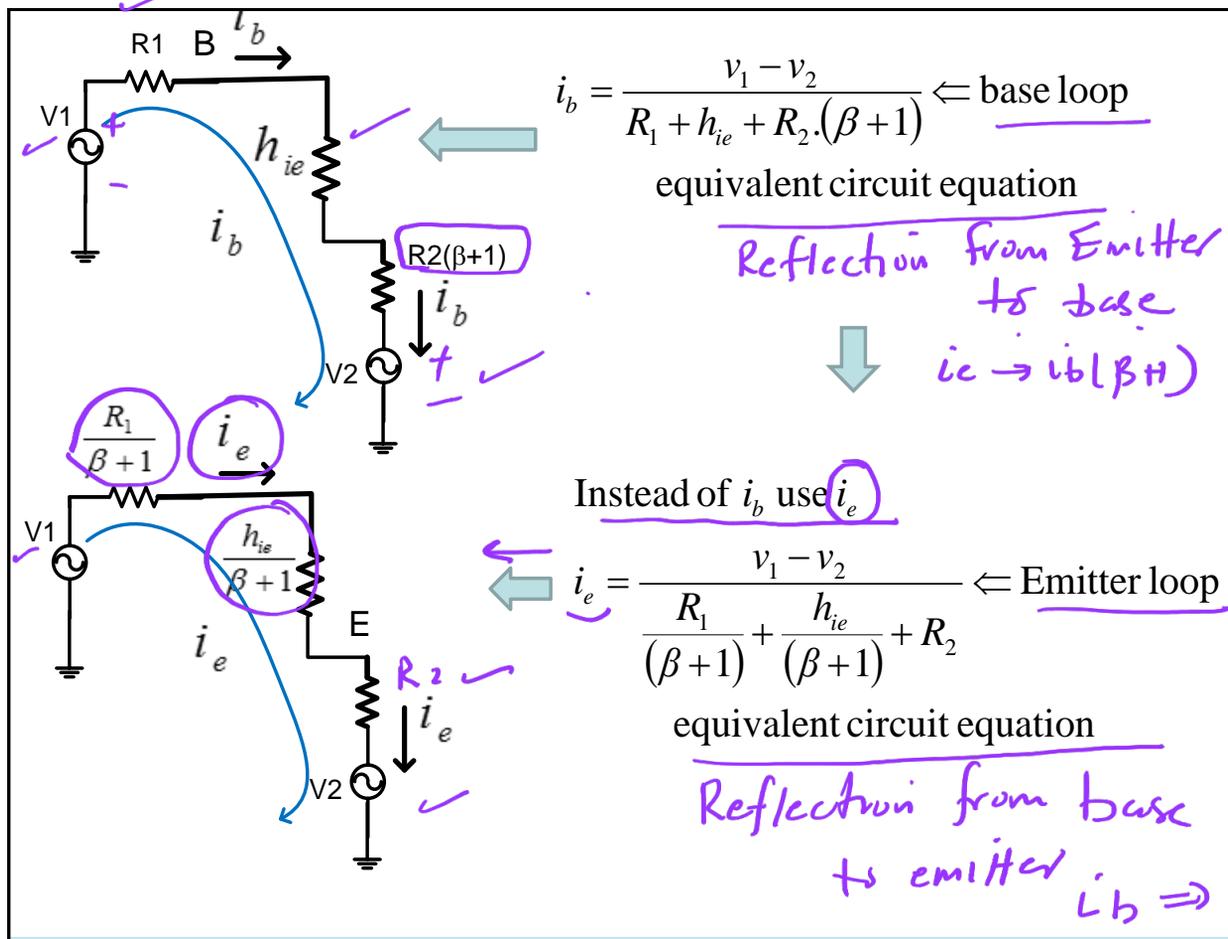

*Please read*

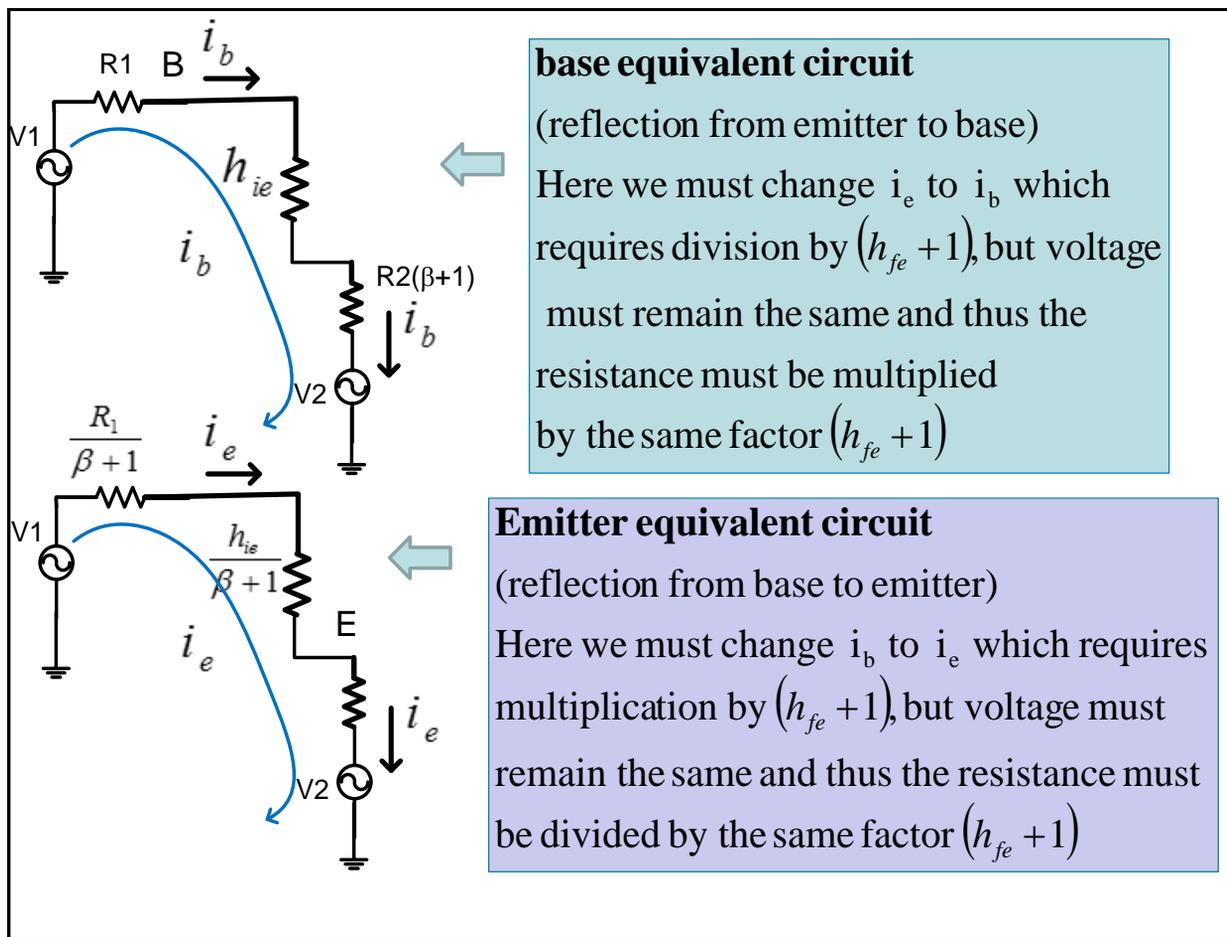


## Collector Equivalent Circuit

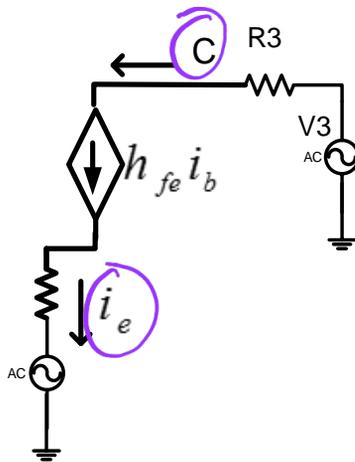

Note: there is no reflection from emitter to collector or vice versa since the  $i_e$  and  $i_c$  are almost the same

\* \* \*  
↖ ↗

# Common Collector Amplifier

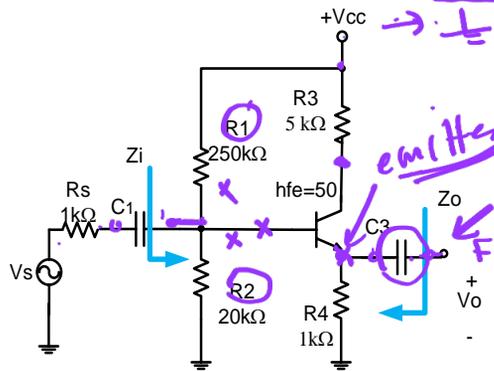


Given

$$h_{ie} = 1k\Omega$$

$$h_{fe} = \beta = 50$$

Find  $A_v, A_i, Z_i, Z_o$

AC small signal Equivalent Circuit

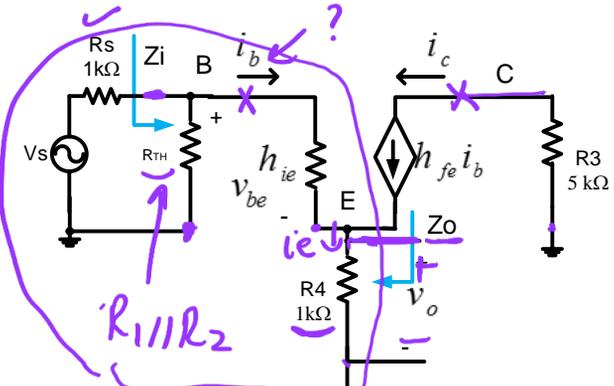

$$1) A_v = \frac{v_o}{v_s}$$


$$v_o = 1k\Omega \cdot i_e$$

$$i_e = i_b (h_{fe} + 1)$$

①


②

ac ss eq. circuit

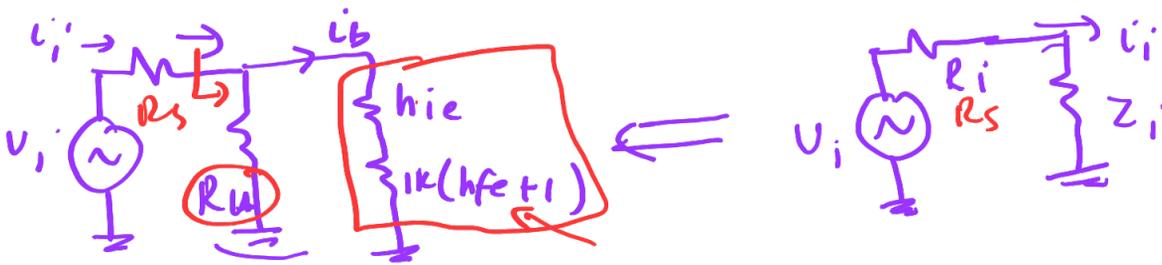

$$i_i = \frac{V_i}{Z_i + R_i}$$

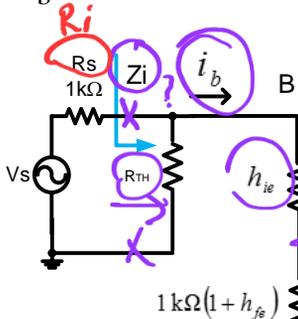$i_b$  can be found from base equivalent circuit



$$R_{TH} = 20 \text{ k}\Omega // 250 \text{ k}\Omega$$

$$i_b = i_i \frac{R_{TH}}{(R_{TH}) + (h_{ie} + 1 \text{ k}\Omega(h_{fe} + 1))} \quad (3)$$

$$i_i = \frac{V_S}{R_S + (R_{TH} // (h_{ie} + 1 \text{ k}\Omega(h_{fe} + 1)))} \quad (4)$$

$$\therefore A_v = \frac{v_o}{v_s} = \frac{v_o}{i_e} \cdot \frac{i_e}{i_b} \cdot \frac{i_b}{i_i} \cdot \frac{i_i}{v_s} =$$

$$= (1 \text{ k}\Omega) \cdot (h_{fe} + 1) \left( \frac{R_{TH}}{(R_{TH}) + (h_{ie} + 1 \text{ k}\Omega(h_{fe} + 1))} \right) \left( \frac{1}{R_S + (R_{TH} // (h_{ie} + 1 \text{ k}\Omega(h_{fe} + 1)))} \right)$$

$$= 0.915 < 1$$

*cc amplifier doesn't provide any voltage gain*  
 $A_v \leq 1$

2)  $A_i = \frac{i_o}{i_i}$

$i_o = \frac{v_o}{1\text{ k}\Omega}$  ✗

$i_o = i_e = i_b(h_{fe} + 1)$  ✓


$i_b = i_i \frac{R_{TH}}{(R_{TH}) + (h_{ie} + 1\text{ k}\Omega)(h_{fe} + 1)}$  ✓

$A_i = \frac{i_o}{i_i} = \frac{i_o}{i_e} \cdot \frac{i_e}{i_b} \cdot \frac{i_b}{i_i}$

$= 1(h_{fe} + 1) \left( \frac{R_{TH}}{R_{TH} + [h_{ie} + 1\text{ k}(h_{fe} + 1)]} \right) = 13.39 > 1$

$$3) Z_i = (R_{TH} // (h_{ie} + 1k\Omega(h_{fe} + 1)))$$

$$= 13.66 k\Omega \text{ (high)}$$

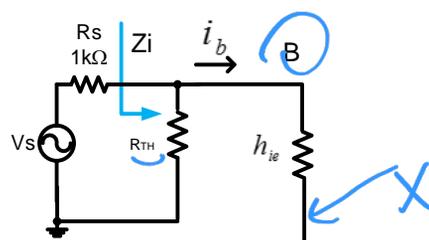


Emitter Equivalent Circuit  
&  $V_s = 0$

$$Z_o|_{V_s=0} = \left( \frac{(R_S // R_{TH}) + h_{ie}}{(h_{fe} + 1)} // 1k\Omega \right)$$

$$= \left( \left( \left( \frac{R_S}{(h_{fe} + 1)} // \frac{R_{TH}}{(h_{fe} + 1)} \right) + \frac{h_{ie}}{(h_{fe} + 1)} \right) // 1k\Omega \right)$$

$$= 36.8 \Omega \text{ (low)}$$

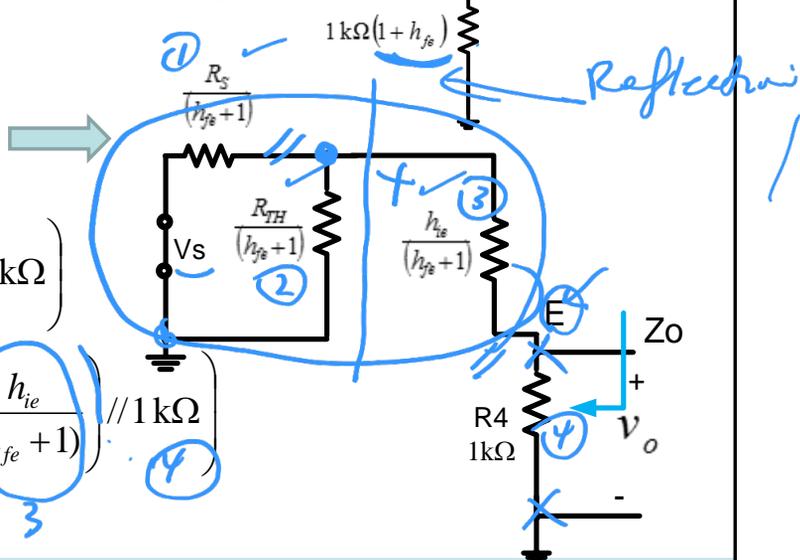

cc amplifier

$$A_v \leq 1$$

$$A_i \gg 1$$

$$Z_i \uparrow \uparrow$$


$$Z_o \downarrow \downarrow$$

End of L14

L15  
5/18/2021  
←  
see separate pdf  
file
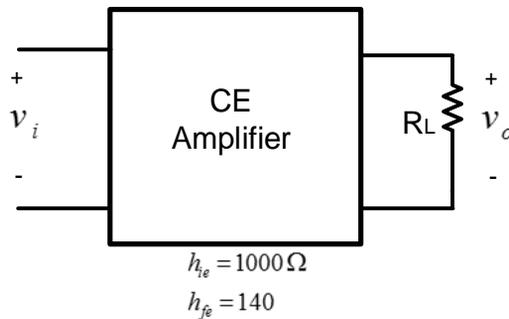
## CC Amplifier as a Buffer


- The value of load resistor  $R_L$  affects the voltage gain  $A_v$ ,
- This effect is called loading effect and can be substantial



- A buffer (interface) can be used between the amplifier and the load to reduce this loading effect and keep the high gain
- CC Amplifier is also known as Emitter Follower

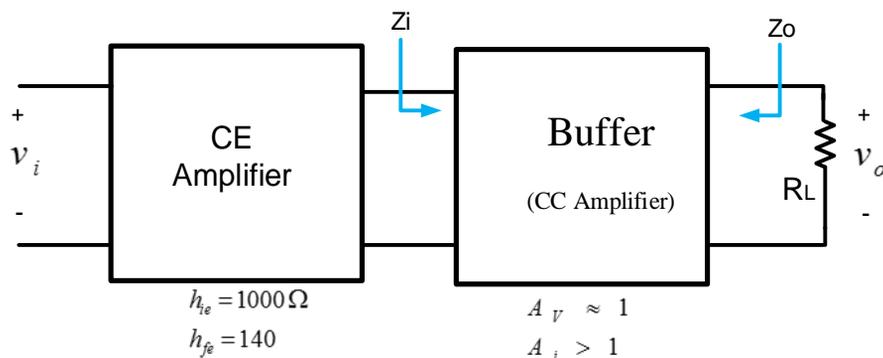
## CC Amplifier as a Buffer

- The buffer must have the following characteristic:
  - $A_v \approx 1$
  - $A_i > 1$
  - $Z_i \gg \text{high}$
  - $Z_o \ll \text{low}$
- The above characteristic are present in the CC amplifier the load to reduce this loading effect and keep the high gain


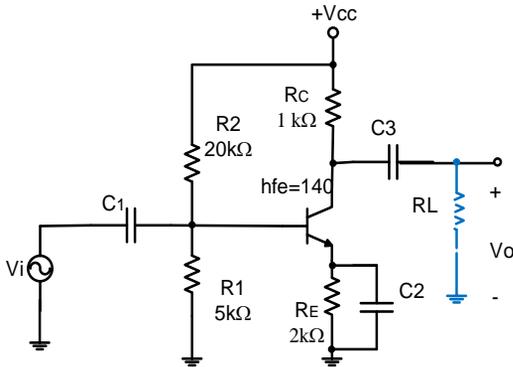
## Example

- First we consider effect of load ( $R_L$ ) on amplifier voltage gain
- Then we use a buffer and see its effect on reducing effect of  $R_L$




1) with  $R_L = \infty$

$$v_o = -h_{fe} i_b \cdot (R_C)$$

$$i_b = \frac{v_i}{h_{ie}}$$

$$A_V = \frac{v_o}{v_i} = (-h_{fe} R_C) \cdot \frac{1}{h_{ie}} = -140$$

2) with  $R_L = 50 \Omega$

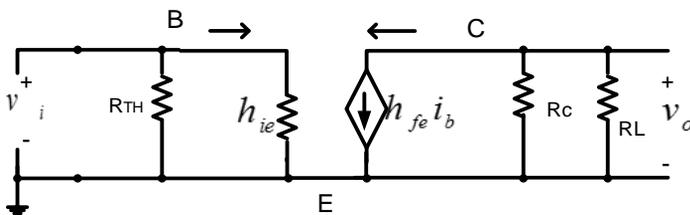


$$A_V = \frac{v_o}{v_i} = (-h_{fe} R_C // R_L) \cdot \frac{1}{h_{ie}} = -6.87$$


$A_V$  have been reduced from -140 to -6.87
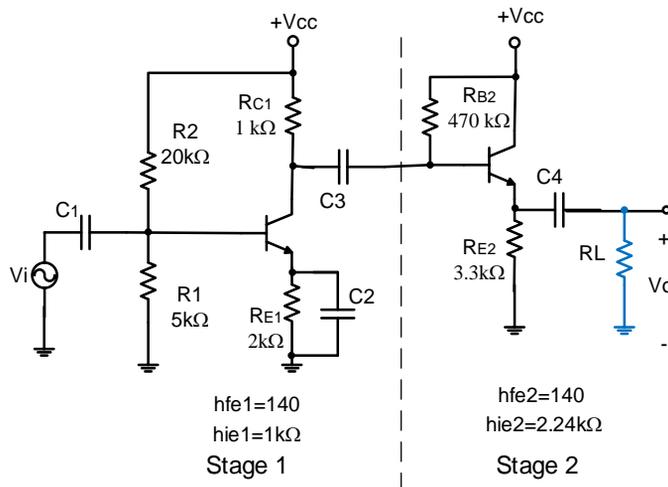
# Amplifier + Buffer + Load

Now let us look at the new circuit with the buffer



## ac ss equivalent Circuit

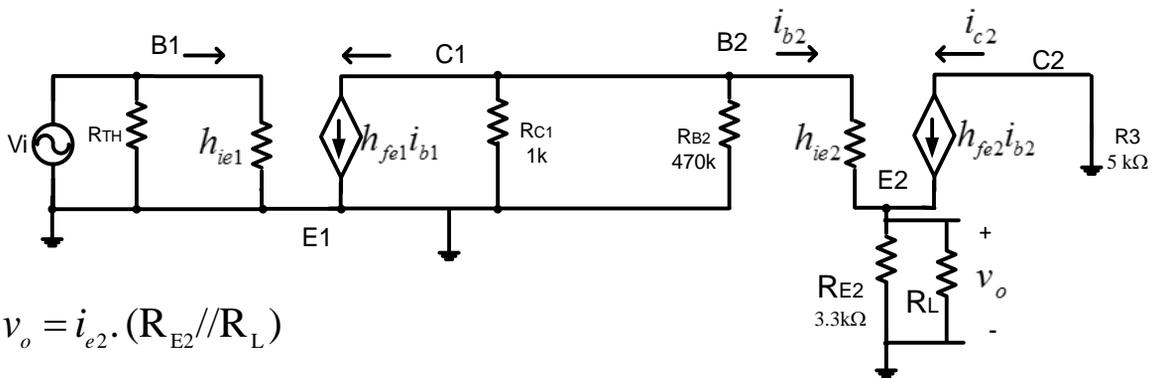

$$v_o = i_{e2} \cdot (R_{E2} // R_L)$$

$$i_{e2} = i_{b2} (1 + h_{fe2})$$


$$i_{b2} = -h_{fe1} \cdot i_{b1} \frac{(R_{C1} // R_{B2})}{((R_{C1} // R_{B2}) + (h_{ie2} + (R_{E2} // R_L)(1 + h_{fe2})))}$$

$$i_{b1} = \frac{V_i}{h_{ie1}}$$

$$\Rightarrow Av = \frac{v_o}{v_i} = \frac{v_o}{i_{e2}} \cdot \frac{i_{e2}}{i_{b2}} \cdot \frac{i_{b2}}{i_{b1}} \cdot \frac{i_{b1}}{v_i} = -95.6$$


This is much better than the case without buffer

## Multistage Amplifiers

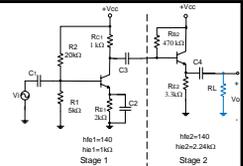

- The previous example of a CE amplifier with a CC buffer is an example of a multistage amplifier (two-stage amplifier)
- Multistage amplifiers can be used to get more gain and to improve the performance of the amplifier
- These amplifiers such that the Output of first stage is connected to input of second stage
- Capacitor C3 is a decoupling capacitor that separates the two stages for DC bias point stability, this makes the two stages completely separate in DC analysis and their Q-points are not affected by each other
- C2 is used as a bypass capacitor for stage 1 and allows stabilization of the Q-point, if C2 is removed the input impedance of the amplifier can be improved

## Cascaded Systems

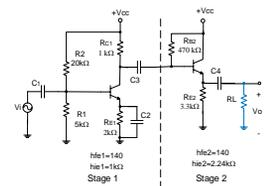

- The output of one amplifier is the input to the next amplifier
- The overall voltage gain is determined by the product of gains of the individual stages
- The DC bias circuits are isolated from each other by the coupling capacitors
- The DC calculations are independent of the cascading
- The AC calculations for gain and impedance are interdependent


# R-C Coupled BJT Amplifiers

Voltage gain:

$$A_v = A_{v1} A_{v2}$$

Input impedance,  
 first stage:
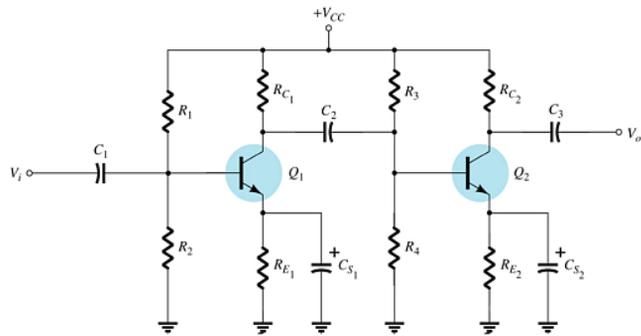
$$Z_i = R_1 \parallel R_2 \parallel h_{ie1}$$



Output impedance,  
 second stage:


$$Z_o = R_C$$

## Darlington Connection

- The Darlington circuit provides very high current gain, equal to the product of the individual current gains:

$$\bullet \beta_D = \beta_1 \beta_2$$

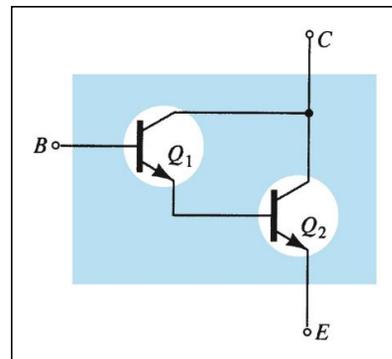- The practical significance is that the circuit provides a very high input impedance.



## DC Bias of Darlington Circuits

**Base current:**  $I_{BD} = I_{B1} = \frac{V_{CC} - V_{BED}}{R_B + (\beta_D + 1)R_E}$

**Emitter current:**  $I_{ED} = I_{E2}$   
 $I_{E2} = I_{B2}(\beta_2 + 1)$

$$I_{B2} = I_{E1}$$

$$I_{E1} = I_{B1}(\beta_1 + 1)$$

$$I_{E2} = I_{B1}(\beta_2 + 1)(\beta_1 + 1)$$


$$I_{ED} = \beta_D I_{BD}$$

**Emitter voltage:**  $V_E = I_{ED} R_E$


**Base voltage:**  $V_B = V_E + V_{BE}$   
 $V_{BED} = V_{BE1} + V_{BE2} \cong 1.4 \text{ V}$

**KVL for input loop :**  
 $V_{CC} - I_{B1} R_B - V_{BE1} - V_{BE2} - I_{E2} R_E = 0$
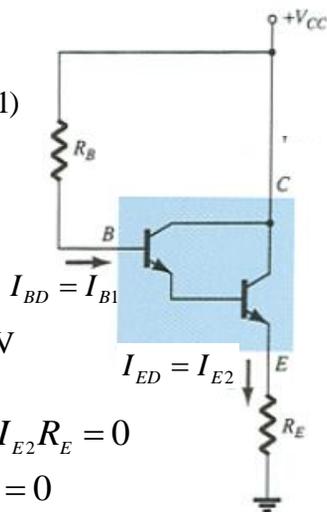
$$V_{CC} - I_{BD} R_B - V_{BED} - I_{ED} R_E = 0$$



## Darlington Pair

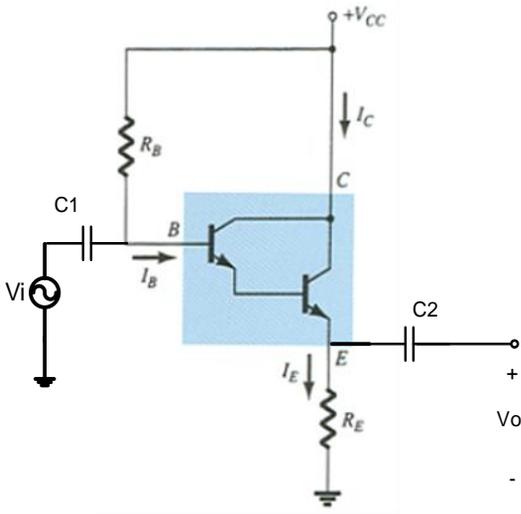


Find Ratio of  $\frac{i_{e2}}{i_{b1}}$  and  $A_v$

$$i_{e2} = i_{b2}(h_{fe2} + 1)$$

$$i_{b2} = i_{e1}$$

$$i_{e1} = i_{b1}(h_{fe1} + 1)$$

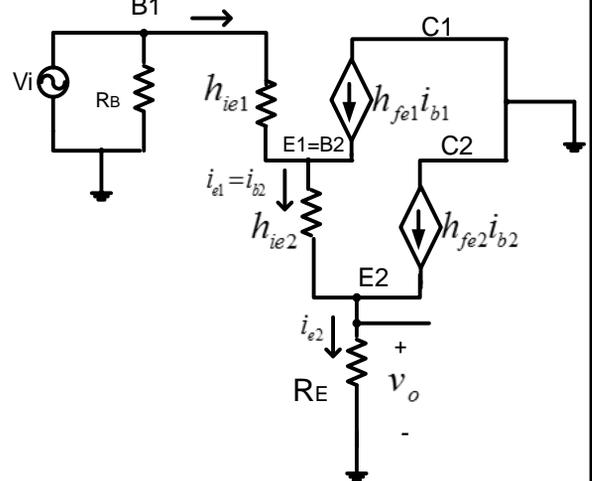

$$i_{e2} = i_{b1}(h_{fe1} + 1)(h_{fe2} + 1)$$

$$i_{ed} = h_{fed}i_{bd}$$

$$h_{fed} = (h_{fe1} + 1)(h_{fe2} + 1)$$

$$\cong h_{fe1}h_{fe2}$$


$$\cong h_{fe}^2, \text{ (if } h_{fe1} = h_{fe2} = h_{fe} \text{)}$$

2) Find  $A_v = \frac{v_o}{v_i}$

$v_o = i_{e2} R_E$

$i_{e2} = i_{b1} (h_{fe1} + 1)(h_{fe2} + 1)$

$i_{b1} = \frac{v_i}{Z_i}$

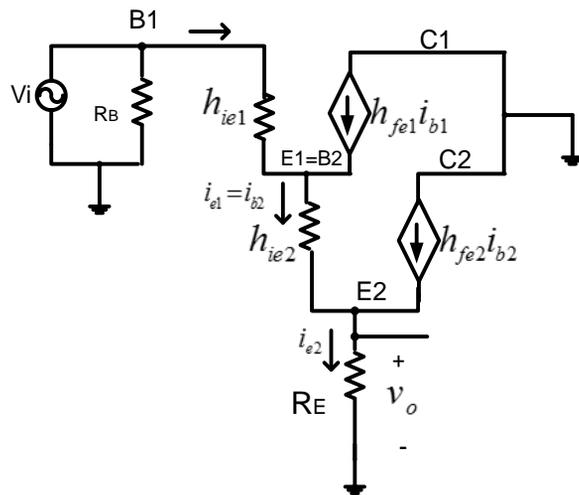

3) Find  $Z_i$   
 base equivalent circuit is needed

$h_{ie2} \Rightarrow h_{ie2}((h_{fe1} + 1))$  since it is reflected from emitter1 to base1

$R_E \Rightarrow R_E(h_{fe1} + 1)(h_{fe2} + 1)$  since it is reflected twice


1) From E2 to B2 (B2 = E1)  
 2) From E1 to B1

$$\Rightarrow Z_i = h_{ie1} + h_{ie2}(h_{fe1} + 1) + R_E(h_{fe1} + 1)(h_{fe2} + 1)$$

4) Find  $Z_o|_{V_s=0}$



**Zo**

Emitter equivalent circuit is needed

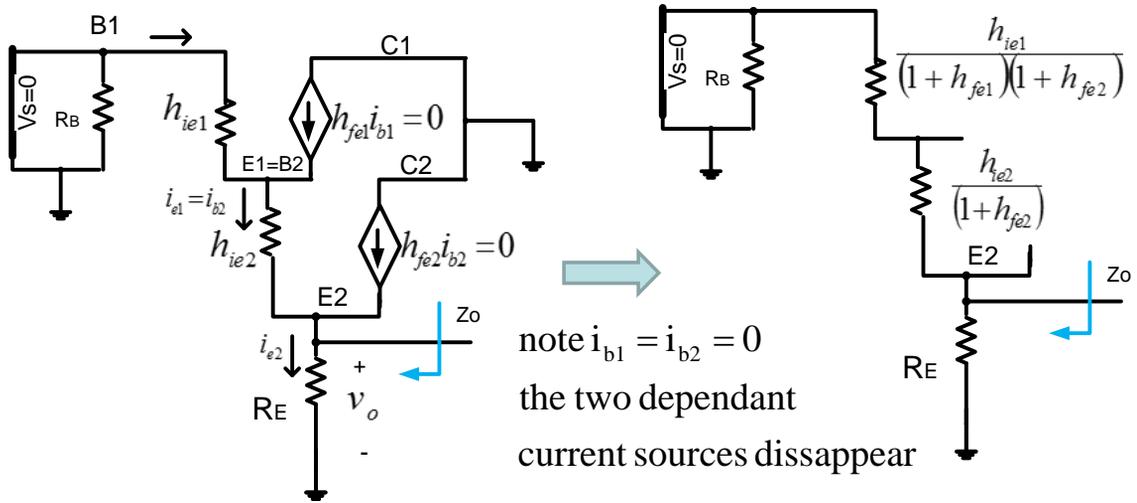

$$Z_o = \left( \frac{h_{ie1}}{(h_{fe1} + 1)(h_{fe2} + 1)} + \frac{h_{ie2}}{(h_{fe2} + 1)} \right) // R_E$$


## Darlington Simplified Model

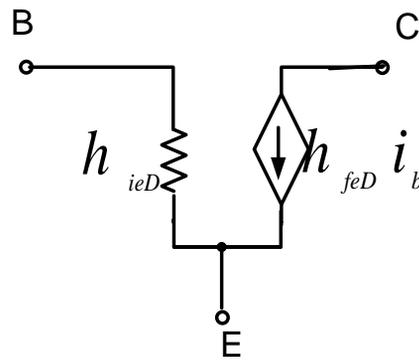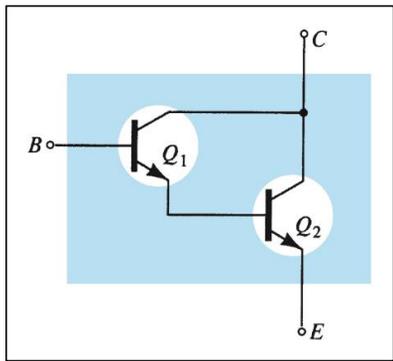

$$h_{ieD} \cong 2h_{ie}$$



$$h_{feD} \cong h_{fe1} \cdot h_{fe2}$$

## Base To Collector Feedback

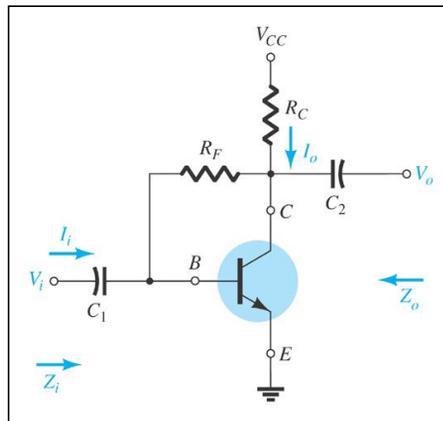



Exercise : Find  $A_v$ ,  $Z_i$  and  $Z_o$

## Base To Collector Feedback

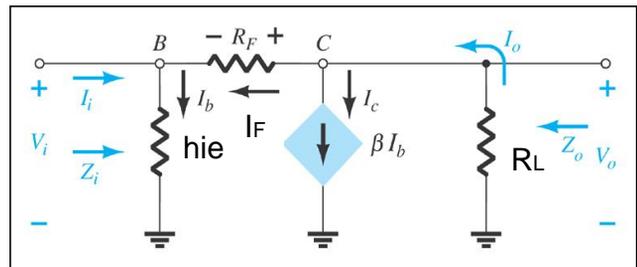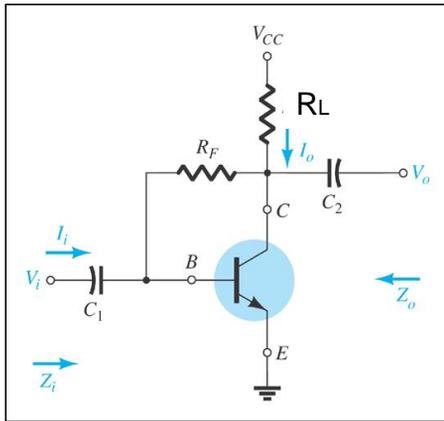

Exercise : Find  $A_v$ ,  $Z_i$  and  $Z_o$

## Base To Collector Feedback

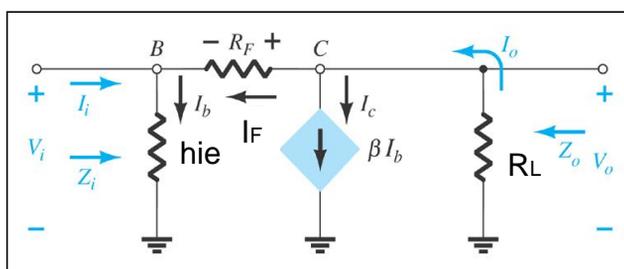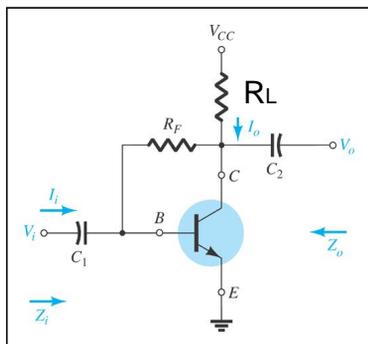

$$v_o = -i_o \cdot R_L$$

$$i_o = h_{fe} \cdot i_b + i_F$$

$$i_F = \frac{v_o - v_i}{R_F}$$

$$i_b = \frac{v_i}{h_{ie}}$$

$$v_o = - \left( h_{fe} \cdot \frac{v_i}{h_{ie}} + \frac{v_o - v_i}{R_F} \right) \cdot R_L$$

$$v_o = -R_L h_{fe} \cdot \frac{v_i}{h_{ie}} - \frac{v_o R_L}{R_F} + \frac{v_i R_L}{R_F}$$

$$v_o \left( 1 + \frac{R_L}{R_F} \right) = v_i \left( \frac{R_L}{R_F} - R_L \cdot \frac{h_{fe}}{h_{ie}} \right)$$

$$A_v = \frac{\left( \frac{R_L}{R_F} - R_L \cdot \frac{h_{fe}}{h_{ie}} \right)}{\left( 1 + \frac{R_L}{R_F} \right)}$$

$$Z_0|_{v_i=0} = R_F // R_L$$


$$Z_i = \frac{v_i}{i_i}$$

$$i_i = i_b - i_F = \left( \frac{v_i}{h_{ie}} - \frac{v_o - v_i}{R_F} \right)$$

$$Z_i = \frac{v_i}{i_i} = \frac{v_i}{\left( \frac{v_i}{h_{ie}} - \frac{v_o - v_i}{R_F} \right)}$$

$$= \frac{v_i}{\left( \frac{R_F v_i - h_{ie} (v_o - v_i)}{R_F h_{ie}} \right)}$$
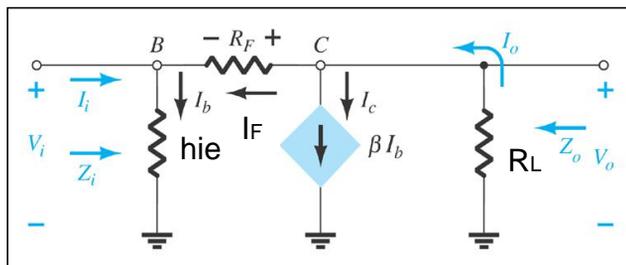
$$= \frac{v_i R_F h_{ie}}{(R_F v_i - h_{ie} (v_o - v_i))}$$



$$= \frac{v_i R_F h_{ie}}{((R_F + h_{ie})v_i - h_{ie}v_o)}$$

$$= \frac{R_F h_{ie}}{\left( (R_F + h_{ie}) - h_{ie} \frac{v_o}{v_i} \right)}$$

$$= \frac{R_F h_{ie}}{((R_F + h_{ie}) - h_{ie} A_v)}$$