

Student Name: _____

Important Notes:

- Turn off your cell phones
- Provide only one solution to each question using the specified method.
- Solve each question on a separate sheet.
- Write question number, Section # and ID on each sheet

Question 1 (25 points) (to assess "a" ABET SO)

Find V_o in Figure 1 using Nodal Analysis Method and Calculate the power absorbed delivered by the dependent source $2V_y$

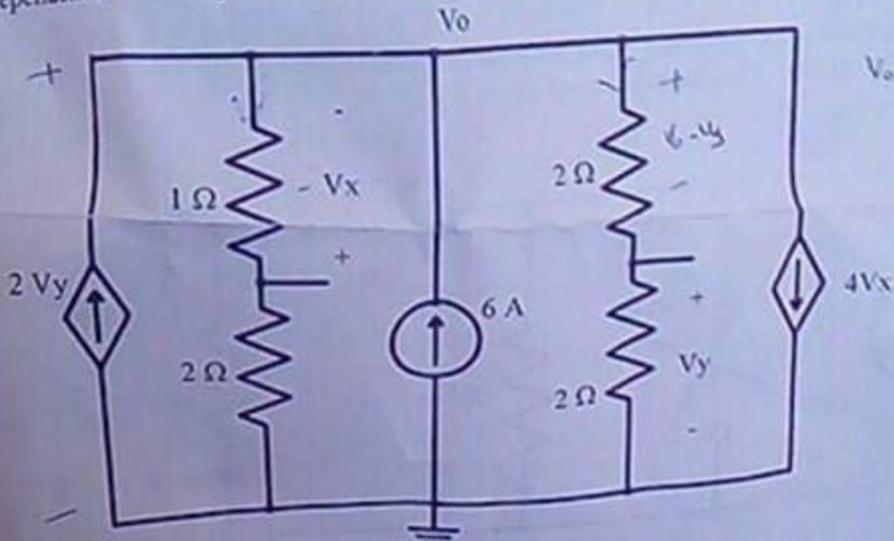


Figure 1

Question 2 (25 points) (to assess "a" ABET SO)

Find the value of R_L in Figure 2 for maximum power transfer, and then calculate the amount of maximum power absorbed by R_L .

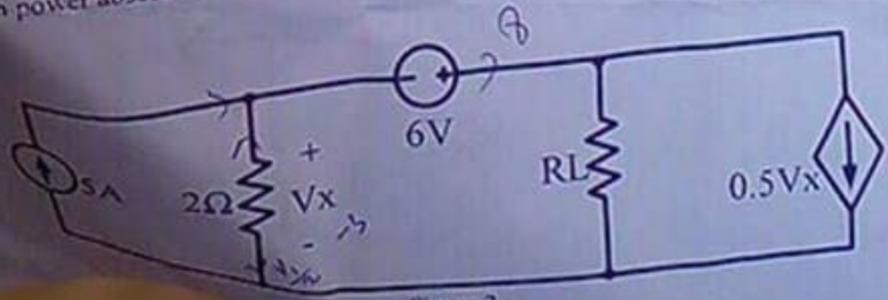


Figure 2

Question 3 (25 points) (to assess "a" ABET SO)

The switch in the circuit shown in Figure 3 has been open for a long time before Closing it at $t = 0$. Find $V_o(t)$ for for $t > 0$.

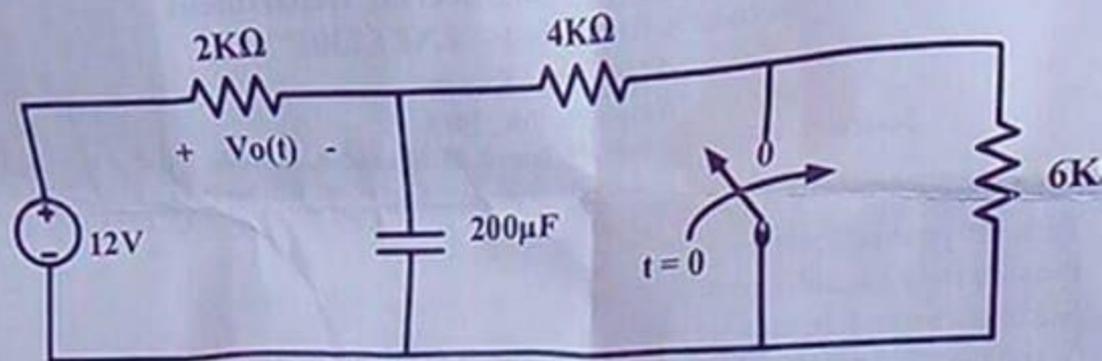


Figure 3

Question 4 (25 points) (to assess "e" ABET SO)

The switch in the circuit shown in Figure 4 has been open for a long time before Closing it at $t = 0$. Find the expression for $i(t)$ for $t > 0$


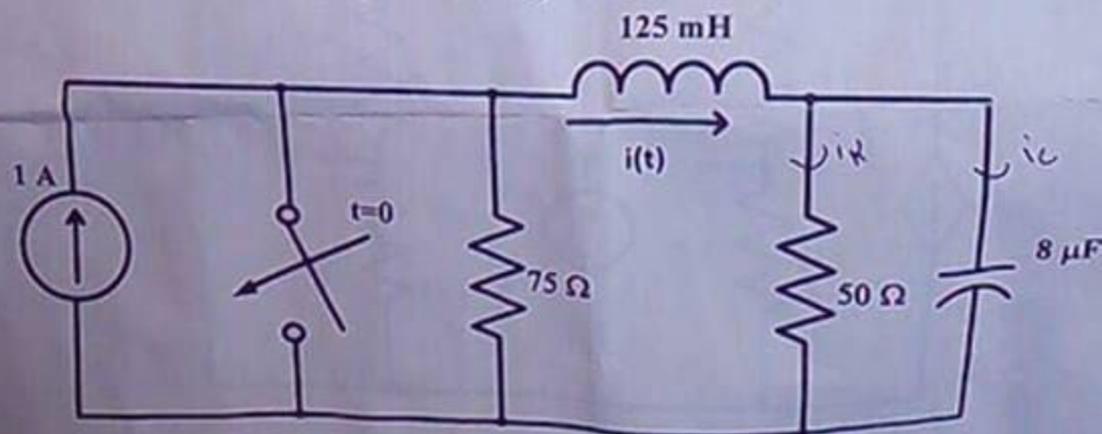



Figure 4

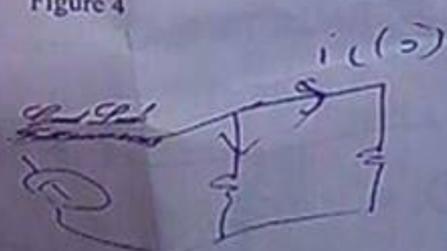

$$V_1 - V_0 = V_x$$

$$\frac{V_0 + V_x}{2} + \frac{V_x}{1} = 0 \dots (3)$$

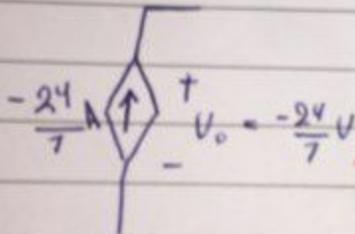
$$V_1 = -\frac{12}{7}V, V_x = \frac{8}{7}V, V_0 = -\frac{24}{7}V \quad \text{by calculation}$$



$$P = -I V_0 = -\left(-\frac{24}{7}\right) \cdot \left(-\frac{24}{7}\right) = -\frac{576}{49} = -11.755 \text{ W}$$

(supplied)

Q2

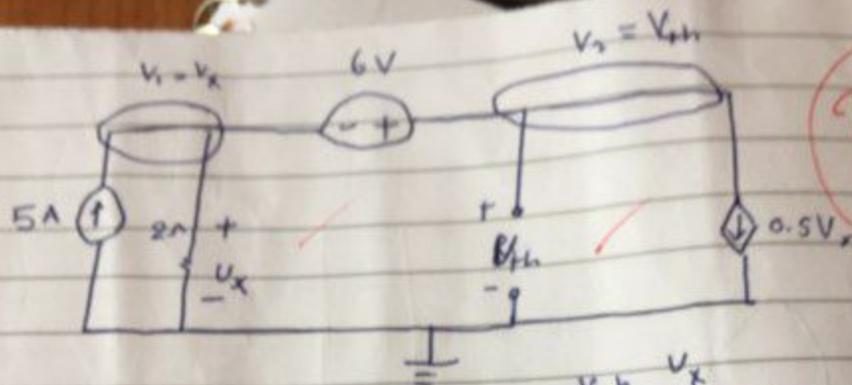

2.5/2.5

KCL at $(V_2, V_1) \rightarrow$ super node $\frac{V_2}{1} - \frac{V_1}{2} = 6V$

$V_1 = V_x$

$V_2 = V_{th}$

$$-5 + \frac{V_x}{2} + 0.5V_x = 0$$


$$1V_x = 5V$$

10/10

$$V_{th} - 5 = 6 \Rightarrow V_{th} = 11V$$

6V
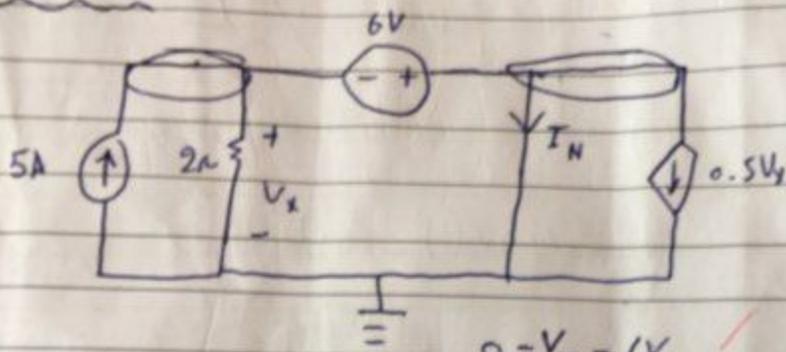
$$V_{th} - 5 = 6 \Rightarrow V_{th} = 11V$$



$$0 - V_x = 6V$$

$$\Rightarrow V_x = -6V$$

$$-5 + \frac{V_x}{2} + I_N + 0.5V_x = 0$$


$$I_N = 11A$$

$$R_L = R_{th} = \frac{V_{th}}{I_N} = \frac{11V}{11A} = 1\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_L} = \frac{11^2}{4} = 30.25W$$

Q.13

at $t=0^-$

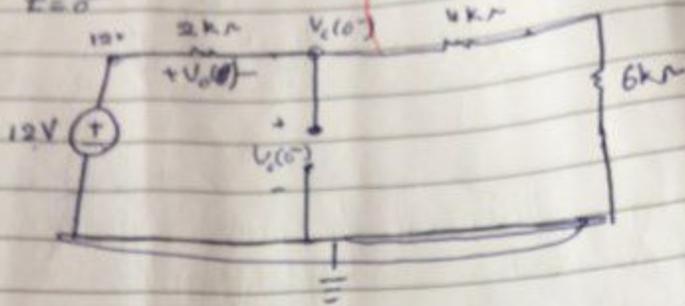

$$12 - V_c(0^-) = V_o(0^-)$$

$$\frac{V_c(0^-) - 12\text{V}}{2\text{k}} + \frac{V_c(0^-)}{10\text{k}} = 0$$

$$\frac{3}{5} V_c(0^-) = 6$$

$$V_c(0^-) = 10\text{V}$$

$$V_o(0^-) = 2\text{V}$$


$$\frac{V_c(0^-) - 12\text{V}}{2\text{k}} + \frac{V_c(0^-)}{10\text{k}} = 0$$

$$\frac{3}{5} V_c(0^-) = 6$$

$$V_c(0^-) = 10\text{V}$$

$$V_o(0^-) = 2\text{V}$$


at $t=0^+$

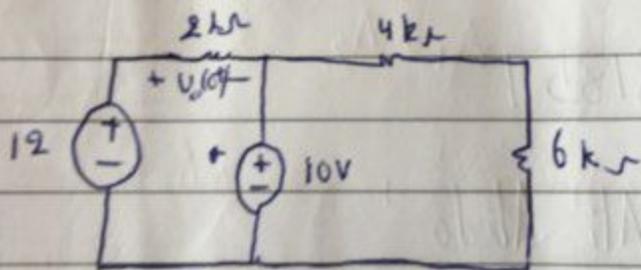

$$V_o(0^+) = 2\text{V}$$

at $t > 0$

$$\frac{24}{25}$$

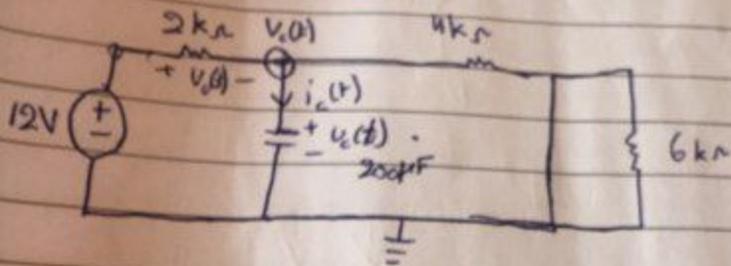

$$12 - V_o(t) = V_o(t)$$

$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t i_c(t) dt$$

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

KCL at $V_o(t)$

$$\frac{V_o(t) - 12}{2k\Omega} + C \frac{dV_o(t)}{dt} + \frac{V_o(t)}{4k\Omega} = 0$$

$$200 \times 10^{-6} \frac{dV_o(t)}{dt} + \frac{3}{4k} V_o(t) = 6$$

(-1)

$$200 \times 10^{-6} \frac{dV_c(t)}{dt} + \frac{3}{4 \times 10^3} V_c(t) = 6$$

$$V_c'(t) + \frac{3}{4 \times 200 \times 10^{-6}} V_c(t) = \frac{6}{200 \times 10^{-6}}$$

$$\Rightarrow V_c'(t) + 3750 V_c(t) = 3 \times 10^4$$

by

$$M(t) = e^{\int 3750 dt}$$

Solving

$$V_c(t) = e^{-3750t} \left[\frac{3 \times 10^4}{3750} e^{3750t} + A_1 \right]$$

$$V_c(t) = 8 + A_1 e^{-3750t}$$


$$V_c(0) = 8 + A_1 = 10 \Rightarrow A_1 = 2V$$

$$V_c(t) = 8 + 2e^{-3750t} \quad (V)$$

$$12 - (8 + 2e^{-3750t}) = V_o(t)$$

$$\therefore \Rightarrow V_o(t) = 4 - 2e^{-3750t} \quad (V) \quad \text{for } t > 0$$

at $t=0^-$

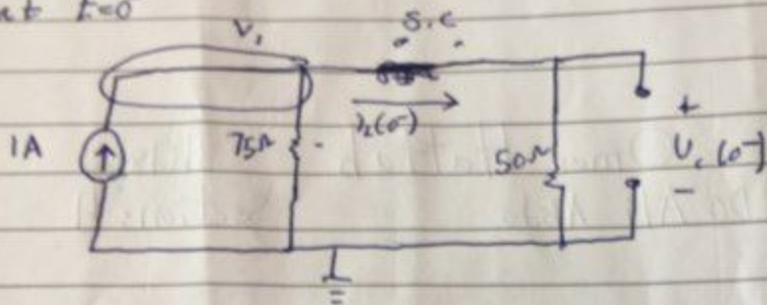


$$-1 + \frac{V_1}{75} + \frac{V_1}{50} = 0$$

$$V_1 = 30\text{V}$$

$$i_L(0^-) = \frac{30}{50} = 0.6\text{A}$$


$$V_C(0^-) = 30\text{V}$$

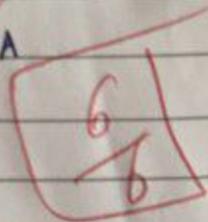

$F_n + \infty$

$V_n(1)$

For $t > 0$

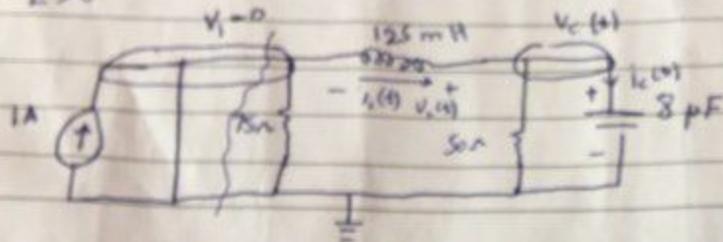

$$V_c(t) - 0 = V_c(t) \Rightarrow V_c(t) = V_c(t)$$

KCL at $V_c(t)$

$$-i_L(t) + \frac{V_c(t)}{50} + i_c(t) = 0$$

$$\Rightarrow i_c(t) = C \left(-L \frac{di_L^2(t)}{dt^2} \right)$$

$$V_c(t) = V_c(t) = -L \frac{di_L(t)}{dt}$$

$$i_L(t) = i_L(0) - \frac{1}{L} \int_0^t V_c(t) dt$$

$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t i_c(t) dt$$

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$\Rightarrow \frac{di_L(t)}{dt} = -\frac{1}{L} V_c(t)$$

$$\frac{di_L^2(t)}{dt} = -\frac{1}{L} dV_c(t)$$

$$-x \quad + i_L(t) + \frac{CL \frac{di_L^2(t)}{dt^2}}{dt^2} + \frac{L \frac{di_L(t)}{dt}}{50 dt} = 0$$

$$\frac{di_L^2}{dt^2} + \frac{di_L(t)}{50C dt} + \frac{1}{LC} i_L(t) = 0$$

$$s^2 + \frac{1}{50 \times 8 \times 10^{-6}} s + \frac{1}{12}$$

↓

$$s^2 + 2500s + 100 \times 10^4 = 0$$

$$s_1 = -500$$

$$s_2 = -2000$$

overdamped
response.

$$\frac{12}{12}$$

$$i_L(t) = A_1 e^{-500t} + A_2 e^{-2000t}$$

$$i_L(0^+) = i_L(0^-) = 0.6 = A_1 + A_2$$

$$\frac{di_L(t)}{dt} = -500A_1 e^{-500t} + -2000A_2 e^{-2000t}$$

$$\frac{di_L(0^+)}{dt} = +240 = +500A_1 + 2000A_2$$

$$\frac{0.6}{1}$$

$$\frac{di_L(t)}{dt} = -\frac{1}{L} V_L(t) = -\frac{1}{L} V(t)$$

$$A_1 = 0.64 \quad A_2 = -0.04$$

$$\frac{di_L(0^+)}{dt} = -\frac{1}{L} V(0^+) = +240$$

OK

$$\therefore i_L(t) = \cancel{0.64} e^{-2000t} - \cancel{0.04} e^{-500t} \quad \text{for } t > 0$$
$$= 0.64 e^{-500t} - 0.04 e^{-2000t}$$