



Electrical and Computer Engineering Department
Network Analysis I, ENEE2304

Name:

Second Makeup Exam


2018-05-13

No.:

Sec:

Q1) For all the time prior to zero, the switch is at position (a), at $t=0$ the switch was moved to position (b).

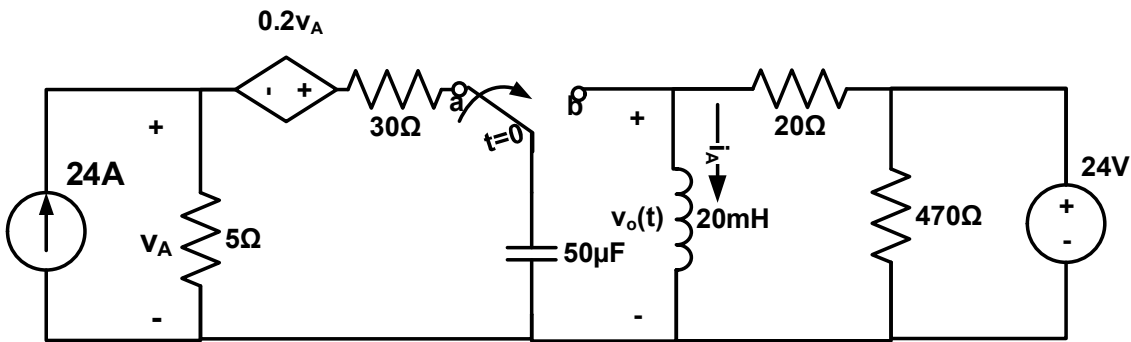- a) Find $V_L(0^+)$ and $i_L(0^+)$? (5 marks)
- b) Show that type of damping is under damped? (5 marks)
- c) For $t \geq 0$ find $i_A(t)$? (15 marks)



$$V_A(0^-) = 24 * 5 = 120V$$

$$V_L(0^+) = V_c(0^-) = V_A(0^-) + 0.2V_A(0^-) = 144V$$

$$i_L(0^+) = i_L(\infty) = i_L(0^-) = \frac{24}{20} = 1.2A$$

$$V_c(\infty) = 0V$$

- d) Show that type of damping is under damped? (10 marks)

$$\alpha = \frac{1}{2RC} = \frac{1}{2(20)(5 * 10^{-5})} = 500$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.02 * 5 * 10^{-5}}} = 1000$$

$$\alpha^2 < \omega^2$$


$$\omega_d = \sqrt{\omega_o^2 - \alpha_o^2} = \sqrt{10^6 - 25 * 10^4} = 1118$$

- e) For $t \geq 0$ find $i_A(t)$? (15 marks)

$$i_A(t) = i_L(\infty) + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$$

$$\begin{aligned}
&= 1.2 + (B_1 \cos 1118t + B_2 \sin 1118t)e^{-500t} \\
i_A(0) = i_L(0) = i_L(\infty) + B_1 &= 1.2 + B_1 = 1.2 \\
B_1 &= 0 \\
\frac{di_L}{dt}(0) = \frac{V_L(0^+)}{L} &= -\alpha B_1 + \omega_d B_2 = \\
&= (-0 + 1118B_2) = \frac{144}{0.2} \\
B_2 &= 0.644 \\
&= 1.2 + 0.644 \sin(96.8t)e^{-500t} \text{ A}
\end{aligned}$$

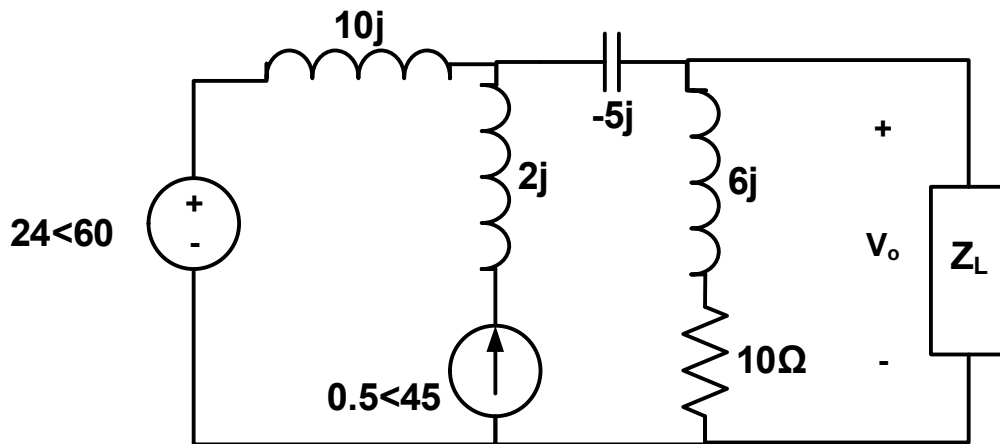Q2) Find the load Z_L that absorbs the maximum power? (15 marks)



$$Z_{th} = \frac{(-5j + 10j) * (10 + 6j)}{(-5j + 10j) + (10 + 6j)} = 1.13 + 3.76i = 3.92 \angle 73.27^\circ \Omega$$


$$Z_L = Z_{th}^* = 1.13 - 3.76i = 3.92 \angle -73.27^\circ \Omega$$

Q3) a) Plot the phasor diagram of voltage and current in the capacitor (5 marks)

b) Calculate the average power that absorbs by the resistor 10Ω . (5 marks)

c) Find the input voltage V_{in} in phasor and its power factor. (15 marks)

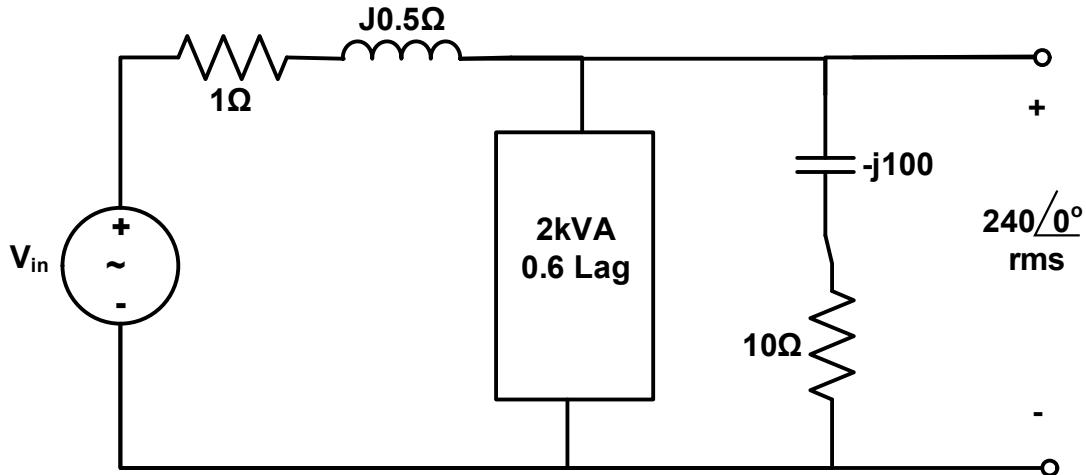d) Calculate the reactive power that absorbs by the inductor 0.5Ω . (5 marks)



a) Plot the phasor diagram of voltage and current in the capacitor (5 marks)

$$I_c = \frac{240\angle 0}{10 - 100j} = 0.24 + j2.38A = 2.4\angle 84A_{rms}$$

$$V_c = -100j * (0.24 + j2.38) = 238 - j 23.8 = 239\angle 5.7V_{rms}$$

b) Calculate the average power that absorbs by the resistor 10Ω. (5 marks)

$$P_{av} = I_c^2 R = 10 * 2.4^2 = 57.6W$$

c) Find the input voltage V_{in} in phasor and its power factor. (15 marks)

$$I_T = I_L + I_c$$

$$S_L = 2k\angle \cos^{-1} 0.6 = 2k\angle 53$$

$$I_L^* = \frac{S_L}{240\angle 0} = \frac{2k\angle 53}{240\angle 0} = \frac{25}{3}\angle 53 = 8.33\angle 53 = 5 + j6.67$$

$$I_L = 5 - j6.67 = 8.33\angle - 53$$

$$I_T = 5 - j6.67 + 0.24 + j2.38 = 5.24 - j4.29A_{rms} = 6.77\angle - 39.3A_{rms}$$

$$V_{in} = I_T(1 + 0.5j) + 240\angle 0 = 247.39 - j1.67 = 247.58\angle - 12.7V_{rms}$$



$$PF = \cos(-12.7 - -53) = 0.76 \text{ Laging}$$

d) Calculate the reactive power that absorbs by the inductor 0.5Ω.(5 marks)

$$Q_L = \omega LI_{rms}^2 = 0.5 * (6.77)^2 = 22.9VAR$$

Q4) a) Find $i_o(t)$? (25 marks)

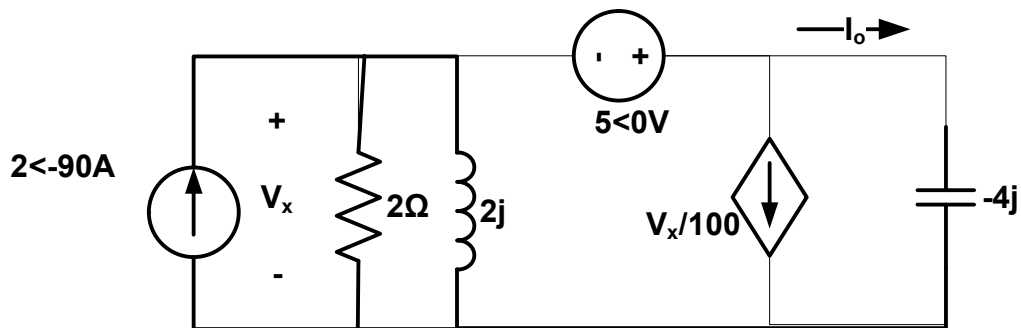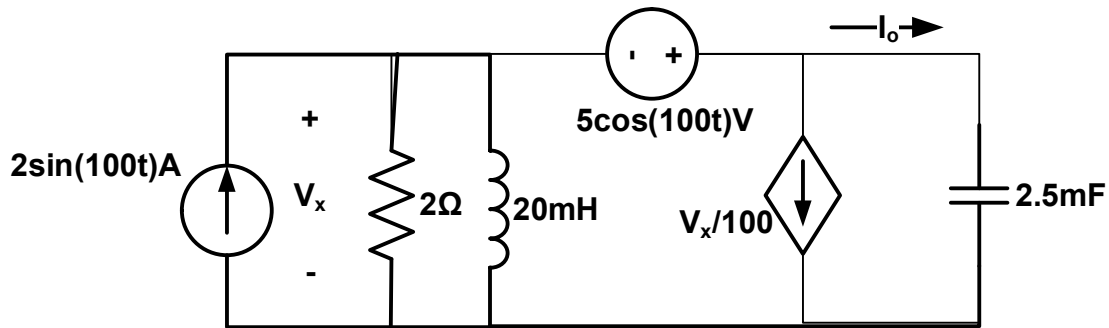b) Find the voltage source power factor?. (5 marks)



$$\begin{aligned}
 I_s &= 2 \sin(100t) = 2 \angle -90 \\
 -2 \angle -90 + \frac{V_x}{2} + \frac{V_x}{2j} + \frac{V_x}{100} + \frac{V_x + 5 \angle 0}{-4j} &= 0 \\
 (0.51 - 0.25j)V_x &= -3.25j \\
 V_x &= -5.14 - 2.52j = 5.72 \angle -153^\circ \\
 I_o = \frac{V_x + 5 \angle 0}{-4j} &= \frac{-5.14 - 2.52j + 5}{-4j} = 1.28 + 1.88j = 2.27 \angle 55.8^\circ \\
 I_o &= 2.27 \sin(100t + 55.8)
 \end{aligned}$$

b) Find the voltage source power factor?. (5 marks)

$$\begin{aligned}
 I_s &= 1.28 + 1.88j + \frac{-5.14 - 2.52j}{100} = 1.31 + 1.83j = 2.25 \angle 54.4^\circ \\
 PF &= \cos(0 - 54.4) = 0.58 \text{ Leading}
 \end{aligned}$$