
Birzeit University
Faculty of Engineering
Electrical Engineering Department
Network Analysis I – ENEE 232
First Hour Exam

6 March 2012 Instructors: Hussein Zeitawi & Ashraf Al-Rimawi Time: 60 min

Student Name: _____ **ID Number:** _____

Question # 1:

From the circuit shown in figure 1, and Figure 2

- a. The value of α constant
- b. The value of μ constant

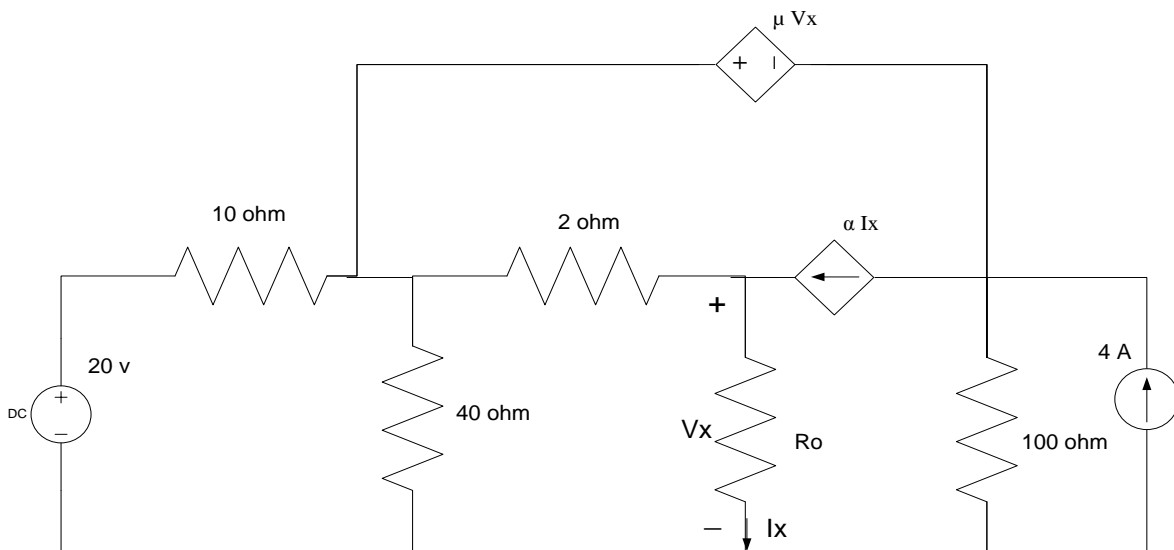


Fig 1

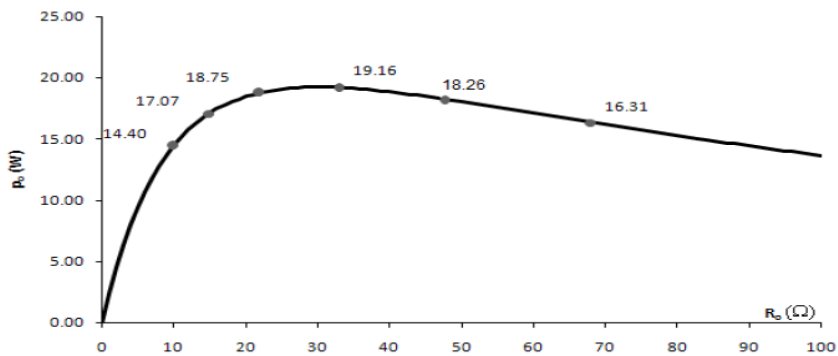


Fig 2

Question # 2:

For Circuit shown in figure 3, Use Superposition Technique to find the value of V_x

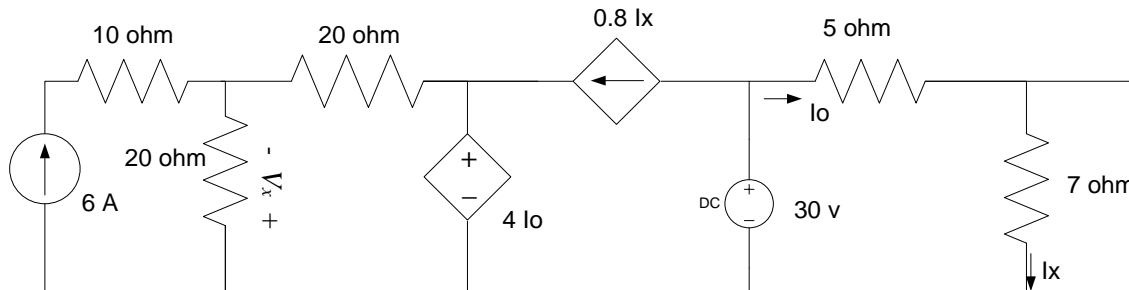


Fig 3

Question # 4:

For the circuit shown in Figure 4, Find $V_o(t)$ for $t > 0$.

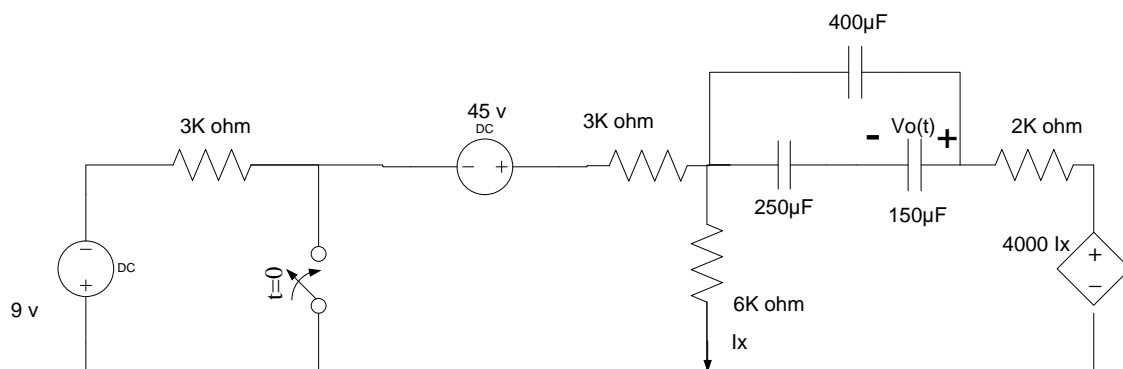


Fig 4

... With Best Wishes ...



DEPARTMENT OF ELECTRICAL ENGINEERING

ENEE231: Network Analysis I

Final Exam

Date: 16 July 2013 Time: 2 pm – 4.30pm – 150 minutes

Calculators must not be used to store text and/or formulae nor be capable of communication.

Invigilators may require calculators to be reset.

Instructors: Mr. Hakam Shehadeh & Mr. Ashraf Al-Rimawi

Question One [10%]

Find V_x using **Nodal Analysis** only.

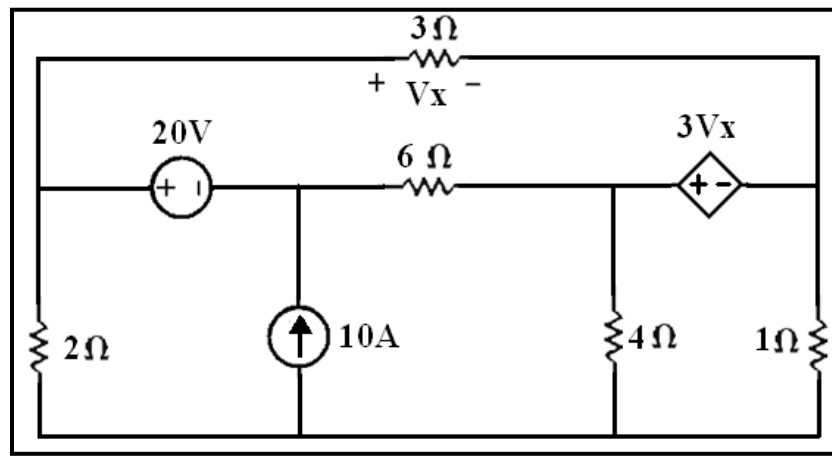


Figure Q1

Question Two [20%]

For the following circuit shown in figure Q2. Find V_x

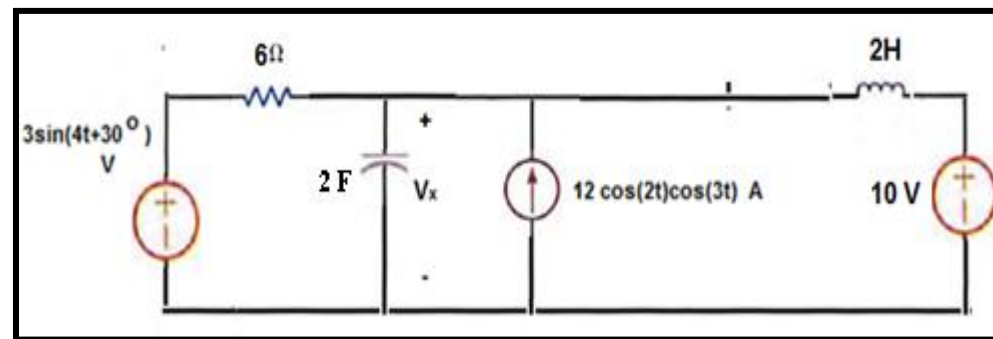


Figure Q2

Question Three [15%]

For the network in figure Q3.

- 1-compute the input source voltage V_s .
- 2-compute the total complex power supplied by the source.
- 3- compute the input power factor.

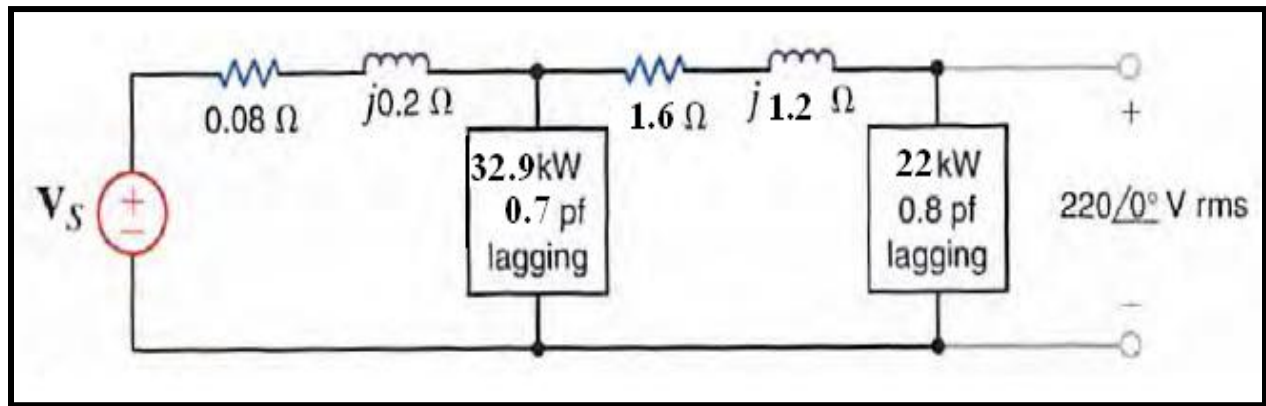


Figure Q3

Question Four [20%]

A three-phase positive sequence supplies **20KVA** with power factor **0.6** lagging to parallel combination of Δ connected and Y-connected loads. The Y-connected uses **10KVA** at reactive factor **0.6** lagging and has c-phase current of **25.7-j30.6 A**

- a. Find the a-phase line current
- b. Find the impedance per phase of the Δ connected load
- c. Find the magnitude of the line voltage
- d. Draw the single phase equivalent for the a-phase

Question Five [15%]

Find n for maximum power supplied to the $80\ \Omega$ load.

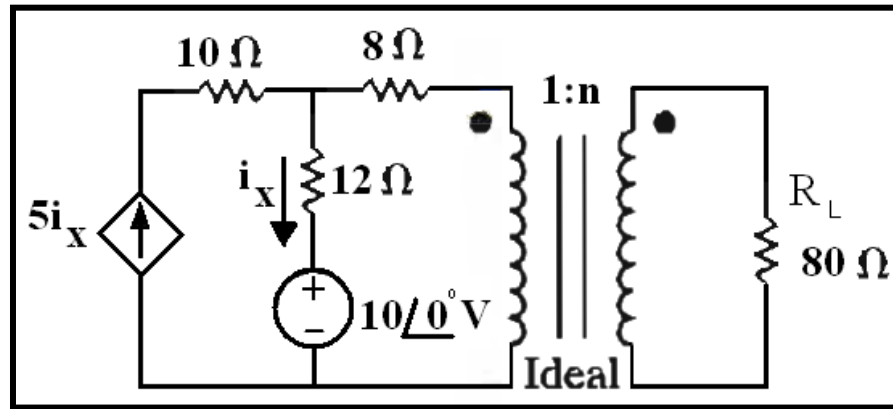


Figure Q5

Question Six [20%]

Find V_o in the following circuit in Figure Q6

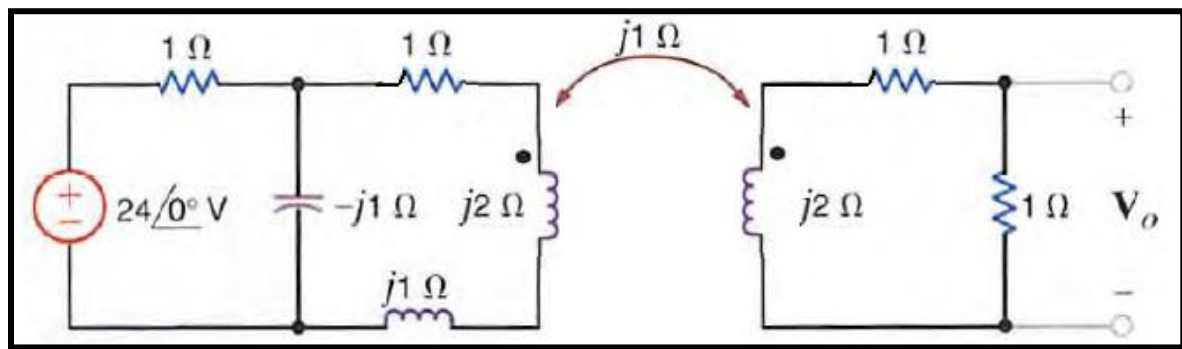


Figure Q6

END OF PAPER

Question #3 (20 Marks_10 each): The unbalanced -three phase loads shown in figure 3 is fed from balanced , positive (abc) sequence three phase Y-connected source, if $Z_A = 20\angle 30^\circ \Omega$, $Z_B = 60\angle 0^\circ \Omega$, $Z_C = 20\angle -30^\circ \Omega$.

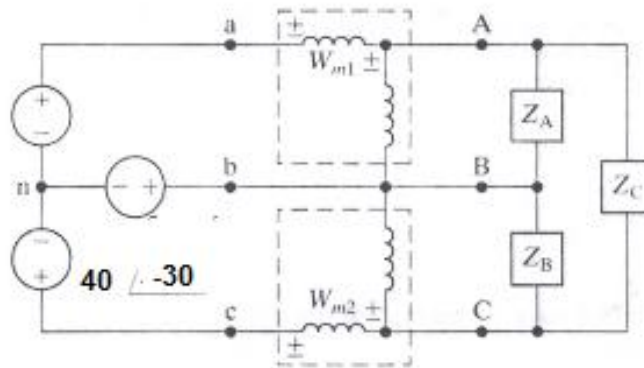


Fig 3

- Calculate the reading of each wattmeter
- Verify that the sum of the two wattmeter readings equals the total average power delivered to the load.

Question #4 (20 Marks):

Three 100 Vrms loads are connected in parallel. Load 1 is a 50 Ω resistor in series with an inductive reactance of 40 Ω. Load 2 absorbs an average power of 500 W at 0.75 lagging power factor. Load 3 absorbs an apparent power of 600 VA at 0.9 lagging power factor. Assume the circuit is operating at 60 Hz. Compute the value of a capacitor that would correct the power factor to 1 if placed in parallel with the loads.

Question #5 (20 Marks_10 each):

- Find the impedance Z_{ab} in the circuit in figure 4 if $Z_L = 200 + j150 \Omega$

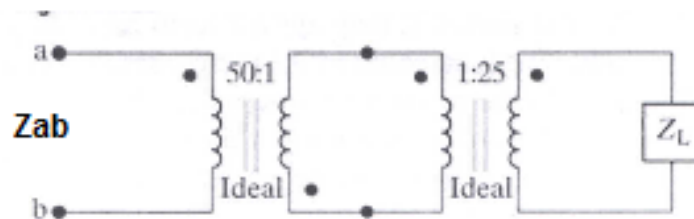


Fig 4

B) For the circuit in figure 5 , find $v_0(t)$ using **Source Transformation**



Best wishes