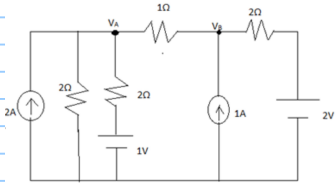


ch4 Quiz

1- Find V_A and V_B using Node-Voltage method in the given circuit.



- a) 2.5V, 3.6V
- b) 2.875V, 3.25V**
- c) 2.66V, 3.47V
- d) 3.15V, 2.76V

$$\textcircled{1} \quad -2 + \frac{V_A}{2} + \frac{V_A - 1}{2} + \frac{V_A - V_B}{1} = 0$$


$$2V_A - V_B = 2.5 \quad \textcircled{1}$$

$$\frac{V_B - V_A}{1} - 1 + \frac{V_B - 2}{2} = 0$$

$$-V_A + \frac{3}{2}V_B = 2 \quad \textcircled{2}$$

$$V_A = 2.875 \text{ V} \quad \times \quad V_B = 3.25 \text{ V}$$

2- Find V_3 in the circuit given below

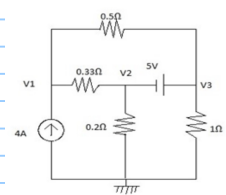

- a) 4.833V**
- b) 2.616V
- c) -4.833V
- d) -2.616V

V_1

$$\frac{V_1 - V_2}{0.33} - 4 + \frac{V_1 - V_3}{0.5} = 0$$

$$\frac{166}{33}V_1 - \frac{10}{33}V_2 - 2V_3 = 4 \quad \textcircled{1}$$

V_2

$$\frac{V_2 - V_1}{0.33} + \frac{V_2}{0.2} + \frac{V_3}{1} + \frac{V_3 - V_1}{0.5} = 0$$

$$-\frac{166}{33}V_1 + \frac{265}{33}V_2 + 3V_3 = 0 \quad \textcircled{2}$$

Super node

$$V_3 - V_2 = 5 \quad \textcircled{3}$$


$$5V_2 + V_3 = 4 \quad \textcircled{1+2}$$

$$5(V_3 - 5) + V_3 = 4$$

$$6V_3 - 25 = 4$$

$$V_3 = 29/6 \Rightarrow V_3 = 4.833 \text{ V}$$

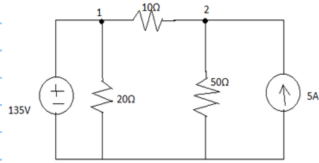4- What is the voltage at 2nd terminal in the given circuit?



- a) 132.57V
- b) 154.16V
- c) 173.25V
- d) 123.57V


$$V_1 = 135 \text{ V}$$

$$\frac{V_2 - 135}{10} + \frac{V_2}{500} - 5 = 0$$

$$\frac{3}{25} V_2 = 18.5$$

$$V_2 = 154.16 \text{ V}$$

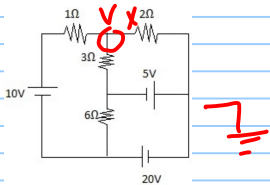5- Find the current flowing through 3Ω resistor in the given circuit.




- a) 2.57A
- b) 3.04A
- c) 4.78A
- d) 5.89A

$$\frac{V_x - 10}{1} + \frac{V_x + 5}{3} + \frac{V_x}{2} = 0$$


$$\frac{11}{6} V_x = \frac{25}{3}$$

$$V_x = \frac{50}{11} \text{ V}$$
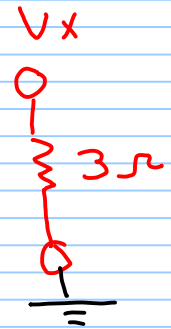
$$I_{3\Omega} = \frac{V_x + 5}{3} = 3.181 \text{ A}$$



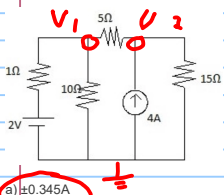6- Calculate the current flowing through 10Ω resistor in the circuit shown below



- a) 0.345A
- b) 0.985A
- c) 1.217A
- d) 2.782A

$$V_1 - 2 + \frac{1}{10} V_1 + \frac{1}{5} V_1 - \frac{1}{5} V_2 = 0$$

$$1.3 V_1 - 0.2 V_2 = 2 \quad \text{--- (1)}$$

$$\frac{1}{5} V_2 - \frac{1}{5} V_1 - 4 + \frac{1}{15} V_2 = 0$$


$$0.2 V_1 + \frac{4}{15} V_2 = 4 \quad \text{--- (2)}$$

$$V_1 = 3.448 \text{ V}$$

$$V_2 = 12.413 \text{ V}$$

$$I_{10\Omega} = \frac{V_1}{10} = 0.3448 \text{ A}$$

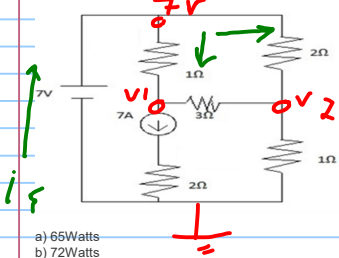7. Find the power delivered by the voltage source in the network given below.



- a) 65Watts
- b) 72Watts
- c) 63Watts
- d) 76Watts

$$7 + \frac{V_1 - V_2}{3} + \frac{V_1 - 7}{1} = 0$$

$$\frac{4}{3}V_1 - \frac{1}{3}V_2 = 0 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{3} + \frac{V_2}{1} + \frac{V_2 - 7}{2} = 0$$

$$-\frac{1}{3}V_1 + \frac{11}{6}V_2 = \frac{7}{2} \quad \text{--- (2)}$$


$$V_1 = 0.5V, V_2 = 2V$$

$$\therefore i_f = i_{1\Omega} + i_{2\Omega} = \frac{7 - 0.5}{1} + \frac{7 - 2}{2} = 9A$$

$$\therefore P = -(7)(9) = -63W$$

$$= 63W \text{ delivered!}$$

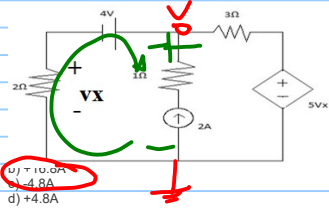8. Find the value of V_x in the circuit given below.



- a) +10.8A
- b) -4.8A
- c) -4.8A
- d) +4.8A

$$\frac{V - 4}{2} - 2 + \frac{V - 5V_x}{3} = 0$$

$$\frac{5}{6}V - 4 - \frac{5}{3}V_x = 0$$

$$\frac{5}{6}V - 4 - \frac{5}{3}V + \frac{20}{3} = 0$$

But $V_x = (V - 4)$

$$-V_x - 4 + V = 0$$

$$V_x = V - 4$$

$$\frac{5}{6}V - \frac{5}{3}V - 4 - \frac{20}{3} = 0$$

$$\frac{5}{6}V = \frac{32}{3}$$

$$V = 12.8V$$

$$+ 3.2V$$

$$\therefore V_x = -16.8V$$