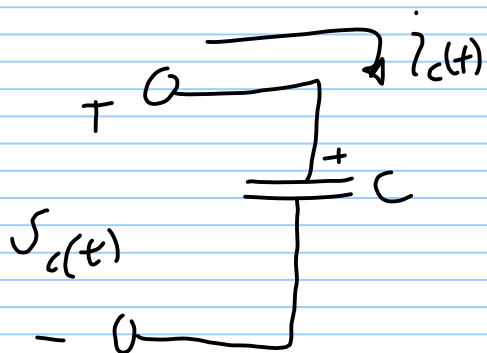


Response of first-order RL & RC circuits



$$i_c(t) = C \frac{d}{dt} v_c(t)$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(t) dt + \underline{v_c(0)}, \text{ for } t > 0$$


initial voltage of the capacitor

at $t = 0^+$

$$v_c(0^+) = \frac{1}{C} \int_{0^-}^{0^+} i_c(t) dt + v_c(0^-)$$

$$v_c(0^+) = v_c(0^-)$$

at $t = 0$

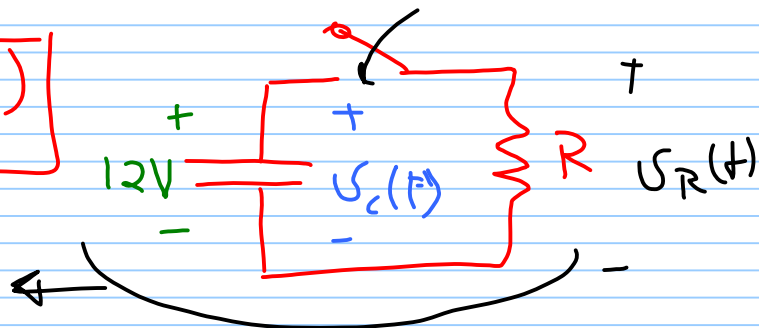

$$v_c(0^-) = 12V$$


$$v_c(0^+) = 12V$$

$$v_c(\infty) = \text{zero}$$

$$v_R(0^-) = \text{zero}$$

$$v_R(0^+) = 12V$$

0.0000001

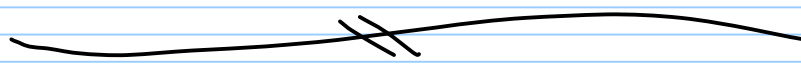


1. The current through a capacitor is zero if the voltage across it is not changing with time.


$$i_c(t) = C \frac{dV_c(t)}{dt} \quad \rightarrow \text{steady state}$$

∴ at steady state
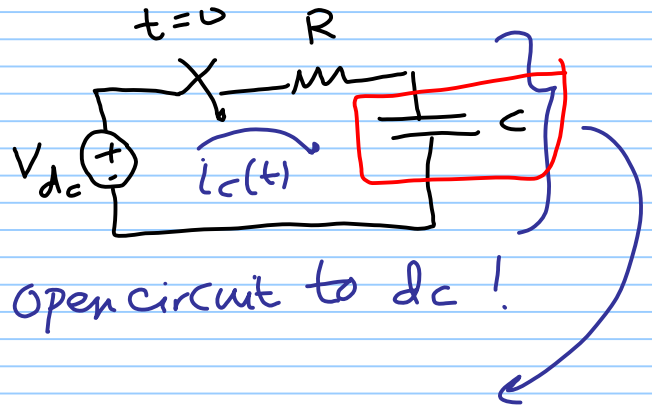
$$\boxed{i_c(\infty)} \text{ OR } \boxed{i_c(\text{steady state})} = \text{zero}$$



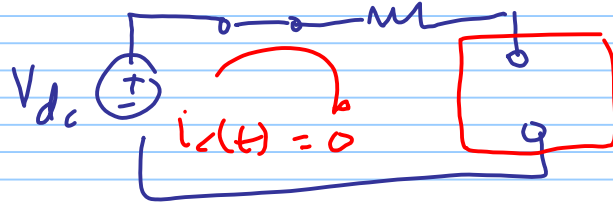A capacitor is therefore an open circuit to dc!





2. A finite amount of energy can be stored in a capacitor even if the current through the capacitor is zero.
3. The capacitor never dissipate energy, but only store it.

$$V_c(0^-) = V_c(0^+)$$


4. it is impossible to change the voltage across a capacitor by a finite amount in zero time,

5. At $t = 0^+$

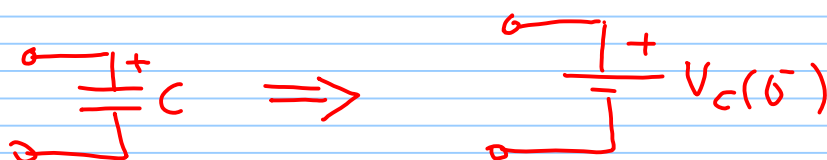


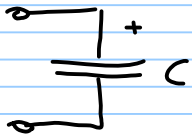

@ $t = 0^+$

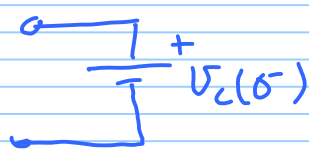


@ $t = \infty$

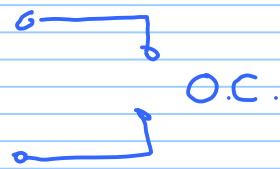


charging


discharging

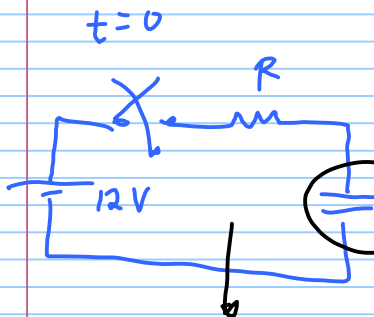

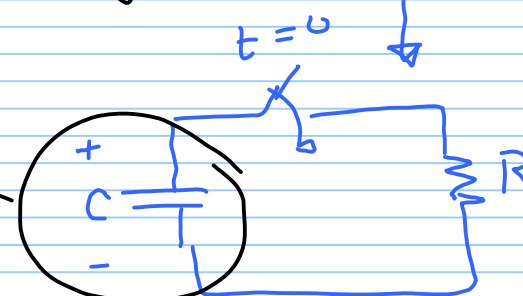@ $t = \infty$
 $V_C(\infty) = 12V$
 $i_C(\infty) = \text{zero}$



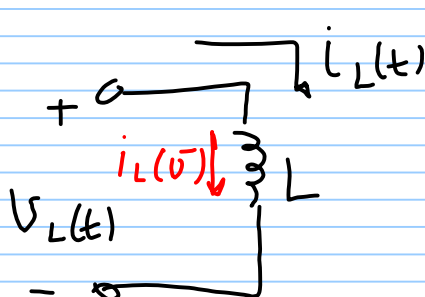@ $t = 0^-$
 $V_C(0^-) = 12V$
 $V_C(0^+) = 12V$
 @ $t = \infty$
 $V_C(\infty) = \text{zero}$
 $i_C(\infty) = \text{zero}$



$$V_L(t) = L \frac{d}{dt} i(t)$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t V_L(t) dt, \text{ for } t \geq 0$$

1. There is no voltage across an inductor if the current through it is not changing with time.
 An Inductor is therefore a short circuit to dc.

@ $t = \infty$

$$V_L(\infty) = L \frac{d}{dt} \underbrace{i_L(\infty)}_{\text{const.}} \\ = \text{zero}$$

2. A finite amount of energy can be stored in an inductor even if the voltage across the inductor is zero.
3. The inductor never dissipate energy, but only store it.

4.
$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(t) dt, t \geq 0$$




@ $t = 0^+$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} \cancel{V_L(t) dt}^{\text{zero}}$$

$$\boxed{i_L(0^+) = i_L(0^-)}$$

it is impossible to change the current through an inductor by a finite amount in zero time, for this requires an infinite voltage across the inductor.


@ $t = 0^+$

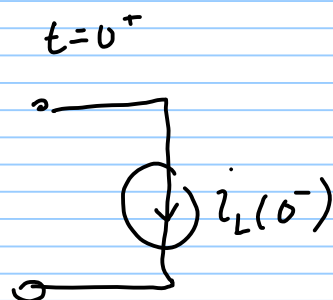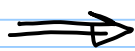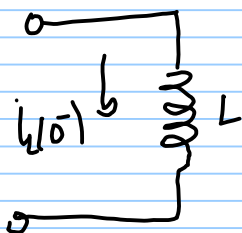

$t = \infty$

$$V_L(t) = L \frac{d}{dt} i_L(t)$$

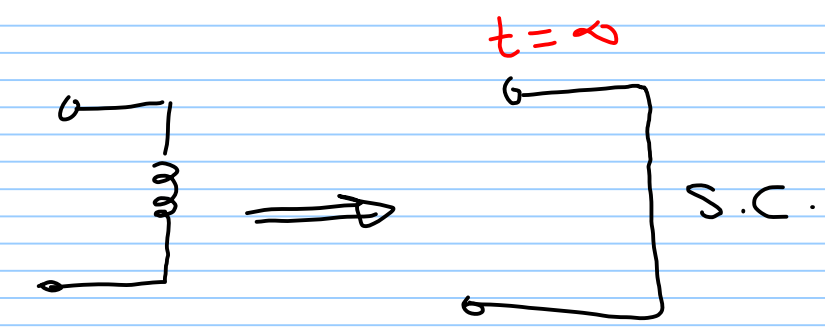An inductor is therefore a short circuit to dc.




First Order Circuit

$R + L$ } RL, RC circuits.
 OR $R + C$ }

Natural Response of 1st order circuit


↳ discharging.

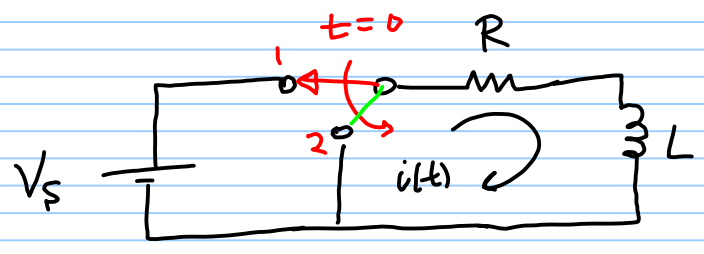

find $i(t)$ for $t > 0$


$$V_L = L \frac{di}{dt}$$

1) for $t < 0$; $t = 0^-$

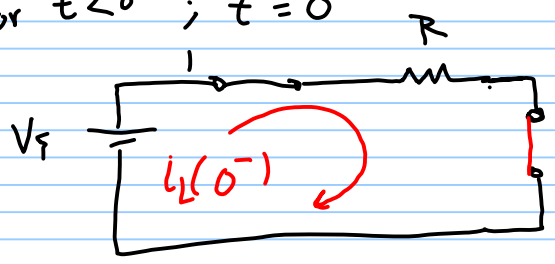

$$\text{so } i_L(0^-) = \frac{V_S}{R}$$

2) for $t > 0$

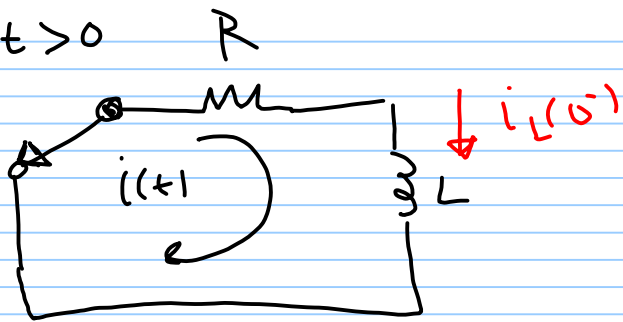

→ KVL

$$R i(t) + L \frac{d}{dt} i(t) = 0$$

$$i(t) = A e^{st} \quad \text{for } t > 0$$