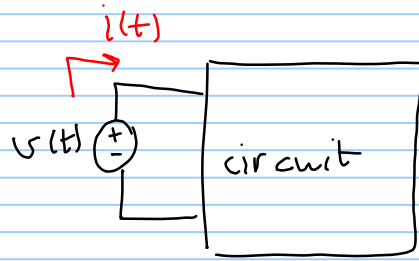


Chapter 10 Sinusoidal steady state Power calculation

Instantaneous Power $P(t)$



$$P(t) = v(t) i(t)$$

$$= V_m \cos(\omega t + \theta_v) I_m \cos(\omega t + \theta_i)$$

$$= \frac{1}{2} V_m I_m [\underbrace{\cos(\theta_v - \theta_i)}_{\text{constant}} + \underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{\text{Twice the excitation frequency}}]$$

$$\rightarrow v(t) = V_m \cos(\omega t + \theta_v)$$

$$\rightarrow i(t) = I_m \cos(\omega t + \theta_i)$$

Average Power: Real Power

$$P_{av} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\therefore P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \boxed{W} \text{ watt}$$

R

$$\begin{cases} \theta_v - \theta_i = \text{Zero} \\ \theta_z = 0^\circ \end{cases}$$

$$\therefore P_{av} = \frac{1}{2} V_m I_m$$

$$= \frac{1}{2} \frac{V_m^2}{R}$$

$$= \frac{1}{2} I_m^2 R$$

L

$$\begin{cases} \theta_v - \theta_i = 90^\circ \\ \theta_z = 90^\circ (j\omega L) \end{cases}$$

$$P_{av} = \text{Zero}$$

$$\boxed{\cos(90^\circ) = 0}$$

C

$$\begin{cases} \theta_v - \theta_i = -90^\circ \\ \theta_z = -90^\circ (-j \frac{1}{\omega C}) \end{cases}$$

$$P_{av} = \text{Zero}$$

$$\boxed{\cos(-90^\circ) = 0}$$


Reactive Impedances absorb NO average power

Effective OR rms value

RMS:- Root Mean Square

$$V_{eff} = V_{rms} = \frac{V_m}{\sqrt{2}} \quad , \quad I_{eff} = I_{rms} = \frac{I_m}{\sqrt{2}}$$
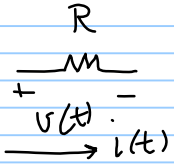
$$\begin{aligned} P_{av} &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= V_{rms} I_{rms} \cos(\theta_v - \theta_i) \end{aligned}$$



$$P_{av} = V_{rms} I_{rms} \cos(0^\circ), \text{ where } \theta_v - \theta_i = 0^\circ \text{ (R)}$$

$$\Rightarrow V_{rms} = R I_{rms}$$

$$P_{av} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

Apparent Power & Power Factor

$$P_{av} = \underbrace{V_{rms} I_{rms}}_{\text{apparent power}} \underbrace{\cos(\theta_v - \theta_i)}_{\text{power factor}}, (W)$$

P_a
(VA)

PF

$$\infty P_{av} = P_a \cdot PF$$

 $\theta_v - \theta_i = 0$ $\therefore PF = 1$ unity PF	 $\theta_v - \theta_i = 90^\circ$ $\therefore PF = 0$	 $\theta_v - \theta_i = -90^\circ$ $\therefore PF = 0$
--	---	--

\rightarrow for inductive load

$$90^\circ > \theta_v - \theta_i > 0$$

$$1 > PF > 0$$

\rightarrow for capacitive load

$$0 > \theta_v - \theta_i > -90^\circ$$

$$1 > PF > 0$$

} lagging PF (since i lags v)

$$\cos(\alpha) = \cos(-\alpha)$$

} leading PF (since i leads v)


Complex Power

$$\vec{S} = \vec{V}_{rms} \cdot \vec{I}_{rms}^*$$

$$= V_{rms} I_{rms} \angle \theta_v - \theta_i$$

(Polar)
(Rectangular)

$$\vec{V}_{rms}$$

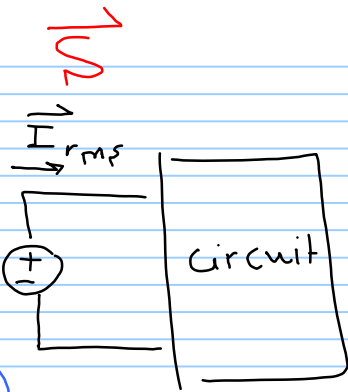

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

Par
average power W

Q
Reactive Power VAR
 $\vec{I}_{rms} = I_{rms} \angle \theta_i$

$$\vec{V}_{rms} = V_{rms} \angle \theta_v$$

$$\vec{S} = P_{av} + jQ$$

VA W VAR

$\rightarrow P_{av} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$
 $\rightarrow Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$

$$P_{av} = \text{Real}[\vec{S}]$$

$$Q = \text{Imaginary}[\vec{S}]$$

$$|\vec{S}| = \sqrt{P_{av}^2 + Q^2} \quad \angle \tan^{-1} \frac{Q}{P_{av}}$$

$$\vec{S} = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$\vec{S} = P_{av} + jQ$$

R

$$\theta_v - \theta_i = 0$$

$$P_{av} = V_{rms} I_{rms}$$

$$Q_R = \text{Zero}$$

L ($j\omega L$)

$$\theta_v - \theta_i = 90^\circ$$

$$P_{av} = \text{Zero}$$

$$Q_L = V_{rms} I_{rms}$$

θ_i V_{rms} (not \vec{V}_{rms})

$$V_{rms} = (\omega L) I_{rms}$$

$$Q_L = \omega L I_{rms}^2 = \frac{V_{rms}^2}{\omega L}$$

C ($-j \frac{1}{\omega C}$)

$$\theta_v - \theta_i = -90^\circ$$

$$P_{av} = \text{Zero}$$

$$\sin(-90^\circ) = -1$$

$$Q_C = -V_{rms} I_{rms}$$

$$I_{rms} = \omega C V_{rms}$$

$$Q_C = -\frac{I_{rms}^2}{\omega C} = -\omega C V_{rms}^2$$

R
 $\theta_v - \theta_i = 0$
 $P_{av} = V_{rms} I_{rms}$
 $Q_R = \text{Zero}$

L ($j\omega L$)
 $\theta_v - \theta_i = 90^\circ$
 $P_{av} = \text{Zero}$

C ($-j\frac{1}{\omega C}$)
 $\theta_v - \theta_i = -90^\circ$
 $P_{av} = \text{Zero}$

$$Q_L = V_{rms} I_{rms}$$

$\delta: V_{rms}$ (not \vec{V}_{rms})

$$V_{rms} = (\omega L) I_{rms}$$

$$Q_L = \omega L I_{rms}^2 = \frac{V_{rms}^2}{\omega L}$$

X_L

$$Q_L = (X_L) I_{rms}^2$$

$$Q_C = -V_{rms} I_{rms}$$

$$I_{rms} = \omega C V_{rms}$$

$$Q_C = -\frac{I_{rms}^2}{\omega C} = -\omega C V_{rms}^2$$

X_C

$$Q_C = X_C I_{rms}^2$$

chapter 9

$$Z = R + jX$$


impedance

reactance


for $j\omega L$ $X_L = \omega L$

for $-j\frac{1}{\omega C}$ $X_C = -\frac{1}{\omega C}$

Power Triangle

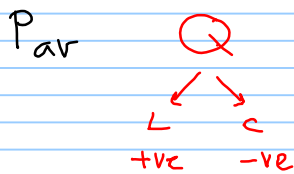


\vec{S}

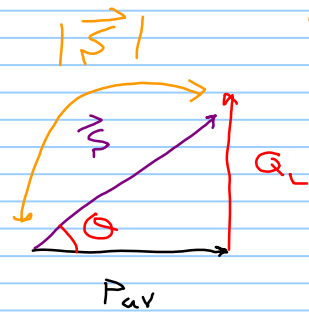

$$\vec{S} = P_{av} + jQ_L$$

$-ve$
 $\vec{S} = P_{av} + jQ_C$

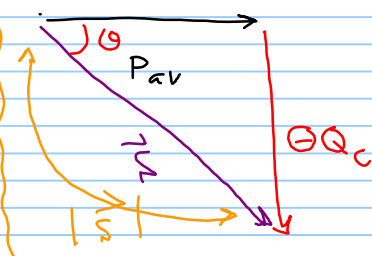

$$\theta = \theta_v - \theta_i$$

$$\text{PF} = \cos \theta = \frac{P_{av}}{|\vec{S}|}$$

$$X \sin \theta = \frac{Q_L}{|\vec{S}|}$$

$$\tan \theta = \frac{Q}{P_{av}} \Rightarrow \theta = \tan^{-1} \frac{Q}{P_{av}}$$


$$P_a = |\vec{S}| = \sqrt{P_{av}^2 + Q^2}$$

\vec{S} → apparent power

Conservation of AC Power

The complex, Real, and Reactive powers of the sources equal the respective sum of the complex, real, and reactive powers of the individual loads.
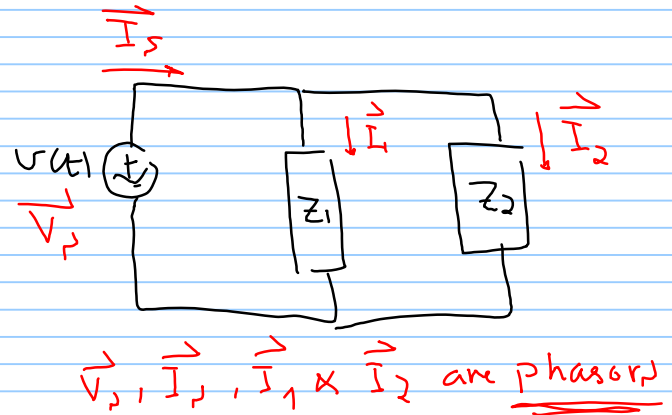
$$\begin{aligned}
 \vec{S}_{\text{source}} &= \vec{V}_s \cdot \vec{I}_s^* \\
 &= \vec{V}_p \cdot (\vec{I}_1^* + \vec{I}_2^*) \\
 &= \vec{V}_p \vec{I}_1^* + \vec{V}_s \cdot \vec{I}_2^* \\
 &= \vec{S}_1 + \vec{S}_2
 \end{aligned}$$




→ The same results can be obtained for a series connection →

$$\begin{cases}
 \rightarrow P_{av_T} = P_{av_1} + P_{av_2} + \dots + P_{av_n} \\
 \rightarrow Q_T = Q_1 + Q_2 + \dots + Q_n \\
 \rightarrow \vec{S}_T = P_{av_T} + j Q_T = \vec{S}_1 + \vec{S}_2 + \dots + \vec{S}_n
 \end{cases}$$

Power Factor Correction

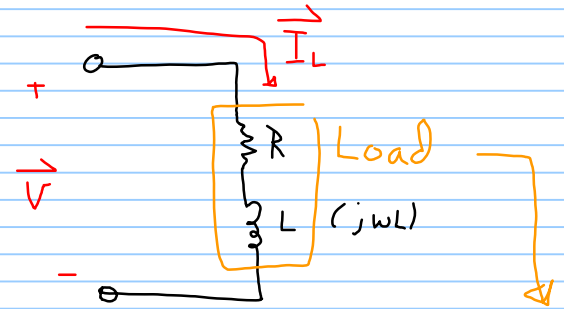
→ The power factor correction is the process of increasing the power factor without altering the voltage or currents to the original load.



→ Power factor correction is necessary for economic reason.

$$PF = \cos(\theta_v - \theta_i)$$

→ for R $PF = 1$ & $Q_R = 0$

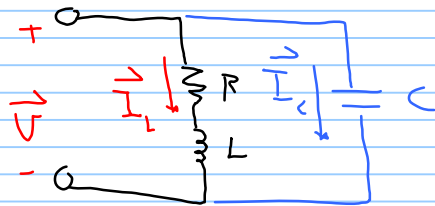

→ To improve the PF, we must decrease the reactive power!

→ for inductive circuit, we add a capacitor in parallel to the load

$$Q_c = Q_{Final} - Q_{init.}$$

$$Q_c = \frac{V_{rms}^2}{X_c} = -\omega C V_{rms}^2$$

$$C = \frac{-Q_c}{\omega V_{rms}^2}$$