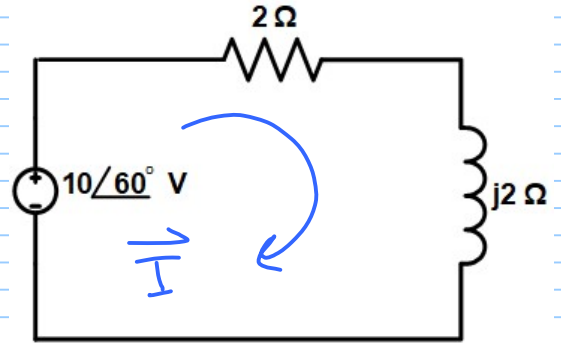


Example :

find the average power absorbed by each element.



$$P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P_{av, j2} = Z_{avg}$$

$$\vec{I} = \frac{10 \angle 60^\circ}{2 + j2} = 3.53 \angle 15^\circ \text{ A}$$

$$\vec{V}_R = \frac{2}{2 + j2} * 10 \angle 60^\circ = 7.07 \angle 15^\circ \text{ Volt.}$$

OR  $\vec{V}_R = \vec{I} R = 7.06 \angle 15^\circ \text{ Volt.}$


$$\begin{aligned} P_{av, R} &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= \frac{1}{2} * 7.07 * 3.53 \cos(15^\circ - 15^\circ) \\ &= 12.47 \text{ W} \end{aligned}$$

$$P_{av, R} = \frac{I_m^2 R}{2} = \frac{1}{2} * (3.53)^2 * (2) = 12.46 \text{ W}$$

→ The average power supplied by the source

$$\begin{aligned} P_{av} &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= \frac{1}{2} (10) (3.53) \cos(60^\circ - 15^\circ) \\ &= 12.48 \text{ W} \end{aligned}$$

Example :

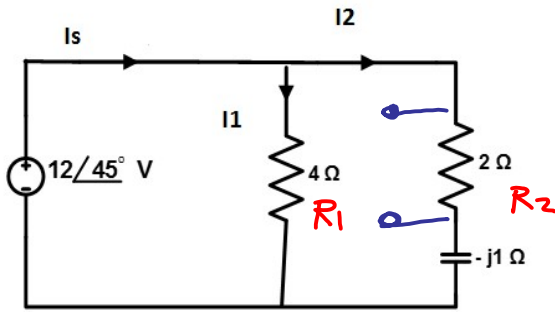

Determine the average power absorbed by each resistor .  
Determine the total average power supplied by the source .

$$\rightarrow P_{av R_1} = \frac{V_m^2}{2R_1} = \frac{12^2}{2 \times 4} = \underline{\underline{18 W}}$$

$$\rightarrow \vec{I}_2 = \frac{12 \angle 45^\circ}{2 - j} = 5.366 \angle 71.56^\circ \text{ A}$$

$$\frac{V_{R_2}}{2 - j} * 12 \angle 45^\circ$$

$$\rightarrow P_{av R_2} = \frac{1}{2} I_{m_2}^2 R_2 = \frac{1}{2} \times 5.366^2 \times 2 = \underline{\underline{28.79 W}}$$

$$\rightarrow P_{av V_S} = 18 + 28.79 = \underline{\underline{46.79 W}}$$

del.

$$\underline{\underline{OR}} \quad \vec{I}_f = \frac{\vec{V}_f}{Z_{eq}} = \vec{I}_1 + \vec{I}_2$$

$$= \frac{12 \angle 45^\circ}{4} + 5.366 \angle 71.56^\circ$$

$$= \underline{\underline{8.16 \angle 62.1^\circ \text{ A}}}$$

$$P_{av V_S} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$


$$= \frac{1}{2} \times 12 \times 8.16 \times \cos(45 - 62.1)$$

$$= \underline{\underline{46.785 W}}$$

$$P_{abs.} = P_{del.}$$

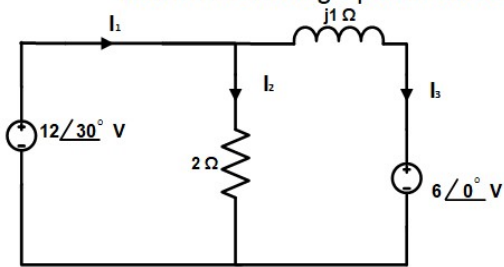Example :

Determine average power absorbed or supplied by each element .



$$\vec{I}_2 = \frac{12 \angle 30^\circ}{2} = 6 \angle 30^\circ \text{ A}$$

$$\vec{I}_3 = \frac{(12 \angle 30^\circ) - (6 \angle 0^\circ)}{j1 \angle 90^\circ} = 7.43 \angle -36.2^\circ \text{ A}$$

$$\vec{I}_1 = \vec{I}_2 + \vec{I}_3 = 6 \angle 30^\circ + 7.43 \angle -36.2^\circ = 11.28 \angle -7.08^\circ \text{ A}$$


$$\rightarrow P_{av_{2\Omega}} = \frac{1}{2} I_{2m}^2 \times 2 = 36 \text{ W (absorbed)}$$
$$\frac{1}{2} I_m^2 R$$

$$\rightarrow P_{av_{j1\Omega}} = \text{Zero}$$

$$\rightarrow P_{av_{12\angle 30^\circ}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} 12 \times 11.28 \cos(30 - (-7.08))$$
$$= 54 \text{ W (supplied)}$$

$$\rightarrow P_{av_{6\angle 0^\circ}} = \frac{1}{2} \times 6 \times 7.43 \cos(0 - (-36.2))$$
$$= 18 \text{ W (absorbed)}$$

## Maximum Power Transfer

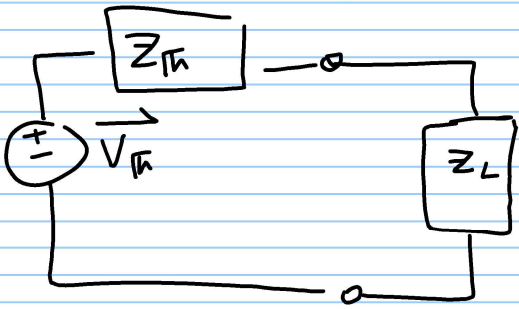

$$Z_{th} = R_{th} + jX_{th}$$

$$Z_L = R_L + jX_L$$

$$\rightarrow P_L = \frac{1}{2} I_{Lm}^2 R_L$$

$$\begin{aligned} \vec{I} &= \frac{\vec{V}_{th}}{Z_{th} + Z_L} \\ &= \frac{\vec{V}_{th}}{(R_{th} + R_L) + j(X_{th} + X_L)} \end{aligned}$$

$$\therefore P_L = \frac{1}{2} \frac{V_{th}^2 \cdot R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

$$\textcircled{1} \frac{\partial P_L}{\partial X_L} = 0 \quad \& \quad \textcircled{2} \frac{\partial P_L}{\partial R_L} = 0$$

$$\* \Rightarrow \frac{\partial P_L}{\partial X_L} = \frac{1}{2} \frac{-2 V_{th}^2 R_L (X_L + X_{th})}{[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]^2}$$

$$\text{for } \frac{\partial P_L}{\partial X_L} = 0 \rightarrow \boxed{X_L = -X_{th}}$$

$$\* \Rightarrow \frac{\partial P_L}{\partial R_L} = \frac{V_{th}^2 [(R_L + R_{th})^2 + (X_L + X_{th})^2 - 2R_L(R_L + R_{th})]}{2 [(R_L + R_{th})^2 + (X_L + X_{th})^2]^2}$$


$$\text{for } \frac{\partial P_L}{\partial R_L} = 0 \rightarrow \boxed{R_L = R_{th}}$$

$$\boxed{Z_L = Z_{th}^*}$$

$$P_{L, \max} = \frac{1}{8} \frac{V_{th}^2}{R_{th}}$$

$$R_{th} = R_L$$

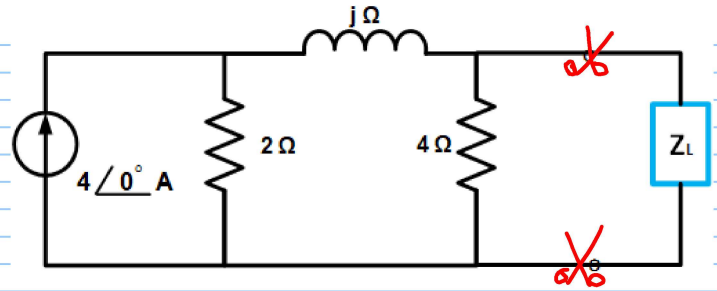Example : Find  $Z_L$  for maximum average power transfer .  
 Compute the maximum average power supplied to the load .



$$Z_{Th} = 4 \parallel (2 + j)$$

$$= 1.4 + j0.43 \Omega$$



$$Z_L = Z_{Th}^* = 1.4 - j0.43 \Omega$$

$$P_{max} = \frac{1}{8} \frac{V_{Th}^2}{R_{Th}}$$

$$V_{Th} = \left( \frac{2 \times 4}{6 + j} \right) \times 4$$

$$= 5.28 \angle -9.46^\circ$$
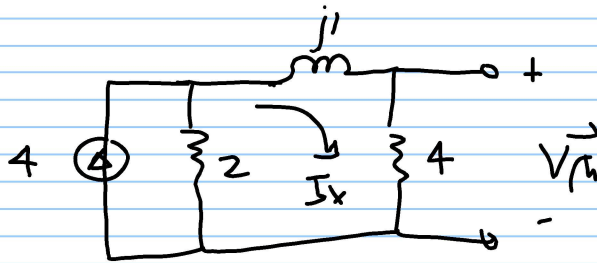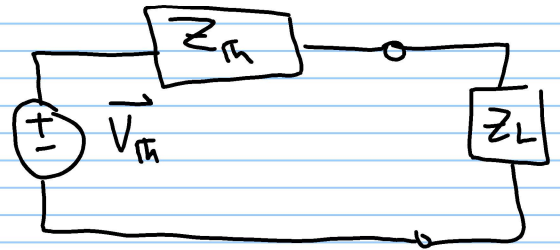
$$\therefore P_{max} = \frac{1}{8} \frac{(5.28)^2}{1.4} = 2.489 \text{ W}$$



$$V_{Th} = 2I - 4 \angle 0^\circ$$

$$I = \frac{V_x + 4 \angle 0^\circ}{2 + j4}$$

$$V_x = -2I$$


$$I = 0.707 \angle -45^\circ \text{ A}$$

$$I = \frac{-2I + 4}{2 + j4}$$

$$2I + j4I + 2I = 4$$


$$(4 + j4)I = 4$$
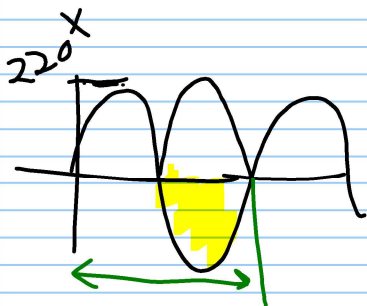
$$I = \frac{4}{\sqrt{4^2 + 4^2}} \angle 45^\circ$$



$$220 \cos(2\pi \times 50t + 0^\circ)$$

rms

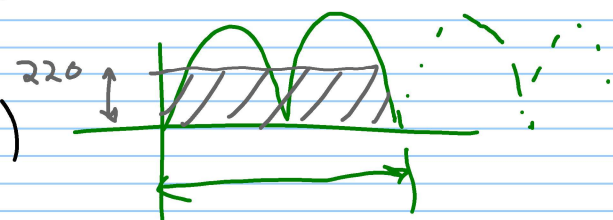

$$\underline{V_{rms} = \frac{V_m}{\sqrt{2}}}$$

$$\underline{I_{rms} = \frac{I_m}{\sqrt{2}}}$$

$$P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad (\text{frowny face})$$

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i) \quad (\text{happy face})$$

$$P_{avR} = \frac{V_{rms}^2}{R} = I_{rms}^2 R \quad (\text{happy face}) = V_{rms} I_{rms}$$

$$P_{av} = \underbrace{V_{rms} I_{rms}}_{P_a \text{ (VA)}} \underbrace{\cos(\theta_v - \theta_i)}_{\text{PF}} \quad (\text{W})$$

apparent Power

Power Factor

unity

lagging PF


leading PF




$$\theta_v = \theta_i$$



$i$  lags  $v$  by  $\theta$

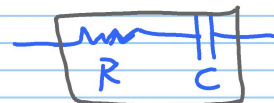


$i$  leads  $v$  by  $\theta$

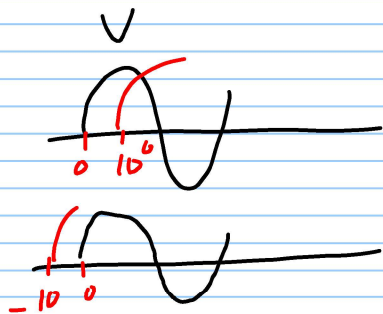

$$\cos(\theta) = \cos(-\theta)$$
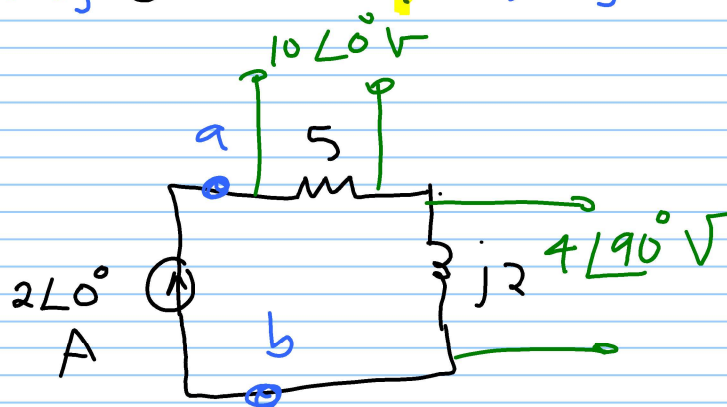
$$\text{P.F.} = \cos(21.8) = 0.928 \text{ lagging}$$



$$\left\{ \begin{aligned} V_{ab} &= (2L0)(5 + j2) \\ &= 10 + j4 = 10.77 \angle 21.8^\circ \end{aligned} \right.$$

