
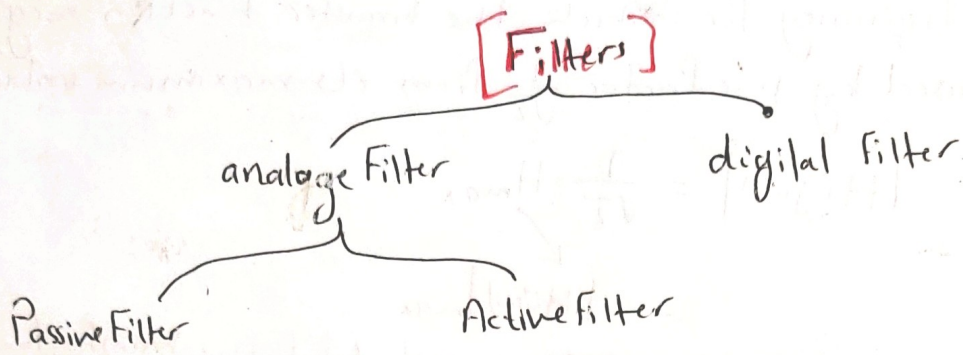


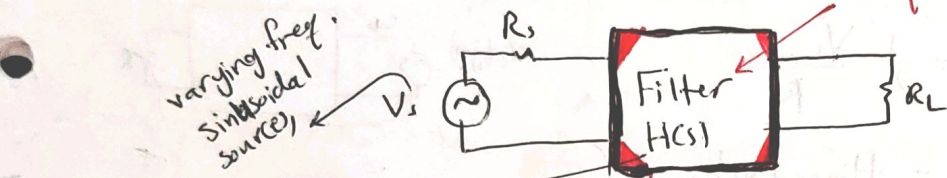Introduction to Frequency Selective Circuits:-






- ↳ low-pass filter.
- ↳ high-pass filter.
- ↳ bandpass filter.
- ↳ bandreject filter.

Frequency-selective circuits.







$$H(j\omega) = \frac{X(j\omega)}{Y(j\omega)}$$

Frequency Response

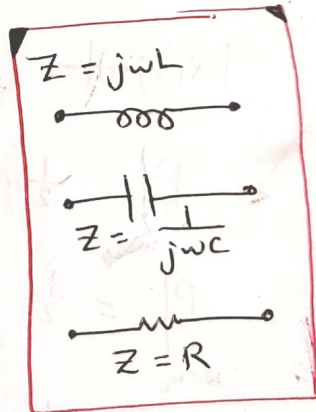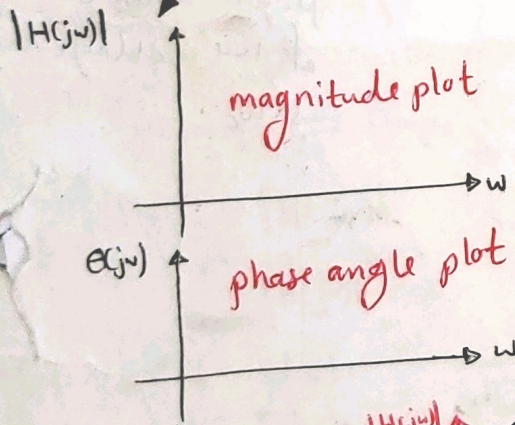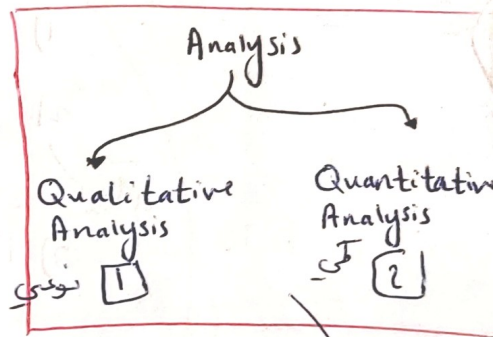

Low-Pass Filter

- ① RC circuit
- ② RL circuit

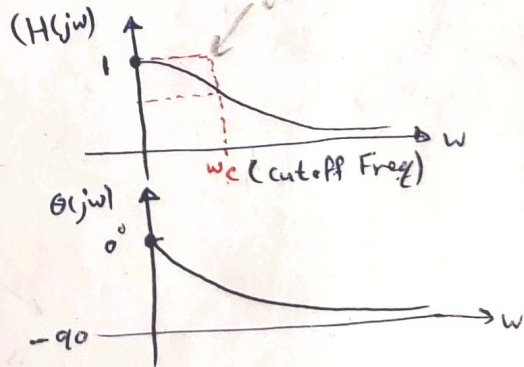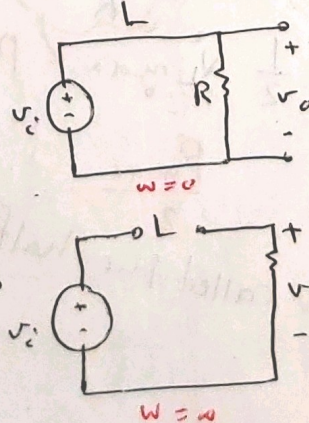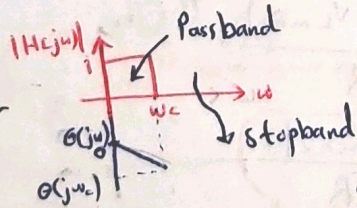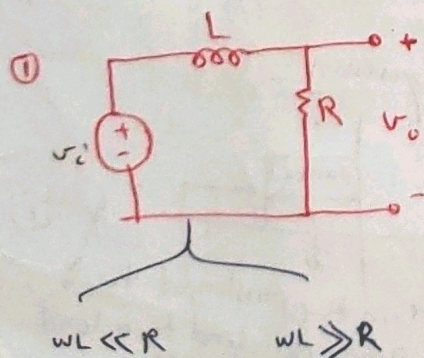

Defining the Cutoff Freq

Cutoff freq: is the frequency for which the transfer function magnitude is decreased by the factor $\frac{1}{\sqrt{2}}$ from its maximum value.

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{max}$$

$|H(j\omega)|_{max}$
max magnitude of the transfer function.

amp of the voltage drop across the load

(average power delivered by any circuit to a load)

$$P = \frac{1}{2} \frac{V_L^2}{R}$$

2 notes

$$1) P_{max} = \frac{1}{2} \frac{V_{Lmax}^2}{R}$$

$$2) V_{Lmax} = H_{max} |V_i|$$

$$3) |V_L(j\omega_c)| = |H(j\omega_c)| |V_i|$$

$$= \frac{1}{\sqrt{2}} H_{max} |V_i|$$

$$|V_L(j\omega_c)| = \frac{1}{\sqrt{2}} V_{Lmax}$$

$$P = \frac{1}{2} \frac{V_L^2}{R}$$

$$P = \frac{1}{2} \frac{|V_L(j\omega_c)|^2}{R}$$


$$= \frac{1}{2} \frac{\left(\frac{1}{\sqrt{2}} V_{Lmax}\right)^2}{R}$$

$$= \frac{1}{2} \frac{V_{Lmax}^2 / 2}{R}$$


$$= \frac{1}{2} P_{max}$$

$$= \frac{P_{max}}{2}$$

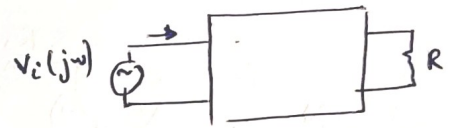ω_c is also called the half-power frequency




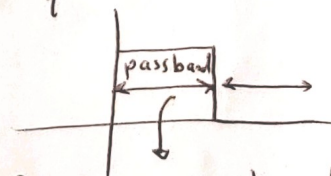Now consider what happens to the average power when the freq of the voltage source is ω_c .



Therefore, in the passband the average power delivered to a load is at least 50% of the max average

⇒ Low-Pass Filter



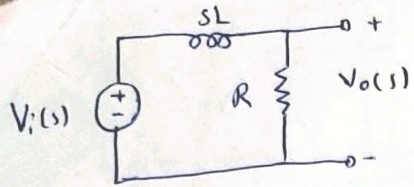


$$H(s) = \frac{R}{R+sL}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R/L}{s+R/L}$$

$$H(j\omega) = \frac{R/L}{j\omega+R/L}$$

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}}$$

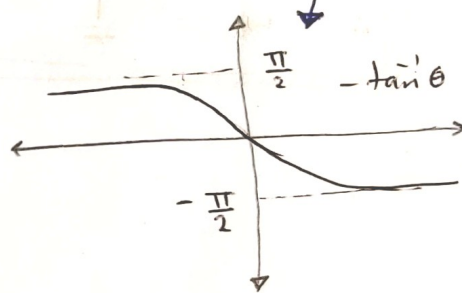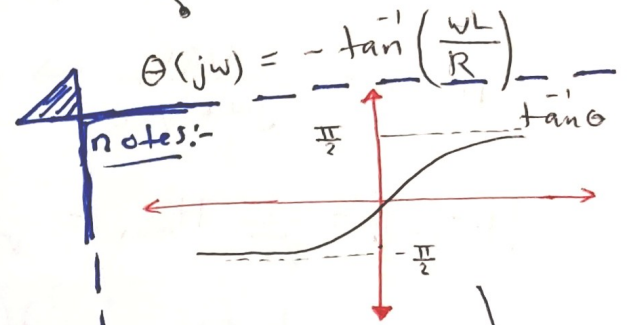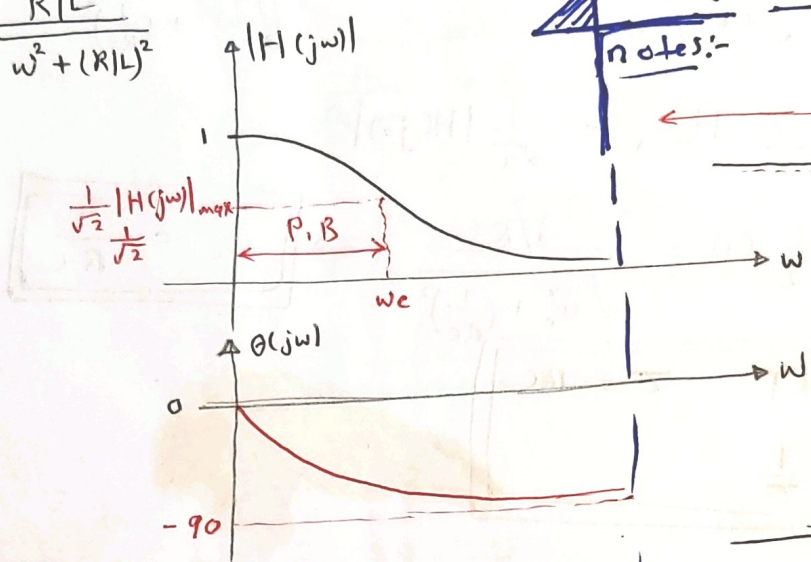

Cutoff frequency

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{max} \quad \text{at } \omega=0$$

$$H_{max} = |H(j\omega)|_{\omega=0} = |H(j0)|$$

$$\Rightarrow |H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{R/L}{\sqrt{\omega_c^2 + (\frac{R}{L})^2}}$$


$$\therefore \Rightarrow \omega_c = \frac{R}{L}$$

$$H(s) = \frac{\omega_c}{s + \omega_c}$$

for RL circuit $\tau = \frac{L}{R}$

$$\therefore \omega_c = \frac{1}{\tau}$$

2

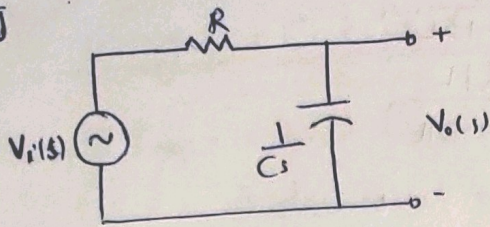

$$(a) \quad H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1/Cs}{R + 1/Cs} = \frac{1}{RCs + 1} = \frac{1/RC}{s + 1/RC}$$

$$H(j\omega) = \frac{1/RC}{j\omega + 1/RC} \Rightarrow |H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + (1/RC)^2}}, \quad \theta(j\omega) = 0 - \tan^{-1}(\omega RC) = -\tan^{-1}(\omega RC)$$

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{max} = \frac{1}{\sqrt{2}} |H(j0)|$$

$$= \frac{1}{\sqrt{2}} (1) = \frac{1/RC}{\sqrt{\omega_c^2 + (1/RC)^2}} \Rightarrow \boxed{\omega_c = \frac{1}{RC}}$$

For RC CKT $\tau = RC$
 $\therefore \omega_c = \frac{1}{\tau}$

$$H(s) = \frac{\omega_c}{s + 1/RC \omega_c}$$


* Choose values for R, C that will yield a low-pass filter with a cutoff frequency of 3 kHz.

$$C = 1 \mu F$$

$$\frac{1}{RC} = \omega_c = 2\pi(3 \times 10^3) = \frac{1}{R \times 1 \times 10^{-6}}$$



$$R = \frac{1}{10^6 \times 2\pi \times 3 \times 10^3} = 53 \Omega$$

?! Design

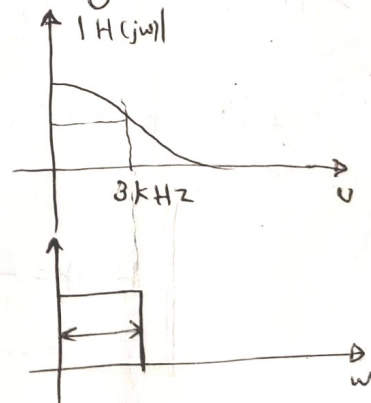

4

Loaded Low-pass filter :-

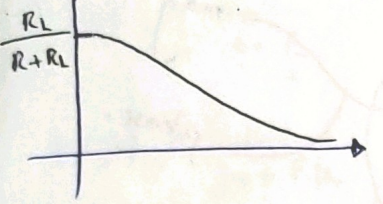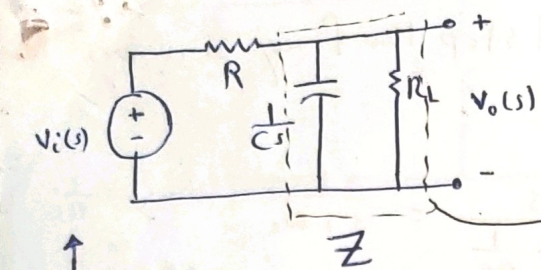

$$\frac{R_L (1/sC)}{R_L + 1/sC} = \frac{R_L}{R_L C s + 1}$$

$$H(s) = \frac{R_L}{R_L C s + 1} \cdot \frac{R}{R_L C s + 1}$$

$$= \frac{R_L}{R_L C s + 1} \cdot \frac{R_L C s + 1}{R_L + R_L (R_L C s + 1)}$$

$$= \frac{R_L}{R R_L C s + R + R_L}$$

$$= \frac{R_L}{R R_L C} \cdot \frac{1}{s + \frac{R + R_L}{R R_L C}} = \frac{1/R C}{s + \frac{R + R_L}{R R_L C}}$$

$$H(s) = \frac{1/R C}{s + \frac{R + R_L}{R R_L C}}$$

$$|H(j\omega)| = \frac{1/R C}{\sqrt{\omega^2 + [(R + R_L)/R R_L C]^2}}$$

$\omega = 0$

$$|H(j\omega)|_{\max} = \frac{R_L}{R + R_L}$$

$$\Rightarrow \frac{1}{\sqrt{2}} \left[\frac{R_L}{R + R_L} \right] = \frac{1}{\sqrt{\omega_c^2}}$$


$$\therefore \omega_c = \frac{R + R_L}{R R_L C} = \frac{1}{R_{eq} C} = \frac{1}{\tau}$$

$$R_{eq} = (R \parallel R_L)$$

$$\tau = R_{eq} C$$

High-Pass Filters

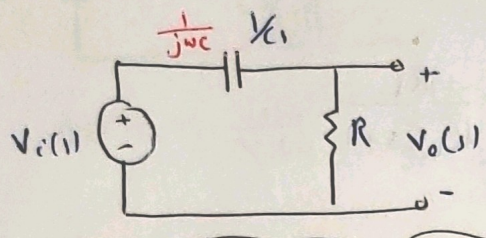Are used to pass the high freq sinwaves and stop low freq sinwaves





$$H(s) = \frac{V_o(s)}{V_c(s)} = \frac{R}{R + \frac{1}{Cs}} = \frac{s}{s + \frac{1}{RC}} \approx \frac{j\omega}{j\omega + \frac{1}{RC}}$$

$\omega_c = \frac{1}{RC}$
 $\text{mag} = \frac{1}{\sqrt{2}}$
 phase

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (\frac{1}{RC})^2}} = \frac{1}{\sqrt{1 + (\frac{1}{RC\omega})^2}}$$


$\omega = 0 \Rightarrow |H(j\omega)| = 0$
 $\omega = \infty \Rightarrow |H(j\omega)| = 1$

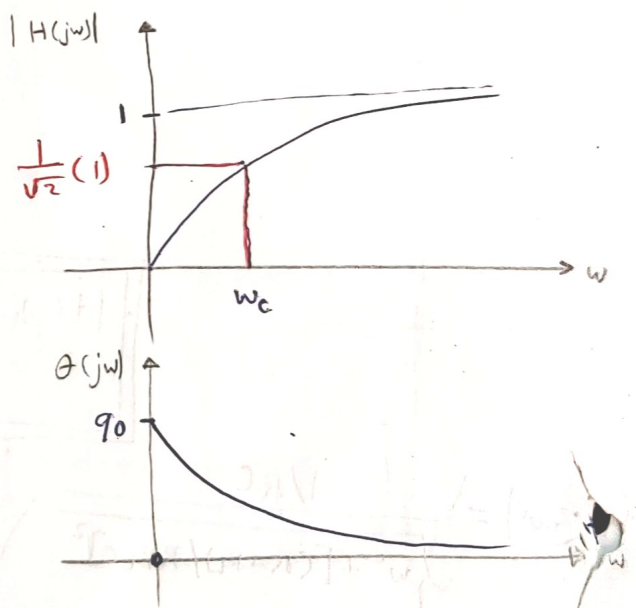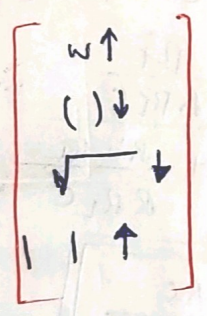


Phase

$$\theta(j\omega) = 90 - \tan^{-1}\left(\frac{\omega}{\frac{1}{RC}}\right)$$

$$= 90 - \tan^{-1}(\omega RC)$$

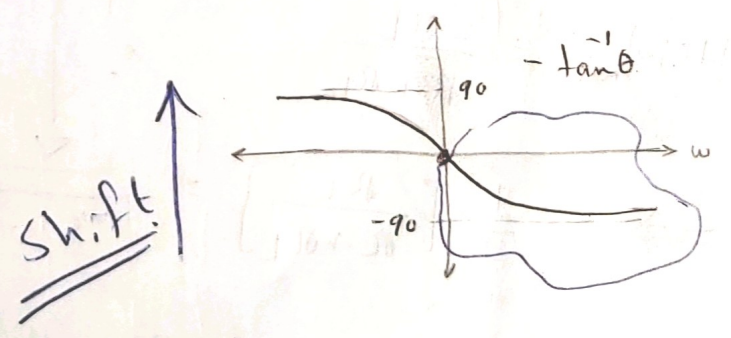

2.


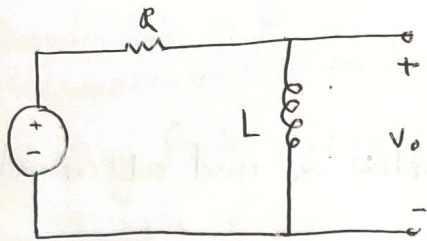


$$H(s) = \frac{s}{s + \frac{R}{L}}$$

$$H(j\omega) = \frac{j\omega}{j\omega + R/L}$$

$$\omega_c = \frac{R}{L} \Rightarrow H(s) = \frac{s}{s + \omega_c}$$

3. Loaded High pass Filters :-

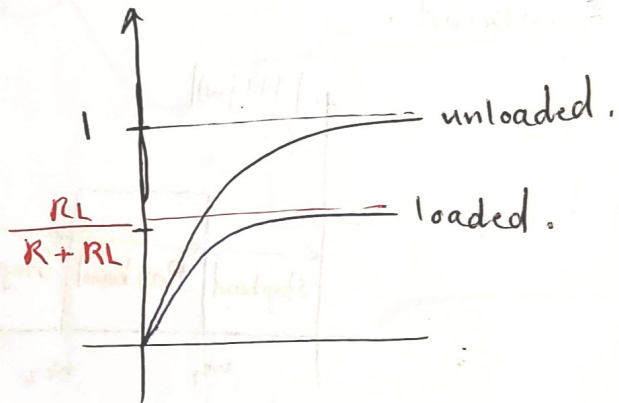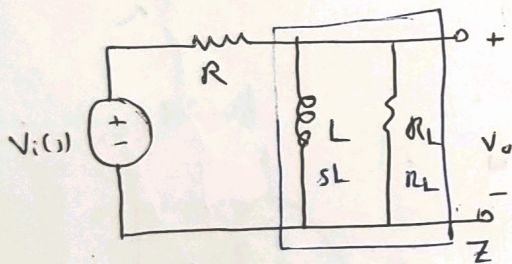

$$\tau = \frac{L}{R_{eq}}, \quad R_{eq} = (R \parallel R_L)$$

$$\omega_c = \frac{1}{\tau} = R_{eq}/L$$

$$\omega_c = \left(\frac{R R_L}{R + R_L} \right) / L$$

$$H(s) = \frac{\left[\frac{R_L s L}{R_L + sL} \right]}{\left[R + \frac{R_L s L}{R_L + sL} \right]}$$



Can be written

$$= \frac{\left(\frac{R_L}{R + R_L} \right) s}{s + \left(\frac{R_L}{R + R_L} \right) \frac{R}{L}}$$

$$H(s) = \frac{\left(\frac{R_L}{R + R_L} \right) s}{s + \omega_c}$$

Bandpass Filters

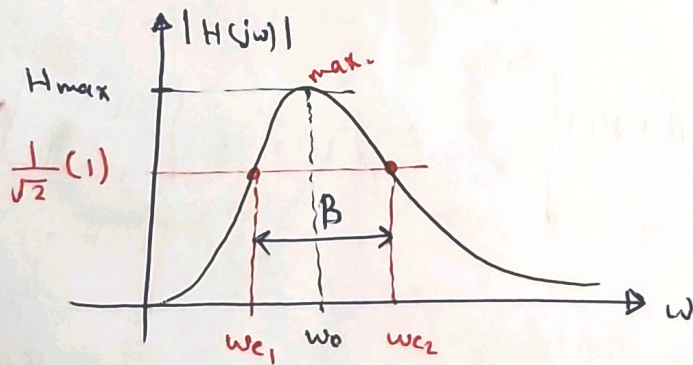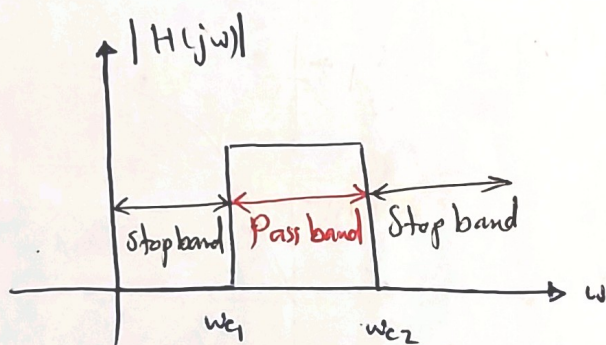- » A low-pass filter passes voltages at frequencies below ω_c and attenuates frequencies above ω_c .
- » A high-pass filter passes voltages at frequencies above ω_c , and attenuates voltages at frequencies below ω_c .
- » A bandpass filter passes voltages at frequencies within the passband which is between ω_{c1} and ω_{c2} . It attenuates frequencies outside of the passband.



⇒ Second order ⇒ RLC, CKT

① $\omega_c \equiv$ cutoff frequency

② $\omega_0 \equiv$ center frequency, ω_0 , defined as the frequency for which a circuit's transfer function is purely real.

\equiv resonant frequency,

\equiv geometric center of the passband.
mean





$$\equiv \sqrt{\omega_{c1} \omega_{c2}}$$

$$H_{max} = |H(j\omega_0)| \quad \text{For bandpass Filters}$$

③ $\beta \equiv$ Bandwidth $= \beta$
 $=$ the width of the passband.

④ $Q \equiv$ quality factor, which is the ratio of the center frequency to the bandwidth $\equiv \frac{\omega_0}{\beta}$

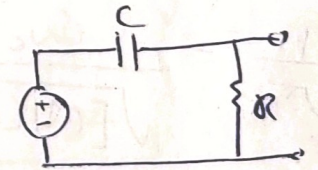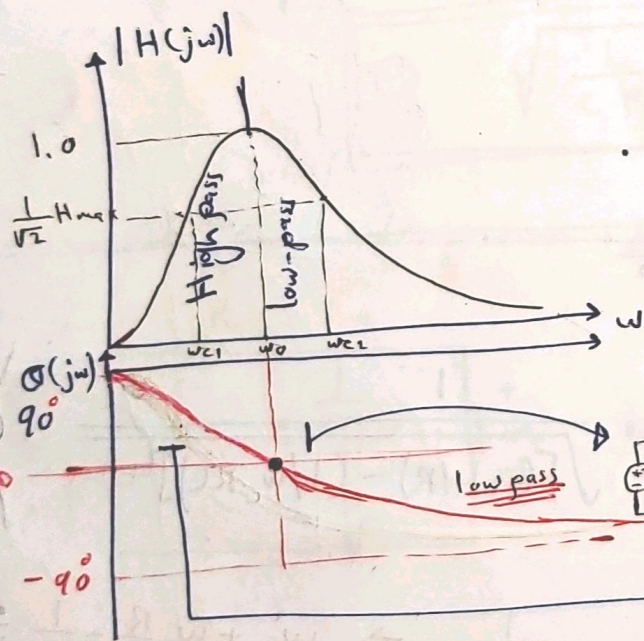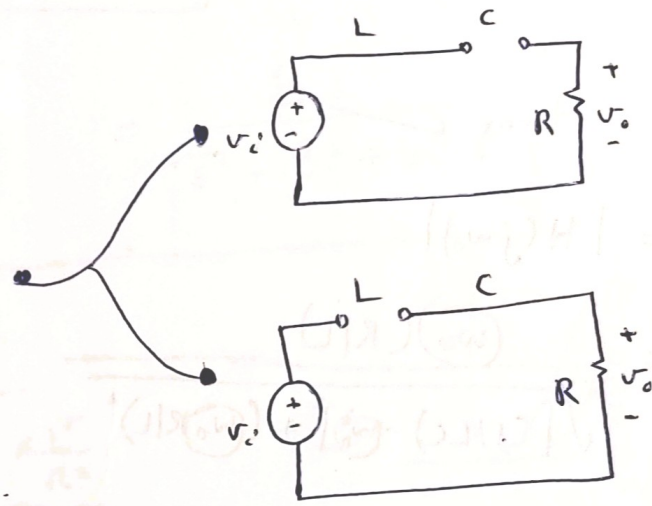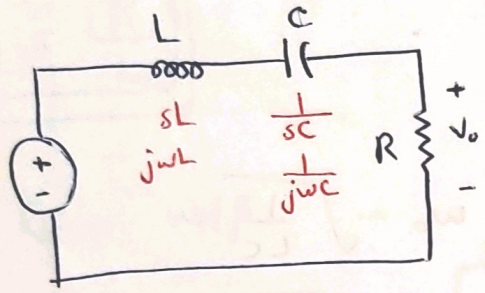$\omega_{c1}, \omega_{c2}, \omega_0, \beta, Q$
 $\omega \rightarrow \text{ok}$



$$H(s) = \frac{v_o(s)}{v_i(s)} = \frac{\frac{s}{L} \cdot R}{\frac{s}{L} R + sL + \frac{1}{Cs}} = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC} = \frac{R/L j\omega}{- \omega^2 + \frac{R}{L} j\omega + \frac{1}{LC}}$$

$$= \frac{R/L j\omega}{(\frac{1}{LC} - \omega^2) + \frac{R}{L} j\omega}$$

$$|H(j\omega)| = \frac{\omega(R/L)}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + [\omega(\frac{R}{L})]^2}}$$

$$\theta(j\omega) = 90 - \tan^{-1} \left[\frac{\omega(R/L)}{(\frac{1}{LC} - \omega^2)} \right]$$

$\omega_0, \omega_{c1}, \omega_{c2}, \beta, Q$?!?

ω_0

$$j\omega_0 L + \frac{1}{j\omega_0 C} = 0$$

$$j\omega_0 L = \frac{j}{\omega_0 C} \Rightarrow \omega_0^2 LC = 1$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

ω_{c1}, ω_{c2}

H_{max} ✓

$$H_{max} = |H(j\omega_0)|$$

$$= \frac{\omega_0 (R/L)}{\sqrt{[(1/LC) - \omega_0^2]^2 + (\omega_0 R/L)^2}}, \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$H_{max} = 1$$

$$|H(j\omega)| = \frac{\omega (R/L)}{\sqrt{[(1/LC) - \omega^2]^2 + [\omega (R/L)]^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c (R/L)}{\sqrt{[(1/LC) - \omega_c^2]^2 + (\omega_c R/L)^2}} = \frac{1}{\sqrt{[(\omega_c L/R) - (1/\omega_c RC)]^2 + 1}}$$

$$\pm 1 = \omega_c \frac{L}{R} - \frac{1}{\omega_c RC} \Rightarrow \omega_c^2 \pm \omega_c \frac{R}{L} - \frac{1}{CL} = 0$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} + 4(1)(\frac{1}{CL})}}{2(1)}$$

2 (positive) ✓
2 (negative) ✗

ω₀

$$\omega_0 = \sqrt{\omega_{c1} \cdot \omega_{c2}}$$

≡ geometric mean of the two cutoff frequencies.

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

β

$$\beta = \omega_{c2} - \omega_{c1}$$

$$\beta = \frac{R}{L}$$

$$H(s) = \frac{(R/L)s}{s^2 + (\frac{R}{L})s + \frac{1}{LC}}$$


$$= \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

Q



$$Q = \omega_0 / \beta$$

$$= \frac{\sqrt{1/LC}}{R/L} = \sqrt{\frac{1}{LC} \cdot \frac{L^2}{R^2}}$$

$$Q = \sqrt{\frac{L}{CR^2}}$$

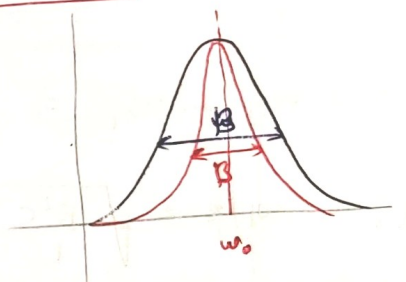

Z

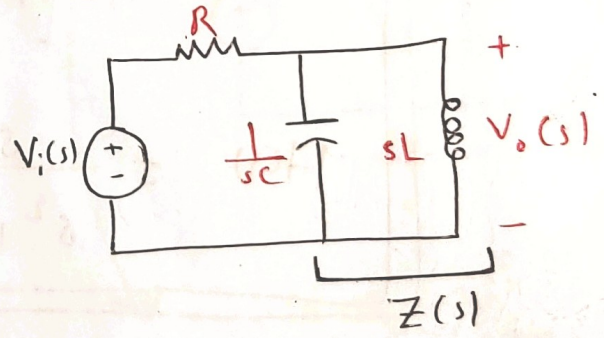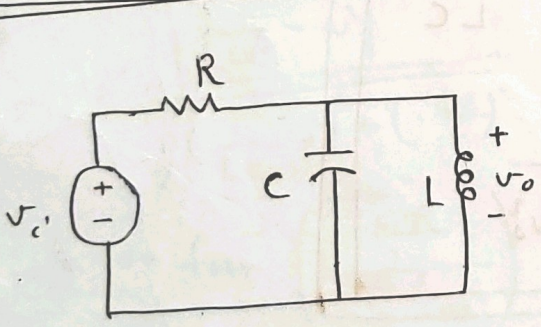

$$\frac{1}{j\omega C} + j\omega L = 0$$

$$Z(s) = \frac{\frac{1}{sC} \cdot sL}{\frac{1}{sC} + sL} = \frac{L}{sL + \frac{1}{sC}}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{s/RC}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$H(j\omega) = \checkmark \quad (s = j\omega)$$

$$|H(j\omega)| = \frac{\omega/RC}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega}{RC})^2}}$$


$$= \frac{1}{\sqrt{1 + \left(\omega RC - \frac{1}{\omega L}\right)^2}}$$

$\left(\omega RC - \frac{1}{\omega L}\right)^2$
 $\left(\omega^2 - \frac{1}{LC}\right)^2$
 $\left(\frac{1}{LC} - \omega^2\right)^2$
 $\left(\frac{1}{LC} - \omega^2\right)^2 = 0$
 (MAX)

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$H_{\max} = |H(j\omega_0)| = 1$$

$$\frac{1}{\sqrt{2}} H_{\max} = |H(j\omega_c)|$$

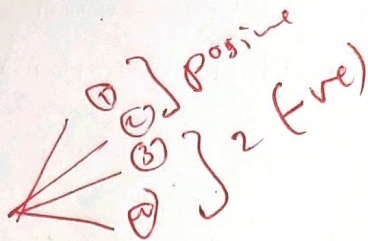

$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC}$$




$$Q = \omega_0 / \beta = \sqrt{\frac{R^2 C}{L}}$$

$$H(s) = \frac{s/RC}{s^2 + s/RC + \frac{1}{LC}}$$

$$H(s) = \frac{s\beta}{s^2 + \beta s + \omega_0^2}$$

Band reject Filter &
Band Stop Filter

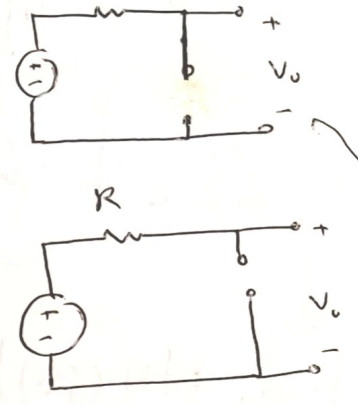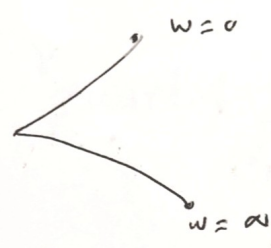
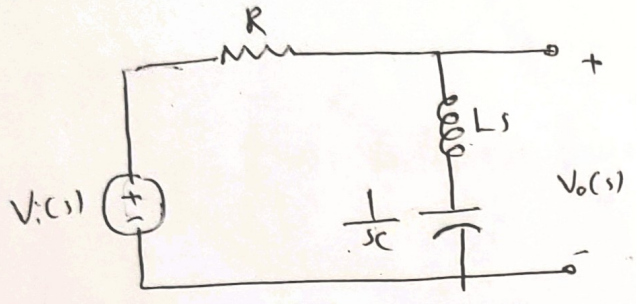
attenuates voltages at frequencies within the stopband, which is between ω_{c1} and ω_{c2} . It passes frequencies outside of the stopband.




$$H(s) = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{-\omega^2 + \frac{1}{LC}}{-\omega^2 + \frac{R}{L}j\omega + \frac{1}{LC}}$$

$$|H(j\omega)| = \frac{|\frac{1}{LC} - \omega^2|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega R}{L})^2}}$$
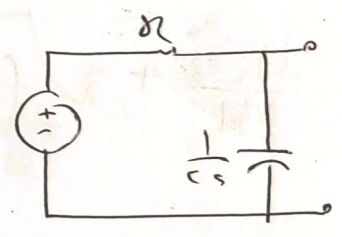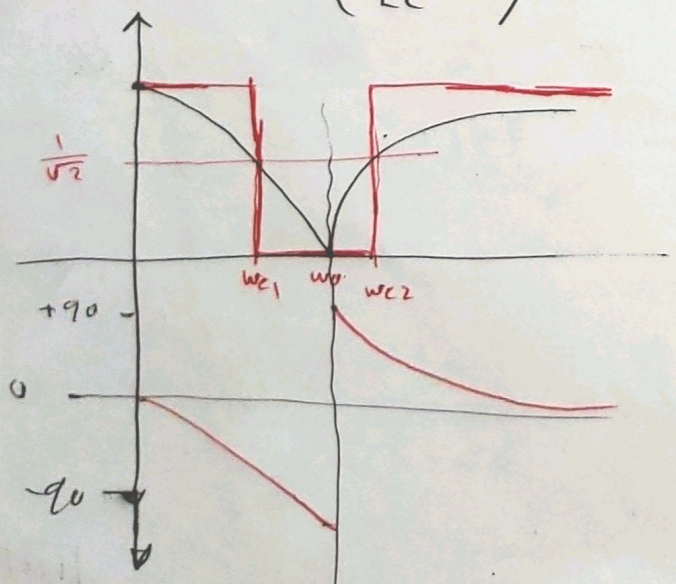
$$\theta(j\omega) = 0 - \tan^{-1} \left(\frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2} \right)$$



low-pass filter

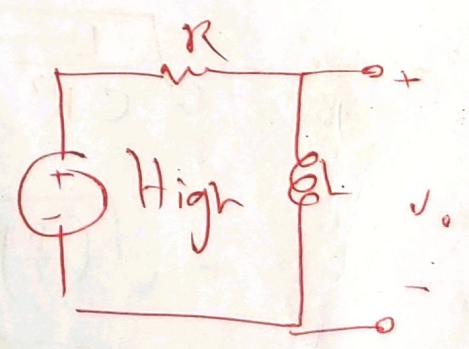

High

$\omega_0 \equiv$ center frequency \equiv resonant freq

$$j\omega_0 L + \frac{1}{j\omega_0 C} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\boxed{|H(j\omega_0)| = 0 \text{ (min)}}$$

$$\left(\frac{1}{\sqrt{2}} H_{\max}\right) \leftarrow \begin{array}{l} \omega_{c1} \\ \omega_{c2} \end{array}$$

$$H_{\max} = |H(j\omega)| = |H(j\infty)|$$

$$\text{Here } H_{\max} = 1$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\beta = \frac{R}{L}$$

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{L}{CR^2}}$$

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$
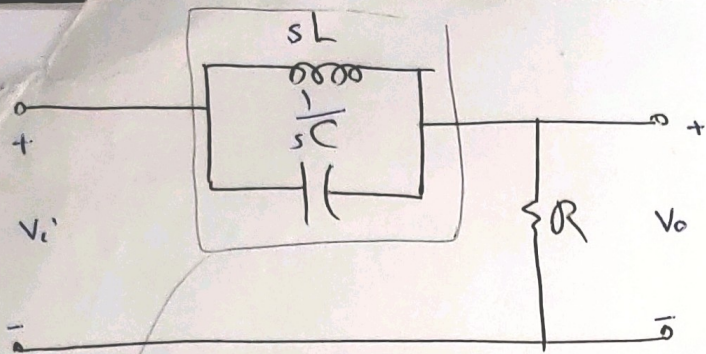
$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$



at $\omega = \omega_0$

$$\frac{sL \cdot \frac{1}{sC}}{s} \rightarrow \infty$$

$$s \rightarrow 0$$

$V_0 = 0$

qualitative analysis
نوعي

quantitative analysis
كمي

at $\omega = 0$

$$V_0 = V_i$$

at $\omega = \infty$

$$V_0 = V_i$$

at $\omega = \omega_0$

$$V_0 = 0$$

$$Z = \frac{sL \left(\frac{1}{sC} \right)}{sL + \frac{1}{sC}} = \frac{sL}{s^2 LC + 1}$$

$$H(s) = \frac{V_0}{V_i} = \frac{R}{R + Z} = \frac{s^2 + 1/LC}{s^2 + \left(\frac{1}{RC}\right)s + \frac{1}{LC}}$$

$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

$$H(j\omega) = \frac{\omega_0^2 - \omega^2}{\omega_0^2 - \omega^2 + j\omega\beta}$$

$H(j\omega) = 0$ when $\omega = \omega_0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$|H(j\omega)| = \frac{\omega_0^2 - \omega^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \omega^2 \beta^2}} \Rightarrow \frac{1}{\sqrt{2}} = |H(j\omega)|$$

$$\omega^2 \beta^2 = (\omega_0^2 - \omega^2)^2 \Rightarrow \pm \omega \beta = \omega_0^2 - \omega^2$$

$$\omega^2 \pm \beta \omega - \omega_0^2 = 0$$

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

