

Analog Electronics


ENEE236

Instructor: Nasser Ismail

L8- DC Biasing - BJTs

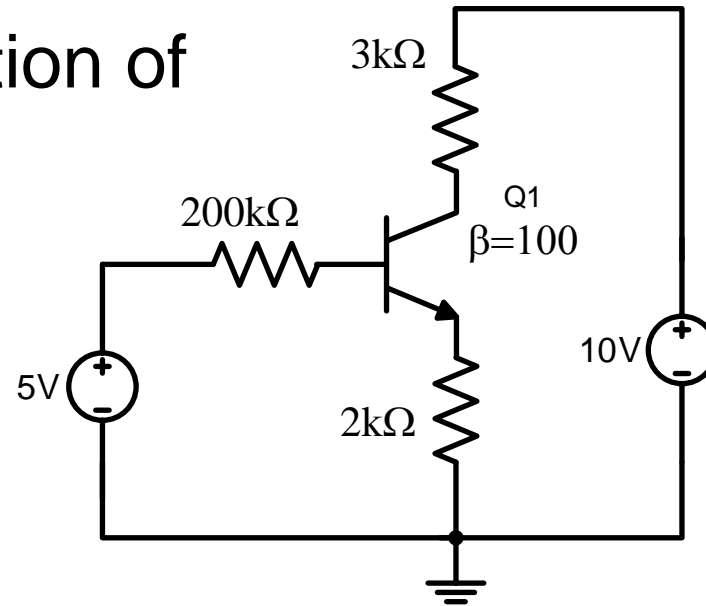Example

- Assume $V_{CE(sat)}=0.2\text{ V}$
- Find mode of operation of Q1 ?



Determine Mode of Operation of BJT?

- Solution:
- 1) Since BE junction is forward biased \implies Q1 can be either in Active (Linear) or Saturation mode
- Assume it is in Active Mode


$$5 = 200 \text{ k}\Omega \cdot I_B + V_{BE} + 2 \text{ k}\Omega \cdot I_E$$

But, $I_E = (1 + \beta)I_B$

$$\text{Solve for } I_B = \frac{5 - V_{BE}}{200 \text{ k}\Omega + (1 + \beta) \cdot 2 \text{ k}\Omega}$$

$$I_B = \frac{5 - 0.7}{200 \text{ k}\Omega + (1 + 100) \cdot 2 \text{ k}\Omega}$$

 
$$= \frac{4.3 \text{ V}}{402 \text{ k}\Omega} = 10.7 \text{ } \mu\text{A}$$



$$\begin{aligned}
 I_C &= \beta I_B \\
 &= (100) \cdot (10.7 \mu\text{A}) \\
 &= 1.07 \text{ mA} \\
 I_E &= (\beta + 1) I_B \\
 &= 1.0807 \text{ mA}
 \end{aligned}$$

Now we find V_{CE} from output circuit
 
$$\begin{aligned}
 10 - I_C \cdot 3 \text{ k}\Omega - I_E \cdot 2 \text{ k}\Omega &= V_{CE} \\
 \Rightarrow V_{CE} &= 4.63 \text{ V} > V_{CE(\text{sat})}
 \end{aligned}$$



∴ Q1 is in active mode and the assumption is true
 we can also verify that the BC junction is reverse
 biased which is required so that the BJT operates
 in active mode


$$10 - I_C \cdot 3 \text{ k}\Omega - I_E \cdot 2 \text{ k}\Omega = V_{CE}$$

$$\Rightarrow V_{CE} = V_{CB} - V_{EB}$$

$$\Rightarrow V_{CB} = V_{CE} - V_{BE} = 4.63 - 0.7 = 3.93 \text{ V}$$

$$\therefore V_{BC} = -V_{CB} = -3.33 \text{ V}$$

BC junction is reverse biased

 

- Solution:
- 1) Since BE junction is forward biased \implies Q1 can be either in Active (Linear) or Saturation mode
- Assume it is in saturation mode:

$$10 - I_{C(sat)} \cdot 3k\Omega - I_{E(sat)} \cdot 2k\Omega = V_{CE(sat)}$$

assume $I_{E(sat)} = I_{C(sat)}$

$$\therefore I_{C(sat)} = \frac{10 - 0.2}{5k\Omega} = 1.96 \text{ mA}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = 19.6 \text{ } \mu\text{A}$$

Now we find the actual value of I_B



$$I_{B(actual)} = 10.7 \text{ } \mu\text{A} \text{ (it was found previously)}$$

since

$$I_{B(actual)} < I_{B(sat)} = I_{B(min)} \implies \text{the assumption}$$

made earlier that BJT in saturation mode

 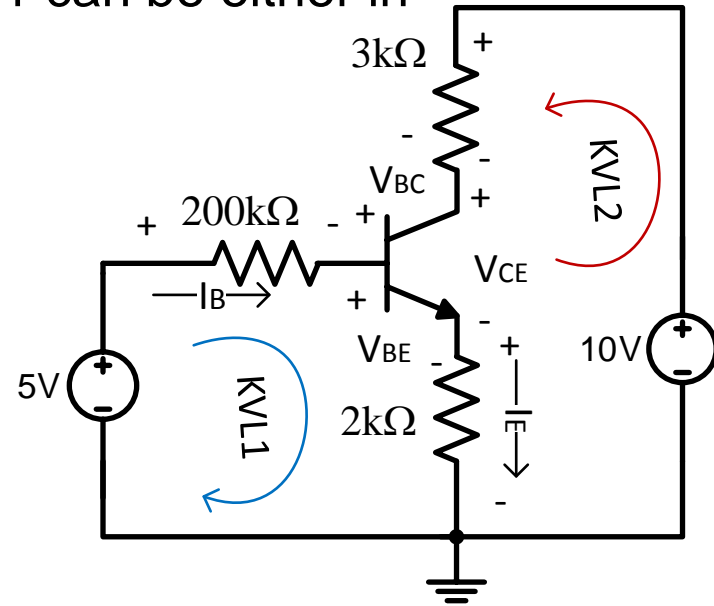is wrong, and actually it is in active mode




Biasing

Biasing: Applying DC voltages to a transistor in order to establish fixed level of voltage and current. For Amplifier (active/Linear) mode, the resulting dc voltage and current establish the operation point to turn it on so that it can amplify AC signals.

Operating Point

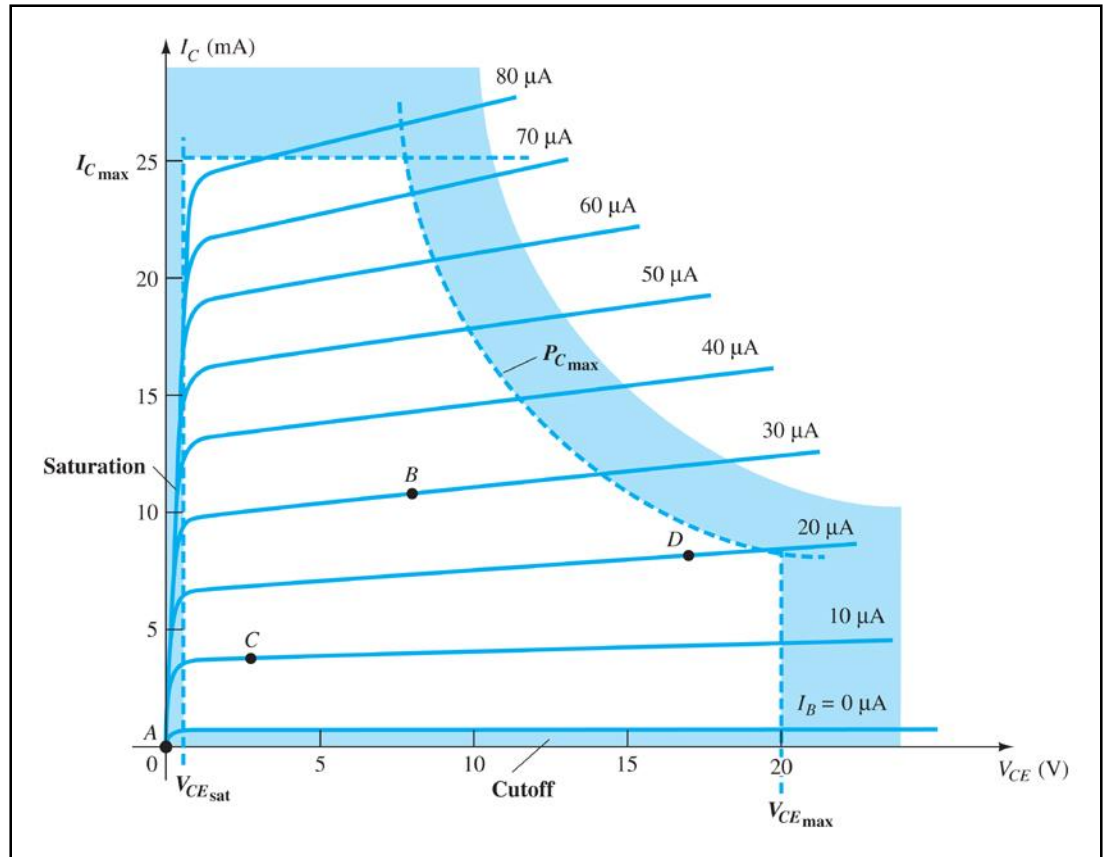The DC input establishes an operating or *quiescent point* called the ***Q-point***.



The Three Operating Regions

Active or Linear Region Operation

- Base–Emitter junction is forward biased
- Base–Collector junction is reverse biased

Cutoff Region Operation

- Base–Emitter junction is reverse biased


Saturation Region Operation

- Base–Emitter junction is forward biased
- Base–Collector junction is forward biased

DC Biasing Circuits


1. Fixed-bias circuit
2. Emitter-stabilized bias circuit
3. DC bias with voltage feedback
4. Voltage divider bias circuit

1) Fixed Bias Configuration

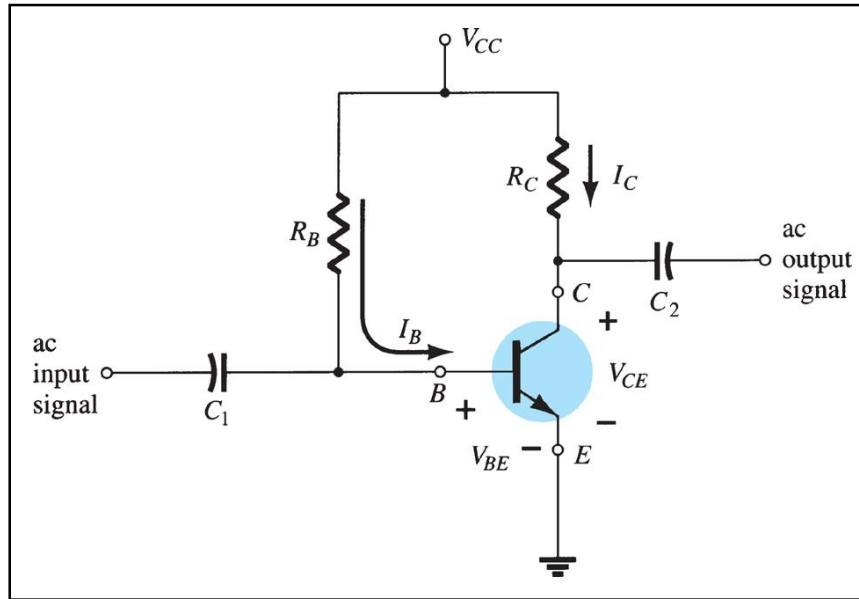

DC equivalent circuit
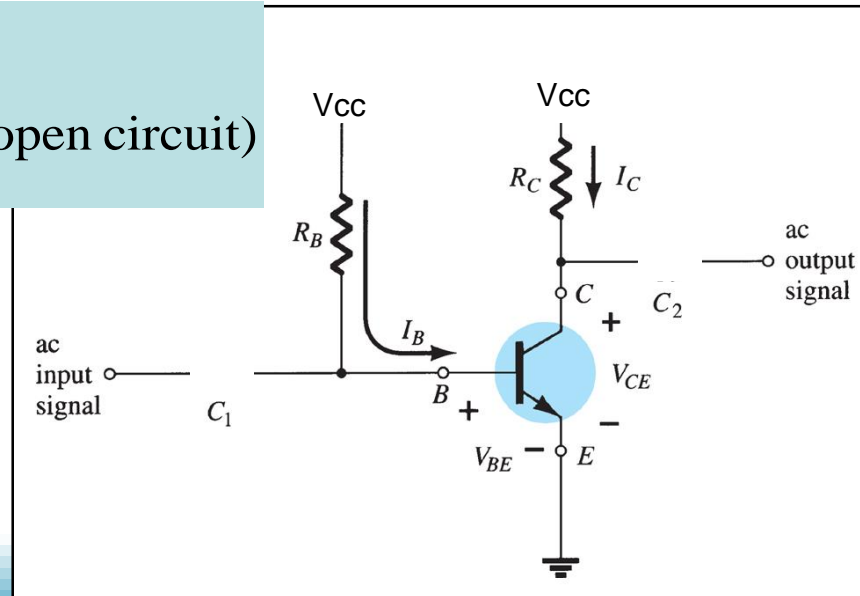
$$f = 0 \Rightarrow X_c = \frac{1}{2\pi f C} \cong \infty \text{ (open circuit)}$$



The Base-Emitter Loop


From Kirchhoff's voltage law for Input:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

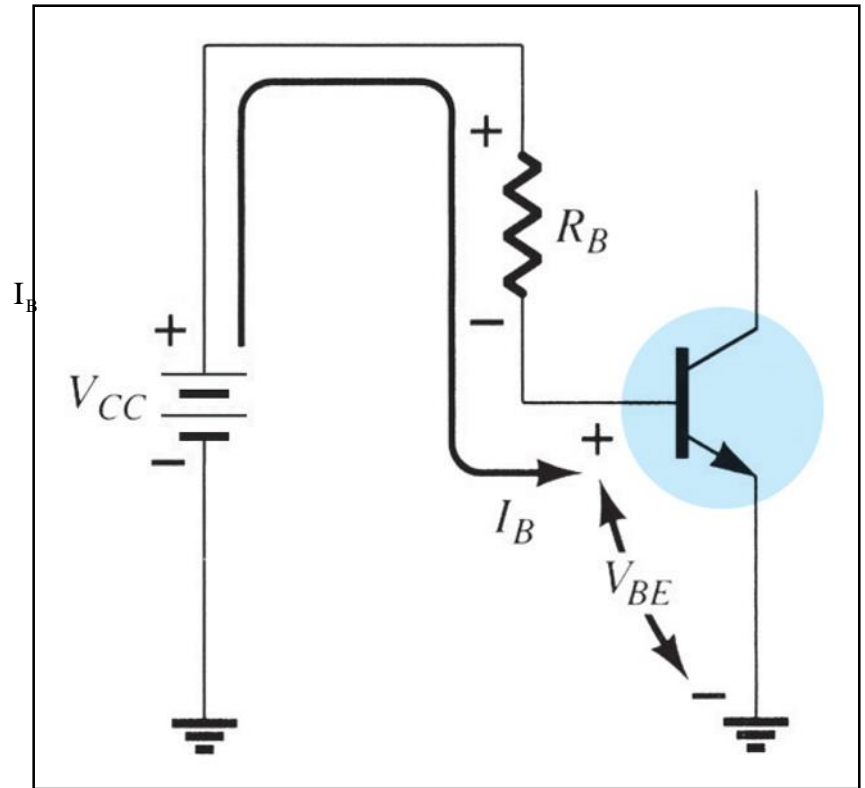Choosing R_B will establish the required level of I_B



Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$



Since $V_E = 0 \Rightarrow \therefore V_{CE} = V_C$

$$V_{CE} = V_{CC} - I_C R_C$$

Also

$$V_{BE} = V_B - V_E$$

$$\therefore V_{BE} = V_B$$

  

$$V_{BE} - V_{CE} - V_{BC} = 0$$

$$\therefore V_{BC} = V_{BE} - V_{CE}$$

Saturation

When the transistor is operating in **saturation**, current through the transistor is at its *maximum* possible value.

$$I_{Csat} = \frac{V_{CC}}{R_C}$$

$$V_{CE} = V_{CE(sat)} \cong 0 \text{ V}$$

Load Line Analysis

The load line end points are:

I_{Csat}


$$I_C = V_{CC} / R_C$$

$$V_{CE} = 0 \text{ V}$$

$V_{CEcuttoff}$


$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$

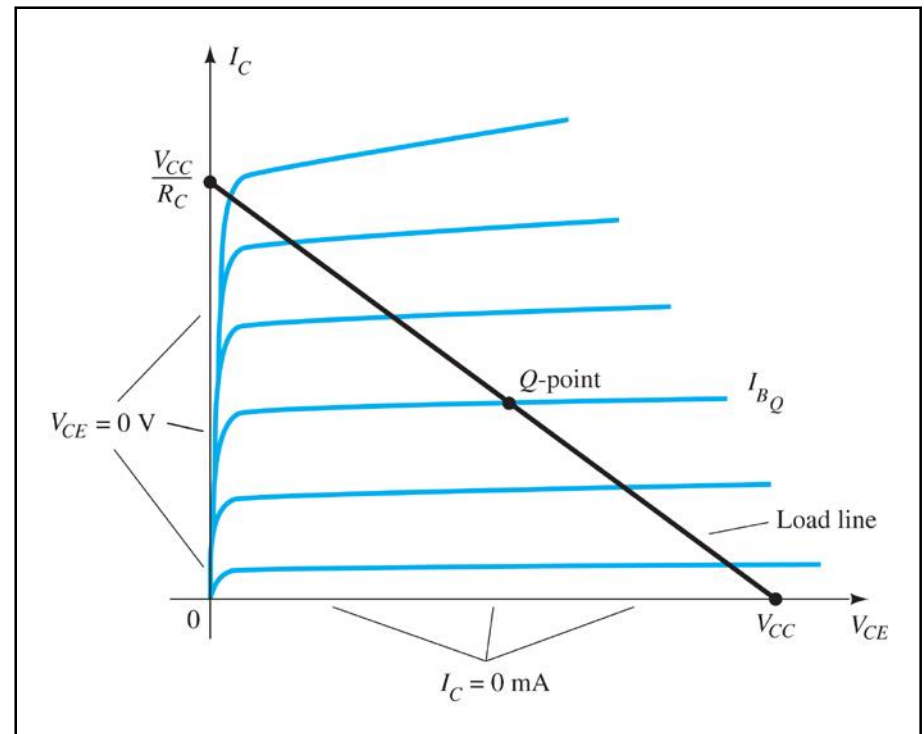


The Q -point is the operating point where the value of R_B sets the value of I_B that controls the values of V_{CE} and I_C .


The Effect of V_{CC} on the Q-Point

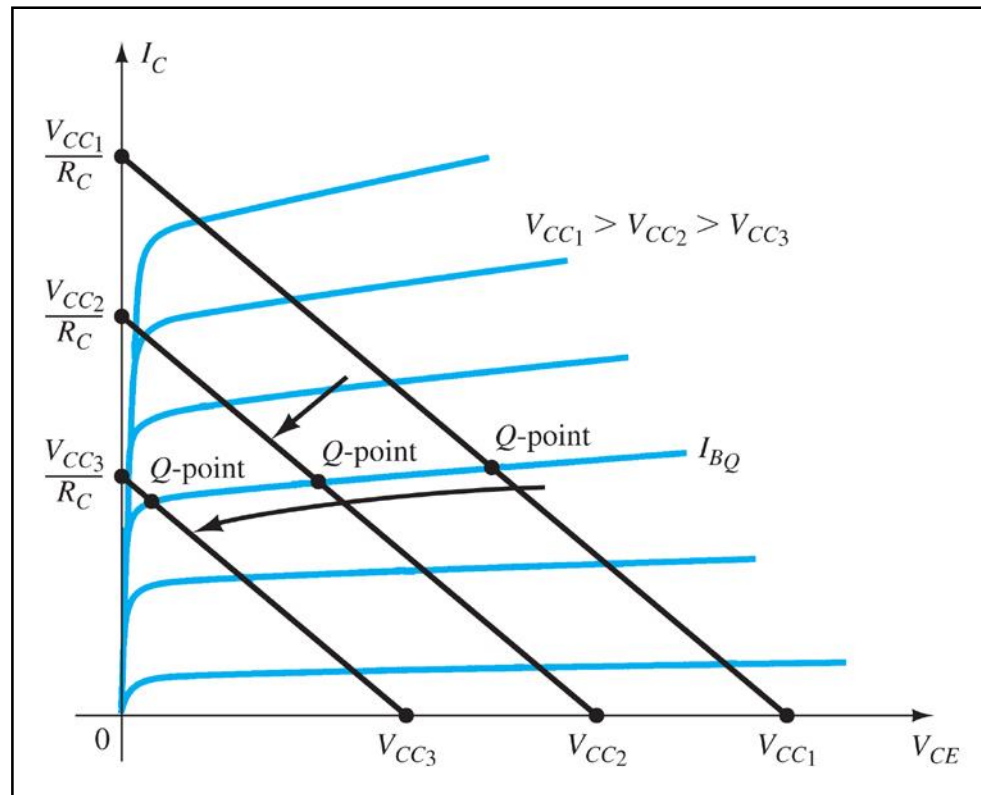

The Effect of R_C on the Q-Point

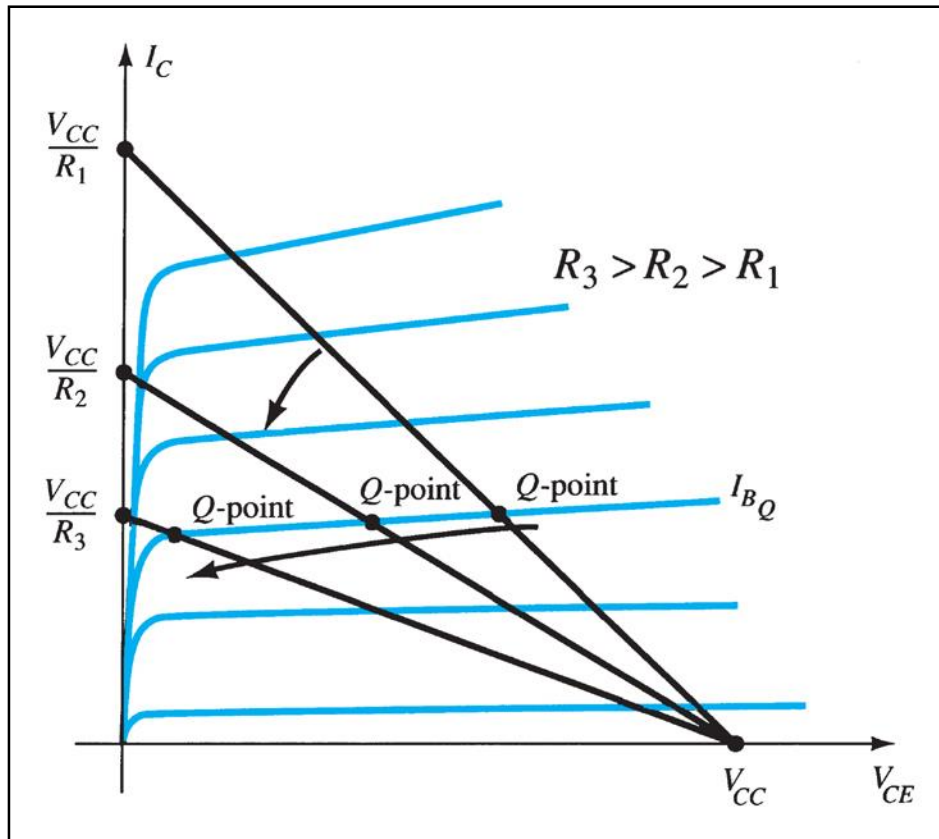

The Effect of I_B on the Q-Point

 

Design: Fixed bias

Assume $V_{CC} = 10\text{V}$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q-point: $V_{CEQ} = 5\text{V}$, $I_{CQ} = 1\text{mA}$

Solution

$$I_{BQ} = \frac{I_{CQ}}{\beta_{\text{nominal}}} = \frac{1\text{ mA}}{100} = 10\ \mu\text{A}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow$$


$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{10 - 0.7}{10\ \mu\text{A}}$$

$$= 930\ \text{k}\Omega$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 5 = 10 - I_C R_C$$
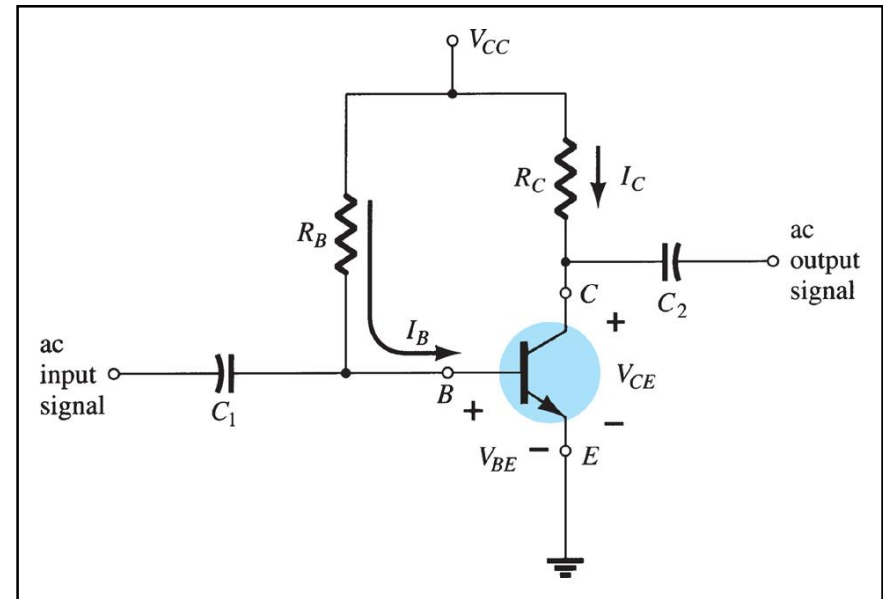
$$\therefore R_C = \frac{5}{1\text{ mA}} = 5\ \text{k}\Omega$$



Fixed bias Stability

Assume $V_{CC} = 10\text{V}$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} =$

Design for Q - point : $V_{CEQ} = 5\text{V}$, $I_{CQ} = 1\text{mA}$

Solution – continued

If $\beta = \beta_{\text{min}} = 50$

$$I_B = 10 \mu\text{A}$$

$$I_C = \beta I_B = (50)(10 \mu\text{A}) = 0.5 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 10 - (0.5 \text{ mA})(5 \text{ k}\Omega) = 7.5 \text{ V}$$


If $\beta = \beta_{\text{max}} = 150$

$$I_B = 10 \mu\text{A}$$

$$I_C = \beta I_B = (150)(10 \mu\text{A}) = 1.5 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$
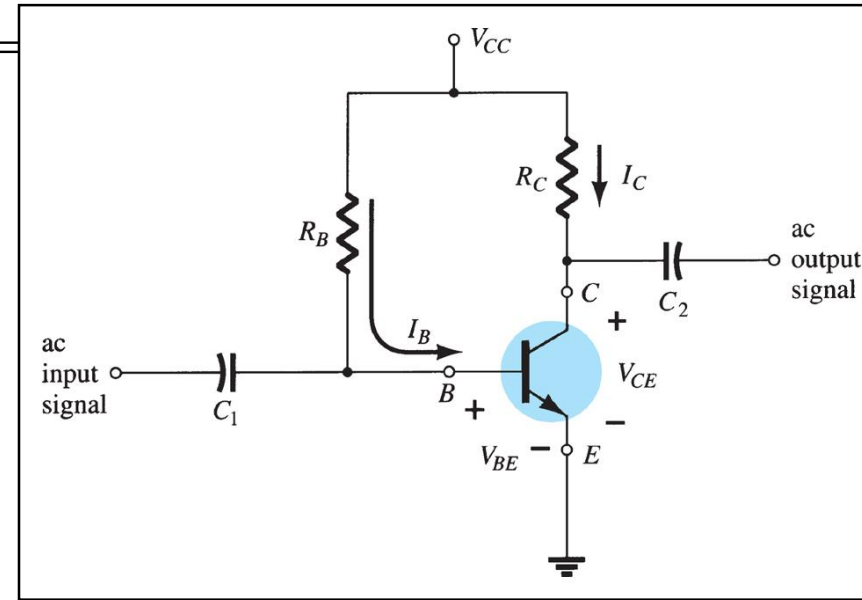
$$V_{CEQ} = 10 - (1.5 \text{ mA})(5 \text{ k}\Omega) = 2.5 \text{ V}$$



for

$$50 \leq \beta \leq 150$$

$$I_B = 10 \mu\text{A} \text{ fixed}$$

$$0.5 \text{ mA} \leq I_C \leq 1.5 \text{ mA}$$


$$7.5 \text{ V} \geq V_{CE} \geq 2.5 \text{ V}$$

$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.5 \text{ mA}}{0.5 \text{ mA}} = 3$$

Not very stable

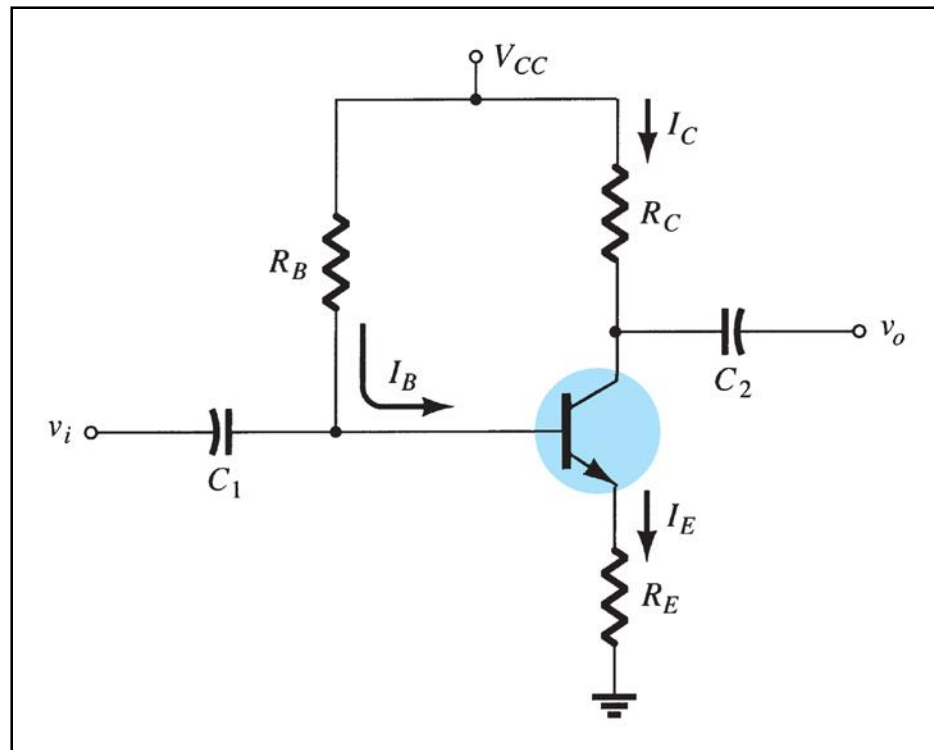2) Emitter-Stabilized Bias Circuit

Adding a resistor (R_E) to the emitter circuit stabilizes the bias circuit.



Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$


Since $I_E = (\beta + 1)I_B$:

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

Solving for I_B :

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

 $(\beta + 1)R_E$ ← is the emitter resistor as it appears
in the base emitter loop



Base-Emitter Loop

Solving for I_E :

$$I_E = \frac{V_{CC} - V_{BE}}{\frac{R_B}{(\beta + 1)} + R_E}$$


In order to get I_E almost independent of β we choose:

$$R_E \gg \frac{R_B}{(\beta + 1)}$$

$$\Rightarrow I_E \cong \frac{V_{CC} - V_{BE}}{R_E}$$

Also, in order to guarantee operation in linear mode

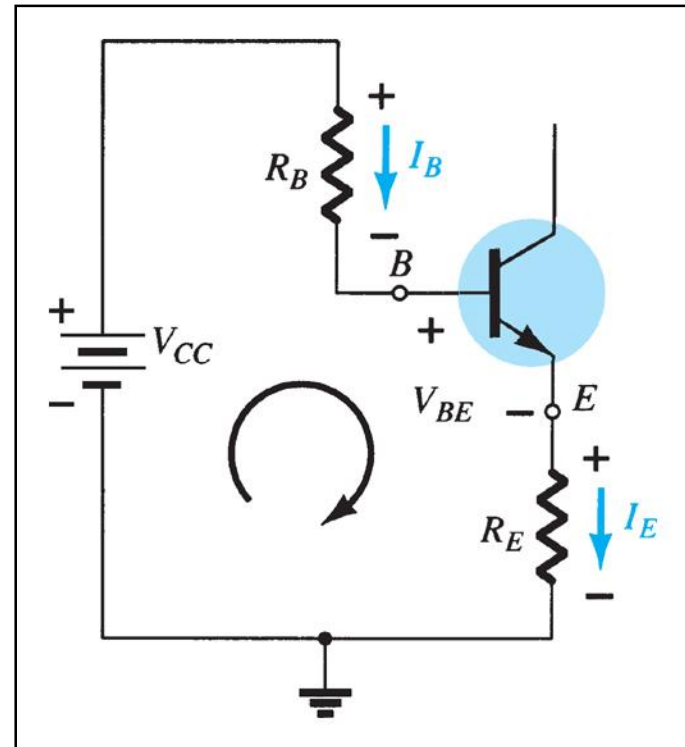we choose $0.1 V_{CC} \leq V_E < 0.2 V_{CC}$



Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since $I_E \cong I_C$:


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
 
$$V_B = V_{CC} - I_R R_B = V_{BE} + V_E$$



Design: Emitter Stabilization bias

Assume $V_{CC} = 10\text{V}$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q - point : $V_{CEQ} = 5\text{V}$, $I_{CQ} = 1\text{mA}$

Solution

$$\text{— let } V_E = 0.1 V_{CC}$$

$$V_E = 1\text{V}$$

$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1\text{V}}{1.01\text{mA}} \cong 1\text{k}\Omega$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \Rightarrow$$

$$R_B I_B + I_B (\beta + 1)R_E = V_{CC} - V_{BE}$$

$$R_B = \frac{V_{CC} - V_{BE} - I_B (\beta + 1)R_E}{I_B}$$

$$= \frac{10 - 0.7 - 10\mu\text{A}(100 + 1)1\text{k}\Omega}{10\mu\text{A}}$$

$$= 829\text{k}\Omega$$

 

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 5 = 10 - 1 - I_C R_C$$

$$\therefore R_C = \frac{4}{1\text{mA}} = 4\text{k}\Omega$$

Emitter bias Stability

If $\beta = \beta_{\min} = 50$

$$I_B = \frac{9.3}{829k\Omega + 51k\Omega} = 10.56 \mu\text{A}$$

$$I_C = \beta I_B = (50)(10.56 \mu\text{A}) = 0.528 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 10 - (0.528 \text{ mA})(4 \text{ k}\Omega) - 1 = 6.89 \text{ V}$$


If $\beta = \beta_{\max} = 150$

$$I_B = \frac{9.3}{829k\Omega + 151k\Omega} = 9.489 \mu\text{A}$$

$$I_C = \beta I_B = (150)(9.489 \mu\text{A}) = 1.423 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$
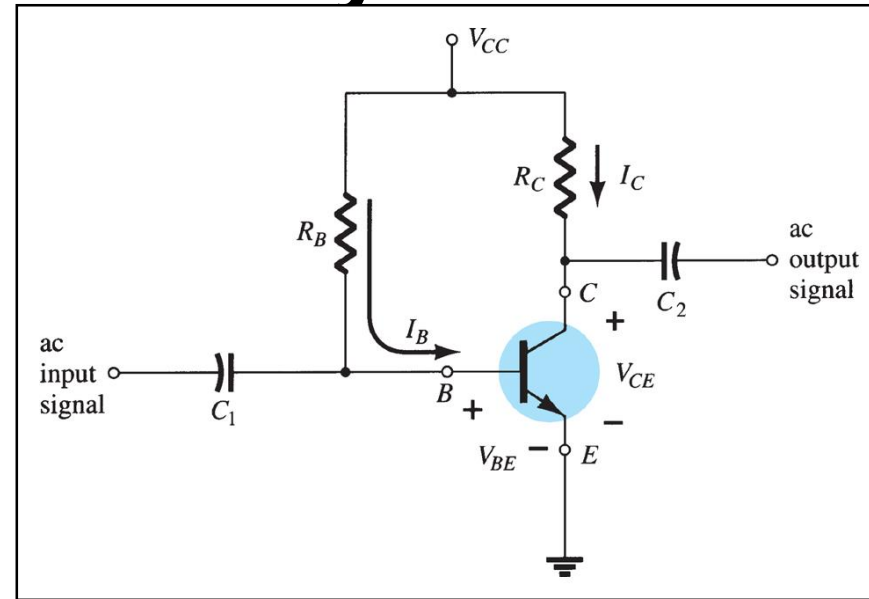
$$V_{CEQ} = 10 - (1.423 \text{ mA})(4 \text{ k}\Omega) - 1 = 3.31 \text{ V}$$



for

$$50 \leq \beta \leq 150$$

$$10.56 \mu\text{A} \geq I_B \geq 9.489 \mu\text{A}$$

$$0.528 \text{ mA} \leq I_C \leq 1.423 \text{ mA}$$

$$6.89 \text{ V} \geq V_{CE} \geq 3.31 \text{ V}$$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.423 \text{ mA}}{0.528 \text{ mA}} \cong 2.7$$



Improved,
but not
very
stable

Improved Biased Stability

Stability refers to a condition in which the currents and voltages remain fairly constant over a wide range of temperatures and transistor Beta (β) values.

Adding R_E to the emitter improves the stability of a transistor.

Saturation Level

 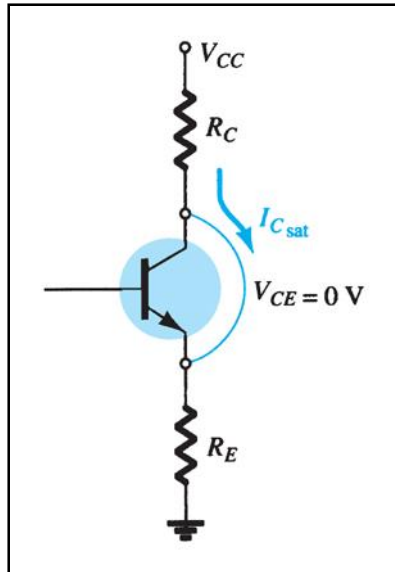

The endpoints can be determined from the load line.

$V_{CE\text{cutoff}}$:

$$V_{CE} = V_{CC}$$
$$I_C = 0\text{ mA}$$


$I_{C\text{sat}}$:

$$V_{CE} = 0\text{ V}$$
$$I_C = \frac{V_{CC}}{R_C + R_E}$$

 3) DC Bias With Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

In this bias circuit the Q-point is only slightly dependent on the transistor beta, β .



Base-Emitter Loop

From Kirchhoff's voltage law:

$$V_{CC} - I.R_L - I_B R_B - V_{BE} = 0$$

$$I = I_C + I_B$$

$$I_C = \beta I_B$$


Solving for I_B :

$$I_B = \frac{V_{CC} - V_{BE}}{R_L (\beta + 1) + R_B}$$

$$V_{CC} = I.R_L + V_{CE}$$

$$I = I_C + I_B$$

$$V_{CE} = V_{CC} - (I_C + I_B)R_L$$

 

suppose $\beta \uparrow$, $I_B \downarrow$, $I_C = \uparrow \beta \cdot I_B \downarrow \cong \text{const}$
there is some kind of compensation effect

Design: Voltage feedback bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q-point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

$$R_L = \frac{V_{CC} - V_{CE}}{I_C + I_B} = \frac{10 - 5}{1mA + \frac{1mA}{100}}$$

$$= 4.95 \text{ k}\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$\therefore R_B = 430 \text{ k}\Omega$$

If $\beta = \beta_{\text{min}} = 50$

$$I_B = 0.013627 \text{ mA}$$

$$I_C = 0.68 \text{ mA}$$

If $\beta = \beta_{\text{max}} = 150$

$$I_B = 0.00793 \text{ mA}$$

$$I_C = 1.19 \text{ mA}$$


for

$$50 \leq \beta \leq 150$$

$$0.68 \text{ mA} \leq I_C \leq 1.19 \text{ mA}$$

$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.19 \text{ mA}}{0.68 \text{ mA}} \cong 1.75$$

Better
Q-point
stability

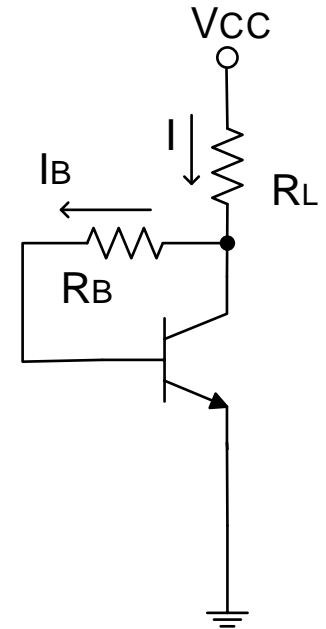

Base-Emitter Bias Analysis

Transistor Saturation Level

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_L}$$

Load Line Analysis

Cutoff

$$V_{CE} = V_{CC}$$
$$I_C = 0 \text{ mA}$$


Saturation

$$I_C = \frac{V_{CC}}{R_L}$$
$$V_{CE} = 0 \text{ V}$$

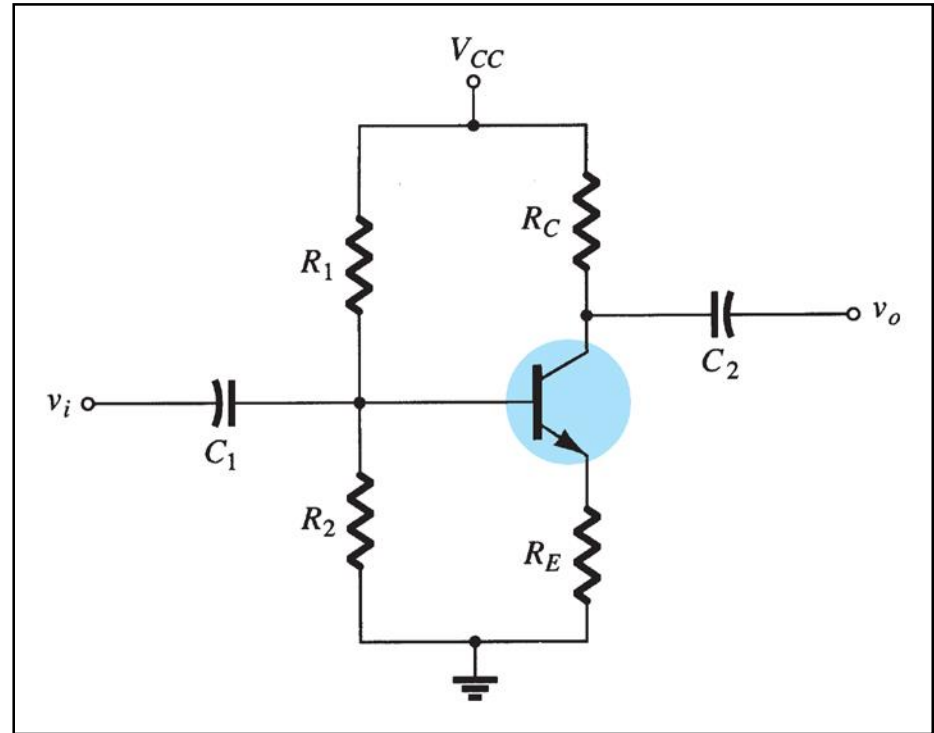4) Voltage Divider Bias

This is a very stable bias circuit.

The currents and voltages are nearly independent of any variations in β if the circuit is designed properly




Approximate Analysis

Where $I_B \ll I_1$ and $I_1 \cong I_2$:

$$V_B = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$
 
$$I_{E(\text{approximate})} = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E}$$



From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Here we got I_C independent of β which provides good Q-point stability

Exact Analysis

We must try to make I_B as close as possible to zero

Thevenin Equivalent circuit for the circuit left of the base is done



$$V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$\text{but } I_B = \frac{I_E}{\beta + 1}$$
  
$$\therefore I_{E(\text{exact})} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$




Exact Analysis

$$\therefore I_{E(\text{exact})} = \frac{V_{\text{th}} - V_{\text{BE}}}{\frac{R_{\text{th}}}{\beta + 1} + R_E}$$

if we compare to approximate solution

$$I_{E(\text{approximate})} = \frac{V_B - V_{\text{BE}}}{R_E}$$

 \Rightarrow we must make the quantity $\frac{R_{\text{th}}}{\beta + 1} \ll R_E$




Here we got I_c independent of β

$$\therefore R_{\text{th}} \ll (\beta + 1)R_E$$

$$\text{as a rule let } R_{\text{th}} \ll \frac{(\beta + 1)R_E}{10}$$

or
 
$$R_{\text{th}} \ll \frac{\beta R_E}{10}$$



Design: Voltage Divider bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q - point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

1) let $V_E = 0.1 V_{CC}$

$$V_E = 1V$$


$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01mA} \cong 1k\Omega$$

2) let $R_{th} = \frac{R_E \cdot \beta_{\text{nominal}}}{50} = \frac{1k\Omega \cdot 100}{50} = 2k\Omega$

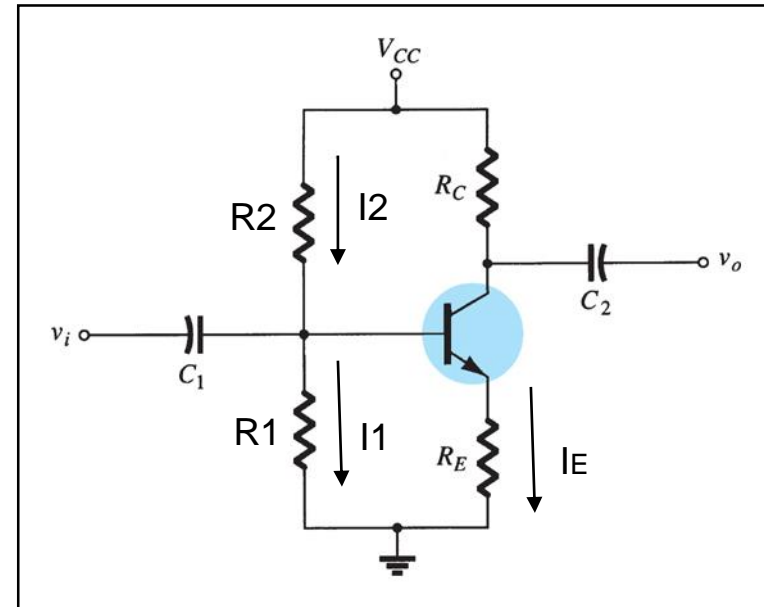3) $V_{CC} = R_C I_C + I_E R_E + V_{CE}$

$$V_{CEQ} = 5$$

$$\therefore R_C = \frac{V_{CC} - V_{CE} - V_E}{1mA} = \frac{10 - 5 - 1}{1mA} = 4k\Omega$$



Design: Voltage Divider bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q - point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution – continued

$$4) I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$


$$\therefore V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2} = I_E \left(\frac{R_{th}}{\beta + 1} + R_E \right) + V_{BE} = 1.72V \dots(1)$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = 2 \text{ k}\Omega \dots\dots\dots(2)$$

solving (1) & (2) yields:

$$R_1 = 2.42 \text{ k}\Omega$$

$$R_2 = 11.64 \text{ k}\Omega$$

 

Voltage Divider bias Stability

$$\text{If } \beta = \beta_{\min} = 50$$

$$I_C = 0.982 \text{ mA}$$

$$\text{If } \beta = \beta_{\max} = 150$$

$$I_C = 1.0069 \text{ mA}$$

for

$$50 \leq \beta \leq 150$$

$$0.982 \text{ mA} \leq I_C \leq 1.0067 \text{ mA}$$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.0067 \text{ mA}}{0.982 \text{ mA}} \cong 1.0254$$

Very good
Q-point
stability

Voltage Divider Bias Analysis

Transistor Saturation Level

$$I_{Csat} = I_{Cmax} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff:

$$V_{CE} = V_{CC}$$
$$I_C = 0 \text{ mA}$$

Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$
$$V_{CE} = 0 \text{ V}$$

PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *npn* transistor circuits. The only difference is that the currents are flowing in the opposite direction.

DC and AC Load Lines

Assume $V_{CC} = 18V$, $\beta = 100$

$R_B = 576\text{ k}\Omega$; $R_C = 3\text{ k}\Omega$; $V_{BE} = 0.65\text{ V}$

FIRST: DC ANALYSIS

$$V_{CC} = V_{CE} + I_C R_C$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \Leftarrow I_C = f(V_{CE})$$


This is a straight line equation

$$Y = mX + b$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{18 - 0.65}{576\text{ k}\Omega} = 30\text{ }\mu\text{A}$$

$$I_C = \beta I_B = 3\text{ mA}$$
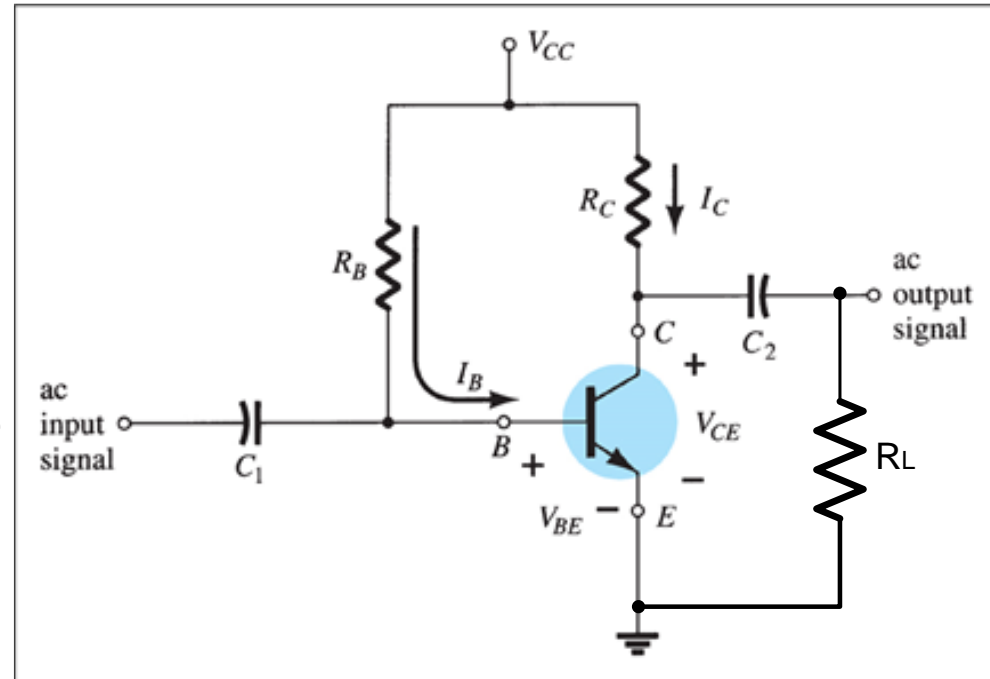
$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C = 18 - (3\text{ mA})(3\text{ k}\Omega) \\ &= 9\text{ V} \end{aligned}$$



DC Load Line

I_{Csat}

$$I_{Csat} = \frac{V_{CC}}{R_C}$$


$$V_{CE} = V_{CE(sat)} \cong 0 V$$

$V_{CEcutoff}$

$$V_{CE(cutoff)} = V_{CC}$$


$$I_C = 0 \text{ mA}$$
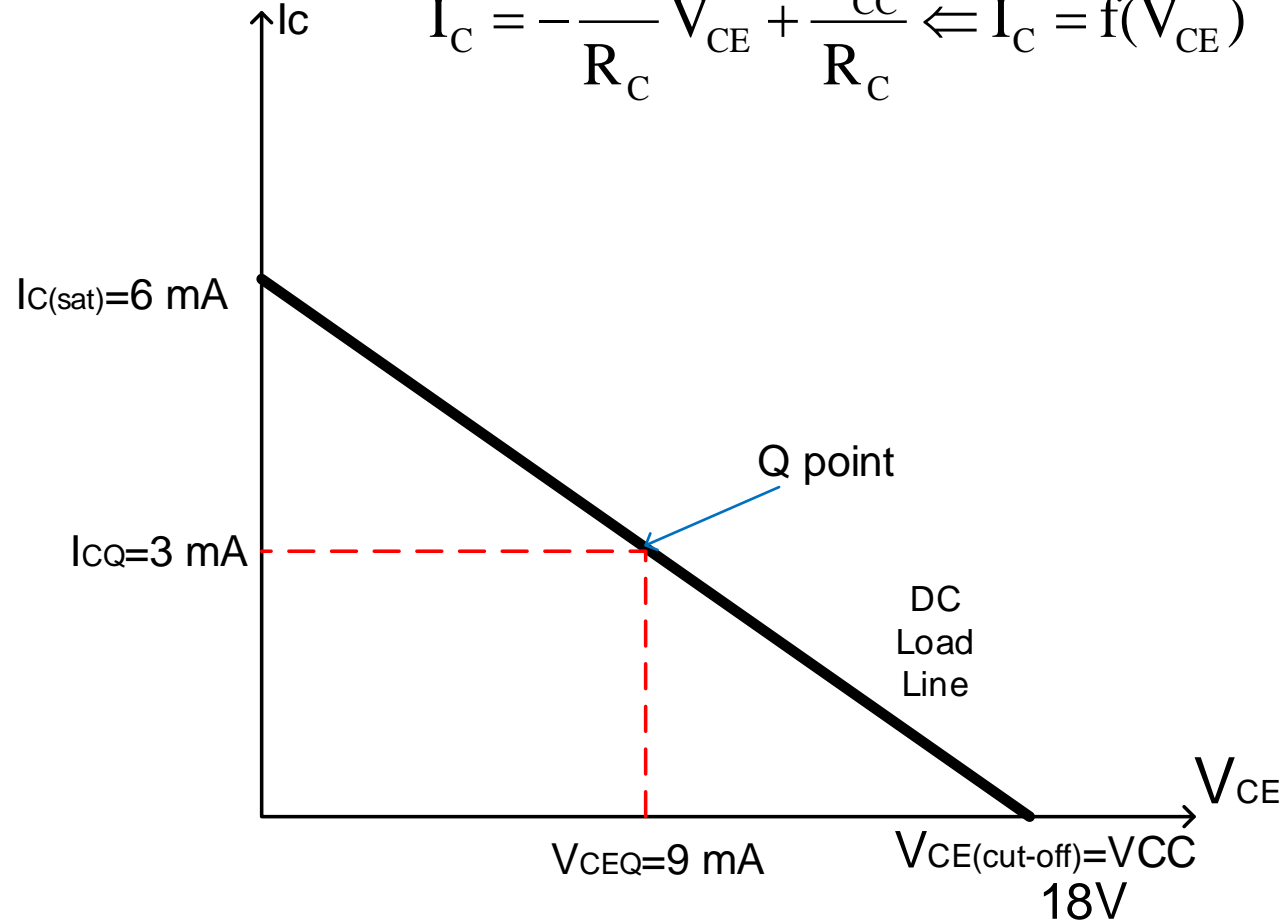
$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \Leftarrow I_C = f(V_{CE})$$



AC Load Line

AC Equivalent Circuit

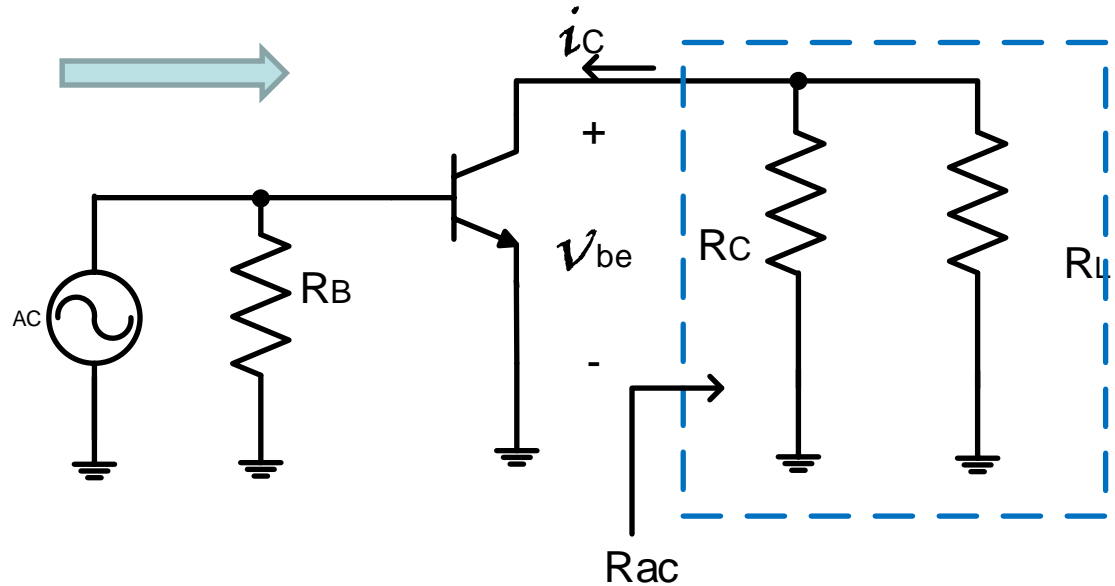

Since we have dc and ac quantities,

let us define the notation

total DC ac

$$V_{BE}(t) = V_{BE} + v_{be}$$

$$V_{CE}(t) = V_{CE} + v_{ce}$$

$$I_C(t) = I_C + i_c$$

$$I_B(t) = I_B + i_b$$


$$v_{ce} = -R_{ac} \cdot i_c$$

$$\text{where } R_{ac} = R_c // R_L$$

is the ac resistance seen from collector terminal
+ resistance seen from emitter terminal

AC Load Line

AC Equivalent Circuit

 

$$v_{ce} = V_{CE}(t) - V_{CE}$$

$$i_c = I_C(t) - I_C$$

$$v_{ce} = -R_{ac} \cdot i_c$$

$$(V_{CE}(t) - V_{CEQ}) = -R_{ac} \cdot (I_C(t) - I_{CQ})$$


Ac load line equation

To Draw ac load line

we find $(V_{CE}(t)_{\max})$ and $(I_C(t)_{\max})$

AC Load Line

AC Equivalent Circuit

 


$$(V_{CE}(t) - V_{CEQ}) = -R_{ac} \cdot (I_C(t) - I_{CQ})$$


$$(V_{CE}(t)_{\max} - V_{CEQ}) = R_{ac} \cdot I_{CQ}$$

$$V_{CE}(t)_{\max} = V_{CEQ} + R_{ac} \cdot I_{CQ}, \text{ when } I_C(t) = 0$$

$$(V_{CE}(t) - V_{CEQ}) = -R_{ac} \cdot (I_C(t) - I_{CQ})$$
 
$$I_C(t)_{\max} = \frac{V_{CEQ}}{R_{ac}} + I_{CQ} \text{ when } V_{CE}(t) = 0$$



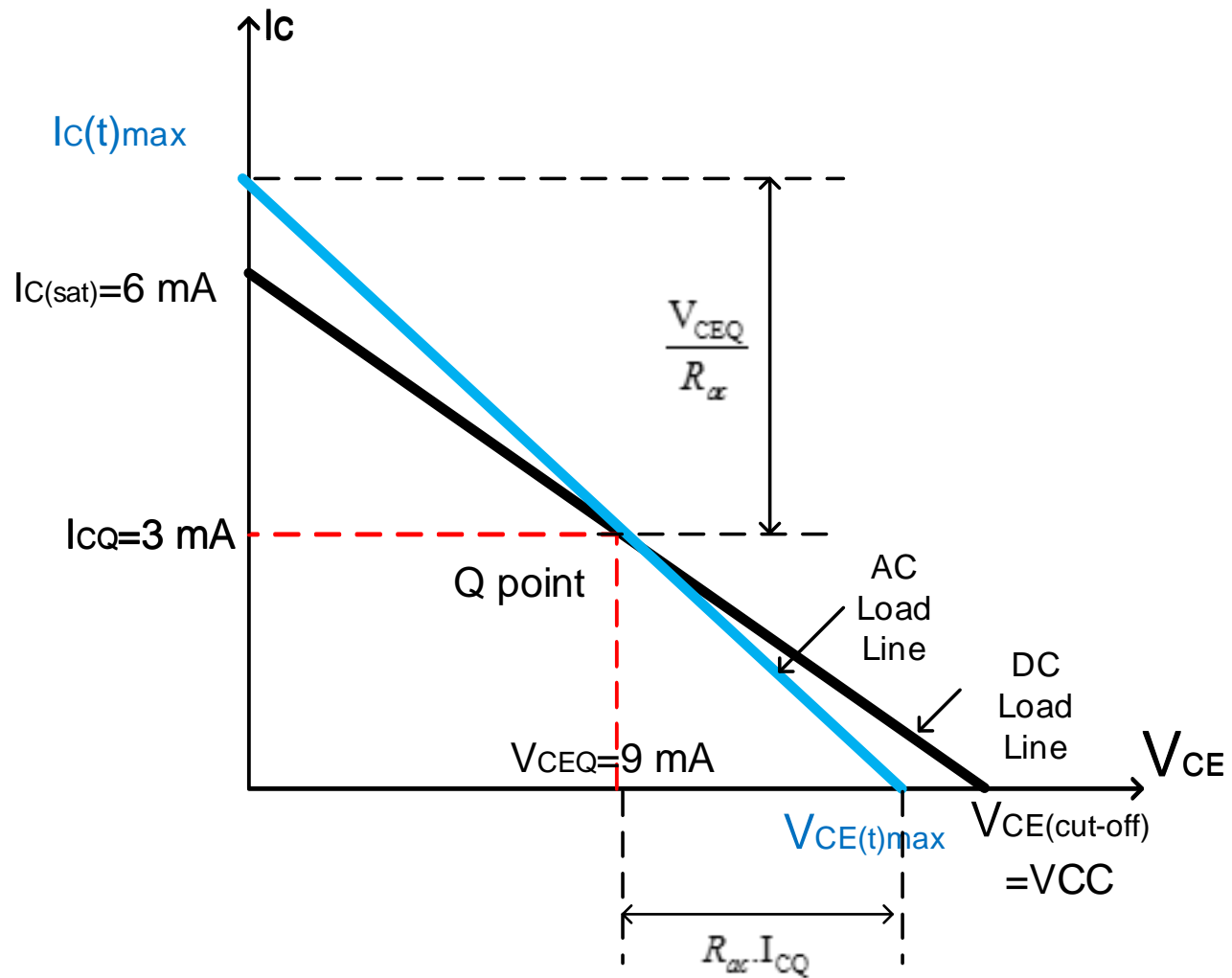

Design

- In order to have the amplifier to amplify an input ac signal without distortion (by going into saturation or cut-off)
- We choose the Q-point in the middle of ac load line

$$I_{CQ} = \frac{1}{2} I_{C(t)\max}$$

$$V_{CEQ} = \frac{1}{2} V_{CE(t)\max}$$



$$2I_{CQ} = I_{C(t)\max}$$

$$2I_{CQ} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

$$\therefore I_{CQ} = \frac{V_{CEQ}}{R_{ac}}$$

DC Analysis

$$V_{CC} = V_{CE} + I_C R_C$$

define $R_{dc} = R_C$

$$V_{CC} = V_{CE} + I_C R_{dc}$$

at the Q - point

$$V_{CC} = V_{CEQ} + I_{CQ} R_{dc}$$

For maximum Symmetrical swing



$$I_{CQ} = \frac{V_{CEQ}}{R_{ac}} \Rightarrow V_{CEQ} = I_{CQ} R_{ac}$$

$$V_{CC} = I_{CQ} \cdot R_{ac} + I_{CQ} \cdot R_{dc}$$

$$\therefore I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}}$$



To design for maximum
Symmetrical Swing

DC Analysis

Also

$$V_{CEQ} = V_{CC} - I_{CQ} R_{dc}$$

$$= V_{CC} - R_{dc} \frac{V_{CC}}{R_{ac} + R_{dc}}$$


$$= V_{CC} \left(1 - \frac{R_{dc}}{R_{ac} + R_{dc}} \right)$$

$$= V_{CC} \left(\frac{R_{ac} + R_{dc} - R_{dc}}{R_{ac} + R_{dc}} \right)$$

$$= V_{CC} \left(\frac{R_{ac}}{R_{ac} + R_{dc}} \right) = \left(\frac{V_{CC}}{1 + \frac{R_{dc}}{R_{ac}}} \right) \text{***** For maximum Symmetrical swing}$$

Design Example

 Design for maximum symmetrical swing of the collector current? Find the Q-point?
Find the required Value of R_B ?
Draw AC and DC load lines
What is the power dissipation of the transistor at the Q-point?



Solution

$$R_{ac} = R_C = 1 \text{ k}\Omega$$

$$R_{dc} = R_C + R_E = 1.5 \text{ k}\Omega$$

For Maximum Symmetrical Swing of I_c

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}} = \frac{15}{1 \text{ k}\Omega + 1.5 \text{ k}\Omega} = 6 \text{ mA}$$


$$V_{CEQ} = \frac{V_{CC}}{1 + \frac{R_{dc}}{R_{ac}}} = \frac{15}{1 + \frac{1.5 \text{ k}\Omega}{1 \text{ k}\Omega}} = 6 \text{ V}$$

Maximum Swing (peak) of I_c

$$I_{CM} = I_{CQ} = 6 \text{ mA}$$

Maximum Symmetrical Swing (peak - peak) of I_c

$$I_{Cp-p} = 2I_{CQ} = 12 \text{ mA}$$

 


Solution

For Maximum Symmetrical Swing of I_c


$$I_C(t)_{\text{Max}} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 6 \text{ mA} + \frac{6}{1 \text{ k}\Omega} = 12 \text{ mA}$$

For Maximum Symmetrical Swing of I_c
 
$$V_{CE}(t)_{\text{Max}} = I_{CQ} R_{ac} + V_{CEQ} = 6 \text{ mA} \cdot 1 \text{ k}\Omega + 6 = 12 \text{ V}$$



Example -Continued

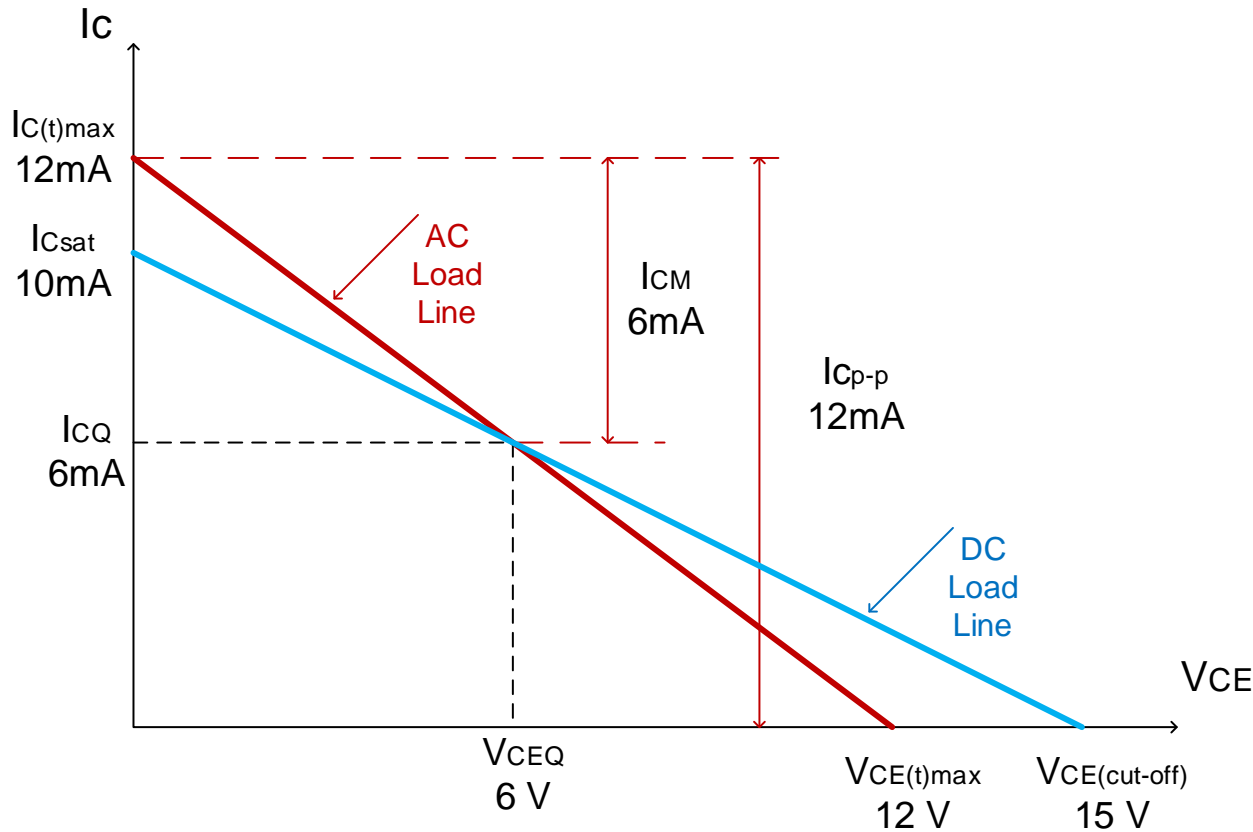

$$I_B = \frac{4.7 - 0.7}{R_E(100 + 1) + R_B} = \frac{I_{CQ}}{100} = 60 \mu\text{A}$$

$$\therefore R_B = 33 \text{ k}\Omega$$

$$P_Q = V_{CEQ} \cdot I_{CQ} = 6\text{V} \cdot 6\text{mA} = 36 \text{ mW}$$


Analysis Example

$R_B = 50 \text{ k}\Omega$

Find the maximum collector current swing and the Q-point?

Draw AC and DC load lines

 What is the power dissipation of the transistor at the Q-point?



$$R_{ac} = R_C = 1 \text{ k}\Omega$$

$$R_{dc} = R_C + R_E = 1.5 \text{ k}\Omega$$

Value of I_C

$$I_B = \frac{4.7 - 0.7}{R_E(100 + 1) + R_B}$$

$$= \frac{4.7 - 0.7}{500(100 + 1) + 50\text{k}\Omega}$$

$$= 40 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 4 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) = 9 \text{ V}$$

Maximum Swing (peak) of I_C


$$I_{CM} \neq I_{CQ}$$

$$I_{CM} = 4 \text{ mA}$$

Maximum Symmetrical Swing (peak - peak) of I_C

$$I_{Cp-p} = 2I_{CM} = 8 \text{ mA}$$



Solution

 

Solution

$$I_C(t)_{\text{Max}} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 4 \text{ mA} + \frac{9}{1 \text{ k}\Omega} = 13 \text{ mA}$$
 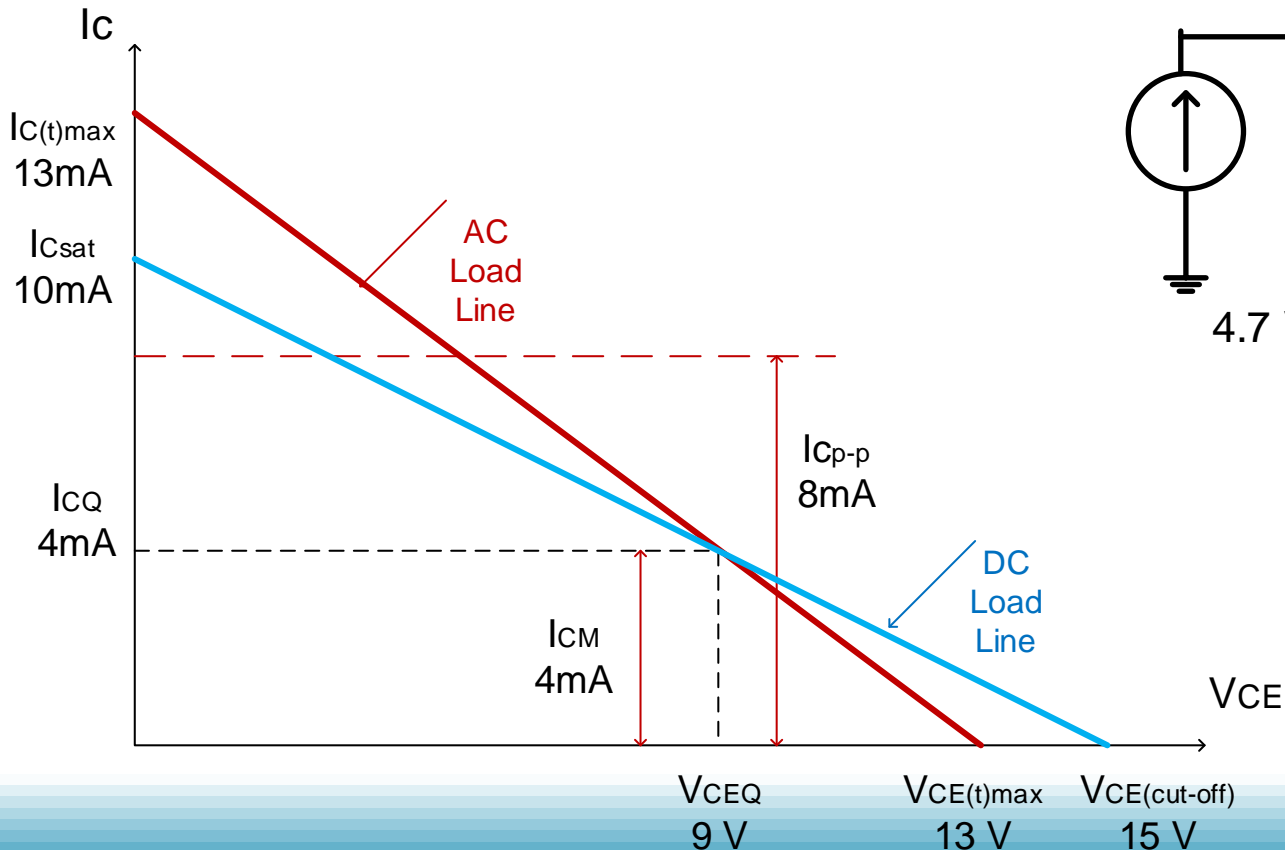
$$V_{CE}(t)_{\text{Max}} = I_{CQ}R_{ac} + V_{CEQ} = 4 \text{ mA} \cdot 1 \text{ k}\Omega + 9 = 13 \text{ V}$$






Maximum Swing was reduced because the Q-point was not placed properly

Example -Continued

Basic BJT Amplifiers Circuits

Graphical Analysis

   - Can be useful to understand the operation of BJT circuits.
- First, establish DC conditions by finding I_B (or V_{BE})
- Second, figure out the DC operating point for I_C





Can get a feel for whether the BJT will stay in active region of operation

– What happens if R_C is larger or smaller?

Basic BJT Amplifiers Circuits

Graphical Analysis

 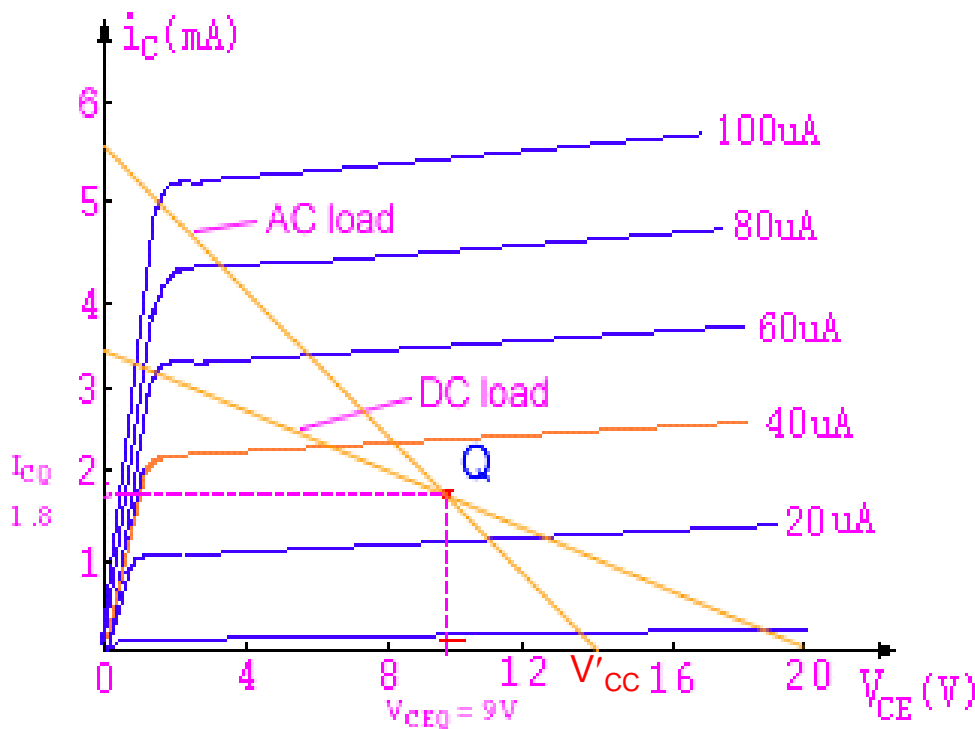




$$v_{ce} = -i_c (R_C \parallel R_L) = -i_c R'_L$$

$$V_{CC}' = V_{CEQ} + I_{CQ} R'_L$$

Basic BJT Amplifiers Circuits

Graphical Analysis




Q-point is centered on the ac load line:

   

Basic BJT Amplifiers Circuits

Graphical Analysis

Q-point closer to cutoff:

   




Clipped at cutoff
(cutoff distortion)

Basic BJT Amplifiers Circuits

6.2 Single-Stage BJT Amplifiers

Graphical Analysis



Q-point closer to saturation:

   

**Clipped at cutoff
(saturation distortion)**


Basic BJT Amplifiers Circuits

Graphical Analysis

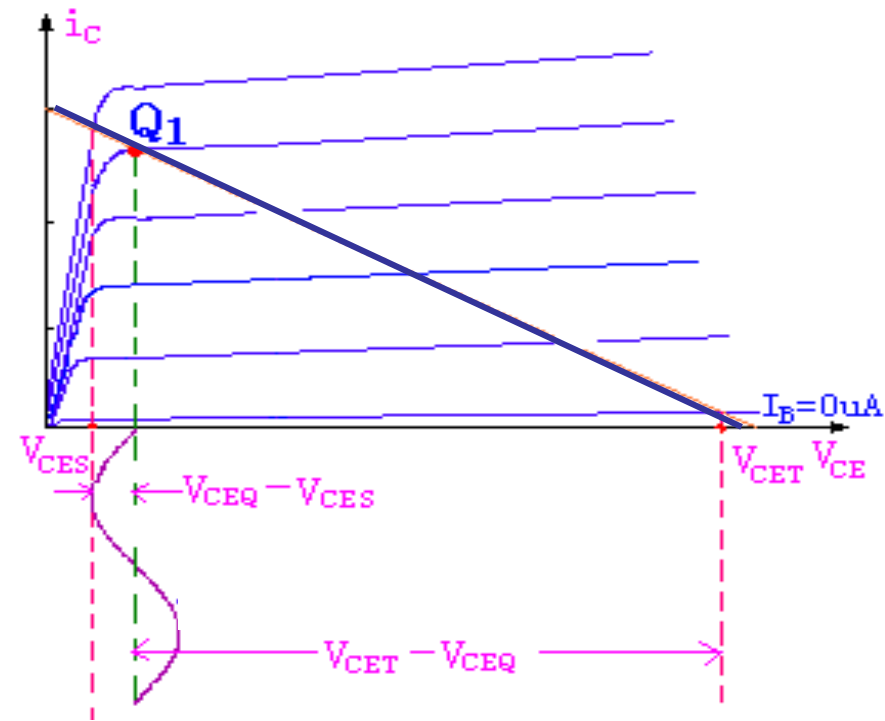 

Transistor Switching Networks

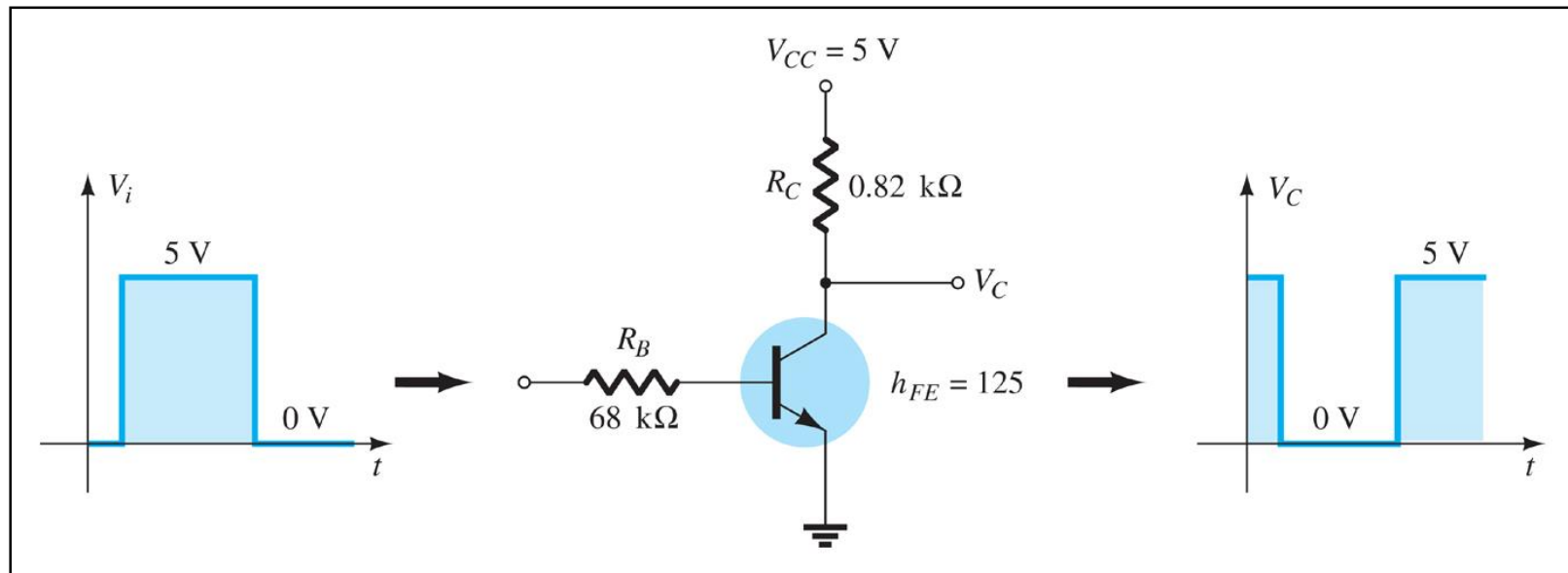Transistors with only the DC source applied can be used as electronic switches.



For $V_i = 5\text{V}$

$$I_B = \frac{5 - 0.7}{68\text{ k}\Omega} = 63.24\ \mu\text{A}$$


$$I_C = (125)(63.24\ \mu\text{A}) = 7.9\ \text{mA}$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 5 - (7.9\ \text{mA})(0.82\text{ k}\Omega) \\ &= -1.482\text{ V} < V_{CE(\text{sat})} \end{aligned}$$

\therefore BJT is in Sat. Mode & $V_C = V_{CE(\text{sat})}$

Transistor Switching Networks

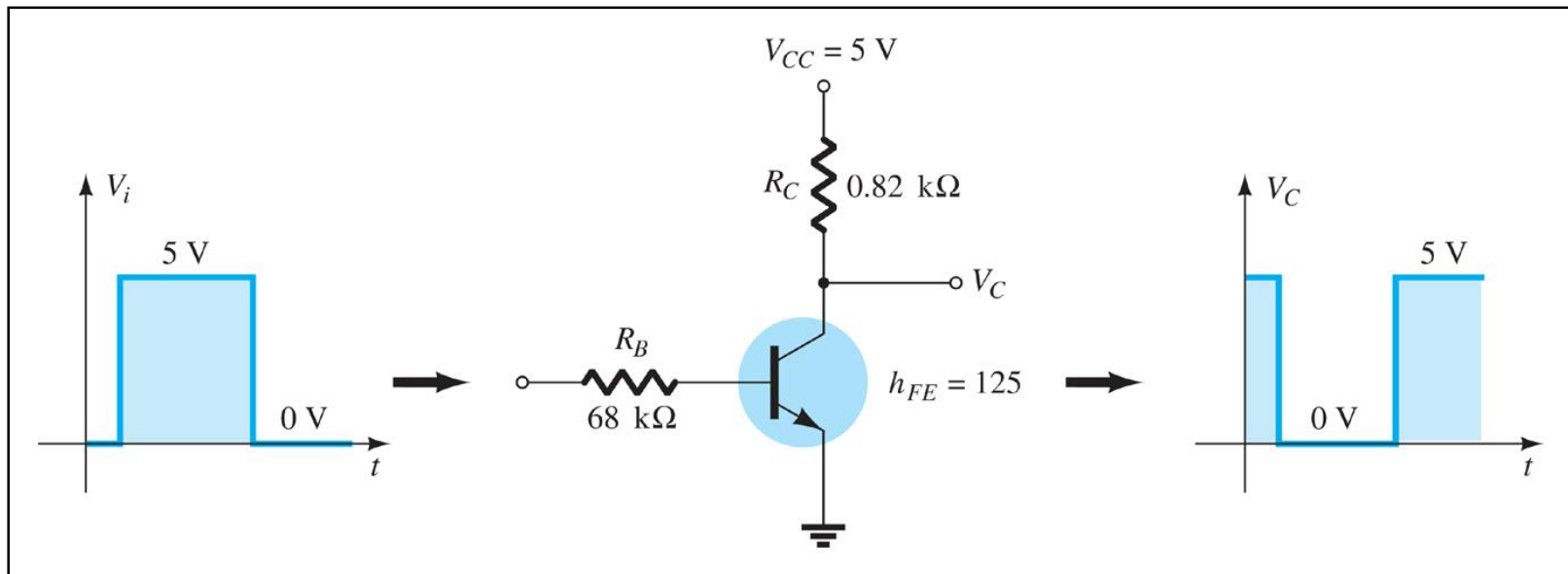
Transistors with only the DC source applied can be used as electronic switches.



$$\Rightarrow I_{C(\text{sat})} = \frac{5}{0.82 \text{ k}\Omega} = 6.1 \text{ mA}$$
$$V_O = V_{CE(\text{sat})} \cong 0.2 \text{ V}$$

Transistor Switching Networks

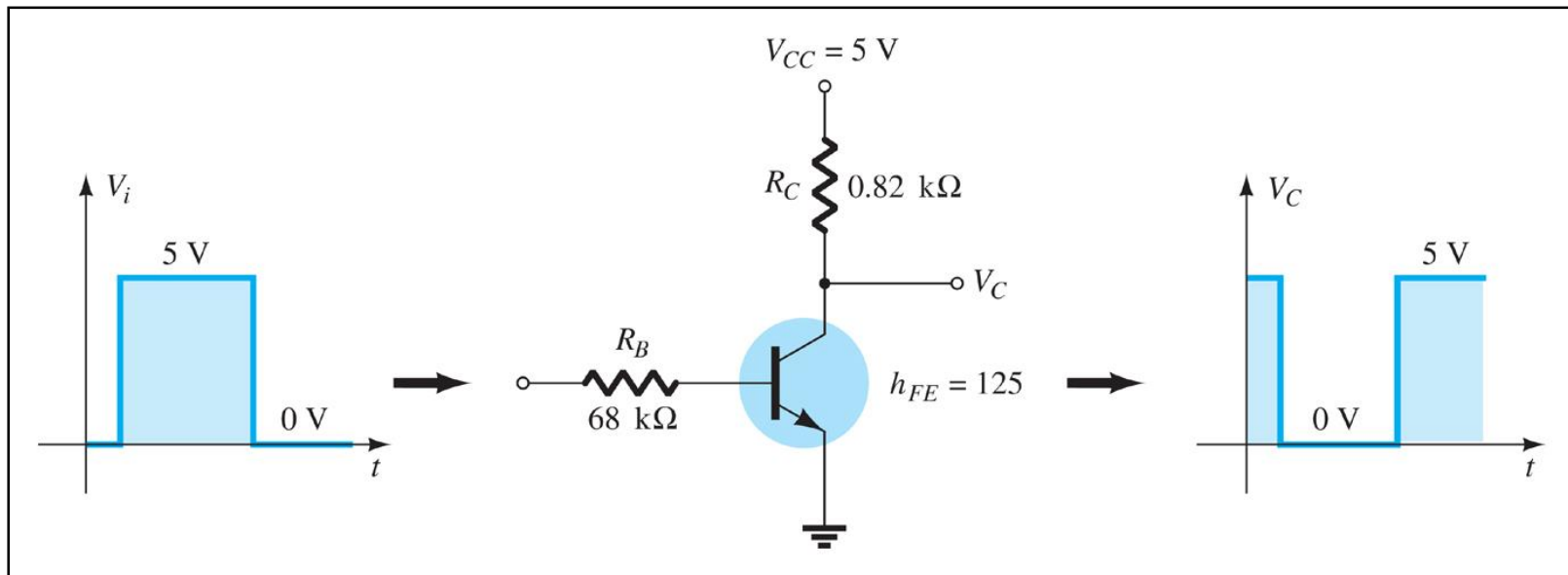Transistors with only the DC source applied can be used as electronic switches.



For $V_i = 0\text{V}$

$$I_B = 0$$

$$I_C = 0$$

$$V_{CE} = V_{CC}$$

\therefore BJT is in Cut - off Mode & $V_C = V_{CE(\text{cut0ff})} = V_{CC} = 5\text{V}$