

# **Analog Electronic**

ENEE236

## **BJT AC Analysis**


**Chapter 5**

# Small Signal ac Equivalent Circuit

- In order to simplify the analysis, we replace the Transistor by an equivalent circuit (model)
- An AC model represents the AC characteristics of the transistor.
- A model uses circuit elements that approximate the behavior of the transistor.
- There are two models commonly used in small signal AC analysis of a transistor:
  - **$r_e$  model**
  - **Hybrid equivalent model**

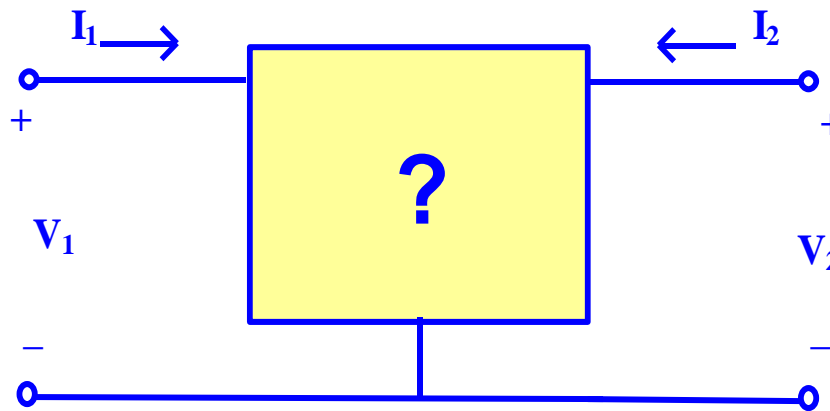
## Modeling Two-Port Networks

- Two-port parameters can be determined for a given network.
- Additionally, two-port parameters might be specified for a certain device by the manufacturer (such as h-parameter values for a transistor).
- How are these parameters used?
- They are used to form a circuit model for the device or circuit. A circuit model is developed using the two-port parameter equations.



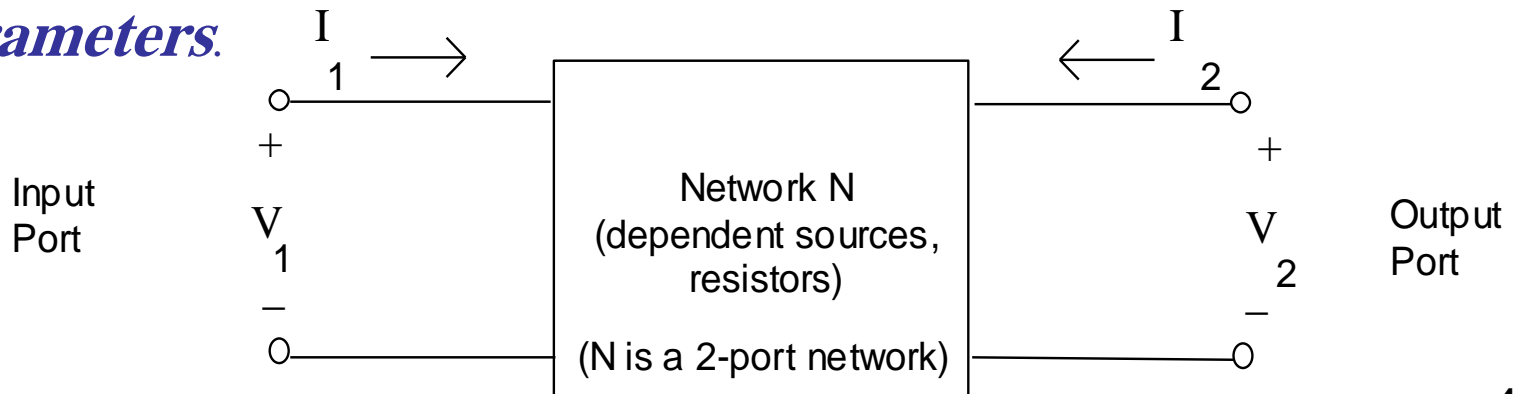
## Two-port networks

- Suppose that a network N has two ports as shown below. How could it be represented or modeled?
- A common way to represent such a network is to use one of 6 possible *two-port networks*.
- These networks are circuits that are based on one of 6 possible sets of *two-port equations*. These equations are simply different combinations of two equations that relate the variables  $V_1$ ,  $V_2$ ,  $I_1$ , and  $I_2$  to one another. The coefficients in these equations are referred to as *two-port parameters*.



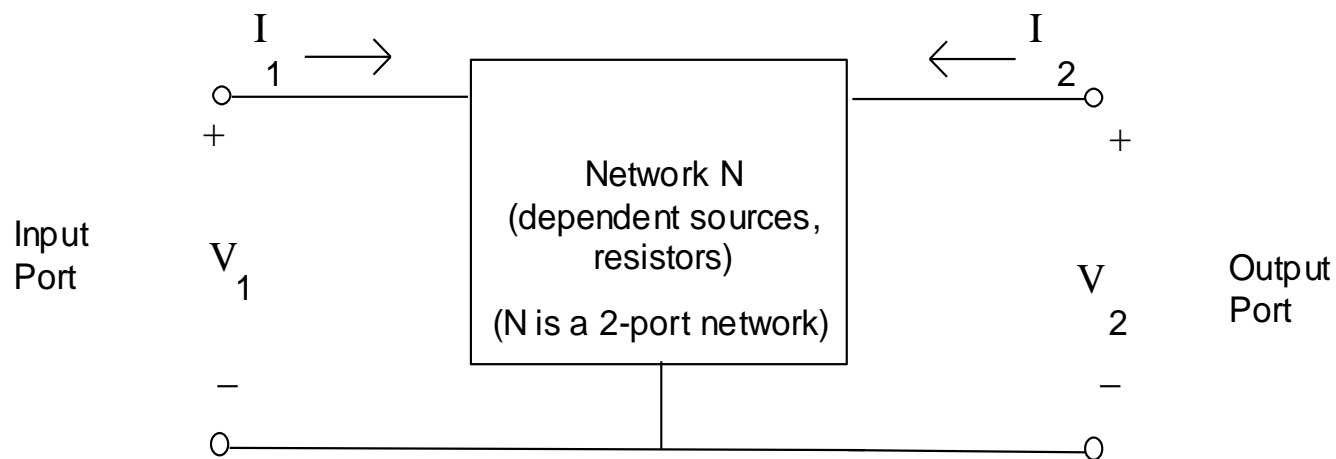Note that  $I_1$ ,  $I_2$ ,  $V_1$ , and  $V_2$  are labeled as shown by convention. Often there is a common negative terminal between the input and the output so the figure above could be redrawn as:




**Development of the h-parameter model:**

One possible circuit model could be developed by treating one of the two-port parameter equations as a KVL equation and the other as a KCL equation (illustrate). This results in the following circuit.

h - parameter equations :

$$V_1 = h_{11} \cdot I_1 + h_{12} \cdot V_2$$
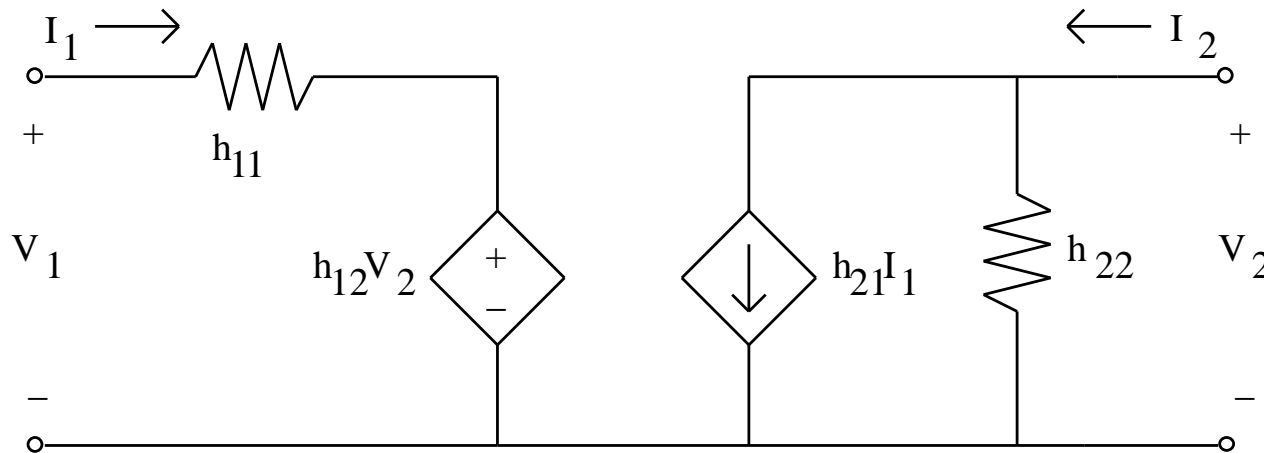
$$I_2 = h_{21} \cdot I_1 + h_{22} \cdot V_2$$



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$


**Development of the h-parameter model of BJT:**

For A BJT the equivalent h parameter model can be described by the following equations:

**h - parameter equations :**

$$V_1 = h_i \cdot I_1 + h_r \cdot V_2$$

$$I_2 = h_f \cdot I_1 + h_o \cdot V_2$$

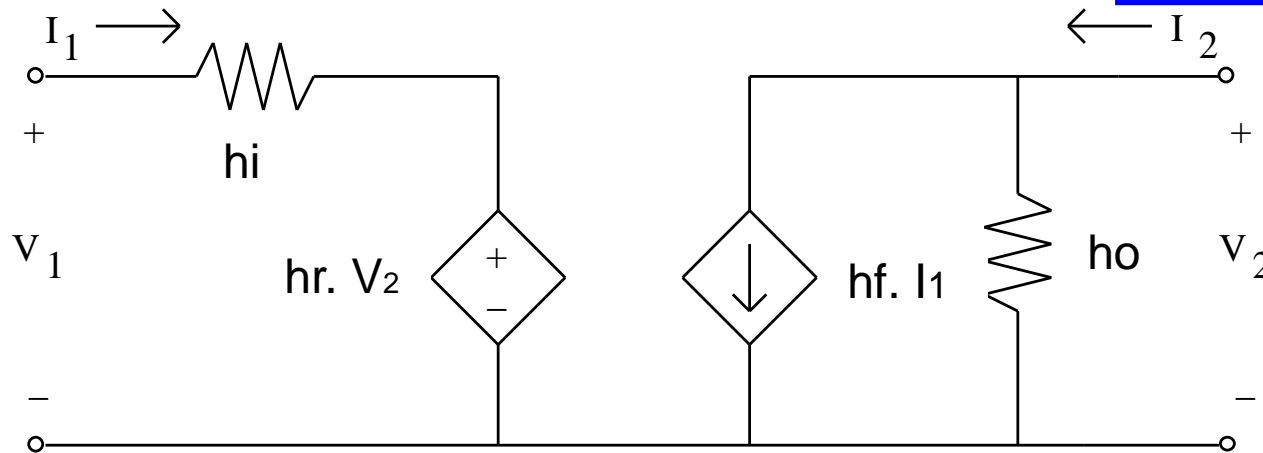

$$h_i = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$


$$h_r = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_f = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_o = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

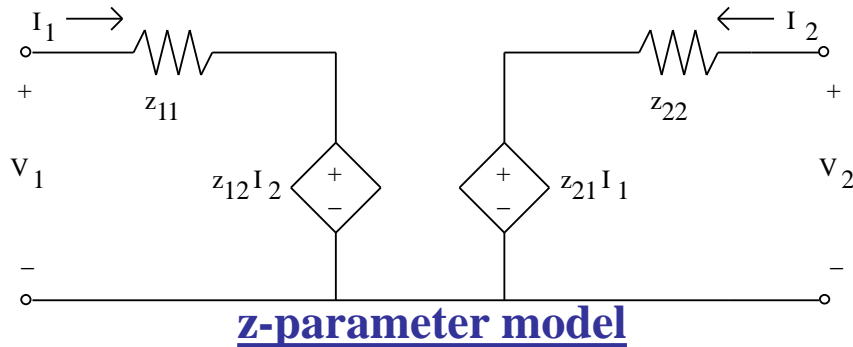**Summary:**


**Note:** This page is for information only



z - parameter equations :

$$V_1 = z_{11} \cdot I_1 + z_{12} \cdot I_2$$

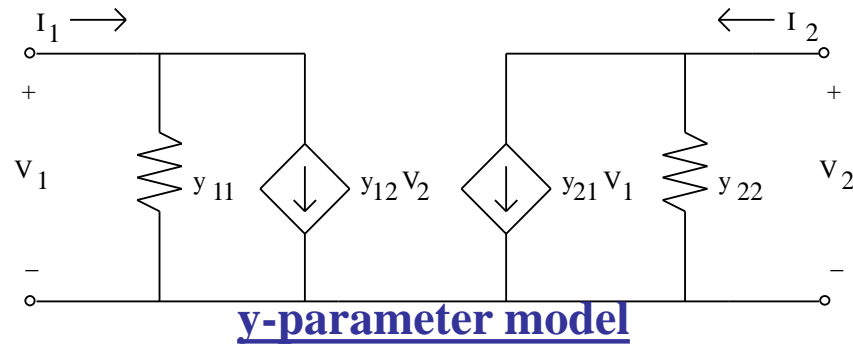
$$V_2 = z_{21} \cdot I_1 + z_{22} \cdot I_2$$



y - parameter equations :

$$I_1 = y_{11} \cdot V_1 + y_{12} \cdot V_2$$
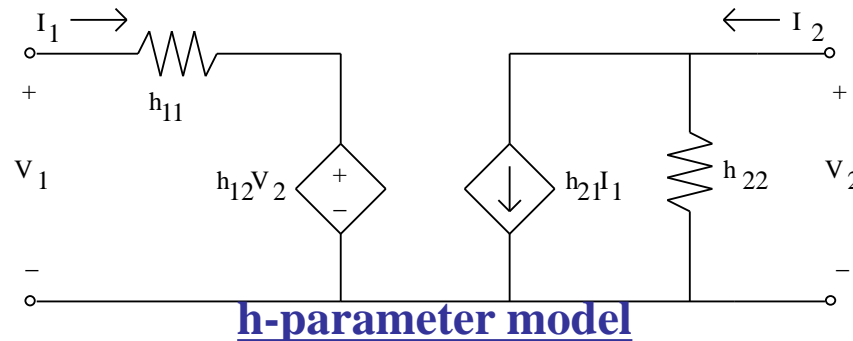
$$I_2 = y_{21} \cdot V_1 + y_{22} \cdot V_2$$



h - parameter equations :


$$V_1 = h_{11} \cdot I_1 + h_{12} \cdot V_2$$

$$I_2 = h_{21} \cdot I_1 + h_{22} \cdot V_2$$


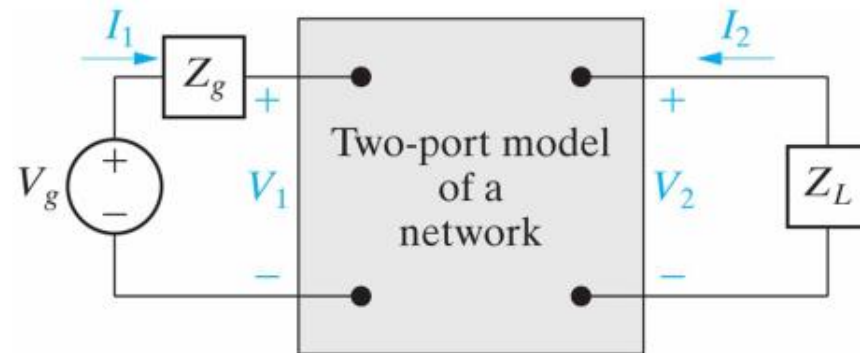
# BJT Configurations

- Common Emitter
- Common Base
- Common Collector



Terminated Two port network  
Includes source and load


# Common Emitter Configuration

(inverting configuration, provides voltage and current gain)


h - parameter equations :

$$V_{be} = h_{ie} \cdot I_b + h_{re} \cdot V_{ce}$$

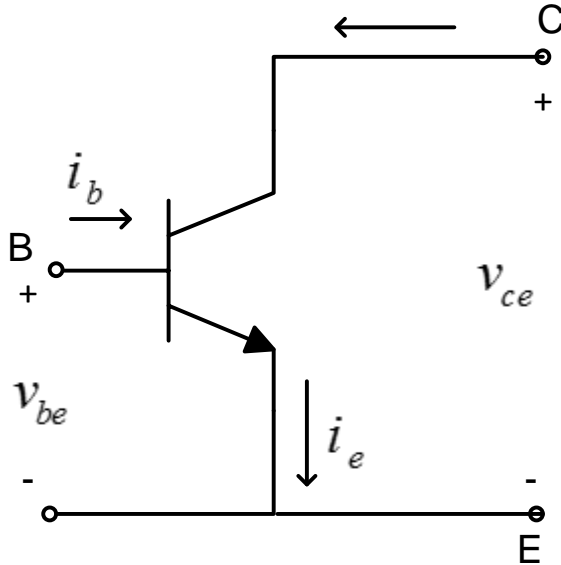
$$I_c = h_{fe} \cdot I_b + h_{oe} \cdot V_{ce}$$



Detailed Model

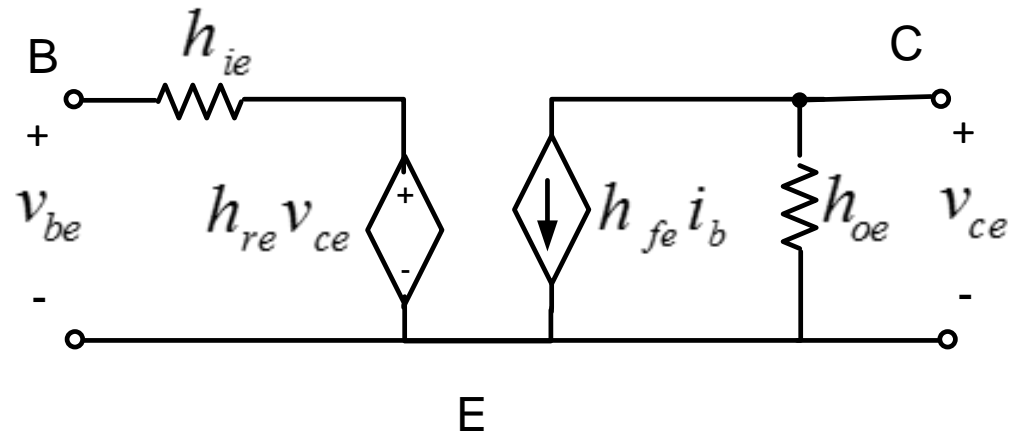

Simplified Model

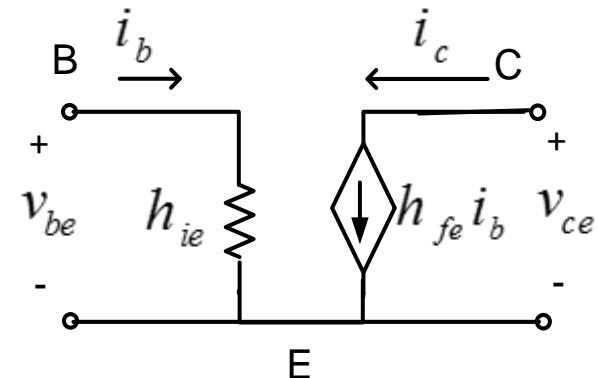

Typical Data sheet parameter values




$$h_{ie} \approx 1600 \Omega$$

$$h_{re} \approx 0.0002$$

$$h_{fe} \approx 80$$

$$h_{oe} \approx 20 \cdot 10^{-6} \text{ Siemens}$$
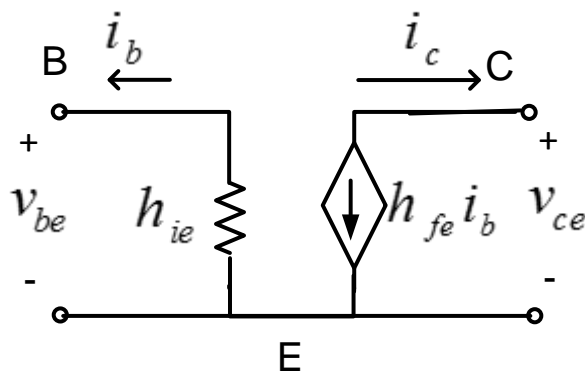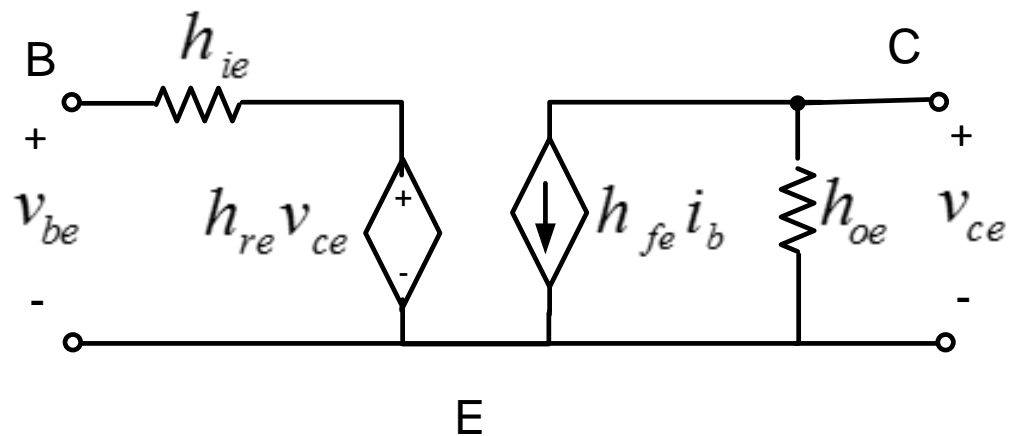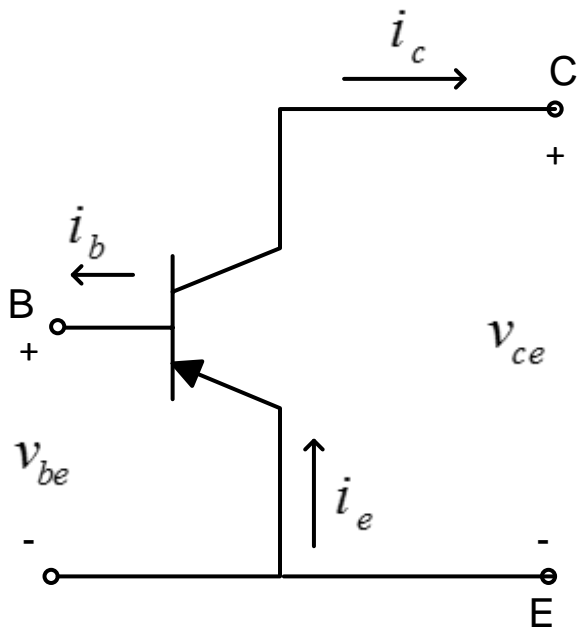
# Common Emitter and Common Collector Configuration



# Value of $h_{ie}$

Base Emitter is a pn junction similar to a diode  
 $h_{ie}$  is the dynamic resistance of the pn junction

In a diode:

$$r_d = \frac{V_T}{I_{DQ}} \Rightarrow$$

$$h_{ie} = \frac{V_T}{I_{BQ}} = \frac{V_T}{\frac{I_{CQ}}{h_{fe}}} = \frac{h_{fe} V_T}{I_{CQ}}$$

$I_{BQ}$  dc value of base current

$I_{CQ}$  dc value of collector current



$$h_{fe} = \beta$$

$$V_T = 25.69 \text{ mV @ } 25 \text{ }^\circ\text{C}$$

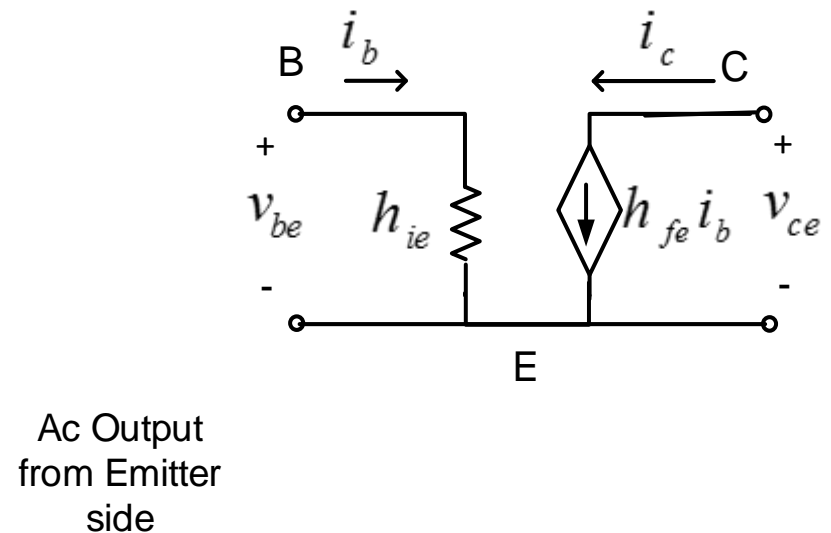
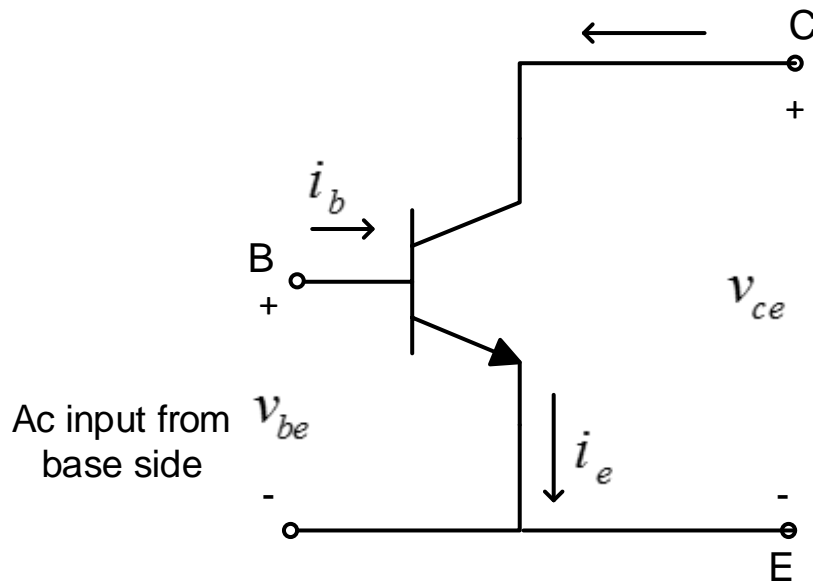
# Common Collector

provides current gain and no voltage gain)

Same Model of Common Emitter will be used due to the similarities between them and for simplicity



# Common-Base Configuration

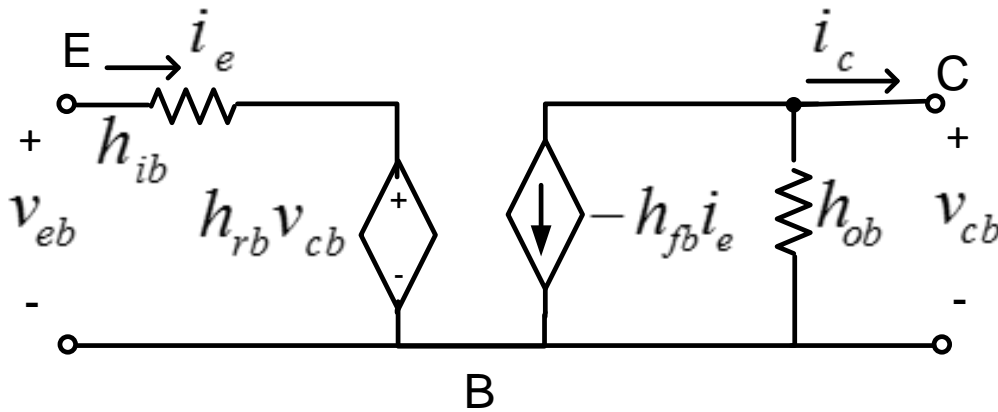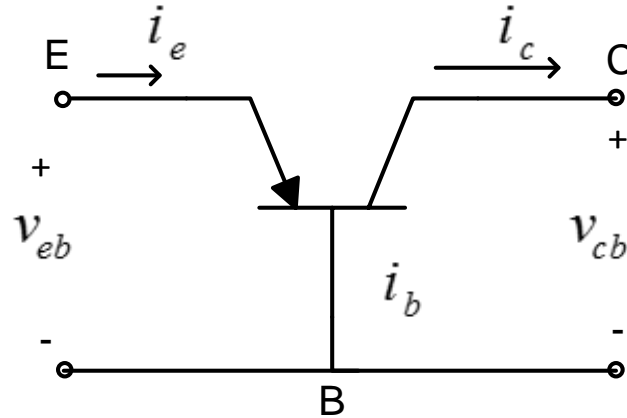

h - parameter equations :

$$V_{eb} = h_{ib} \cdot I_e + h_{rb} \cdot V_{cb}$$

$$I_c = h_{fb} \cdot I_e + h_{ob} \cdot V_{cb}$$

$$h_{ib} = \left. \frac{V_{EB}}{I_E} \right|_{V_{CB}=0}$$




$$h_{fb} = \alpha = \left. \frac{I_C}{I_E} \right|_{V_{CB}=0}$$

$$h_{rb} = \left. \frac{V_{EB}}{V_{CB}} \right|_{I_E=0}$$


$$h_{ob} = \left. \frac{I_C}{V_{CB}} \right|_{I_E=0}$$
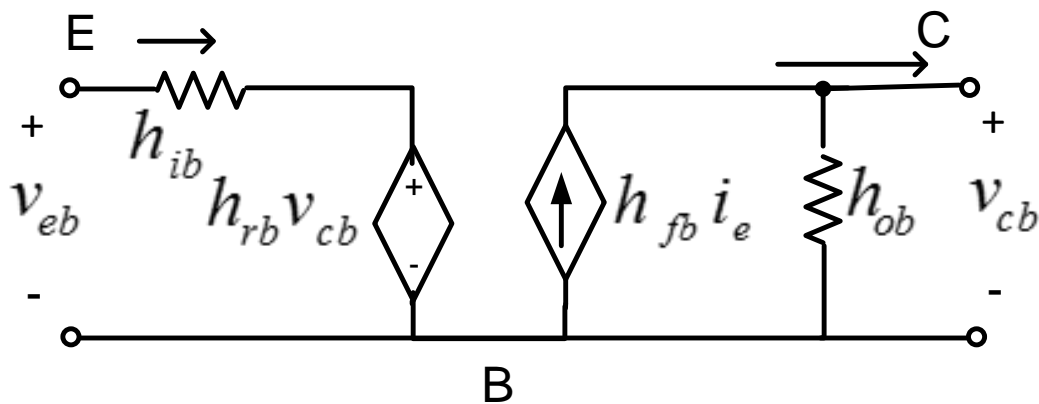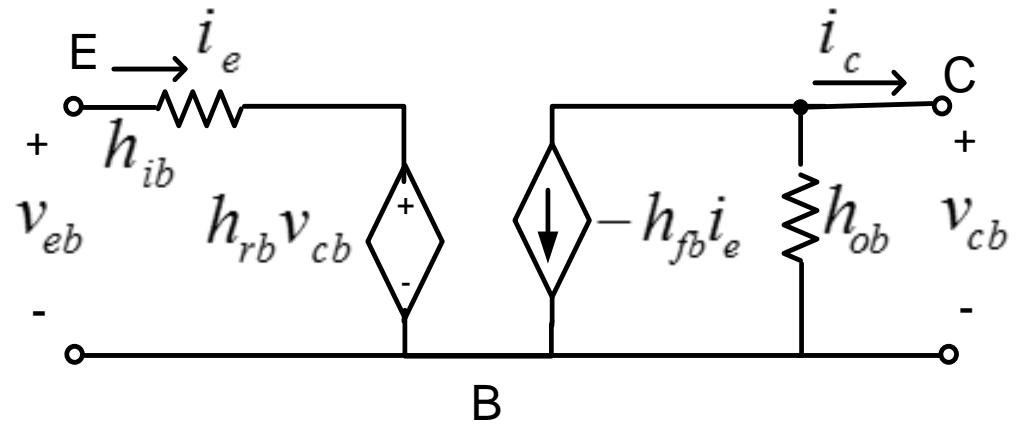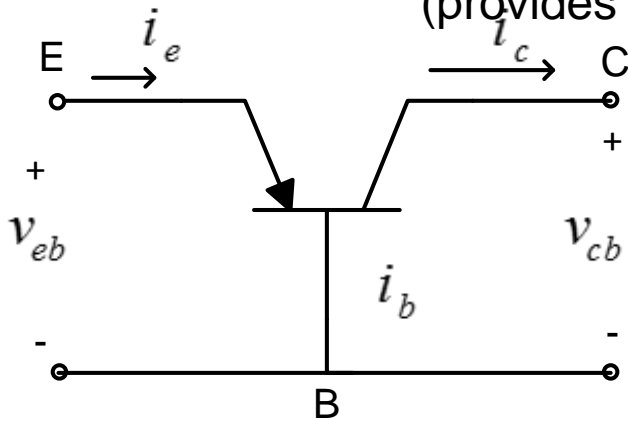
# Common-Base Configuration

(provides current gain and some voltage gain)



Simplified Equivalent Circuit

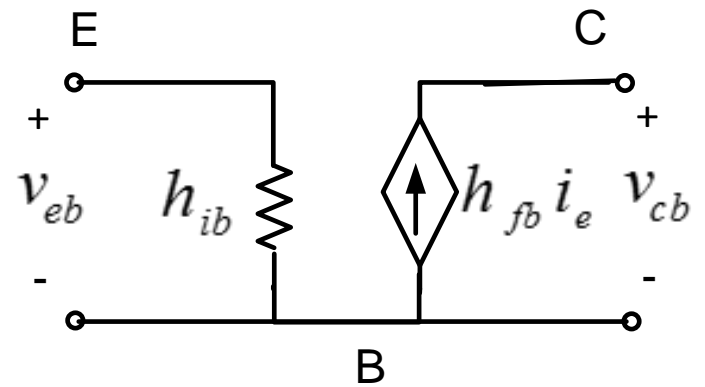

# Common-Base Configuration

$$h_{ib} = \frac{V_T}{I_{EQ}}$$


$$h_{fb} = \alpha$$

$$V_T = 25.69 \text{ mV @ } 25 \text{ }^\circ\text{C}$$

$$h_{ie} > h_{ib}$$




# BJT Amplifier Analysis Example

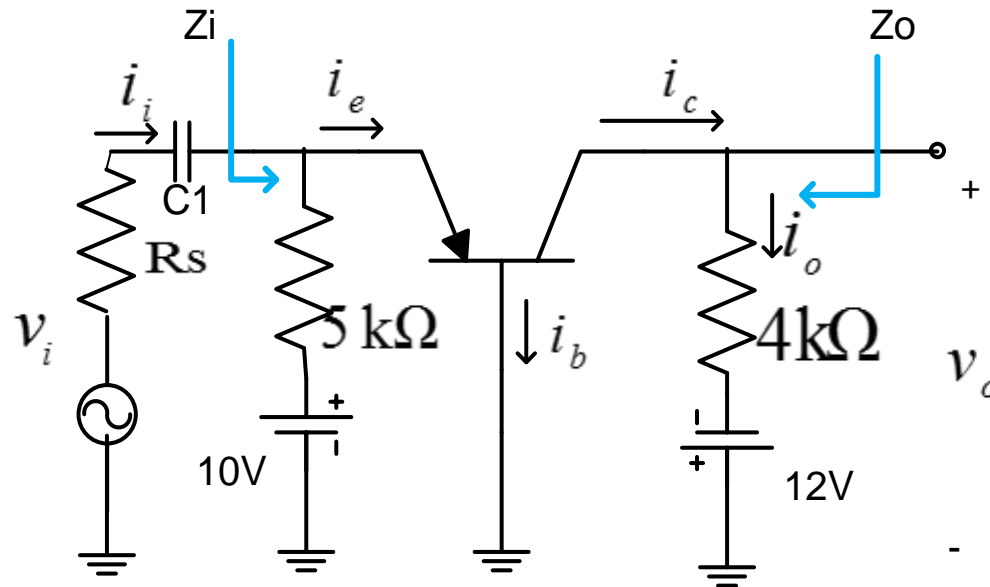

# BJT Amplifier Analysis

When Analyzing Amplifier Circuits, we usually want to find some or all of the following quantities:

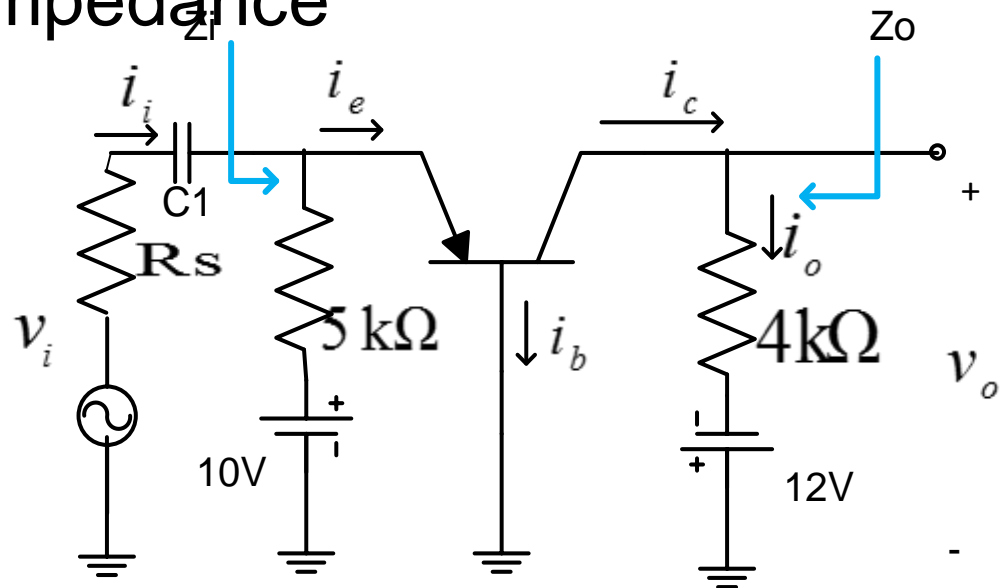- 1)  $A_v = V_o/V_i$ , small signal voltage gain
- 2)  $A_i = i_o/i_i$ , small signal current gain
- 3)  $Z_i$  Input Impedance
- 4)  $Z_o$  Output Impedance




# BJT Amplifier Analysis

Solution: (with  $R_s=0$ )

We draw the ac small signal equivalent circuit

Capacitors  $\implies$  replaced by short circuit

DC sources are killed ,

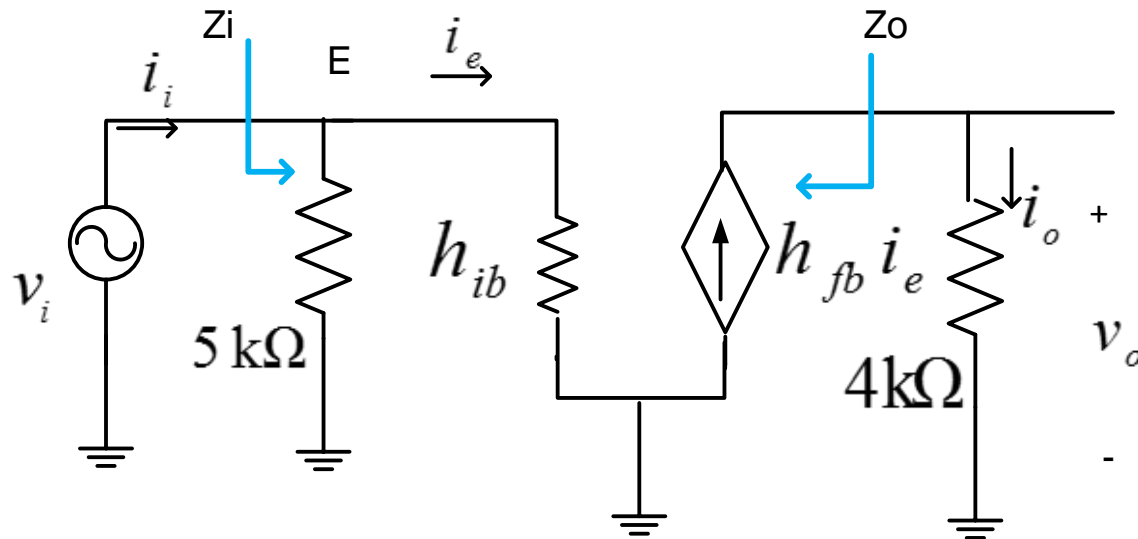

$$h_{ib} = \frac{V_T}{I_{EQ}}$$


$$h_{fb} = \alpha \cong 1$$

$I_{EQ}$  must be calculated from DC analysis

# DC Analysis

DC Equivalent Circuit:

- Cap ==> open
- Kill ac sources ==>

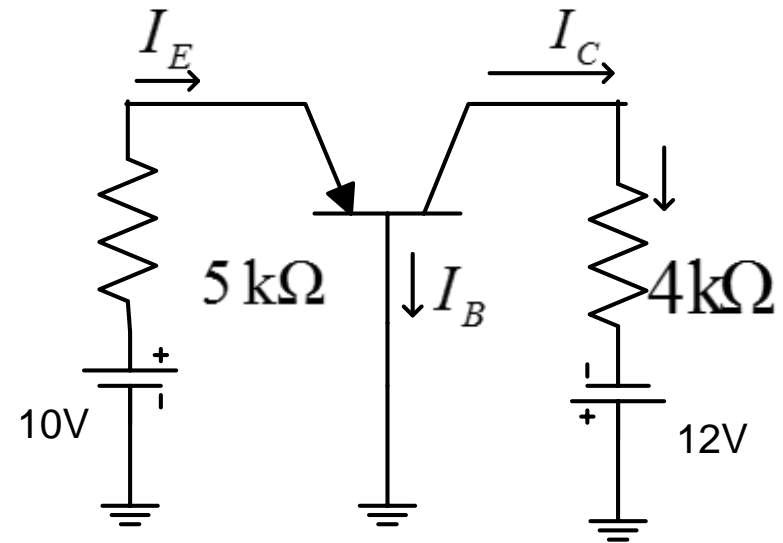

$$10 = 5 \text{ k}\Omega \cdot I_{EQ} + V_{EB}$$

$$I_{EQ} = \frac{10 - 0.7}{5 \text{ k}\Omega} = 1.86 \text{ mA}$$

$$h_{ib} = \frac{V_T}{I_{EQ}} = \frac{25.69 \text{ mV}}{1.86 \text{ mA}} = 13.98 \Omega$$


# Ac ss equivalent circuit

$$1) A_v = \frac{v_o}{v_i}$$

$$v_o = i_o \cdot 4 \text{ k}\Omega$$

$$i_o = h_{fb} \cdot i_e$$

$$i_e = \frac{v_i}{h_{ib}}$$

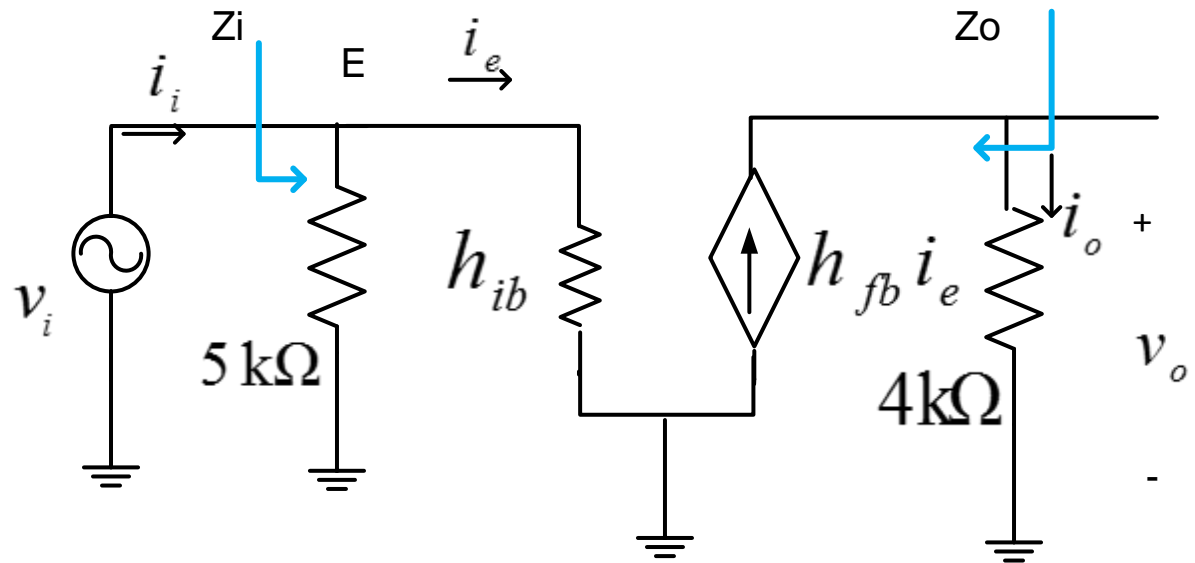

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{i_o} \cdot \frac{i_o}{i_e} \cdot \frac{i_e}{v_i}$$



$$A_v = (4 \text{ k}\Omega) \cdot (h_{fb}) \cdot \left( \frac{1}{h_{ib}} \right)$$


$$= (4 \text{ k}\Omega) \cdot (1) \cdot \left( \frac{1}{13.98} \right) = 286 > 1$$

# Current Gain $A_i$

$$2) A_i = \frac{i_o}{i_i}$$

$$i_o = h_{fb} \cdot i_e$$
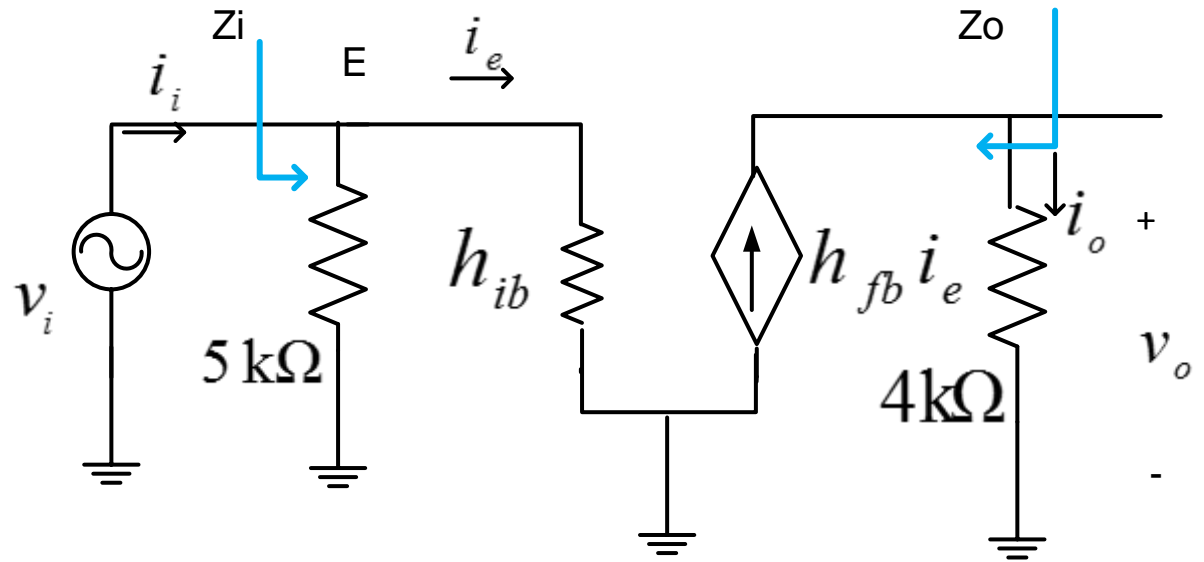
$$i_e = i_i \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + h_{ib}}$$




$$\Rightarrow A_i = \frac{i_o}{i_i} = \frac{i_o}{i_e} \cdot \frac{i_e}{i_i}$$

$$\Rightarrow A_i = (h_{fb}) \left( \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + h_{ib}} \right)$$

$$= (1) \left( \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + 13.98} \right) < 1$$

# Zi & Zo

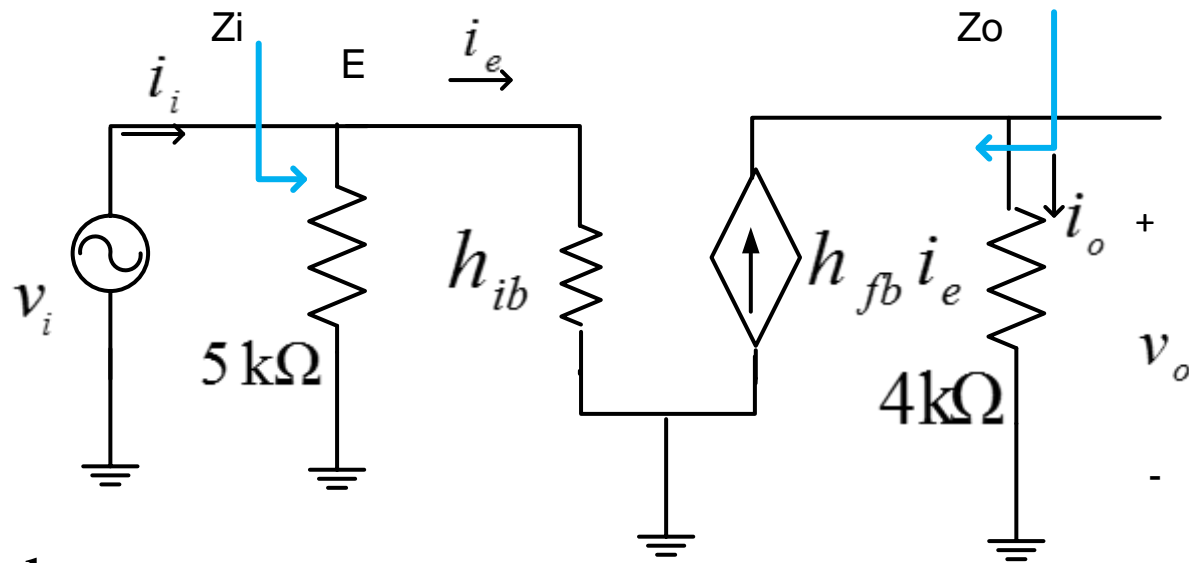

## 3) Input Impedance

$$Z_i = (h_{ib} // 5\text{ k}\Omega) = \left( \frac{h_{ib} \cdot 5\text{ k}\Omega}{5\text{ k}\Omega + h_{ib}} \right)$$


## 4) Output Impedance

$$Z_o \Big|_{\text{all independent sources killed (i.e. } v_i=0 \text{ or short)}} = 4\text{ k}\Omega$$

# With Presence of $R_s$

with  $R_s$

$$i_i = \frac{v_i}{Z_i + R_s}$$

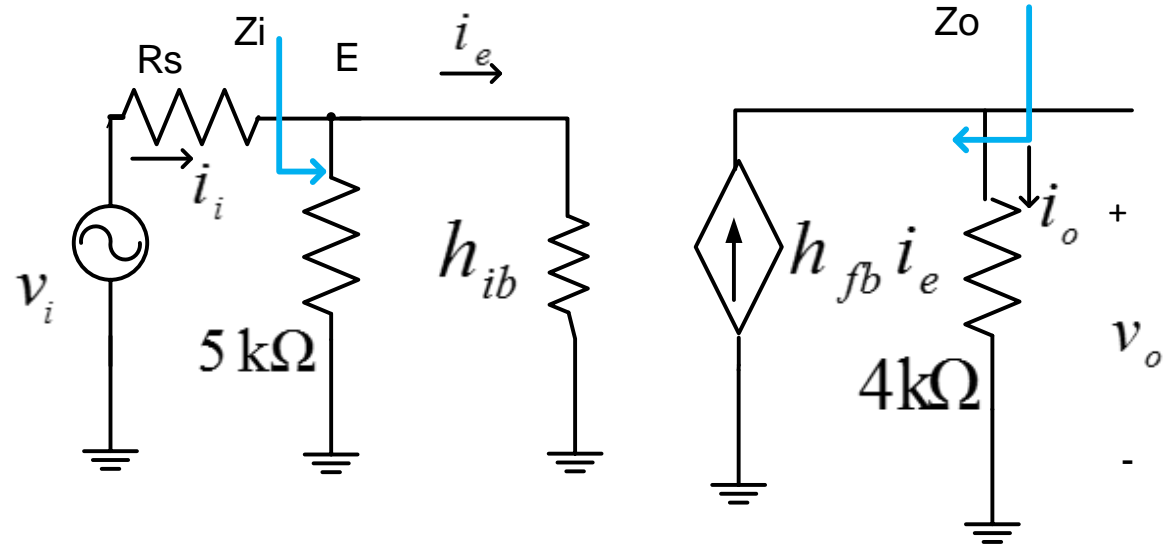

For  $R_s = 50\ \Omega$

$$A_v = 62.5$$

For  $R_s = 10\ \text{k}\Omega$

$$A_v = 0.4$$



# Example: Common Emitter (CE)


1) From DC Analysis,  
we find Q - point and value of


$$h_{ie} = \frac{V_T}{I_{BQ}}$$

Thevenin's equivalent circuit  
as seen from the base

$$V_{TH} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 50 \text{ k}\Omega} \cdot 24 \text{ V} = 4 \text{ V}$$
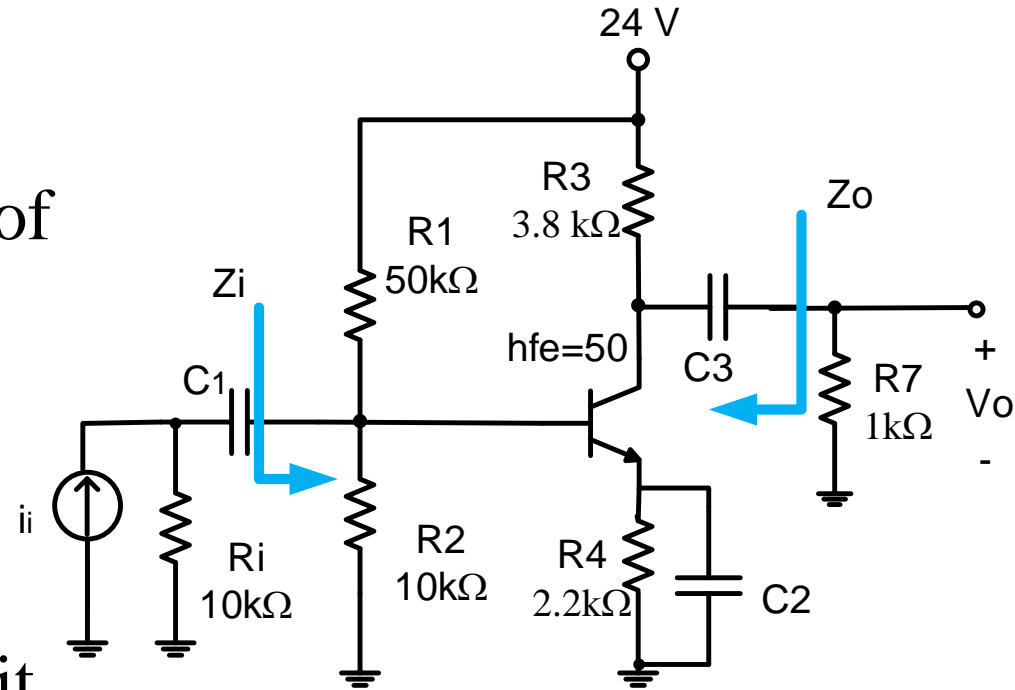
$$R_{TH} = 10 \text{ k}\Omega // 50 \text{ k}\Omega = 8.33 \text{ k}\Omega$$



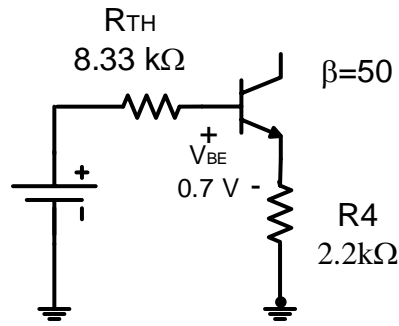


$$4 = 8.33 \text{ k}\Omega \cdot I_B + V_{BE} + 2.2 \text{ k}\Omega \cdot I_E$$

But,  $I_E = (1 + \beta)I_B$

$$\text{Solve for } I_E = \frac{4 - 0.7}{\frac{8.33 \text{ k}\Omega}{(1 + 50)} + 2.2 \text{ k}\Omega} = 1.4 \text{ mA}$$

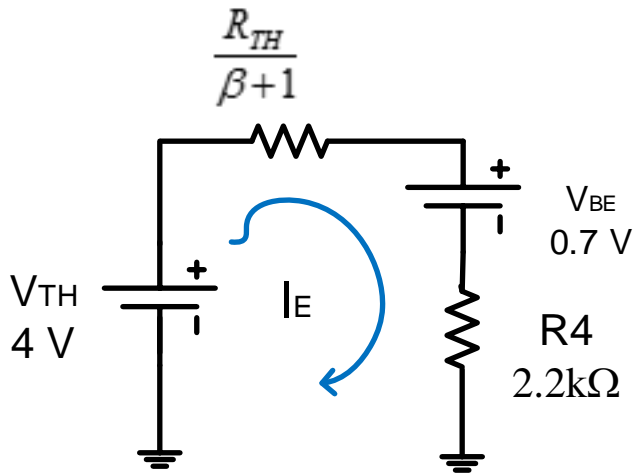
$$h_{ie} = \frac{V_T}{I_{BQ}} = \frac{25.69 \text{ mV}}{\frac{1.4 \text{ mA}}{51}} = 928 \Omega$$




Here we have base reflected to emitter

$$I_B \Rightarrow I_E = (\beta + 1)I_B$$
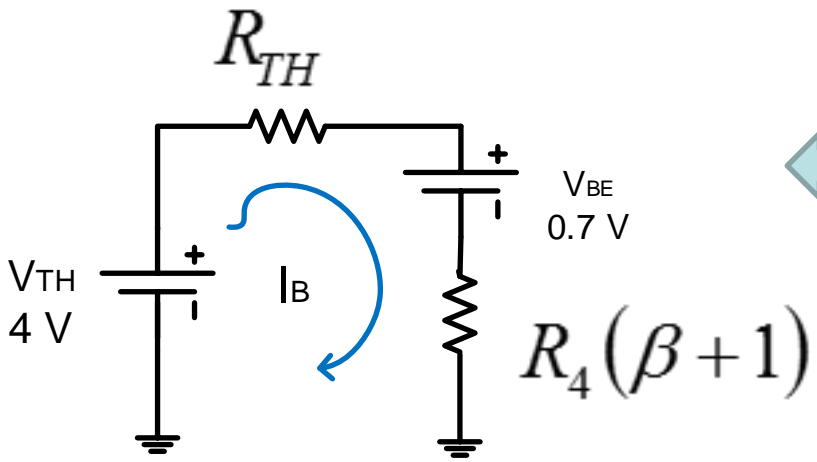
$$R_B \Rightarrow \frac{R_B}{\beta + 1}$$




Here we have emitter reflected to base

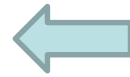

$$I_E \Rightarrow I_B = \frac{I_E}{(\beta + 1)}$$

$$R_E \Rightarrow R_E(\beta + 1)$$

# AC small signal Equivalent Circuit

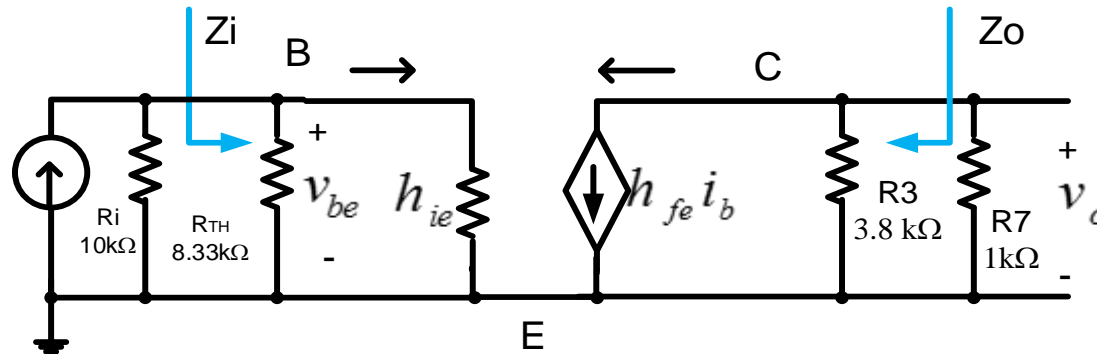


$$1) A_V = \frac{v_o}{v_i}$$

$$A_V = \frac{v_o}{v_i} = \frac{v_o}{i_b} \cdot \frac{i_b}{v_i}$$

$$v_o = -h_{fe} i_b \cdot (R_3 // R_7) \quad \Rightarrow \quad = -h_{fe} \cdot (R_3 // R_7) \cdot \left( \frac{1}{h_{ie}} \right)$$

$$i_b = \frac{v_i}{h_{ie}} \quad = -50 \cdot (3.8 \text{ k}\Omega // 1 \text{ k}\Omega) \cdot \left( \frac{1}{928 \Omega} \right) = -42.7$$

# AC small signal Equivalent Circuit

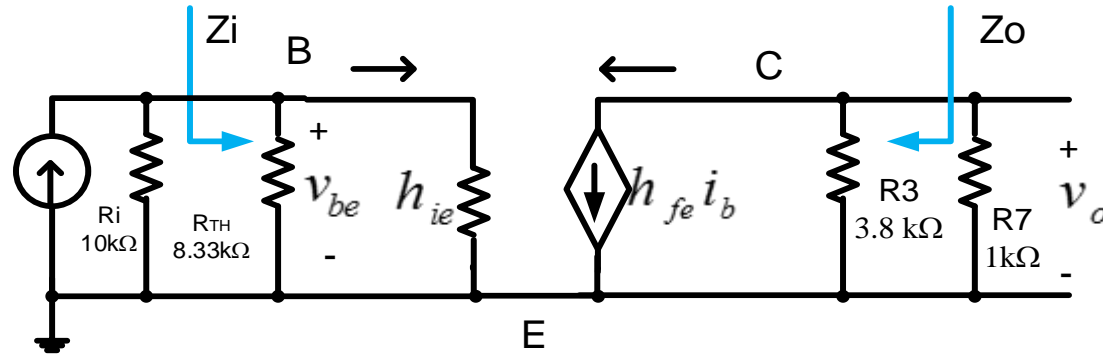

$$2) Z_I = R_{TH} // h_{ie}$$


$$= 8.33 \text{ k}\Omega // 928 \Omega$$

only elements to the right of arrow are considered  
according to the given direction of the arrow

$$3) Z_o \Big|_{\text{all independent sources killed (i.e. } v_i=0 \text{ or short)}} = 3.8 \text{ k}\Omega$$

here  $h_{fe} \cdot i_b = 0$  since  $i_b = 0$  ( $v_i = 0$  - killed)

# AC small signal Equivalent Circuit

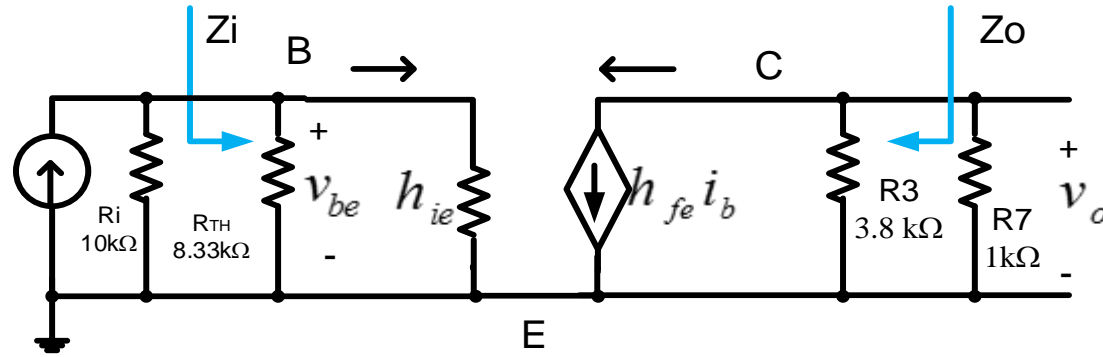


$$4) A_i = \frac{i_o}{i_i}$$

$$i_o = -h_{fe} i_b \left( \frac{R_3}{R_3 + R_7} \right)$$


$$i_b = (i_i) \left( \frac{R_i // R_{TH}}{(R_i // R_{TH}) + h_{ie}} \right)$$

$$A_i = \frac{i_o}{i_i} = \frac{i_o}{i_b} \cdot \frac{i_b}{i_i} = -h_{fe} \left( \frac{R_3}{R_3 + R_7} \right) \cdot \left( \frac{R_i // R_{TH}}{(R_i // R_{TH}) + h_{ie}} \right) = -33$$

# Impedance Reflection

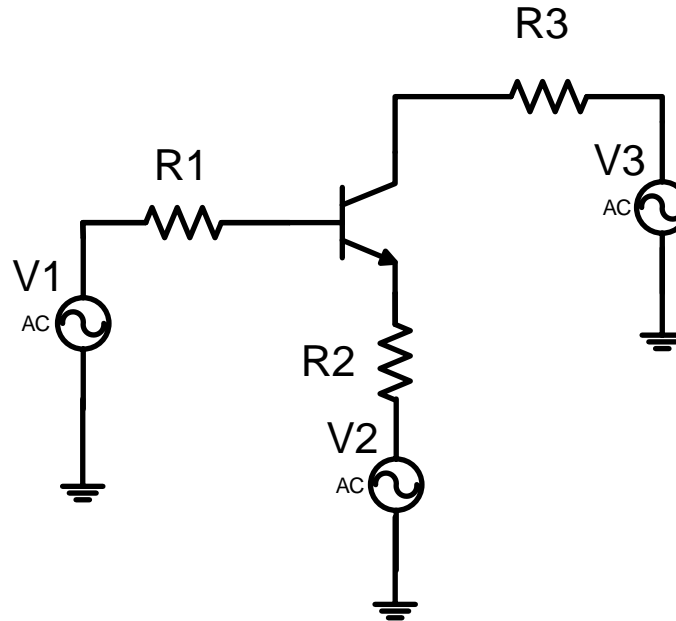

ac ss equivalent circuit

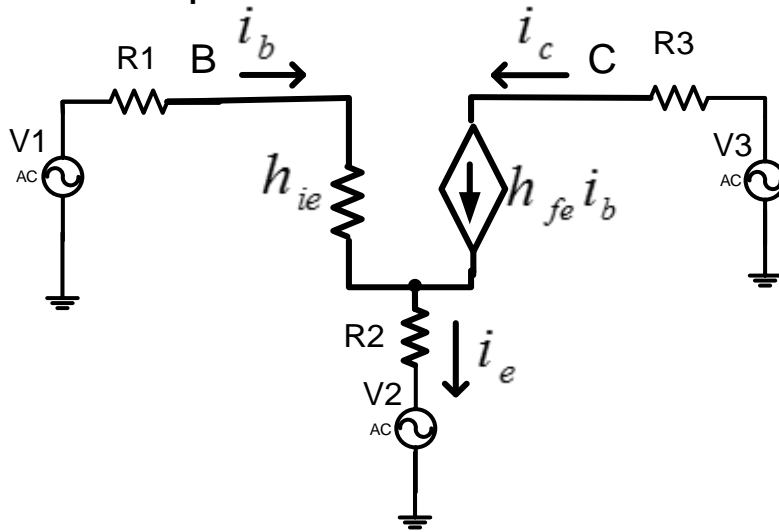


$$v_1 = R_1 \cdot i_b + h_{ie} \cdot i_b + R_2 \cdot i_e + v_2$$

$$\text{but } i_e = (\beta + 1)i_b$$

$$v_1 = R_1 \cdot i_b + h_{ie} \cdot i_b + R_2 \cdot (\beta + 1)i_b + v_2$$

$$i_b = \frac{v_1 - v_2}{R_1 + R_2 \cdot (\beta + 1)} \Leftarrow \text{base loop}$$

equivalent circuit equation

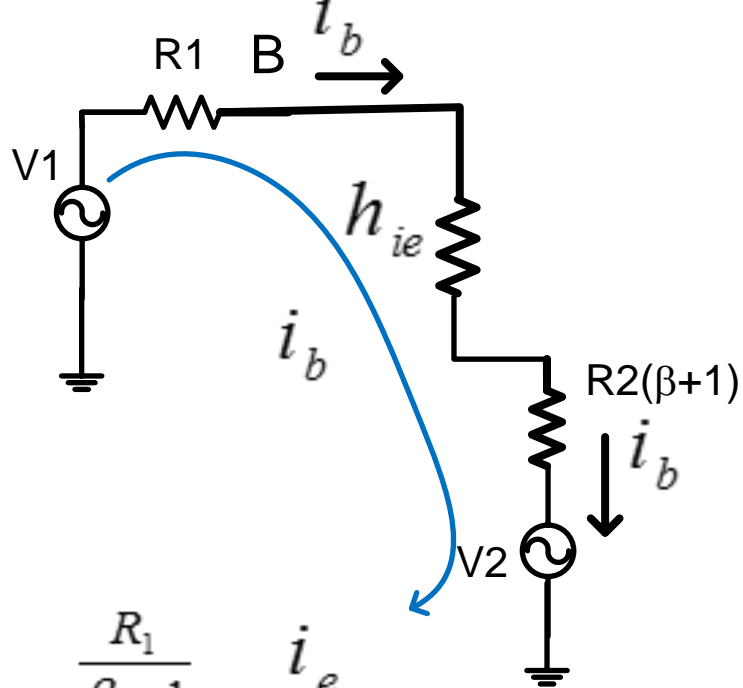


$$i_b = \frac{v_1 - v_2}{R_1 + h_{ie} + R_2(\beta+1)} \leftarrow \text{base loop}$$

equivalent circuit equation




Instead of  $i_b$  use  $i_e$

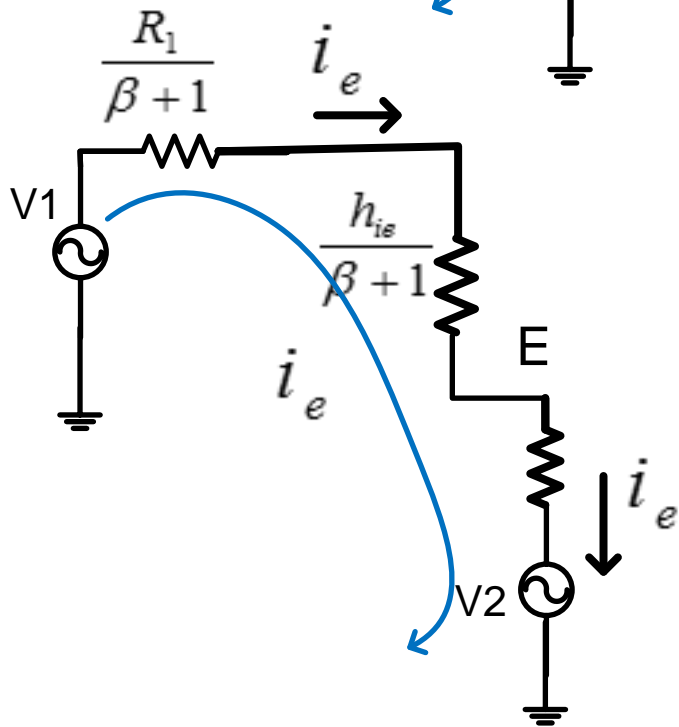

$$i_e = \frac{v_1 - v_2}{\frac{R_1}{(\beta+1)} + \frac{h_{ie}}{(\beta+1)} + R_2} \leftarrow \text{Emitter loop}$$

equivalent circuit equation




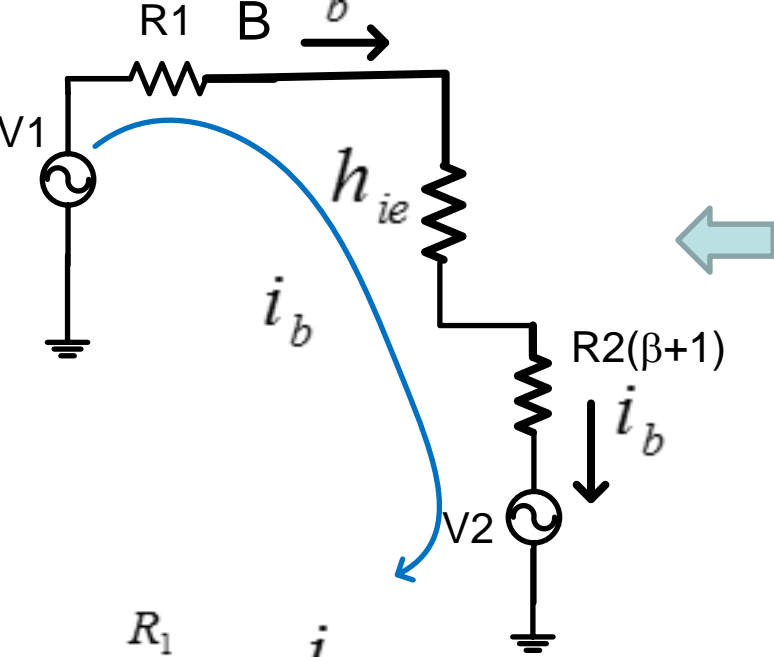
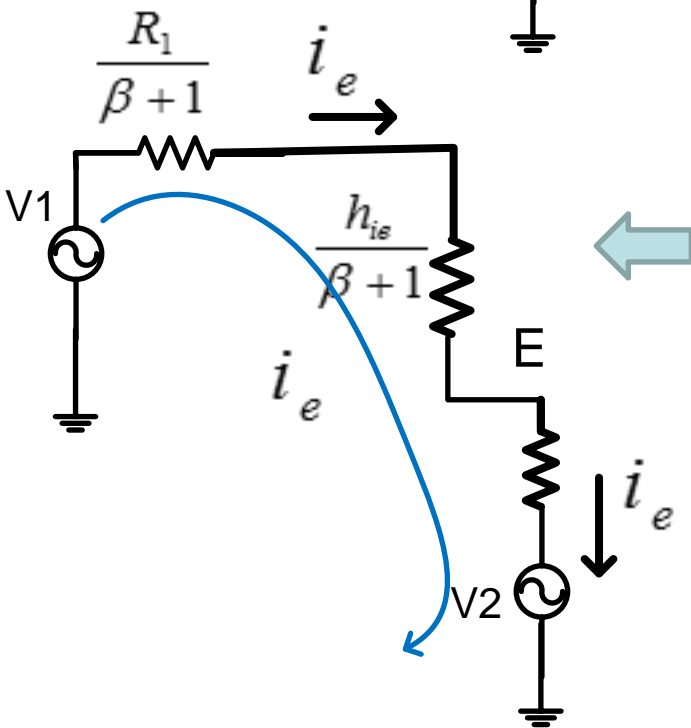
### base equivalent circuit

(reflection from emitter to base)

Here we must change  $i_e$  to  $i_b$  which requires division by  $(h_{fe} + 1)$ , but voltage must remain the same and thus the resistance must be multiplied by the same factor  $(h_{fe} + 1)$




### Emitter equivalent circuit

(reflection from base to emitter)


Here we must change  $i_b$  to  $i_e$  which requires multiplication by  $(h_{fe} + 1)$ , but voltage must remain the same and thus the resistance must be divided by the same factor  $(h_{fe} + 1)$

# Collector Equivalent Circuit

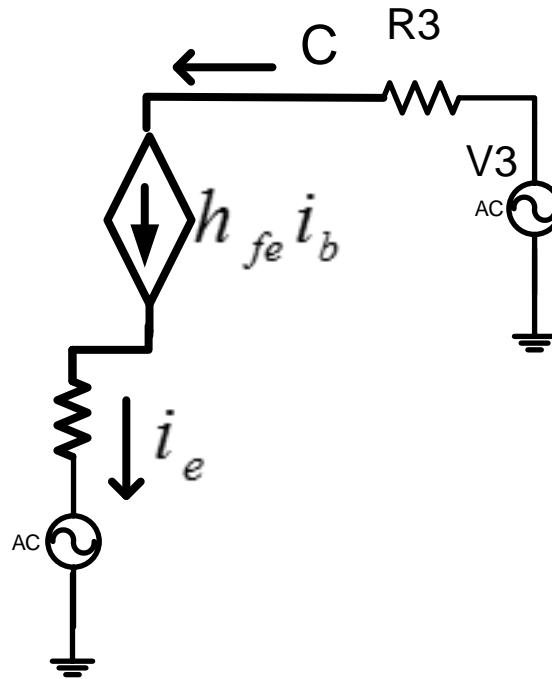

Note: there is no reflection from emitter to collector or vice versa since the  $i_e$  and  $i_c$  are almost the same

# Common Collector Amplifier

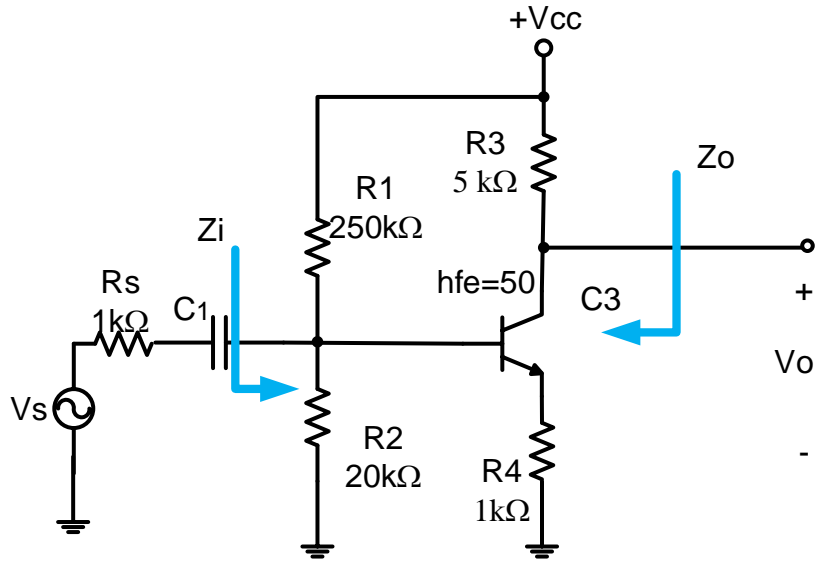

AC small signal Equivalent Circuit

