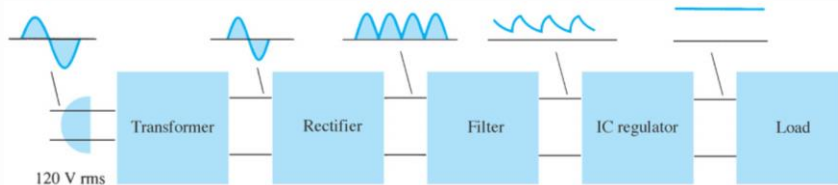


Voltage Regulator

ENEE236 – Analog Electronics
Instructor
Nasser Ismail

Introduction



- **Power supply**: a group of circuits that convert the **standard ac voltage** (220 V, 50 Hz or 110 V, 60 Hz) provided by the wall outlet to **constant dc voltage**
- **Transformer**: a device that step up or step down the **ac voltage** provided by the wall outlet to a desired amplitude through the *action* of a *magnetic field*

Introduction

- **Rectifier:** a diode circuits that converts the **ac input voltage** to a **pulsating dc voltage**
- The pulsating dc voltage is **only suitable** to be used as a battery charger, but **not good enough** to be used as a dc power supply in a radio, stereo system, computer and so on.

Introduction

- There are two basic types of rectifier circuits:
 - Half-wave rectifier
 - Full-wave rectifier - Center-tapped & Bridge full-wave rectifier
- In summary, a full-wave rectified signal has **less ripple** than a half-wave rectified signal and is thus better to apply to a filter.


Introduction

- Filter:** a circuit used to reduce the fluctuation in the rectified output voltage or ripple. This provides a **steadier** dc voltage.
- Regulator:** a circuit used to produces a **constant** dc output voltage by reducing the ripple to negligible amount. One part of power supply.

Voltage Regulators

Regulator - Zener diode regulator

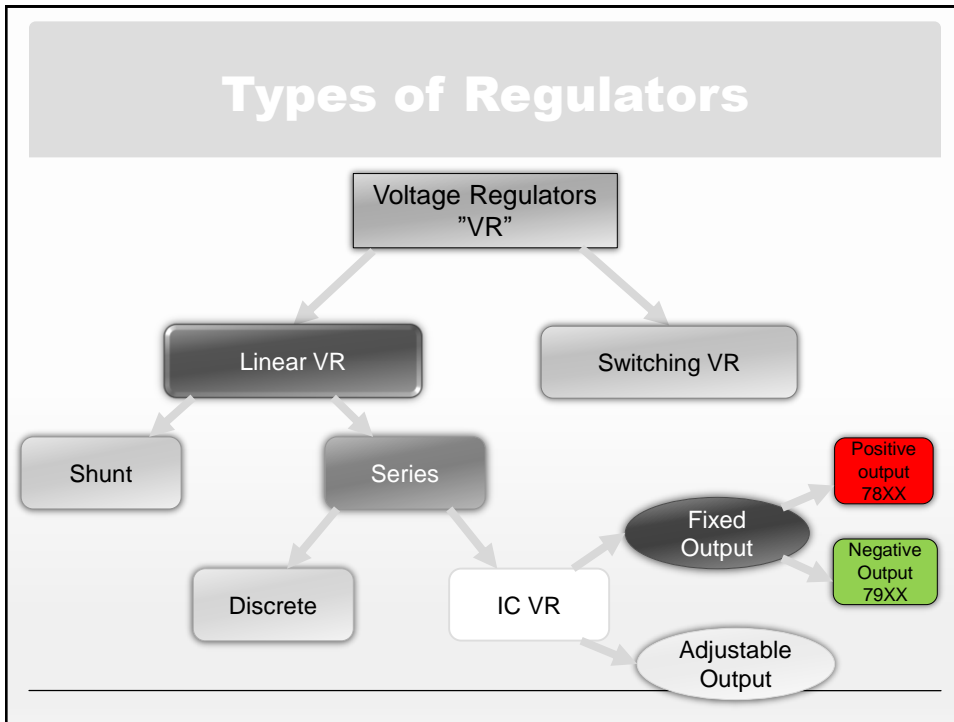- For low current power supplies - a simple voltage regulator can be made with a resistor and a zener diode connected in reverse.
- Zener diodes are rated by their breakdown voltage V_z and maximum power P_z (typically 400mW or 1.3W)





Types of Regulator

- Fundamental classes of voltage regulators are **linear regulators** and **switching regulators**.
- Two basic types of linear regulator are the **series regulator** and the **shunt regulator** .
- The series regulator is connected in **series** with the load and the shunt regulator is connected in **parallel** with the load.

(a)

(b)

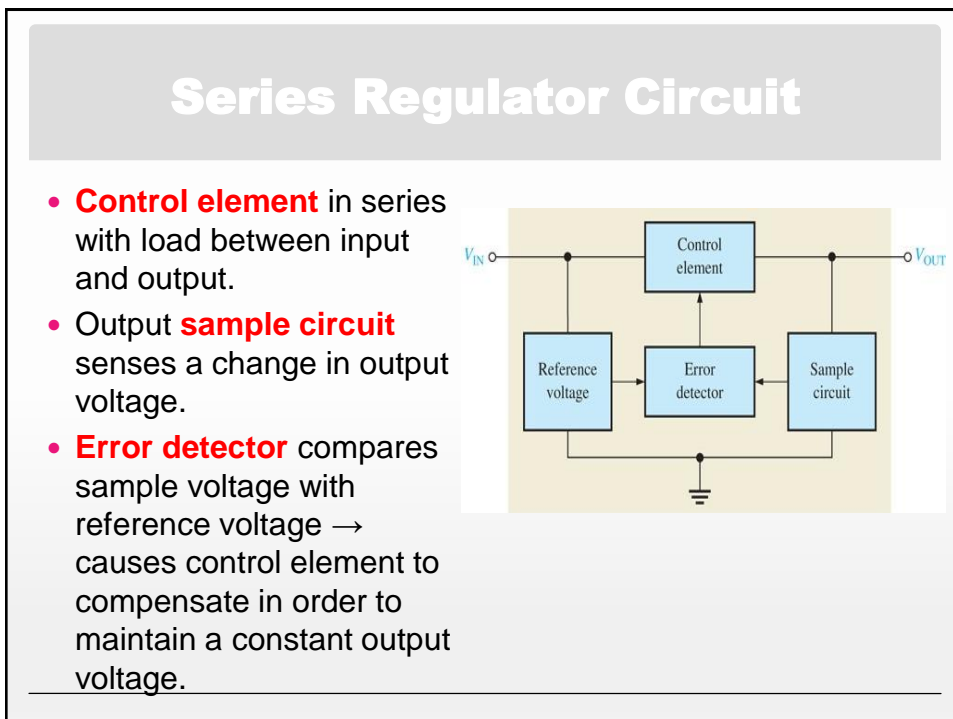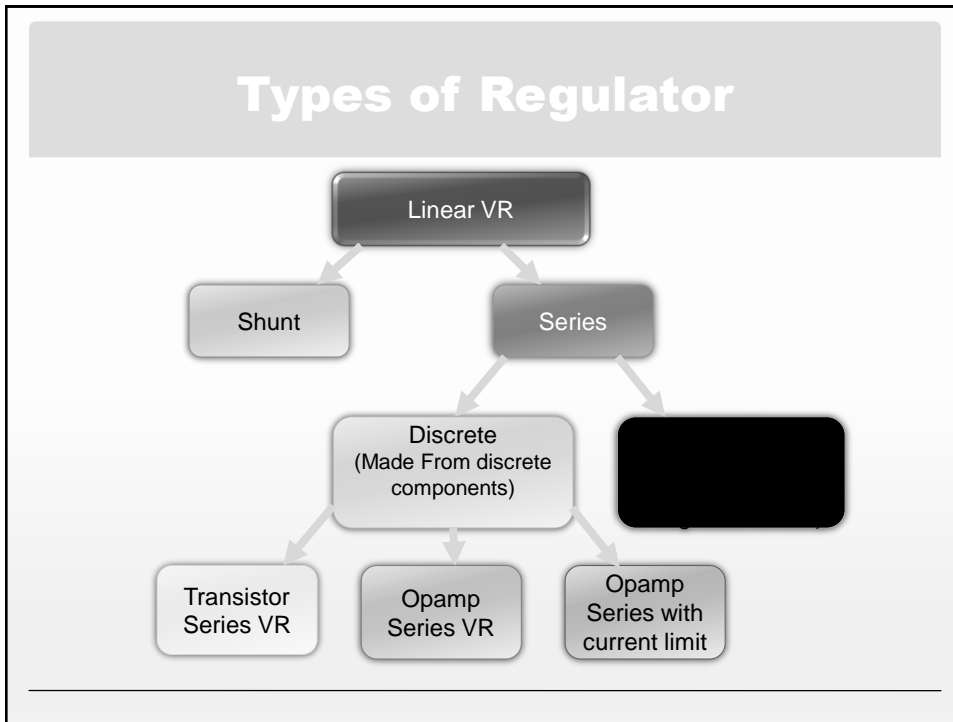

Transistor Series VR

The Transistor behaves like a simple variable resistor whose resistance is determined by the operating conditions

$$V_o = \frac{R_L}{R_L + R_T} V_{IN}$$

Ratio of $\frac{R_L}{R_T}$ must remain constant to keep V_o constant assuming V_{IN} is constant

Transistor Series VR

$V_o + V_{be} = V_Z$

$V_o = V_Z - V_{be}$

$V_{be} = V_Z - V_o$


$\Leftarrow V_{be}$ is the control signal

remember $I_C = I_S \left(e^{\frac{V_{be}}{V_T}} - 1 \right)$


If $V_o \downarrow$, $(V_{be} = V_Z - V_o) \uparrow$,
 $I_C \uparrow$, $R_T \downarrow$, $V_o \uparrow$

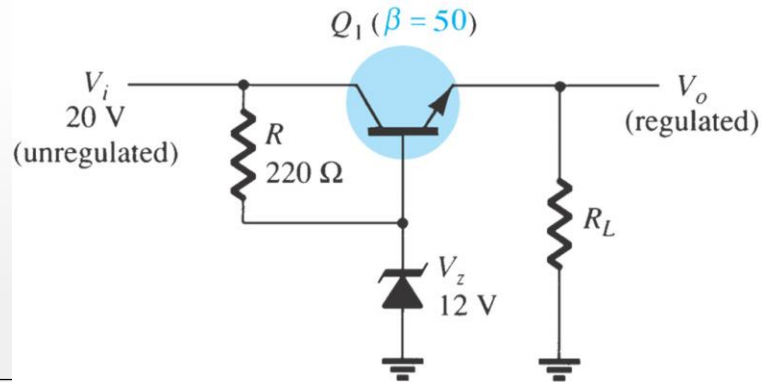Example

- Calculate the output voltage and Zener current for $R_L=1k\Omega$.
(Solution: $V_o=V_z-V_{be}=12-0.7=11.3\text{ V}$;
 $I_z\approx(20-12)/220=36\text{ mA}$)




Opamp Series VR

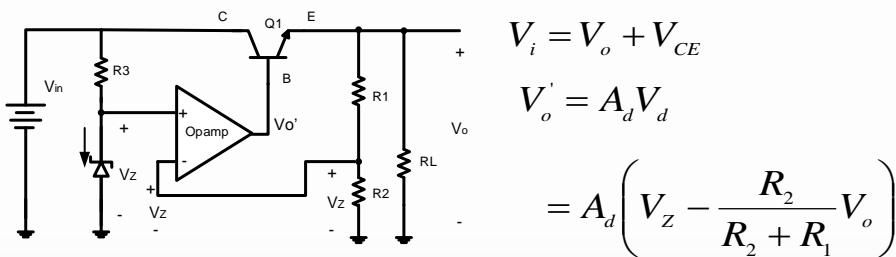

If $V_o \downarrow, V_o' \uparrow, V_{be} \uparrow, I_E \uparrow, V_o \uparrow$

Opamp Series VR

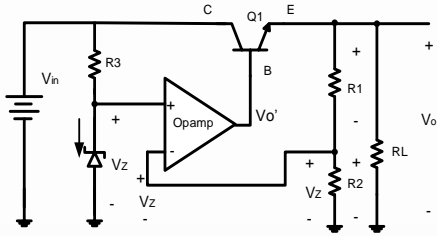

Resistors R_1, R_2 are for sampling of V_o

(the current through these resistors must be small)

$$V_o = V_{R1} + V_{R2}$$

$$I_{R1} = I_{R2} = I$$

$$V_{R2} = V_Z$$

$$I = \frac{V_Z}{R_2}$$

$$V_Z = V_o \frac{R_2}{R_1 + R_2}$$

$$V_o = V_Z \left(1 + \frac{R_1}{R_2} \right)$$

Summary of Op-Amp Series VR


- The resistor R_1 and R_2 sense a change in the output voltage and provide a feedback voltage.
- The error detector compares the feedback voltage with a Zener diode reference voltage.
- The resulting difference voltage causes the transistor Q_1 to control the conduction to compensate the variation of the output voltage.
- The output voltage will be maintained at a constant value of:

$$V_o = \left(1 + \frac{R_1}{R_2} \right) V_Z$$

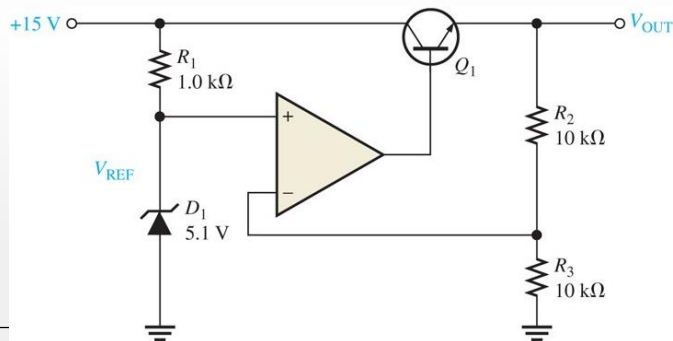Example

- Determine the output voltage for the regulator below.


$$V_o = \left(1 + \frac{R_2}{R_3}\right) V_Z \quad \Rightarrow \quad V_o = \left(1 + \frac{10k}{10k}\right) 5.1 = 10.2 \text{ V}$$



Opamp Series VR with current limit

Current Limiting Circuit

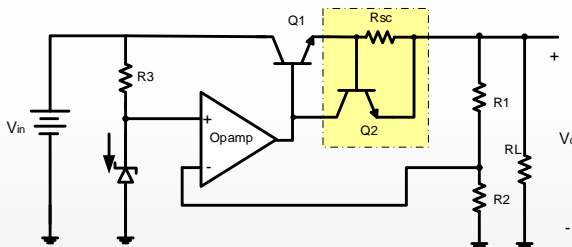In order to protect the transistor from damage when a very high current passes through it due to a short circuit or excessive current demand at the load



1) In normal operation Q2 is off since $V_{be2} = V_{Rsc} < 0.7 \text{ V}$

$$2) R_{SC} = \frac{V_{be}}{I_{L(Max)}} = \frac{0.7 \text{ V}}{I_{L(Max)}}$$

Opamp Series with current limit

3) When $I > I_{L(Max)}$, Q2 conducts since $V_{be2} = V_{Rsc} \cong 0.7 V$

4) Some of I_{B1} is diverted through Q2 (I_{C2})
 I_{B1} is reduced so that I_L is limited to a maximum value
 calculated as : $I_{L(Max)} = \frac{V_{be}}{R_{SC}} = \frac{0.7 V}{R_{SC}}$

5) Since V_{be2} cannot exceed $0.7 V$, V_{Rsc} is limited

6) This is constant current limiting

Voltage Regulators example

- Given the following series voltage regulator
- 1) Complete the design of the following voltage regulator (Find of R1, R2 and R3) assuming that the voltage across the load resistor R_L is equal to 12V. Assume $I_z(min) = 2mA$.
- 2) Show how to modify the circuit to limit the load current to 1A.
- 3) Find the output voltage for the modified circuit of part 2) when the load resistor $R_L = 100\Omega$ and when $R_L = 8\Omega$.
- 4) Choose a transistor with suitable power rating

Example Continued

• **SOLUTION**

$$1) R_3 \leq \frac{V_{IN(\text{Min})} - V_Z}{I_{Z(\text{Min})}}$$

$$R_3 \leq \frac{20 - 4}{2 \text{ mA}} = 8 \text{ k}\Omega \text{ in order to make sure } I_Z > I_{Z(\text{Min})}$$


If $I_{Z(\text{max})}$ was known, then lower limit for R_3 can also be found

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z = 12 \text{ V}$$

$$\therefore \frac{R_1}{R_2} = \frac{V_o}{V_Z} - 1 = \frac{12}{4} - 1 = 2$$




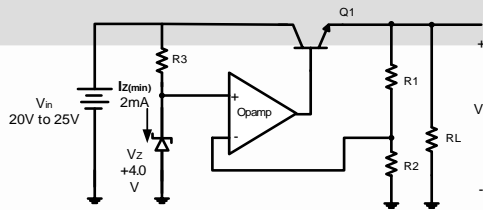choose $R_1 = 20 \text{ k}\Omega$
 $\therefore R_2 = 10 \text{ k}\Omega$



Voltage Regulators

• **SOLUTION**

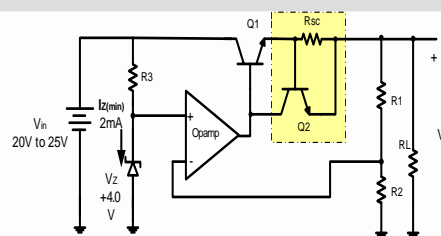


2) — The change for current limit is done by adding Q2 and R_{SC} as shown

$$\& R_{SC} = \frac{V_{be}}{I_{L(\text{Max})}} = \frac{0.7 \text{ V}}{1 \text{ A}} = 0.7 \Omega$$

Ex. Continued

• SOLUTION

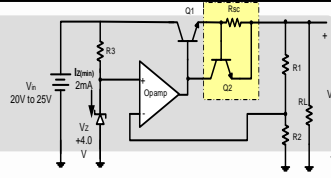

For $R_L = 100 \text{ ohm}$, $V_o = 12\text{V}$, then $I_L = \frac{12\text{V}}{100\Omega} = 0.12\text{A}$

which is smaller than $I_{L(\text{max})}$,

$\therefore V_o = 12 \text{ V}$ and is not affected by the current limit circuit

For $R_L = 8 \text{ ohm}$, $V_o = 12\text{V}$, then $I_L = \frac{12\text{V}}{8\Omega} = 1.5\text{A}$

which is bigger than $I_{L(\text{max})}$, and the current limit circuit

limits the current to the maximum allowable value which is 1 A

$\therefore V_o = I_{L(\text{Max})} * R_L = 1\text{A} * 8\Omega = 8 \text{ V}$

Example Continued


$$P_{Q1} = V_{CE(\text{MAX})} * I_{E(\text{MAX})}$$

$$V_{CE(\text{MAX})} = V_{IN(\text{MAX})} - V_{O(\text{MIN})} = 25 - 8 = 17 \text{ V}$$

$$I_{E(\text{MAX})} = I_{R1} + I_{L(\text{MAX})} = \frac{V_Z}{R_1} + I_{L(\text{MAX})}$$

$$= \frac{8 \text{ V}}{20 \text{ k}\Omega} + 1 \text{ A} = 1.0004 \text{ A}$$
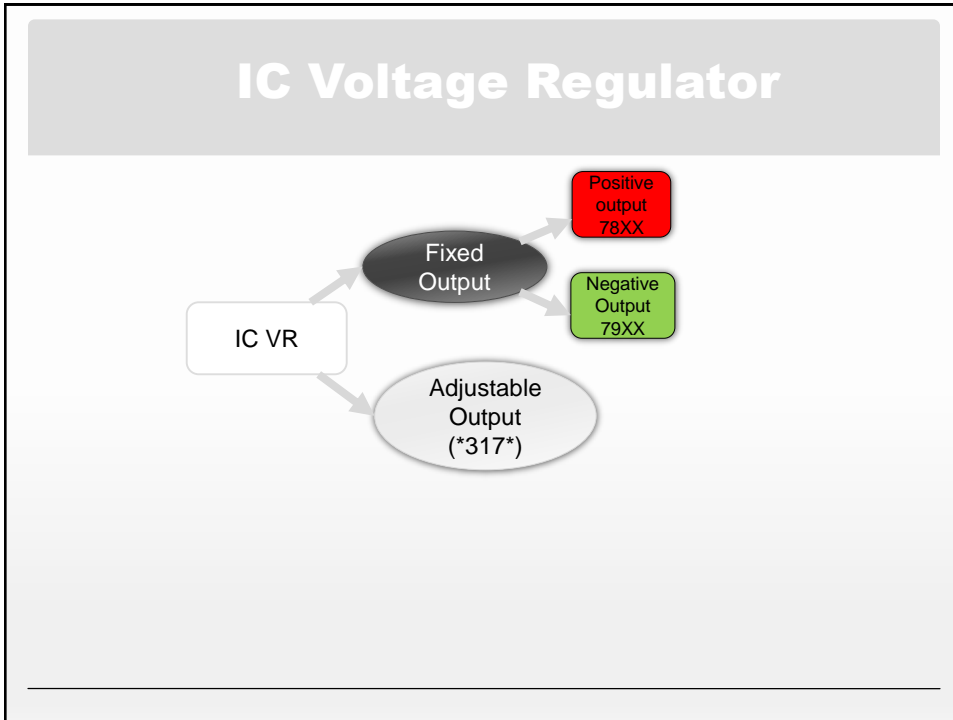
$$P_{Q1} = 17 \text{ V} * 1.0004 \text{ A} = 17.0068 \text{ W}$$



3 Terminal IC Voltage Regulators

- Fixed output voltage type
- Two families exist:
 - Fixed positive output (78xx) , where xx defines the value of output voltage such as 5, 6, 8,9,12 ...etc
 - Fixed negative output (79xx) , where xx defines the value of output voltage such as -5, -6, -8,-9,-12 ...etc


LM78XX / LM78XXA
3-Terminal 1 A Positive Voltage Regulator

Fixed Voltage Regulator (for reference only)

- The fixed voltage regulator has an unregulated dc input voltage V_i applied to one input terminal, a regulated output dc voltage V_o from a second terminal, and the third terminal connected to ground.

Fixed-Positive Voltage Regulator

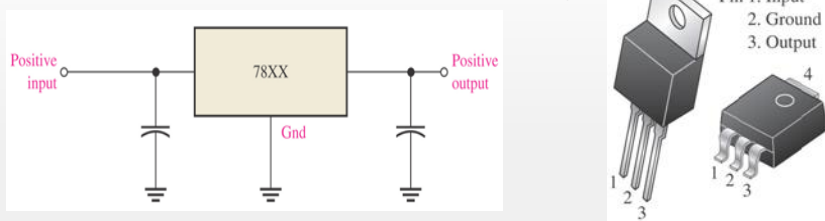- The series 78XX regulators are the three-terminal devices that provide a fixed positive output voltage.



Fixed Voltage Regulator

Positive-Voltage Regulators in the 78XX Series


IC Part	Output Voltage (V)	Minimum V_i (V)
7805	+5	+7.3
7806	+6	+8.3
7808	+8	+10.5
7810	+10	+12.5
7812	+12	+14.5
7815	+15	+17.7
7818	+18	+21.0
7824	+24	+27.1

V_{in} must be higher than V_o by at least 2V for proper operation of the voltage regulator

Fixed Voltage Regulator

Fixed-Negative Voltage Regulator

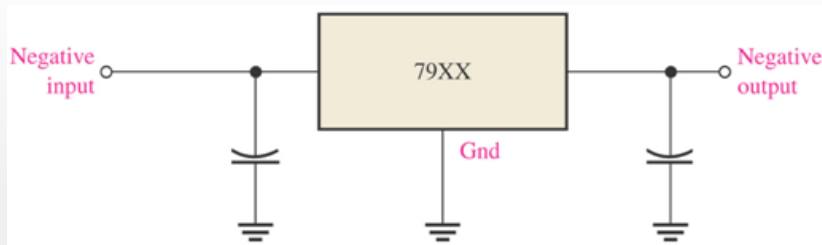- The series 79XX regulators are the three-terminal IC regulators that provide a fixed negative output voltage.
- This series has the same features and characteristics as the series 78XX regulators except the pin numbers are different.




Fixed Voltage Regulator

Negative-Voltage Regulators in the 79XX Series

IC Part	Output Voltage (V)	Minimum V_i (V)
7905	-5	-7.3
7906	-6	-8.4
7908	-8	-10.5
7909	-9	-11.5
7912	-12	-14.6
7915	-15	-17.7
7918	-18	-20.8
7924	-24	-27.1

Adjustable Voltage Regulator based on 78xx family

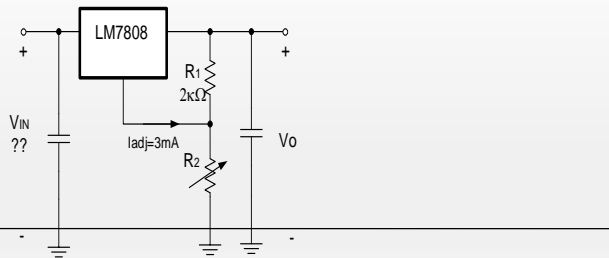- Find the minimum and maximum output voltage (V_o) for the following IC voltage regulator. Note that R_2 is a variable resistor that can be varied from 0 to $3k\Omega$
- What is the range of values of V_{IN} required for proper operation of the circuit
- What is the power dissipation of the LM7808 when $V_o=V_o(\min)$ and $V_{in}=V_{in}(\max)$ and load current = $0.25A$



• Solution Voltage Regulators

$$V_{o(\text{MIN})} = V_{\text{REG}} = 8 \text{ V (when } R_2 = 0 \Omega)$$

$$V_{o(\text{MAX})} = V_{R_1} + V_{R_2} = I_{\text{REG}} (R_1) + (I_{\text{REG}} + I_{\text{adj}})(R_2)$$

$$I_{\text{REG}} = \frac{V_{\text{REG}}}{R_1}$$

$$V_{o(\text{MAX})} |_{R_2=3k\Omega} = \frac{V_{\text{REG}}}{R_1} (R_1 + R_2) + I_{\text{adj}} (R_2)$$

$$= \frac{8\text{V}}{2k\Omega} (2k\Omega + 3k\Omega) + 3\text{mA} \cdot (3k\Omega)$$

$$= (4\text{mA}) \cdot (5k\Omega) + 9\text{V} = 29\text{V}$$

Voltage Regulators

- **Solution**

V_{IN} must be higher than V_O by at least 2 volts

when $V_O = 8V$, $V_{IN(MIN)} = 8 + 2 = 10 V$

when $V_O = 29V$, $V_{IN(MAN)} = 29 + 2 = 31 V$

Power Dissipation of LM7808 :


$$P_{(LM7808)} \cong (V_{IN} - V_O) * I_L = (31 - 8) * 0.25 = 5.75 W$$

ENEE236 Analog Electronics
Nasser Ismail

Adjustable-Voltage Regulator


Adjustable-Voltage Regulator

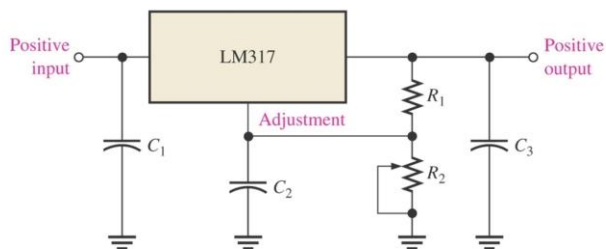- Voltage regulators are also available in circuit configurations that allow to set the output voltage to a desired regulated value.
- The LM317 is an example of an adjustable-voltage regulator, can be operated over the range of voltage from 1.25 to 35 V




Voltage Regulators

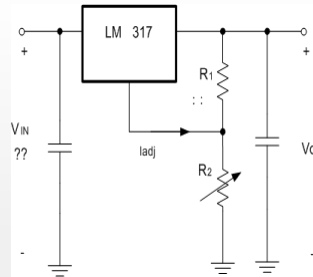- $I_{adj} \approx 50 \mu\text{A}$ (constant From data sheet)
- $V_{REF} = 1.25$ (always true for the 317 family)
- $V_o \approx 1.25 - 35\text{V}$
- V_o is defined by proper choice of R_1 & R_2
- $V_o = V_{R1} + V_{R2}$
- $V_{R1} = V_{REF} = I_{R1} * R_1$
- $I_{R1} = I_{REF} = V_{REF} / R_1$
- $V_{R2} = (I_{REF} + I_{ADJ}) * R_2$
- $V_o = I_{REF} * (R_1 + R_2) + I_{adj} * R_2$



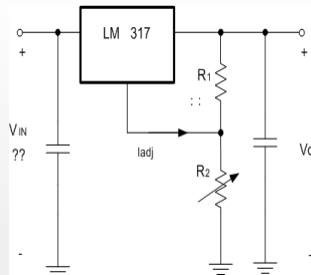Example

- Given $R_1 = 220 \Omega$; $R_2 = 5\text{k}\Omega$ potentiometer
- $I_{adj} \approx 50 \mu\text{A}$ (constant From data sheet)
- Find $V_o(\text{min})$ and $V_o(\text{max})$
- Find range of V_{in} ?



Voltage Regulators

$$I_{REF} = \frac{V_{REF}}{R_1} = \frac{1.25}{220 \Omega}$$

$$V_O = I_{REF}(R_1 + R_2) + I_{adj}(R_2)$$

$$V_{O(MAX)} |_{R2=5k\Omega} = (26.66 + 0.25) = 29.91 \text{ V}$$

$$V_{O(MIN)} |_{R2=0k\Omega} = V_{REF} = 1.25 \text{ V}$$

The input voltage must be higher than the output by at least 2 V

$$V_{IN(MIN)} \cong 1.25 + 2 = 3.25 \text{ V}$$

$$V_{IN(MAX)} \cong 29.91 + 2 = 31.91 \text{ V}$$