

Analog Electronics

ENEE236

Instructor: Nasser Ismail


L8- DC Biasing - BJTs

Biasing

Biasing: Applying DC voltages to a transistor in order to establish fixed level of voltage and current.
For Amplifier (active/Linear) mode, the resulting dc voltage and current establish the operation point to turn it on so that it can amplify AC signals.

Operating Point

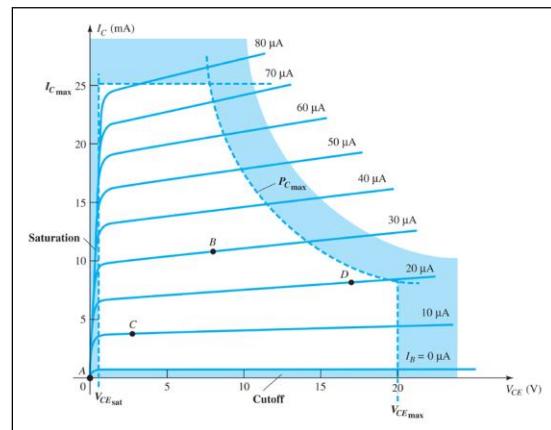
The DC input establishes an operating or *quiescent point* called the ***Q-point***.



DC Biasing Circuits


1. Fixed-bias circuit
2. Emitter-stabilized bias circuit
3. DC bias with voltage feedback
4. Voltage divider bias circuit

1) Fixed Bias Configuration

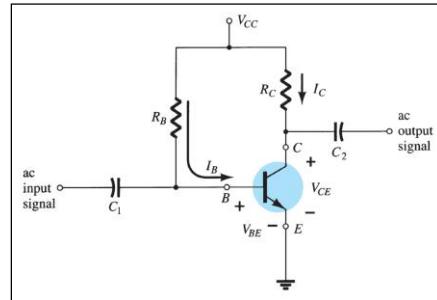

DC equivalent circuit
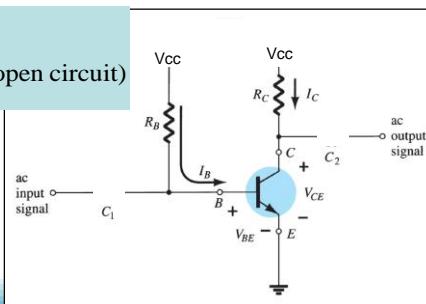
$$f = 0 \Rightarrow X_C = \frac{1}{2\pi f C} \approx \infty \text{ (open circuit)}$$



The Base-Emitter Loop


From Kirchhoff's voltage law for Input:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

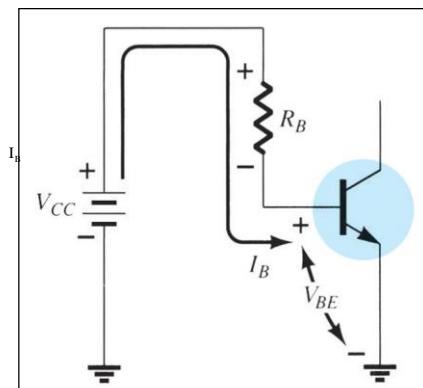Choosing R_B will establish the required level of I_B



Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$



$$\text{Since } V_E = 0 \Rightarrow V_{CE} = V_C$$

$$V_{CE} = V_{CC} - I_C R_C$$

Also

$$V_{BE} = V_B - V_E$$

$$\therefore V_{BE} = V_B$$

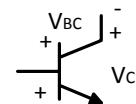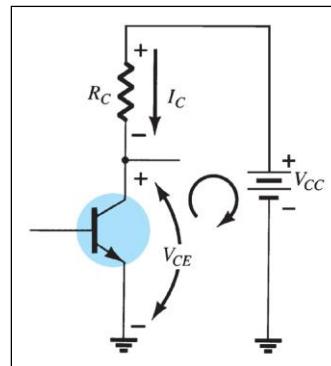

$$V_{BE} - V_{CE} - V_{BC} = 0$$

$$\therefore V_{BC} = V_{BE} - V_{CE}$$

Design: Fixed bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\min} = 50$, $\beta_{\max} = 150$

Design for Q-point: $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

$$I_{BQ} = \frac{I_{CQ}}{\beta_{\text{nominal}}} = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow$$


$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{10 - 0.7}{10 \mu\text{A}}$$

$$= 930 \text{ k}\Omega$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 5 = 10 - I_C R_C$$
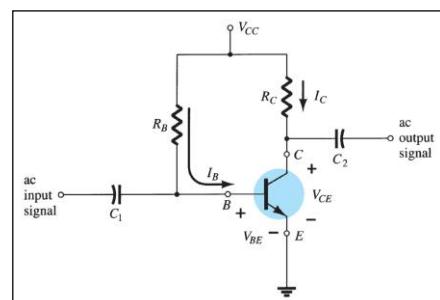
$$\therefore R_C = \frac{5}{1 \text{ mA}} = 5 \text{ k}\Omega$$



Fixed bias Stability

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q-point: $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution – continued

If $\beta = \beta_{\text{min}} = 50$

$$I_B = 10 \mu A$$

$$I_C = \beta I_B = (50)(10 \mu A) = 0.5 mA$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 10 - (0.5 mA)(5 k\Omega) = 7.5 V$$


If $\beta = \beta_{\text{max}} = 150$

$$I_B = 10 \mu A$$

$$I_C = \beta I_B = (150)(10 \mu A) = 1.5 mA$$

$$V_{CE} = V_{CC} - I_C R_C$$
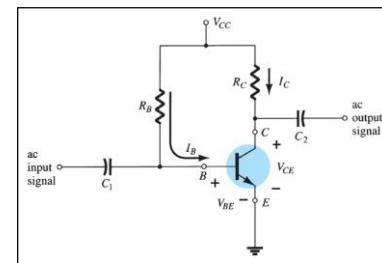
$$V_{CEQ} = 10 - (1.5 mA)(5 k\Omega) = 2.5 V$$



for

$$50 \leq \beta \leq 150$$

$$I_B = 10 \mu A \text{ fixed}$$


$$0.5 mA \leq I_C \leq 1.5 mA$$

$$7.5 V \geq V_{CE} \geq 2.5 V$$

$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.5 mA}{0.5 mA} = 3 \quad \text{Not very stable}$$

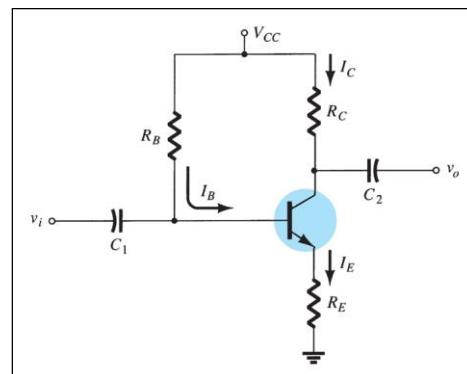2) Emitter-Stabilized Bias Circuit

Adding a resistor (R_E) to the emitter circuit stabilizes the bias circuit.



Base-Emitter Loop

From Kirchhoff's voltage law:


$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

Since $I_E = (\beta + 1)I_B$:

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

Solving for I_B :
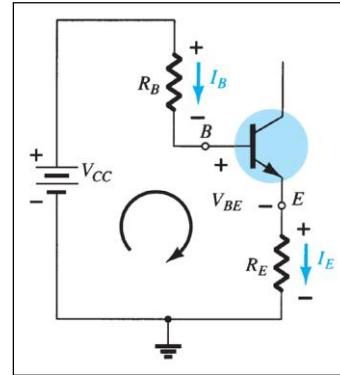
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$



$(\beta + 1)R_E$ ← is the emitter resistor as it appears
in the base emitter loop

Base-Emitter Loop


Solving for I_E :

$$I_E = \frac{V_{CC} - V_{BE}}{\frac{R_B}{(\beta + 1)} + R_E}$$

In order to get I_E almost independent of B
we choose :

$$R_E \gg \frac{R_B}{(\beta + 1)}$$
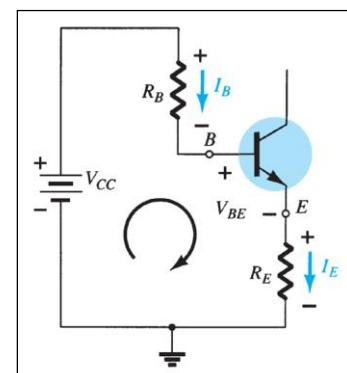
$$\Rightarrow I_E \approx \frac{V_{CC} - V_{BE}}{R_E}$$



Also, in order to guarantee operation in linear mode
we choose $0.1 V_{CC} \leq V_E < 0.2 V_{CC}$

Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since $I_E \approx I_C$:


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
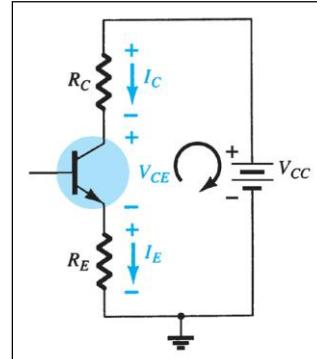
$$V_B = V_{CC} - I_R R_B = V_{BE} + V_E$$



Design: Emitter Stabilization bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\min} = 50$, $\beta_{\max} = 150$

Design for Q-point: $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

$$\text{let } V_E = 0.1 V_{CC}$$

$$V_E = 1V$$

$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01 \text{ mA}} \approx 1 \text{ k}\Omega$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \Rightarrow$$

$$R_B I_B + I_B (\beta + 1) R_E = V_{CC} - V_{BE}$$

$$R_B = \frac{V_{CC} - V_{BE} - I_B (\beta + 1) R_E}{I_B}$$

$$= \frac{10 - 0.7 - 10 \mu\text{A} (100 + 1) 1 \text{ k}\Omega}{10 \mu\text{A}}$$

$$= 829 \text{ k}\Omega$$

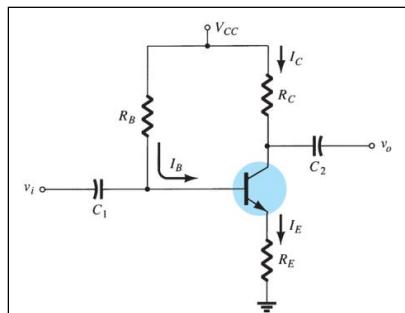

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 5 = 10 - 1 - I_C R_C$$

$$\therefore R_C = \frac{4}{1 \text{ mA}} = 4 \text{ k}\Omega$$

Emitter bias Stability


If $\beta = \beta_{\min} = 50$

$$I_B = \frac{9.3}{829k\Omega + 51k\Omega} = 10.56 \mu A$$

$$I_C = \beta I_B = (50)(10.56 \mu A) = 0.528 mA$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$
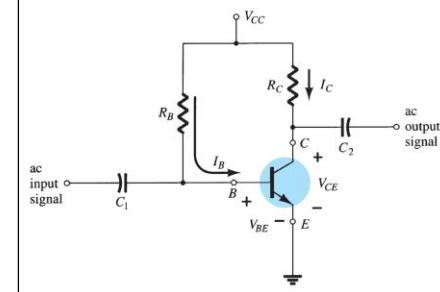
$$V_{CEQ} = 10 - (0.528 mA)(4 k\Omega) - 1 = 6.89 V$$



If $\beta = \beta_{\max} = 150$

$$I_B = \frac{9.3}{829k\Omega + 151k\Omega} = 9.489 \mu A$$

$$I_C = \beta I_B = (150)(9.489 \mu A) = 1.423 mA$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 10 - (1.423 mA)(4 k\Omega) - 1 = 3.31 V$$

for

$$50 \leq \beta \leq 150$$

$$10.56 \mu A \geq I_B \geq 9.489 \mu A$$

$$0.528 mA \leq I_C \leq 1.423 mA$$

$$6.89 V \geq V_{CE} \geq 3.31 V$$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.423 mA}{0.528 mA} \approx 2.7$$

Improved,
but not
very
stable

Improved Biased Stability


Stability refers to a condition in which the currents and voltages remain fairly constant over a wide range of temperatures and transistor Beta (β) values.

Adding R_E to the emitter improves the stability of a transistor.

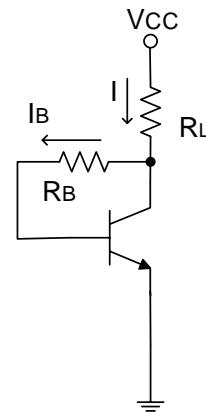3) DC Bias With Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

In this bias circuit the Q-point is only slightly dependent on the transistor beta, β .



Base-Emitter Loop

From Kirchhoff's voltage law:

$$V_{CC} - I \cdot R_L - I_B \cdot R_B - V_{BE} = 0$$

$$I = I_C + I_B$$

$$I_C = \beta I_B$$


Solving for I_B :

$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$V_{CC} = I \cdot R_L + V_{CE}$$

$$I = I_C + I_B$$

$$V_{CE} = V_{CC} - (I_C + I_B)R_L$$

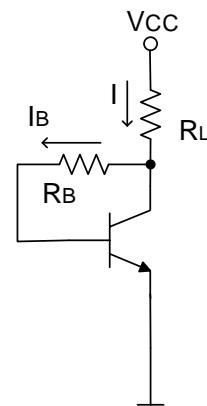

suppose $\beta \uparrow, I_B \downarrow, I_C = \uparrow \beta \cdot I_B \downarrow \approx \text{const}$

there is some kind of compensation effect

Design: Voltage feedback bias

Assume $V_{CC} = 10V$, $\beta_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$


Design for Q-point: $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

$$R_L = \frac{V_{CC} - V_{CE}}{I_C + I_B} = \frac{10 - 5}{1mA + \frac{1mA}{100}} = 4.95 k\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$\therefore R_B = 430 k\Omega$$

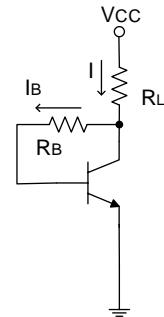

If $\beta = \beta_{min} = 50$

$$I_B = 0.013627 mA$$

$$I_C = 0.68 mA$$

If $\beta = \beta_{max} = 150$

$$I_B = 0.00793 mA$$

$$I_C = 1.19 mA$$

for

$$50 \leq \beta \leq 150$$

$$0.68 mA \leq I_C \leq 1.19 mA$$


$$\therefore \frac{I_{C(max)}}{I_{C(min)}} = \frac{1.19 mA}{0.68 mA} \cong 1.75$$

Better Q-point stability

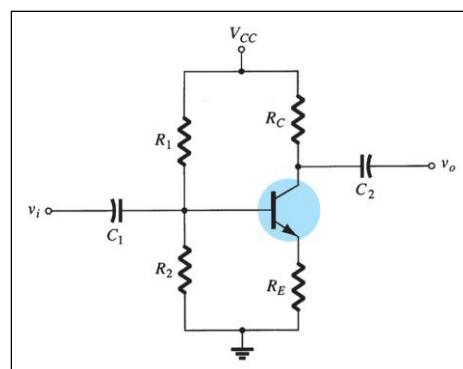4) Voltage Divider Bias

This is a very stable bias circuit.

The currents and voltages are nearly independent of any variations in β if the circuit is designed properly




Approximate Analysis

Where $I_B \ll I_1$ and $I_1 \approx I_2$:

$$V_B = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$
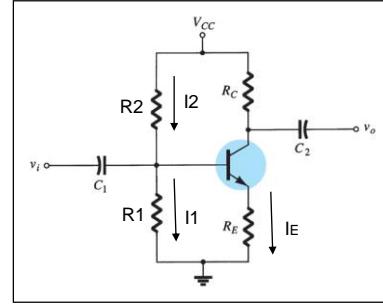
$$I_{E(\text{approximate})} = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E}$$



From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \approx I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Here we got I_C independent of β which provides good Q-point stability

Exact Analysis

We must try to make I_B as close as possible to zero

Thevenin Equivalent circuit for the circuit left of the base is done



$$V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$\text{but } I_B = \frac{I_E}{\beta + 1}$$
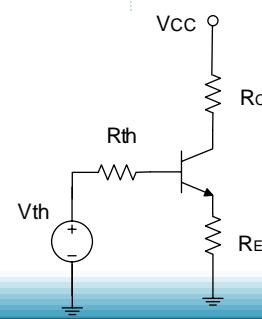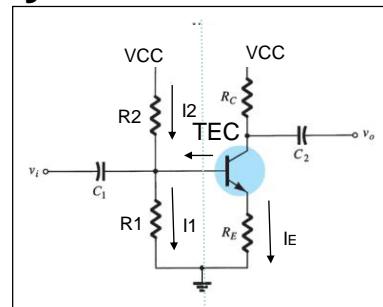
$$\therefore I_{E(\text{exact})} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$




Exact Analysis

$$\therefore I_{E(exact)} = \frac{V_{th} - V_{BE}}{R_{th} + R_E}$$

if we compare to approximate solution

$$I_{E(approximate)} = \frac{V_B - V_{BE}}{R_E}$$

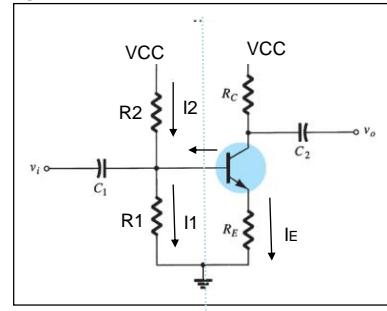\Rightarrow we must make the quantity $\frac{R_{th}}{\beta+1} \ll R_E$




Here we got I_C independent of β

$$\therefore R_{th} \ll (\beta+1)R_E$$

as a rule let $R_{th} \ll \frac{(\beta+1)R_E}{10}$

or

$$R_{th} \ll \frac{\beta R_E}{10}$$

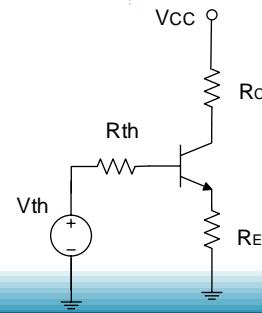

Design: Voltage Divider bias

Assume $V_{CC} = 10V$, $\beta_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$

Design for Q-point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

$$1) \text{let } V_E = 0.1 V_{CC}$$

$$V_E = 1V$$


$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01 \text{ mA}} \cong 1k\Omega$$

$$2) \text{ let } R_{th} = \frac{R_E \cdot \beta_{nominal}}{50} = \frac{1k\Omega \cdot 100}{50} = 2k\Omega$$

$$3) V_{CC} = R_C I_C + I_E R_E + V_{CE}$$

$$V_{CEQ} = 5$$
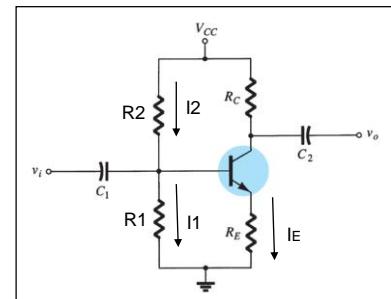
$$\therefore R_C = \frac{V_{CC} - V_{CE} - V_E}{1 \text{ mA}} = \frac{10 - 5 - 1}{1 \text{ mA}} = 4k\Omega$$



Design: Voltage Divider bias

Assume $V_{CC} = 10V$, $\beta_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$

Design for Q-point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution – continued

$$4) I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$


$$\therefore V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2} = I_E \left(\frac{R_{th}}{\beta + 1} + R_E \right) + V_{BE} = 1.72V \dots (1)$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = 2 \text{ k}\Omega \dots \dots \dots (2)$$

solving (1) & (2) yields:

$$R_1 = 2.42 \text{ k}\Omega$$

$$R_2 = 11.64 \text{ k}\Omega$$

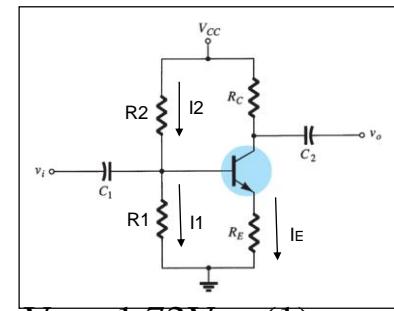

Voltage Divider bias Stability

If $\beta = \beta_{min} = 50$

$$I_C = 0.982 \text{ mA}$$

If $\beta = \beta_{max} = 150$

$$I_C = 1.0069 \text{ mA}$$

for

$$50 \leq \beta \leq 150$$

$$0.982 \text{ mA} \leq I_C \leq 1.0067 \text{ mA}$$

$$\therefore \frac{I_{C(max)}}{I_{C(min)}} = \frac{1.0067 \text{ mA}}{0.982 \text{ mA}} \approx 1.0254$$


Very good
Q-point
stability

PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *npn* transistor circuits. The only difference is that the currents are flowing in the opposite direction.

Basic BJT Amplifiers Circuits

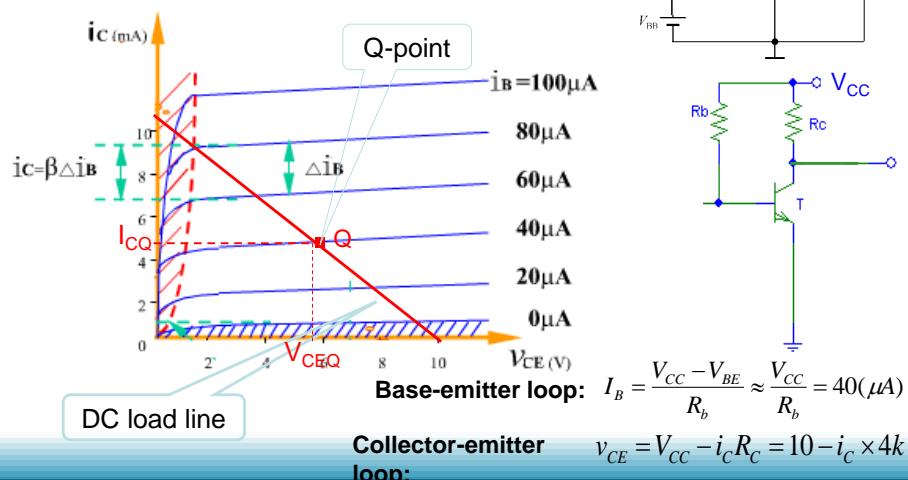DC Load Line and Quiescent Operation Point



DC and AC Load Lines

Assume $V_{CC} = 18V$, $\beta = 100$
 $R_B = 576 k\Omega$; $R_C = 3k\Omega$; $V_{BE} = 0.65 V$


FIRST: DC ANALYSIS

$$V_{CC} = V_{CE} + I_C R_C$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \Leftarrow I_C = f(V_{CE})$$

This is a straight line equation

$$Y = mX + b$$

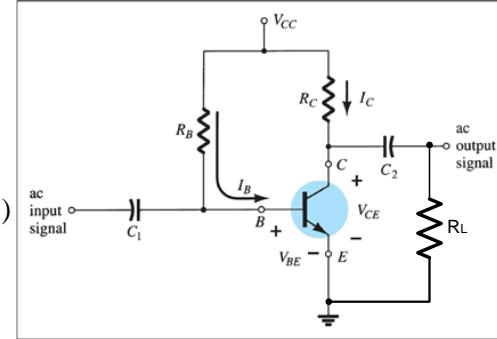

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{18 - 0.65}{576 \text{ k}\Omega} = 30 \mu\text{A}$$

$$I_C = \beta I_B = 3 \text{ mA}$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C = 18 - (3\text{mA})(3\text{k}\Omega) \\ &= 9 \text{ V} \end{aligned}$$

I_{Csat}

$$I_{Csat} = \frac{V_{CC}}{R_C}$$


$$V_{CE} = V_{CE(sat)} \approx 0 \text{ V}$$

DC Load Line

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \Leftarrow I_C = f(V_{CE})$$


$V_{CEcutoff}$
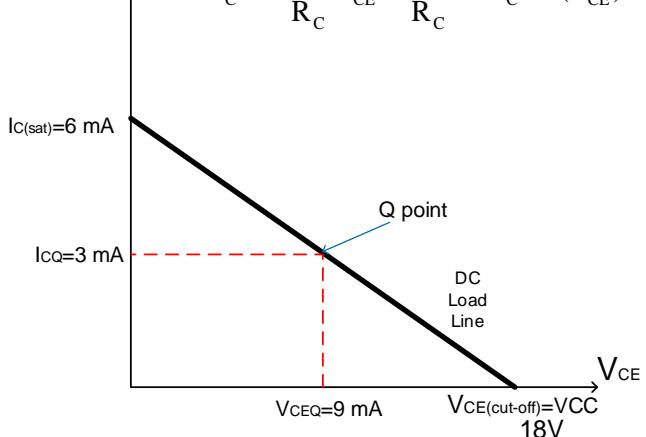
$$\begin{aligned} V_{CE(cutoff)} &= V_{CC} \\ I_C &= 0 \text{ mA} \end{aligned}$$



AC Load Line

AC Equivalent Circuit

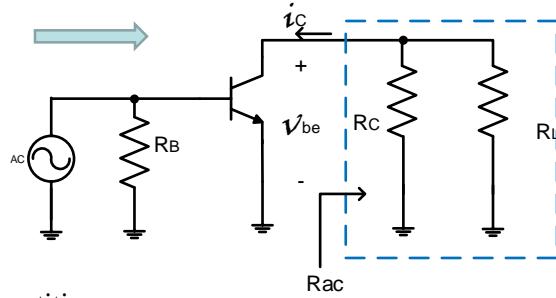

Since we have dc and ac quantities,

let us define the notation

total DC ac

$$V_{BE}(t) = V_{BE} + v_{be}$$

$$V_{CE}(t) = V_{CE} + v_{ce}$$

$$I_C(t) = I_C + i_c$$

$$I_B(t) = I_B + i_b$$


$$v_{ce} = -R_{ac} \cdot i_c$$

$$\text{where } R_{ac} = R_C // R_L$$

is the ac resistance seen from collector terminal
+ resistance seen from emitter terminal

AC Load Line

AC Equivalent Circuit

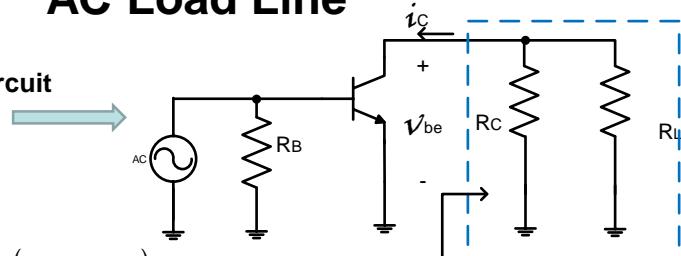


$$(V_{CE}(t) - V_{CEQ}) = -R_{ac} (I_C(t) - I_{CQ})$$


$$(V_{CE}(t)_{\max} - V_{CEQ}) = R_{ac} I_{CQ}$$

$$V_{CE}(t)_{\max} = V_{CEQ} + R_{ac} I_{CQ}, \text{ when } I_C(t) = 0$$

$$(V_{CE}(t) - V_{CEQ}) = -R_{ac} (I_C(t) - I_{CQ})$$

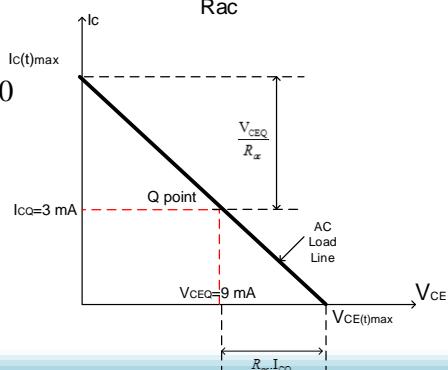
$$I_C(t)_{\max} = \frac{V_{CEQ}}{R_{ac}} + I_{CQ} \text{ when } V_{CE}(t) = 0$$



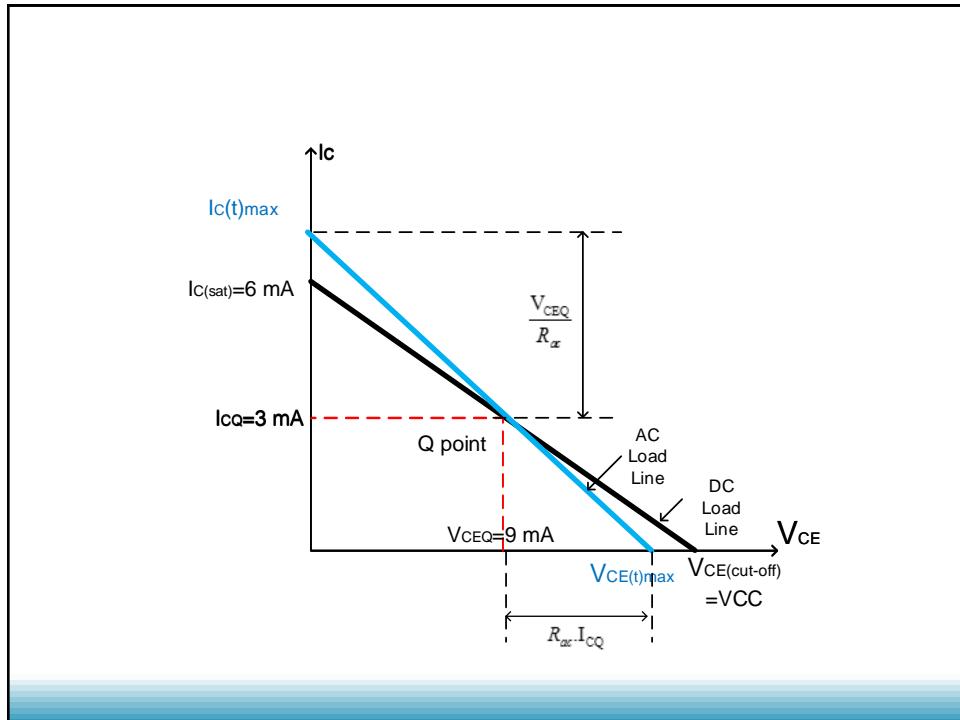

AC Load Line

AC Equivalent Circuit

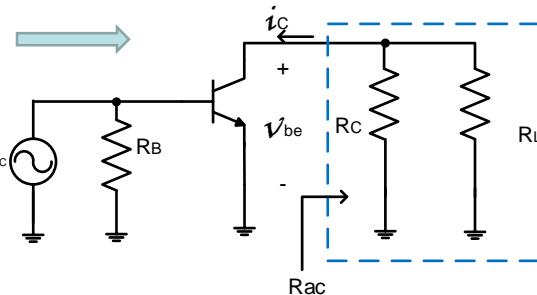

$$v_{ce} = V_{CE}(t) - V_{CE}$$

$$i_c = I_C(t) - I_C$$

$$v_{ce} = -R_{ac} \cdot i_c$$

$$(V_{CE}(t) - V_{CEQ}) = -R_{ac} (I_C(t) - I_{CQ})$$

To Draw ac load line

Ac load line equation we find $(V_{CE(t)_{\max}})$ and $(I_C(t)_{\max})$

Design Criteria

- In order to have the amplifier to amplify an input ac signal without distortion (by going into saturation or cut-off)
- We must choose the Q-point in the middle of ac load line

$$I_{CQ} = \frac{1}{2} I_C(t)_{\max}$$

$$V_{CEQ} = \frac{1}{2} V_{CE}(t)_{\max}$$



$$2I_{CQ} = I_C(t)_{\max}$$

$$2I_{CQ} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

$$\therefore I_{CQ} = \frac{V_{CEQ}}{R_{ac}}$$

DC Analysis

$$V_{CC} = V_{CE} + I_C R_C$$

define $R_{dc} = R_C$

$$V_{CC} = V_{CE} + I_C R_{dc}$$

at the Q - point

$$V_{CC} = V_{CEQ} + I_{CQ} R_{dc}$$

For maximum Symmetrical swing



$$I_{CQ} = \frac{V_{CEQ}}{R_{ac}} \Rightarrow V_{CEQ} = I_{CQ} R_{ac}$$

$$V_{CC} = I_{CQ} \cdot R_{ac} + I_{CQ} \cdot R_{dc}$$

$$\therefore I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}}$$

**** To design for maximum Symmetrical Swing

Also

DC Analysis

$$V_{CEQ} = V_{CC} - I_{CQ} R_{dc}$$

$$= V_{CC} - R_{dc} \frac{V_{CC}}{R_{ac} + R_{dc}}$$

$$= V_{CC} \left(1 - \frac{R_{dc}}{R_{ac} + R_{dc}} \right)$$

$$= V_{CC} \left(\frac{R_{ac} + R_{dc} - R_{dc}}{R_{ac} + R_{dc}} \right)$$

$$= V_{CC} \left(\frac{R_{ac}}{R_{ac} + R_{dc}} \right) = \left(\frac{V_{CC}}{1 + \frac{R_{dc}}{R_{ac}}} \right)$$

***** For maximum

Symmetrical swing


Design Example

Design the amplifier for maximum symmetrical swing of the collector current?
 Find the Q-point?

Find the required Value of R_B ?

Draw AC and DC load lines

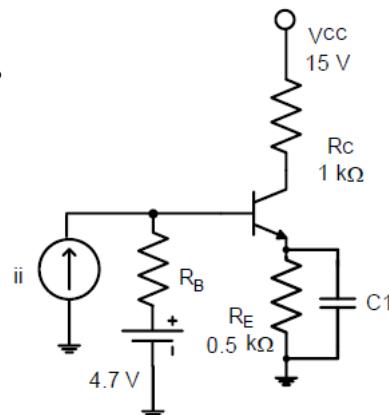What is the power dissipation of the transistor at the Q-point?



Solution

$$R_{ac} = R_C = 1 \text{ k}\Omega$$

$$R_{dc} = R_C + R_E = 1.5 \text{ k}\Omega$$

For Maximum Symmetrical Swing of I_C

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}} = \frac{15}{1 \text{ k}\Omega + 1.5 \text{ k}\Omega} = 6 \text{ mA}$$


$$V_{CEQ} = \frac{V_{CC}}{1 + \frac{R_{dc}}{R_{ac}}} = \frac{15}{1 + \frac{1.5 \text{ k}\Omega}{1 \text{ k}\Omega}} = 6 \text{ V}$$

Maximum Swing (peak) of I_C

$$I_{CM} = I_{CQ} = 6 \text{ mA}$$

Maximum Symmetrical Swing (peak - peak) of I_C


$$I_{CP-P} = 2I_{CQ} = 12 \text{ mA}$$

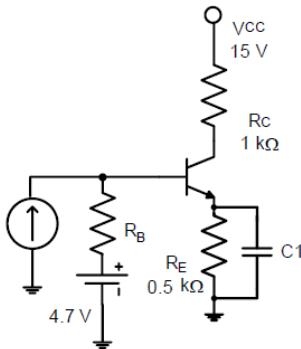

Solution


Maximum value of I_C :
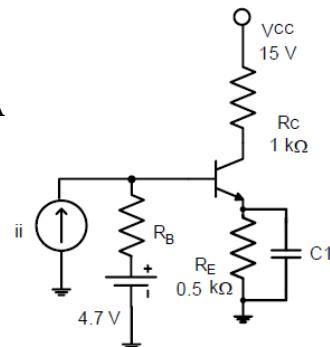
$$I_C(t)_{Max} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 6 \text{ mA} + \frac{6}{1 \text{ k}\Omega} = 12 \text{ mA}$$



Maximum Value of V_{CE}

$$V_{CE}(t)_{Max} = I_{CQ} R_{ac} + V_{CEQ} = 6 \text{ mA} \cdot 1 \text{ k}\Omega + 6 = 12 \text{ V}$$

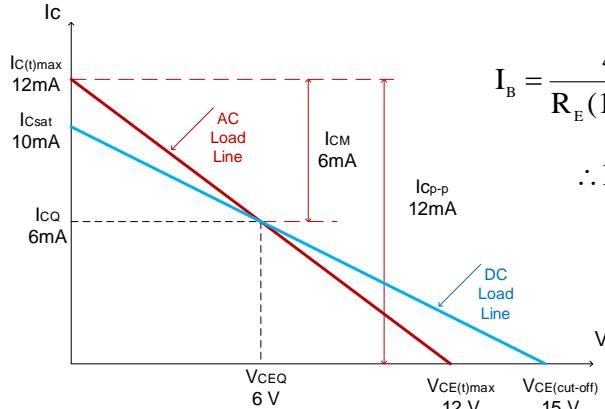Example -Continued

$$I_B = \frac{4.7 - 0.7}{R_E(100+1) + R_B} = \frac{I_{CQ}}{100} = 60 \mu\text{A}$$

$$\therefore R_B = 33 \text{ k}\Omega$$

$$\begin{aligned} P_Q &= V_{CEQ} \cdot I_{CQ} \\ &= 6V \cdot 6mA = 36 \text{ mW} \\ &= 6V \cdot 6mA = 36 \text{ mW} \end{aligned}$$


Analysis Example

Given $R_B = 50 \text{ k}\Omega$

Find the maximum collector current swing and the Q-point?

Draw AC and DC load lines

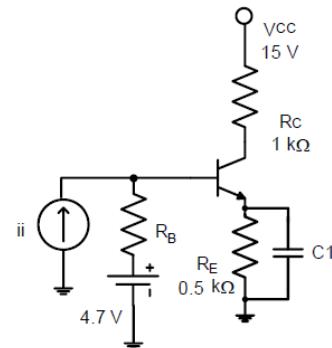What is the power dissipation of the transistor at the Q-point?



$$R_{ac} = R_C = 1 \text{ k}\Omega$$

$$R_{dc} = R_C + R_E = 1.5 \text{ k}\Omega$$

Solution

Value of I_B and I_C


$$I_B = \frac{4.7 - 0.7}{R_E(100+1) + R_B}$$

$$= \frac{4.7 - 0.7}{500(100+1) + 50\text{k}\Omega}$$

$$= 40 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 4 \text{ mA}$$
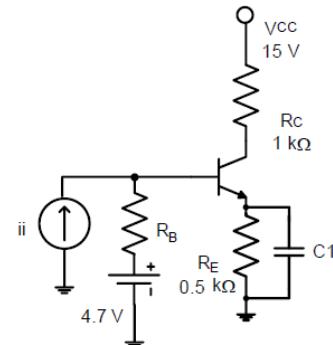
$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) = 9 \text{ V}$$



Maximum Swing (peak) of I_C

$$I_{CM} \neq I_{CQ}, \Rightarrow I_{CM} = 4 \text{ mA}$$



Maximum Symmetrical Swing (peak - peak) of I_C

$$I_{CP-P} = 2I_{CM} = 8 \text{ mA}$$

Solution

$$I_C(t)_{Max} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 4 \text{ mA} + \frac{9}{1 \text{ k}\Omega} = 13 \text{ mA}$$
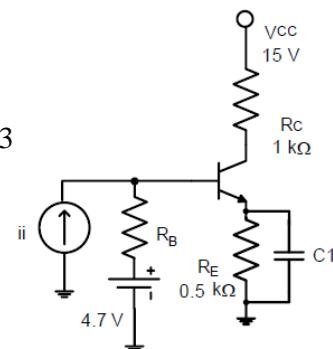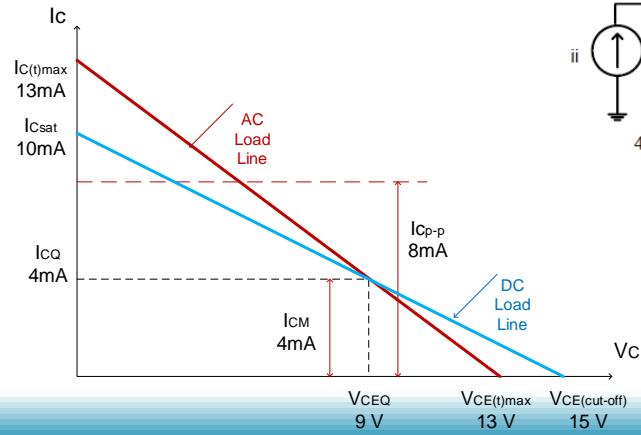
$$V_{CE}(t)_{Max} = I_{CQ}R_{ac} + V_{CEQ} = 4 \text{ mA} \cdot 1 \text{ k}\Omega + 9 = 13$$






Maximum Swing was reduced because the Q-point was not placed properly

Basic BJT Amplifiers Circuits

Graphical Analysis

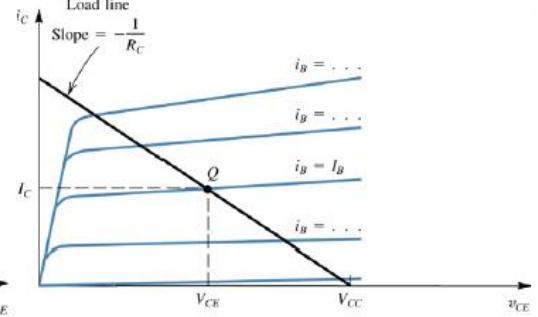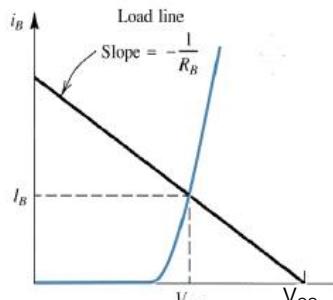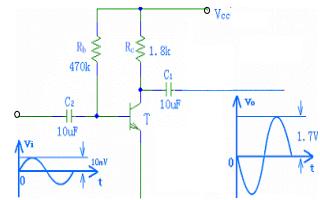- Can be useful to understand the operation of BJT circuits.
- First, establish DC conditions by finding I_B (or V_{BE})
- Second, figure out the DC operating point for I_C





Can get a feel for whether the BJT will stay in active region of operation

– What happens if R_C is larger or smaller?

Basic BJT Amplifiers Circuits

Graphical Analysis

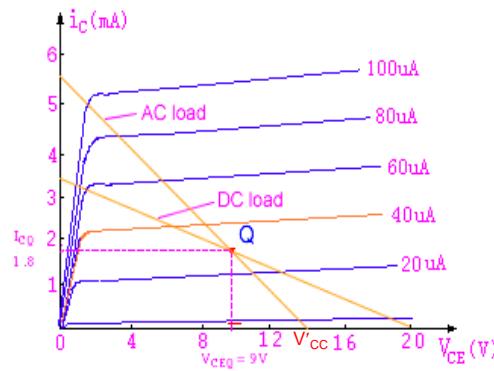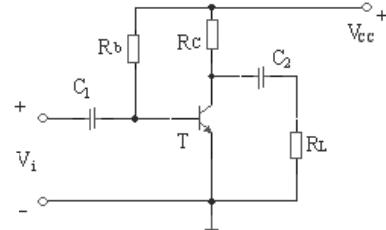



$$v_{ce} = -i_c(R_C // R_L) = -i_c R_L$$

$$V_{CC}' = V_{CEO} + I_{CQ}R_L'$$

Basic BJT Amplifiers Circuits

Graphical Analysis



Q-point is centered on the ac load line:

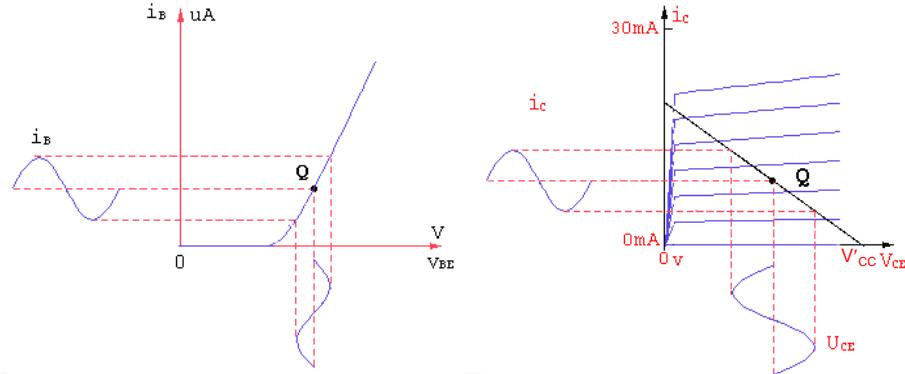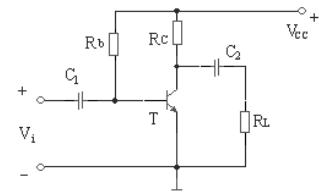

Basic BJT Amplifiers Circuits

Graphical Analysis


Q-point closer to cutoff:

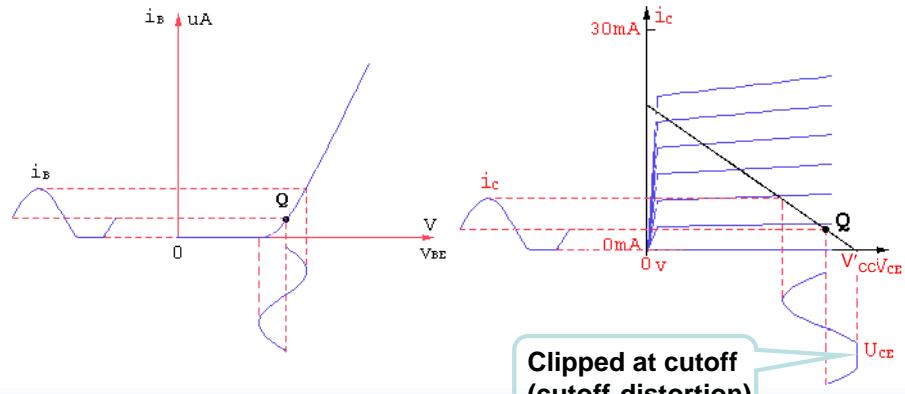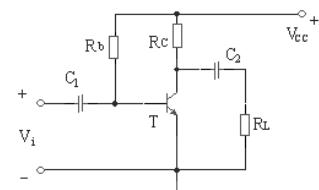

Basic BJT Amplifiers Circuits

Graphical Analysis

Q-point closer to saturation:

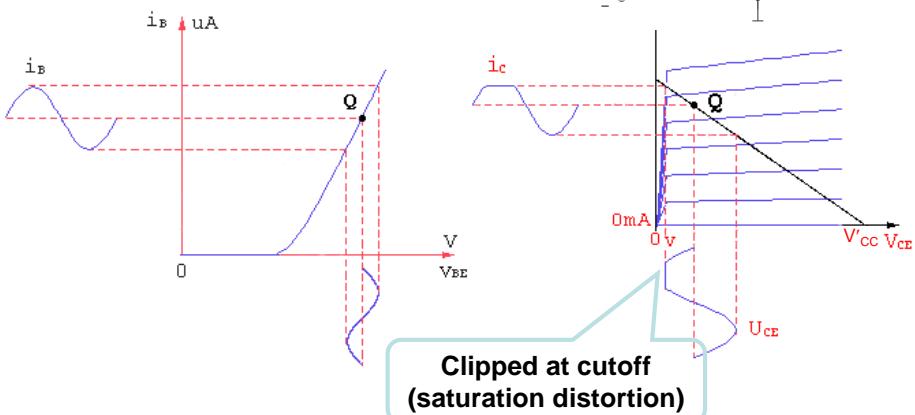

Basic BJT Amplifiers Circuits

Graphical Analysis

