

## CH 11: Balanced Three-phase Circuits

Three sources  
Three-phase  $\equiv$  3- $\phi$   
single-phase  $\equiv$  1- $\phi$

### Balanced 3- $\phi$ Voltages:

They are 3 voltage sources that have identical amplitudes and frequency, but are out of phase with each other by exactly  $120^\circ$


sequences of balanced 3- $\phi$  systems

1) Positive sequence "abc sequence"

$$V_a(t) = V_m \cos(\omega t + \theta_v) \quad , \quad \vec{V}_a = V_m \angle \theta_v$$


$$V_b(t) = V_m \cos(\omega t + \theta_v - 120^\circ) \quad , \quad \vec{V}_b = V_m \angle \theta_v - 120^\circ$$
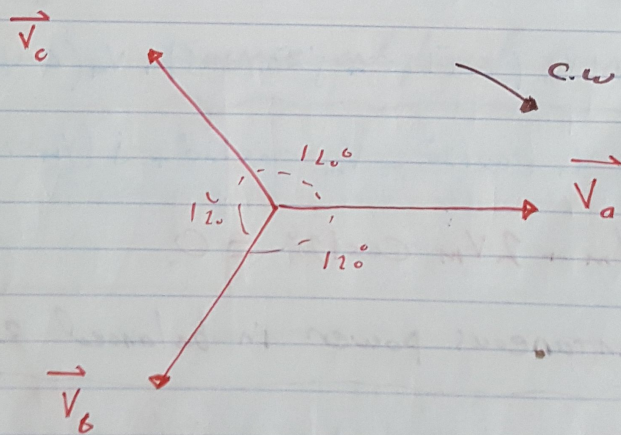
$$V_c(t) = V_m \cos(\omega t + \theta_v + 120^\circ) \quad , \quad \vec{V}_c = V_m \angle \theta_v + 120^\circ$$



2) Negative sequence "acb sequence"

$$\begin{aligned}\vec{V}_a &= V_m \angle 0^\circ \\ \vec{V}_b &= V_m \angle 0^\circ + 120^\circ \\ \vec{V}_c &= V_m \angle 0^\circ - 120^\circ\end{aligned}$$

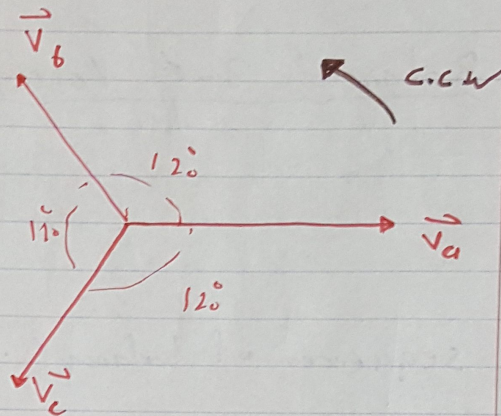

Balanced 3- $\phi$  voltages:

$$\boxed{e_v = 0}$$

$$V_a(t) + V_b(t) + V_c(t) \quad \text{t-domain}$$

$$\vec{V}_a + \vec{V}_b + \vec{V}_c \quad \text{phasor-domain}$$




$$= V_m \angle 0^\circ + V_m \angle -120^\circ + V_m \angle 120^\circ$$

$$= V_m + V_m (\cos 120^\circ + j \sin(-120^\circ)) + V_m (\cos 120^\circ + j \sin 120^\circ)$$

$$= V_m + V_m \cos 120^\circ + V_m \cos 120^\circ + j (V_m \sin 120^\circ - V_m \sin 120^\circ)$$

$$= V_m + 2V_m \cos 120^\circ = 0$$

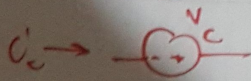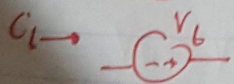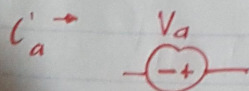Instantaneous power in balanced 3- $\phi$  systems



$$P(t) = P_a(t) + P_b(t) + P_c(t)$$

↑  
Total instantaneous power

$$P_a = V_a(t) i_a(t) \quad , \quad P_b = V_b(t) i_b'(t) \quad , \quad P_c = V_c(t) i_c'(t)$$

Assume:

$$V_a(t) = V_m \cos(\omega t + \theta_v) \quad , \quad i_a = I_m \cos(\omega t + \theta_i)$$

$$V_b(t) = V_m \cos(\omega t + \theta_v - \frac{2\pi}{3}) \quad , \quad i_b' = I_m \cos(\omega t + \theta_i - \frac{2\pi}{3})$$

$$V_c(t) = V_m \cos(\omega t + \theta_v + \frac{2\pi}{3}) \quad , \quad i_c' = I_m \cos(\omega t + \theta_i + \frac{2\pi}{3})$$

$$P(t) = V_a(t) i_a(t) + V_b(t) i_b'(t) + V_c(t) i_c'(t)$$

$$P(t) = \frac{3}{2} V_m I_m \cos(\theta_v - \theta_i) = \text{Average Power}$$

↑  
3-φ

(No double frequency component!)


Instantaneous  
Power



$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + P(2\omega t)$$

1-φ


Source and Load Connections

Source Y on Δ

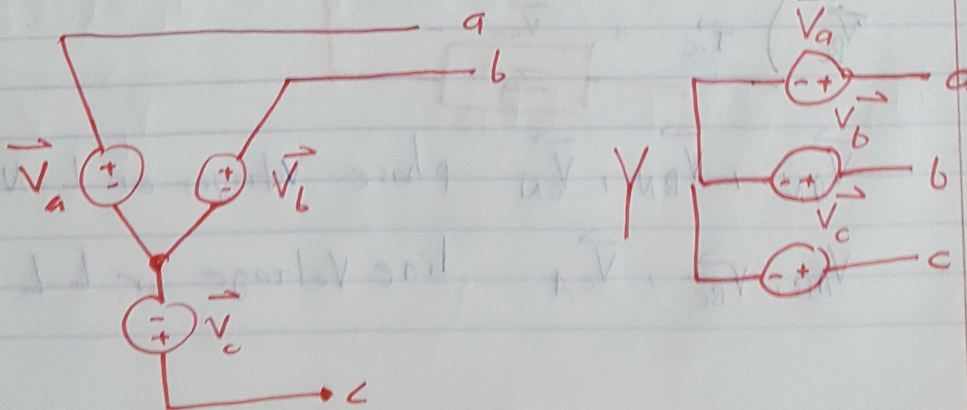

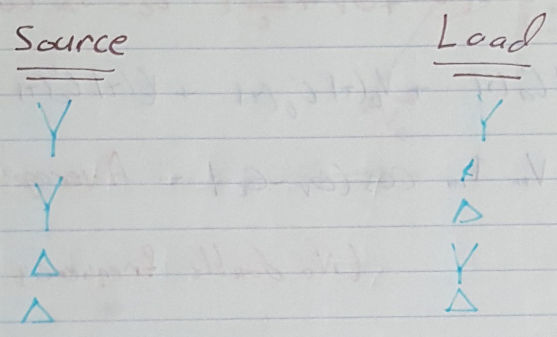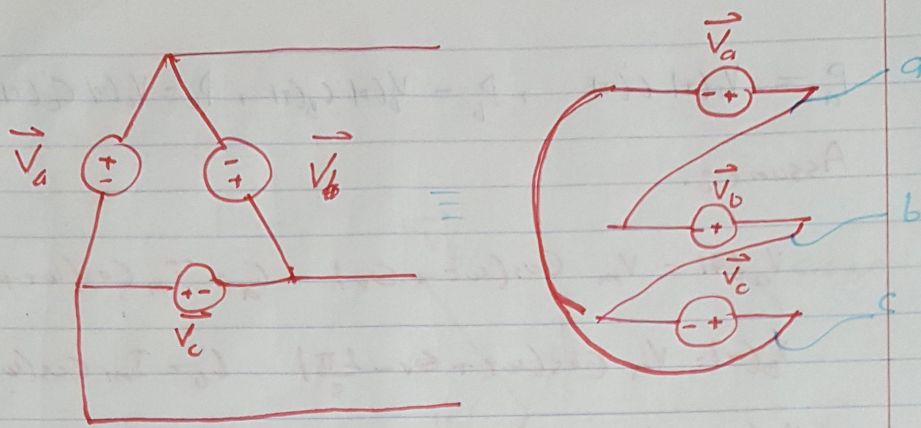

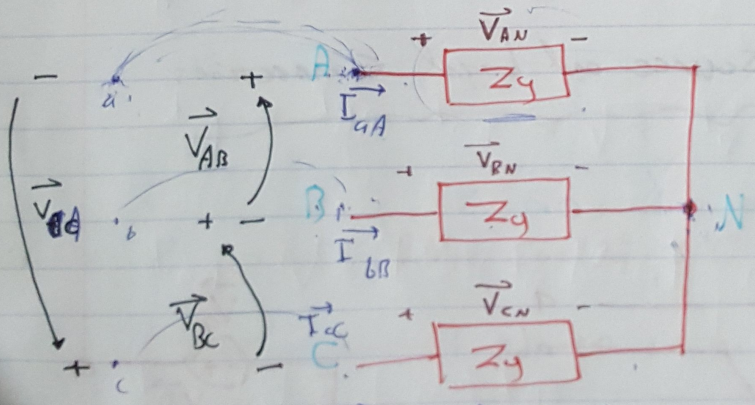line and phase voltages in Y-connected load or source.



in this case  
 $\vec{I}_L = \vec{I}_\phi$

$\vec{V}_{AN}, \vec{V}_{BN}, \vec{V}_{CN}$  phase voltages on L-N voltages  
 $\vec{V}_{AB}, \vec{V}_{BC}, \vec{V}_{CA}$  line voltage or L-L voltages

$\vec{I}_{aA}, \vec{I}_{bB}, \vec{I}_{cC}$  line currents.

Assume  $\phi_c$ .

$$\vec{V}_{AN} = V_\phi \angle 0^\circ$$

$$\vec{V}_{BN} = V_\phi \angle 0^\circ - \frac{2\pi}{3}$$

$$\vec{V}_{CN} = V_\phi \angle 0^\circ + \frac{2\pi}{3}$$

$$\vec{V}_{AB} = \vec{V}_{AN} - \vec{V}_{BN} = V_\phi \angle 0^\circ - V_\phi \angle 0^\circ - \frac{2\pi}{3}$$


$$\vec{V}_{AB} = (V_\phi \cos(0^\circ) + j V_\phi \sin(0^\circ)) - (V_\phi \cos(0^\circ - \frac{2\pi}{3}) + j V_\phi \sin(0^\circ - \frac{2\pi}{3}))$$

$$\vec{V}_{AB} = \sqrt{3} V_\phi \angle 30^\circ$$

$$\vec{V}_{AB} = (\sqrt{3} \angle 30^\circ) \vec{V}_{AN}$$

$$\vec{V}_{LL} = (\sqrt{3} \angle 30^\circ) \vec{V}_{L-N}$$

## $\Delta$ - connected Load on source

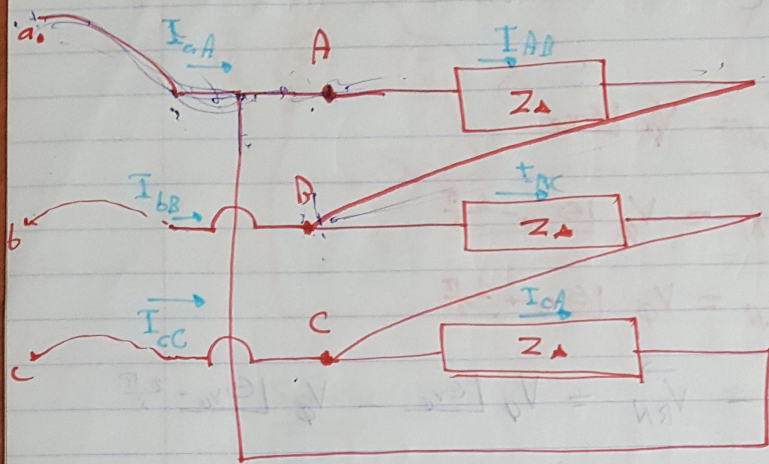

$I_{AB}, I_{BC}, I_{CA} \Rightarrow$  phase current

$I_{aA}, I_{bB}, I_{cC} \Rightarrow$  line current

$V_{AB}, V_{BC}, V_{CA}$  Phase Voltages

$$\vec{I}_{AB} = I_\phi \angle \theta_\phi, \quad \vec{I}_{BC} = I_\phi \angle \theta_\phi - \frac{2\pi}{3}, \quad \vec{I}_{CA} = I_\phi \angle \theta_\phi - \frac{4\pi}{3}$$

$$\vec{I}_{aA} = \vec{I}_{AB} - \vec{I}_{CA} = \sqrt{3} I_\phi \angle \theta_\phi - 30^\circ$$

$$I_{aA} = (\sqrt{3} \angle 30^\circ) (I_\phi \angle \theta_\phi) \quad , \quad \vec{I}_L = (\sqrt{3} \angle -30^\circ) \vec{I}_\phi$$

$$\vec{I}_{aA} = (\sqrt{3} \angle -30^\circ) \vec{I}_{AB} \quad \vec{V}_L = \vec{V}_\phi$$

Y-connected load or source

$$\vec{V}_L = (\sqrt{3} \angle 30^\circ) \vec{V}_\phi$$

$$\vec{I}_L = \vec{I}_\phi$$

Δ-Connected load or source


$$\vec{V}_L = \vec{V}_\phi$$

$$\vec{I}_L = (\sqrt{3} \angle -30^\circ) \vec{I}_\phi$$

### Y-Y Analysis

Source Load

winding impedance

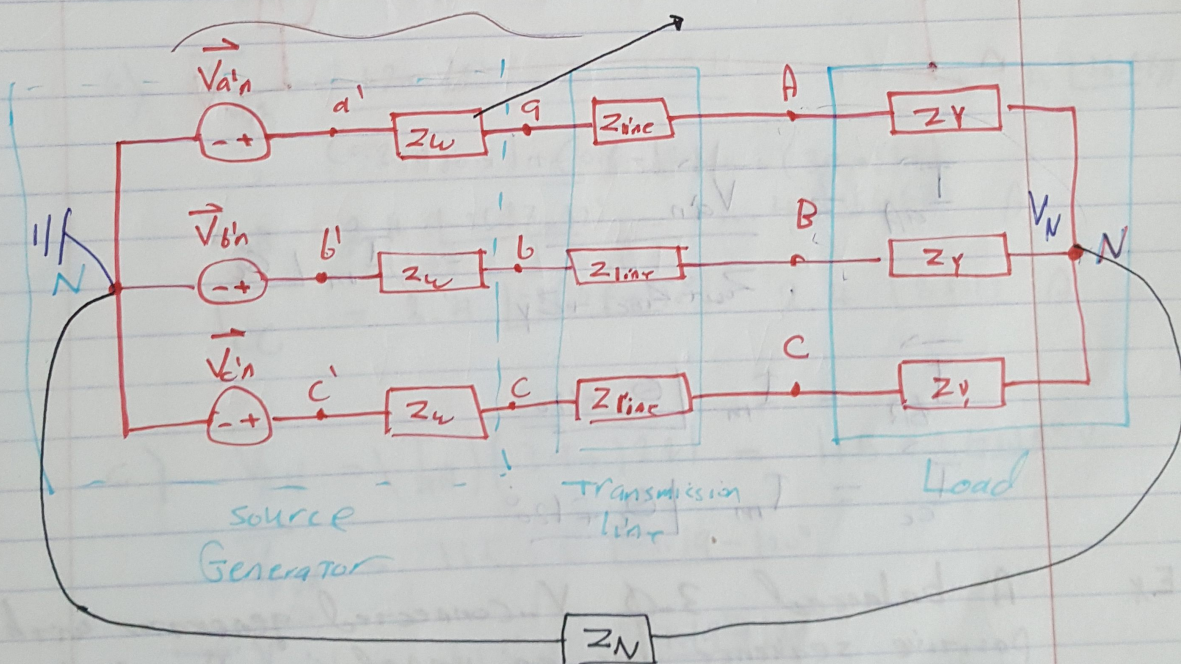

Kcl at Node N


$$\frac{\vec{V}_N - \vec{V}_{a'n}}{Z_\phi} + \frac{\vec{V}_N - \vec{V}_{b'n}}{Z_\phi} + \frac{\vec{V}_N - \vec{V}_{c'n}}{Z_\phi} + \frac{\vec{V}_N}{Z_N} = 0$$

$$\frac{3}{Z_0} \vec{V}_N - \frac{1}{Z_0} (\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn}) + \frac{V_N}{Z_N} = 0$$

$$\left( \frac{3}{Z_0} + \frac{1}{Z_N} \right) \vec{V}_N = 0$$

$$\boxed{\vec{V}_N = 0} \Rightarrow \boxed{I_N = 0}$$

1- $\phi$  equivalent circuit

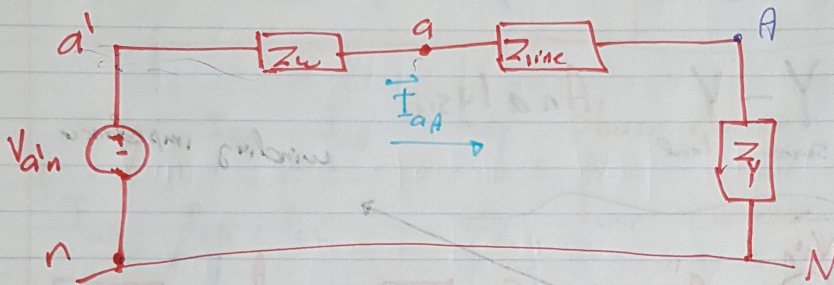

$$\vec{I}_{aA} = \frac{\vec{V}_{an}}{Z_w + Z_{line} + Z_Y} = I_m \angle \theta_c$$

$$\vec{I}_{BR} = I_m \angle \theta_c + 120^\circ$$


$$\vec{I}_{CC} = I_m \angle \theta_c + 120^\circ$$

EX

A balanced 3- $\phi$  Y-connected generator with positive sequence has an impedance of  $0.2 + j0.5 \Omega/\phi$  and an internal voltage  $120V/\phi$ . The generator feeds a balanced 3- $\phi$  Y-connected load having an impedance of  $39 + j28 \Omega/\phi$ . The impedance of TLI is  $0.8 + j1.5 \Omega/\phi$



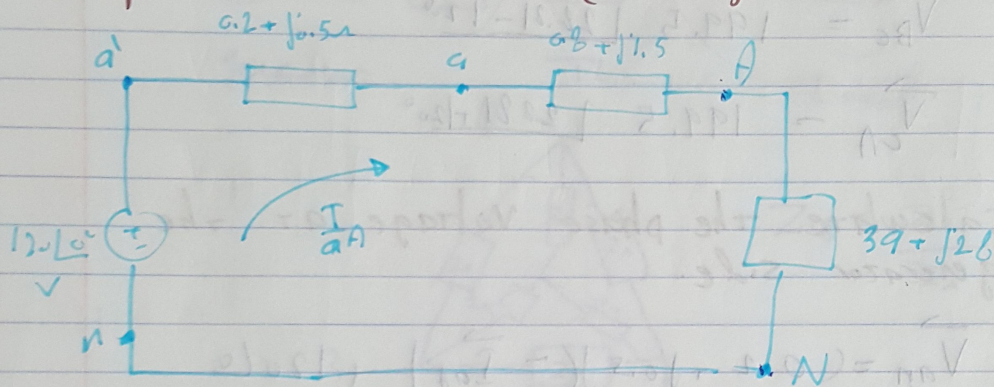- a) Draw the  $\Pi$ - $\phi$  equivalent circuit  
 b) Calculate the line current  
 c) Calculate the phase voltage at the load side.  
 d) " " " " " " " " " "



$$b) \vec{I}_{aA} = \frac{120 \angle 0^\circ}{(0.2 + j0.5) + (0.6 + j1.5) + (39 + j26)} = 2.4 \angle -36.87^\circ \text{ A}$$

$$\vec{I}_{bB} = 2.4 \angle -36.87^\circ - 120^\circ = 2.4 \angle -156.87^\circ \text{ A}$$

$$\vec{I}_{cC} = 2.4 \angle -36.87^\circ + 120^\circ = 2.4 \angle 83.13^\circ \text{ A}$$

$$c) \vec{V}_{AN} = (\vec{I}_{aA}) (39 + j26) = 115.22 \angle -1.19^\circ \text{ V}$$

$$\vec{V}_{BN} = 115.22 \angle -1.19^\circ - 120^\circ$$



$$\vec{V}_{CN} = 115.22 \angle -1.19^\circ + 120^\circ$$

$$\begin{aligned} \vec{V}_{AB} &= \sqrt{3} \angle 20^\circ (\vec{V}_{AN}) \\ \vec{V}_{AB} &= (\sqrt{3} \angle 30^\circ) (115,22 \angle -119^\circ \text{ V}) \\ &= 199,5 \angle 28,61^\circ \\ \vec{V}_{BC} &= 199,5 \angle 28,61 - 120^\circ \\ \vec{V}_{CA} &= 199,5 \angle 28,61 + 120^\circ \end{aligned}$$

E Calculate the phase voltage at the generator side.


$$\begin{aligned} \vec{V}_{an} &= (0,2 + j0,5) (-\vec{I}_{aA}) + 120 \angle 0^\circ \\ \vec{V}_{an} &= 118,9 \angle -0,32^\circ \\ \vec{V}_{bn} &= 118,9 \angle -0,32 - 120^\circ \\ \vec{V}_{cn} &= 118,9 \angle -0,32 + 120^\circ \end{aligned}$$

$Y \rightarrow \Delta$

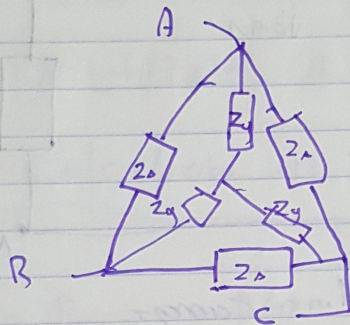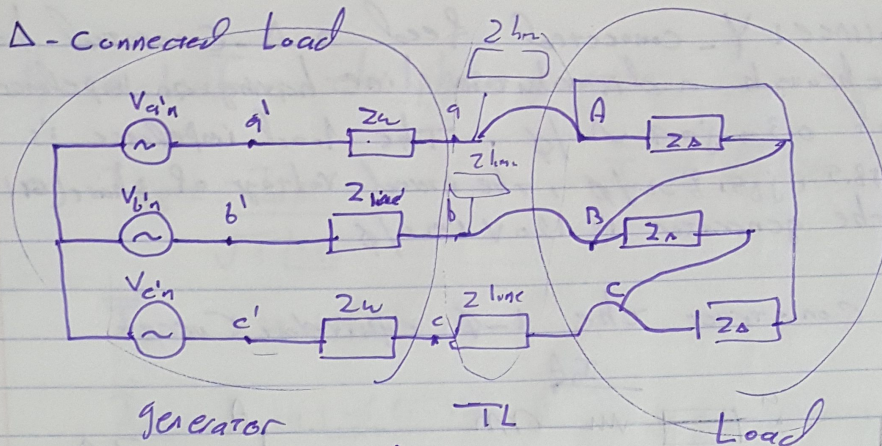

$$Z_Y = \frac{Z_{\Delta}^2}{3Z_{\Delta}} = \frac{Z_{\Delta}}{3}$$

1- $\phi$  equivalent circuit

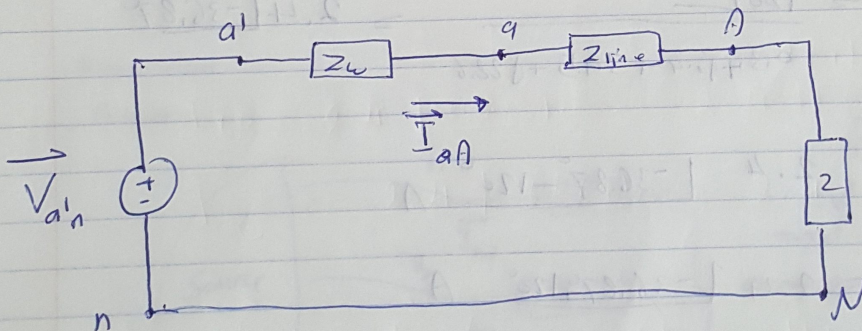

$$\vec{I}_{aA} = \frac{\vec{V}_{a'n}}{Z_w + Z_{line} + \frac{2Z_{\Delta}}{3}}$$


$$\vec{I}_L = (\sqrt{3} \angle -30^\circ) \vec{I}_a$$

$$\vec{V}_L = \vec{V}_{\phi}$$

positive sequence.

Source:  $Y$ -connected feed a  $\Delta$ -connected load through a distribution line having an impedance of  $0.3 + j0.9 \Omega/\phi$ . The load impedance is  $118.5 + j85.8 \Omega/\phi$ , the internal voltage of phase (a) of the generator is  $120 \text{ V rms}/\phi$

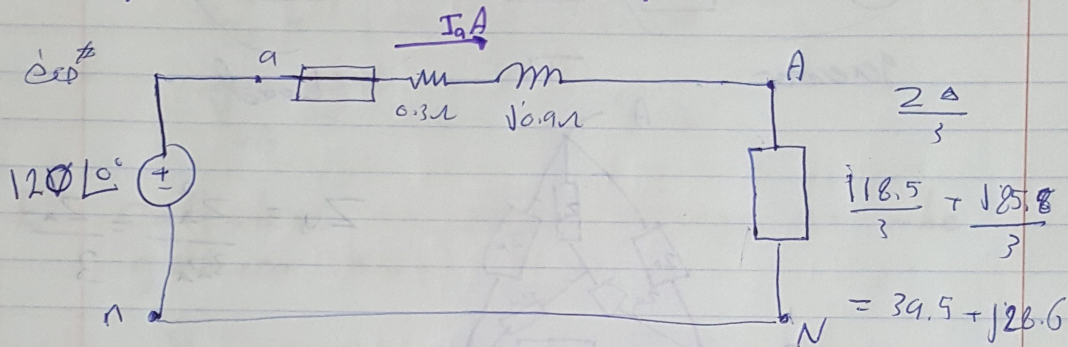a) construct the 1- $\phi$  equivalent circuit



b) calculate the line current

$$\vec{I}_{aA} = \frac{120 \angle 0^\circ}{0.3 + j0.9 + 39.5 + j28.6} = 2.4 \angle -36.87^\circ$$

$$\vec{I}_{bB} = 2.4 \angle -36.87^\circ - 120^\circ \text{ A}$$

$$\vec{I}_{cC} = 2.4 \angle -36.87^\circ + 120^\circ \text{ A}$$

Here  $\otimes$  c) calculate the phase voltages at the load sides.

$$\vec{V}_{AN} = \left(\frac{Z_A}{3}\right) (\vec{I}_{aA}) = 114.04 \angle -0.96^\circ$$

$$\vec{V}_{AB} = (\sqrt{3} \angle 30^\circ) \vec{V}_{AN} = 202.72 \angle 29.04^\circ \text{ V}$$

$$\vec{V}_{BC} = 202.72 \angle 29.04^\circ - 120^\circ$$

$$\vec{V}_{CA} = 202.72 \angle 29.04^\circ + 120^\circ$$

with  $\Delta$  &  
v using phase  
line &  
also  
AB

d) calculate the phase current.

$$\vec{I}_{AB} = \frac{I_{aA}}{\sqrt{3} \angle -30^\circ}$$

$$\vec{I}_L = \sqrt{3} \angle -30^\circ \vec{I}_\phi$$

$$\vec{I}_{AR} = 1.39 \angle -6.87^\circ \text{ A}$$


$$\vec{I}_{BC} = 1.39 \angle -6.87^\circ - 120^\circ \text{ A}$$

$$\vec{I}_{CA} = 1.39 \angle -6.87^\circ + 120^\circ \text{ A}$$

power calculation in 3- $\phi$  circuit

$$P_{3-\phi} (+) = P_{avg} \quad , \quad P_{(-)} = P_{avg} + f(2wC)$$

↑  
INSTANTANEOUS  
POWERS

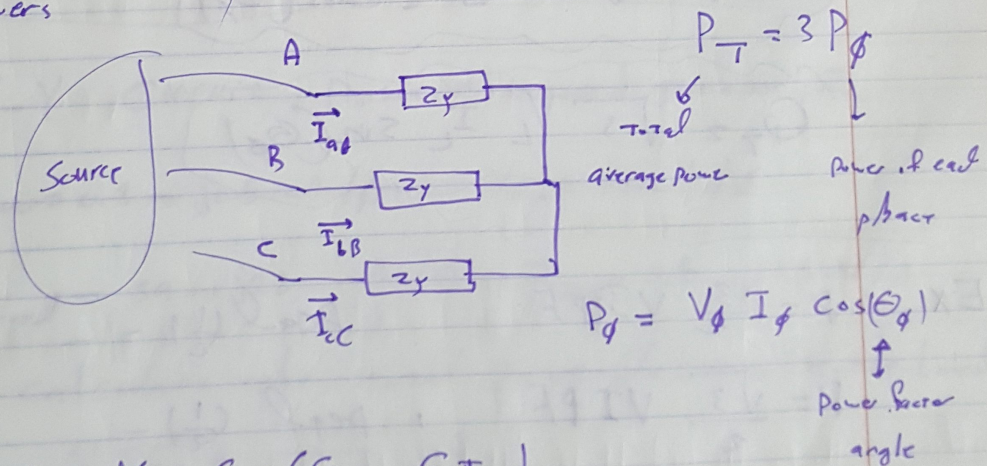

$$P_a = V_{AN} \cos(\theta_{V_{AN}} - \theta_{I_{aA}})$$

$$P_b = V_{BN} I_{bB} \cos(\theta_{V_{BN}} - \theta_{I_{bB}})$$

$$P_c = V_{CN} I_{cC} \cos(\theta_{V_{CN}} - \theta_{I_{cC}})$$

$$V_{AN} = V_{BN} = V_{CN} = V_{\phi}$$

$$I_{aA} = I_{bB} = I_{cC} = I_{\phi}$$

$$\theta_{V_{AN}} - \theta_{I_{aA}} = \theta_{V_{BN}} - \theta_{I_{bB}} = \theta_{V_{CN}} - \theta_{I_{cC}} = \theta_{\phi}$$

$$P_a = P_b = P_c = P_{\phi}$$

$$P_T = 3 V_{\phi} I_{\phi} \cos(\theta_{\phi})$$

$$V_L = \sqrt{3} V_{\phi}$$

$$I_L = I_{\phi}$$

$$P_T = 3 \left( \frac{V_L}{\sqrt{3}} \right) (I_L) \cos(\theta_{\phi})$$

$$P_T = \sqrt{3} V_L I_L \cos(\theta_{\phi})$$

$$Q_T = \sqrt{3} V_L I_L \sin(\theta_{\phi})$$

Ex  $P = \frac{3}{2} VI \cos \theta$        $\cos \theta = \frac{1}{2}$  —


$P = \frac{\sqrt{3}}{2} VI \cos \theta$        $\cos \theta = \frac{1}{2}$  —



$$\vec{S} = P_T + jQ_T$$

$$\vec{S} = \sqrt{3} V_L I_L \angle \theta_\phi$$

$$\theta_{V\phi} - \theta_{I\phi}$$

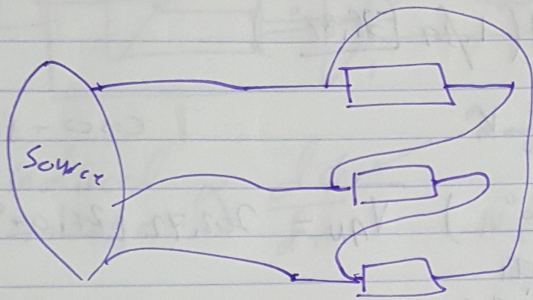

$$P_T = 3 V_\phi I_\phi \cos(\theta_\phi)$$

$$V_L = V_\phi \quad I_L = \sqrt{3} I_\phi$$


$$P_T = 3 V_L \frac{I_L}{\sqrt{3}} \cos(\theta_\phi) = \sqrt{3} V_L I_L \cos(\theta_\phi)$$

EX Y-Y Circuit, positive sequence generator,  $Z_w$

$$Z_w = 0.2 + j0.5 \Omega/\phi, \quad V_{a'n} = 120 \text{ V}/\phi$$

$$Z_{Load} = 39 + j26 \Omega/\phi, \quad Z_{line} = 0.8 + j1.5 \Omega/\phi$$

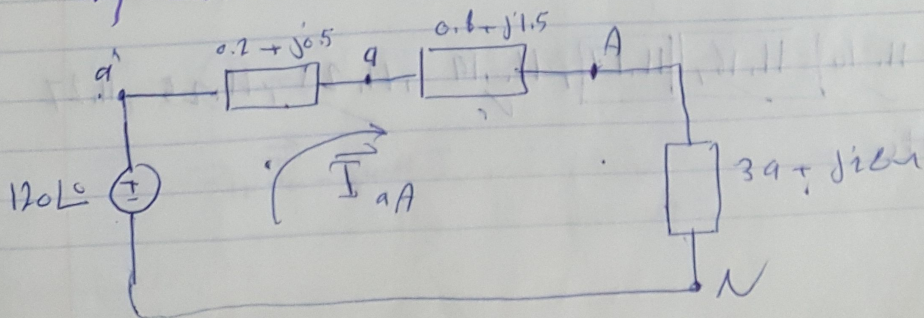a) calculate the total power delivered to the load.



$$e^{j\omega t}$$

$$\vec{I}_{9A} = \frac{120 \angle 0^\circ}{40 + j30} = \frac{2.4}{\sqrt{25}} \angle -6.87^\circ \text{ A}$$

$$\vec{I}_L = 1.39$$

$$\vec{V}_{AN} = (39 + j28) (1.39 \angle 36.87^\circ)$$

$$\vec{V}_{AN} = 115.21 \angle 1.19^\circ \text{ V} \quad \cos 0 + j \sin 0$$

$$\vec{V}_L = (\sqrt{3} \angle 30^\circ) \vec{V}_{AN} = 202.72 \angle 29.04^\circ \text{ V}$$

$$P_T = \sqrt{3} (1.39) (202.72) \cos(-1.19^\circ - 6.87^\circ)$$

$$P_T = 573.96 \text{ W}$$

b) Calculate the total reactive and complex power delivered to the load

$$Q_T = \sqrt{3} (1.39) (202.72) \sin(-1.19^\circ + 6.87^\circ)$$

$$S_T = P_T + jQ_T = 2162$$

c) Calculate the total avg power lost in the TL

$$P_{\text{line}} = 3 I_{9A}^2 (0.2) = (3)(2.4)^2 (0.2) = 13.824 \text{ W}$$


Problems  
to solve.

11.9, 11.10, 11.16, 11.17, 11.19, 11.23, 11.25, 11.27

11.40.




# Transformer

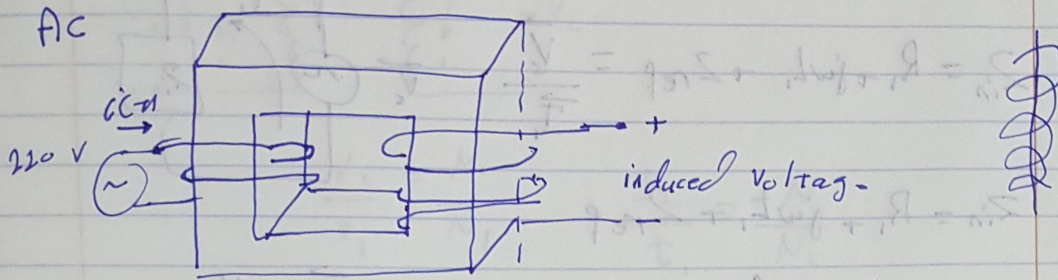

induced voltage  $\propto \frac{d\phi}{dt} \cdot N_2$  "magnetic flux"

$V_s \propto \frac{d\phi}{dt} \cdot N_1$

## Linear Transformer "Real Transformer"

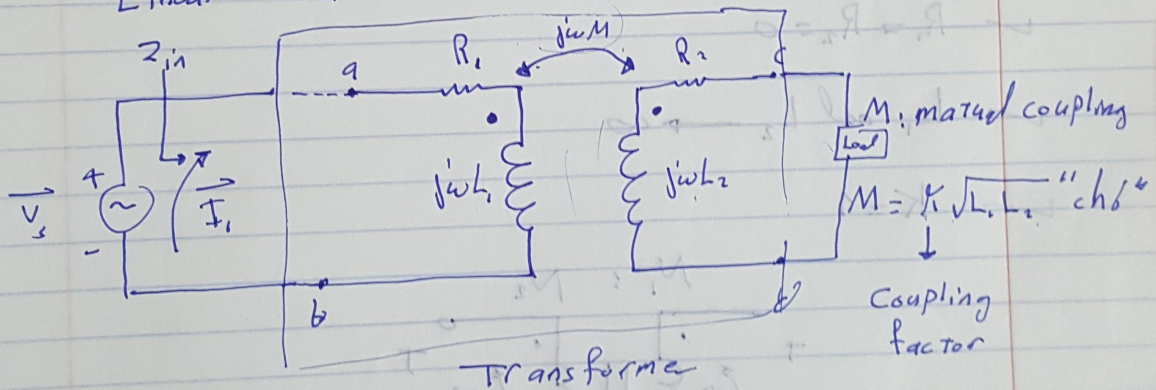

Kvl in loop 1

$$\vec{V}_s = (R_1 + j\omega L_1) \vec{I}_1 - j\omega M \vec{I}_2$$

$$\vec{V}_s = Z_{11} \vec{I}_1 - j\omega M \vec{I}_2$$


Kvl in loop 2:

$$0 = (Z_L + R_2 + j\omega L_2) \vec{I}_2 - j\omega M \vec{I}_1$$

$$0 = Z_{22} \vec{I}_2 - j\omega M \vec{I}_1$$
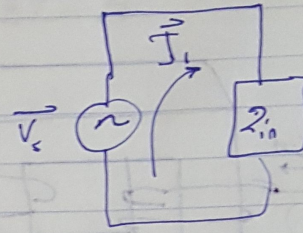
## Reflected impedance

$$Z_{in} = R_1 + j\omega L_1 + Z_{ref} = \frac{\vec{V}_s}{\vec{I}_1}$$



$$Z_{in} = R_1 + j\omega L_1 + Z_{ref}$$

$$Z_{ref} = \left( \frac{\omega M}{|Z_{22}|} \right)^2 \cdot Z_{22}^*$$

$$\vec{I}_1 = \frac{V_s}{Z_{in}}$$


$$|Z_{22}| = |R_2 + j\omega L_2 + Z_L|$$

## Ideal Transformer

$$\checkmark R_1 = R_2 = 0$$


$$\checkmark L_1 \text{ and } L_2 \rightarrow \infty$$

$$\checkmark k = 1$$

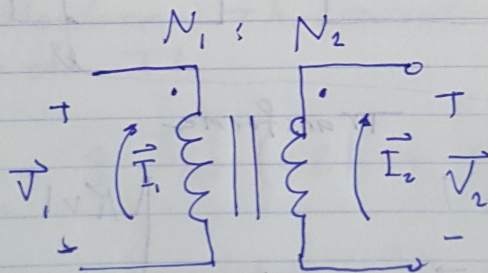

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}, \quad \frac{I_2}{I_1} = \frac{N_1}{N_2}, \quad \frac{N_2}{N_1} = a$$

Transformer  
Transition

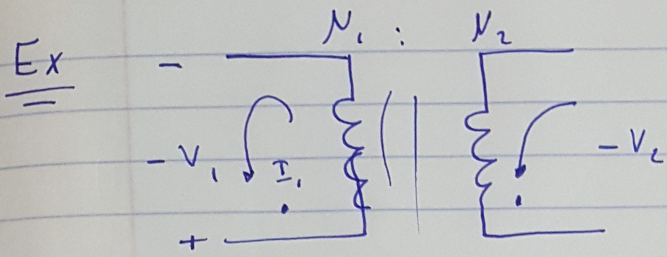

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}, \quad \frac{I_2}{I_1} = -\frac{N_1}{N_2}$$

$$Z_{ref} = \frac{1}{a^2} Z_L$$

$$a = \frac{N_2}{N_1}$$

Ex