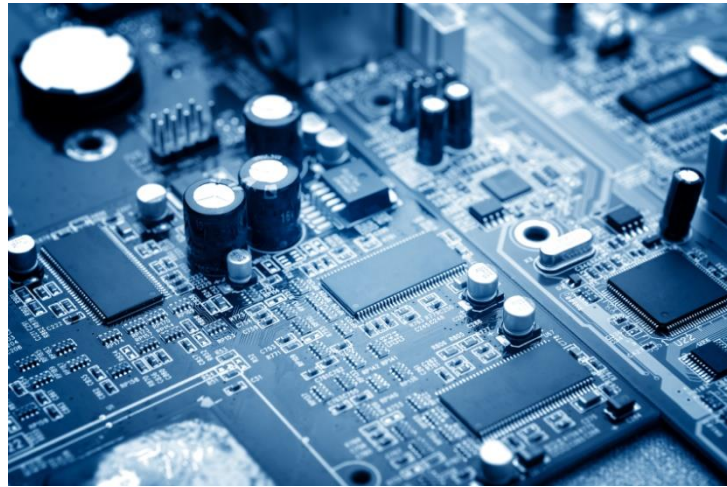





ENEE3304 ELECTRONICS2




Instructor : Mr.Mohammad AL-Jubeh

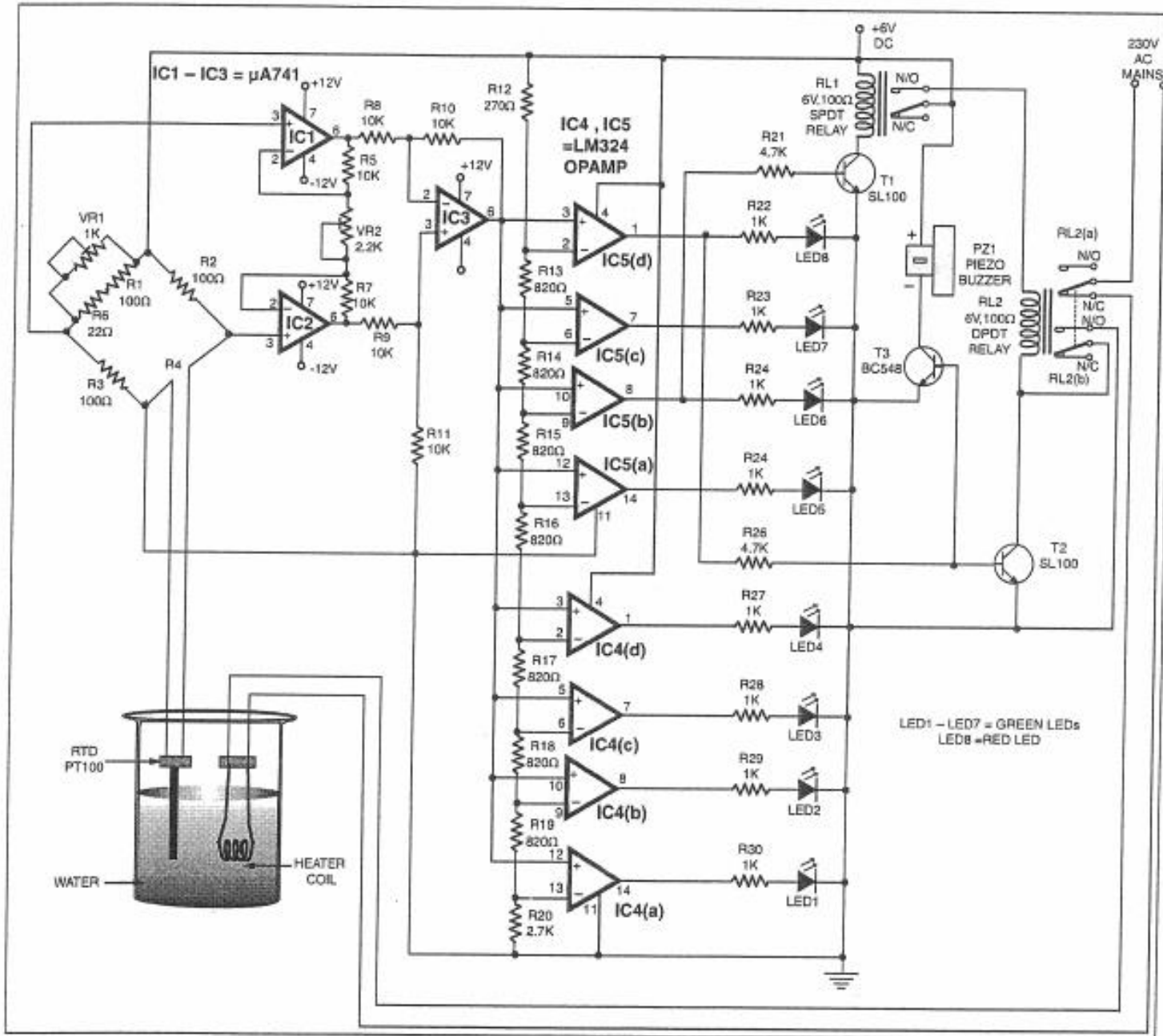
ENEE3304 Project1 : Water Temperature Controller



Power Amplifiers

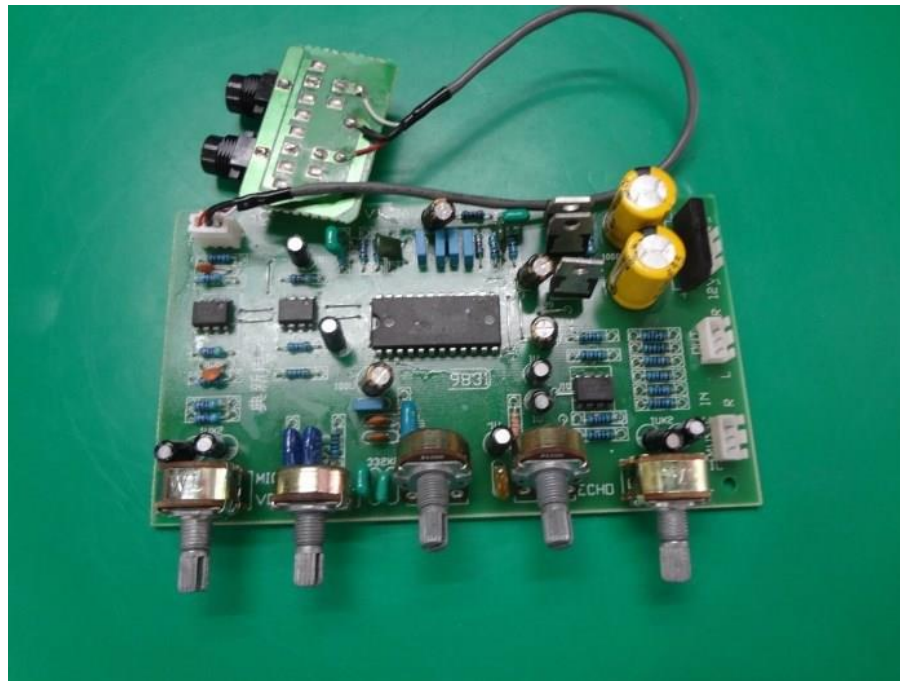

General Audio Amplifier System

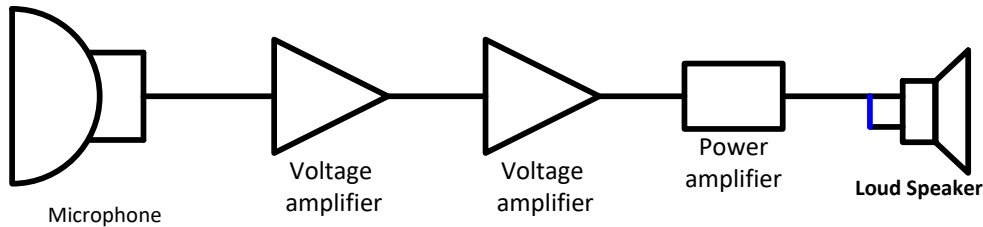

Input transducer : Microphone

Microphone : Used to convert acoustical energy to electrical energy .

Output Transducer : Loud speaker

Loud speaker: Used to convert electrical energy to acoustical energy.


Power Amplifiers

- * A Power amplifier is one that is used to deliver a large amount of power to a load with good efficiency.
- * To do this function , it must be capable of dissipating a large amount of power .
- * It contains a bulky component having large surface area to enhance heat transfer.
- * It is often the last stage of amplifier system.

.

Packaging Schemes


Can/tab is normally the collector (BJT)

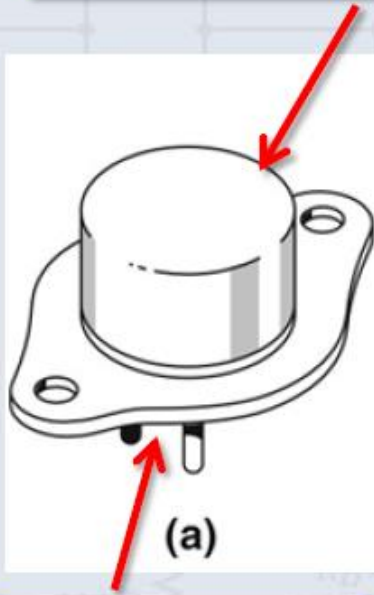

(a)


E & B (BJT)

TO-3

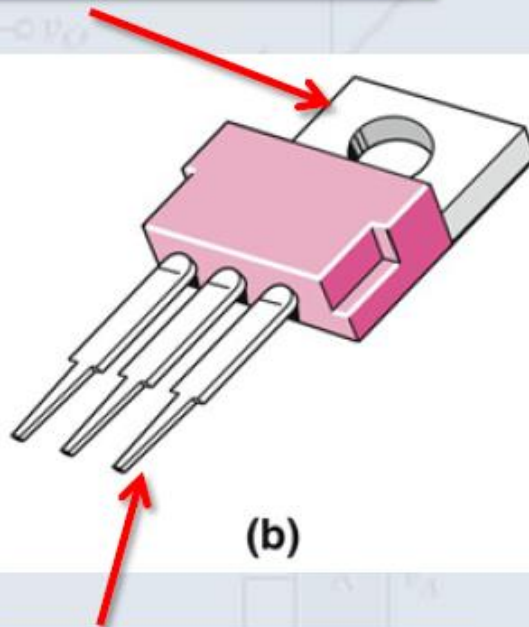

(b)

One of these may also be collector (BJT)

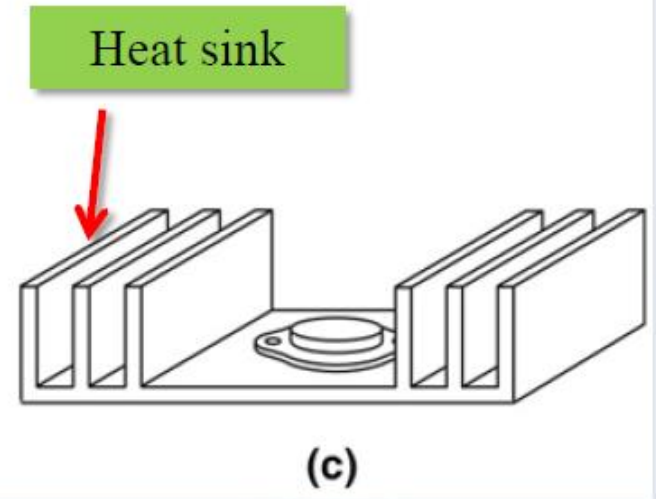


Heat sink

(c)

Power Amplifiers

* It's designed so that the power transistor can operate on the entire range of it's output from saturation to cut off.


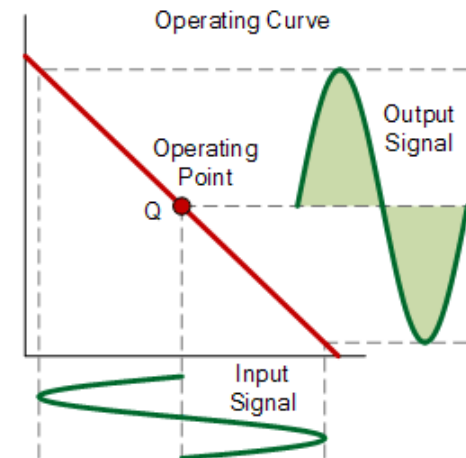
* For a class A power Amplifier, the Q point is designed to meet maximum symmetrical swing



Classes of Power Amplifiers




Power amplifiers are classified according to the percent of time the output transistors are conducting.

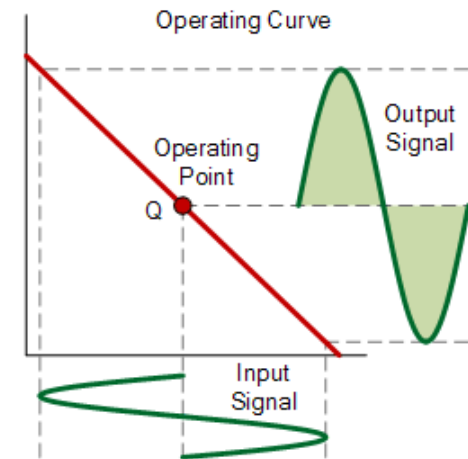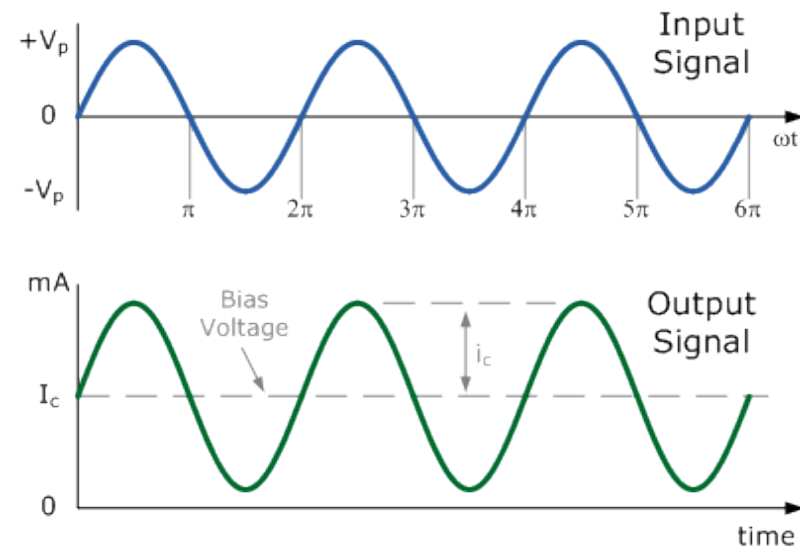1) Class A Power Amplifier: $\theta = 360^\circ$



Classes of Power Amplifiers

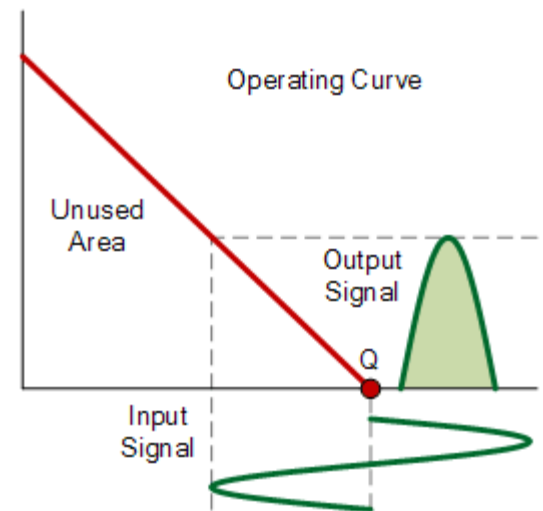
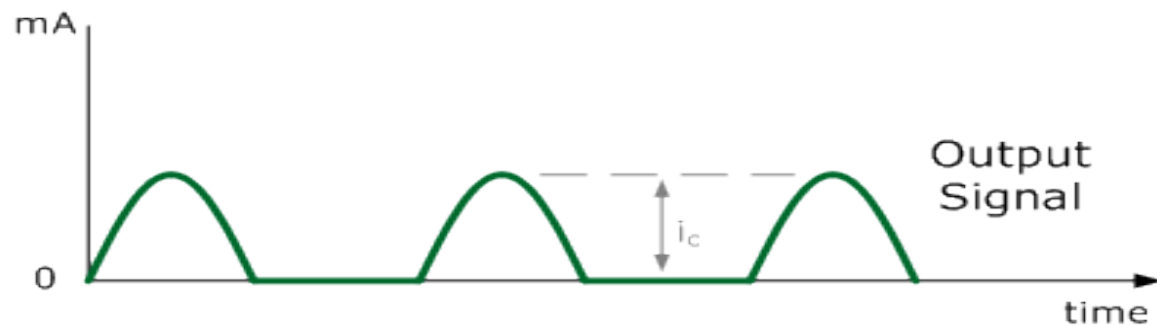
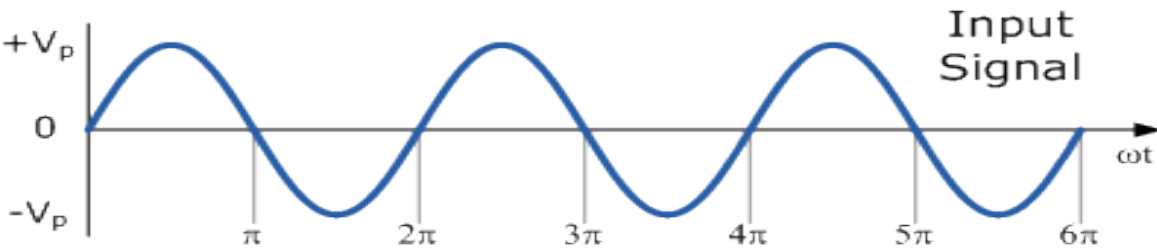
2) Class B Power Amplifier : $\theta = 180^\circ$



Classes of Power Amplifiers

3) Class AB Power Amplifier

$$360^\circ > \theta > 180^\circ$$

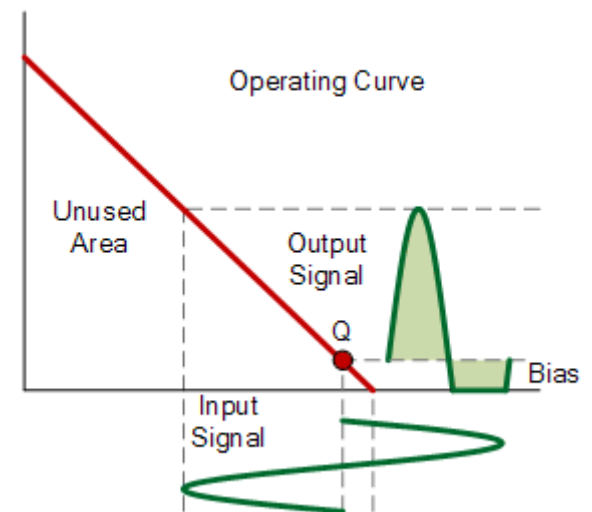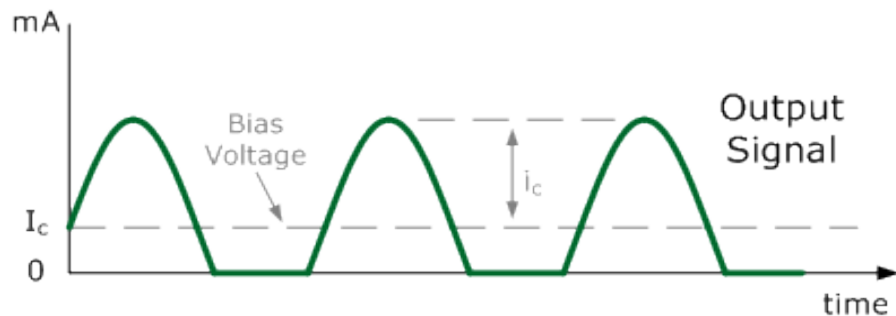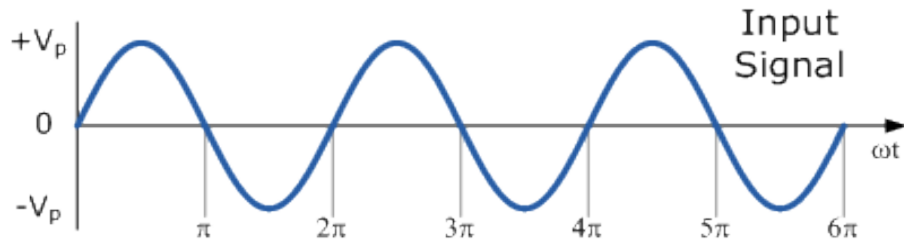


Class A Power Amplifier

Power Calculation :

The average power supplied or dissipated by any linear or nonlinear device is :
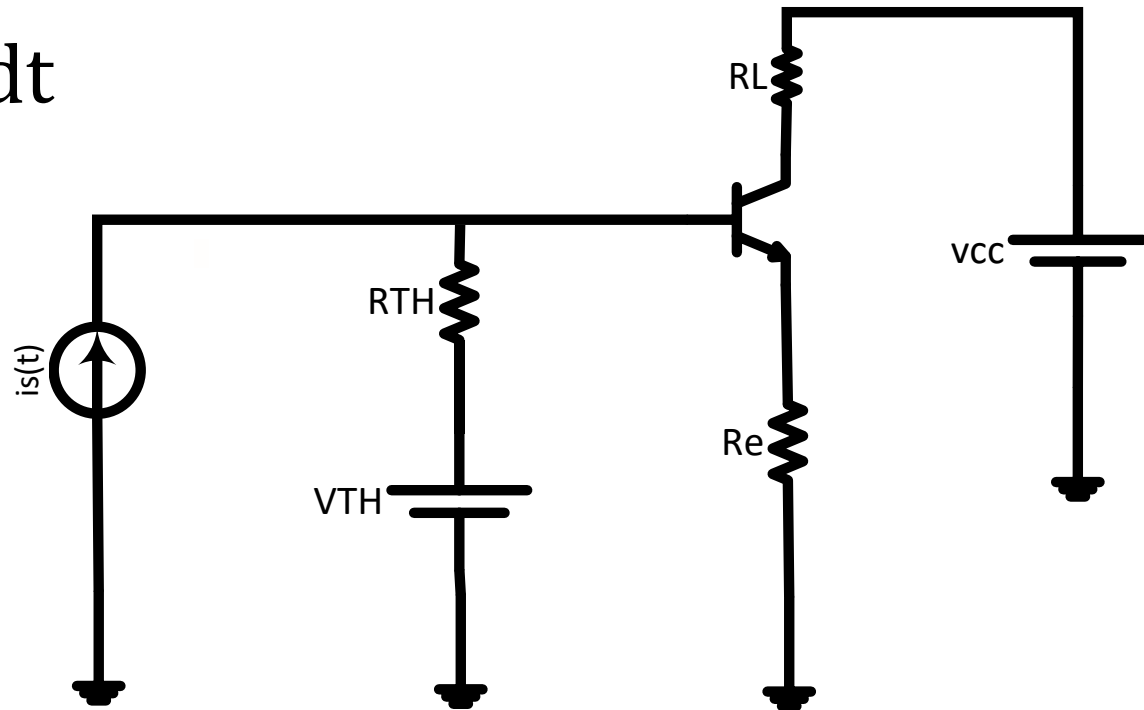
$$P_{av} = \frac{1}{T} \int_0^T V(t) i(t) dt$$



Power Calculation :

$$P_{av} = \frac{1}{T} \int_0^T V(t) i(t) dt$$

$V(t)$: Total voltage across the device

$i(t)$: Total current through the device


$$V(t) = V + v$$

$$v = V_m \cos(\omega t)$$

$$i(t) = I + i$$

$$i = I_m \cos(\omega t)$$
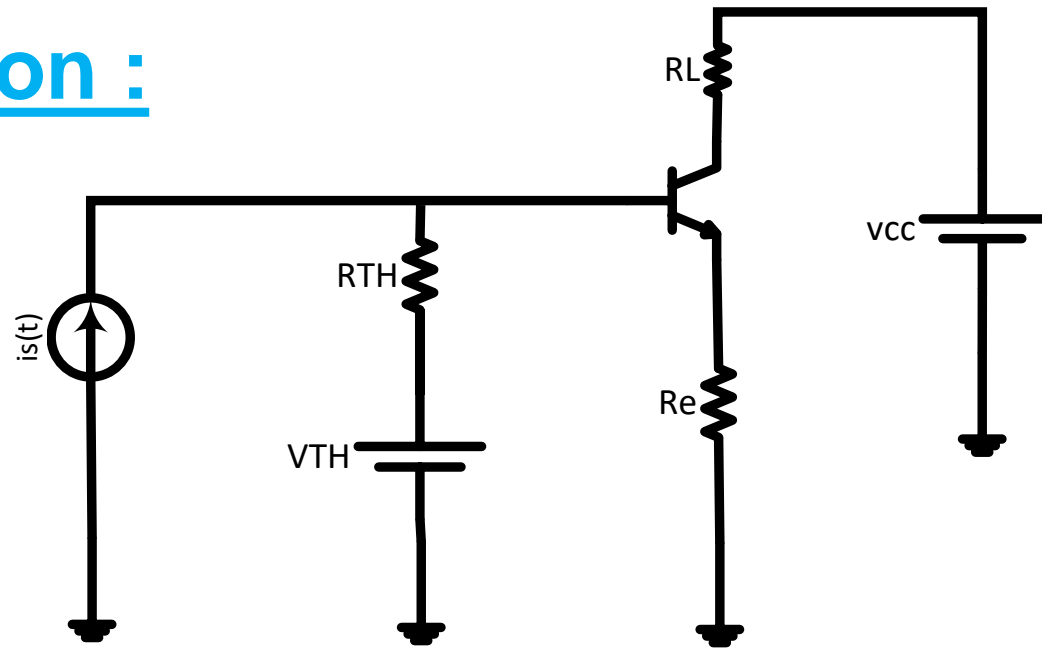
$$P_{av} = \frac{1}{T} \int_0^T (V + v)(I + i) dt$$




The Ac Average Power Dissipated in The Load : $P_{l,ac}$

$$P_{l,ac} = \frac{1}{T} \int_0^T i_c^2(t) R_L dt$$

$$i_c(t) = I_{cm} \cos(\omega t)$$

$$P_{l,ac} = \frac{1}{2} I_{cm}^2 R_L$$

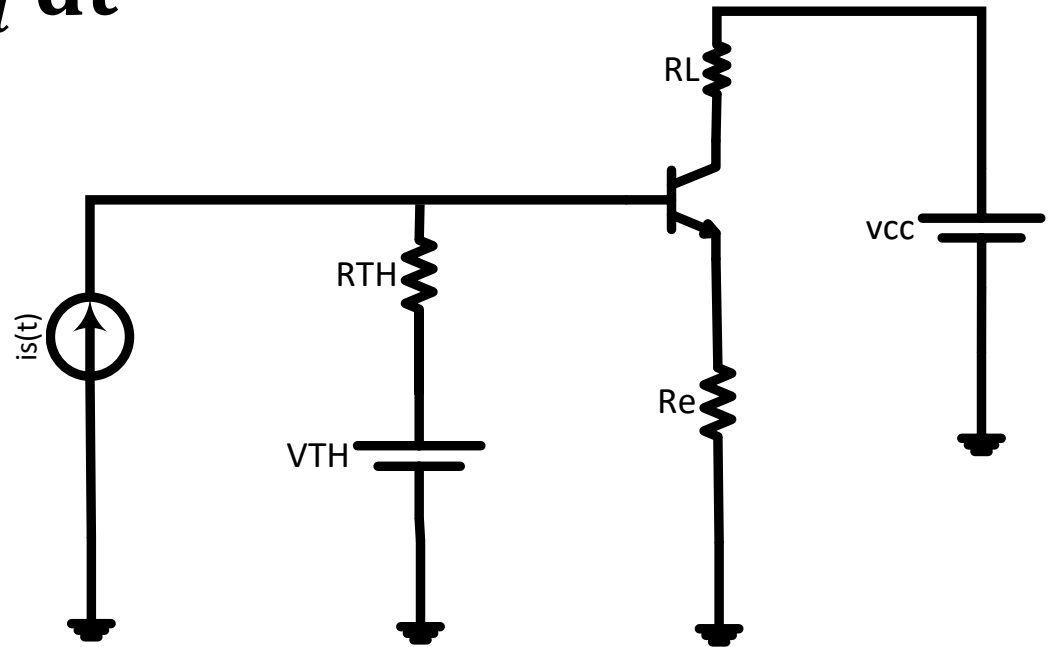

$$(P_{l,ac})_{max} = \frac{1}{2} I_{cm,max}^2 R_L$$

If the Q point is designed to meet maximum symmetrical swing case.


$$I_{cm, max} = I_{CQ}$$

$$(P_{l,ac})_{max} = \frac{1}{2} I_{CQ}^2 R_L$$

$$I_{CQ} = \frac{V_{cc}}{R_{ac+} R_{dc}}$$

$$R_{dc} = R_L + R_e$$

$$R_{ac} = R_L + R_e$$

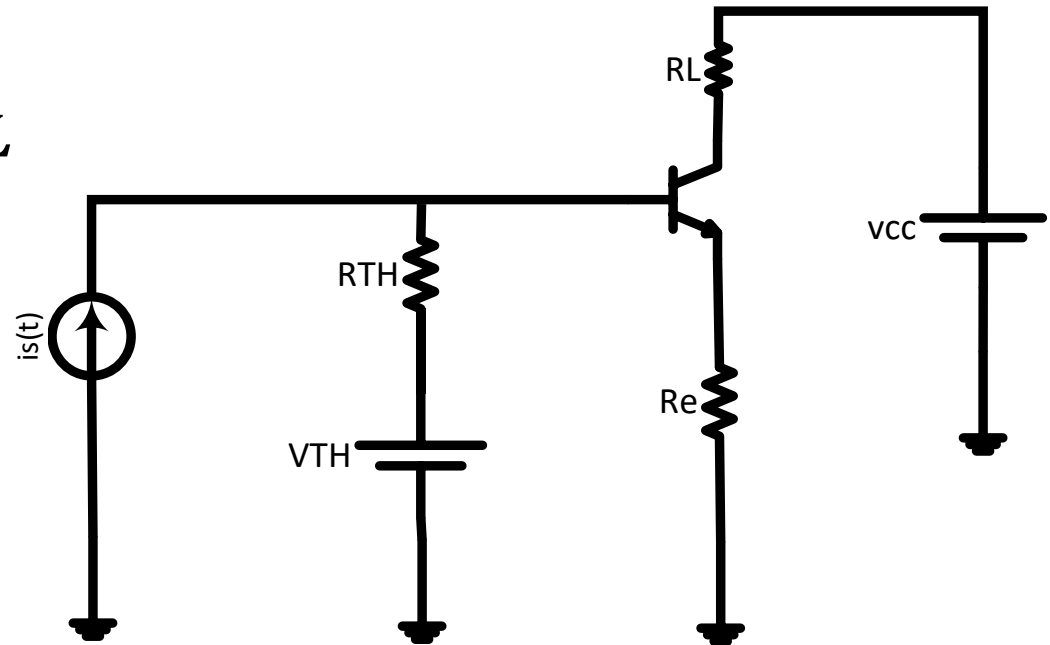


The Average Power Dissipated in The Load

$$I_{CQ} = \frac{V_{CC}}{2(R_L + R_e)}$$

$$(P_{L,ac})_{max} = \frac{V_{CC}^2 R_L}{8(R_L + R_e)^2}$$

If $R_e \ll R_L$
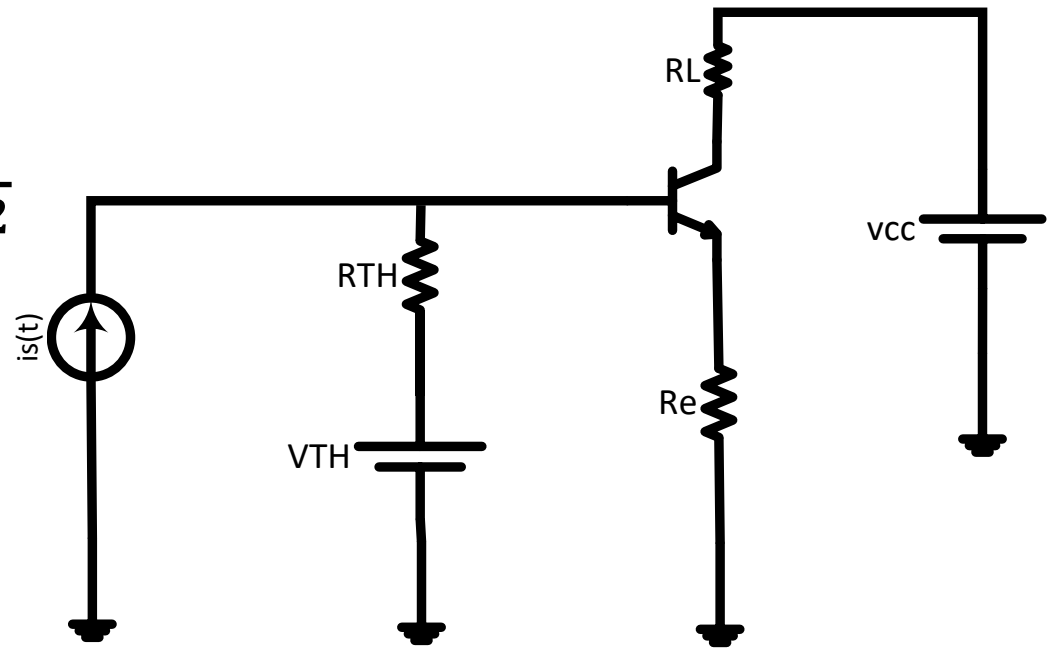
$$(P_{L,ac})_{, max} = \frac{V_{CC}^2}{8 R_L}$$



Average Power Delivered by the Supply : P_{cc}

$$P_{cc} = \frac{1}{T} \int_0^T V_{cc} i_C(t) dt$$

$$P_{cc} = \frac{1}{T} \int_0^T V_{cc} (I_{CQ} + I_{cm} \cos(\omega t)) dt$$


$$P_{cc} = V_{cc} I_{CQ}$$

But : $I_{CQ} = \frac{V_{cc}}{2(R_l + R_e)}$

$$P_{cc} = \frac{V_{cc}^2}{2(R_l + R_e)}$$

If $R_e \ll R_l$


$$P_{cc} = \frac{V_{cc}^2}{2R_l}$$

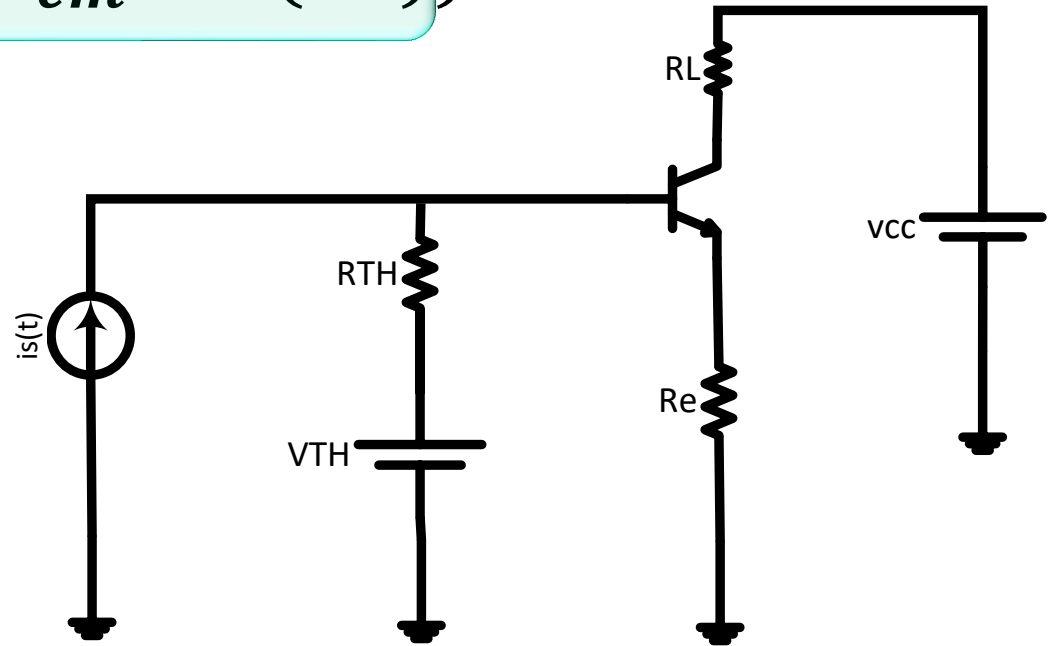

Average Power Dissipated in the Transistor : P_c

$$P_c = \frac{1}{T} \int_0^T V_{CE}(t) i_c(t) dt$$
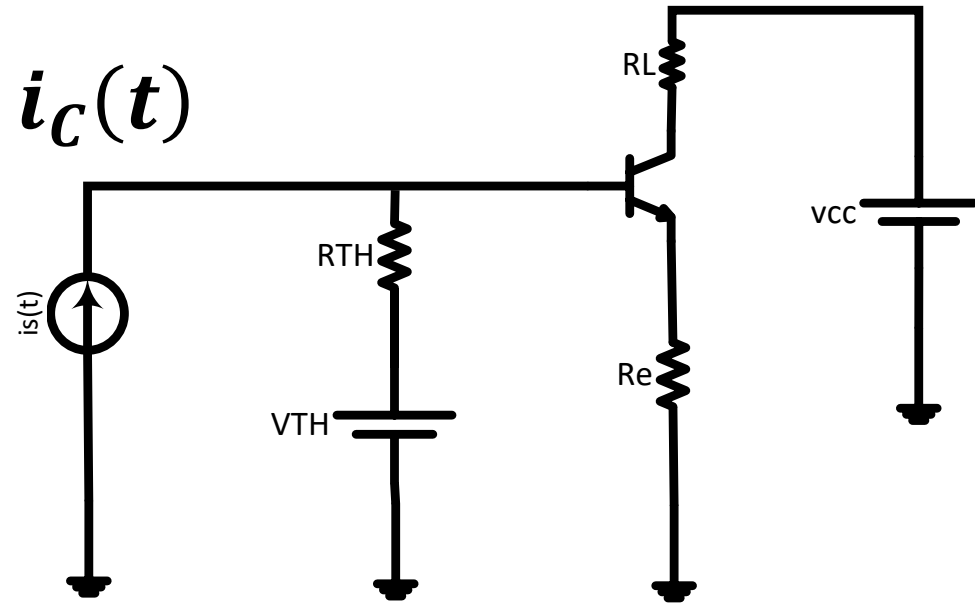
$$V_{CE}(t) = V_{cc} - (R_l + R_e) i_c(t)$$



$$P_c = \frac{1}{T} \int_0^T [V_{cc} - (R_l + R_e) i_c(t)] i_c(t) dt$$

$$P_c = \frac{1}{T} \int_0^T V_{cc} i_c(t) dt - \frac{1}{T} \int_0^T (R_l + R_e) i_c(t)^2 dt$$


P_{cc}

$$\frac{1}{T} \int_0^T i_c(t)^2 dt = I_{CQ}^2 + \frac{I_{cm}^2}{2}$$

Average Power Dissipated in the Transistor

$$P_c = P_{cc} - (R_l + R_e) \left(I_{CQ}^2 + \frac{I_{cm}^2}{2} \right)$$

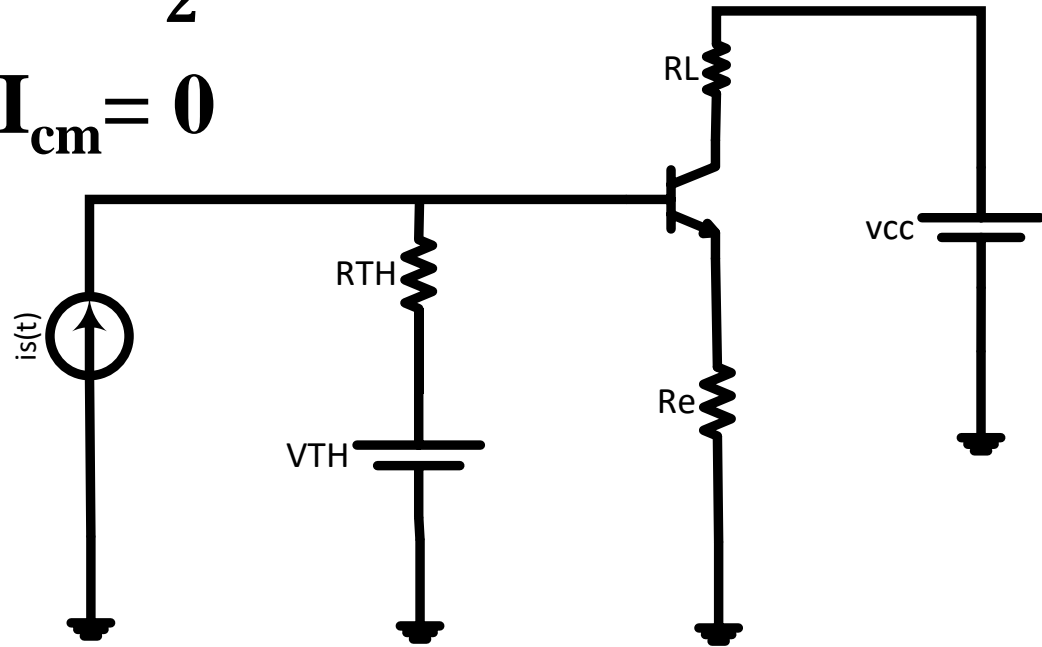$\therefore P_c$ is maximum when $I_{cm} = 0$



$$\therefore P_{c,max} = P_{cc} - (R_l + R_e) (I_{CQ}^2)$$

$$P_{c,max} = \frac{V_{cc}^2}{4(R_l + R_e)}$$

If $R_e \ll R_l$

$$P_{c,max} = \frac{V_{cc}^2}{4R_l}$$

Summary


$$P_{l,ac} = \frac{1}{2} I_{cm}^2 R_L$$

$$\text{If } R_e \ll R_l$$

$$(P_{l,ac})_{max} = \frac{V_{cc}^2}{8R_l}$$

$$P_{c,max} = \frac{V_{cc}^2}{4R_l}$$

$$P_{cc} = \frac{V_{cc}^2}{2R_l}$$

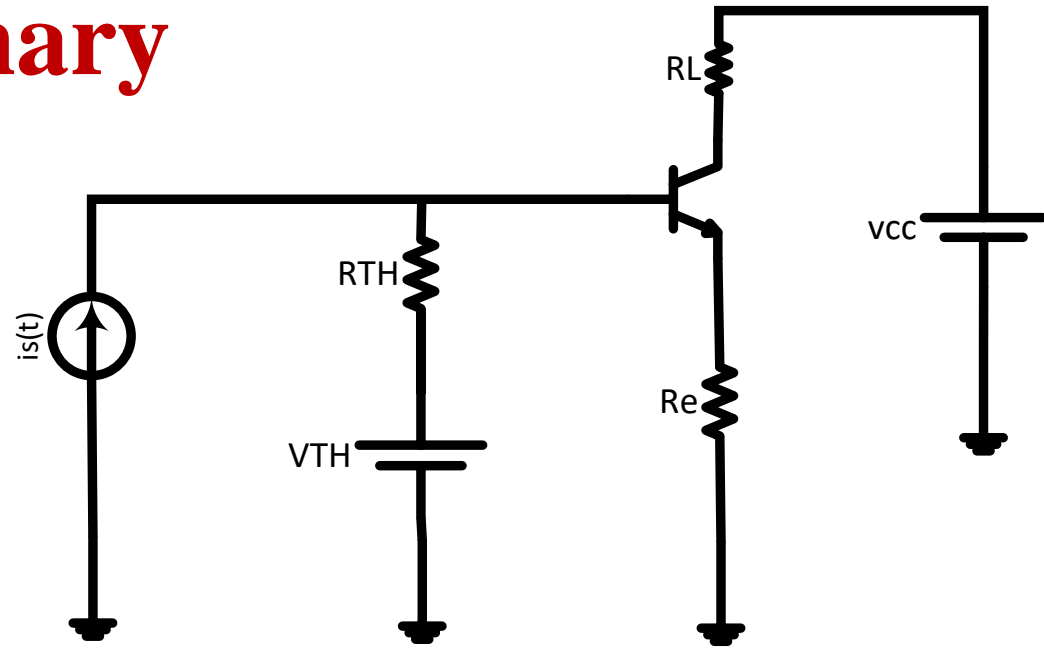

Efficiency: η

$$\eta = \frac{P_{l,ac}}{P_{cc}} * 100\%$$

$$\eta = \frac{\frac{I_{cm}^2 R_l}{2}}{\frac{V_{cc}^2}{2R_l}} * 100\%$$

$$\eta_{max} = \frac{\frac{V_{cc}^2}{8R_l}}{\frac{V_{cc}^2}{2R_l}} * 100\%$$

$$\eta_{max} = 25\%$$

η is max when $I_{cm} = I_{cm, max}$

If the Q point is designed to meet maximum symmetrical swing case.

and $I_{cm, max} = I_{CQ}$

γ : Figure of merit

$$\gamma = \frac{P_{C, \max}}{(P_{l,ac}), \max}$$

$$\gamma = 2$$

$$P_{C, \max} = \frac{V_{cc}^2}{4R_l}$$

$$(P_{l,ac}), \max = \frac{V_{cc}^2}{8R_l}$$

The Class A Common Emitter Power Amplifier with Choke


For Maximum Symmetrical swing:

$$I_{CQ} = \frac{V_{cc}}{(R_{ac} + R_{dc})}$$

$$R_{ac} = R_l$$

$$R_{dc} = R_e$$

$$I_{CQ} = \frac{V_{cc}}{(R_l + R_e)}$$

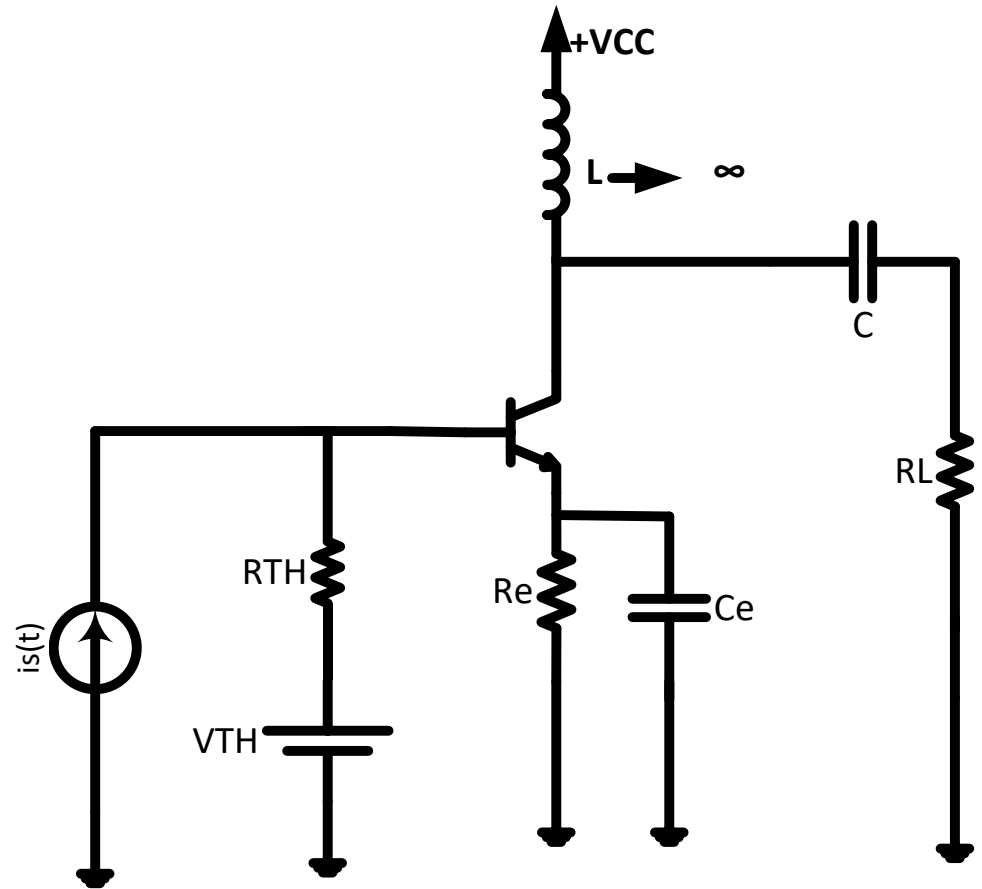


The Class A Common Emitter Power Amplifier with Choke

$$V_{CEQ} = R_{ac} * I_{CQ} = \frac{V_{cc}}{1 + \frac{R_e}{R_l}}$$

If $R_e \ll R_l$

$$I_{CQ} = \frac{V_{cc}}{R_l}$$

$$V_{CEQ} = V_{cc}$$

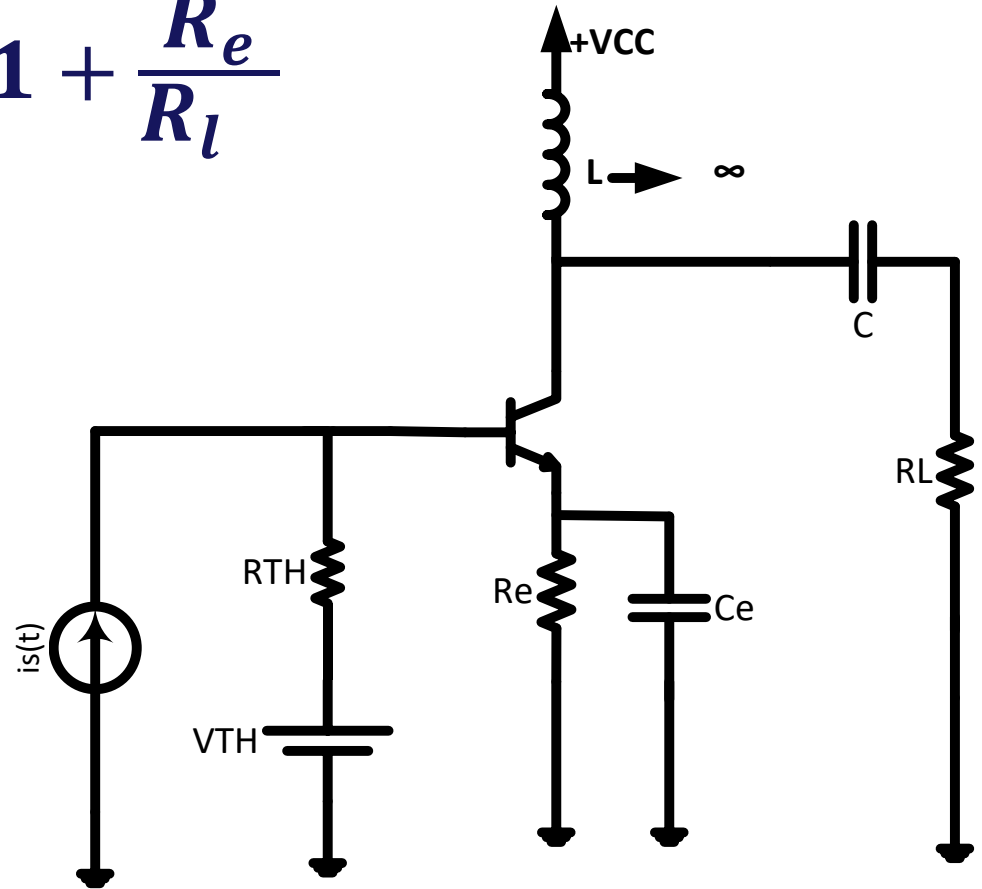

Power Calculation:

$$I_{CQ} = \frac{V_{CC}}{R_L}$$


$$V_{CEQ} = V_{CC}$$

$$P_{l,ac} = \frac{1}{2} I_{lm}^2 R_L$$

$$= \frac{1}{2} I_{cm}^2 R_L$$

$$(P_{l,ac})_{max} = \frac{1}{2} I_{CQ}^2 R_L$$
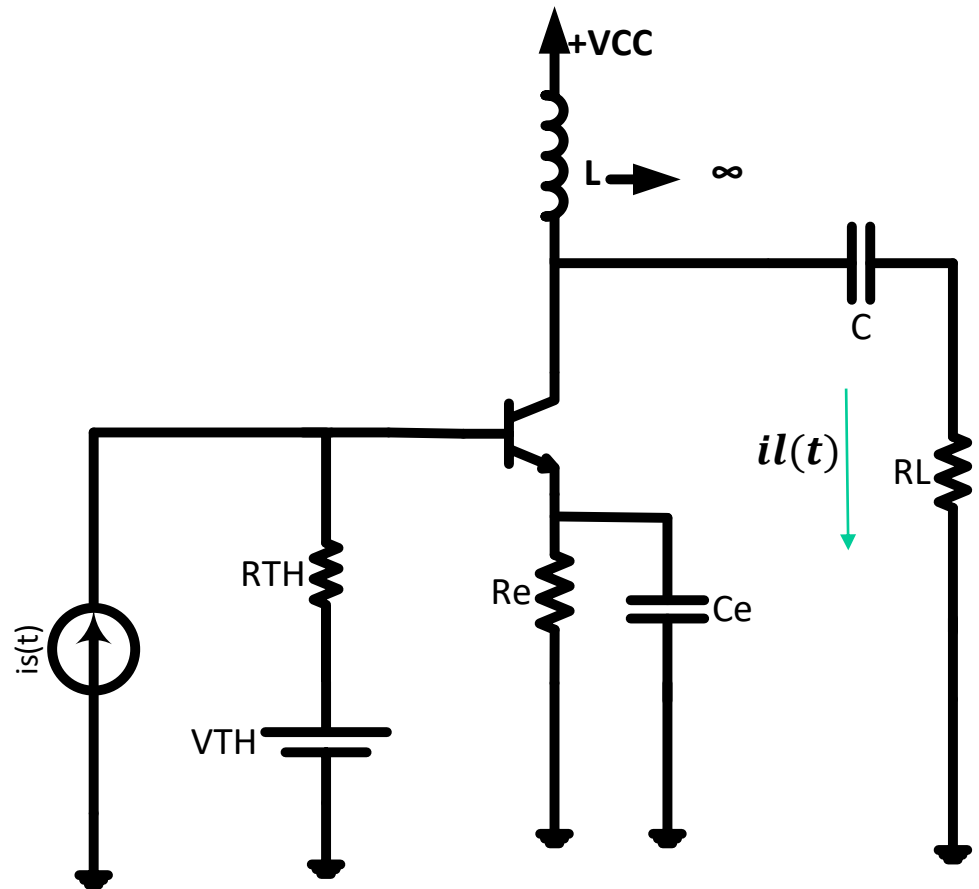
$$(P_{l,ac})_{max} = \frac{V_{CC}^2}{2R_L}$$



Power Calculation:

$$P_{cc} = \frac{1}{T} \int_0^T V_{cc} i_{cc}(t) dt$$

$$i_{cc}(t) = I_{CQ}$$

$$P_{cc} = V_{cc} I_{CQ} = \frac{V_{cc}^2}{R_l}$$


$$P_c = P_{cc} - P_l$$

$$P_c = \frac{V_{cc}^2}{R_l} - \frac{1}{2} I_{cm}^2 R_l$$

$$P_{c,max} = \frac{V_{cc}^2}{R_l} = P_{cc}$$

$$P_{cc} = P_{c,max} = V_{CEQ} I_{CQ}$$

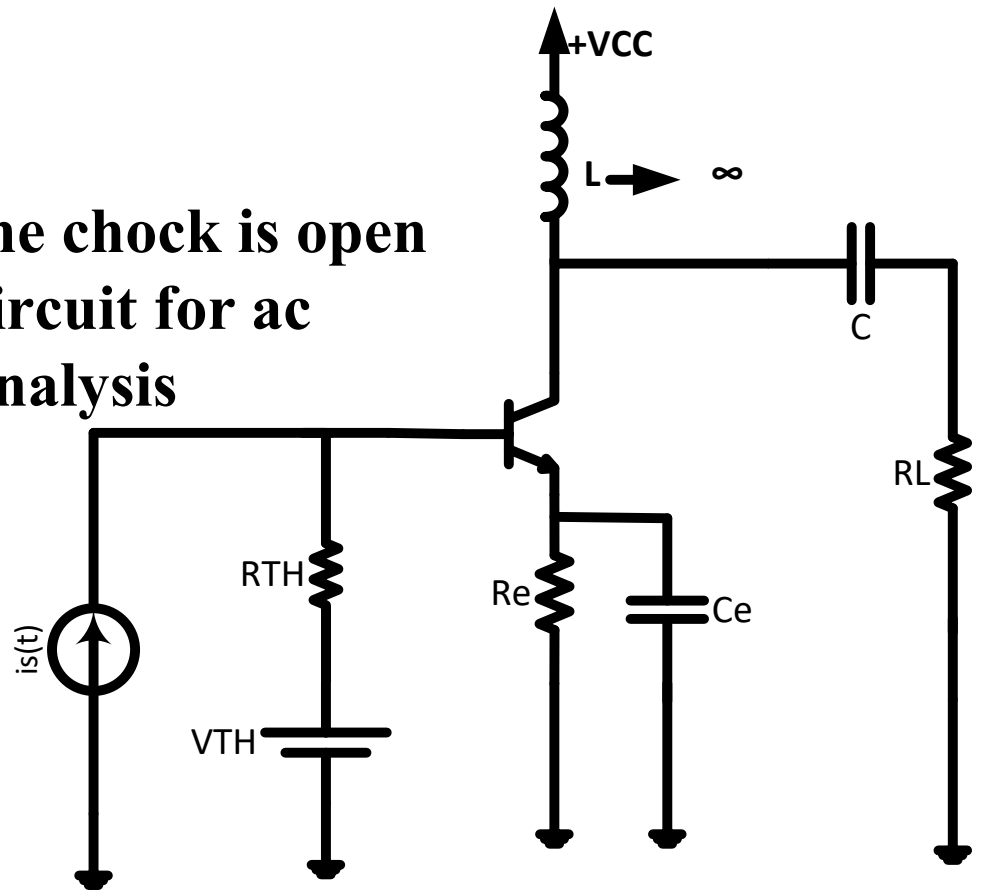the chock is open circuit for ac analysis



Efficiency:

$$\eta = \frac{P_{l,ac}}{P_{cc}} * 100\%$$

$$I_{cm}, max = I_{CQ}$$

$$\eta = \frac{\frac{I_{cm}^2 R_L}{2}}{V_{cc} I_{CQ}} * 100\%$$

$$\eta_{max} = 50\%$$



$$\eta = \frac{\frac{I_{cm}^2 R_L}{2}}{I_{CQ}^2 * R_L} * 100\%$$

$$\gamma = \frac{P_{cmax}}{(P_{l,ac}), max}$$

$$\boxed{\gamma = 2}$$

$$\eta = \frac{1}{2} \left(\frac{I_{cm}}{I_{CQ}} \right)^2 * 100\%$$

Transistor Ratings:


$$i_C(t), \max$$

$$V_{CE}(t), \max = \beta V_{CEO}$$

$$P_{C,\max} = V_{CEQ} \cdot I_{CQ}$$

$$2I_{CQ} < i_C(t), \max$$

$$2V_{CEQ} < \beta V_{CEO}$$

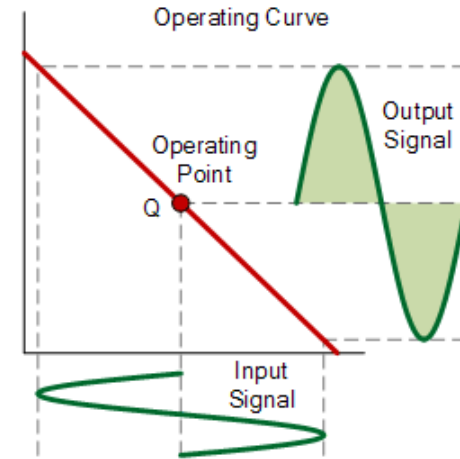

Maximum Symmetrical swing

Transistor Ratings:


EXAMPLE:

A Power Transistor has the following :

$$BV_{CEO} = 40V$$

$$i_C(t), \text{max} = 2A$$

$$P_c, \text{max} = 4W$$

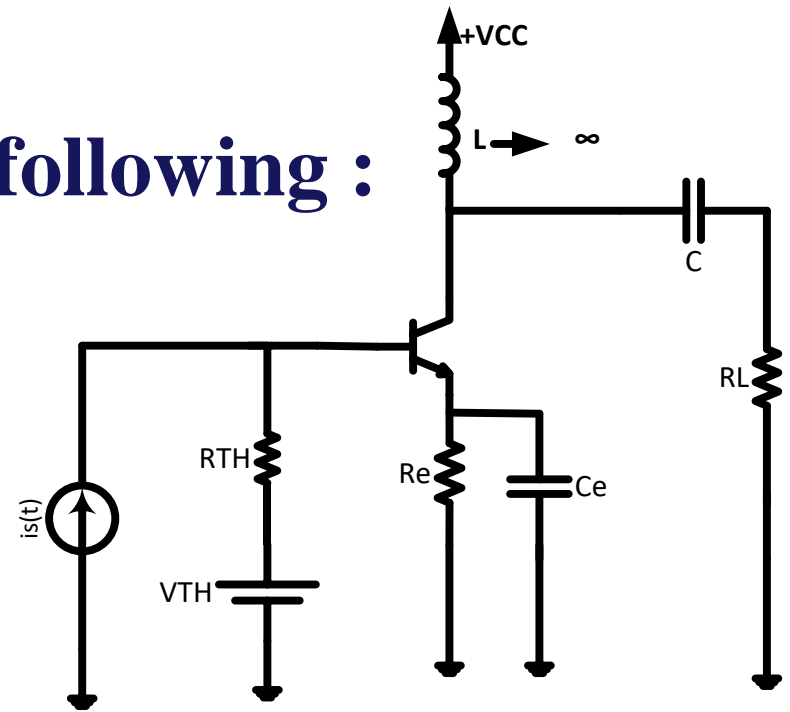

Determine the Q point so that the maximum power dissipated by a 10Ω load



Solution :

$$P_{c, \max} = V_{CEQ} \cdot I_{CQ} \quad (P_{l,ac})_{, \max} = \frac{1}{2} I_{CQ}^2 R_l = 2W$$

$$V_{CEQ} = R_{ac} \cdot I_{CQ} = R_l \cdot I_{CQ} \quad P_{cc} = V_{cc} I_{CQ} = 4W$$

$$I_{CQ} = \sqrt{\frac{P_{c \max}}{R_l}} = 0.63 A$$

$$\eta_{, \max} = 50\%$$

$$V_{CEQ} = \sqrt{P_{c, \max} \cdot R_l} = 6.3V$$

$$I_s \quad 2V_{CEQ} < \beta V_{CEO} = 40V \quad \text{Yes}$$

$$I_s \quad 2I_{CQ} < i_c(t)_{\max} = 2A \quad \text{Yes}$$

$$V_{cc} = V_{CEQ} = 6.3 V$$



Transistor Ratings:

Let us consider the same Problem , But with $i_c(t)_{max} = 1A$

Solution:

$$I_{CQ} = \sqrt{\frac{P_{c\ max}}{R_l}} = 0.63\ A$$

$$V_{CEQ} = \sqrt{P_{c,\ max} \cdot R_L} = 6.3\ V$$

Is $2I_{CQ} < i_c(t)_{max} = 1A$ **NO**

There is A problem !



a) If the Q point left unchanged

$$V_{CEQ} = 6.3V$$

$$V_{CC} = 6.3V$$

$$I_{CQ} = 0.63A$$

$$I_{cm, max} = 0.37A$$

$$(P_{L,ac})_{max} = \frac{1}{2} I_{cm, max}^2 R_L = 0.69W$$


$$P_{CC} = V_{CC} \cdot I_{CQ} = 4W$$

$$\eta_{max} = 17.25\%$$



$$P_{c, max} = V_{CEQ} \cdot I_{CQ} = 4W$$

$$\gamma = 5.8$$

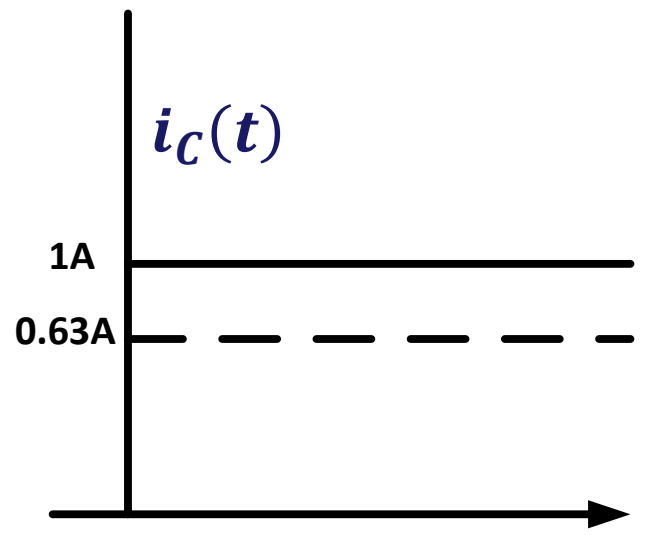

Second solution



Let us consider the same Problem , But with $i_c(t),_{max} = 1A$



b) If we let $ICQ = 0.5 i_c(t),_{max} \rightarrow ICQ = 0.5 A$

$\therefore I_{cm,max} = 0.5 A$

$$(P_{l,ac})_{max} = \frac{1}{2} I_{CQ}^2 R_L = 1.25 W$$


$$V_{CEQ} = R_{ac} \cdot ICQ = 5V$$

$$V_{CC} = V_{CEQ} = 5V$$

$$P_{c,max} = V_{CEQ} \cdot ICQ = 2.5W$$

$$P_{CC} = V_{CC} \cdot ICQ = 2.5W$$

$$\eta_{max} = 50\%$$

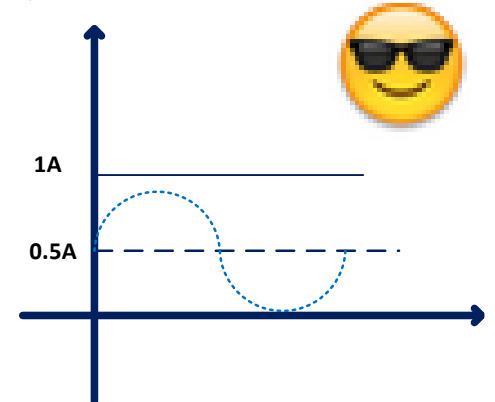

$$\gamma = 2$$



Transformer coupled class A Power Amplifier:

For Maximum symmetrical swing :

$$I_{CQ} = \frac{V_{cc}}{R_{ac} + R_{dc}}$$

$$R_{ac} = N^2 R_L = RL'$$


$$R_{dc} = R_e$$

$$I_{CQ} = \frac{V_{cc}}{RL' + R_e}$$

If $R_e \ll RL'$

$$I_{CQ} = \frac{V_{cc}}{RL'}$$

$$V_{CEQ} = R_{ac} * I_{CQ} = V_{cc}$$

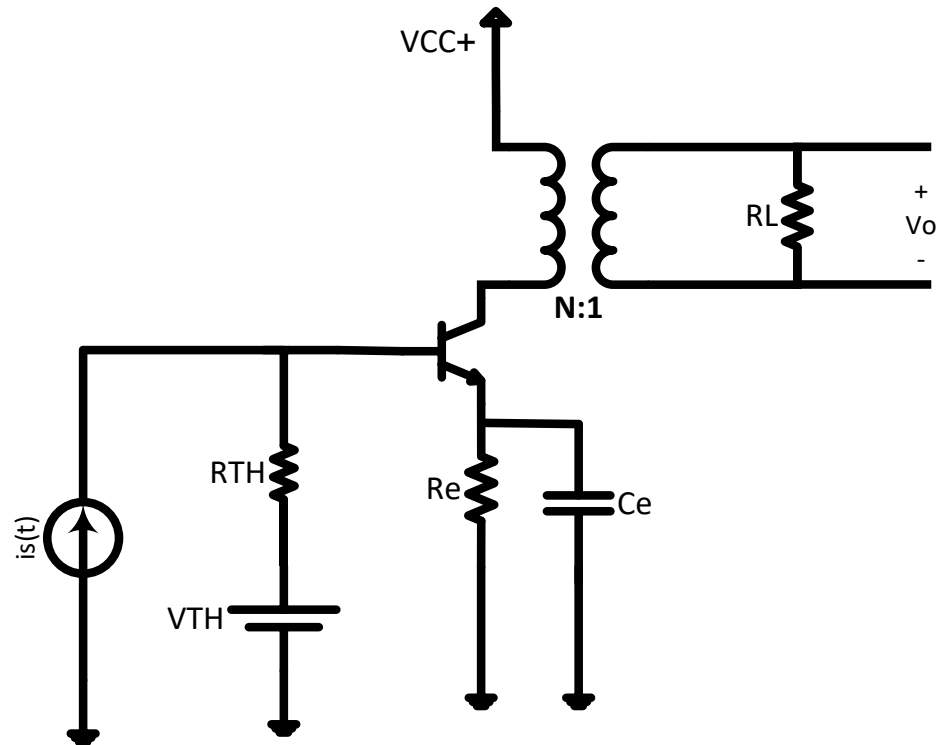

Power Calculation:

$$P_{(l,ac)} = \frac{1}{2} I_{lm}^2 R_l$$


$$I_{lm} = N \cdot I_{cm}$$

$$\therefore PL.ac = \frac{1}{2} I_{cm}^2 R_l'$$

$$(PL.ac), max = \frac{1}{2} I_{cm,max}^2 R_l'$$

$$(PL.ac), max = \frac{1}{2} I_{CQ}^2 R_l'$$
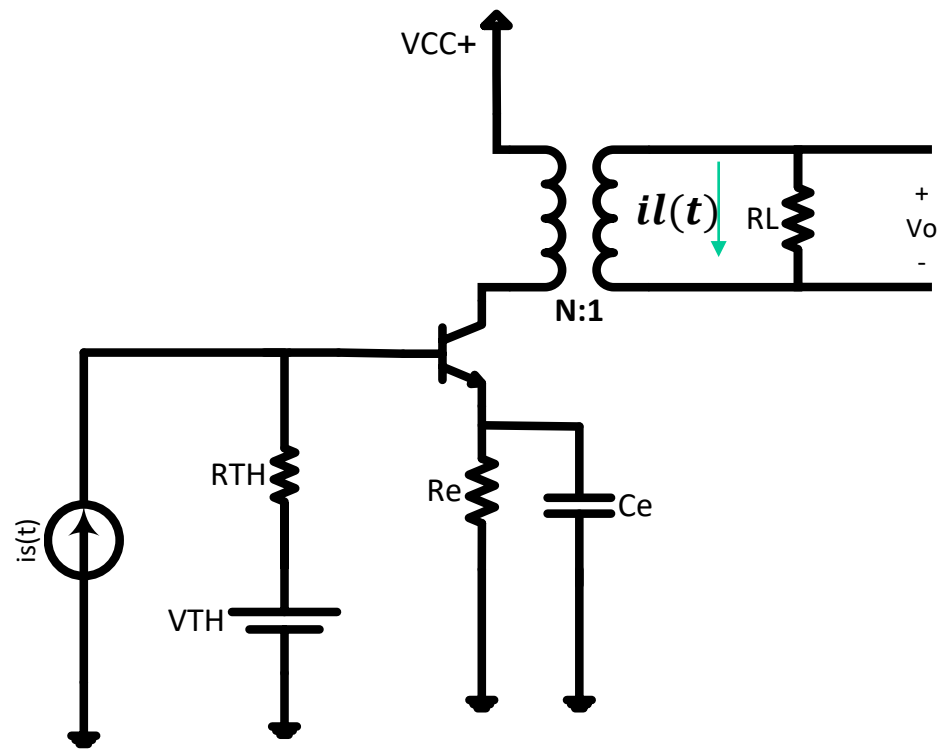
$$P_{(l,ac),max} = \frac{V_{cc}^2}{2R_l'}$$




Power Calculation:

$$P_{cc} = \frac{1}{T} \int_0^T V_{cc} i_{cc}(t) dt$$

$$i_{cc}(t) = i_c(t) = I_{CQ} + I_{cm} \cos \omega t$$
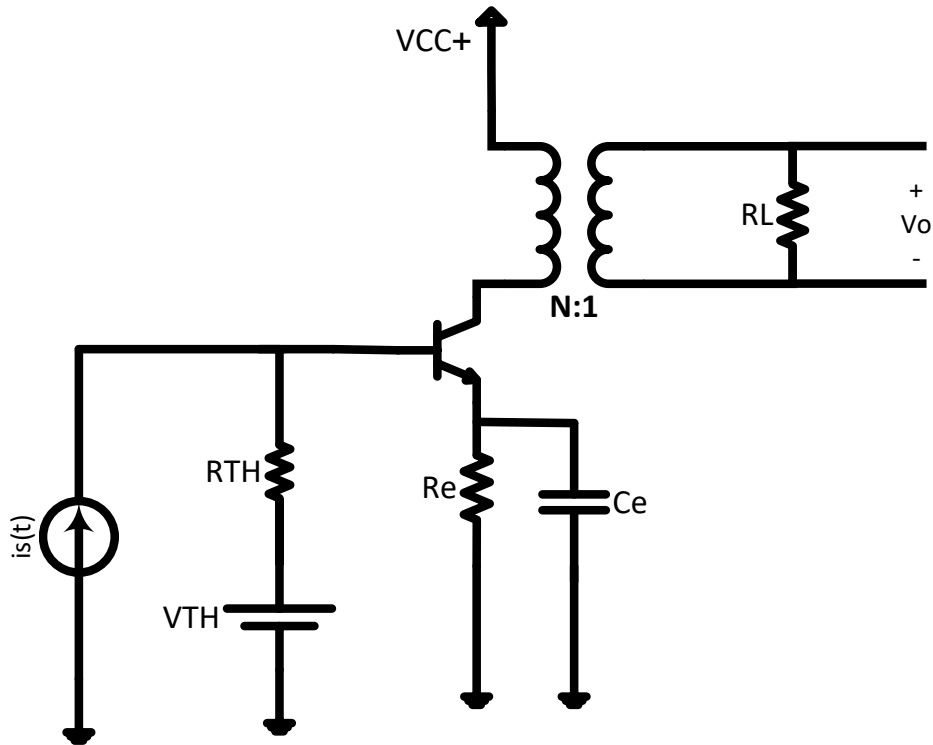
$$P_{cc} = V_{cc} I_{CQ} = \frac{V_{cc}^2}{R_l'} = I_{CQ}^2 R_l'$$



$$P_c = P_{cc} - P_{l,ac}$$

$$P_c = P_{cc} - \frac{1}{2} I_{cm}^2 R_l'$$

$$P_{c,max} = \frac{V_{cc}^2}{R_l'} = P_{cc}$$

Power Calculation:

$$\eta = \frac{P_{l,ac}}{P_{cc}} * 100\%$$

$$I_{cm,max} = I_{cQ}$$

$$\eta_{,max} = 50\%$$



$$\eta = \frac{\frac{I_{cm}^2 R_l'}{2}}{I_{cQ}^2 * R_l'} * 100\%$$

$$\gamma = \frac{P_{C,max}}{(PL, ac), max}$$

$$\eta = \frac{1}{2} \left(\frac{I_{cm}^2}{I_{cQ}^2} \right) * 100\%$$

$$\gamma = 2$$

Ratings:

EXAMPLE:

A Power Transistor has the following :

$$\mathbf{BV_{CEO} = 40V}$$

$$\mathbf{P_c , max = 4W}$$

$$\mathbf{ic(t),max = 1A}$$

Determine the Q point so that the maximum power dissipated by a 10 Ω load.

Solution :

$$P_c , max = V_{CEQ} \cdot I_{CQ} \cdot$$

$$V_{CEQ} = R_{ac} \cdot I_{CQ}$$

$$V_{CEQ} = R_l' \cdot I_{CQ}$$

$$I_{CQ} = \sqrt{\frac{P_{c \max}}{R_l'}} = (0.63/N) A$$

$$V_{CEQ} = \sqrt{P_{c, \max} \cdot R_l'} = (6.3N) V$$

How to choose N ?

The Q point must satisfy :

$$2V_{CEQ} < \beta V_{CEO} = 40V$$

$$2V_{CEQ} = 12.6N < 40 V$$



$$3.17 > N$$

$$2I_{CQ} < i_c(t), \max = 1A$$

$$2I_{CQ} = (1.26/N) < 1A$$



$$N > 1.26$$

$$3.17 > N > 1.26$$

a) Let $N = 2$

$$I_{CQ} = \frac{0.63}{2} = 0.315\text{A}$$

$$V_{CEQ} = 12.6\text{ V}$$

$$(P_{l,ac})_{max} = \frac{1}{2} I_{CQ}^2 R_{l'} = 2\text{W}$$

$$P_{cc} = V_{cc} I_{CQ} = 4\text{W}$$

$$\eta_{,max} = 50\%$$

b) Let $N=3$

$$I_{CQ} = 0.21\text{A}$$

$$V_{CEQ} = 18.9\text{ V}$$

$$V_{cc} = 18.9\text{ V}$$

$$(P_{l,ac})_{max} = \frac{1}{2} I_{CQ}^2 R_{l'} = 2\text{W}$$

$$P_{c,max} = V_{CEQ} I_{CQ} = 4\text{W}$$

$$\eta_{,max} = 50\%$$

Class A Output stage Power Amplifier:

The output stage is designed so that :


$$V_o = 0, I_L = 0, V_i = 0.7V$$

$$I_{E1} = I, V_{CEQ1} = V_{CC}$$


$$V_o(t) = V_i(t) - V_{BE}(t)$$

$$V_o(t) \approx V_i(t) - V_{BE}$$

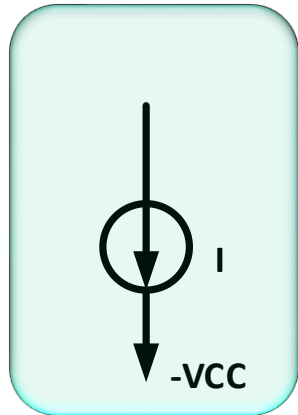Q1 is common collector amplifier
DELIVER A LARGE AMOUNT
OF POWER



Current source

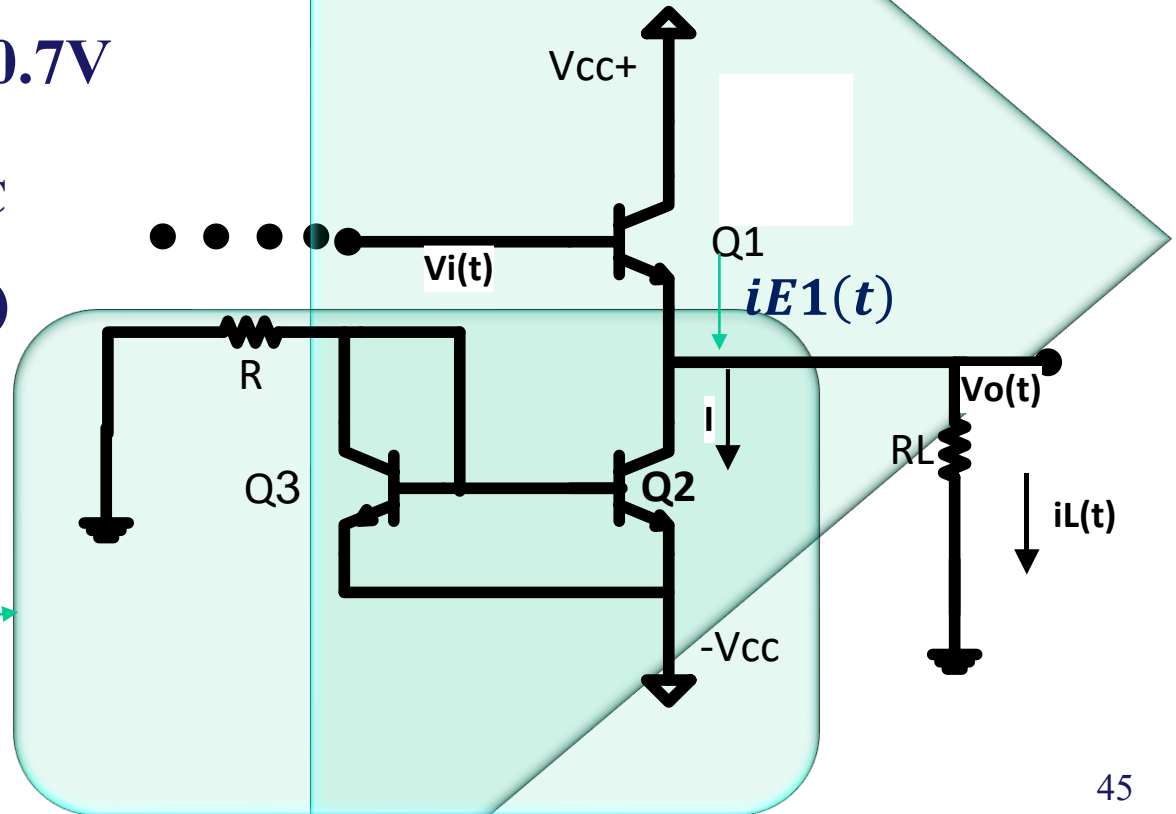

Transfer Curve:

$$V_o(t) = V_i(t) - V_{BE}$$

$$V_o(t) = V_{cc} - V_{CE1}(t)$$

$$V_o(t), \text{max} = V_{cc} - V_{CE1, \text{sat}}$$

(When T1 enters Saturation)

$$V_o(t) = V_{CE2}(t) - V_{cc}$$

$$V_o(t), \text{min} = V_{CE2, \text{sat}} - V_{cc}$$


(When T enters Saturation)

Or:

$$V_o(t), \text{min} = -I_{RL}$$

(When T1 enters Cutoff)

$$i_{E1}(t) = 0$$

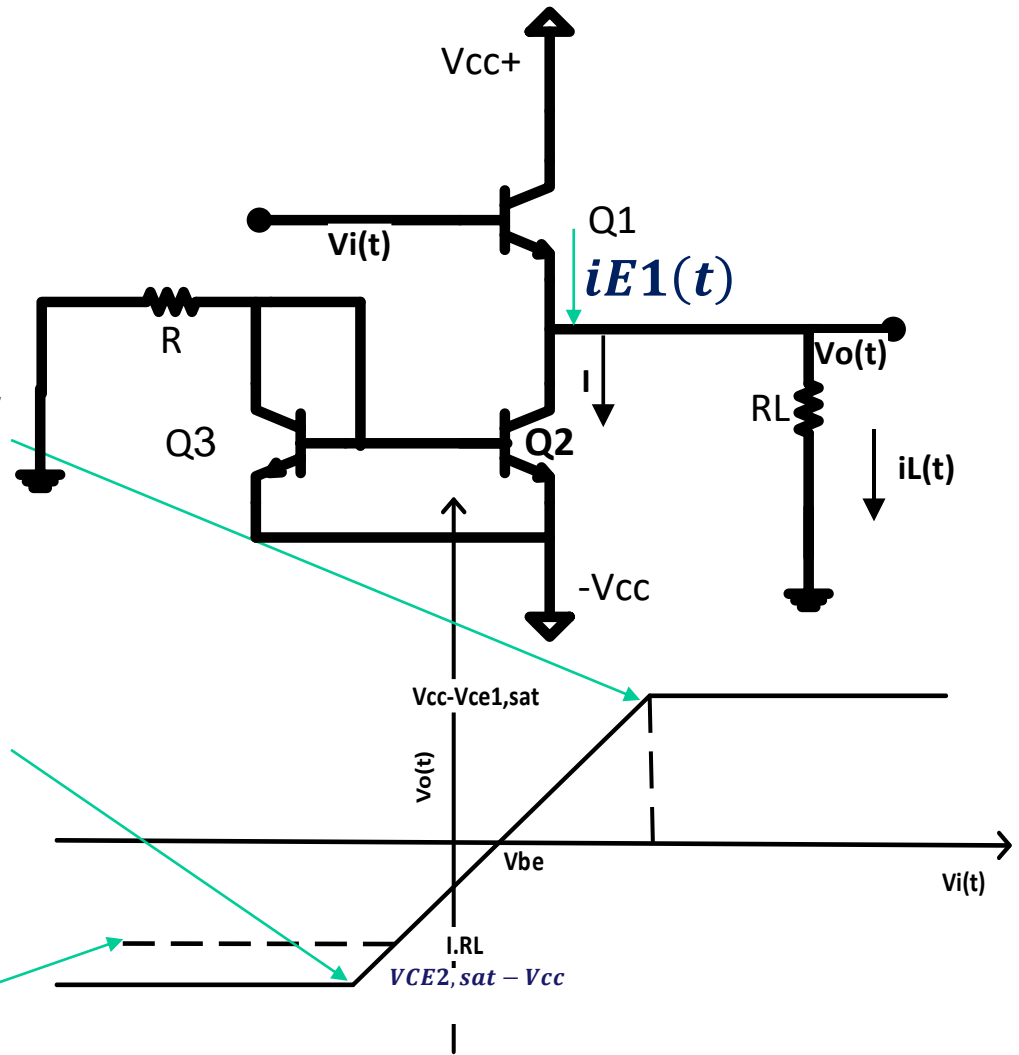



When Q2 gets into saturation:
 $V_{o, \text{min}} = -V_{cc} + V_{ce, \text{sat}}$
 OR
 When Q1 gets into cut-off:
 $i_L = i_{E1} - I \rightarrow i_{E1} = 0 \rightarrow i_L = -I$
 $V_{o, \text{min}} = i_L * R_L = -I * R$

To allow Maximum symmetrical swing :

$$-IRL = -V_{CC} + V_{CE2, sat}$$





$$-IRL \cong -V_{CC}$$

$$\therefore I = \frac{V_{CC}}{RL}$$

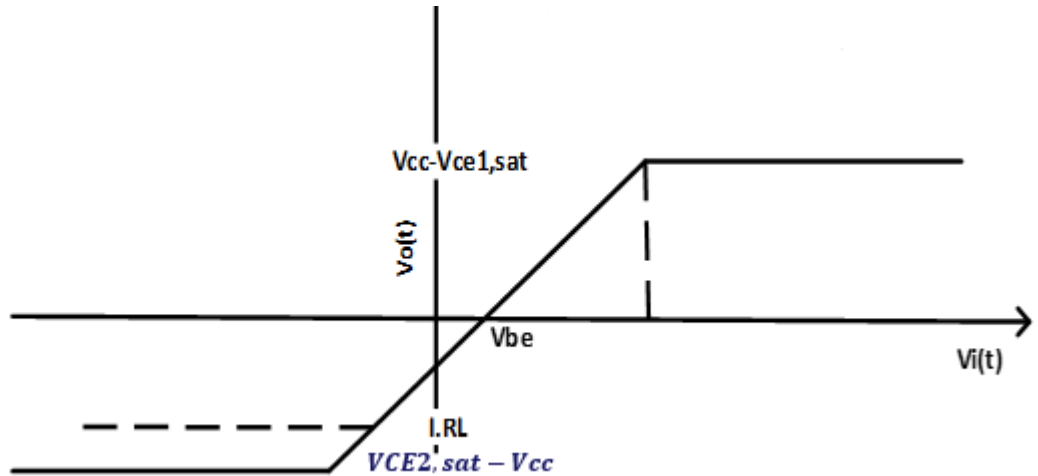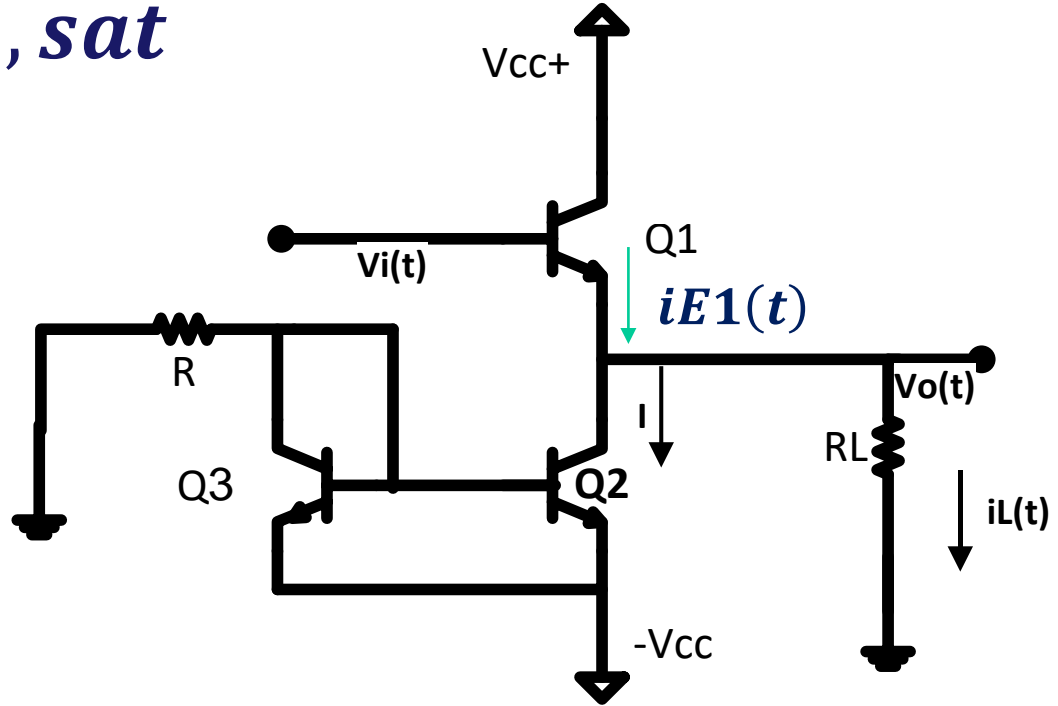

Signal Wave forms: $V_{CE, sat} \approx 0V$

Maximum possible swing

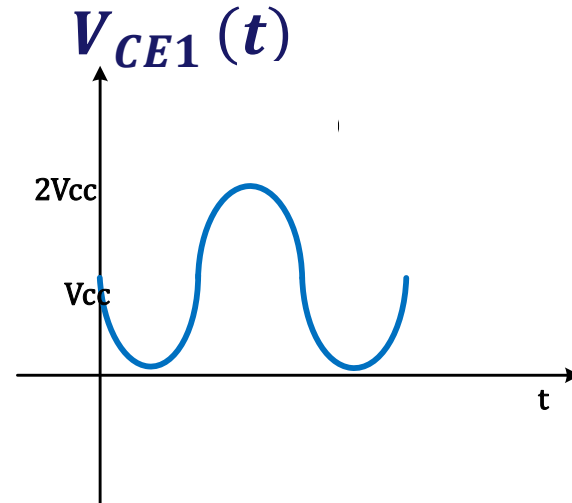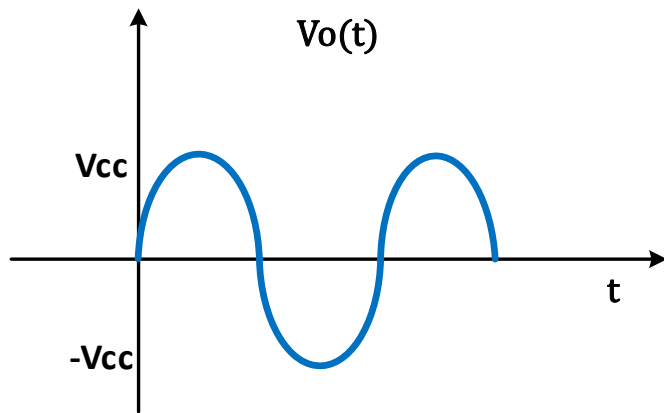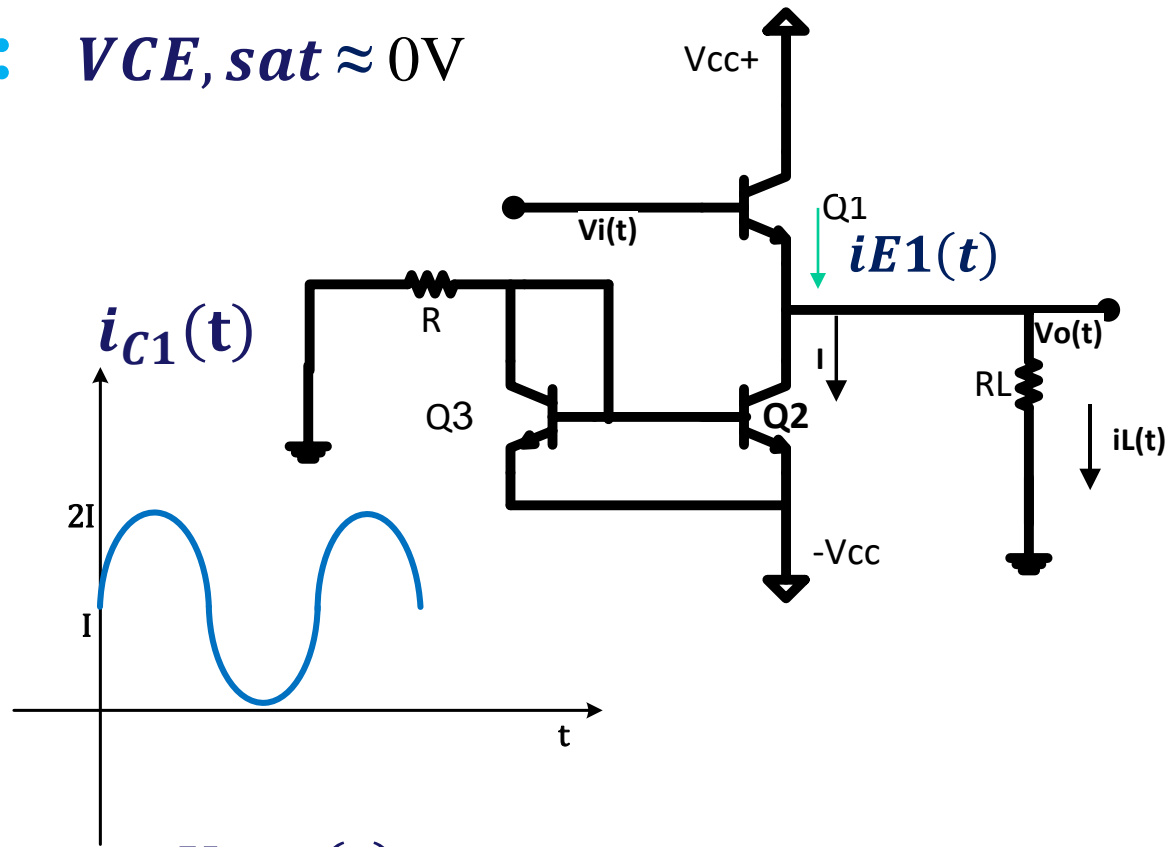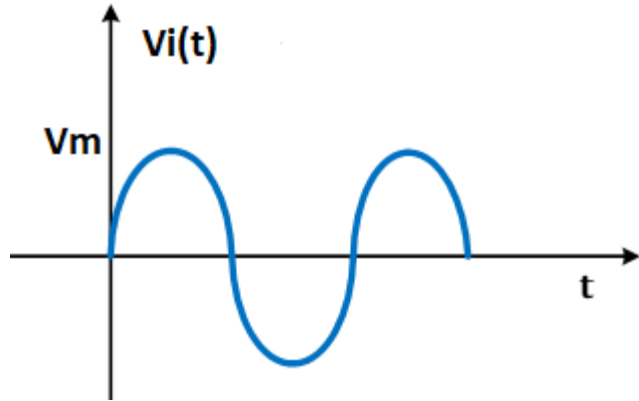

Signal Wave forms:

$$i_{C1}(t) \approx i_{E1}(t)$$

$$V_{CE, sat} \approx 0V$$

$$i_{E1}(t) = I + i_L(t)$$


$$i_{E1}(t), max = I + i_L(t), max$$

$$i_{E1}(t), max = I + \frac{V_o(t), max}{RL}$$

$$i_{E1}(t), max = I + \frac{V_{cc}}{RL}$$

$$i_{E1}(t), max = I + I$$

$$i_{E1}(t), max = 2I$$

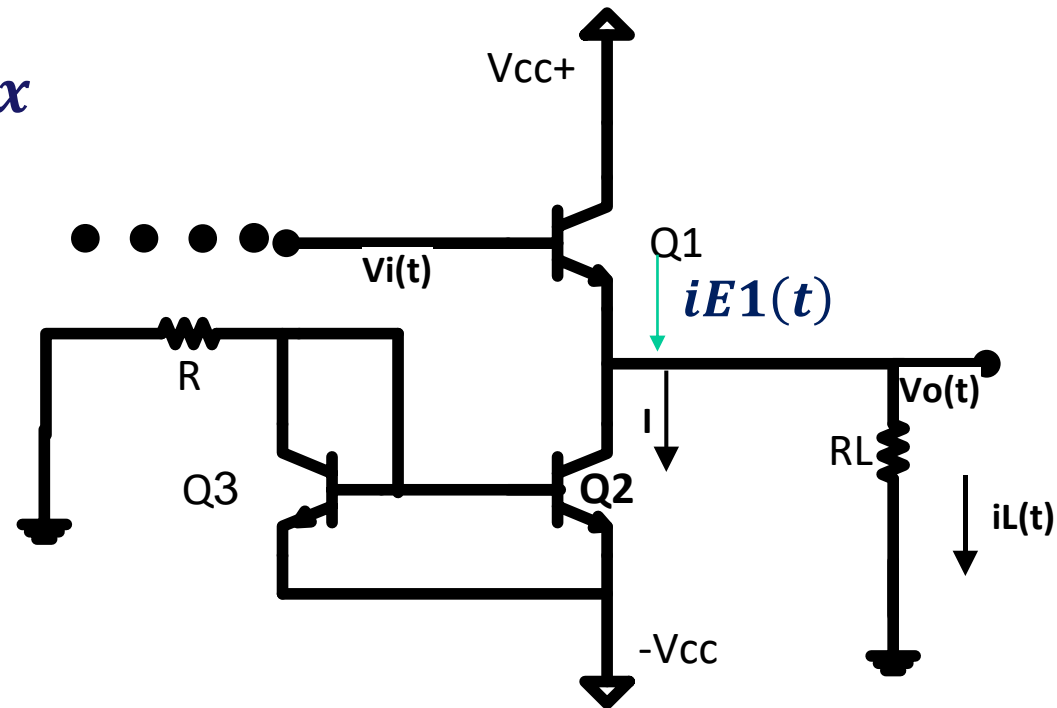


$$V_{CE, sat} \approx 0V$$

$$V_{CE1}(t) = V_{cc} - V_o(t)$$


$$V_{CE1}(t), max = V_{cc} - V_o(t), min$$

$$V_{CE1}(t), max = 2V_{cc}$$

$$V_{CE1}(t), max = 2V_{cc}$$

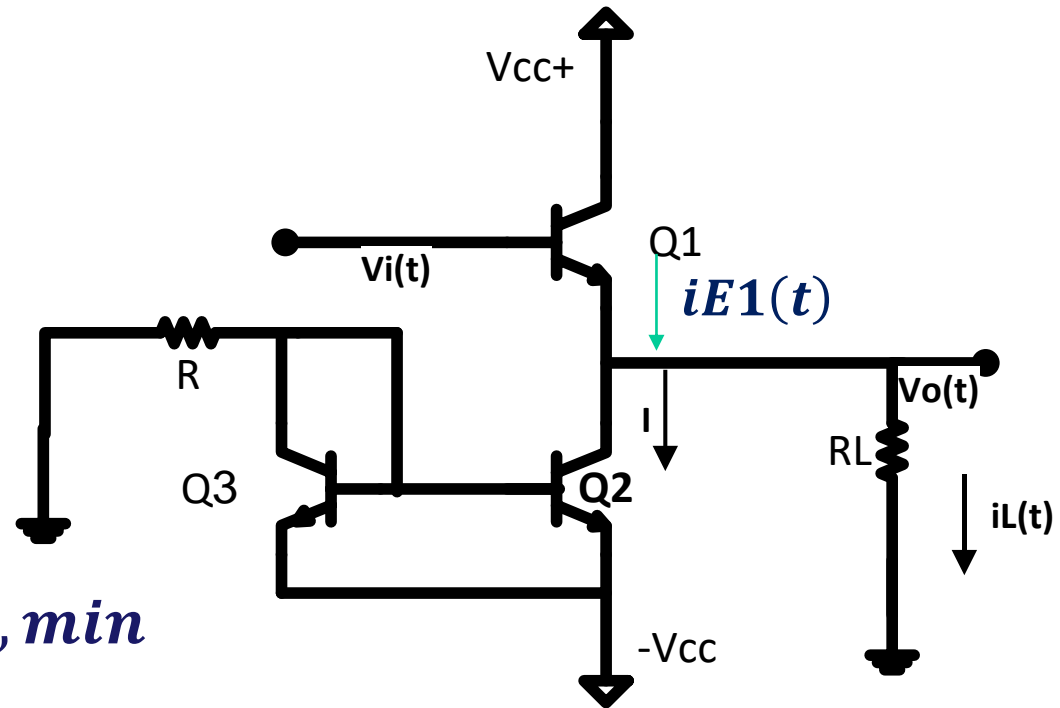

Power Calculation:

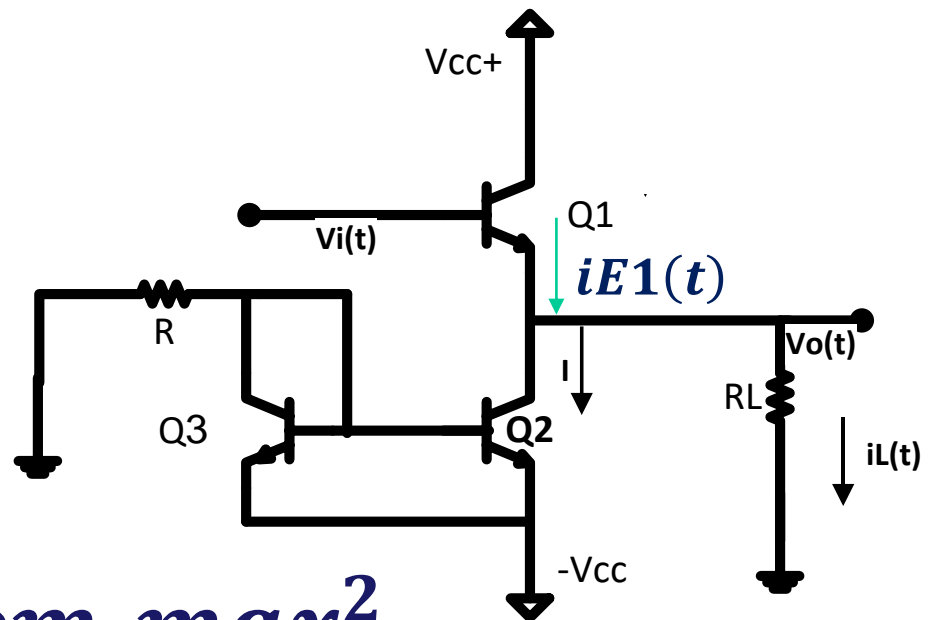

$$(PL, ac) = \frac{V_{om}^2}{2RL}$$

$$(PL, ac), max = \frac{V_{om, max}^2}{2RL} = \frac{V_{cc}^2}{2RL}$$

$$P_{cc} = P_{cc1} + P_{cc2}$$


$$P_{cc} = 2V_{cc} * I$$

$$\eta, max = \frac{(PL, ac), max}{P_{cc}} * 100\%$$


$$\eta = \frac{PL, ac}{P_{cc}} * 100\%$$

$$\eta, max = 25\%$$


Class B Push-Pull Power Amplifier:

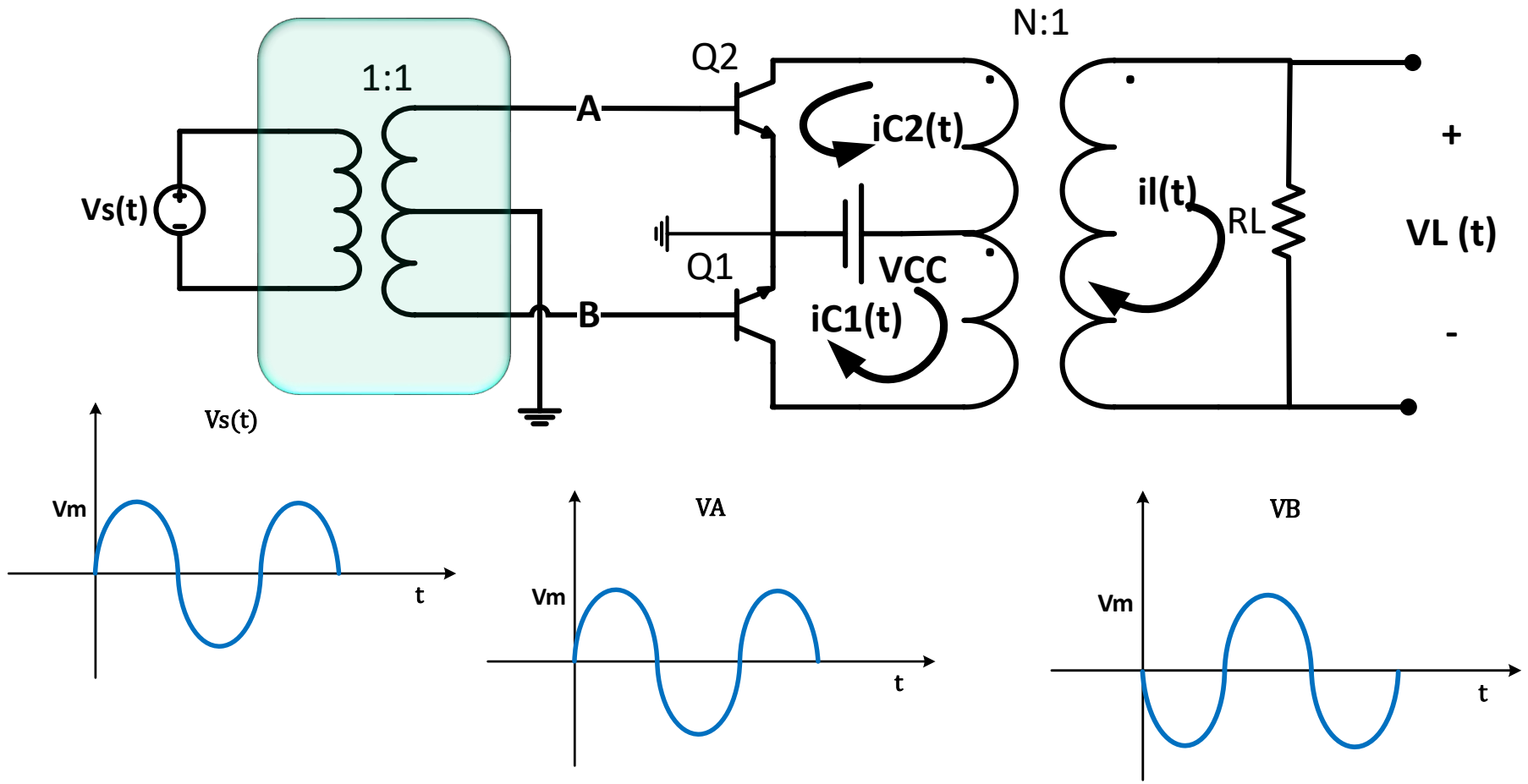

Class B Push-Pull Power Amplifier:

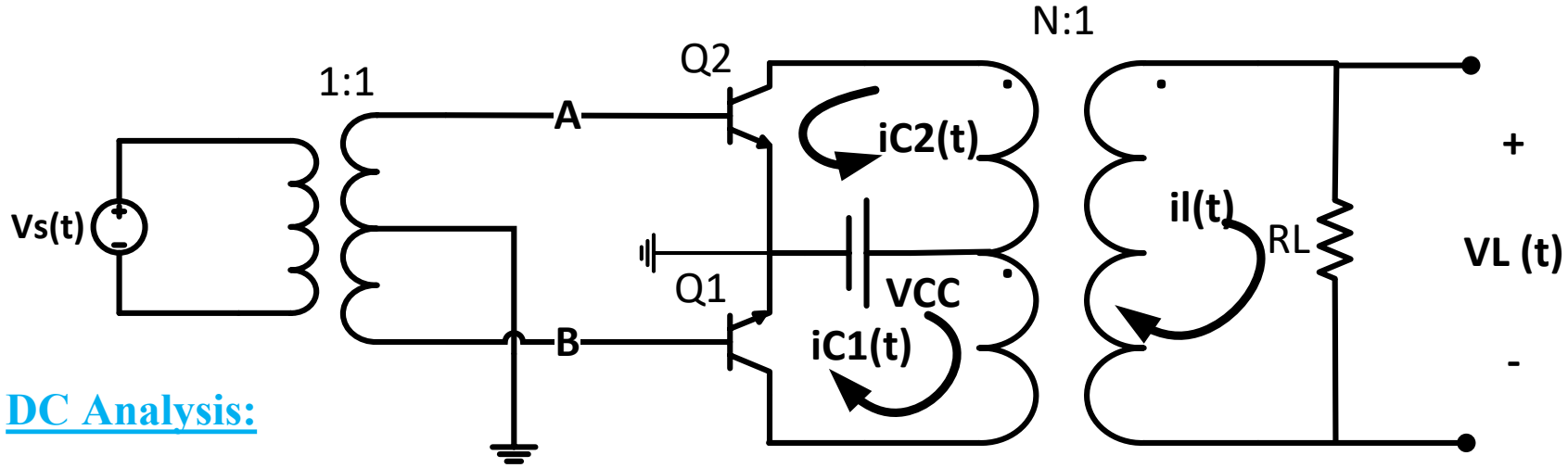

DC Analysis:

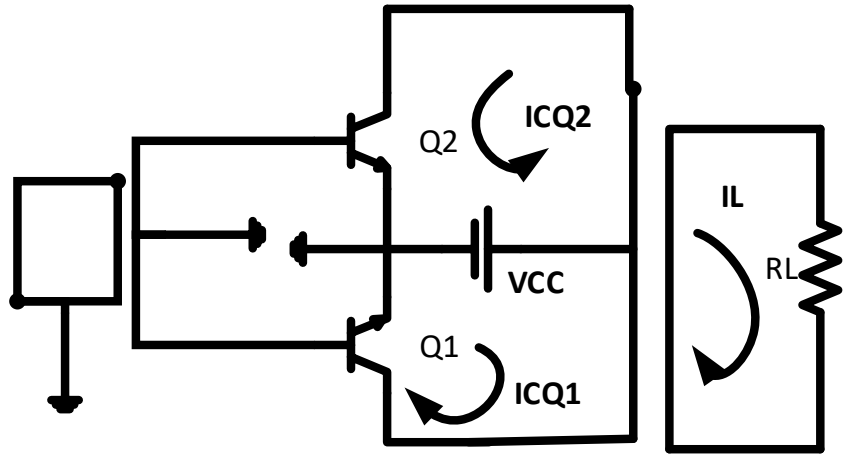

$$V_{BE1} = V_{BE2} = 0$$

Q₁ and Q₂ are cut off


$$I_{CQ1} = I_{CQ2} = 0$$

$$V_{CEQ1} = V_{CEQ2} = V_{CC}$$

$$V_L = 0 \quad I_L = 0$$

Class B Push-Pull Power Amplifier:

AC Analysis:

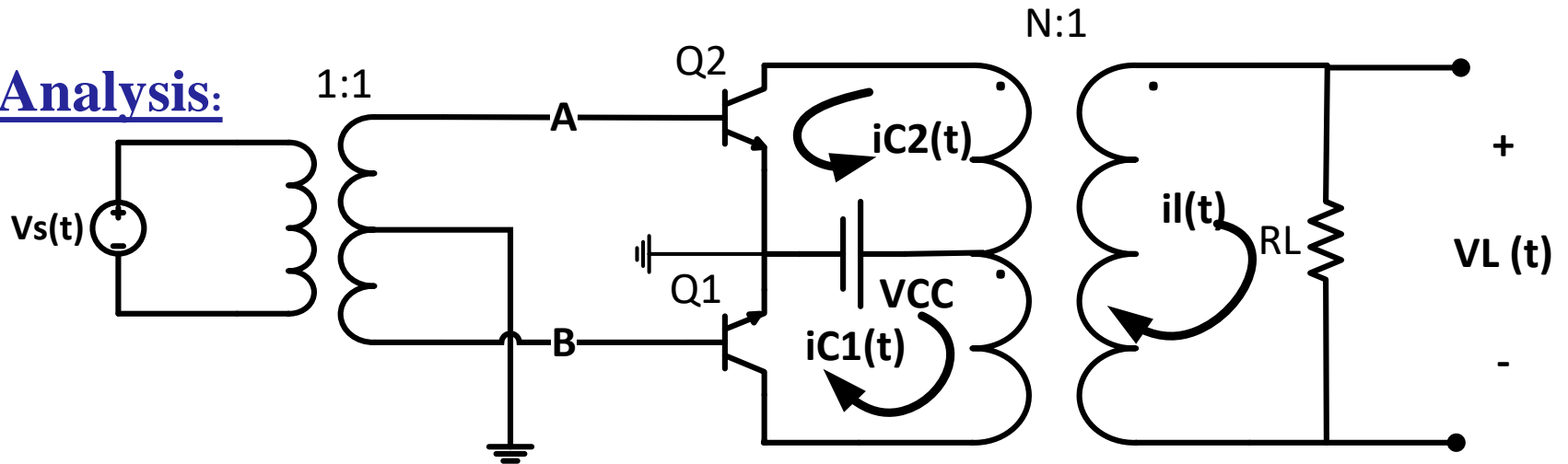

a) when $v_s(t) > 0$

$v_A(t) > 0$; Q_2 is on




$v_B(t) < 0$; Q_1 is off

$$\therefore i_L(t) = -Ni_{C2}(t)$$


and

$$i_s(t) = i_{C2}(t)$$

$$v_L(t) = R_L i_L(t)$$

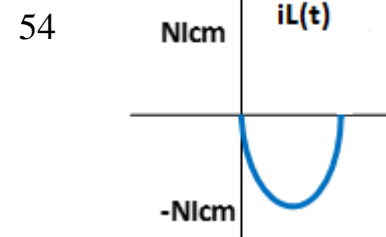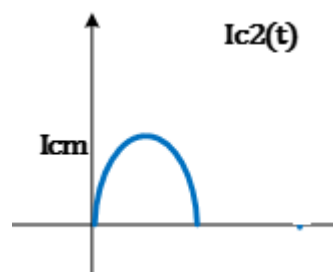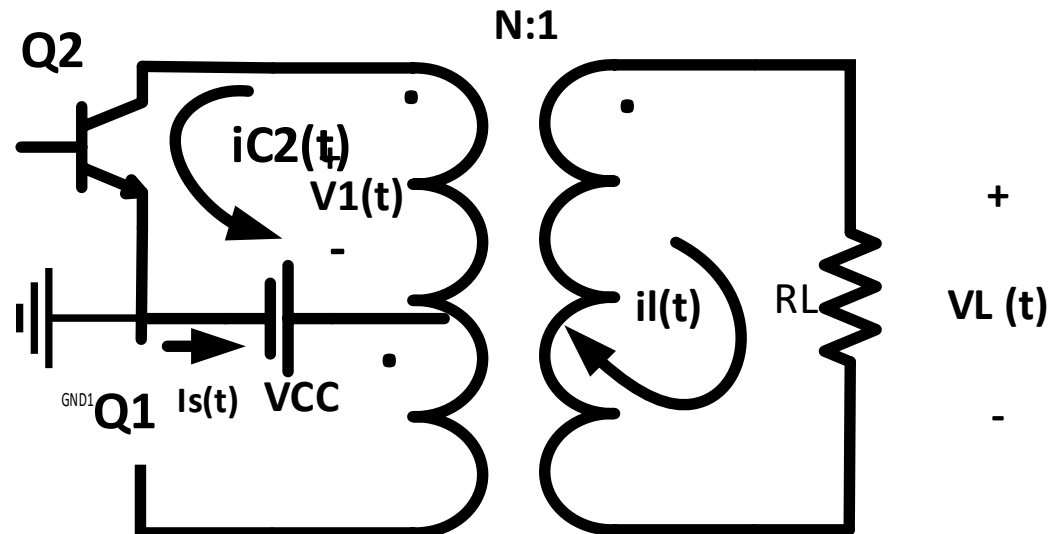

54

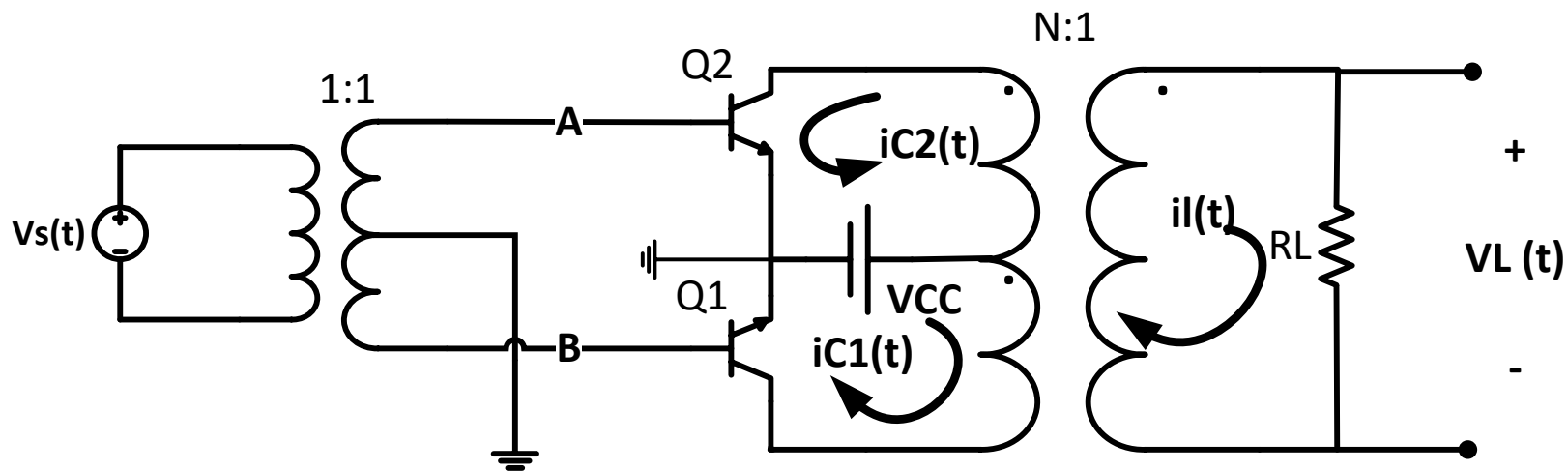

b) when $v_s(t) < 0$

$v_A(t) < 0$; Q_2 is off




$v_B(t) > 0$; Q_1 is on

$$\therefore \mathbf{i_L(t) = +N i_{C1}(t)}$$

and

$$\mathbf{i_s(t) = i_{C1}(t)}$$

$$\mathbf{v_L(t) = R_L i_L(t)}$$

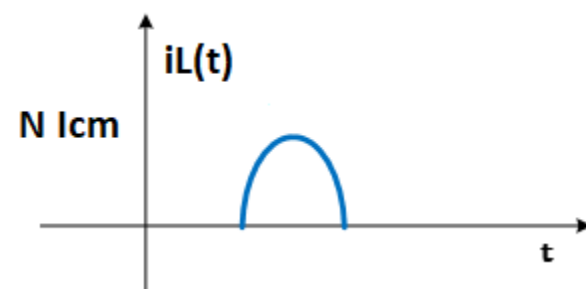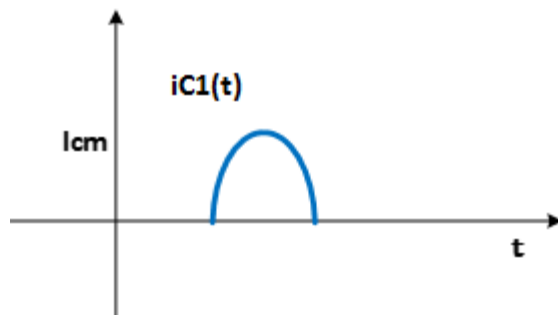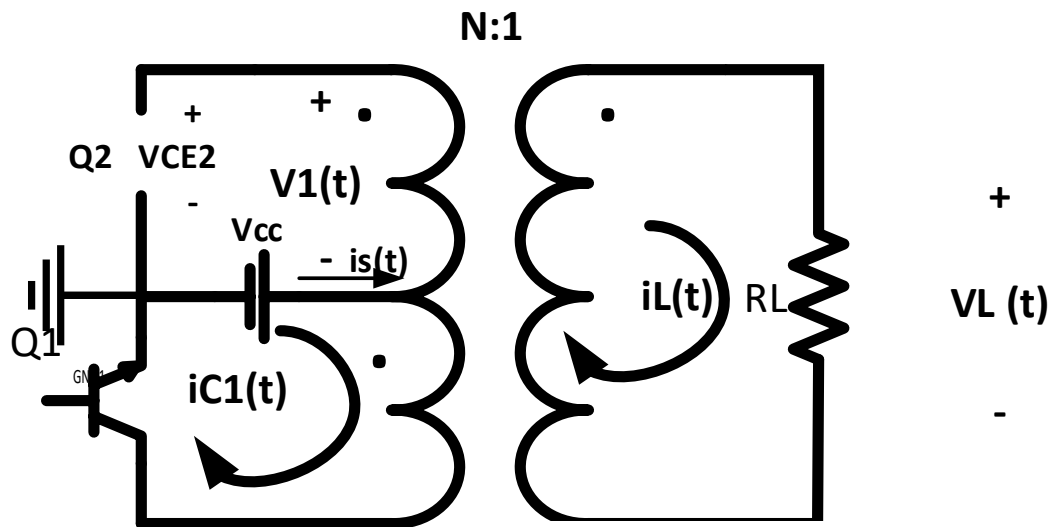






Class B Push-Pull Power Amplifier:

AC Analysis:

c) for the complete cycle

$$i_L(t) = N (i_{C1}(t) - i_{C2}(t))$$

$$i_S(t) = i_{C2}(t) + i_{C1}(t)$$

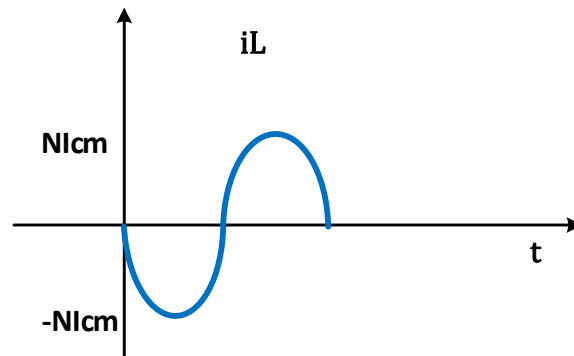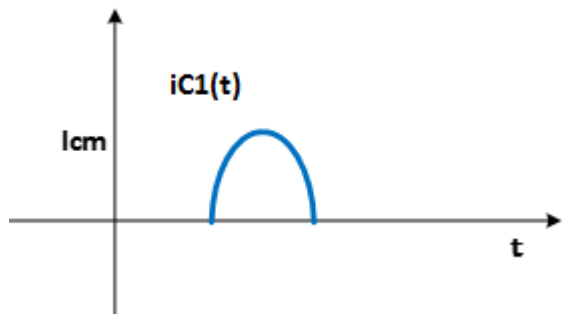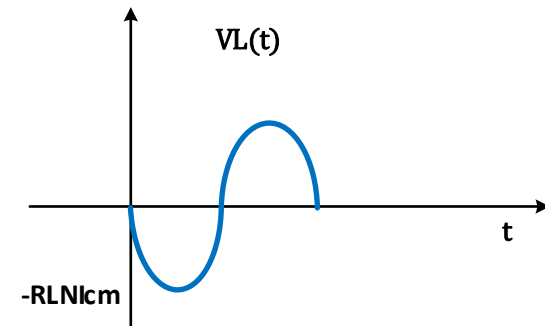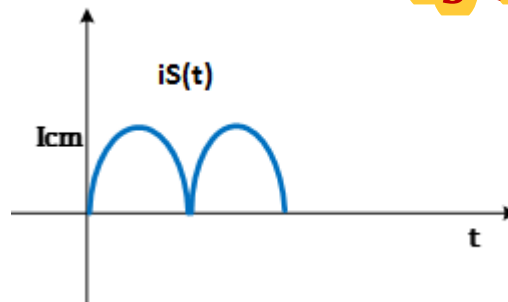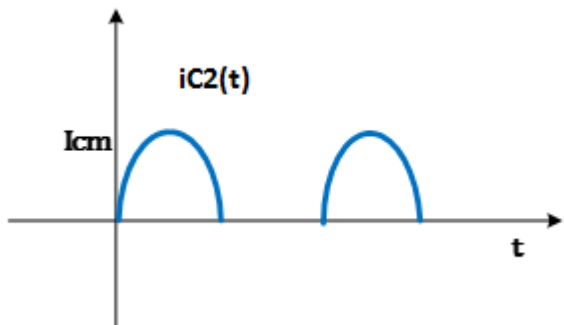

Class B Push-Pull Power Amplifier:


AC Load Line for Q2:

1) when $v_s(t) > 0$

$v_A(t) > 0$; Q_2 is on

$v_B(t) < 0$; Q_1 is off

$$R'_l = N^2 R_L$$

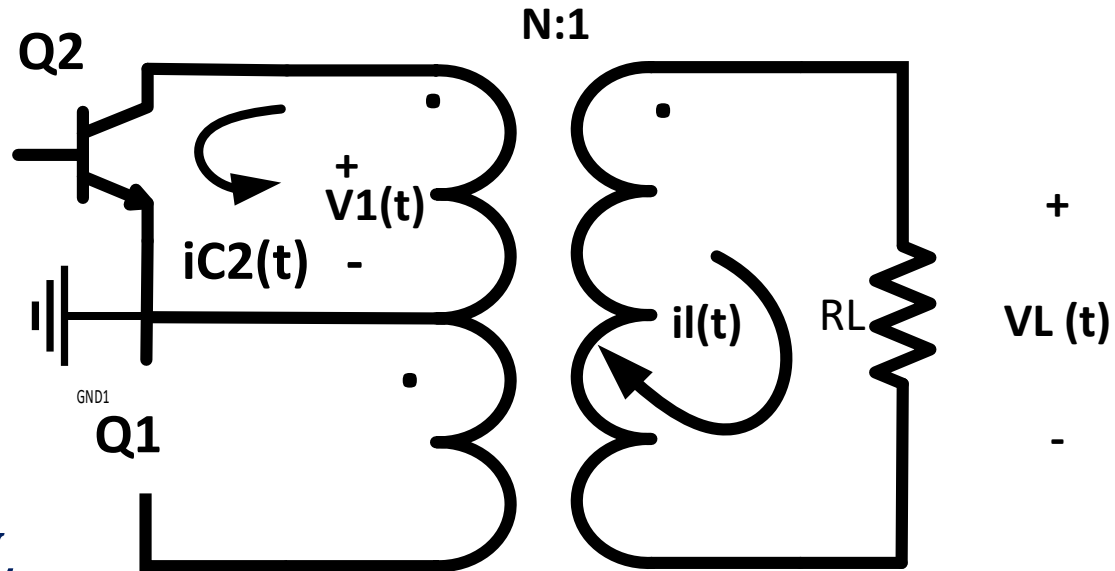

$$v_{ce2} = -R'_l i_{c2} = -(N^2 R_L) i_{c2}$$

$$v_{CE2}(t) - V_{CEQ2} = -R'_l (i_{C2}(t) - I_{CQ2})$$

$$v_{CE2}(t) - V_{CEQ2} = -R'_l i_{C2}(t)$$

$$v_{CE2}(t) - V_{cc} = -R'_l i_{C2}(t)$$

$$V_{cc} - v_{CE2}(t) = R'_l i_{C2}(t)$$

Class B Push-Pull Power Amplifier:

To find $i_{C2}(t)_{max}$

$$\rightarrow v_{CE2}(t) = v_{CE2,sat} = 0$$

$$0 - V_{cc} = -R'_l i_{C2}(t)_{max}$$

$$i_{C2}(t)_{max} = \frac{V_{cc}}{R'_l}$$

$$I_{cm2,max} = \frac{V_{cc}}{R'_l}$$



To find $v_{CE}(t)_{max}$

$$\rightarrow i_{C2}(t) = 0$$

$$v_{CE2}(t)_{max} - V_{cc} = 0$$

$$v_{CE2}(t)_{max} = V_{cc}$$

AC Load Line for Q2:

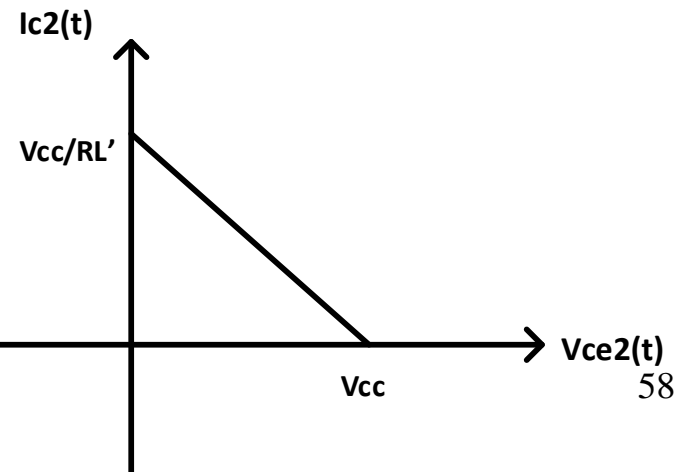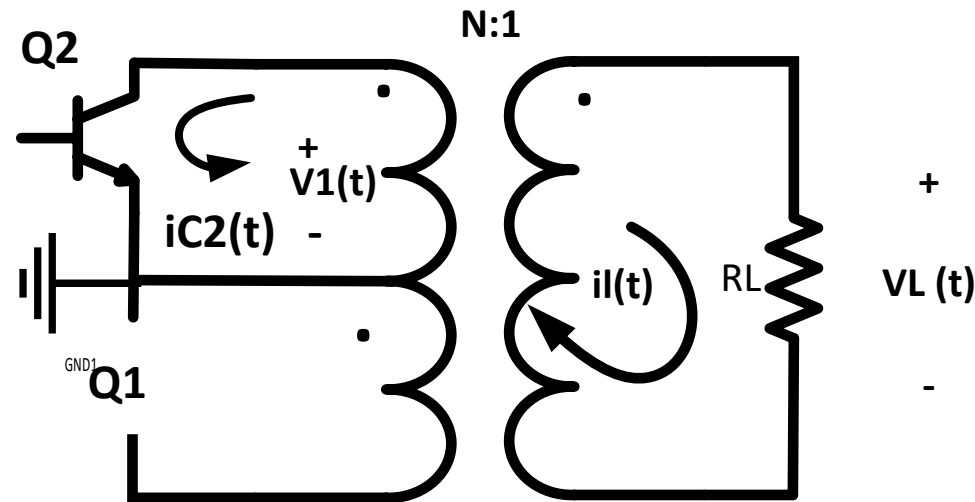


Class B Push-Pull Power Amplifier:

AC Load Line for Q2:

when $v_s(t) < 0$

$v_A(t) < 0$; Q_2 is off

$v_B(t) > 0$; Q_1 is on

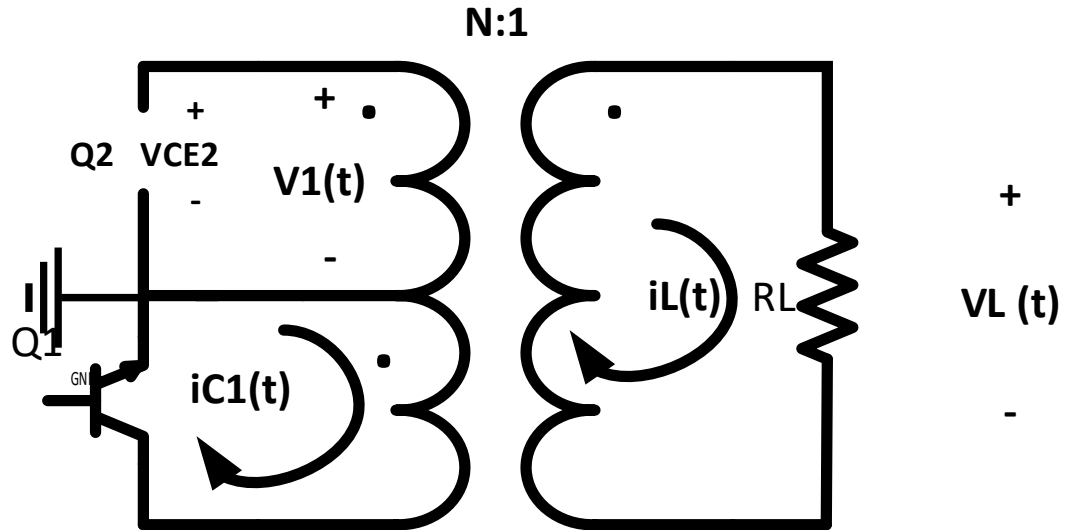

$$v_{ce2} = v_1(t)$$

$$v_{CE2}(t) = V_{cc} + N R_L N i_{C1}(t)$$

$$v_{CE2}(t) - V_{cc} = v_1(t)$$

$$v_{CE2}(t) = V_{cc} + N^2 R_L i_{C1}(t)$$

$$v_{CE2}(t) - V_{cc} = N v_L(t)$$

$$v_{CE2}(t) = V_{cc} + R'_L i_{C1}(t)$$

$$v_{CE2}(t) = V_{cc} + N v_L(t)$$

59

$$\therefore v_{CE2}(t)_{max} = V_{cc} + R'_L i_{C1}(t)_{max}$$



Class B Push-Pull Power Amplifier:

AC Load Line for Q2:

$$v_{CE2}(t)_{max} = V_{cc} + R'_l \frac{V_{cc}}{R'_l}$$


$$v_{CE2}(t)_{max} = V_{cc} + V_{cc}$$

$$v_{CE2}(t)_{max} = 2V_{cc}$$

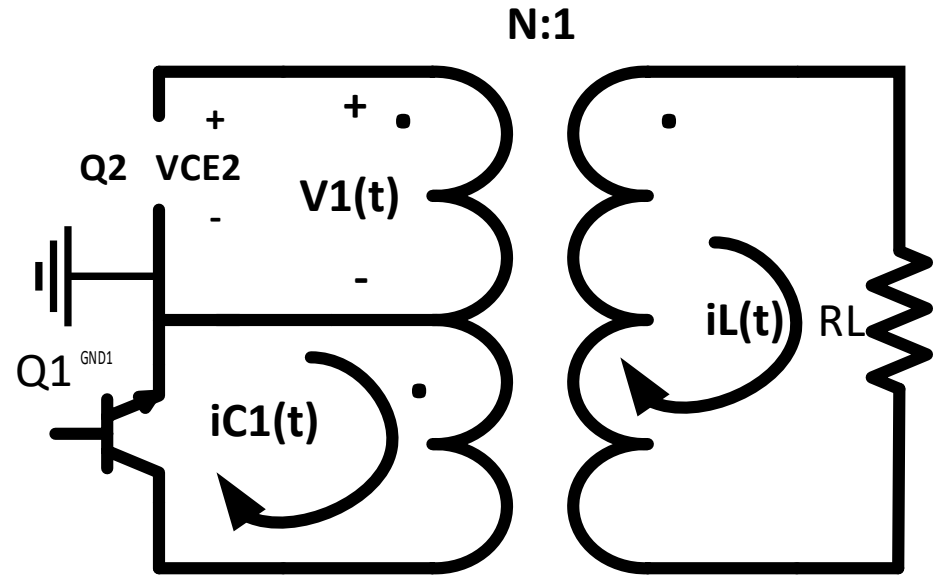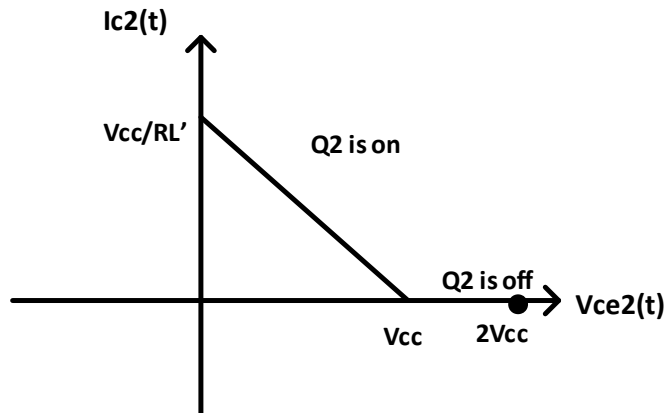

Class B Push-Pull Power Amplifier:

Power calculation:

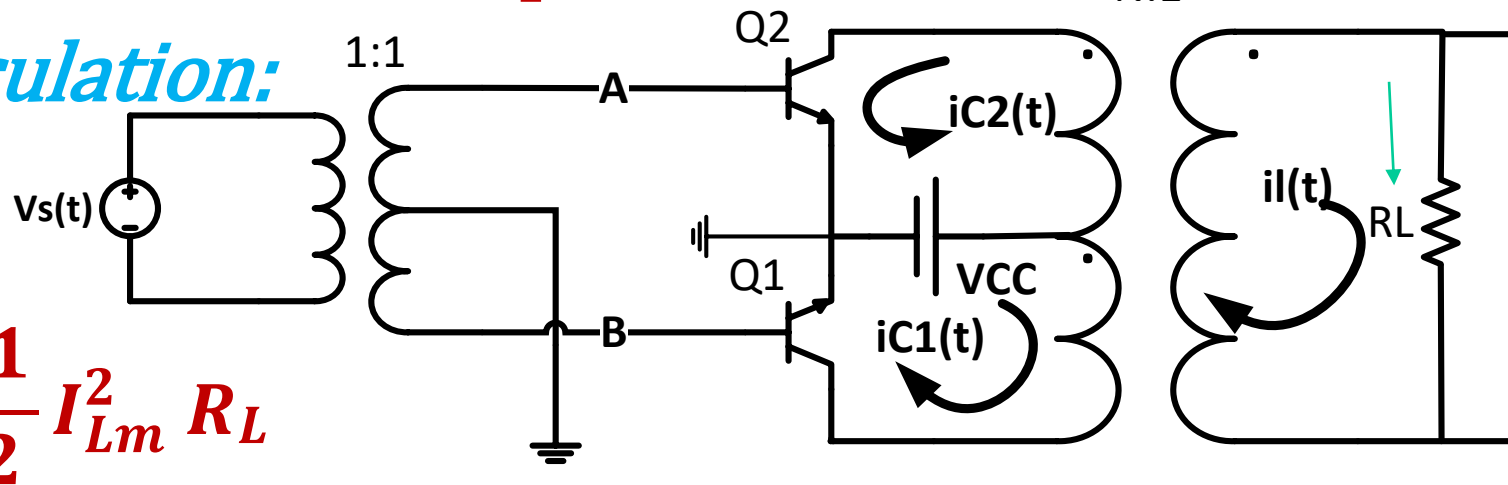

$$P_{L,ac} = \frac{1}{2} I_{Lm}^2 R_L$$

$$I_{Lm} = N I_{cm}$$

$$\therefore P_{L,ac} = \frac{1}{2} I_{cm}^2 R_L'$$

$$P_{L,ac,max} = \frac{1}{2} (I_{cm,max}^2) R_L'$$

$$P_{L,ac,max} = \frac{V_{cc}^2}{2R_L'}$$

Class B Push-Pull Power Amplifier:

Power calculation:

$$P_{cc} = \frac{1}{T} \int_0^T V_{cc} i_s(t) dt = \frac{2V_{cc} I_{cm}}{\pi}$$

$$2P_c = P_{cc} - P_{L,ac}$$


$$P_c = \frac{P_{cc} - P_{L,ac}}{2}$$

$$P_c = \frac{V_{cc} * I_{cm}}{\pi} - \frac{1}{4} I_{cm}^2 R_L'$$

$$\frac{dP_c}{dI_{cm}} = 0$$

$$I_{cm} = \frac{2V_{cc}}{\pi R_L'}$$
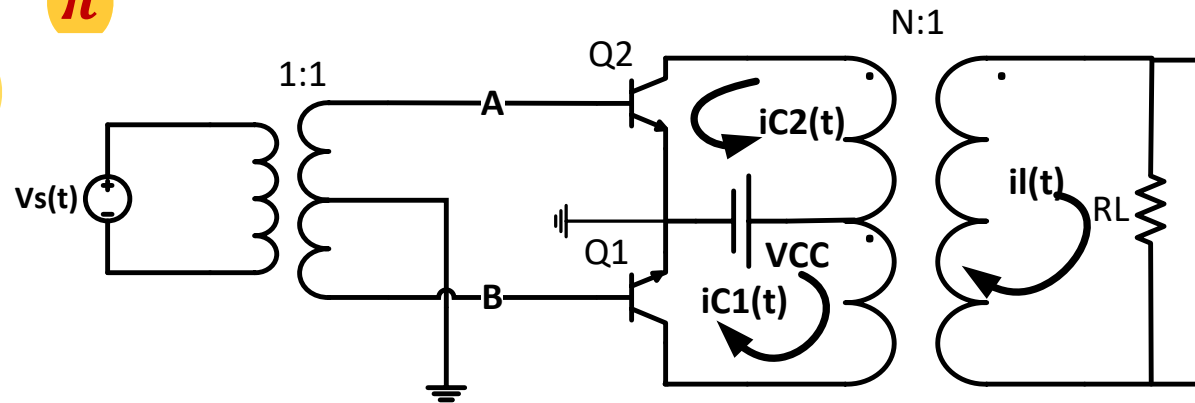
$$\therefore P_{c,max} = \frac{V_{cc}^2}{\pi^2 R_L'}$$



$$\eta = \frac{P_{L,ac}}{P_{cc}} * 100\%$$

$$\eta = \frac{\pi}{4} \left(\frac{I_{cm}}{\frac{V_{cc}}{R_L'}} \right) * 100\%$$

$$\eta_{,max} = \frac{\pi}{4} * 100\% = 78.5\%$$








$$\gamma = \frac{P_{c,max}}{(P_{L,ac}),max}$$

$$\gamma = \frac{2}{\pi^2} \cong 0.2$$



Class B Push-Pull Power Amplifier:


Cross Over Distortion:

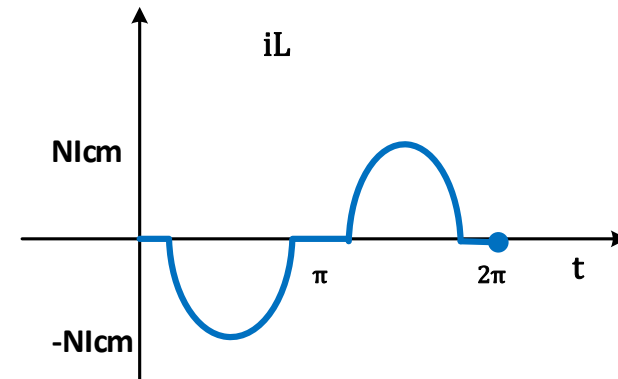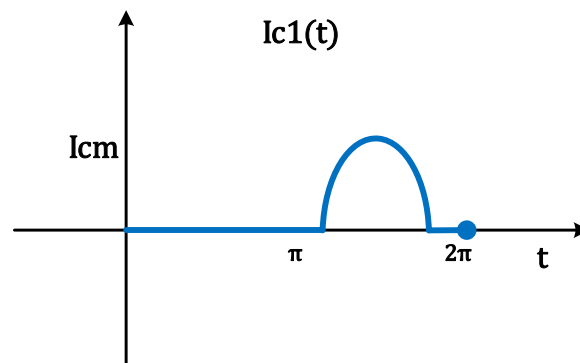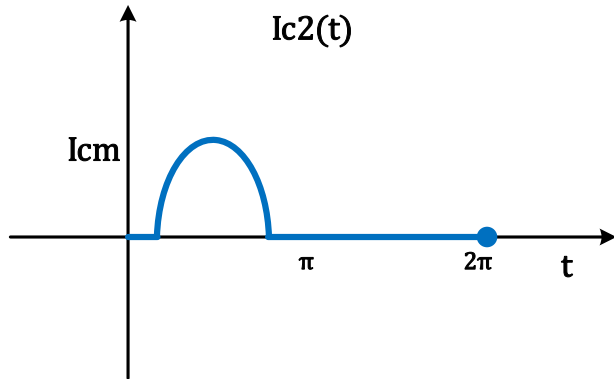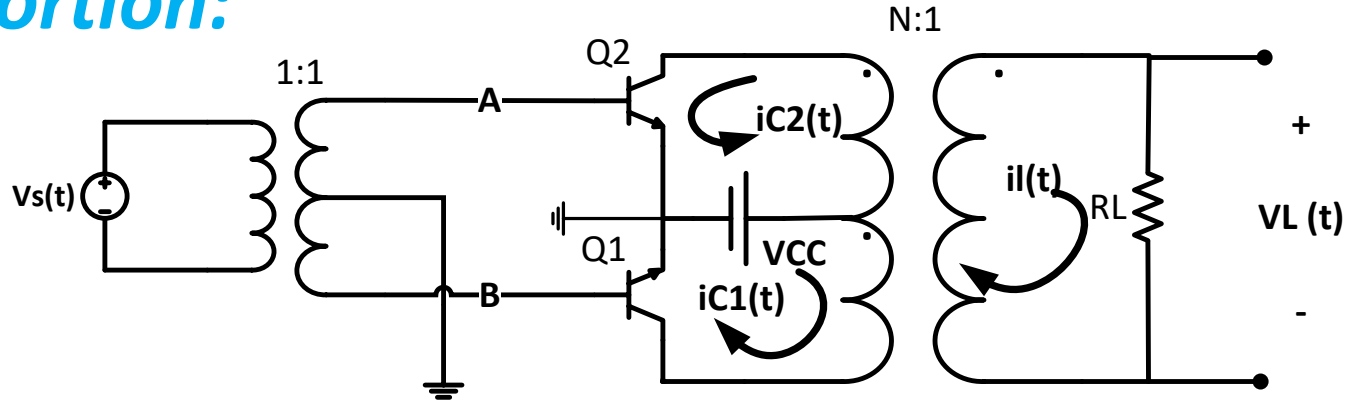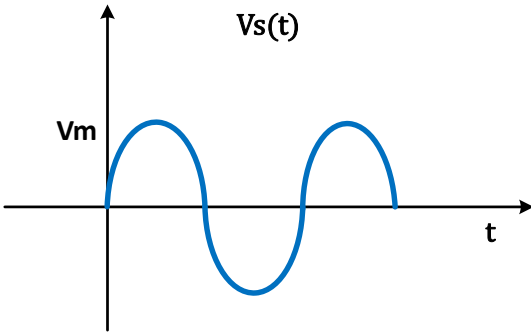


Class AB Push-Pull Power Amplifier:

Cross Over Distortion:

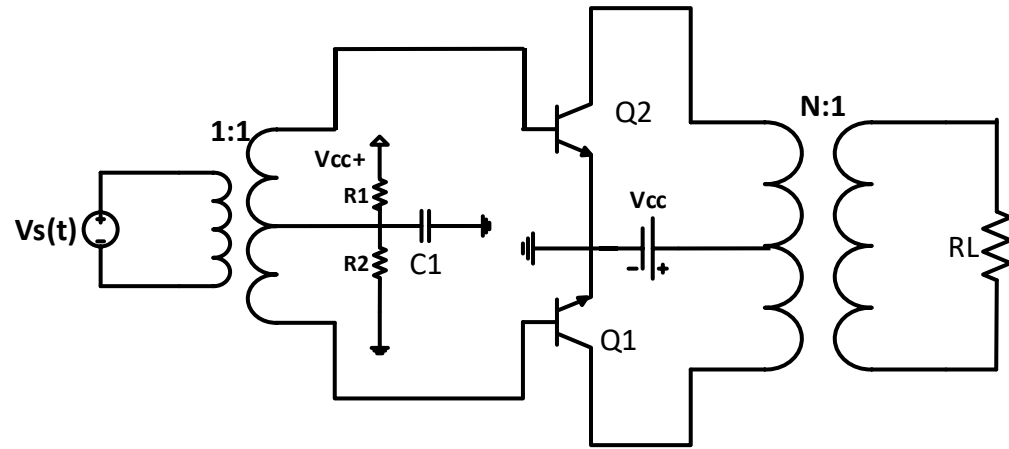1) Cross over distortion can be reduced or eliminated by biasing each transistor slightly into conduction.




2) Typically the base-emitter junction are biased above 0.5V, 0.6V. 

We Choose R1 & R2 So that:

$$\frac{R_2}{R_1 + R_2} \frac{V_{cc}}{V_{cc}} = 0.5, 0.6, \dots$$

3) When a transistor is biased slightly into conduction, the output current will flow during more than one-half cycle of a sinwave input signal.

4) Efficiency is reduced depending on how heavily the transistors are biased.

5) $78.5\% > \eta_{max} > 50\%$ 

Complementary symmetry Class B push pull Power Amplifier

$$V_{BE1} + V_{BE2} = 0$$




$\therefore Q1$ and $Q2$ are in cutoff

$$I_{CQ1} = I_{CQ2} = 0, I_L = 0, V_o = 0$$

$$V_{CEQ1} = V_{CC}, V_{CEQ2} = V_{CC}$$


When $V_i(t) > 0$

, $Q1$ is on , $Q2$ is off

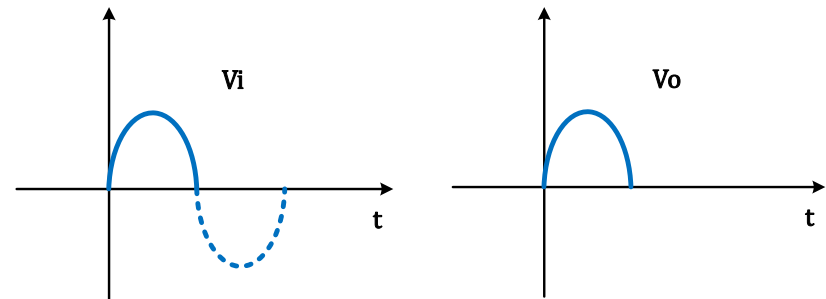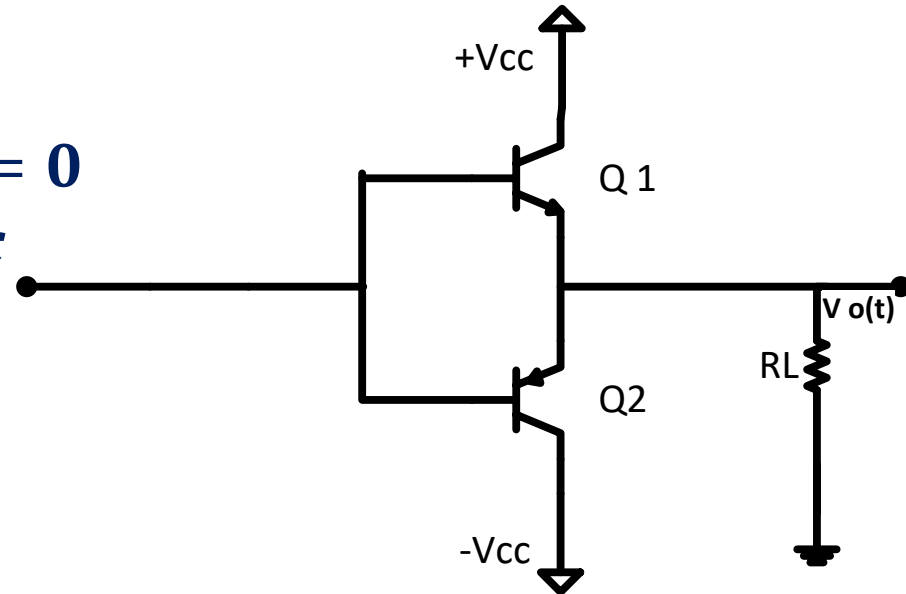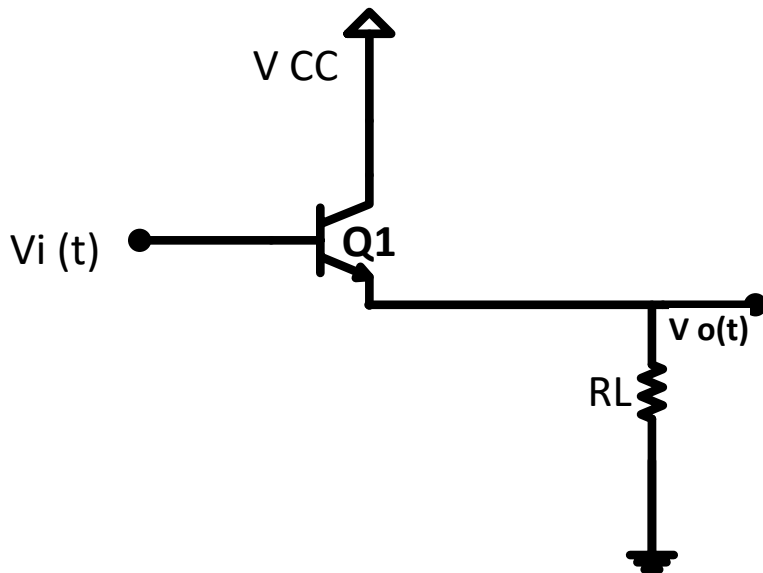


Complementary symmetry Class B push pull Power Amplifier

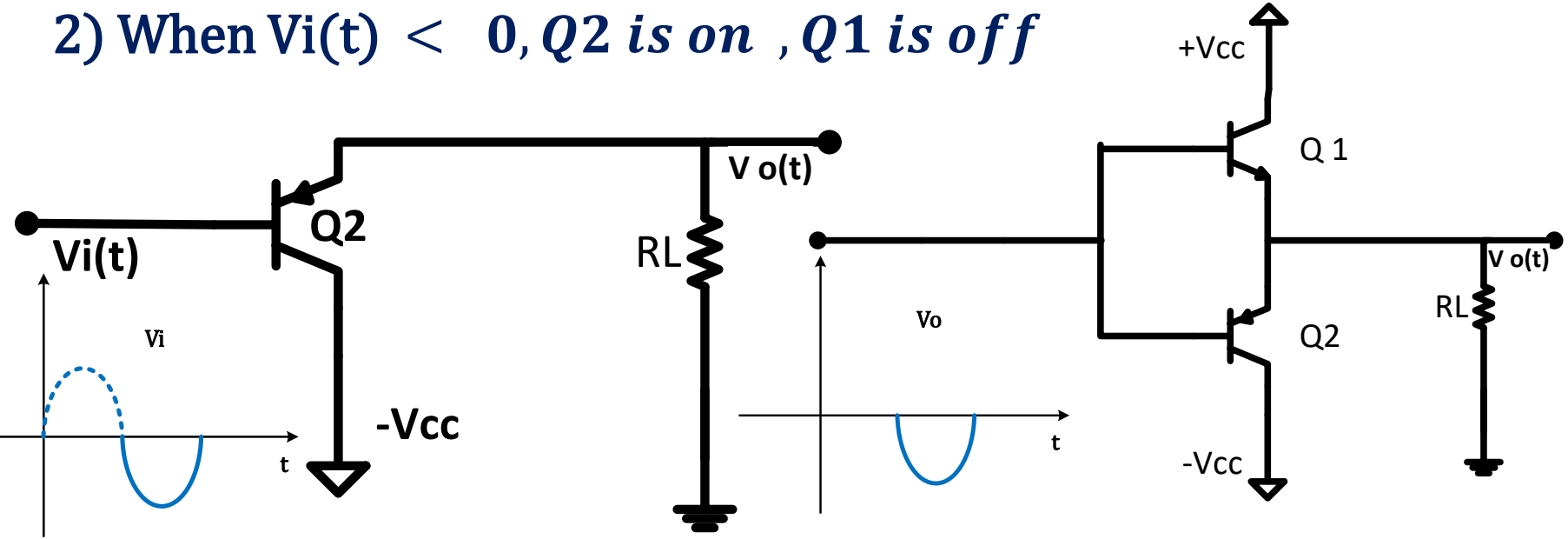2) When $V_i(t) < 0$, $Q2$ is on, $Q1$ is off





For the complete cycle

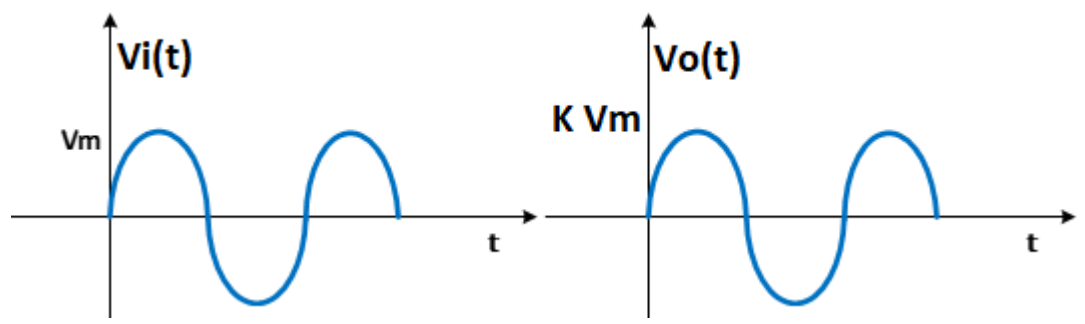

Complementary symmetry Class B push pull Power Amplifier

Power calculation:

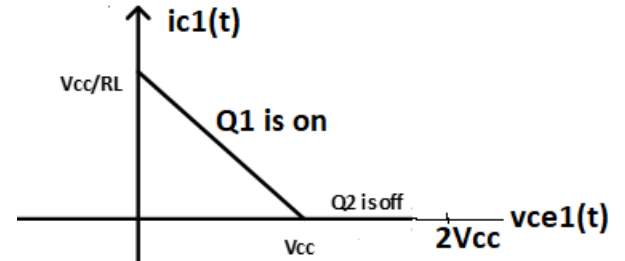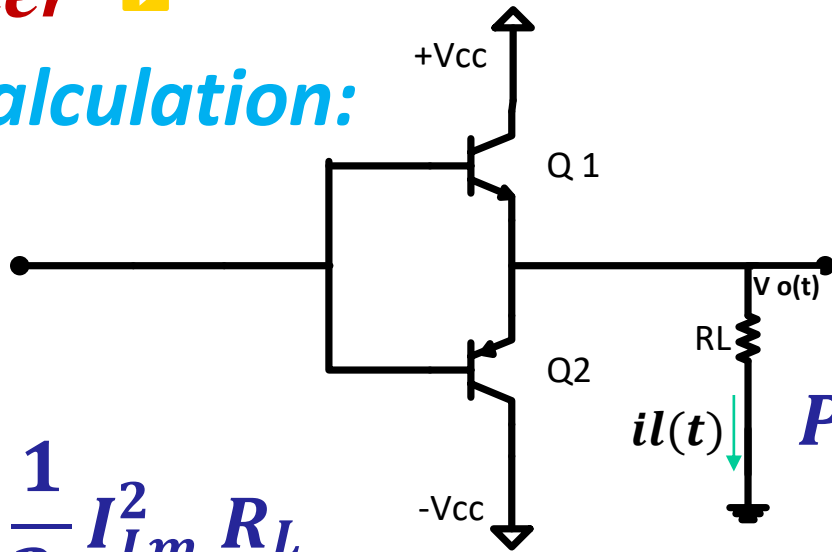

$$P_{L,ac} = \frac{1}{2} I_{Lm}^2 R_L$$

$$\therefore P_{L,ac} = \frac{1}{2} I_{cm}^2 R_L$$

$$P_{L,ac,max} = \frac{1}{2} (I_{cm,max}^2) R_L$$

$$P_{L,ac,max} = \frac{V_{cc}^2}{2R_L}$$

$$P_{cc} = \frac{1}{T} \int_0^T V_{cc} i_s(t) dt$$

$$= \frac{2V_{cc} I_{cm}}{\pi}$$

$$\eta = \frac{P_{L,ac}}{P_{cc}} * 100\%$$

$$\eta_{max} = \frac{\pi}{4} * 100\%$$

$$= 78.5\%$$

Complementary symmetry Class AB push pull Power Amplifier


We Choose R1 & R2 So

that:

$$\frac{R_2 V_{cc}}{R_1 + R_2} = 0.5, 0.6 \dots$$

$$V_{BE1} = V_{BE2} = 0.5, 0.6, \dots$$

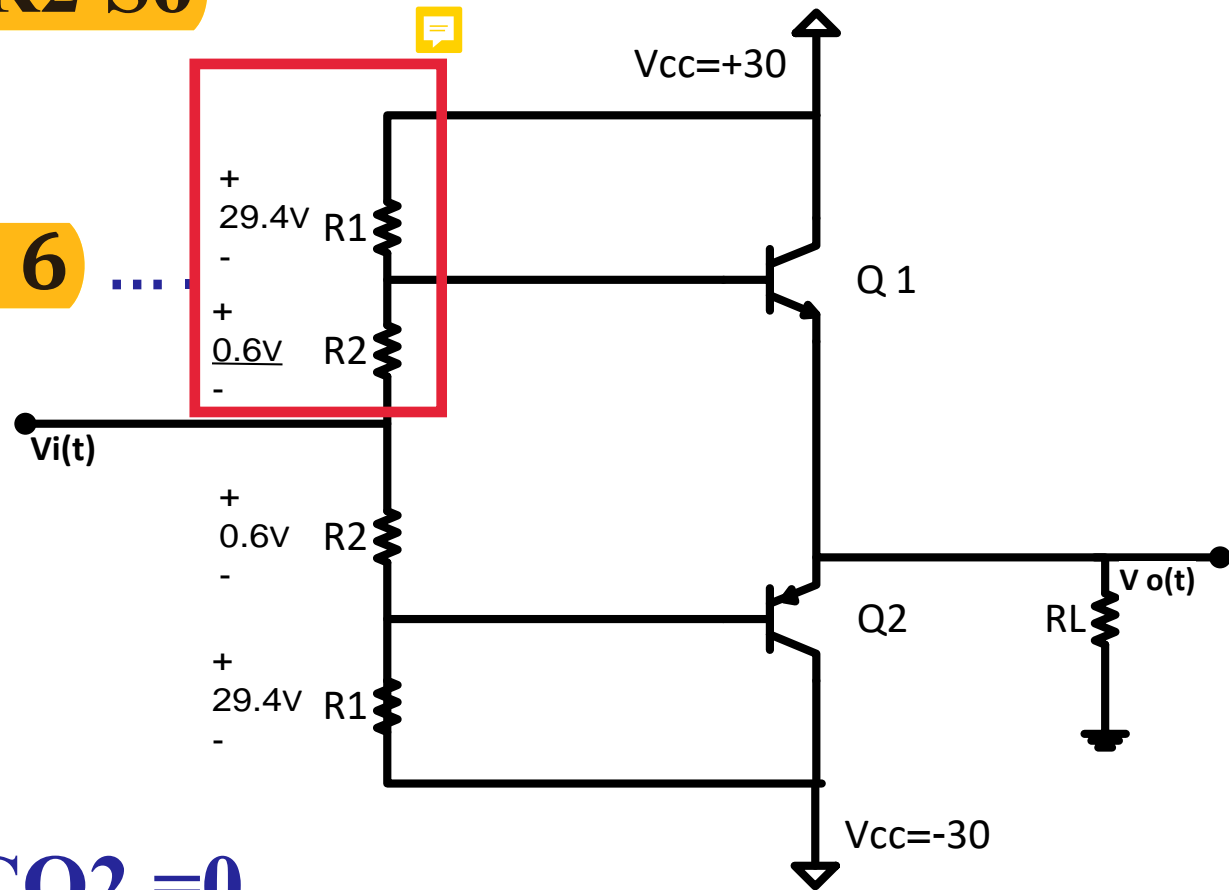So that $I_{CQ1} \approx I_{CQ2} = 0$
and $V_o = 0$



Complementary symmetry Class AB push pull Power Amplifier

Practical Class AB Power Amplifier

To Provide Bias Stability

1) Small R_e for bias Stability .


2) Diodes D1 and D2 for Temperature Compensation.

DC Component

Assume that I_B very small $\rightarrow 0$

$$\therefore I = I_{D1} = I_{D2} = \frac{5.3}{560} = 9.46mA$$

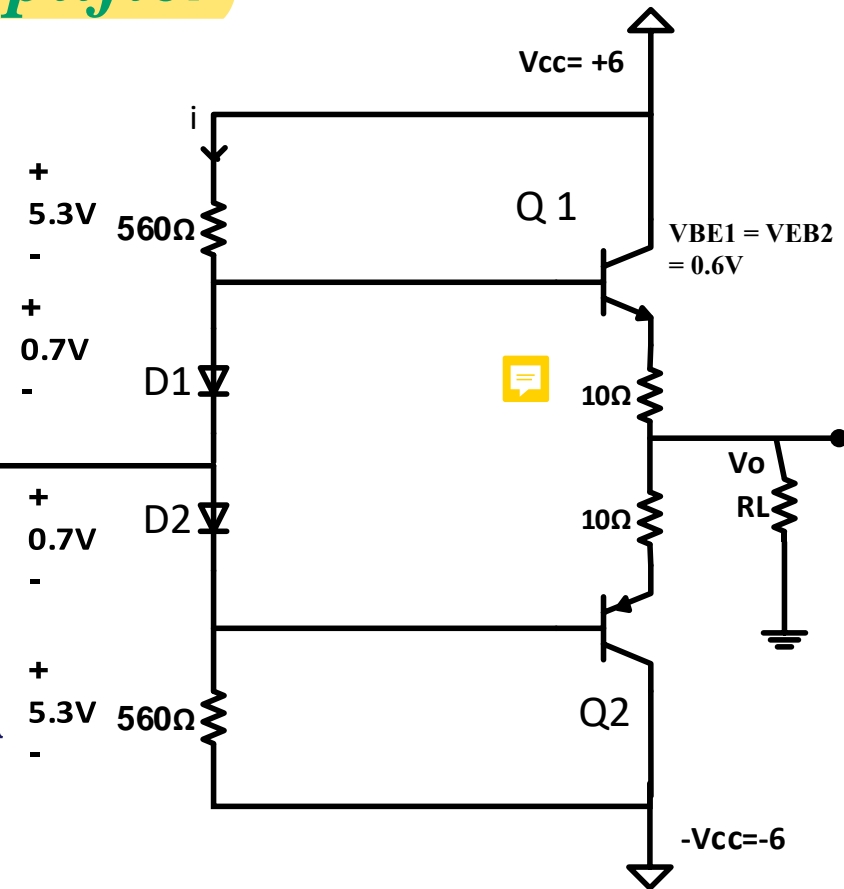
$$\therefore I_{C1} = I_{C2} = \frac{0.1V}{10\Omega} = 10mA$$



Complementary symmetry Class AB push pull Power Amplifier

Practical Class AB Power Amplifier

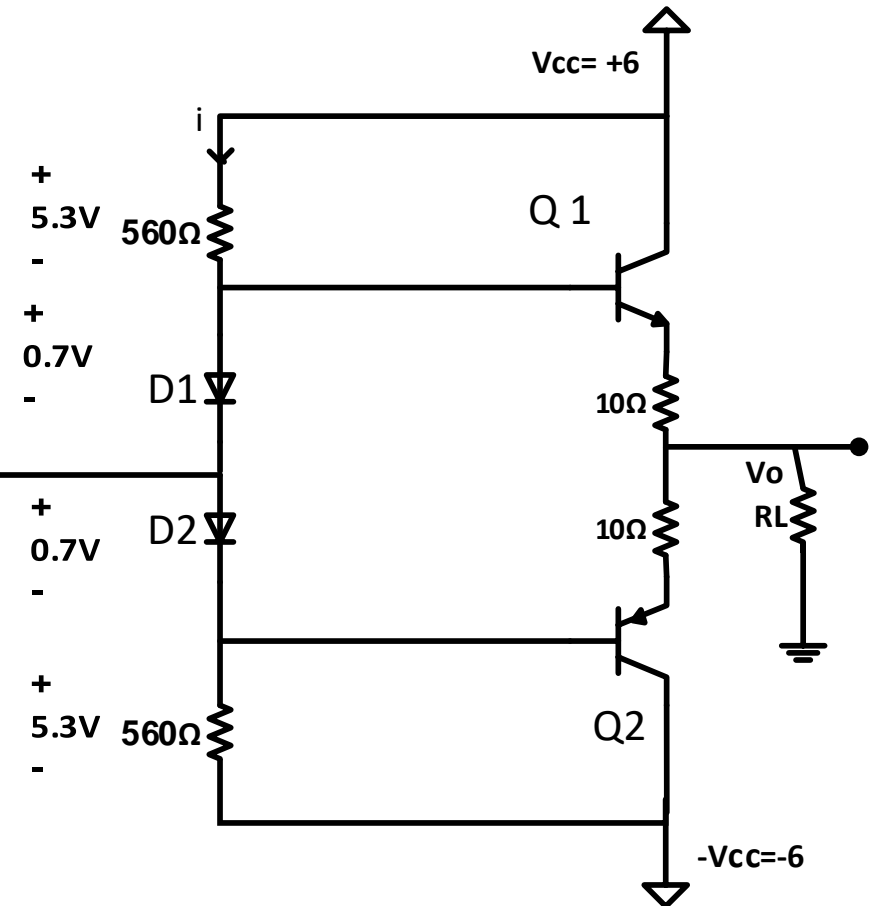- The forward bias required to turn on the output transistor decreases as its temperature increases
- The Diodes are used to adjust the base emitter forward bias automatically as a function of temperature
- D_1, D_2 are always on




Complementary Class AB Power Amplifier using Darlington:

1. This circuit gives a higher power
2. The loading effect is very small

• **To Reduce The loading on the preceeding Stage.**

Show that

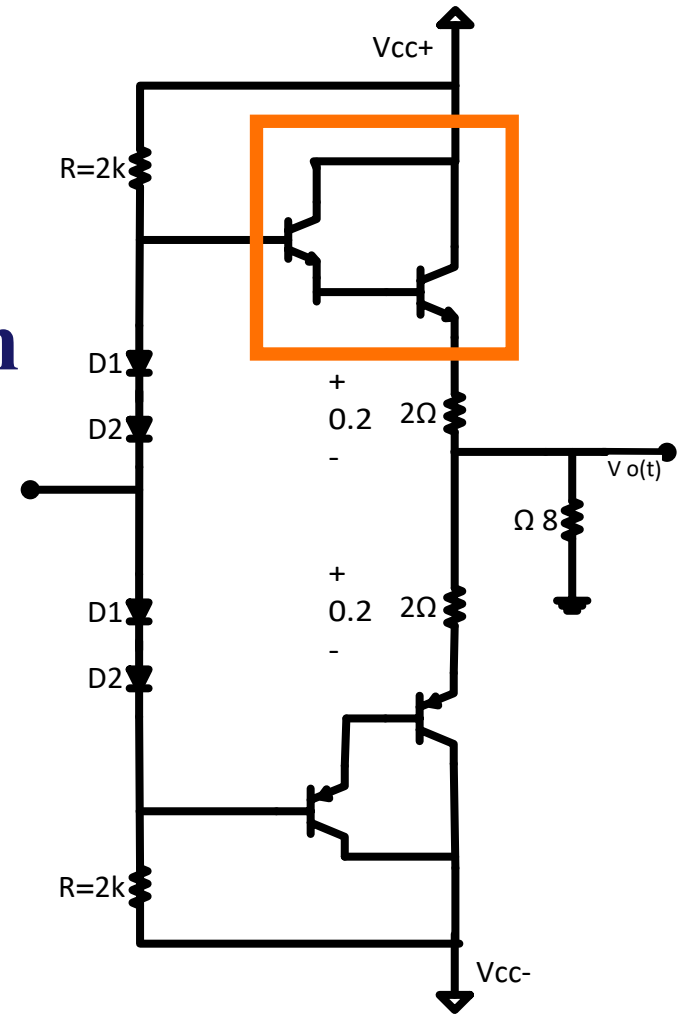

Complementary Class AB Power Amplifier using VBE Multiplier


- If a stable quiescent current is to be maintained, we must provide a bias circuit that decreases the bias voltage as the temperature increase.

$$I = \frac{25 - 1.4}{4.7k} = 5.02mA$$

$$I_{E2} = \frac{0.7}{56\Omega} = 12.5mA$$

$$I_2 \approx I_1; I_B \text{ very small}$$

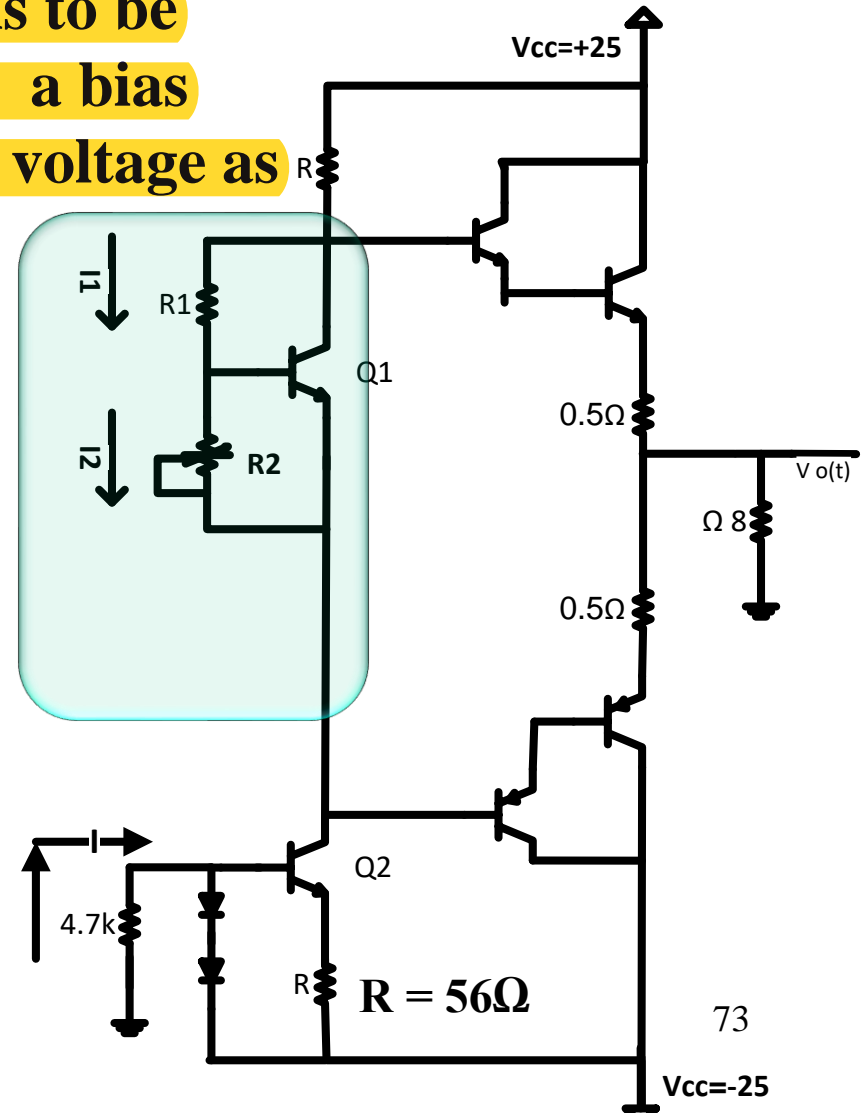
$$\therefore I_1 = I_2 = \frac{V_{BE}}{R_2}$$



$$V_{Bais} = (R_1 + R_2)I_2$$


$$V_{Bias} = \left(1 + \frac{R_1}{R_2}\right)V_{BE}$$

V_{Bias} may be adjusted

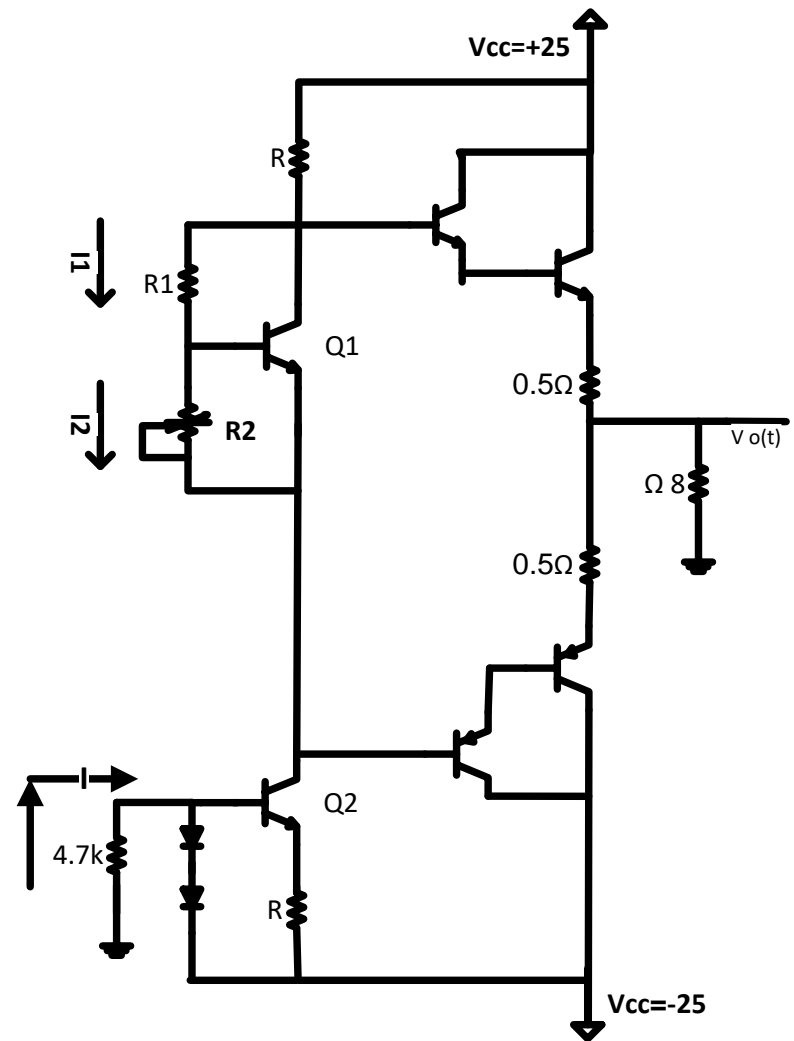

Transistor and Heat sink

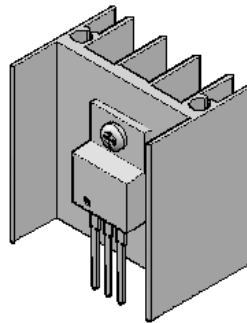The fundamental problem is to remove heat from the Semi-Conductor in order to keep T_j as low as possible



Different types of heat sink



Clip Mount


Screw mount





Thermal paste

OR


Thermal pad

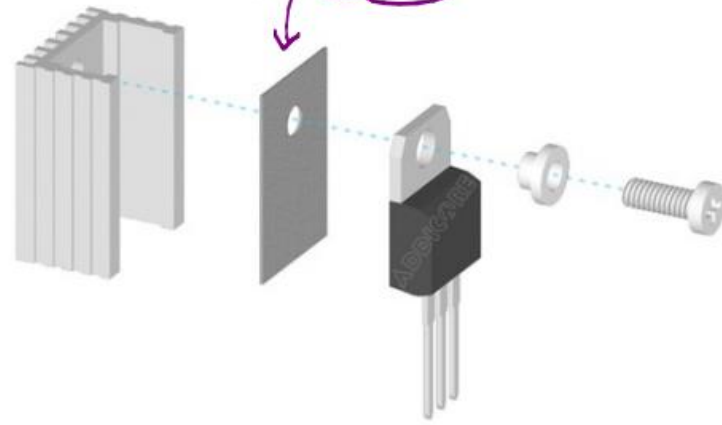

Transistor and Heat Sink

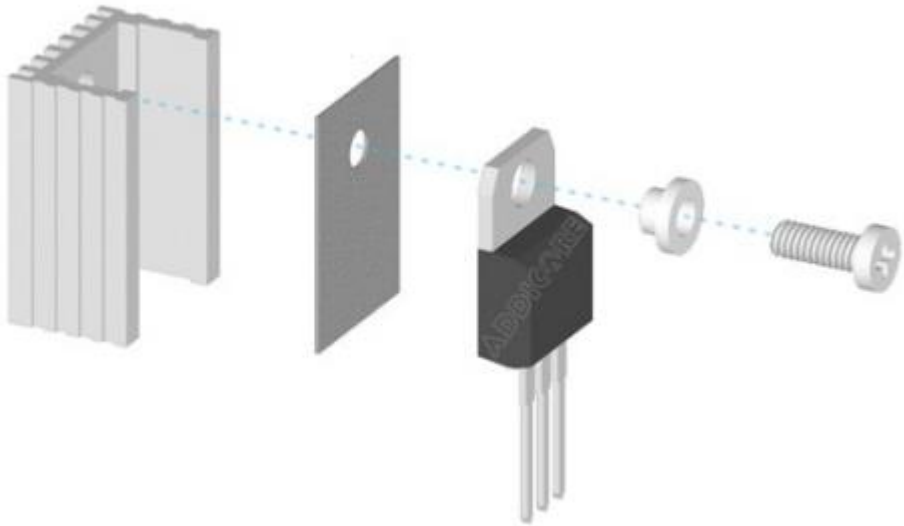
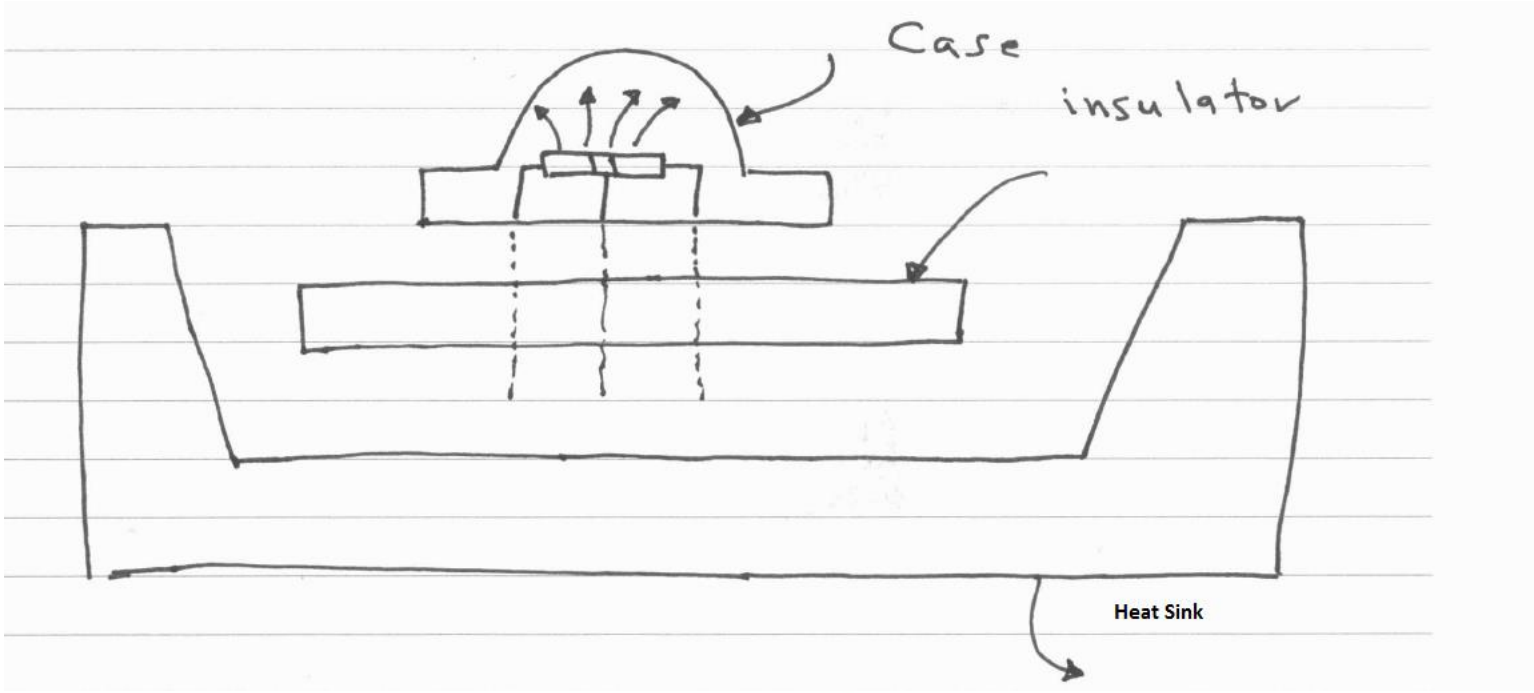


Transistor and Heat Sink

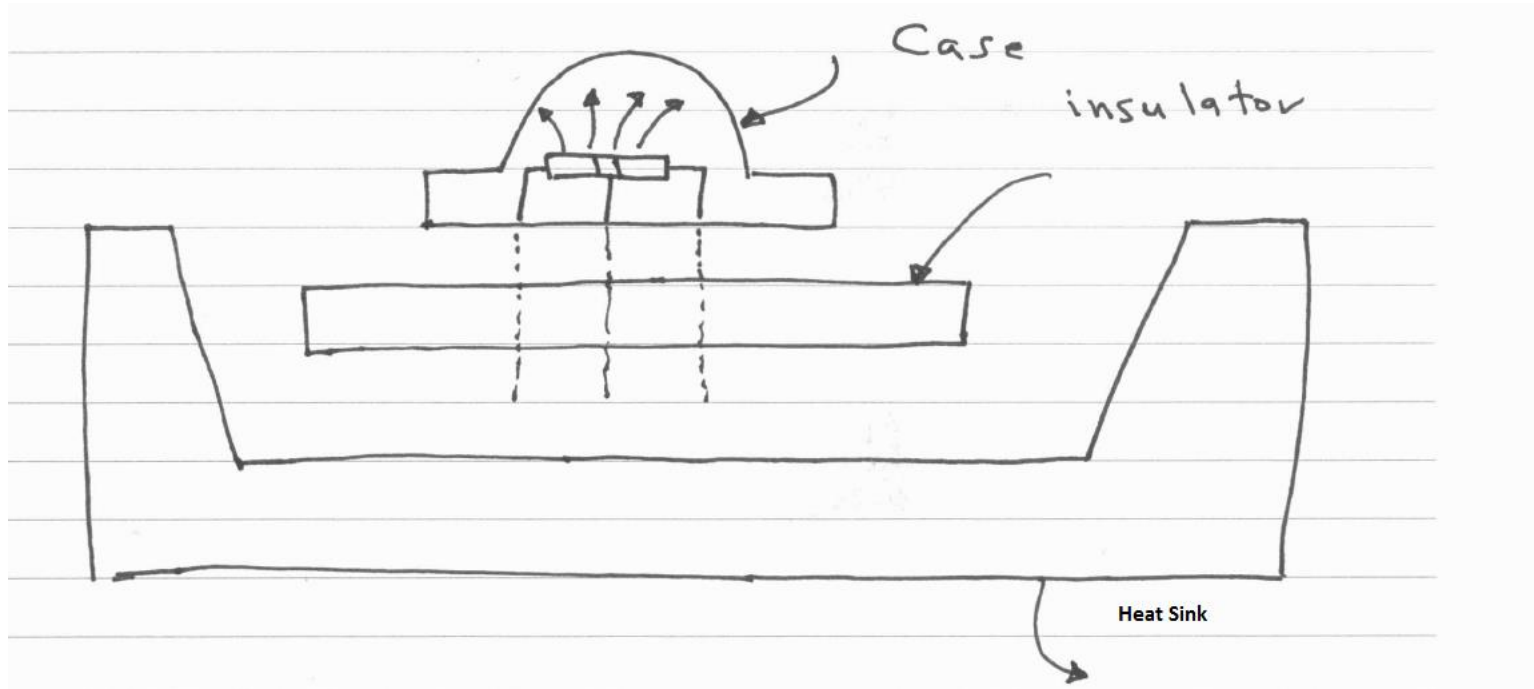

The fundamental Problem is to remove heat from the Semiconductors in order to keep T_j as low as possible

Transistor and Heat sink

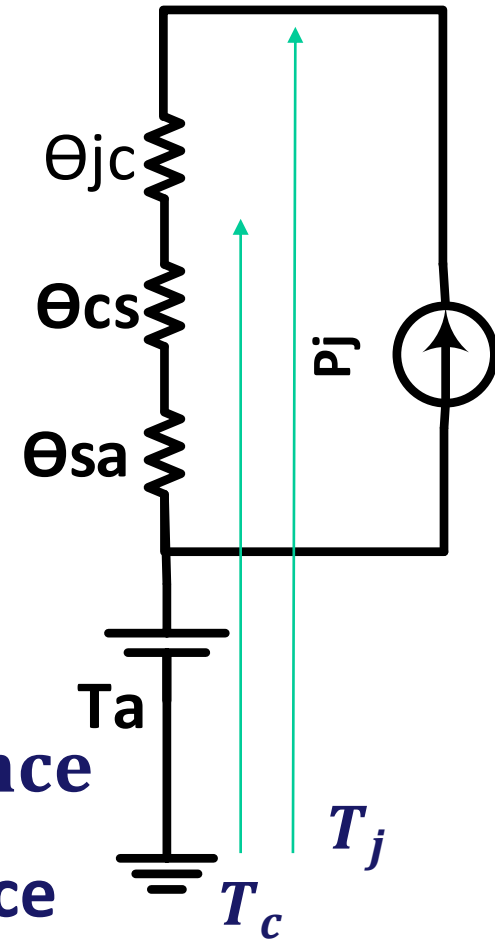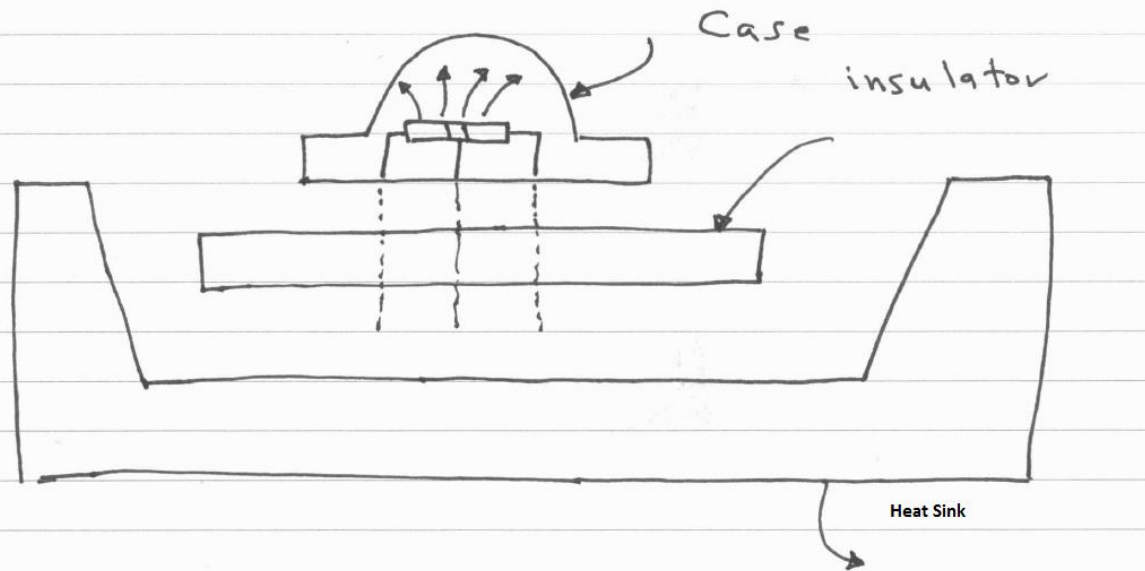

$\theta_{jc} \equiv$ Junction to case thermal resistance

$\theta_{cs} \equiv$ Case to heat sink thermal resistance

$\theta_{sa} \equiv$ Heat sink to ambient thermal resistance

$T_j - T_a = \theta_{ja} P_j$ "Thermal Ohm's Law"

$\theta_{ja} = \theta_{jc} + \theta_{cs} + \theta_{sa}$

Transistor and Heat sink

θ_{jc} : Depends on the construction of the power transistor.



$$\theta_{jc} = 0.875 \text{ } ^\circ\text{C}/\omega$$

θ_{cs} : Depends on the interface between case and sink , silicon grease or without.

θ_{sa} : Depends on the size of the heat sink.



$$\theta_{jc} = 1.92 \text{ } ^\circ\text{C}/\omega$$

Transistor and Heat sink

Power Derating Curve



In Region 1:


$$P_j = P_{j,max}$$

$$\therefore \text{if } T_c < T_{co} ; P_j = P_{j,max}$$

In Region 2:

$$\therefore \text{if } T_c > T_{co} ; T_j = T_{j,max}$$

$$\text{and } P_j < P_{j,max}$$

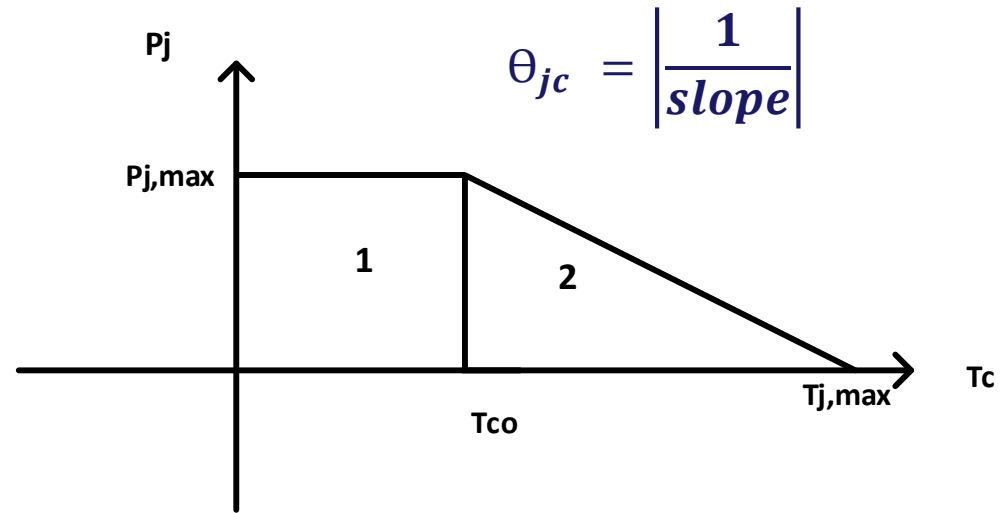

Transistor and Heat sink

Power Derating Curve

$$T_j - T_c = \theta_{jc} P_j$$


region 2 $\rightarrow T_j = T_{j,max}$

$$T_{j,max} - T_c = \theta_{jc} P_j$$

$$\theta_{jc} = \frac{T_{j,max} - T_c}{P_j}$$

$$\theta_{jc} = \frac{T_{j,max} - T_{co}}{P_{j,max}}$$


$$\theta_{jc} = \left| \frac{1}{\text{slope}} \right|$$

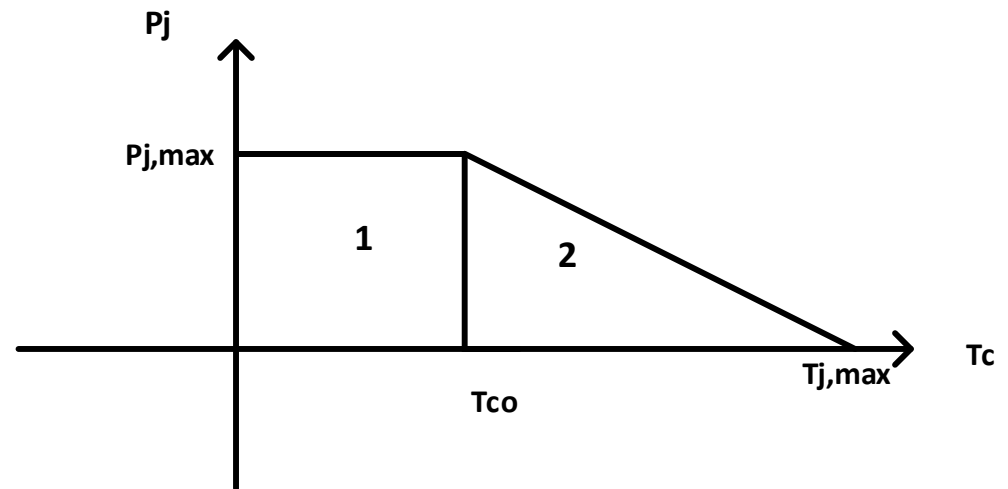

Transistor and Heat sink

A Silicon Power Transistor has a heat sink with $\theta_{sa} = 1.5^\circ\text{C}/\omega$ and using Insulator which has $\theta_{cs} = 0.4^\circ\text{C}/\omega$, and has the given derating curve.

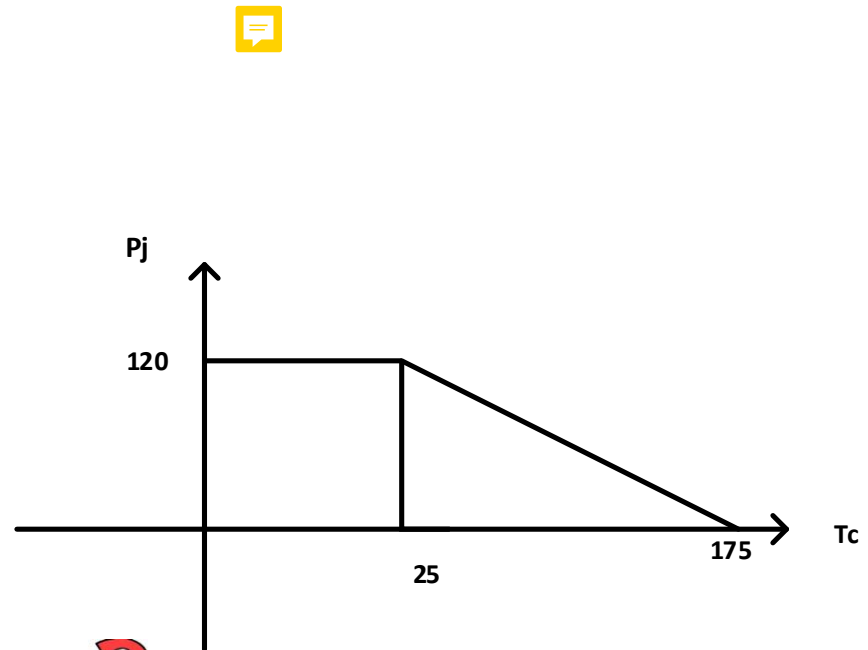What is the power that the transistor can dissipate if $T_a = 40^\circ\text{C}$?



$$T_{j,max} = 175^\circ\text{C}$$

$$T_{co} = 25^\circ\text{C}$$

$$P_{j,max} = 120\text{W}$$

Transistor and Heat sink

$$\theta_{jc} = \frac{T_{j,max} - T_{co}}{P_{j,max}}$$
$$= \frac{175 - 25}{120}$$

$$\theta_{jc} = 1.25 \text{ } ^\circ\text{C}/\omega$$


since $T_{co} = 25^\circ\text{C}$
, and $T_a = 40^\circ$

$$\therefore T_c > T_{co}$$

. region 2 $\rightarrow T_j = T_{j,max}$

$$T_j - T_a = \theta_{ja} P_j$$

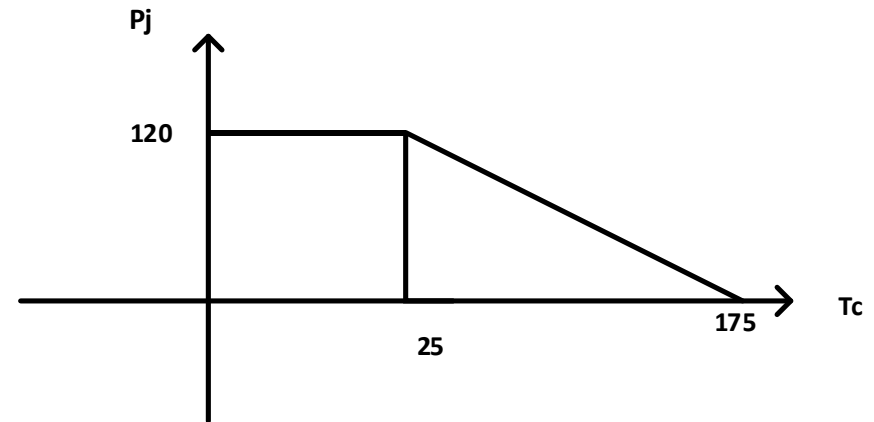
$$\theta_{ja} = \theta_{jc} + \theta_{cs} + \theta_{sa}$$



$$\theta_{ja} = 3.15 \text{ } ^\circ\text{C}/\omega$$

$$\therefore P_j = 42.8 \omega$$

To find T_c :

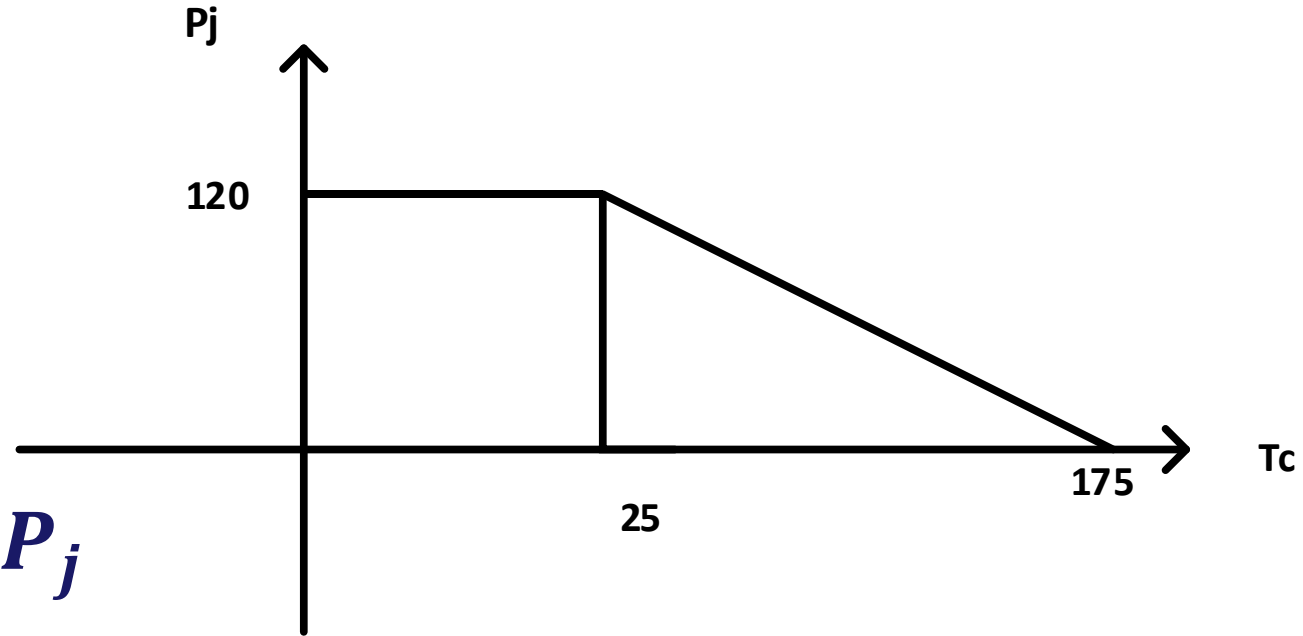

$$T_j - T_c = \theta_{jc} P_j$$

$$T_{j,max} - T_c = \theta_{jc} P_j$$

$$T_c = 121.5^\circ\text{C}$$

$$T_c > T_{co}$$

Region 2 as assumed

Transistor and Heat sink

If we are using infinite heat sink


$$\therefore T_c = T_a$$

$$\therefore \theta_{ca} = 0$$

$$\theta_{ja} = \theta_{jc} + \theta_{ca} = 1.25 \text{ } ^\circ\text{C}/\omega$$

$$T_j - T_a = \theta_{ja} P_j$$

$$\therefore P_j = 108 \omega$$

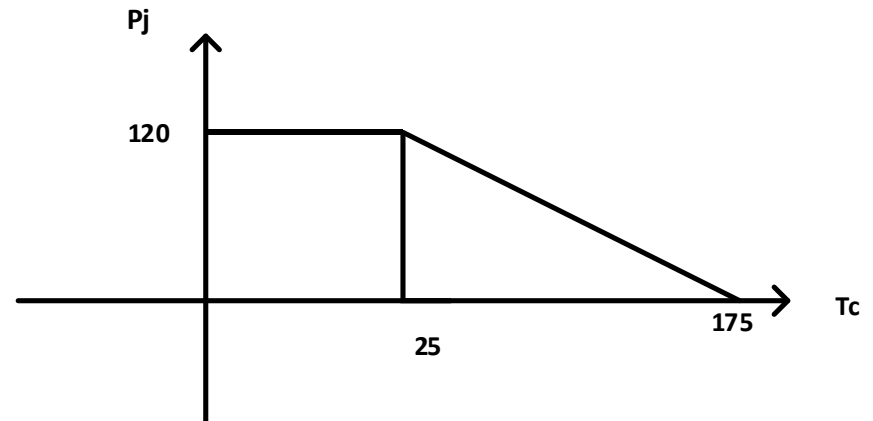

Transistor and Heat sink

For Operation in free air

(No special arrangement for cooling)

θ_{ja} depends on the type of the case in which the transistor is packed

$$\theta_{ja} = \left| \frac{1}{\text{slope}} \right|$$

$$\theta_{ja} = \frac{T_{j,max} - T_{ao}}{P_{j,max}}$$

