

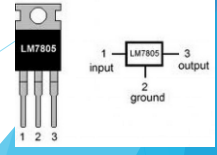
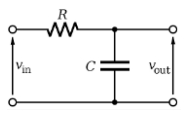



# Voltage Regulator

## Dc Power Supply

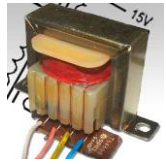

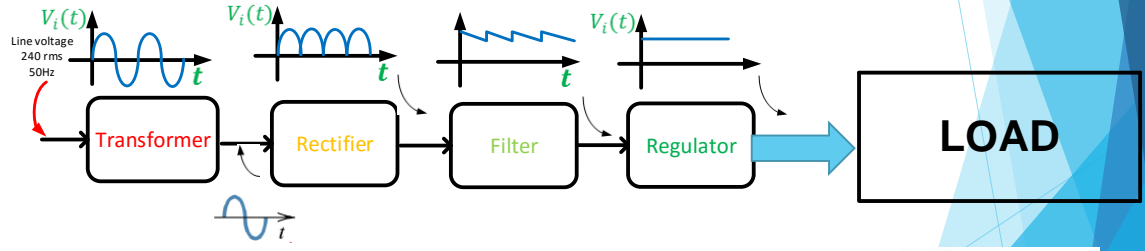- ▶ All electronic circuits and systems require a stable source of dc voltage and current ( or dc power) to operate correctly.



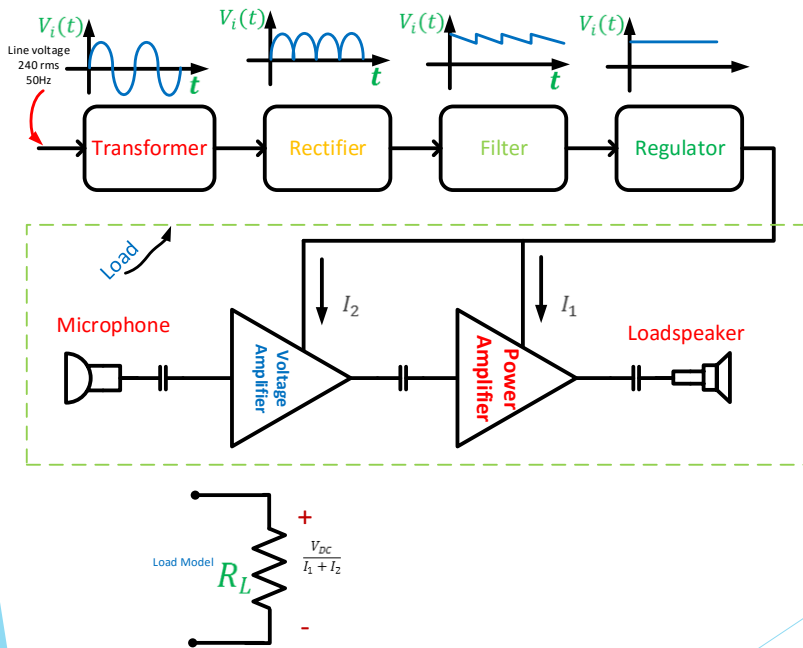

- **Transformer**: Used to increase or decrease the amplitude of the ac line voltage
- **Rectifier**: used to convert the ac voltage (zero-average value) into either positive and negative pulsating dc.
  - 1) Have- Wave Rectifier
  - 2) Full-Wave Rectifier
    - a) Center-tapped transformer full-wave Rectifier
    - b) Bridge full-wave rectifier
- **Filter** : used to smooth out the pulsating dc roduced by the rectifier by removing its ac ripple contents and passing its dc component ( average value)

- **Regulator:** used to maintain a constant DC output voltage under variations in the load current drawn from the supply and under variation in AC line voltage

To determine the effectiveness of the voltage regulator, we define two indicators


a) **Load regulation** =  $\frac{\Delta V_o}{\Delta I_L}$   
assuming  $V_S$  constant

b) **Line regulation** =  $\frac{\Delta V_o}{\Delta v_S}$   
assuming  $R_L$  fixed
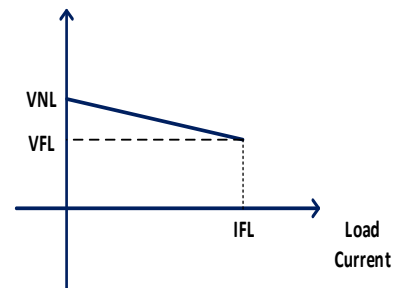
### Voltage Regulator


- An ideal power supply maintains a constant voltage at its output terminal, no matter what current it drawn from it.
- The output voltage of a practical power supply changes with load current.
- One measure of power supply performance is called percent voltage regulation.

$$Vr = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$



## Voltage Regulator

### Simple Voltage Regulator

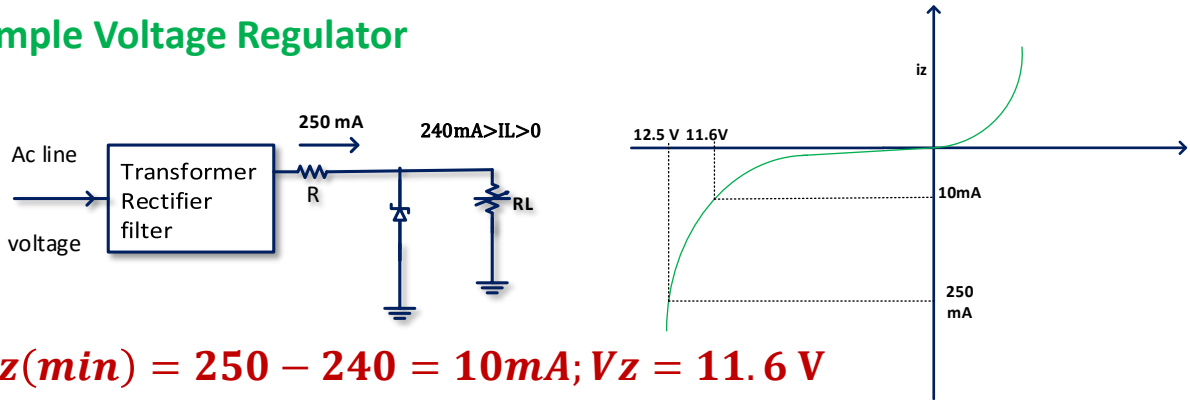

$$I_z(\min) = 250 - 240 = 10\text{mA}; V_z = 11.6\text{ V}$$


$$I_z(\max) = 250 - 0 = 250\text{mA}; V_z = 12.5\text{ V}$$

$$\Delta V_o = \Delta V_z = 12.5 - 11.6 = 0.9\text{ V}$$

$$P_d = V_z I_z$$



$$P_{d,\max} = V_z(\max) I_z(\max)$$
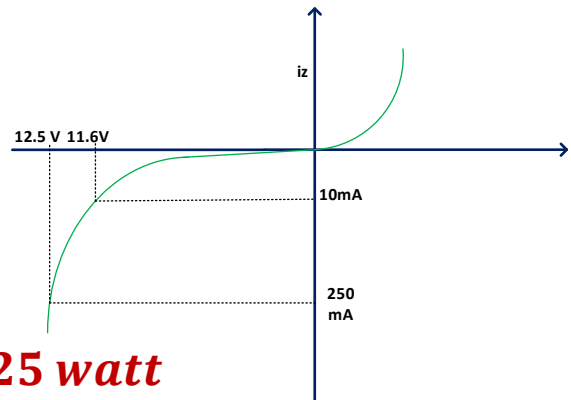
$$P_{d,\max} = 12.5 \times 250 = 3.125\text{ watt}$$



## Voltage Regulator

### Simple Voltage Regulator

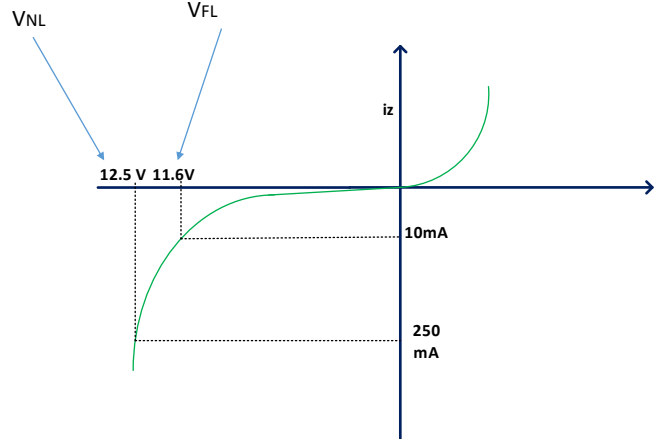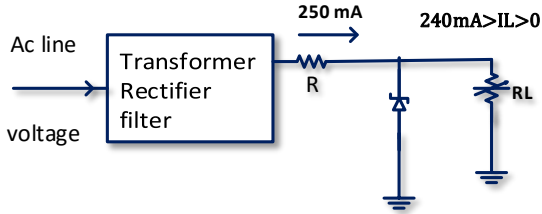



$$V_r = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$V_r = \frac{12.5 - 11.6}{11.6} \times 100\%$$

$$V_r = 7.6\%$$

## Voltage Regulator


### Simple Voltage Regulator

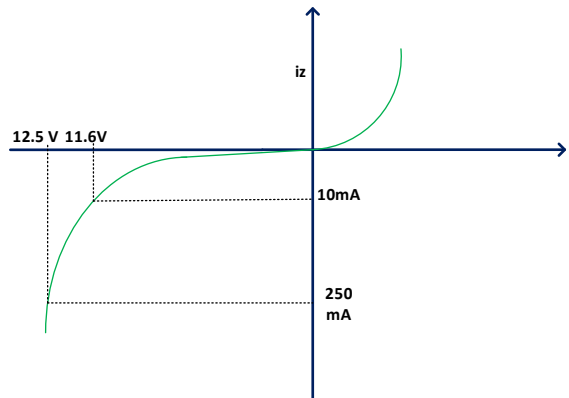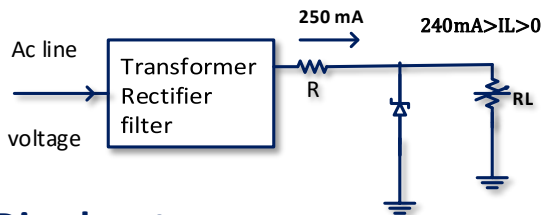

### **Disadvantages:**

1. Variation in  $I_L$  will cause  $I_z$  to vary. This in turns will cause variation in  $V_z = V_o$
2. The Zener power dissipation will increase as  $I_L$  decreases.

Transistorized Voltage regulator

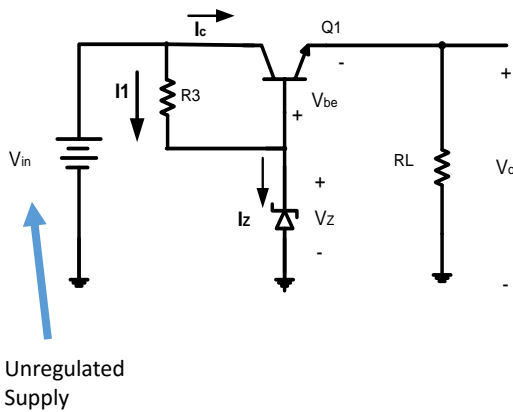

$$V_o = V_Z - V_{BE}$$

$$V_{BE} = V_Z - V_o$$

$$I_C = I_S \left( e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

If  $V_o \downarrow$ ,  $(V_{BE} = V_Z - V_o) \uparrow$ ,  
 $I_C \uparrow, V_o \uparrow$

Example

Calculate the output voltage and Zener current for  $R_L=1k\Omega$ .

Solution:

$$V_o = V_Z - V_{BE} = 12 - 0.7 = 11.3 \text{ V}$$


$$I_E = 11.3 / 1K = 11.3 \text{ mA}$$

$$I_Z = I_E - I_B$$


$$I_1 = (20 - 12) / 220 = 36 \text{ mA}$$

$$I_B = I_E / \beta + 1$$


$$I_Z = 35.78 \text{ mA}$$

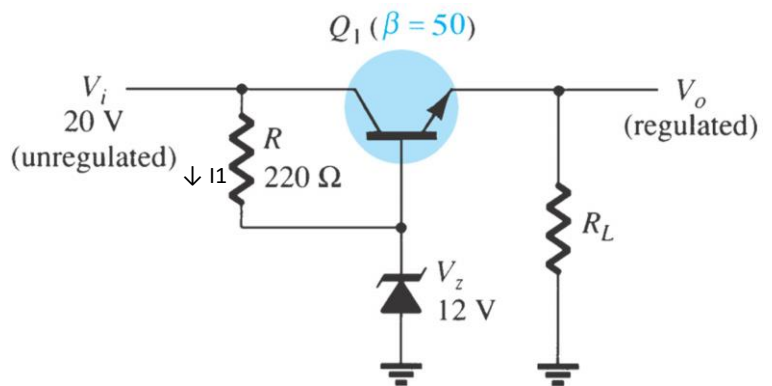

# Types of Regulators

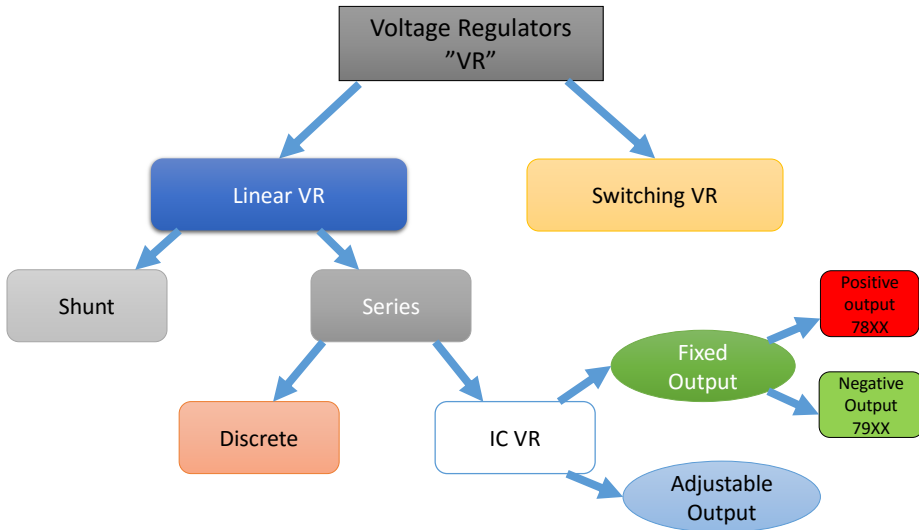


# Types of Regulator

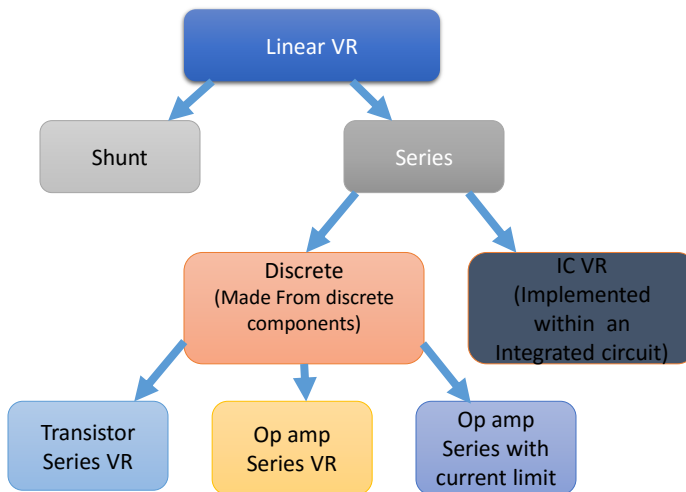
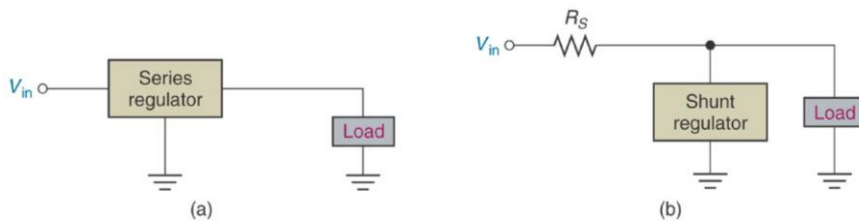
## Types of Regulator

- Fundamental classes of voltage regulators are **linear regulators** and **switching regulators**.
- Two basic types of linear regulator are the **series regulator** and the **shunt regulator**.
- The series regulator is connected in **series** with the load and the shunt regulator is connected in **parallel** with the load.




### Series and shunt Regulators

- The purpose of a regulator is to eliminate any output voltage variation that might occur because of
  - changes in load currents,
  - changes in ac line Voltage ,
  - or changes in temperature.
- It monitors the output voltage and generates feedback signal that automatically Increases or decreases the supply voltage as necessary to compensate for any tendency of the output voltage to change.



## Voltage Regulator

### Series Regulators


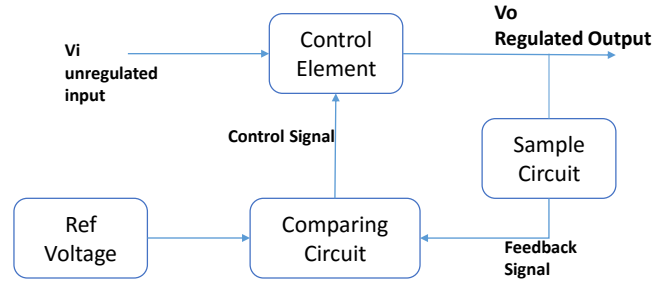


**Control element: is a device whose operating state adjusts as necessary to maintain a constant  $V_o$ .**

**It is in series path between  $V_i$  and  $V_o$**

## Voltage Regulator

### Series Regulators

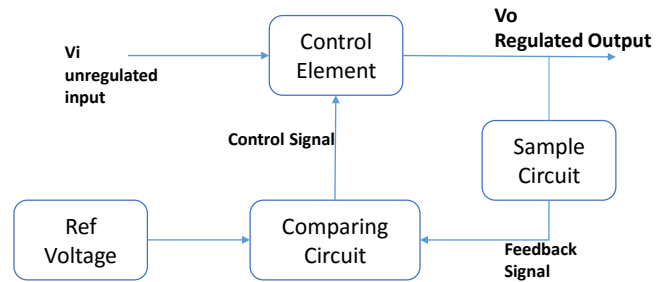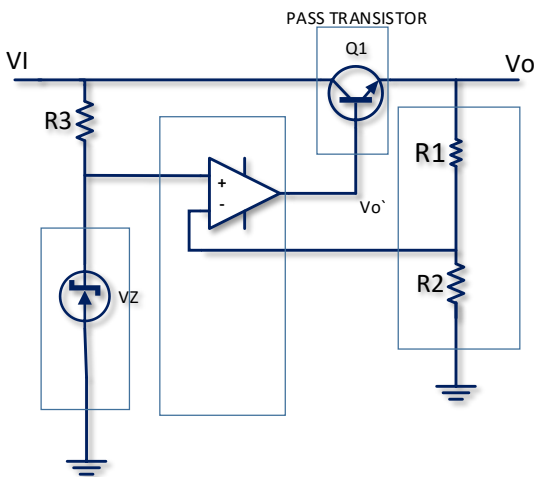

## Voltage Regulator

### Series Regulators

### An Op-amp used in series voltage regulators

$$V(-) = \frac{R2}{R1 + R2} V_o$$

$$V(+) = V_Z$$

$$V(-) = V(+)$$


$$V_o = V_Z \left( 1 + \frac{R1}{R2} \right)$$

#### Operation:

$$V_{o'} = A_d V_d$$

$$V_{o'} = A_d \left( V_Z - \frac{R2}{R1+R2} V_o \right)$$

$$V_{BE} = V_{o'} - V_o$$

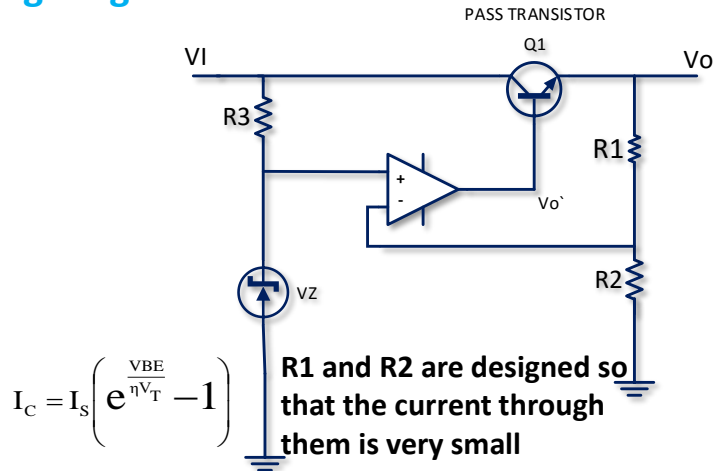


$$I_C = I_S \left( e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

Assume  $V_o \downarrow$ ,  $V_{o'} \uparrow$ ,  $V_{BE} \uparrow$ ,  $I_E \uparrow$ ,  $V_o \uparrow$
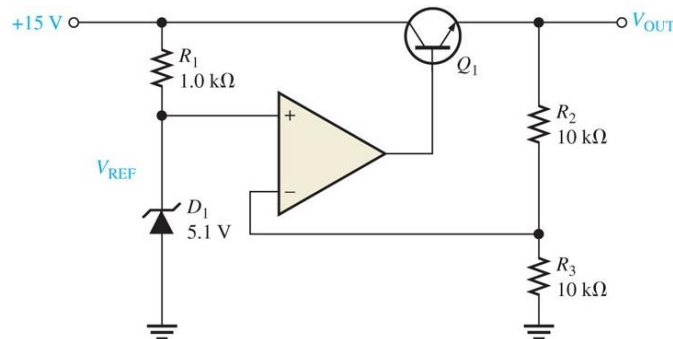
## Example

Determine the output voltage for the regulator below.

$$V_o = \left( 1 + \frac{R_2}{R_3} \right) V_Z \quad \Rightarrow \quad V_o = \left( 1 + \frac{10k}{10k} \right) 5.1 = 10.2 \text{ V}$$



## Voltage Regulator

### An Op-amp used in series voltage regulators

#### Current Limiting:

$$R_{sc} = \frac{0.7}{I_L(\max)}$$

- In normal operation  
Q2 is off ( $V_{BE2} < 0.7V$ )

$$I_{B1} = I_o; I_L = I_E = \beta \cdot I_o$$


- when  $I_L = I_L(\max)$

$$V_{BE2} = 0.7V$$

Q2 turns on;


$$I_o = I_{B1} + I_{C2}$$

Q1 will conduct less current

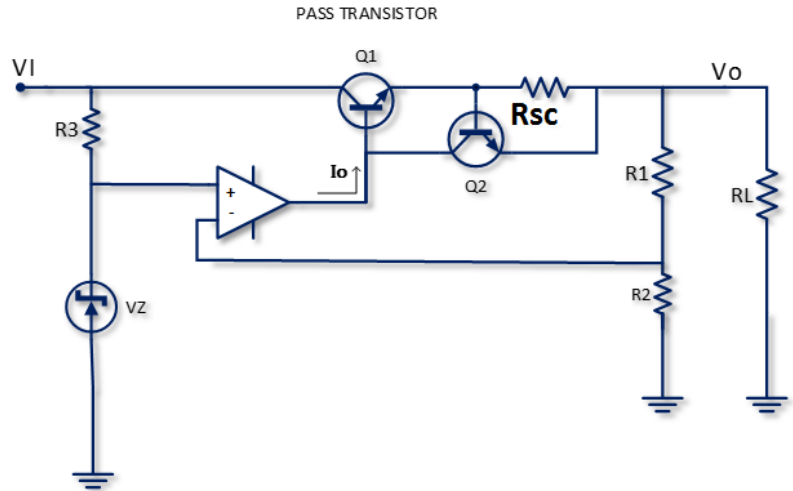
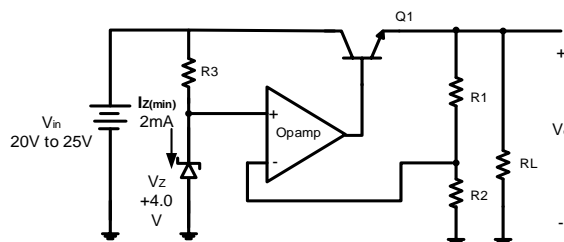
## Voltage Regulators example

- Given the following series voltage regulator
- 1) Complete the design of the following voltage regulator (Find of  $R1$ ,  $R2$  and  $R3$ ) assuming that the voltage across the load resistor  $R_L$  is equal to 12V. Assume  $I_z(\min) = 2mA$ .
- 2) Show how to modify the circuit to limit the load current to 1A.
- 3) Find the output voltage for the modified circuit of part 2) when the load resistor  $R_L = 100\Omega$  and when  $R_L = 8\Omega$ .
- 4) Choose a transistor with suitable power rating



1) Complete the design of the following voltage regulator (Find of R1, R2 and R3) assuming that the voltage across the load resistor  $R_L$  is equal to 12V. Assume  $I_{z(\min)} = 2\text{mA}$ .

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z = 12 \text{ V}$$

$$\therefore \frac{R_1}{R_2} = \frac{V_o}{V_Z} - 1 = \frac{12}{4} - 1 = 2$$


➔ choose  $R_1 = 20 \text{ k}\Omega$   
 $\therefore R_2 = 10 \text{ k}\Omega$

$$I_Z > I_{Z(\text{Min})} = \frac{V_{\text{IN}(\text{Min})} - V_Z}{R_3}$$




$$R_3 \leq \frac{V_{\text{IN}(\text{Min})} - V_Z}{I_{Z(\text{Min})}}$$
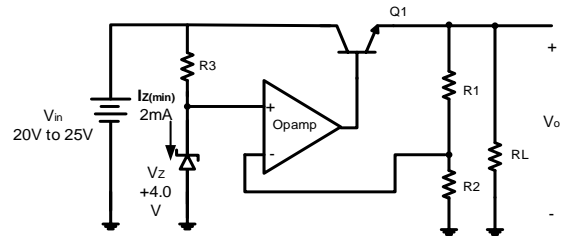
$$R_3 \leq \frac{20 - 4}{2 \text{ mA}} = 8 \text{ k}\Omega$$



## Voltage Regulators

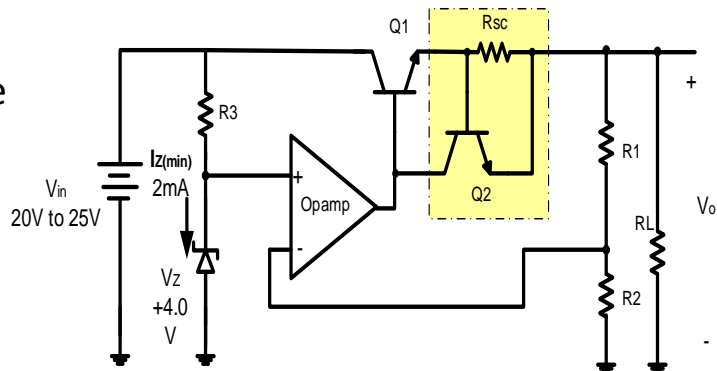
2) Show how to modify the circuit to limit the load current to 1A.



The change for current limit is done by adding Q2 and Rsc as shown

$$\& R_{SC} = \frac{V_{BE}}{I_{L(\text{Max})}} = \frac{0.7 \text{ V}}{1 \text{ A}} = 0.7 \Omega$$

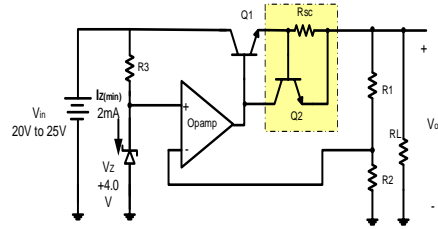3) Find the output voltage for the modified circuit of part 2) when the load resistor  $R_L = 100\Omega$  and when  $R_L = 8\Omega$ .



For  $R_L = 100 \text{ ohm}$ ,  $V_o = 12\text{V}$ , then  $I_L = \frac{12\text{V}}{100\Omega} = 0.12\text{A}$

which is smaller than  $I_{L(\text{max})}$ ,

$\therefore V_o = 12 \text{ V}$  and is not affected by the current limit circuit

For  $R_L = 8 \text{ ohm}$ ,  $V_o = 12\text{V}$ , then  $I_L = \frac{12\text{V}}{8\Omega} = 1.5\text{A}$

which is bigger than  $I_{L(\text{max})}$ , and the current limit circuit

limits the current to the maximum allowable value which is 1 A

$\therefore V_o = I_{L(\text{Max})} * R_L = 1\text{A} * 8\Omega = 8 \text{ V}$

4) Choose a transistor with suitable power rating

$$I_C \approx I_E$$


$$P_{C,\text{MAX}} = V_{CE(\text{MAX})} * I_{C(\text{MAX})}$$

$$V_{CE(\text{MAX})} = V_{IN(\text{MAX})} - V_{O(\text{MIN})} = 25 - 8 = 17 \text{ V}$$

$$I_{E(\text{MAX})} = I_{R1} + I_{L(\text{MAX})} = \frac{V_Z}{R_2} + I_{L(\text{MAX})}$$

$$= \frac{4 \text{ V}}{10 \text{ k}\Omega} + 1 \text{ A} = 1.0004 \text{ A}$$

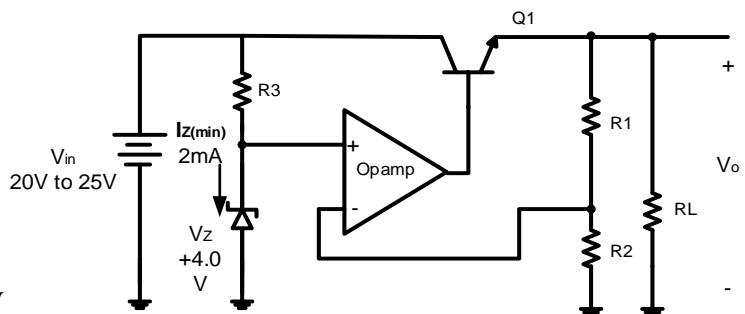
$$P_{C,\text{MAX}} = 17 \text{ V} * 1.0004 \text{ A} = 17.0068 \text{ W}$$



## Voltage Regulator


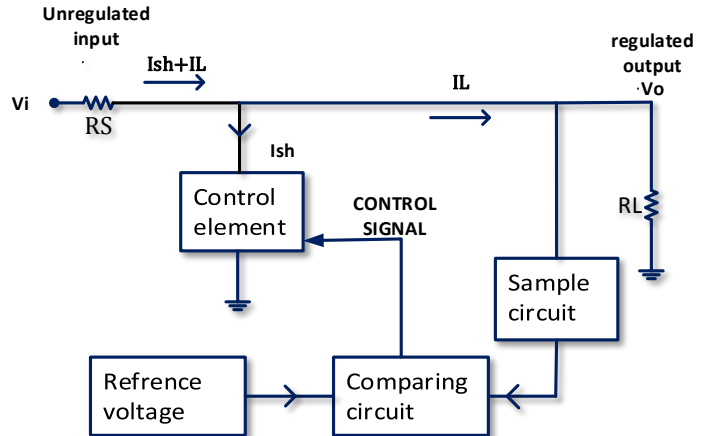
### Shunt Regulators

- The Control element is in parallel with the load



- The control element maintains a constant load voltage by shunting more or less current from the load
- When the load voltage decrease, the control element shunt less current

### Shunt Regulators

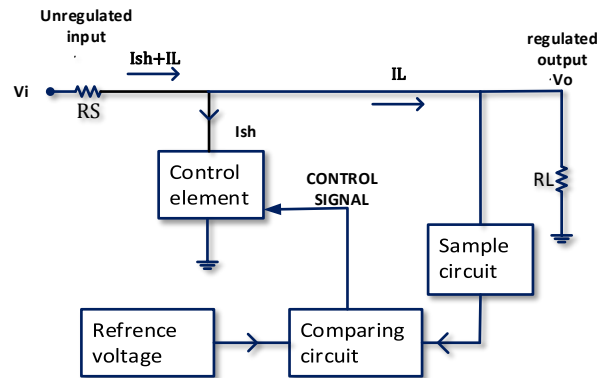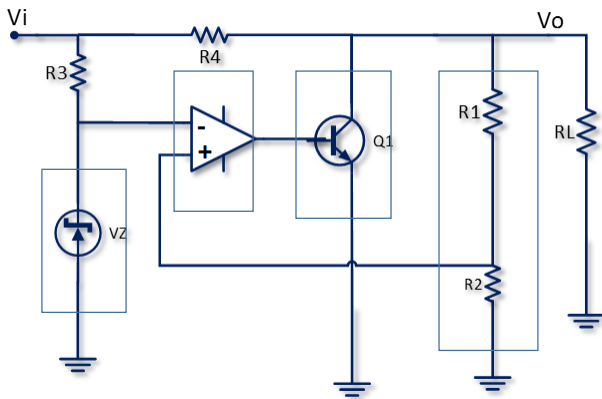

## An Op-amp used in Shunt voltage regulators


$$V_o = V_z \left( 1 + \frac{R_1}{R_2} \right)$$

Operation:

$$V_{op} = A_d V_d$$

$$V_{op} = A_d \left( \frac{R_2}{R_1 + R_2} V_o - V_z \right)$$

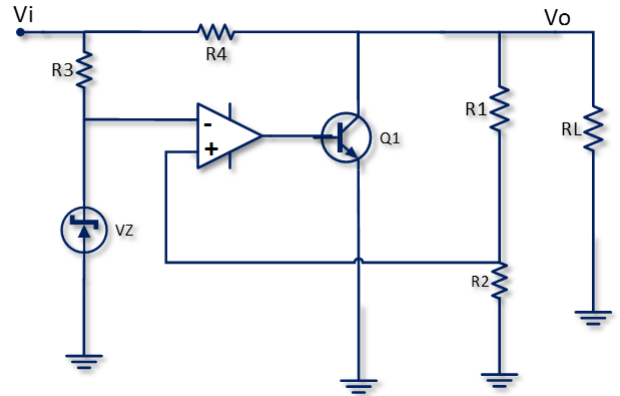IF  $V_o \downarrow$ ,  $V(+)$   $\downarrow$ ,  $V_{op} \downarrow$ ,  $V_{BE} \downarrow$




$$V_{BE} = V_{op}$$


$\therefore$  The transistor conduct Less,  $I_c \downarrow$ ,  $I_L \uparrow$ ,  $V_o \uparrow$   $I_C = I_s \left( e^{\frac{V_{BE}}{nV_T}} - 1 \right)$
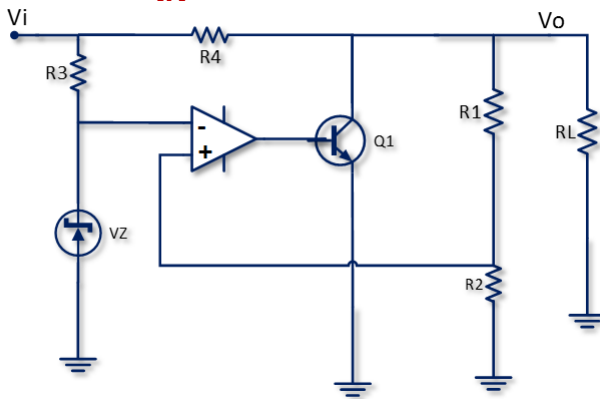
## Current Limiting

$$I_{L, \max} = \frac{V_i}{R_4} \text{ (Current Limiting) When } R_L = 0 \text{ (SHORTED)}$$



# IC Voltage Regulator

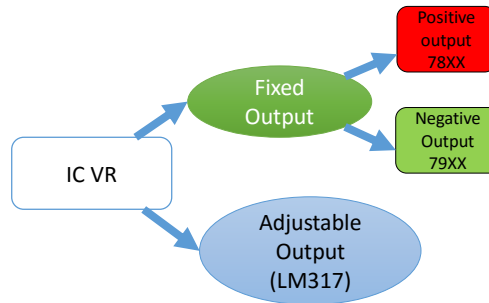

## Voltage Regulator

### Three Terminal Circuit Regulators

#### 1- Fixed voltage regulator

##### a-78xx

7805.....5 V

7812.....12 V



7815.....15V

##### b- 79xx

7905..... -5 V

7912..... -12 V

7915..... -15V

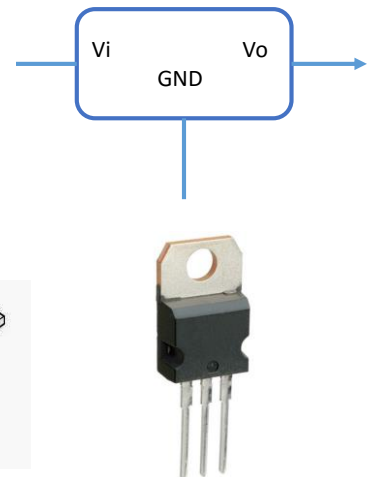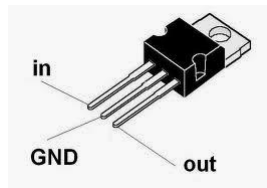



# Fixed Voltage Regulator

## Positive-Voltage Regulators in the 78XX Series

IC Part	Output Voltage (V)	Minimum $V_i$ (V)
7805	+5	+7.3
7806	+6	+8.3
7808	+8	+10.5
7810	+10	+12.5
7812	+12	+14.5
7815	+15	+17.7
7818	+18	+21.0
7824	+24	+27.1

$V_{in}$  must be higher than  $V_o$  by at least 2V for proper operation of the voltage regulator

# Fixed Voltage Regulator


## Negative-Voltage Regulators in the 79XX Series

IC Part	Output Voltage (V)	Minimum $V_i$ (V)
7905	-5	-7.3
7906	-6	-8.4
7908	-8	-10.5
7909	-9	-11.5
7912	-12	-14.6
7915	-15	-17.7
7918	-18	-20.8
7924	-24	-27.1

## Voltage Regulator

### Three Terminal Circuit Regulators


#### Dc Power Supply

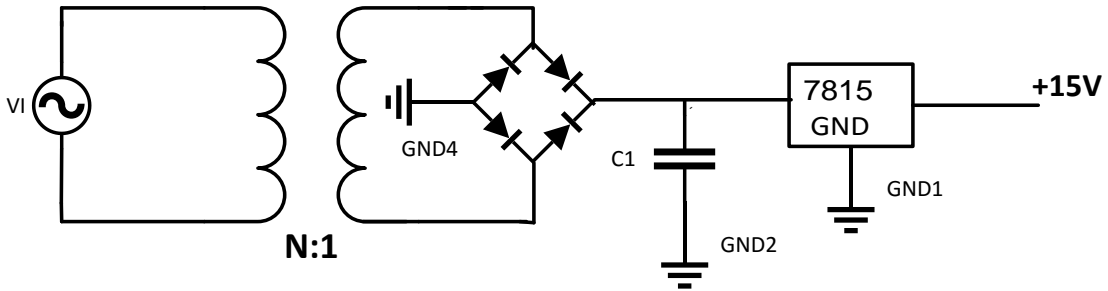

## Voltage Regulator

### Three Terminal Circuit Regulators

#### Dual Polarity Dc Power Supply

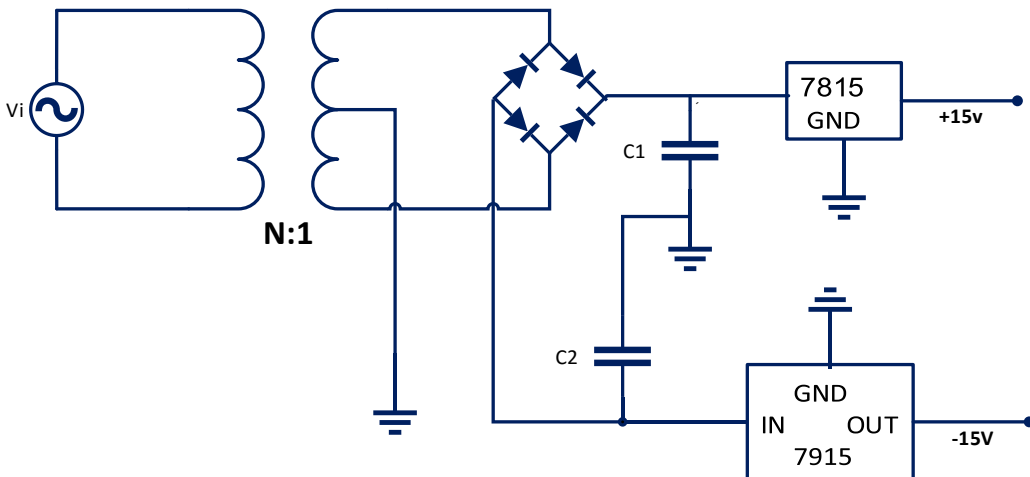

## Voltage Regulator


### Changing the fixed Voltage Regulator to adjustable

$$V_O = V_{REG} + R_2 I_2$$

$$V_O = V_{REG} + R_2 (I_1 + I_Q)$$

$$I_1 = \frac{V_{REG}}{R_1}$$

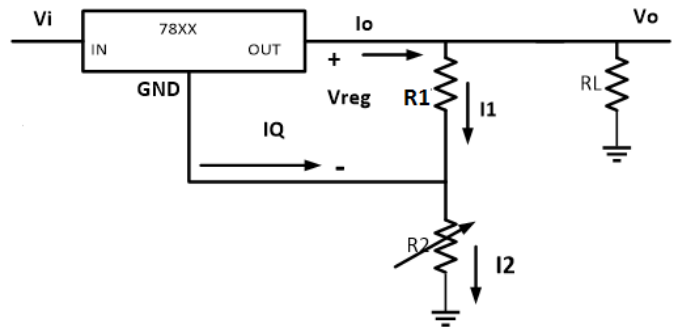
$$\therefore V_O = V_{REG} \left(1 + \frac{R_2}{R_1}\right) + R_2 I_Q$$



$I_Q$  is in milliampere and change with temperature
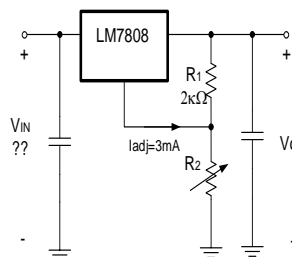
### Example

- Find the minimum and maximum output voltage ( $V_o$ ) for the following IC voltage regulator. Note that  $R_2$  is a variable resistor that can be varied from 0 to  $3k\Omega$
- What is the range of values of  $V_{IN}$  required for proper operation of the circuit
- What is the power dissipation of the LM7808 when  $V_o = V_o(\min)$  and  $V_{in} = V_{in}(\max)$  and load current =  $0.25A$




Find the minimum and maximum output voltage ( $V_o$ ) for the following IC voltage regulator.  
Note that  $R_2$  is a variable resistor that can be varied from 0 to  $3k\Omega$

$$\therefore V_o = V_{REG} \left(1 + \frac{R_2}{R_1}\right) + R_2 I_Q$$

$$V_{O(MIN)} = V_{REG} = 8 \text{ V (when } R_2 = 0 \Omega)$$
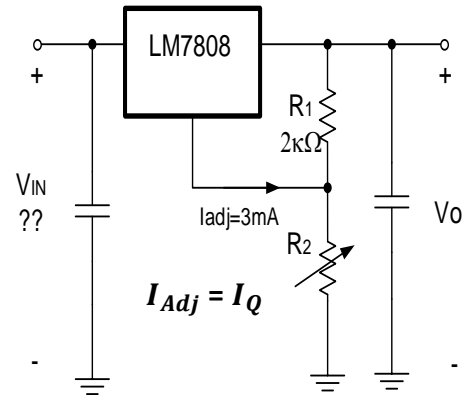
$$\begin{aligned} V_{O(MAX)} &= \frac{V_{REG}}{R_1} (R_1 + R_2) + I_Q (R_2) \\ &= \frac{8V}{2k\Omega} (2k\Omega + 3k\Omega) + 3mA \cdot (3k\Omega) \\ &= (4mA) \cdot (5k\Omega) + 9V = 29V \text{ (when } R_2 = 3k\Omega) \end{aligned}$$



What is the range of values of  $V_{IN}$  required for proper operation of the circuit ?

$V_{in}$  must be higher than  $V_o$  by at least 2V

$$\text{when } V_o = 8V, V_{IN(MIN)} = 8 + 2 = 10 \text{ V}$$


$$\text{when } V_o = 29V, V_{IN(MAX)} = 29 + 2 = 31 \text{ V}$$

What is the power dissipation of the LM7808 when  $V_o = V_o(\min)$  and  $V_{in} = V_{in}(\max)$  and load current = 0.25A ?

$$I_o = I_L + I_1 = 0.25A + 4mA = 0.254A$$

Power Dissipation of LM7808 :

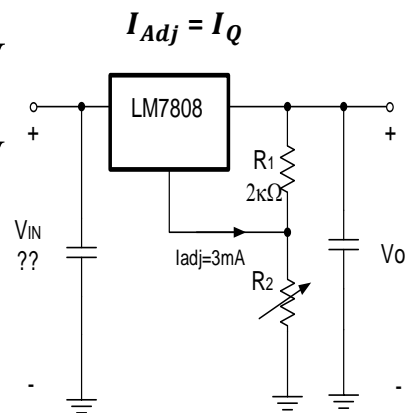
$$P_{(LM7808)} = (V_{IN} - V_O) * I_O = (31 - 8) * 0.254 = 5.842 \text{ W}$$



# Adjustable-Voltage Regulator
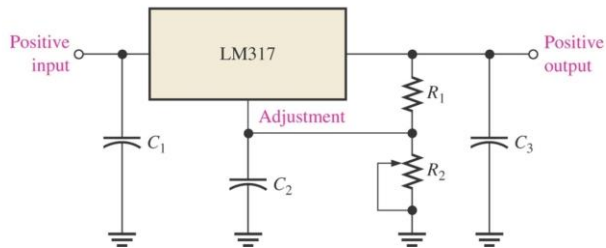
## Adjustable-Voltage Regulator

- Voltage regulators are also available in circuit configurations that allow to set the output voltage to a desired regulated value.
- The LM317 is an example of an adjustable-voltage regulator, can be operated over the range of voltage from 1.25 to 35 V.




## Voltage Regulator

### 2- Adjustable Voltage regulator

$$I_Q = 50\mu A \rightarrow 100\mu A \quad I_{Adj} = I_Q$$

$$I_{o,max} = 1.5 \text{ A}$$

$$V_{REG} = 1.25 \text{ V}$$

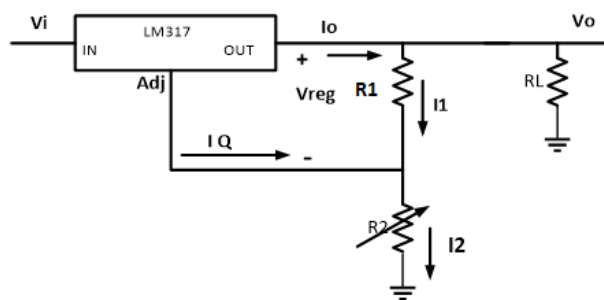


$$V_O = V_{REG} + R_2 I_2$$

$$V_O = V_{REG} + R_2 (I_1 + I_Q)$$

$$I_1 = \frac{V_{REG}}{R_1}$$

$$\therefore V_O = V_{REG} \left(1 + \frac{R_2}{R_1}\right) + R_2 I_Q$$

## IC REGULATOR WITH BOOSTER CURRENT

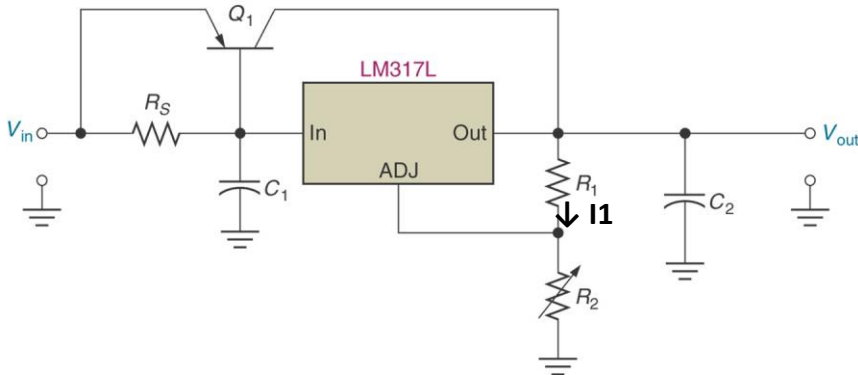


IC regulators are limited to a maximum allowable current before shutting down. The circuit shown uses an external pass transistor to increase the maximum available load current

When  $I_O$  is less than  $I_{O,max}$ ,  $V_{EB1} < 0.7\text{ V}$  So that the Q1 is OFF

When  $I_O$  is equal to  $I_{O,max}$ ,  $V_{EB1} = 0.7\text{ V}$  So that the Q1 is on and  $I_L = I_{O,max} + I_{C1} - I_1$

43

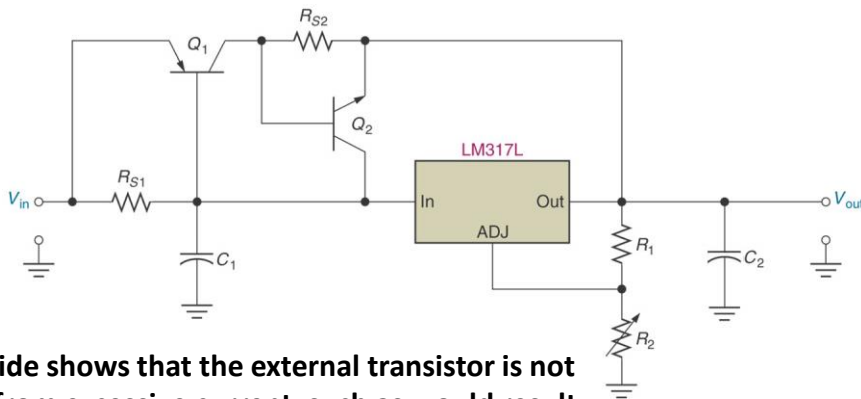

Previous slide shows that the external transistor is not protected from excessive current, such as would result from shorted output. An additional current-limiting circuit (Q2 and Rs2) can be added to protect Q1 from excessive current and possible burn out.

When  $I_{C1}$  is equal to  $I_{C1,max}$ ,  $V_{BE2} = 0.7\text{ V}$  So that the Q2 is on and  $I_L = I_{C1,max} + I_{O1,max} + I_{E2} - I_1$

2

## Types of Voltage Regulators

- **Linear Power Supply.**
  - Used power devices that operated at linear/active region.
  - Dissipates more power.
- **Non-Linear Power Supply.**
  - Used power devices that operated at saturation and cutoff alternately.
  - Dissipates less power.
  - Also named as switching power supply or switching regulator.

### Voltage Regulator

#### Switching Mode regulator

##### The Switching mode regulator components

**Q1:** control element; switch

**L & C:** form a low-pass filter


**D1:** used to suppress the negative voltage transient generated by the inductor when Q2 turns off

**DZ :** Zener diode to provide a reference voltage.

**R1 & R2 :** sample circuit


**Op Amp :** Comparing circuit

**P.W.M :** pulse width modulator

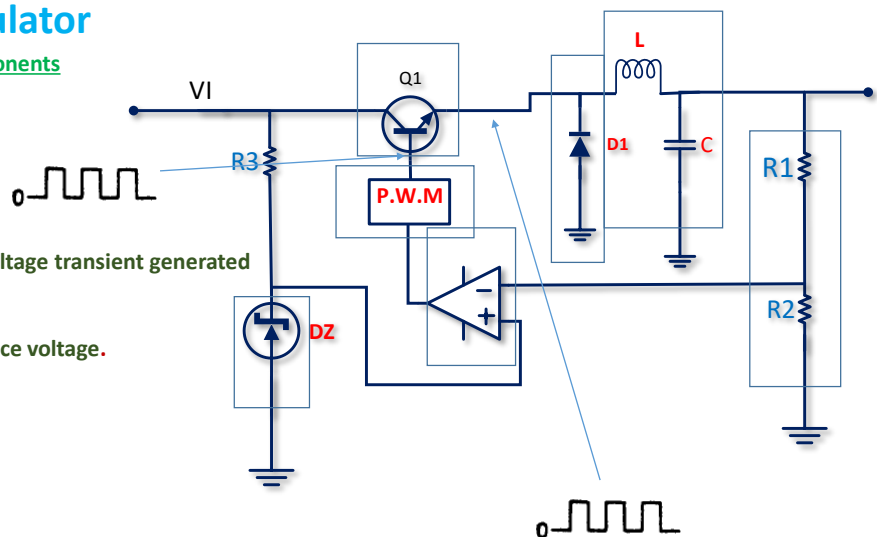

### Voltage Regulator

#### Switching Mode regulator

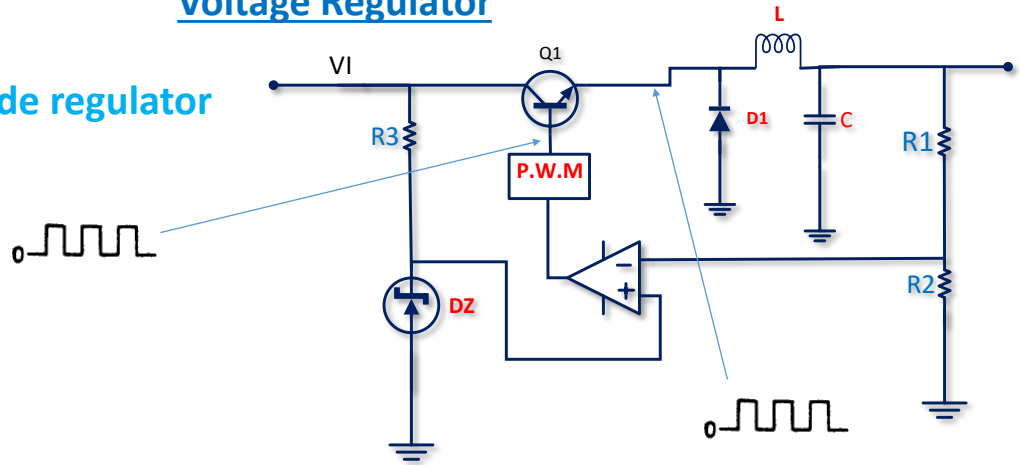


The fundamental component of a switching regulator is a pulse width modulator: P.W.M

P.W.M produces a train of rectangular pulses having width that are proportional to the Device's input.


### Voltage Regulator

#### Switching Mode regulator

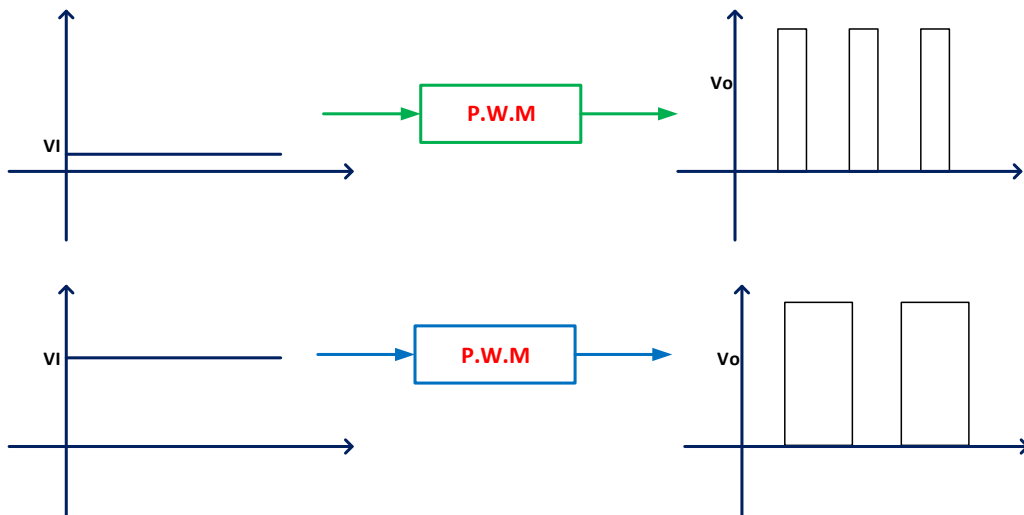




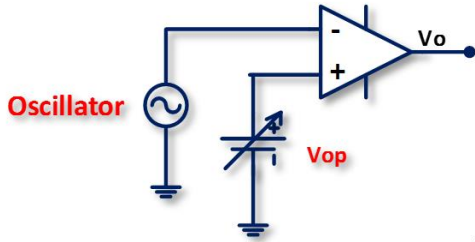
## Voltage Regulator Pulse width Modulator Circuit (P.W.M)





When  $V(+)> V(-)$  ;  $V_o(t) = V_{sat} = V$

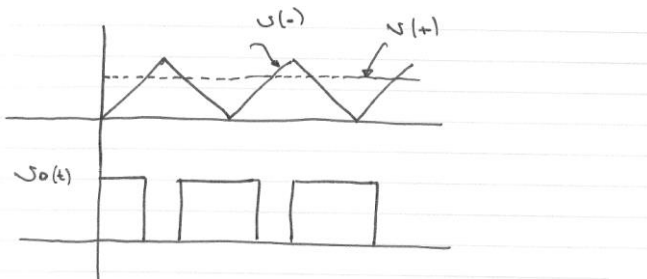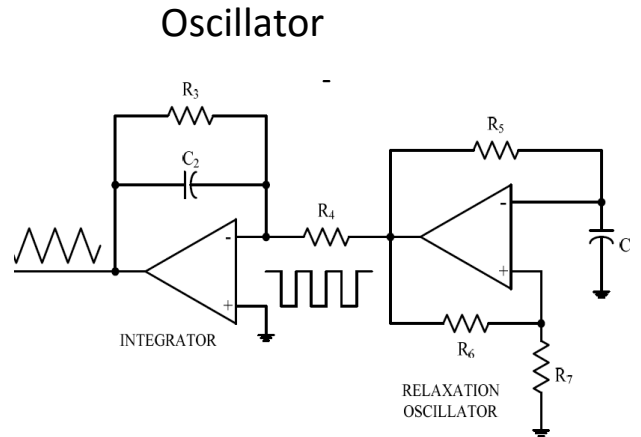When  $V(+)< V(-)$  ;  $V_o(t) = -V_{sat} = 0$



When  $V(+)> V(-)$  ;  $V_o(t) = V_{sat} = V$

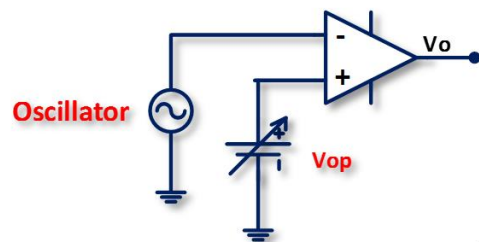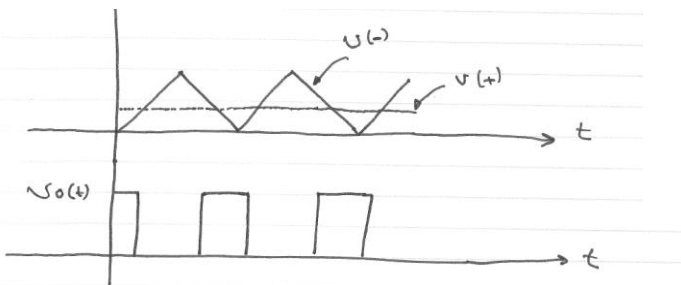When  $V(+)< V(-)$  ;  $V_o(t) = -V_{sat} = 0$



## Voltage Regulator


### Pulse width Modulator Circuit (P.W.M)

$$V_{o,dc} = \frac{1}{T} \int_0^T V_o(t) dt$$

$$V_{o,dc} = \frac{1}{T} (V \cdot Th)$$

$$V_{o,dc} = \frac{Th}{T} \cdot V$$

$$V_{o,dc} = D \cdot V$$

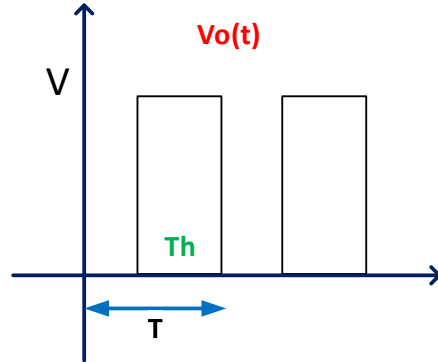

∴ The dc value of a pulse train is directly proportional to its duty cycle


### Switching Mode regulator

Operation :

$$V_{op} = A_d v_d$$

$$V_{op} = A_d (V_z - R_2 \cdot V_o / (R_1 + R_2))$$

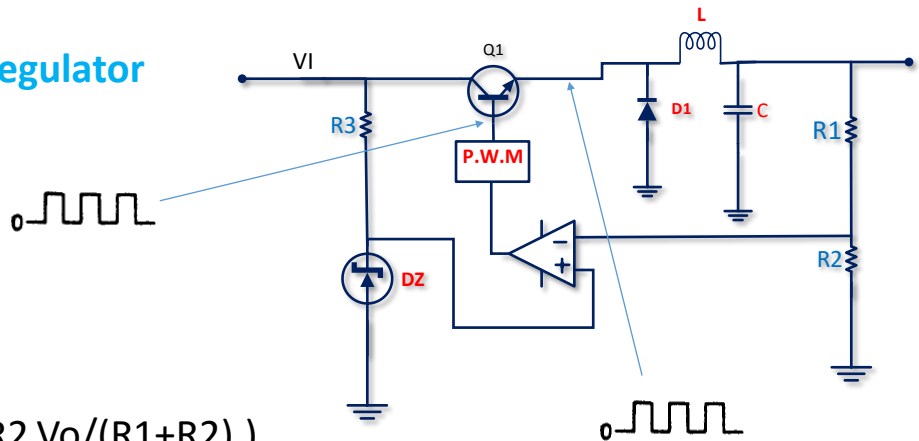$V_o \downarrow$  ,  $V_{op} \uparrow$  , Duty cycle  $\uparrow$  ,  $V_o \uparrow$



## Voltage Regulator

### Pulse width Modulator Circuit (P.W.M)

- A switching mode regulator uses a pulse width modulator to produce a pulse train whose duty cycle is automatically adjusted as necessary to increase or decrease the dc values of the train
- If the load voltage  $V_o$  tends to fall, then the output of the Op Amp increases and a larger voltage is applied to the pulse width modulator
- It therefore produces a pulse train having a larger duty cycle.
- The pulse train switches Q1 on and off with a greater duty cycle, so the dc values of the load voltage raise.

