

Oscillators

Oscillators

Role of oscillators:

*oscillators are used to generate signal

*it converts power from the dc power supply into an ac power

Harmonic oscillators → sinusoidal wave form

Relaxation oscillators → produce non sinusoidal

They are used in :

- 1. Electronic Communication Devices .**
- 2. Lab.**

Oscillators


For the circuit to operate as an oscillator it must satisfy the Barkhausen criterial for sustained oscillation.

#1-The feedback must be positive ,this means that the feedback signal must be phased so that it adds to the amplifiers input signal .

#2-The loop gain (AB) must be greater than unity to allow oscillation to build up and equal to unity to sustain the oscillation .

Audio frequency Oscillators


1) Phase-shift Oscillator

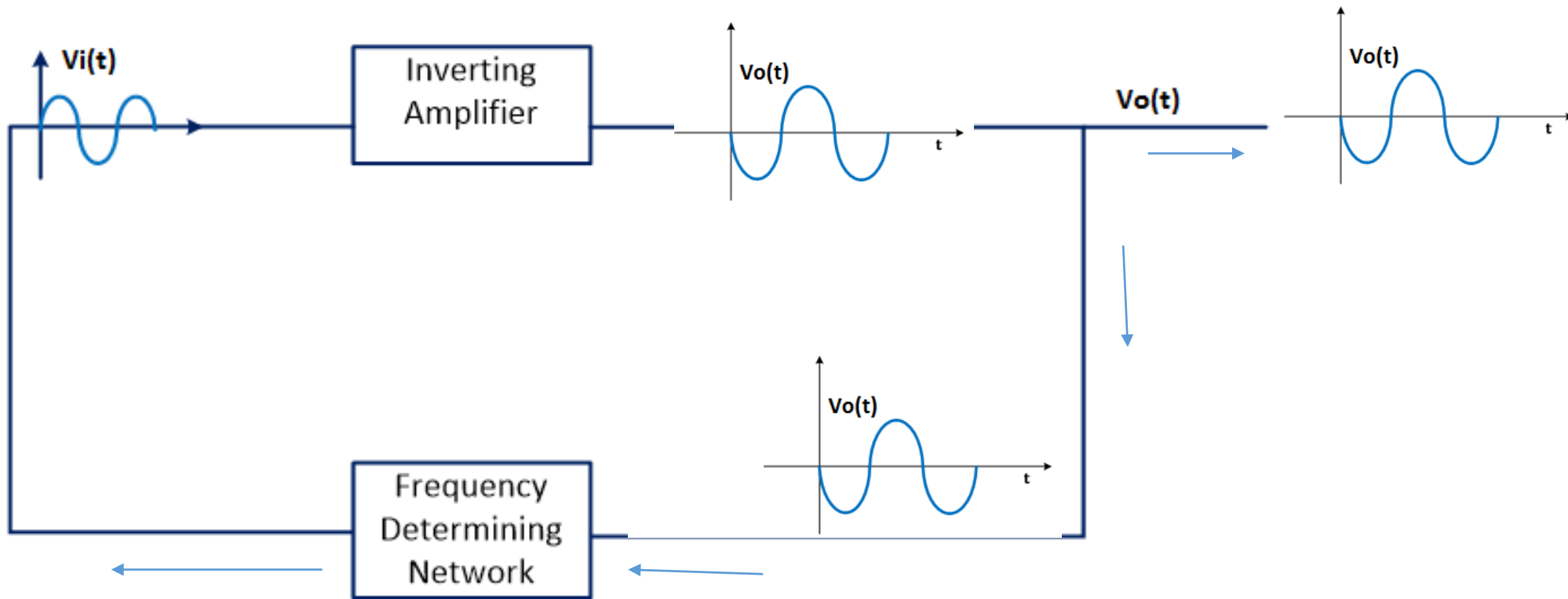

180 phase shift at ω_0

Audio frequency Oscillators

1) Phase-shift Oscillator

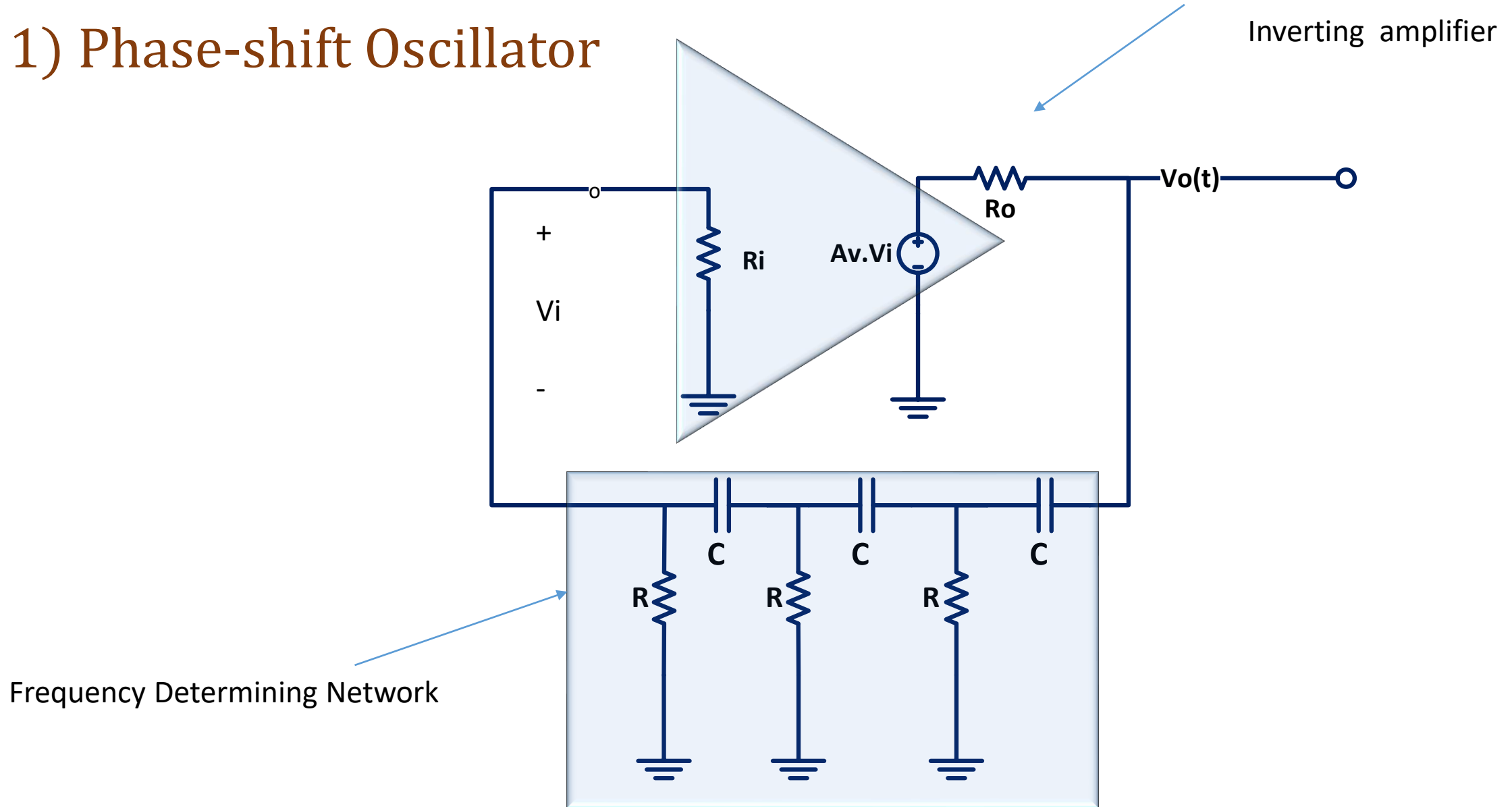

Oscillators

1) Phase-shift Oscillator


To find $\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$(R - j\frac{1}{\omega C}) I_1 - RI_2 = V_i$$


$$-RI_1 + (2R - j\frac{1}{\omega C}) I_2 - RI_3 = 0$$

$$-RI_3 + (2R - j\frac{1}{\omega C}) I_3 = 0$$
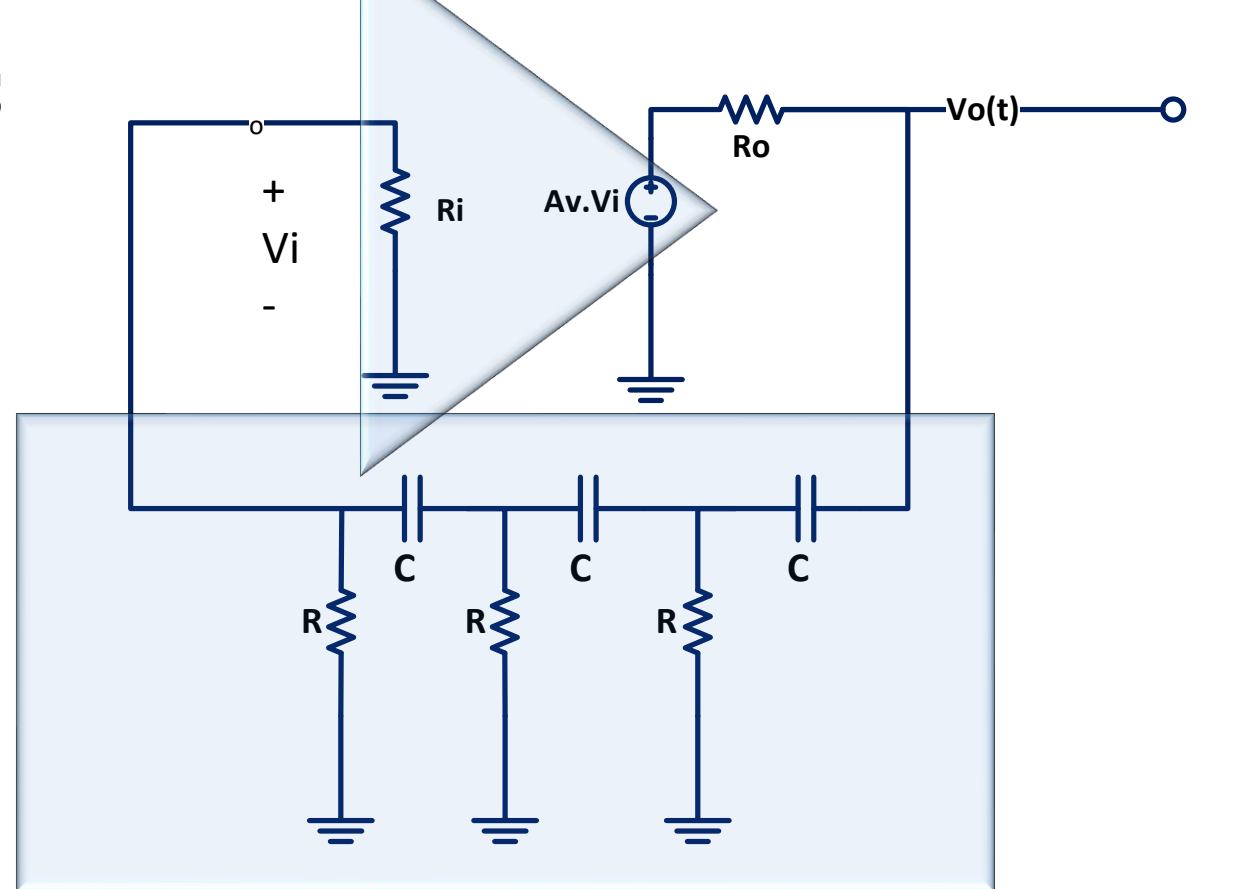
$$I_3 = \frac{R^2 V_i}{R^3 - \frac{5R}{\omega^2 C^2} + j(\frac{1}{\omega^3 C^3} - \frac{6R^2}{\omega C})}$$



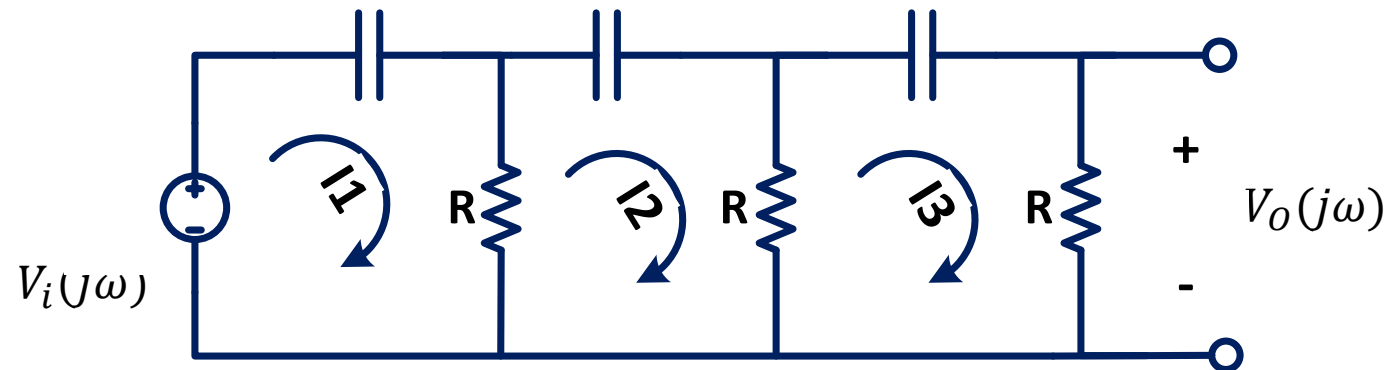$1/j\omega C$ $1/j\omega C$ $1/j\omega C$ $R_i \gg R$




Oscillators

1) Phase-shift Oscillator


To find $\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$I_3 = \frac{R^2 V_i}{R^3 - \frac{5R}{\omega^2 C^2} + j\left(\frac{1}{\omega^3 C^3} - \frac{6R^2}{\omega C}\right)}$$
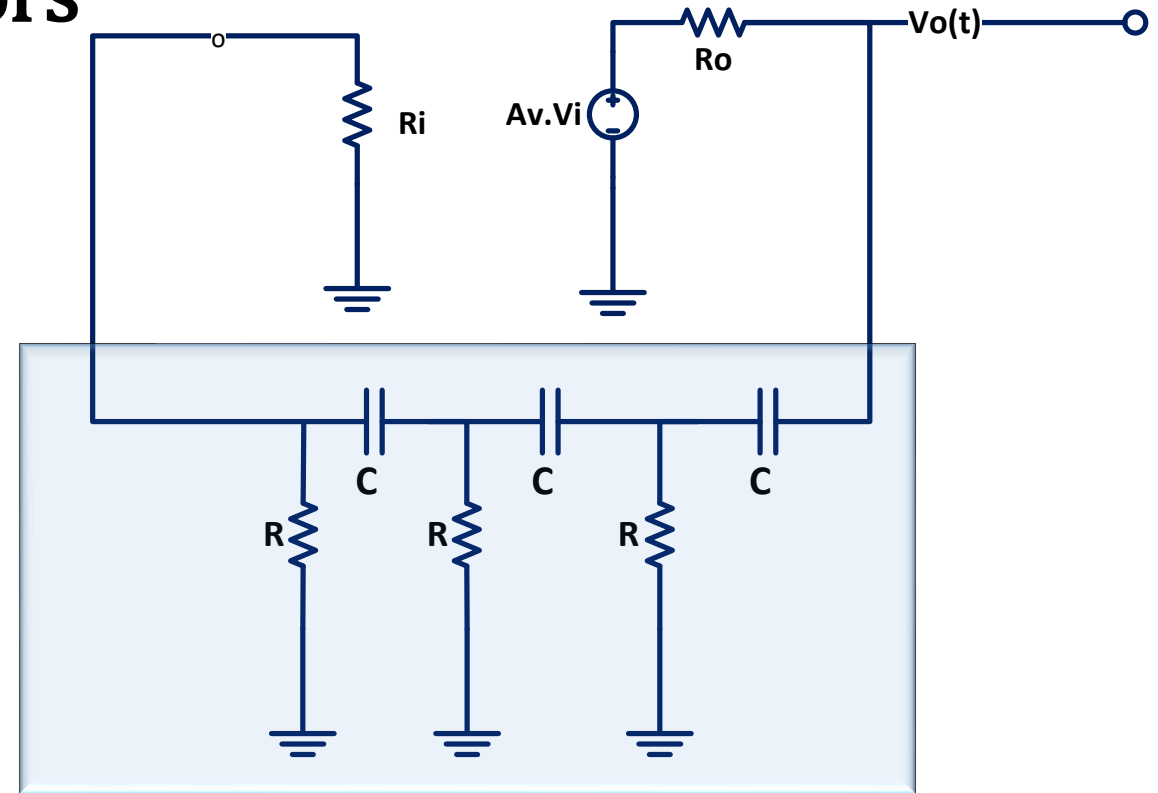
$$V_o = \frac{R^3 V_i}{R^3 - \frac{5R}{\omega^2 C^2} + j\left(\frac{1}{\omega^3 C^3} - \frac{6R^2}{\omega C}\right)}$$



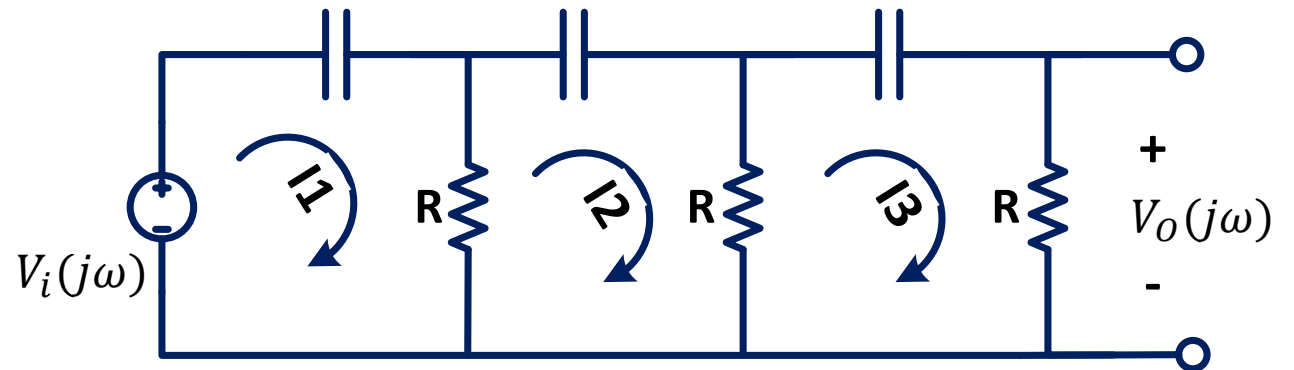$1/j\omega C$ $1/j\omega C$ $1/j\omega C$



Audio frequency Oscillators

1) Phase-shift Oscillator

$$\text{To find } \beta(j\omega) = \frac{V_O(j\omega)}{V_i(j\omega)}$$


$$\beta = \frac{V_O(j\omega)}{V_i(j\omega)}$$

$$\beta(j\omega) = \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2}\right) + j\left(\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR}\right)}$$

At ω_0 ; $\beta(j\omega)$ must be real and negative

$$\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR} = 0$$
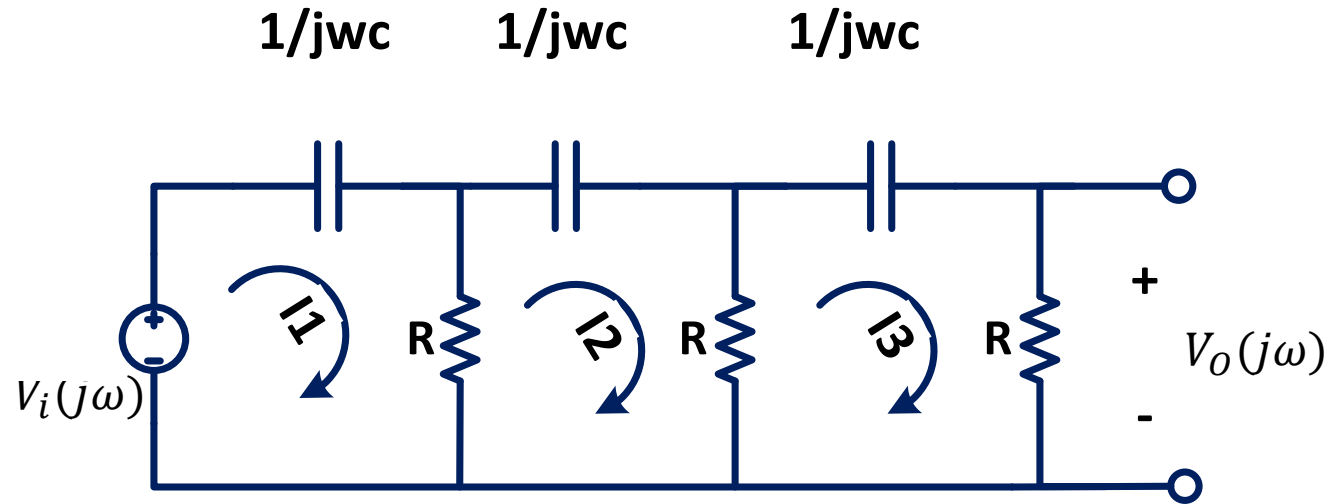
$$\therefore \omega_0 = \frac{1}{\sqrt{6} RC}$$



Audio frequency Oscillators

1) Phase-shift Oscillator


To find $\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$\beta(j\omega) = \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2}\right) + j\left(\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR}\right)}$$

At ω_0 $\beta(j\omega) = -\frac{1}{29} = \frac{1}{29} \angle 180$

$\therefore A_V \geq 29 \angle 180$

$A_V \beta \geq 1 \angle 0$

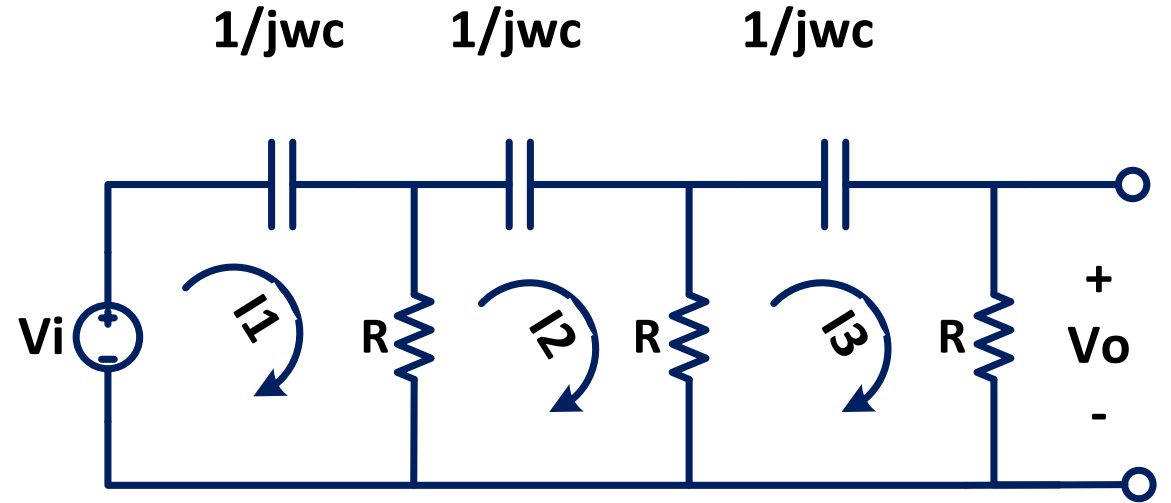


Audio frequency Oscillators

1) Phase-shift Oscillator

$$f_o = \frac{1}{2\pi\sqrt{6}RC} = 197\text{Hz}$$


$$A_V = - \left(\frac{R_2 + R_3}{R_1} \right) = \begin{cases} -33.9 \\ -27.6 \end{cases}$$

$$A_V \leq -29$$

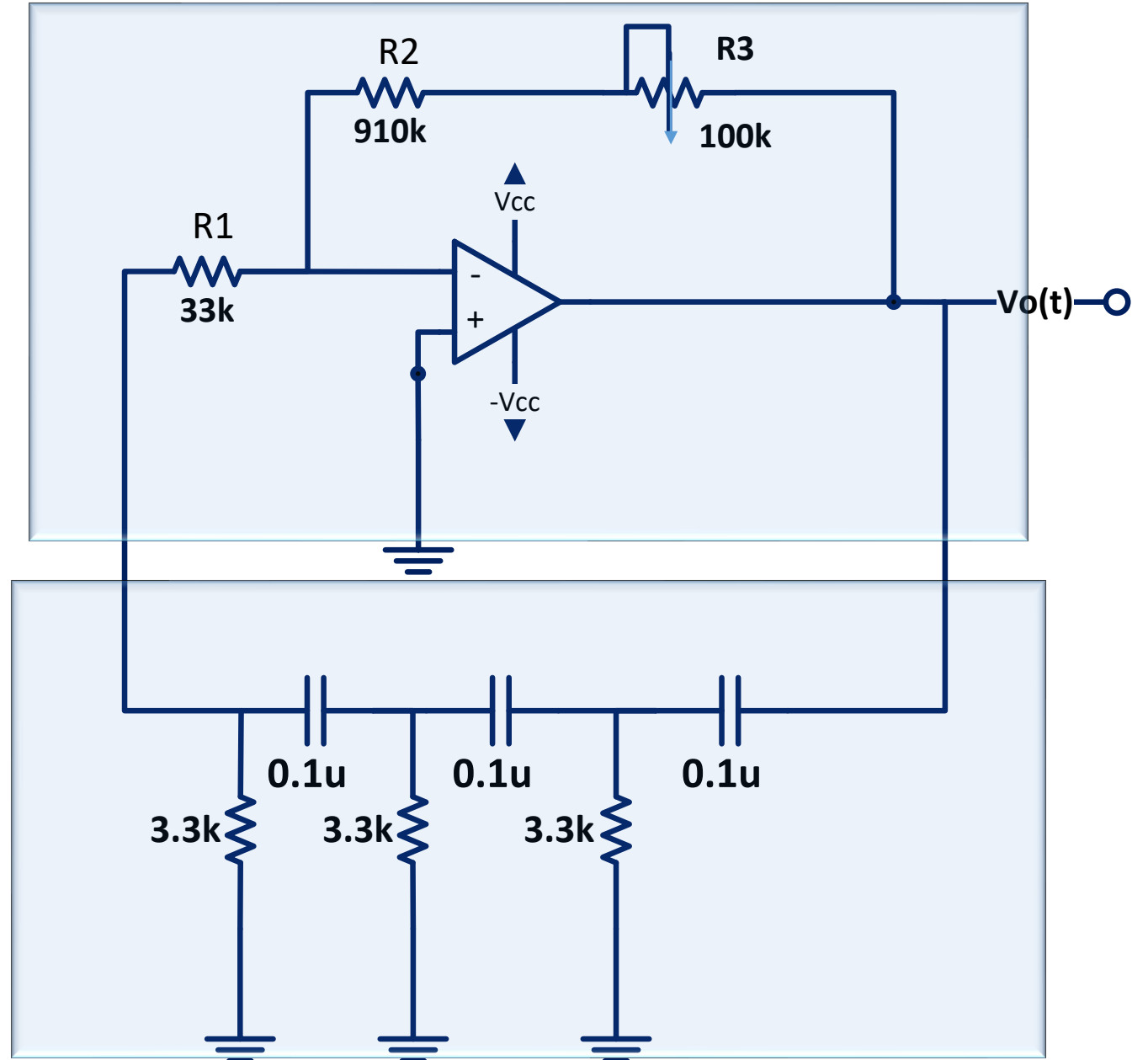

Audio frequency Oscillators



2- Wien Bridge Oscillator

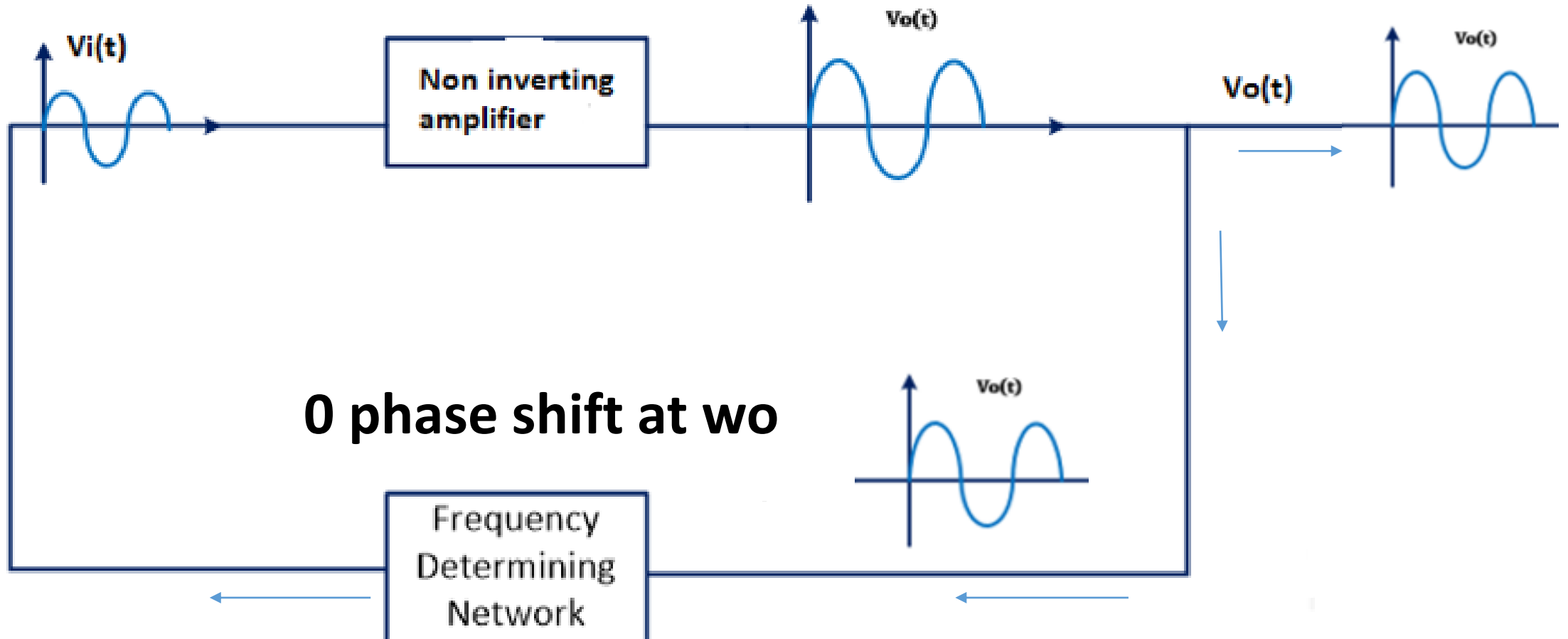

Audio frequency Oscillators

2- Wien Bridge Oscillator

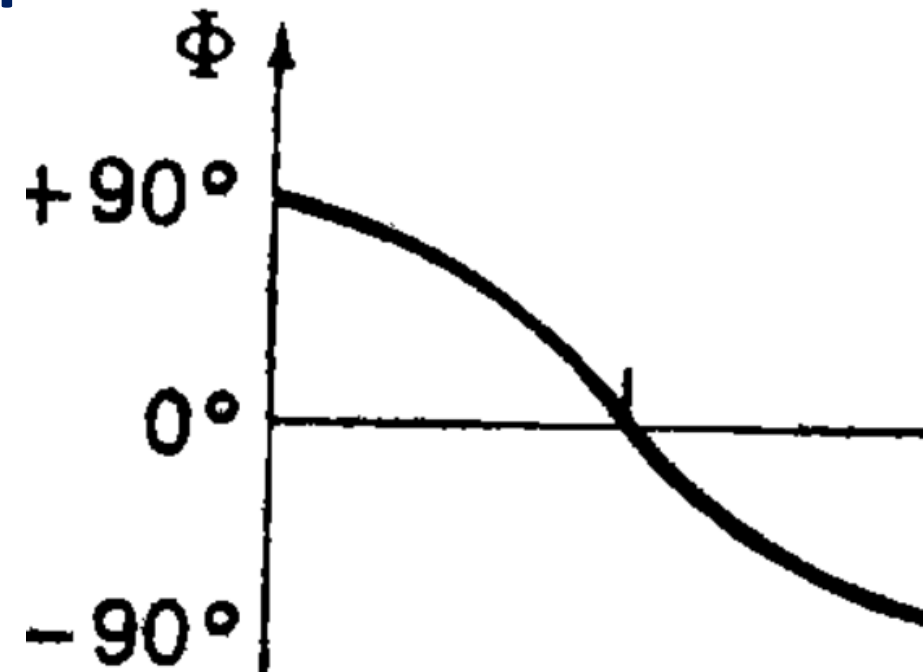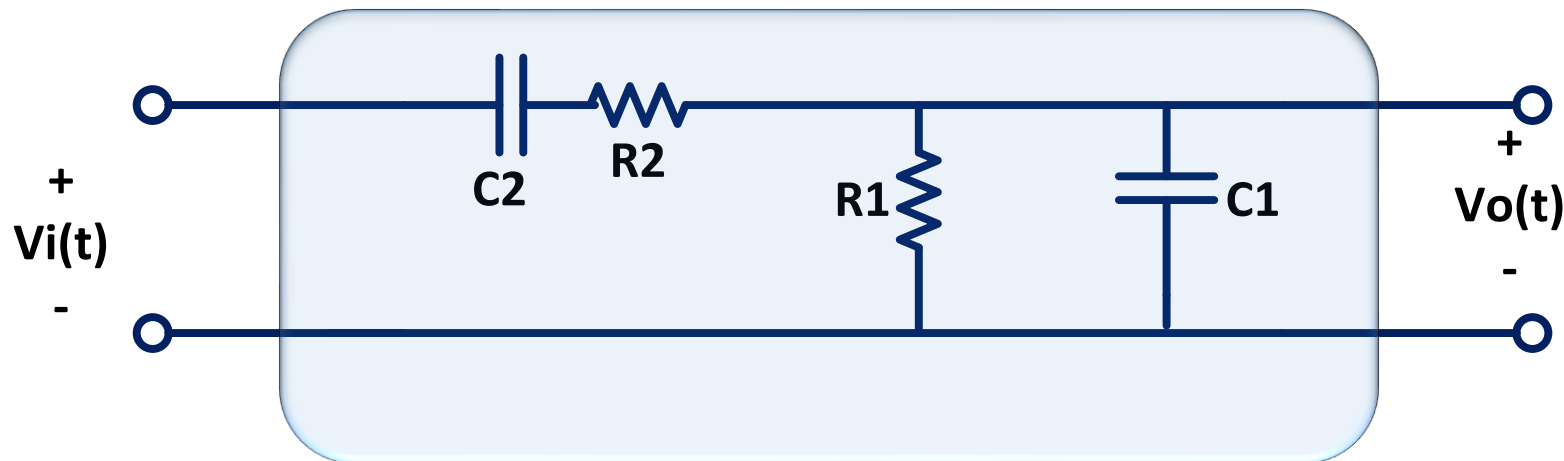- The Wien bridge oscillator employs a lead-lag network.
- At one particular frequency, the phase shift across the network is 0, therefore the feedback network is connected to the Op.Amp's noninverting input terminal.



Audio frequency Oscillators

2- Wien Bridge Oscillator

$$- Z_1 = R_1 \parallel \frac{1}{j\omega C_1} = \frac{R_1}{1+jR_1\omega C_1}$$


$$- Z_2 = R_2 + \frac{1}{j\omega C_2}$$

$$- \beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_1}{Z_1+Z_2}$$

$$- \beta(j\omega) = \frac{\omega R_1 C_2}{\omega(R_1 C_1 + R_2 C_2 + R_1 C_2) + j(\omega^2 R_1 R_2 C_1 C_2 - 1)}$$

At ω_o ; $\beta(j\omega)$ must be real and positive

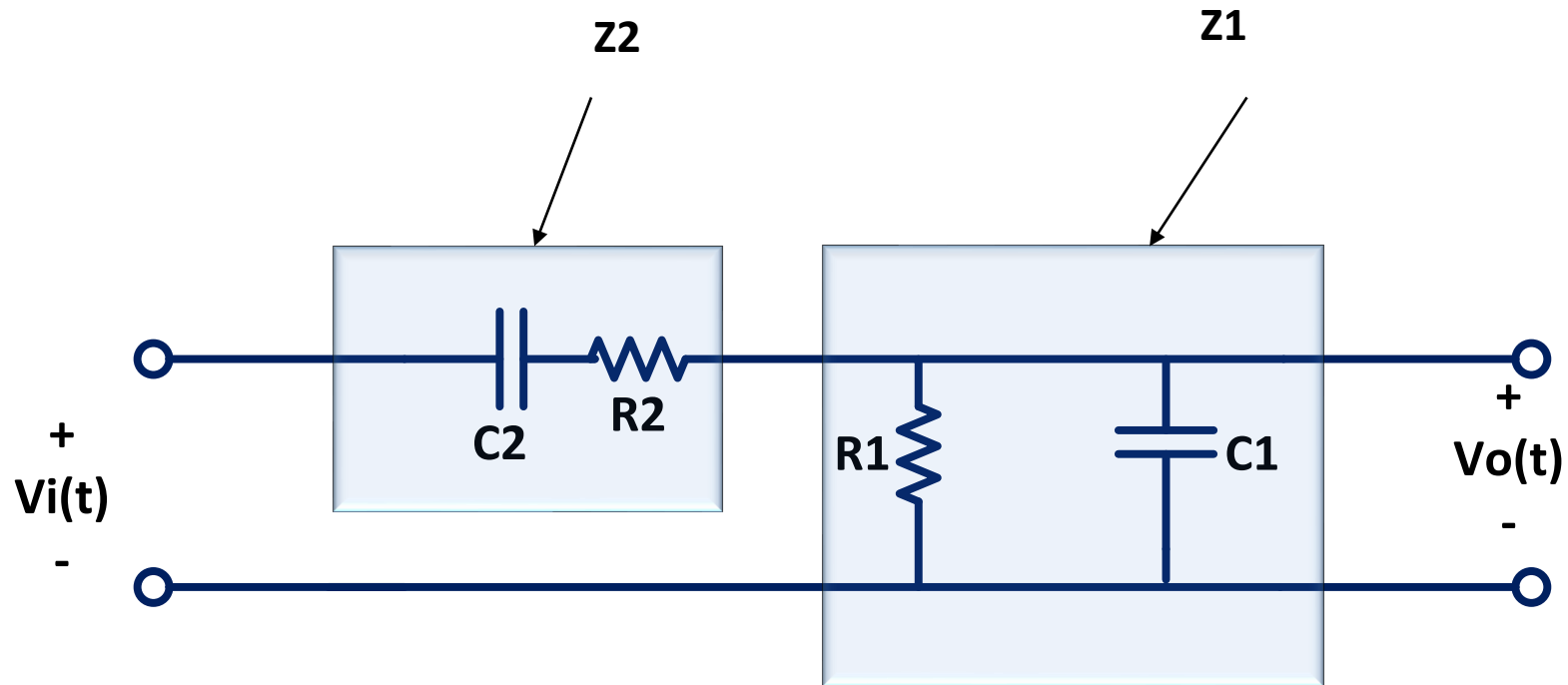
$$- \therefore \omega^2 R_1 R_2 C_1 C_2 - 1 = 0$$



Audio frequency Oscillators

2- Wien Bridge Oscillator

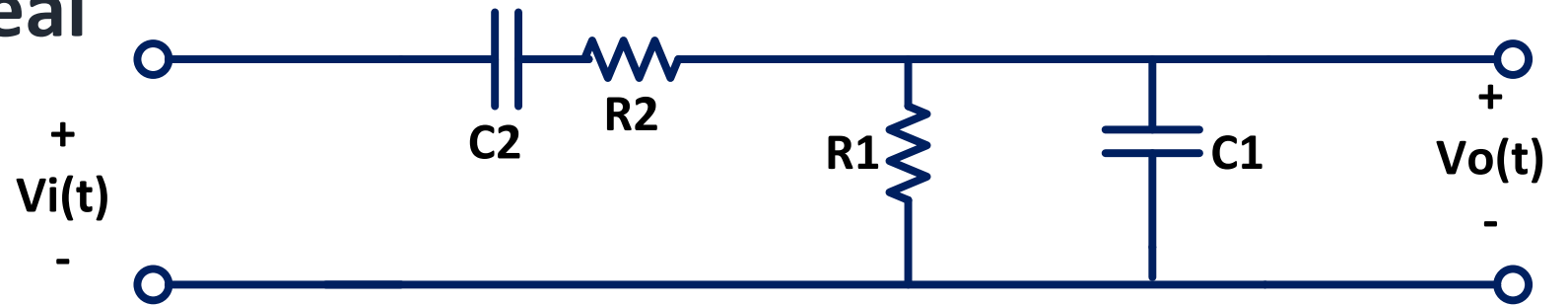At ω_o ; $\beta(j\omega)$ must be real and positive



$$\therefore \omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\text{At } \omega_o ; \beta(j\omega) = \frac{1}{1 + \frac{R_2}{R_1} + \frac{C_1}{C_2}}$$

- If $R_1 = R_2 = R$; and $C_1 = C_2 = C$



$$\omega_o = \frac{1}{RC}$$

$$\beta = \frac{1}{3} = \frac{1}{3} \angle 0$$

$$A_v \beta \geq 1 \angle 0$$

$$\therefore A_v \geq 3 \angle 0$$

Audio frequency Oscillators

2- Wien Bridge Oscillator

Frequency Determining Network


Since $C1 = C2$ and $R1 = R2$

$$- f_o = \frac{1}{2\pi RC} = 1.06\text{KHz}$$

$$\beta = \frac{1}{3}$$

$$\therefore A_v \geq 3$$
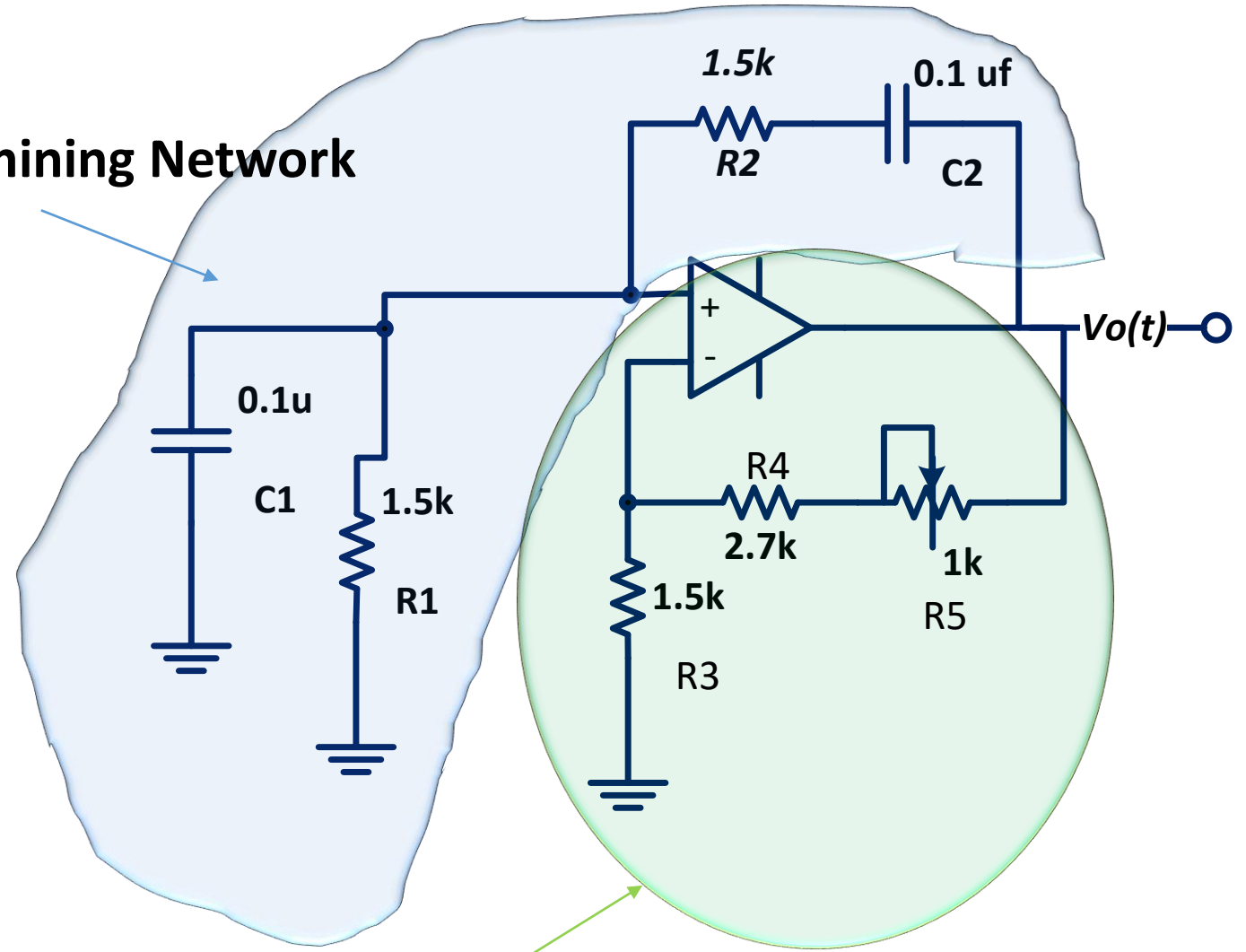
$$A_v = 1 + \frac{R_4 + R_5}{R_3} = \begin{cases} 2.8 \\ 3.47 \end{cases}$$



Non Inverting Amplifier

Audio frequency Oscillators

Adaptive Negative Feedback


At the beginning

D1,D2 are off to build up the oscillation

$$A_v = 1 + \frac{R_4}{R_3} = 3.2 > 3$$


Later on D1,D2 are on

$$A_v = 1 + \frac{R_4 // R_5}{R_3} = 3$$

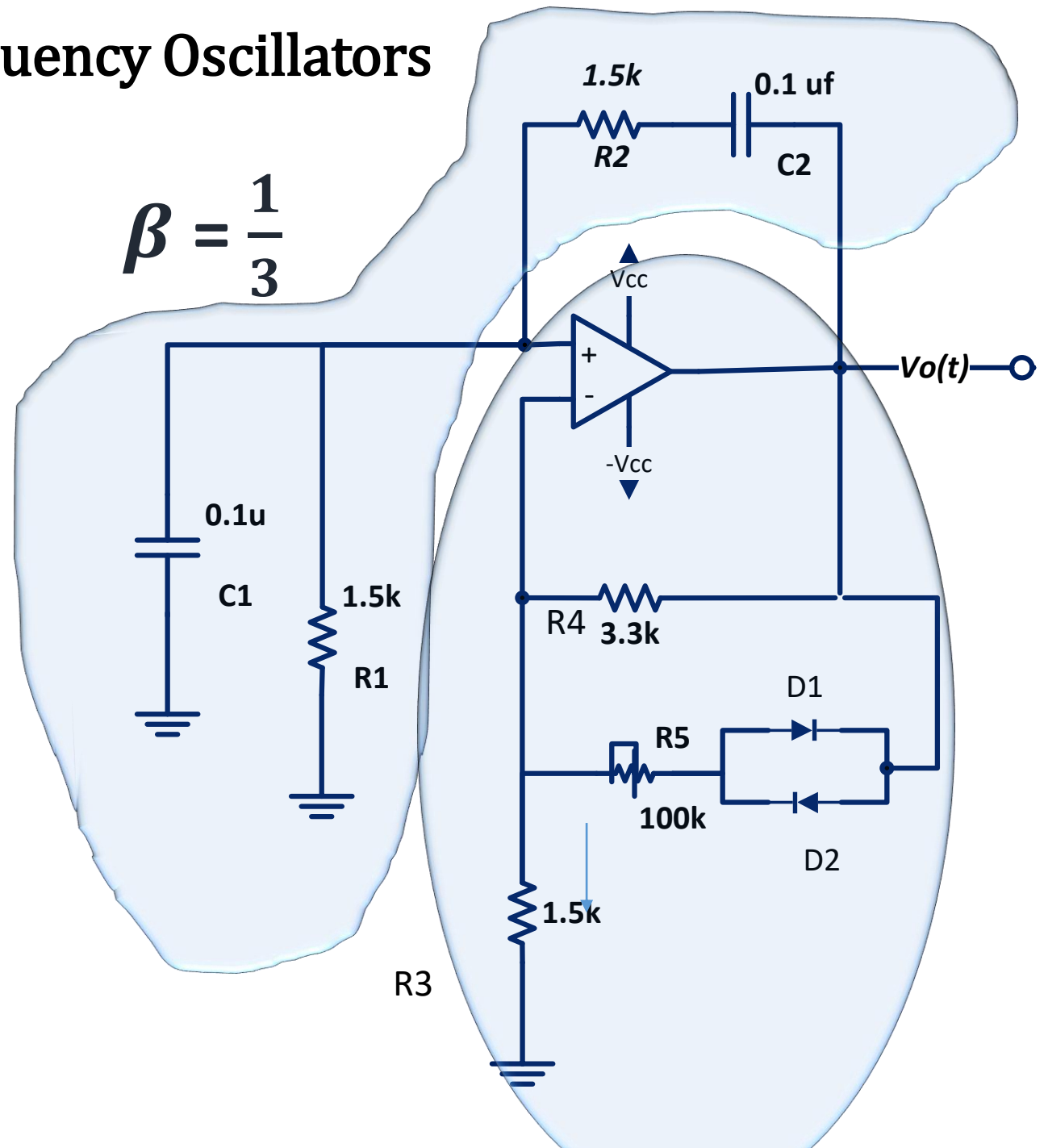


High Frequency Harmonic Oscillators

General LC Oscillator

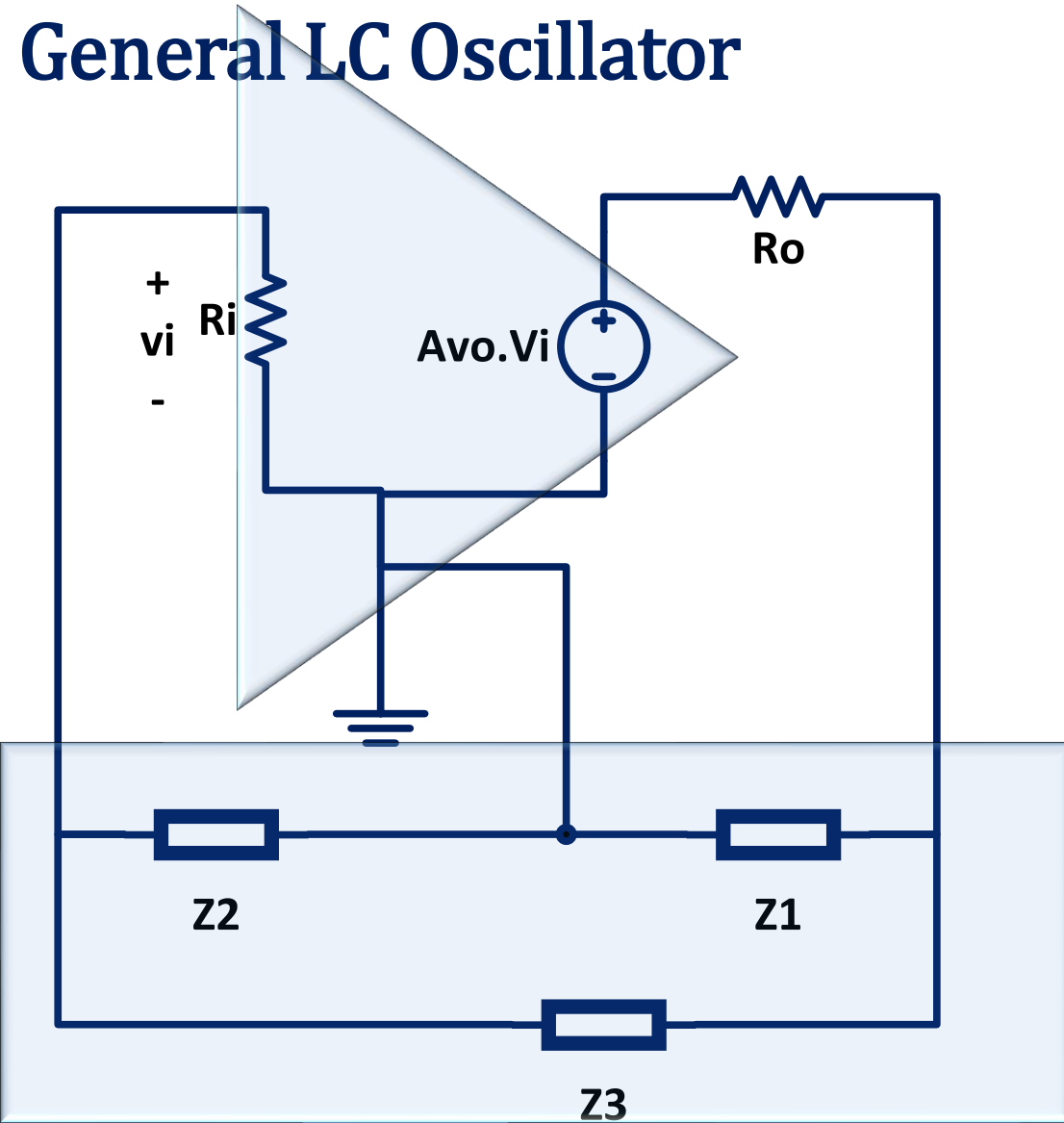

The feedback network

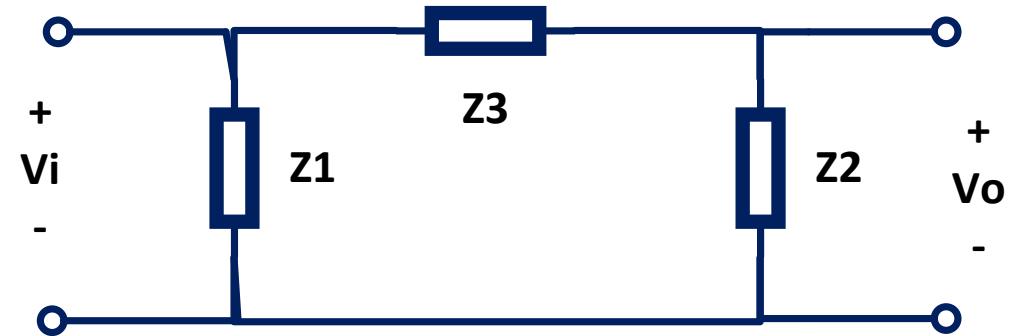

$$R_i \gg Z_2$$

$$\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_2}{Z_2 + Z_3}$$


Z1 , Z2 , and Z3 are pure reactive impedances

High Frequency Harmonic Oscillators

ZL

General LC Oscillator

To determine A_v

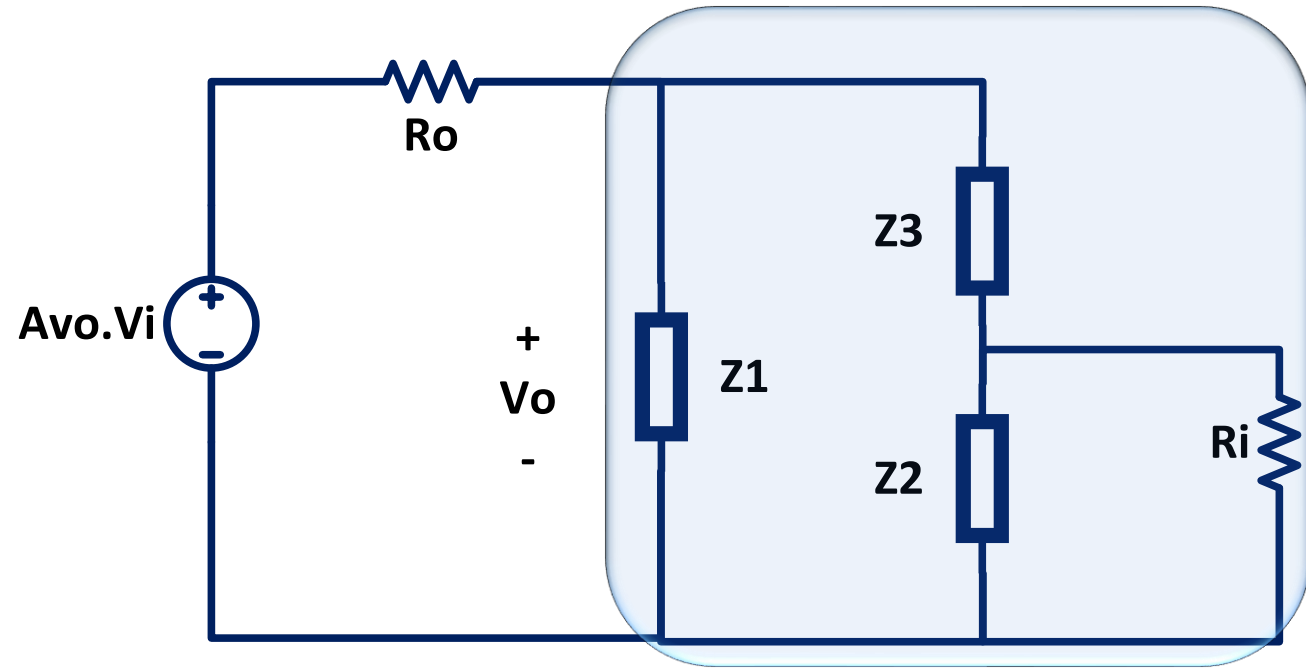

$$A_v(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_l}{Z_l + R_o} A_{vo} V_i$$

$$Z_l = Z_1 \parallel (Z_2 + Z_3)$$

$$\therefore A_v(j\omega) = \frac{Z_1 (Z_2 + Z_3) A_{vo}}{Z_1 (Z_2 + Z_3) + R_o (Z_1 + Z_2 + Z_3)}$$

$$A_v \beta = \frac{Z_1 Z_2 A_{vo}}{Z_1 (Z_2 + Z_3) + R_o (Z_1 + Z_2 + Z_3)}$$

Z_1, Z_2 and Z_3 pure reactive impedances

\therefore At ω_o

$R_i \gg Z_2$

$$1. Z_1 + Z_2 + Z_3 = 0$$

$$2. A_v \beta = -\frac{Z_2}{Z_1} A_{vo}$$

$$A_v \beta \geq 1 \angle 0$$

$$\therefore A_{vo} \leq -\frac{Z_1}{Z_2}$$

High Frequency Harmonic Oscillators

Example of LC Oscillators

Oscillator type	Z1	Z2	Z3	Amplifier
Hartley	L	L	C	Inverting
	L	C	L	Follower
Colpitts	C	C	L	Inverting
	L	C	C	Non-Inverting
Clapp	C	C	LC	Inverting
Pierce crystal	C	C	XTAL	Inverting

High Frequency Harmonic Oscillators

Colpitts Oscillator

At ω_o :

$$Z_1 + Z_2 + Z_3 = 0$$

$$-j \frac{1}{\omega_o C_1} - j \frac{1}{\omega_o C_2} + j \omega_o L = 0$$

$$\therefore \omega_o = \frac{1}{\sqrt{LC_T}} \quad , \quad C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$f_o = \frac{\omega_o}{2\pi} = 1.02 \text{ MHz}$$


$$A_{vo} \leq - \frac{Z_1}{Z_2} = - \frac{C_2}{C_1}$$

$$A_{vo} \leq -2.06$$

$$C_1 = 330 \text{ pF}$$

$$C_2 = 680 \text{ pF}$$



$$L = 110 \mu\text{H}$$

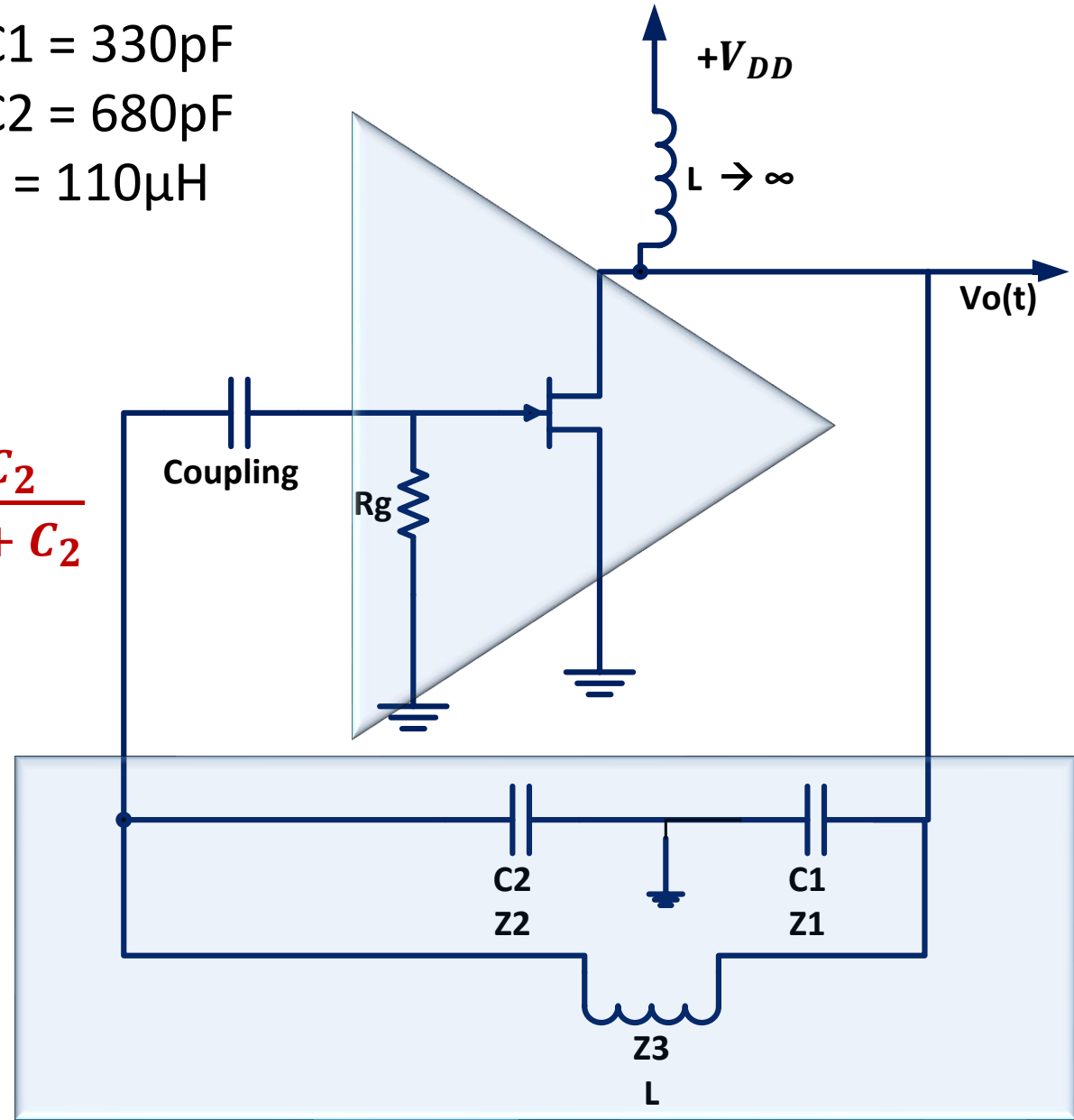

At high frequency

$$C1' = C1 + C_{com}$$

$$C2' = C2 + C_{gs} + C_{im}$$

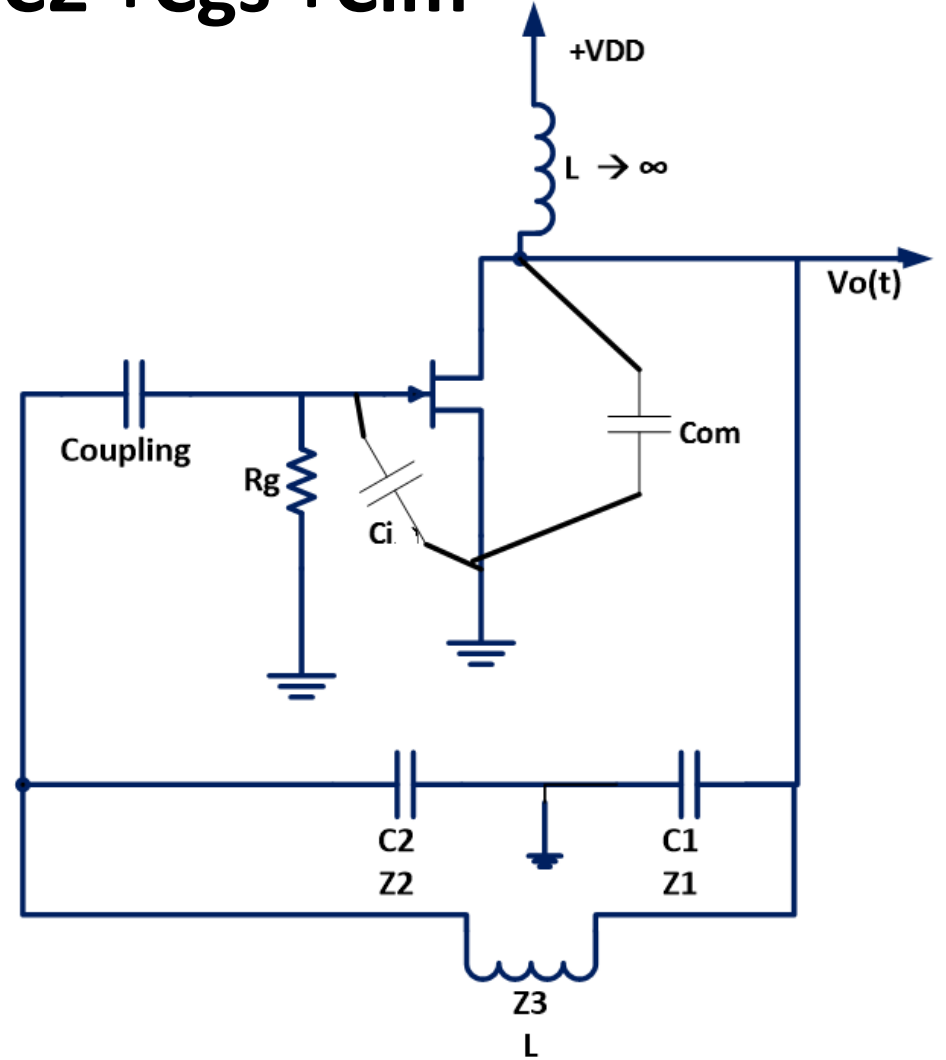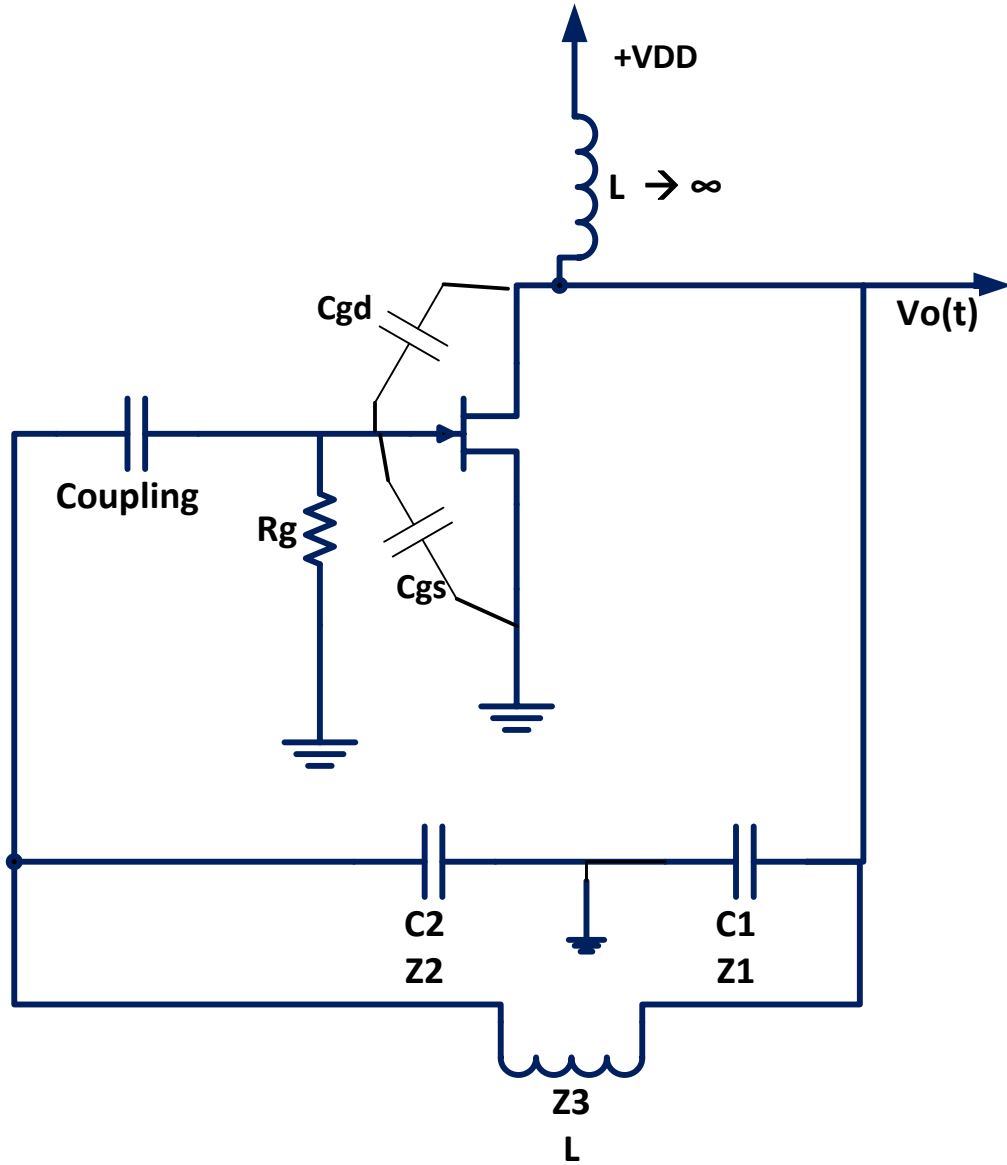

High Frequency Harmonic Oscillators

Clapp Oscillator

At ω_0

$$Z_1 + Z_2 + Z_3 = 0$$

$$-j \frac{1}{\omega_0 C_1} - j \frac{1}{\omega_0 C_2} - j \frac{1}{\omega_0 C_3} + j\omega_0 L = 0$$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC_T}}$$


$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_T = 212.7 \text{PF}$$

$$f_o = \frac{\omega_0}{2\pi} = 1.04 \text{MHz}$$




$$A_{vo} \leq -\frac{Z_1}{Z_2} = -\frac{C_2}{C_1}$$

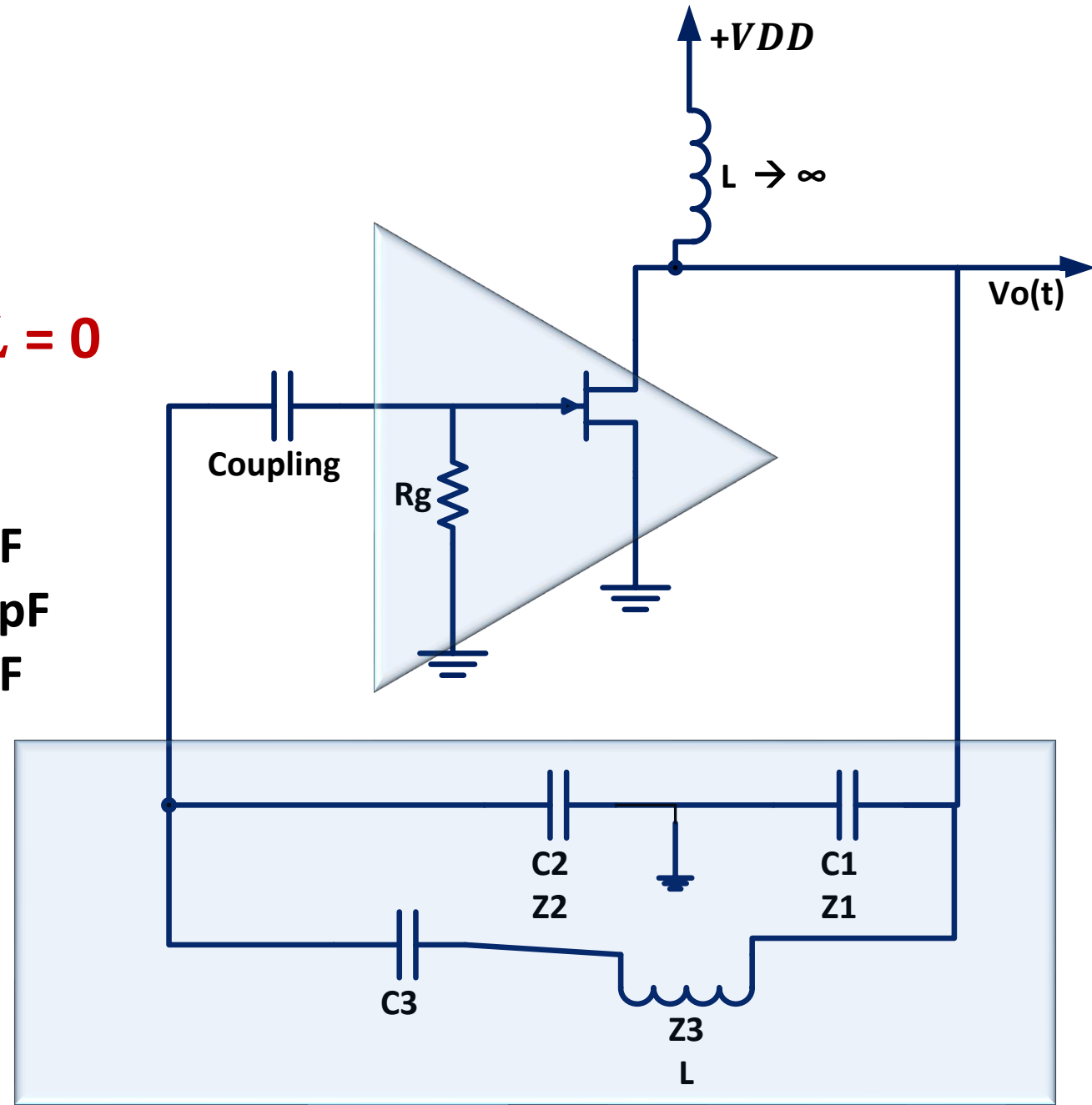$C_1 = 680 \text{pF}$
 $C_2 = 1500 \text{pF}$
 $C_3 = 390 \text{pF}$
 $L = 110 \mu\text{H}$



High Frequency Harmonic Oscillators

The Crystal

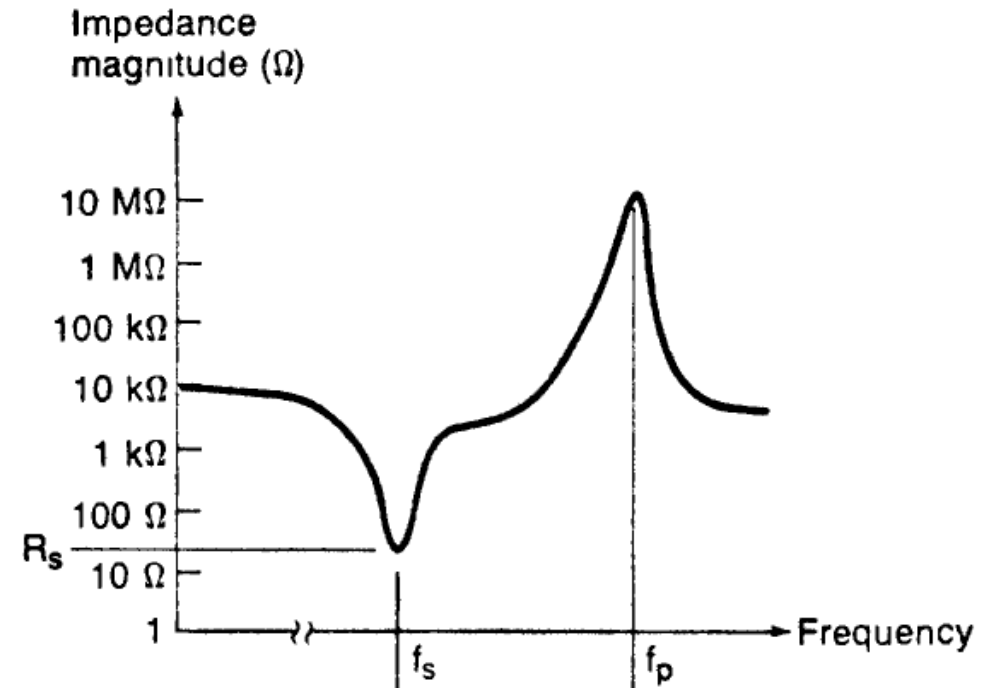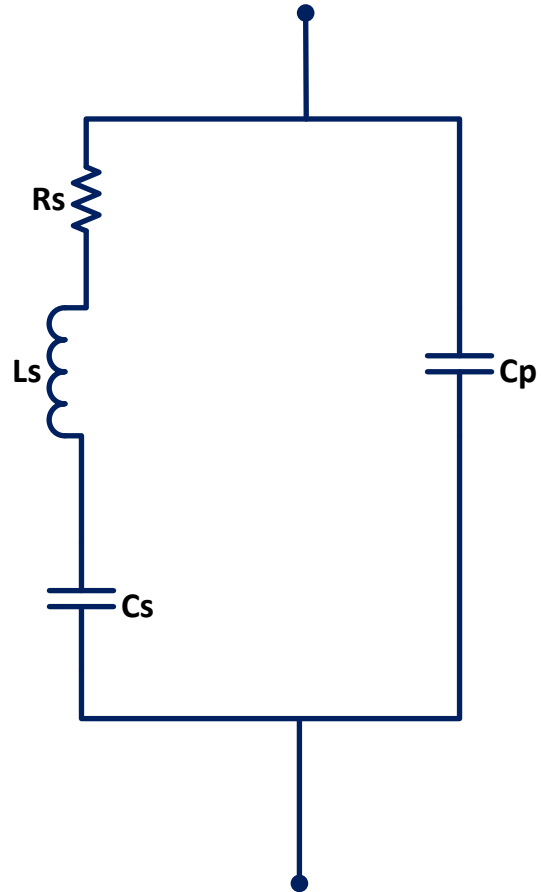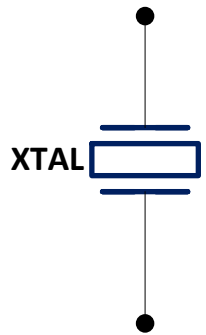

Capacitive

Inductive

Oscillators

High Frequency Harmonic Oscillators

The Crystal

R_s is very small

$$Z(j\omega) = \frac{(j\omega L_s + \frac{1}{j\omega C_3}) \frac{1}{j\omega C_p}}{j\omega_0 L_s + \frac{1}{j\omega C_3} + \frac{1}{j\omega C_p}}$$

$$Z(j\omega) = \frac{-j}{\omega C_p} \frac{\omega^2 - \frac{1}{L_s C_s}}{\omega^2 - \frac{C_s + C_p}{L_s C_s C_p}}$$

$$\omega^2 - \frac{1}{L_s C_s} = 0$$


$$\therefore \omega_s = \frac{1}{\sqrt{L_s C_s}}$$

Series resonance

$$\omega^2 - \frac{C_s + C_p}{L_s C_s C_p} = 0$$

$$\therefore \omega_p = \frac{1}{\sqrt{L_s \left(\frac{C_s C_p}{C_s + C_p} \right)}}$$

Parallel resonance

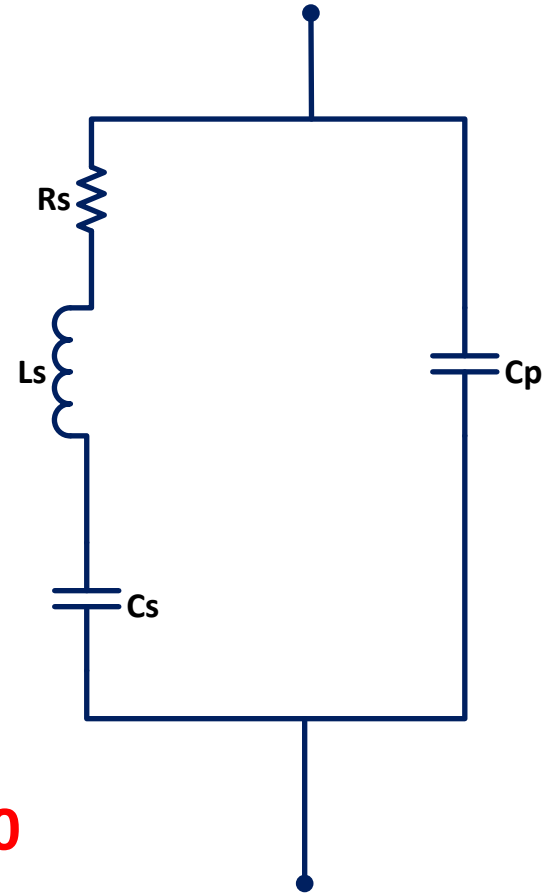

Oscillators

High Frequency Harmonic Oscillators


The Crystal

$$C_s = 0.0060\text{PF}$$

$$L_s = 0.165609\text{H}$$

$$R_s = 10\Omega$$

$$C_p = 13.0\text{PF}$$

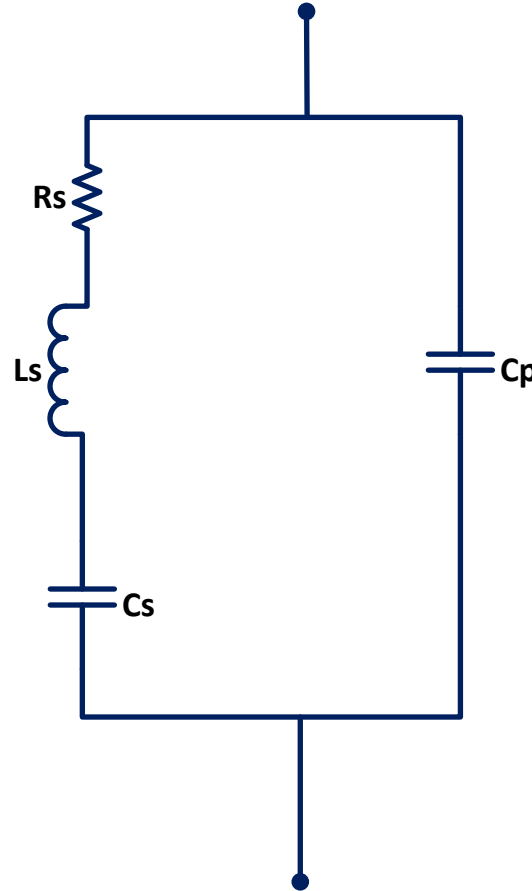

$$f_p - f_s = 1.179\text{KHz}$$

$$f_s = \frac{1}{2\pi \sqrt{L_s C_s}}$$

$$f_s = 5.048967\text{MHz}$$

$$\omega_p = \frac{1}{\sqrt{L_s \left(\frac{C_s C_p}{C_s + C_p} \right)}}$$


$$f_p = 5.050145\text{MHz}$$

Oscillators


High Frequency Harmonic Oscillators

Pierce crystal oscillator.

$$W_p > W_o > W_s$$

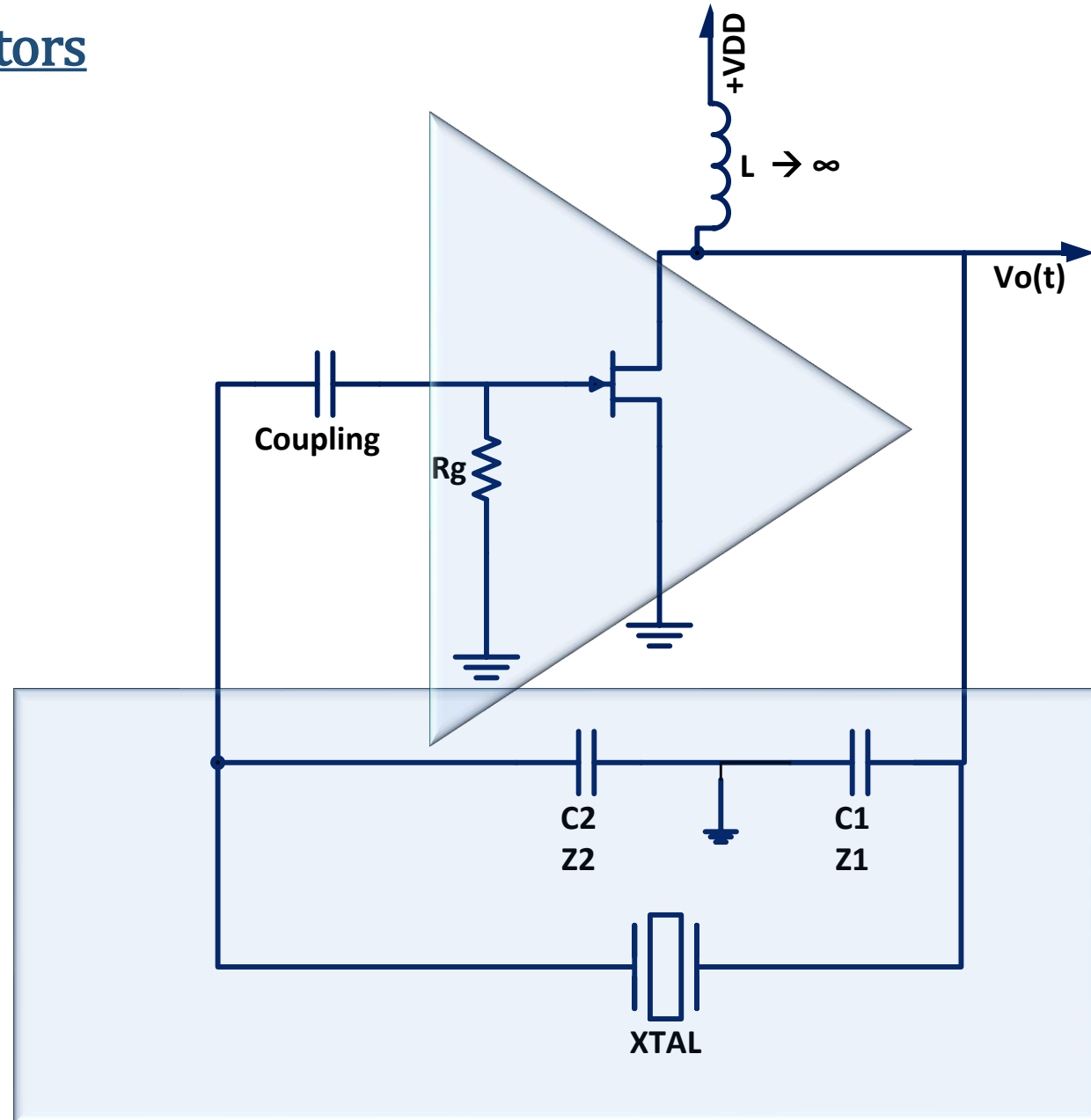

Oscillators

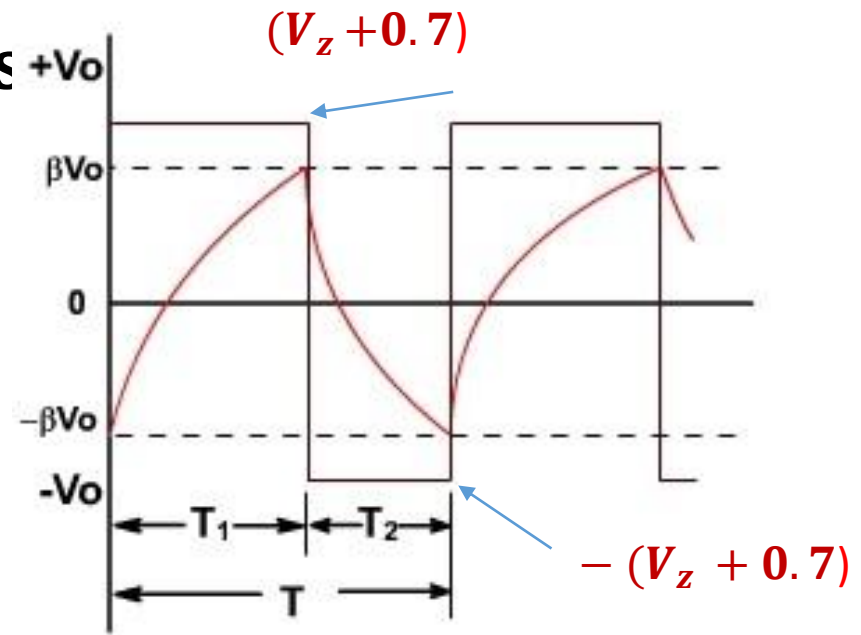


-The Op. Amp relaxation oscillator shown is a square _wave generator .

-The circuit's frequency of oscillation is dependent on the charge and discharge of a capacitor C_1 through a resistor R_1 .

- The "heart" of the oscillator is an inverting Op. Amp comparator . the comparator uses positive feedback .

An OP Relaxation Oscillator


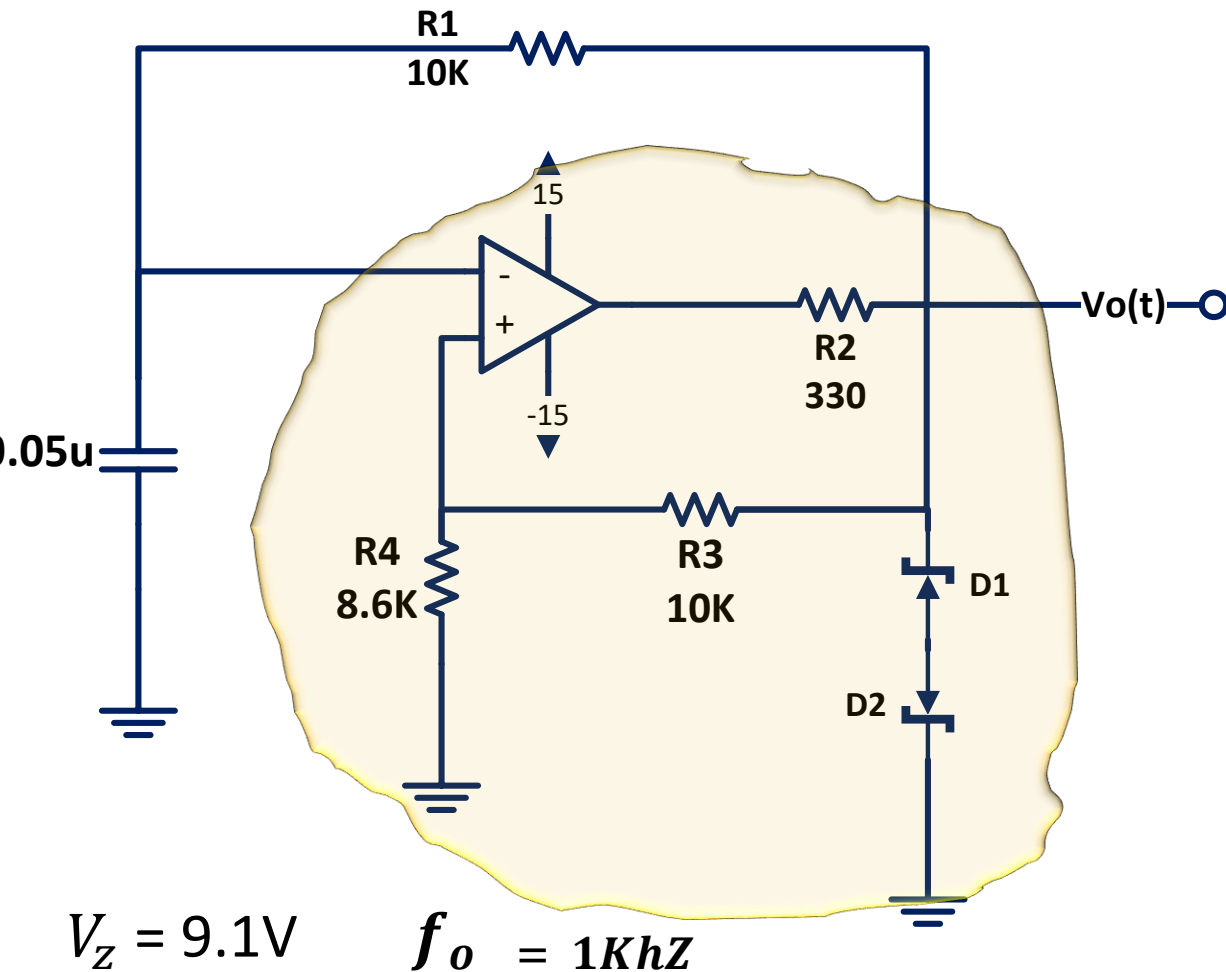


An OP Relaxation Oscillator

Oscillators

- The “heart” of the oscillator is an inverting Op. Amp comparator . the comparator uses positive feedback .



Inverting Schmitt trigger

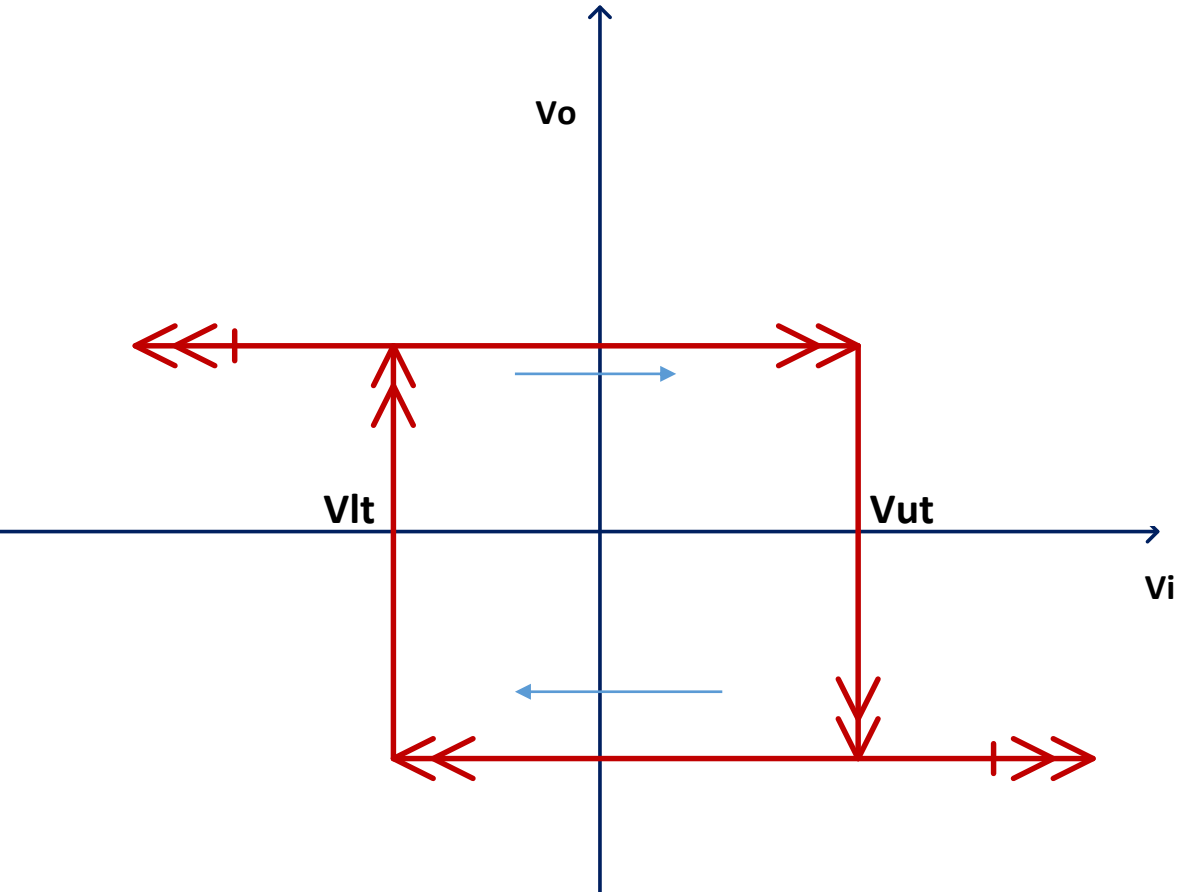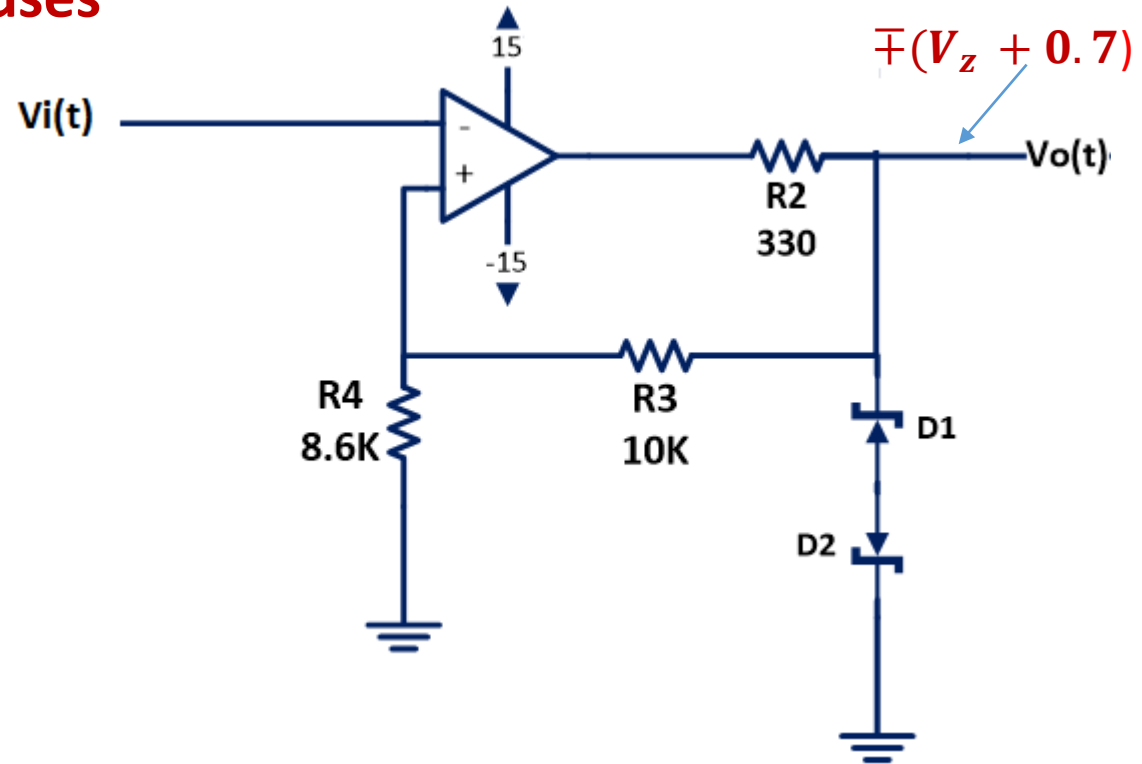

- $V_{UT} = \frac{R_4}{R_4 + R_3} (V_Z + 0.7) = \beta (V_Z + 0.7)$
- $V_{LT} = -\frac{R_4}{R_4 + R_3} (V_Z + 0.7) = -\beta (V_Z + 0.7)$

Oscillators

An OP Relaxation Oscillator


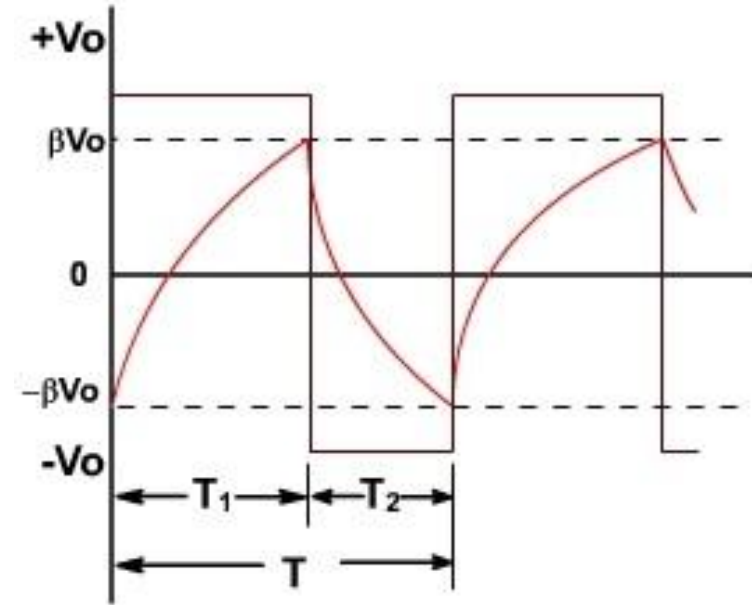
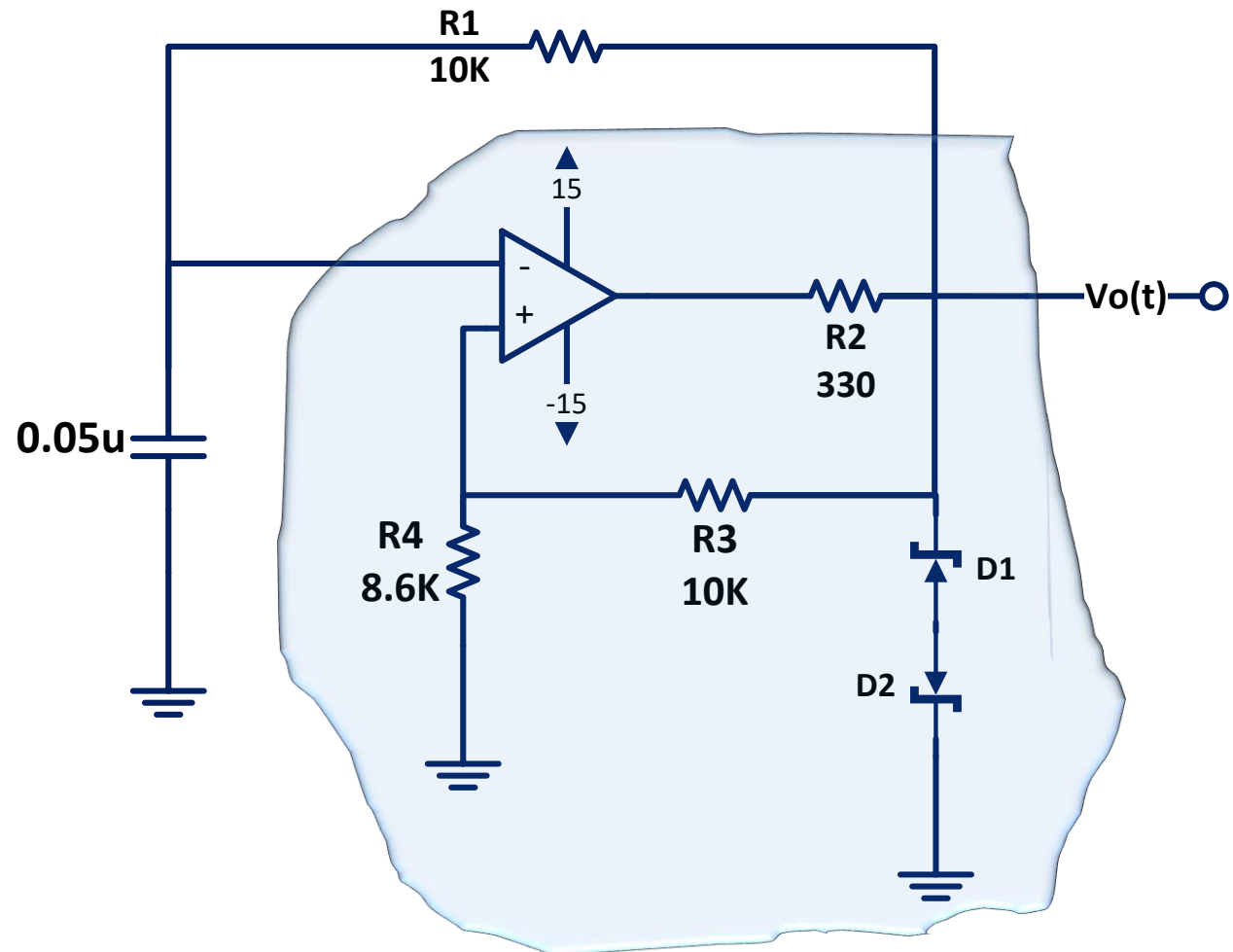


- $V_{out} = \pm(V_Z + 0.7)$
- $V_{UT} = \frac{R_4}{R_4 + R_3} (V_Z + 0.7) = \beta (V_Z + 0.7)$
- $V_{LT} = -\frac{R_4}{R_4 + R_3} (V_Z + 0.7) = -\beta (V_Z + 0.7)$



Oscillators

An OP Relaxation Oscillator

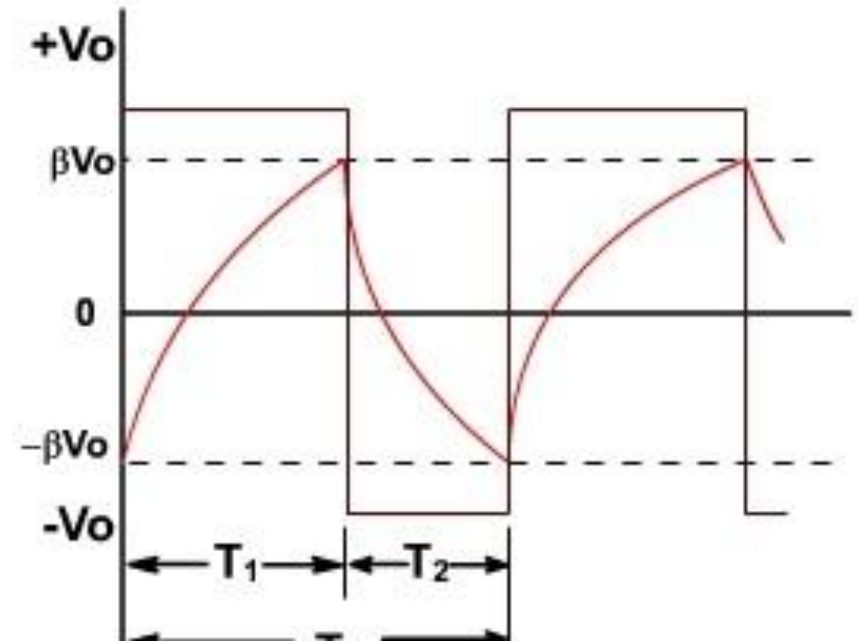
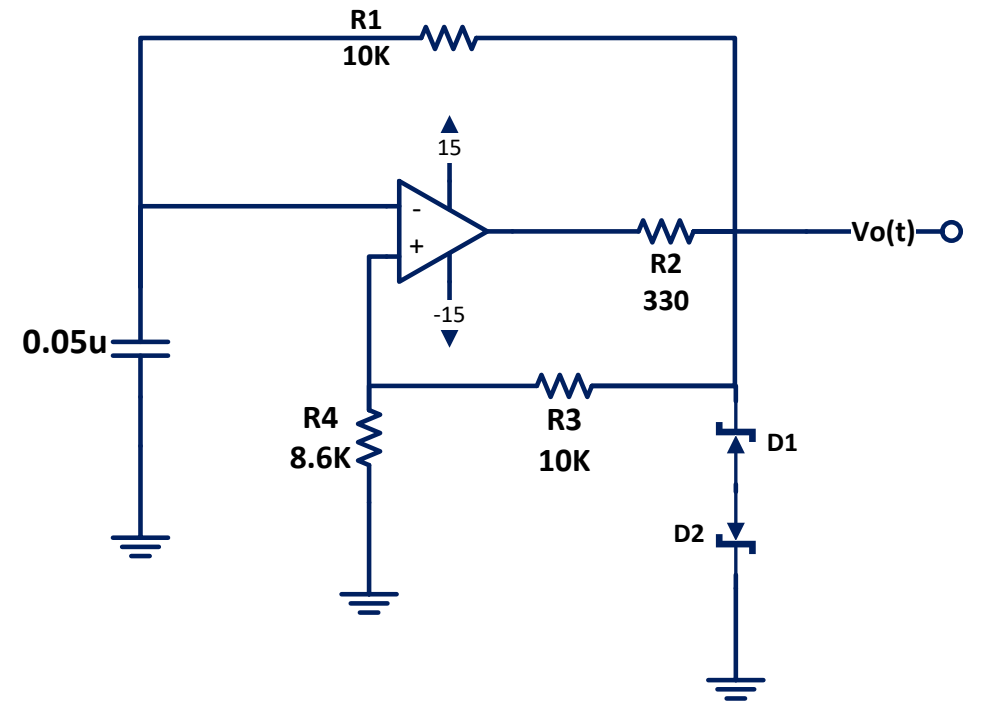
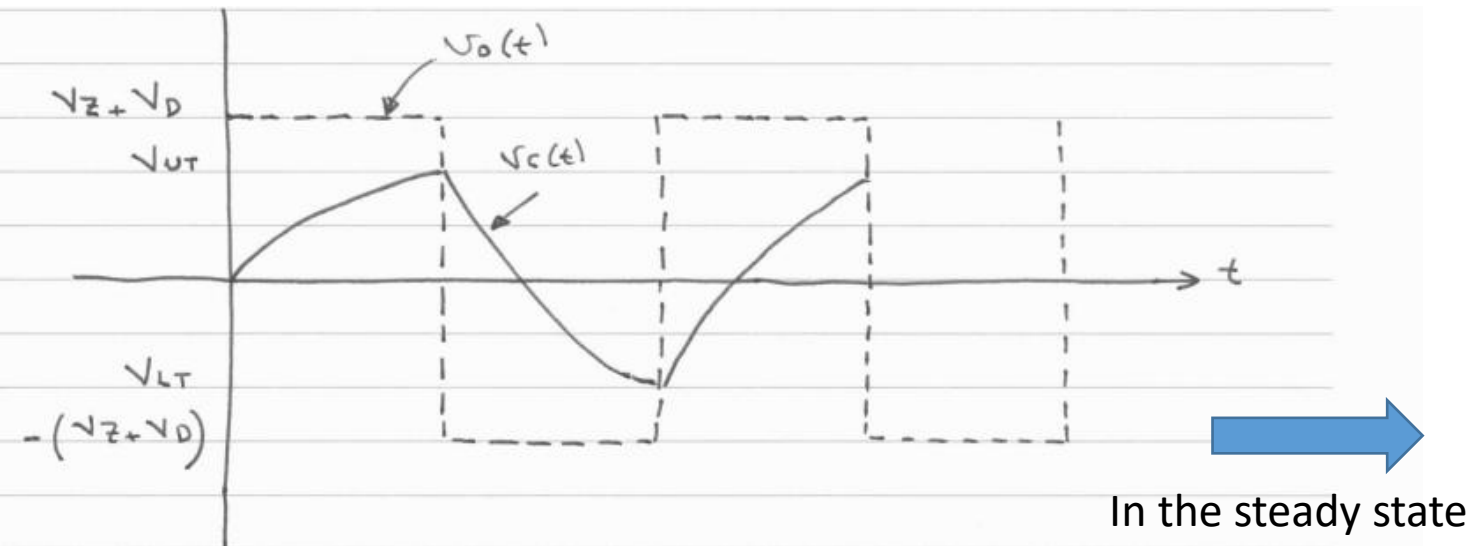
- $V_{out} = \pm(V_Z + 0.7)$
- $V_{UT} = \frac{R_4}{R_4 + R_3} (V_Z + 0.7) = \beta (V_Z + 0.7)$
- $V_{LT} = -\frac{R_4}{R_4 + R_3} (V_Z + 0.7) = -\beta (V_Z + 0.7)$



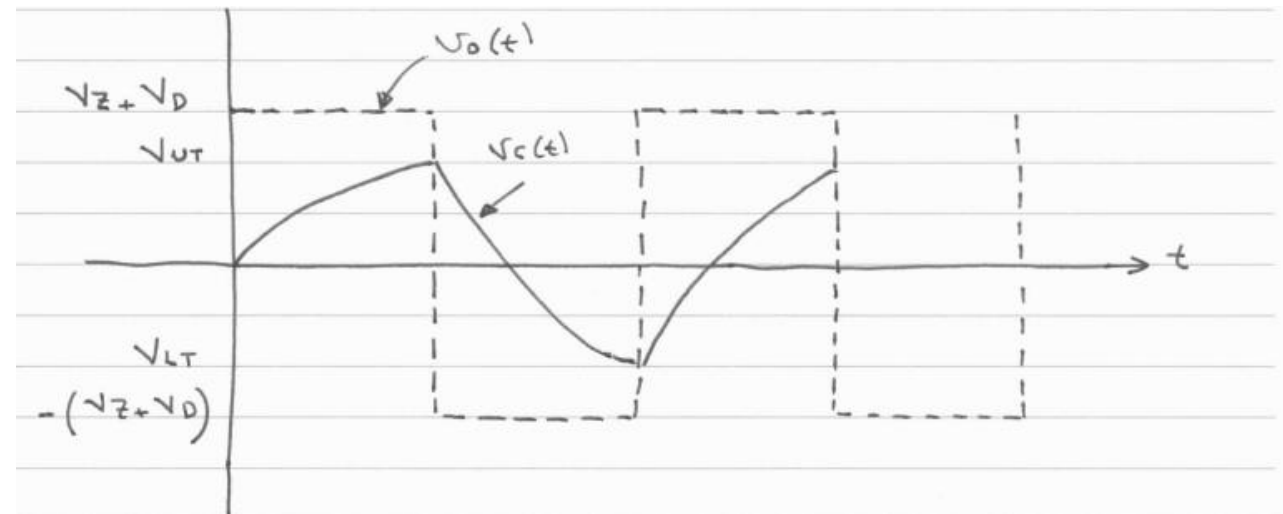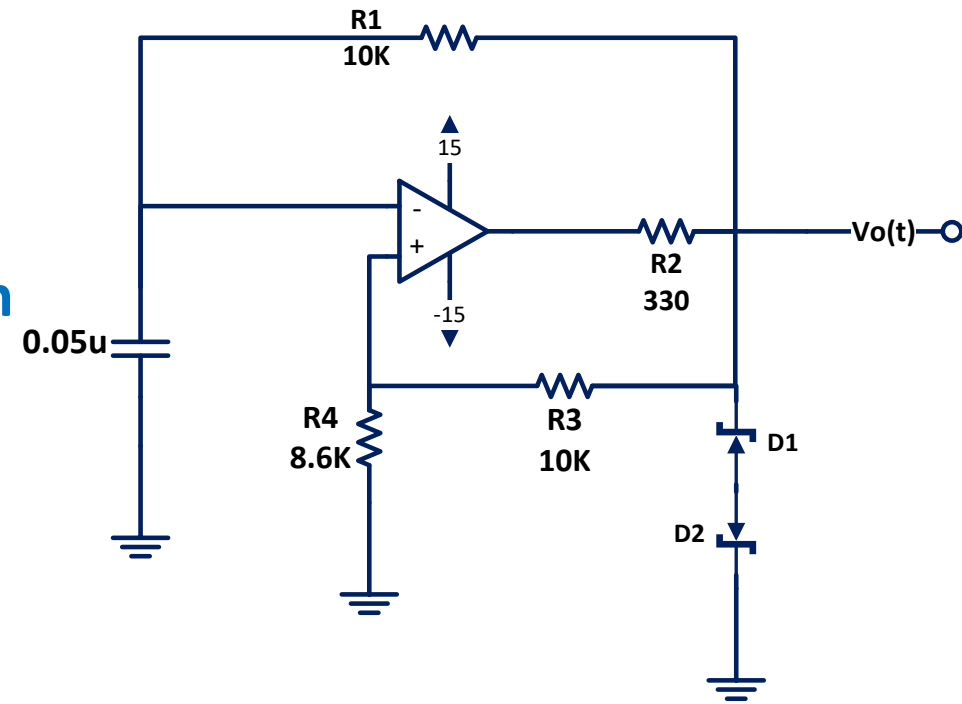- When the output of the comparator is positive, capacitor C_1 will charge through resistor R_1 .
- The capacitor will attempt to charge to $V_{out} = V_z + 0.7$.
- When the voltage across the capacitor reaches the upper threshold voltage V_{UT} , the comparators output will immediately switch to $V_{out} = -(V_z + 0.7)$.



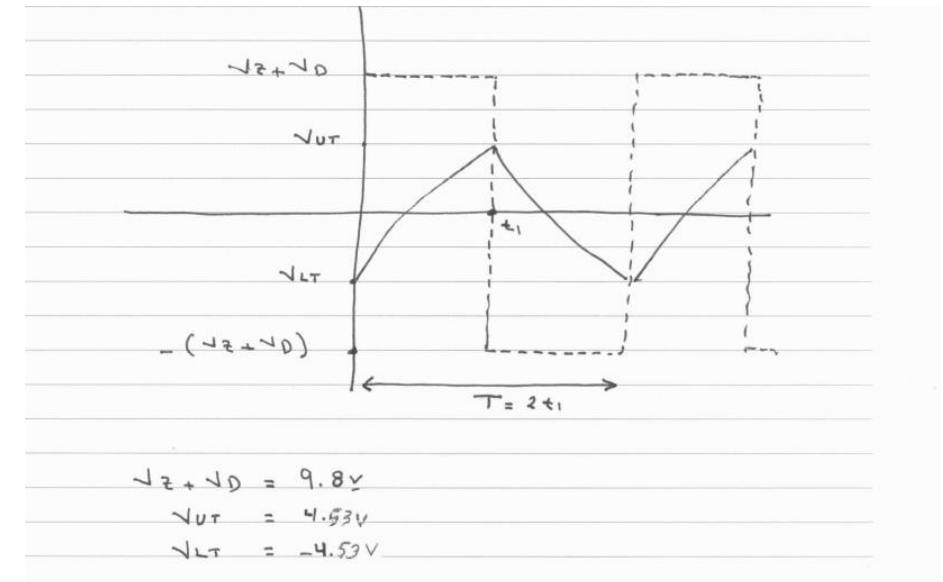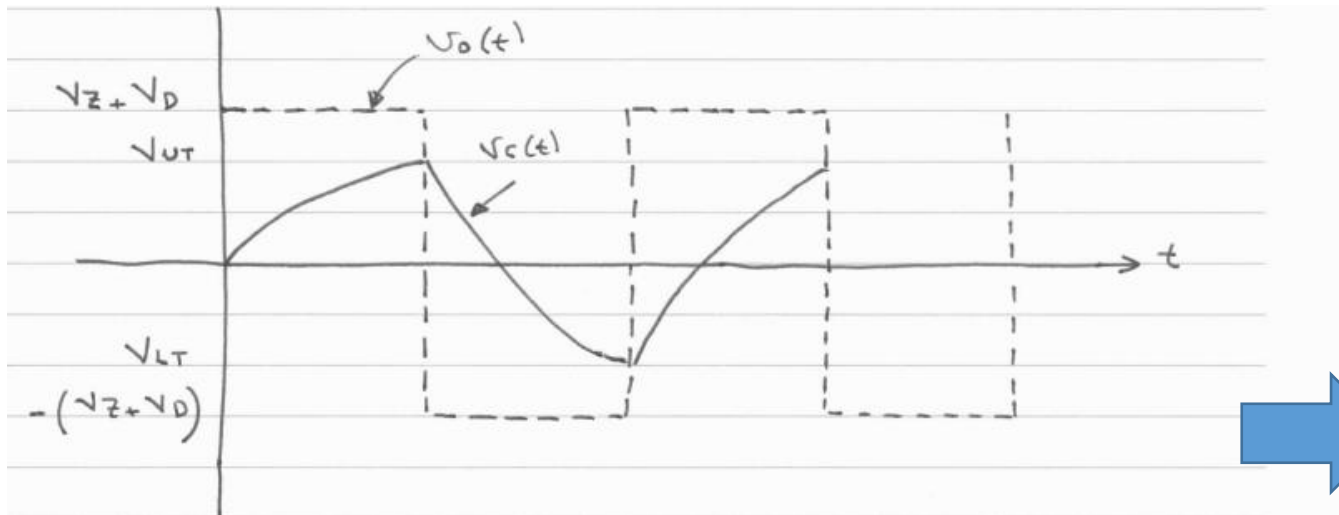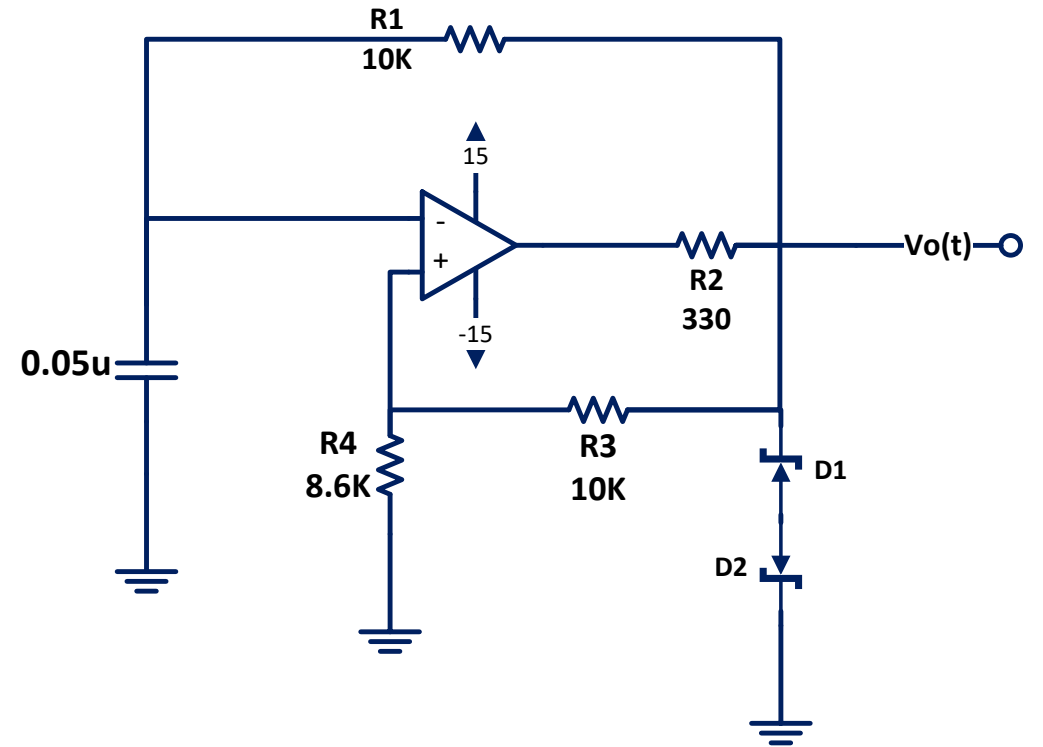- The capacitor will then start to discharge from the positive upper threshold voltage toward the negative output voltage .
- When the voltage across the capacitor reaches the lower threshold voltage V_{LT} , the comparators output will immediately switch to $V_{out} = + (V_Z + 0.7)$.



Oscillators

To determine the frequency of oscillation

- $V_c(t) = V_I + (V_f - V_I)(1 - e^{-\frac{t}{\tau}})$

- At t_1 : $V_c(t_1) = \beta V_{out}$

$$\frac{R_4}{R_4 + R_3} = \beta$$

$$V_{out} = V_z + V_D$$



- $\beta V_{out} = -\beta V_{out} + (V_{out} - (-\beta V_{out})) (1 - e^{-\frac{t_1}{\tau}})$

- dividing both side by V_{out}

- $\beta = -\beta + (1 + \beta) (1 - e^{-\frac{t_1}{\tau}})$

- $2\beta = (1 + \beta) (1 - e^{-\frac{t_1}{\tau}})$

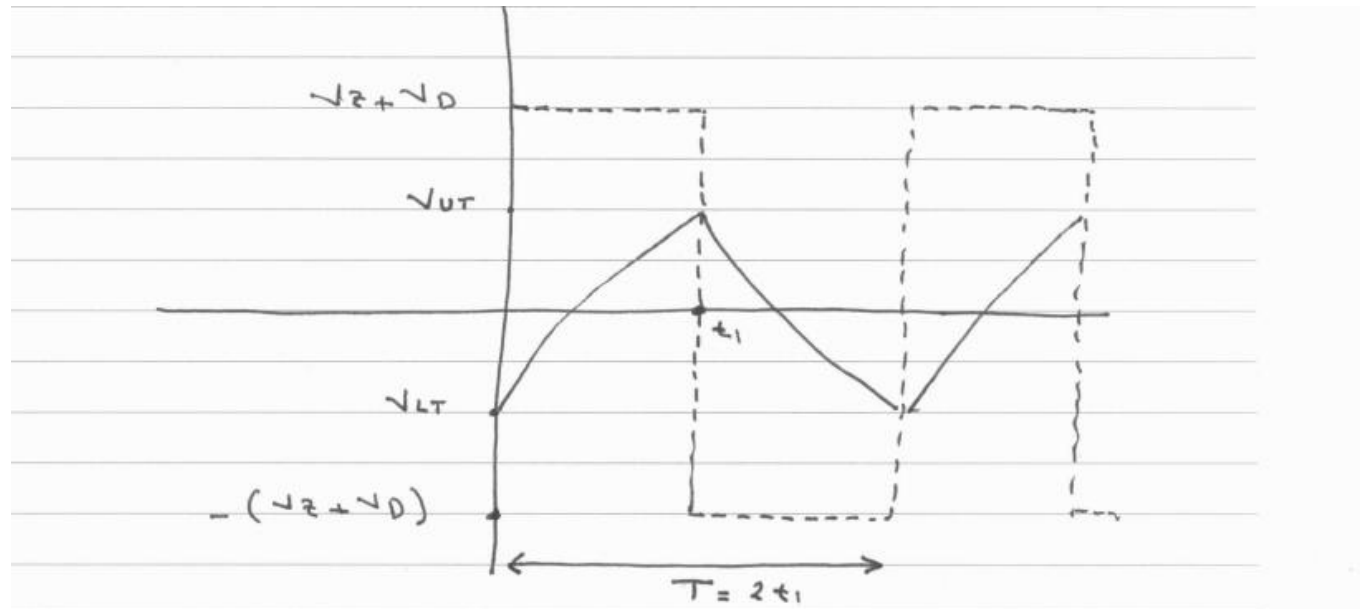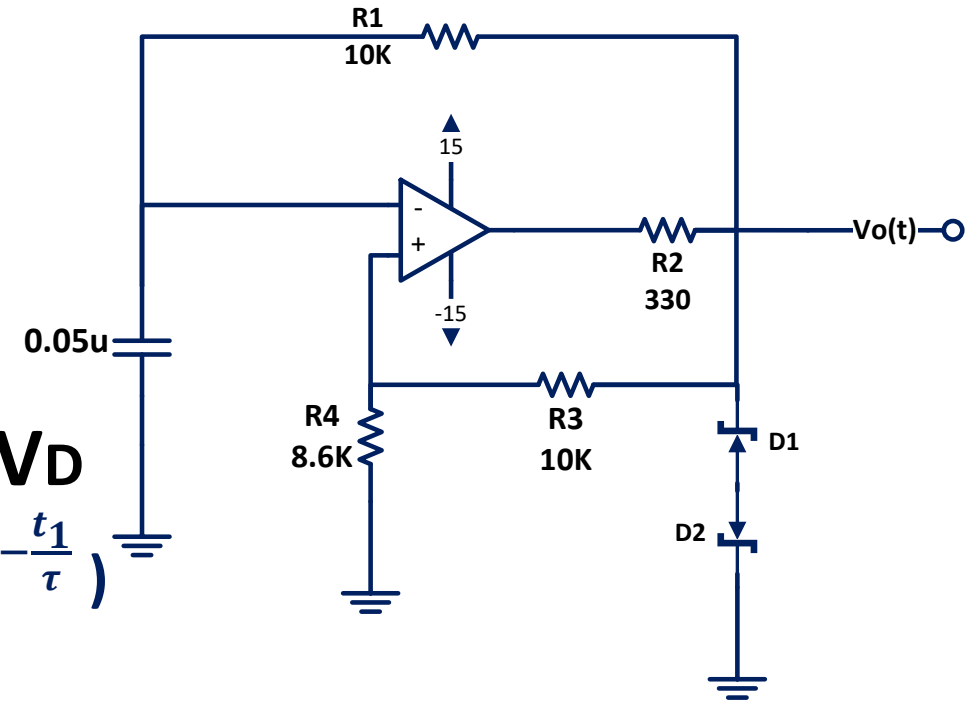- $\frac{2\beta}{(1 + \beta)} = (1 - e^{-\frac{t_1}{\tau}})$



- $e^{-\frac{t_1}{\tau}} = \frac{1-\beta}{1+\beta}$

- $-\frac{t_1}{\tau} = \ln \frac{1-\beta}{1+\beta}$

- $t_1 = \tau \ln \frac{1+\beta}{1-\beta} = R_1 C_1 \ln \frac{1+\beta}{1-\beta}$


- $T = 2t_1 = 2R_1 C_1 \ln \left(\frac{1+\beta}{1-\beta} \right)$

$$f_o = \frac{1}{T}$$

- $\therefore f_o = \frac{1}{T} = \frac{1}{2R_1 C_1 \ln \left(\frac{1+\beta}{1-\beta} \right)}$

- If $R_4 = 0.859R_3 \rightarrow \beta = 0.462$



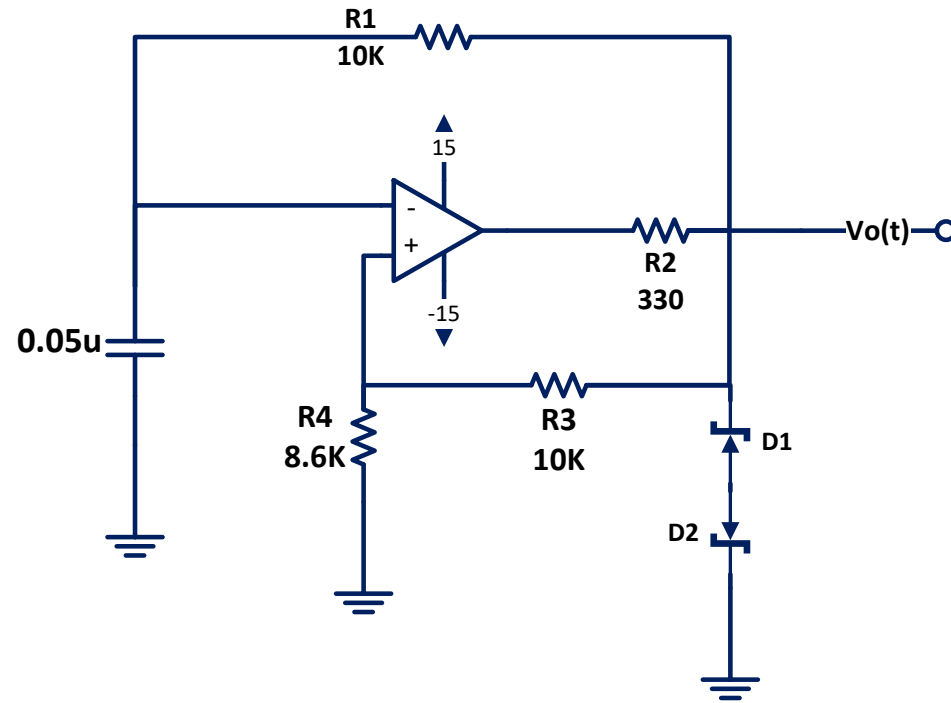
- $\ln \left(\frac{1+\beta}{1-\beta} \right) = 1$



$$\therefore f_o = \frac{1}{2R_1 C_1}$$

Oscillators

An Op-Amp Triangle Generator

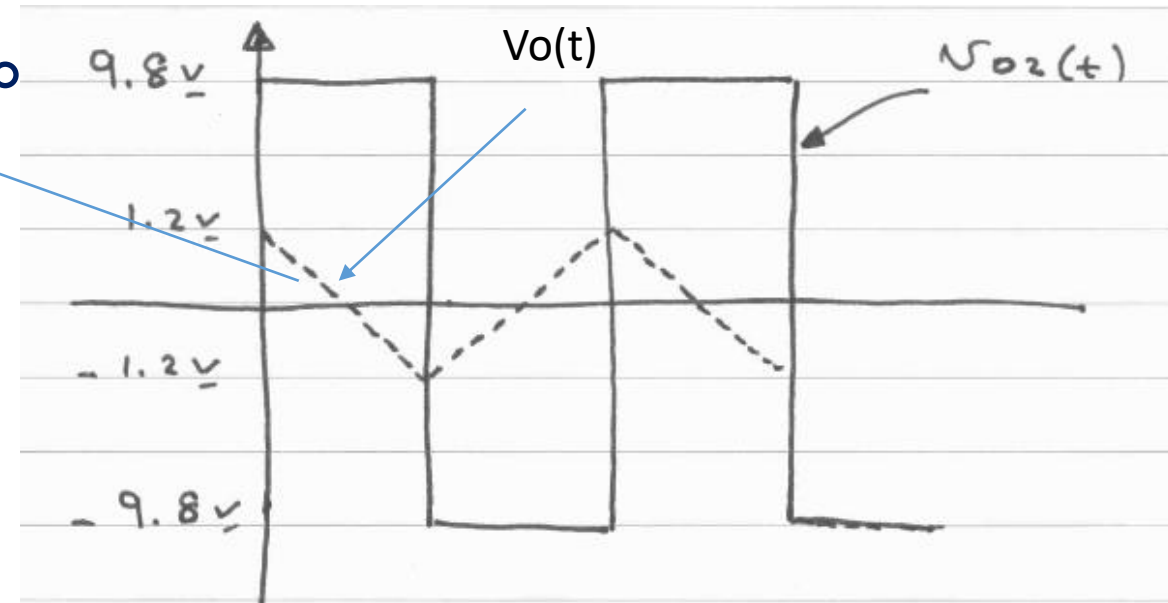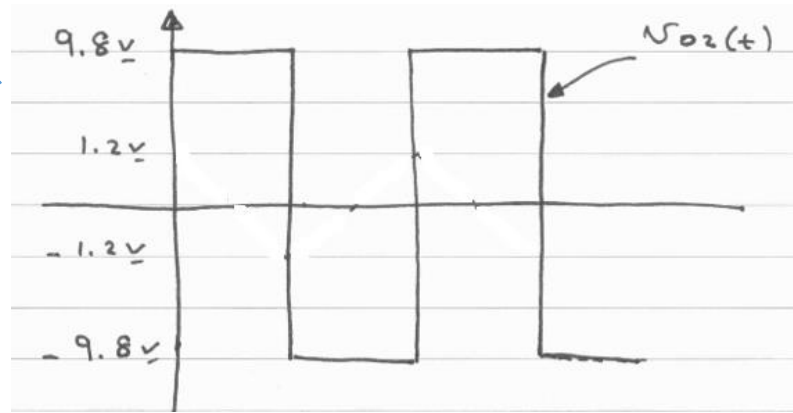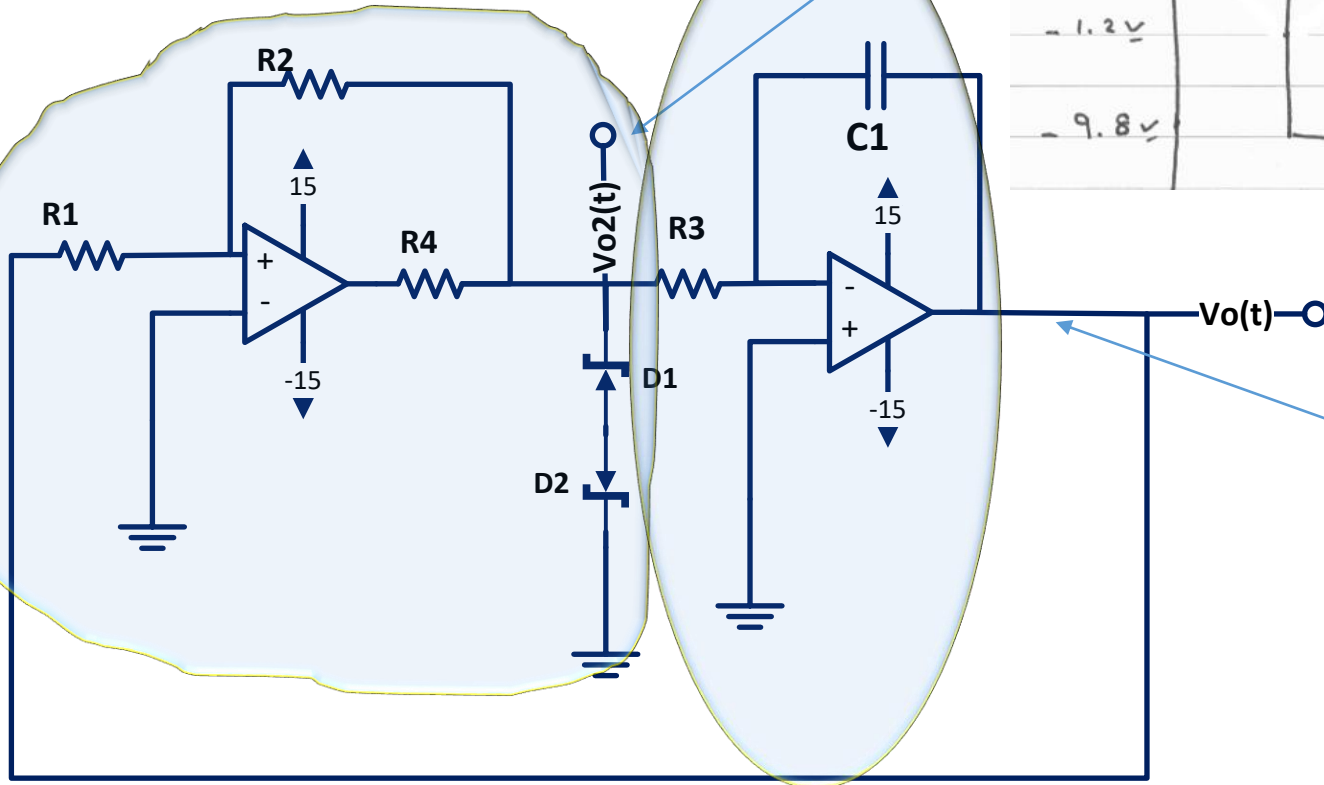

$$V_Z = 9.1\text{v}$$

$$R_1 = 100\text{K}\Omega$$

$$R_2 = 820\text{K}\Omega$$

$$V_Z + V_D = 9.8\text{v}$$

$$\frac{R_1}{R_2} (V_Z + V_D) = 1.2\text{v}$$

Oscillators

An Op-Amp Triangle Generator

It consists of two stages




- a) Non inverting Schmitt trigger comparator
- b) Inverting integrator

It provide two different output waveforms

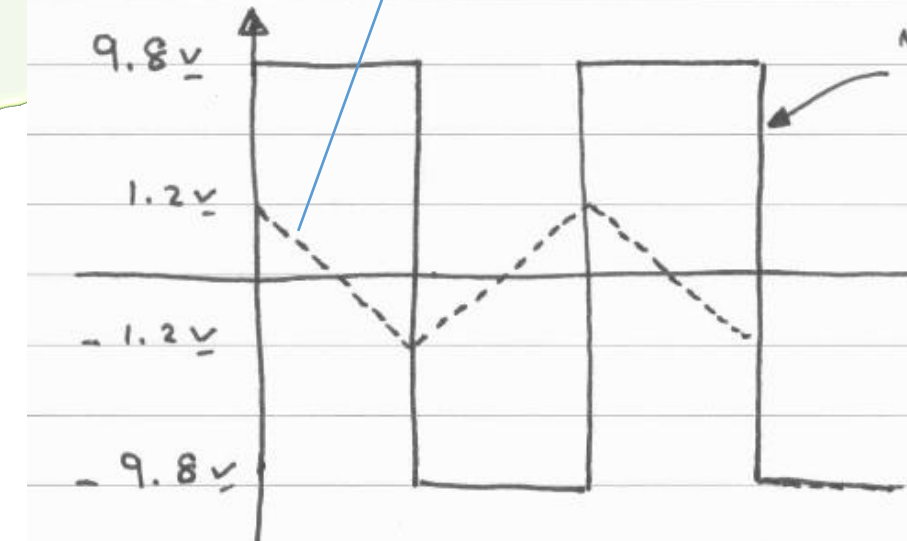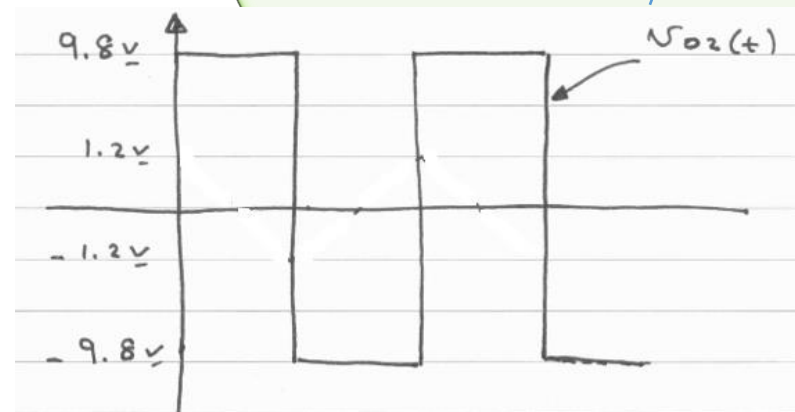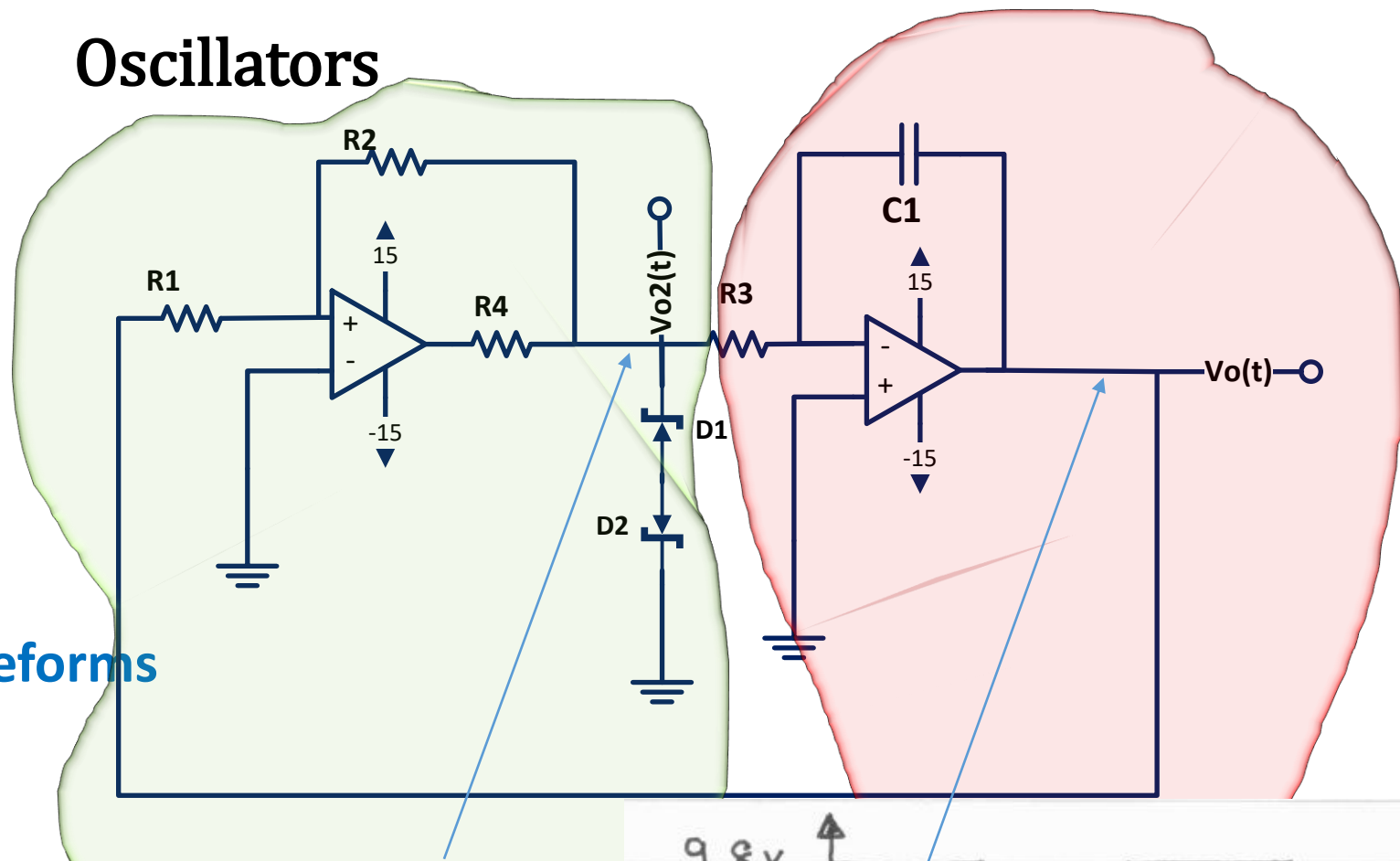- a) Square wave
- b) Triangle wave

$$V_{UT} = \frac{R_1}{R_2} (V_Z + V_D) = 1.2v$$

$$V_{LT} = -\frac{R_1}{R_2} (V_Z + V_D) = -1.2v$$



Inverting Integrator

Assuming that $V_c(0^-) = 0$

$$V_{out} = -V_c(t)$$


$$V_c(t) = \frac{1}{C_1} \int_0^t i_{in}(t) dt$$

$$i_{in}(t) = \frac{V_{in}(t)}{R_3}$$

$$V_{out} = -\frac{1}{R_3 C_1} \int_0^t V_{in}(t) dt$$

$$V_{in}(t) = V_{in}, \text{ DC}$$
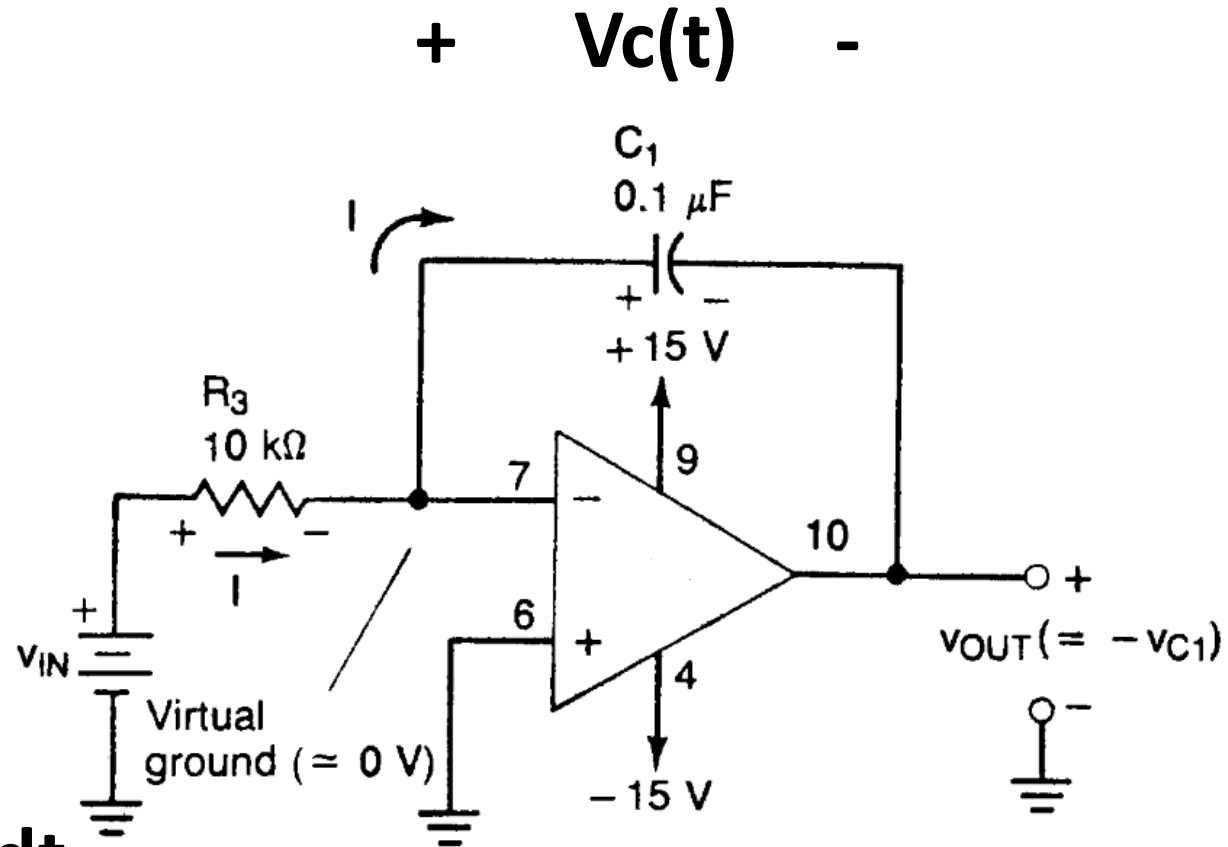
$$\therefore V_{out} = -\frac{V_{in}}{R_3 C_1} t$$



Inverting Integrator

Assuming that $V_i = -10\text{mV}$,

find $V_o(t)$ at 0.1s and 0.2s


$$V_{out} = -\frac{V_{in}}{R_3 C_1} t = -\frac{V_{in}}{(10\text{k}\Omega)(0.1\mu\text{F})} t = -1000V_{in} t$$

If v_{in} is -10mV and t is 0.1s

$$V_{out} = -1000V_{in} t = -(1000)(-10\text{mv})(0.1\text{s}) = 1\text{v}$$

And in 0.2s
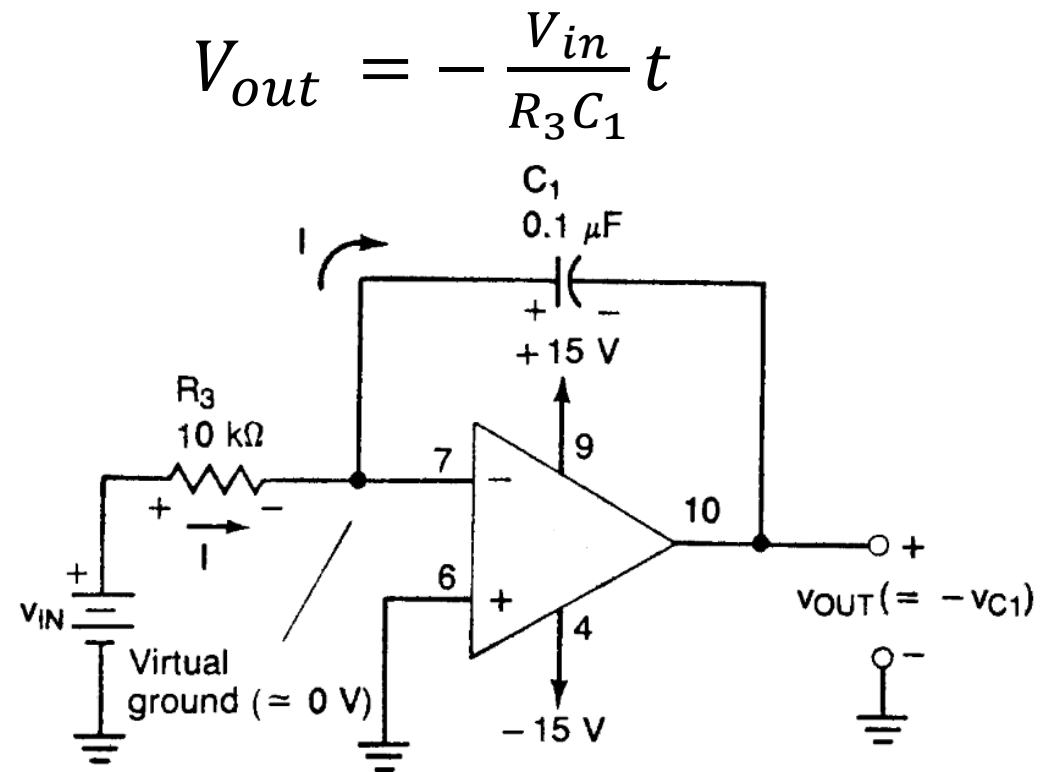
$$V_{out} = -1000V_{in} t = -(1000)(-10\text{mv})(0.2\text{s}) = 2\text{v}$$



Assuming that $+V_{sat}$ is 13 v we may solve the time to reach saturation


$$V_{out} = -\frac{V_{in}}{R_3 C_1} t = +V_{sat}$$

$$t = \frac{+V_{sat}}{-v_{in}} R_3 C_1 = \frac{13\text{v}}{-(-10\text{mv})} (10\text{k}\Omega)(0.1\mu\text{f})$$

$$= (1300)(1\text{ms}) = 1.3\text{s}$$

Oscillators


Inverting Integrator

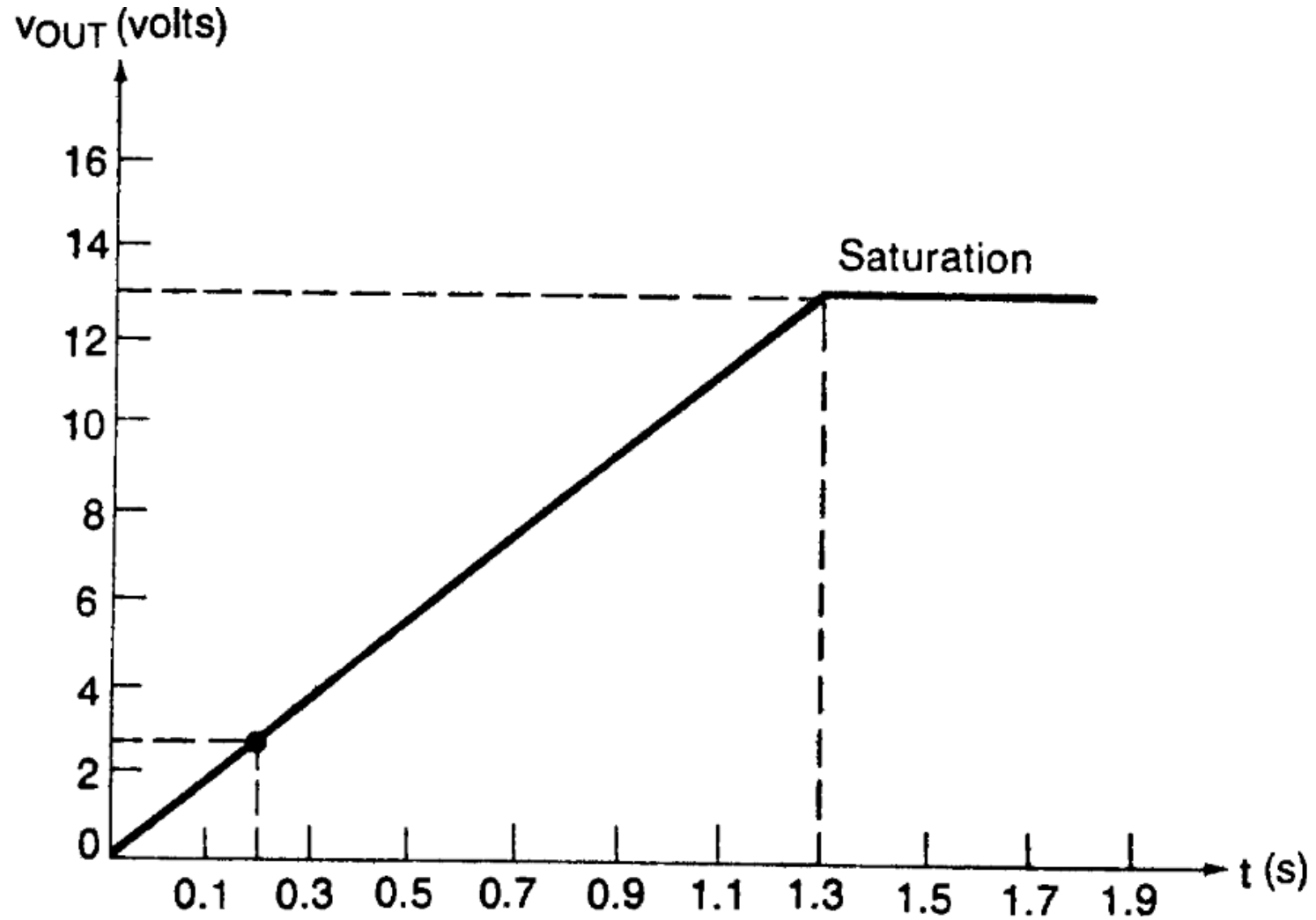

Oscillators

Inverting Integrator

To determine f_o

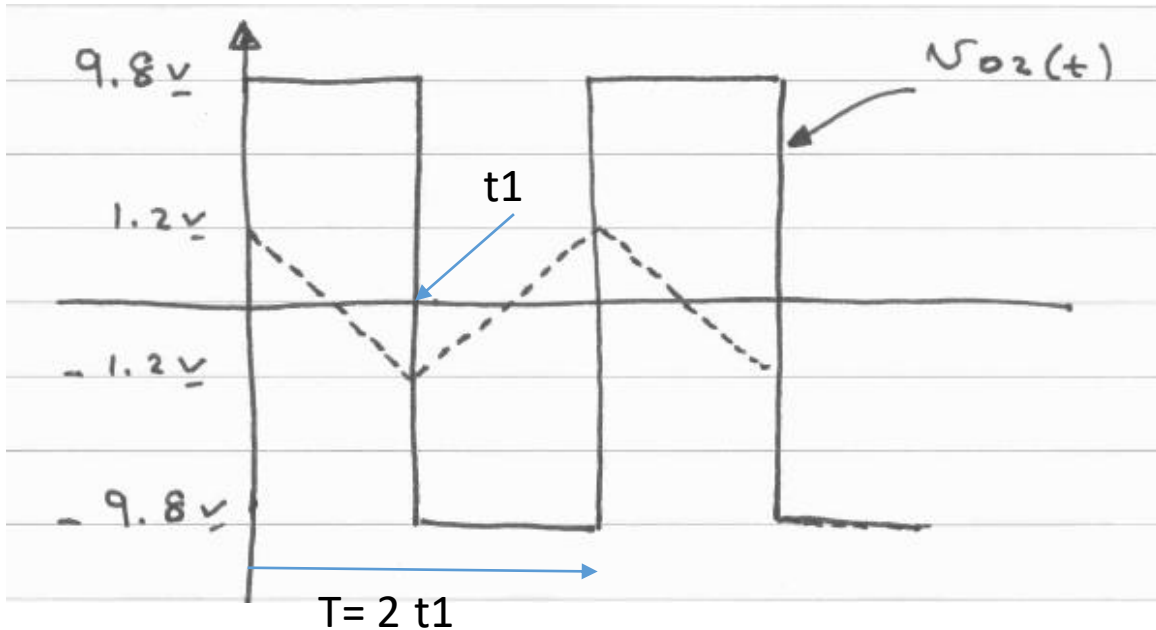

For $t_1 \geq t \geq 0$

$$V_o(t) = V_{UT} - \frac{V_{in}}{R_3 C_1} t$$

$$V_{UT} = \frac{R_1}{R_2} (V_Z + V_D)$$

$$V_{in} = V_Z + V_D$$

$$V_o(t) = \frac{R_1}{R_2} (V_Z + V_D) - \frac{V_Z + V_D}{R_3 C_1} t$$


$$\text{At } t = t_1 ; V_o(t_1) = -\frac{R_1}{R_2} (V_Z + V_D) = V_{LT}$$

$$\therefore t_1 = \frac{2R_1 R_3 C_1}{R_2}$$

$$f_o = \frac{1}{T} = \frac{1}{2t_1} = \frac{R_2}{4R_1 R_3 C_1}$$


Oscillators

The 555 Timer As an Oscillator.

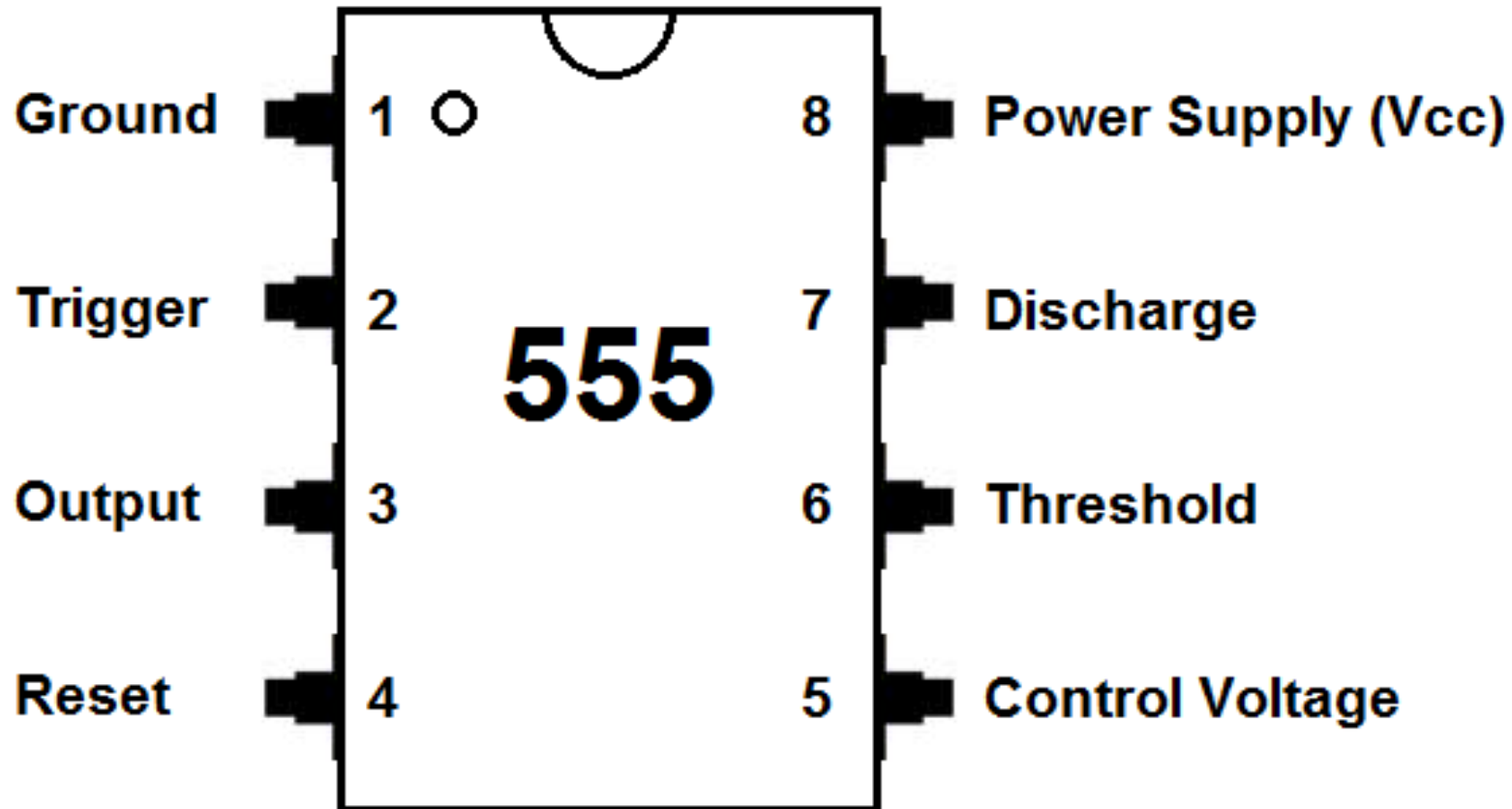

Oscillators


The 555 Timer As an Oscillator.

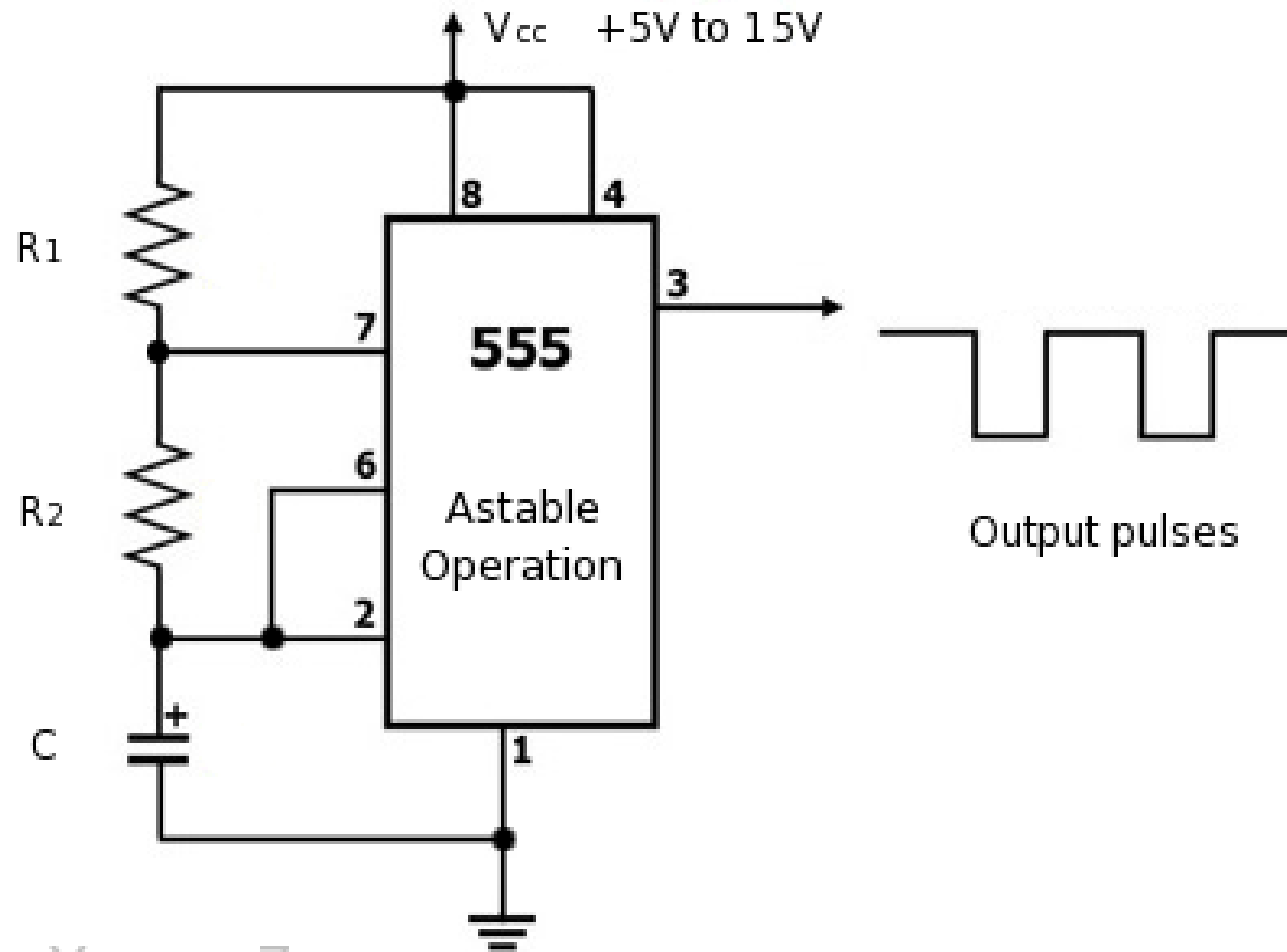

Oscillators

The 555 Timer As an Oscillator.

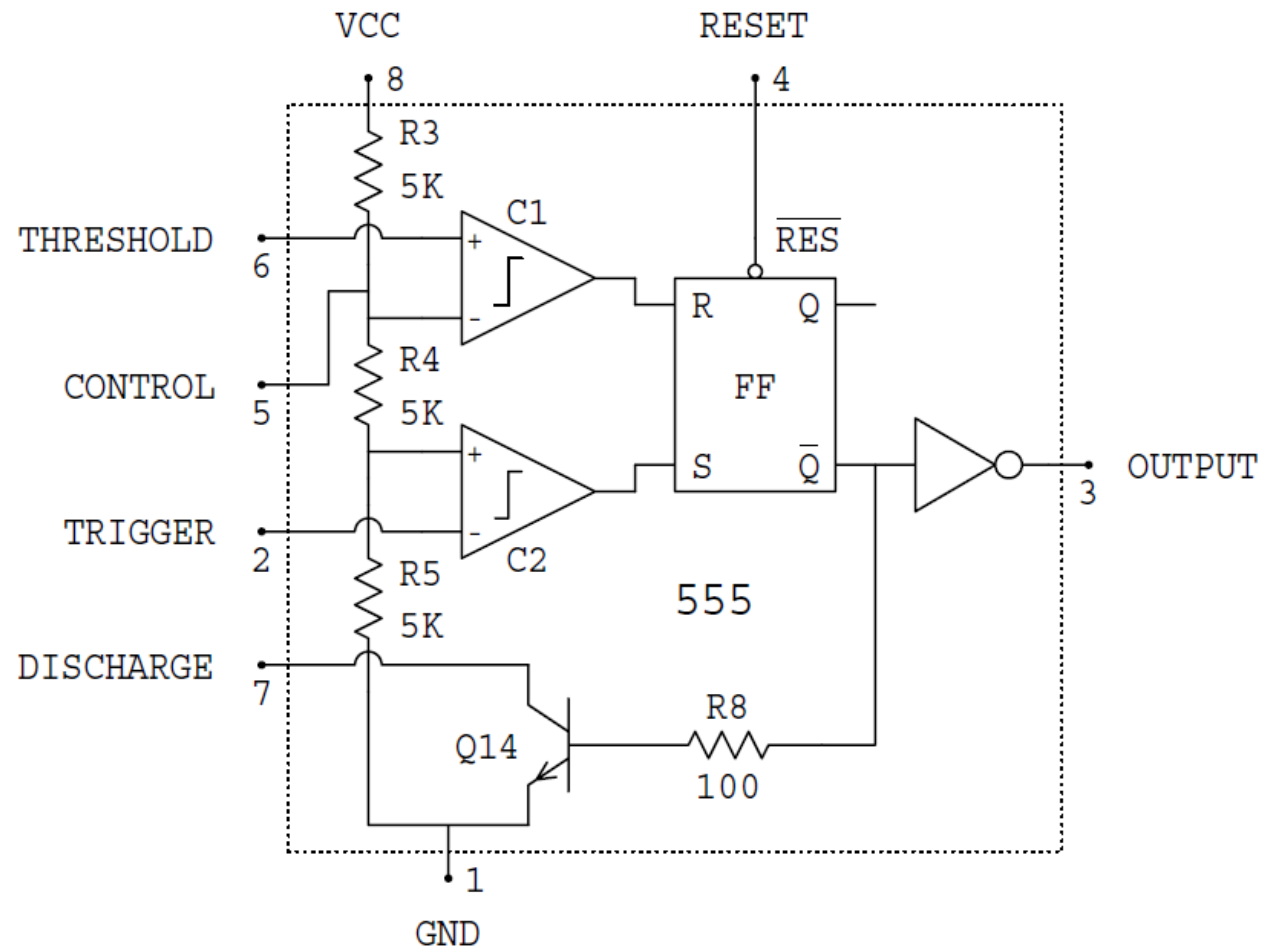Functional block diagram of the 555 integrated circuit timer




Oscillators

The 555 Timer As an Oscillator.

Internal Component of 555

- Two comparators
- Three R (5K) that set the trigger Levels
- Transistor that act as a switch
- S R Latch


S	R	Q_n
0	0	Q_n no change
1	0	1
0	1	0
1	1	Forbidden

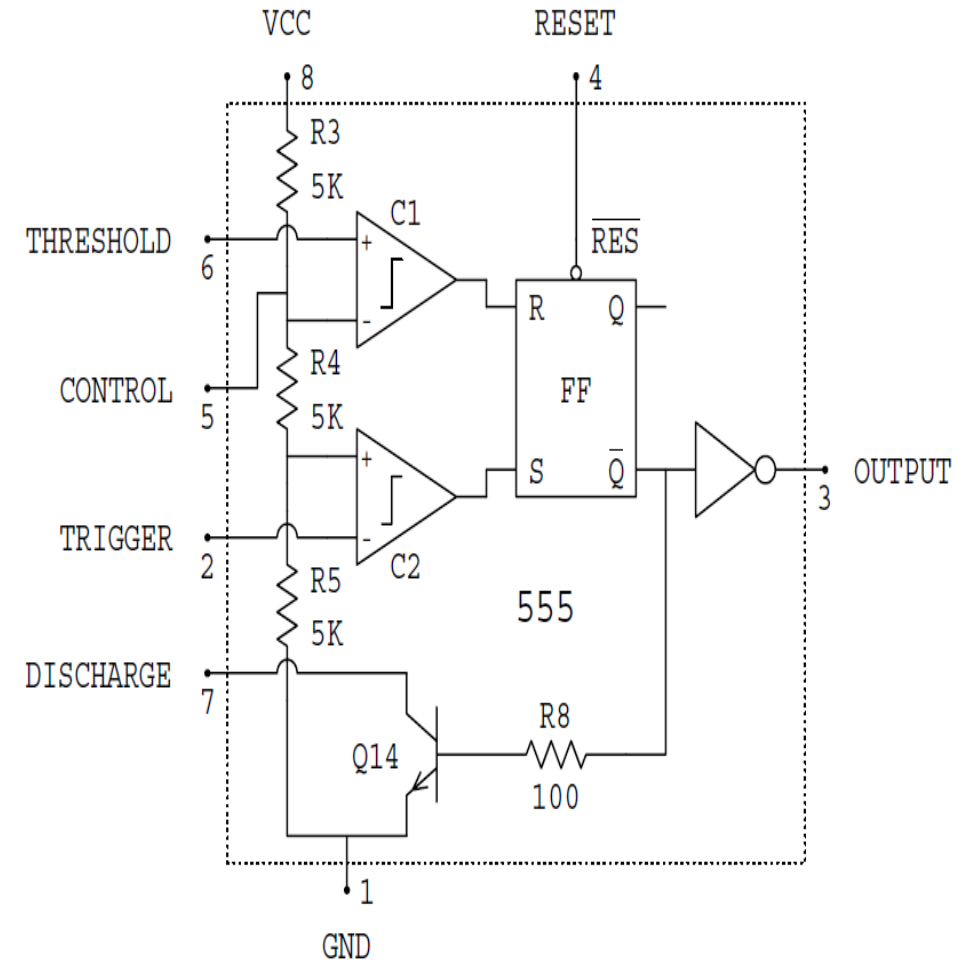

Oscillators

The 555 Timer As an Oscillator.

555 timer as an a stable circuit

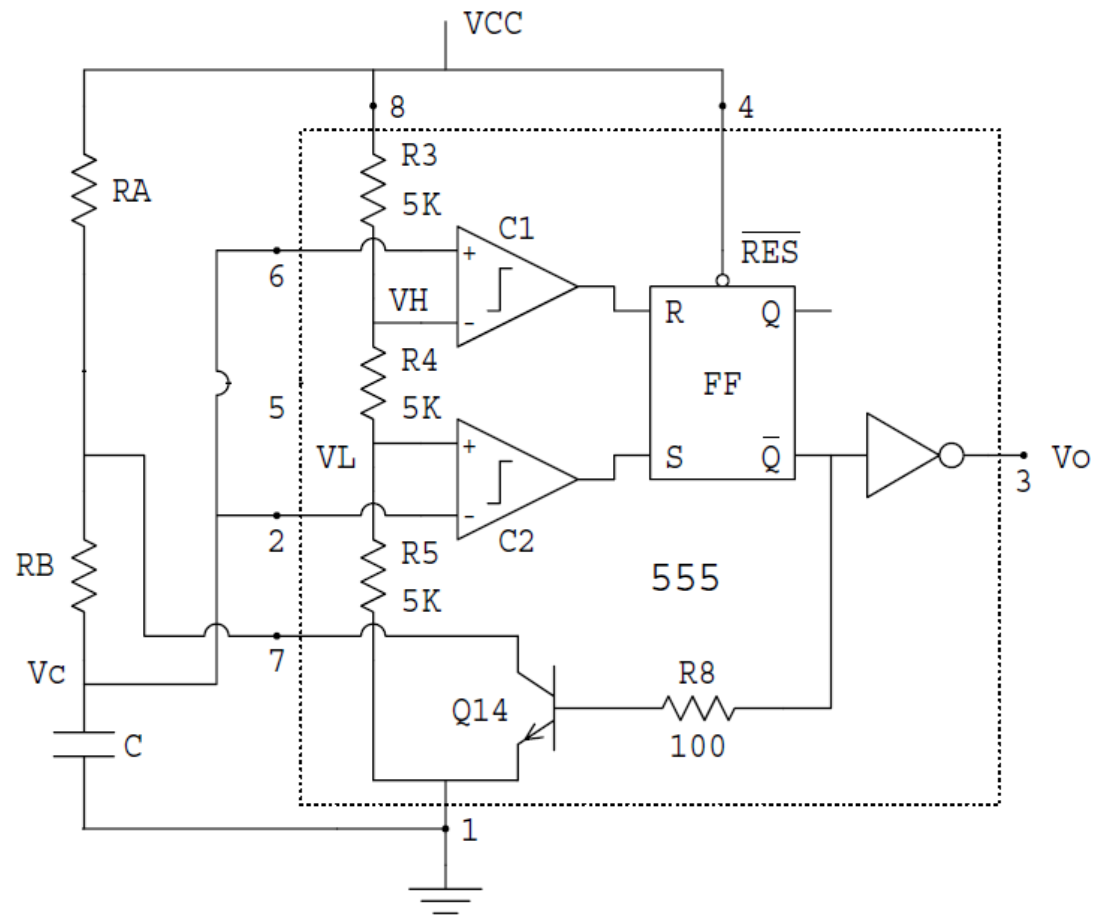

The 555 Timer As an Oscillator.

Operation of the 555 timer oscillator.

At the beginning

$$V_C(0^+) = V_C(0^-) = 0$$



$$\therefore R = 0, S = 1$$

$$\therefore Q = 1, \bar{Q} = 0$$

∴ Transistor is off

∴ The capacitor starts charging

$$\tau_C = (R_A + R_B)C$$

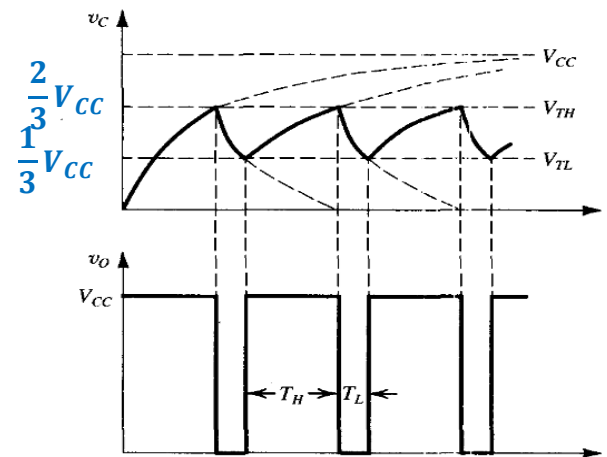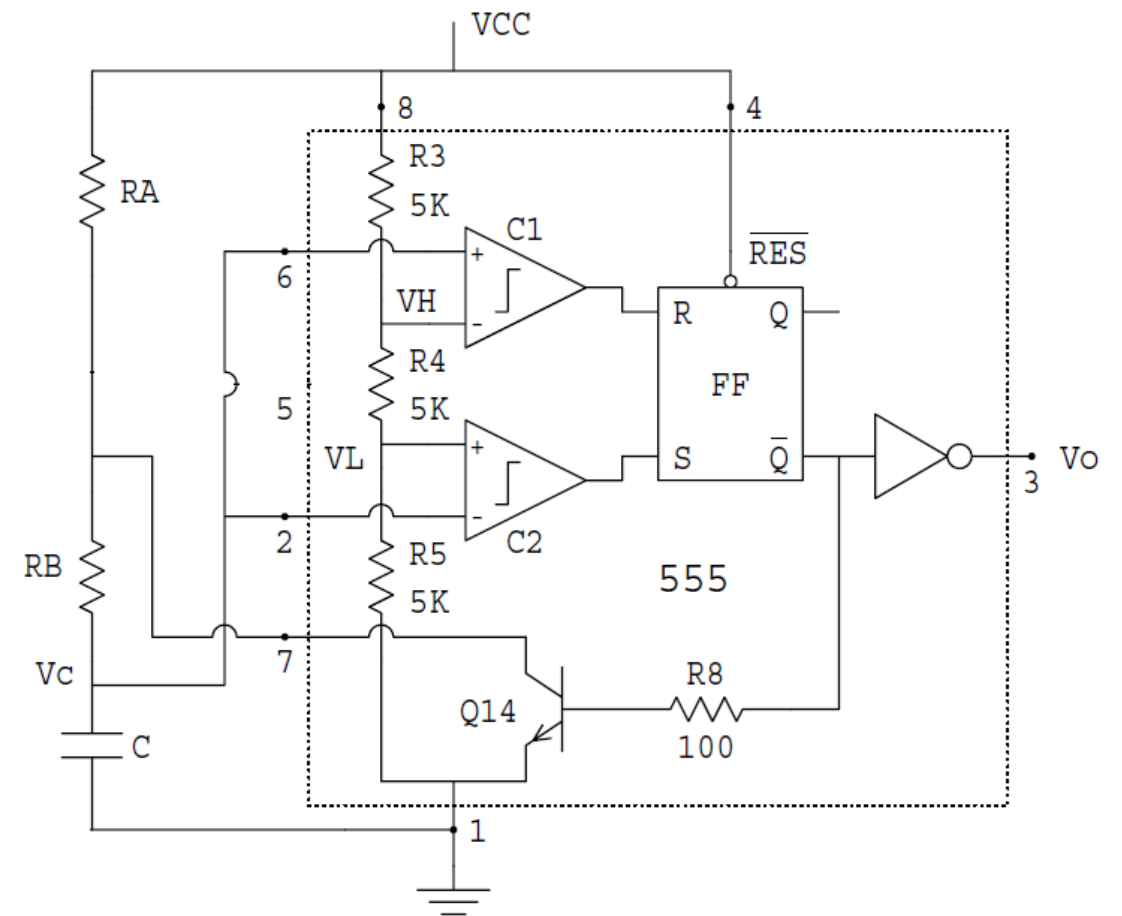

- When $V_C(t) > \frac{1}{3}V_{CC}$

- ∴ $R = 0$, and $S = 0$



No change

- ∴ $Q = 1$, and $\bar{Q} = 0$

- ∴ The transistor is still off

- ∴ The capacitor is still charging

$$\tau_c = (R_A + R_B)C$$

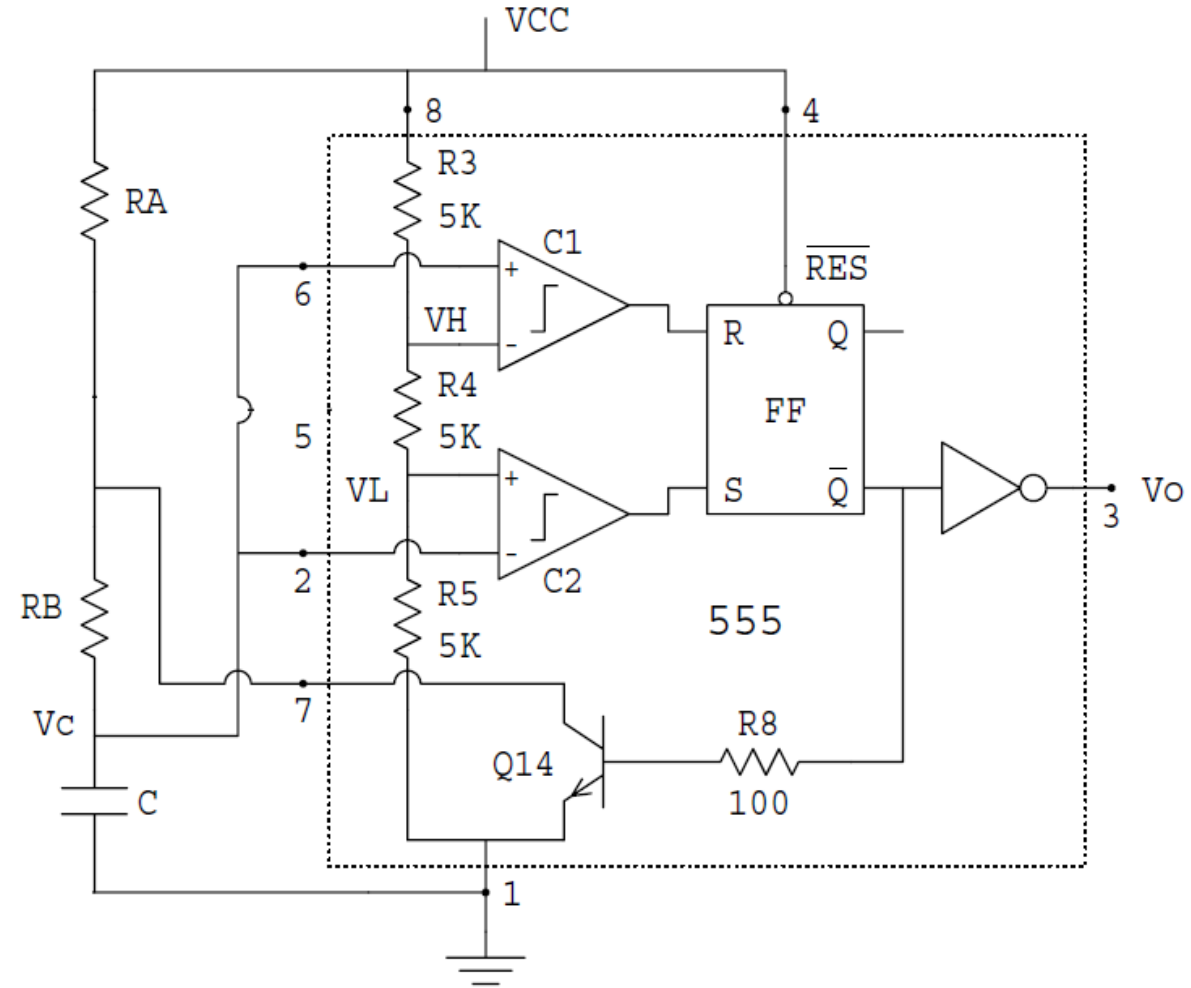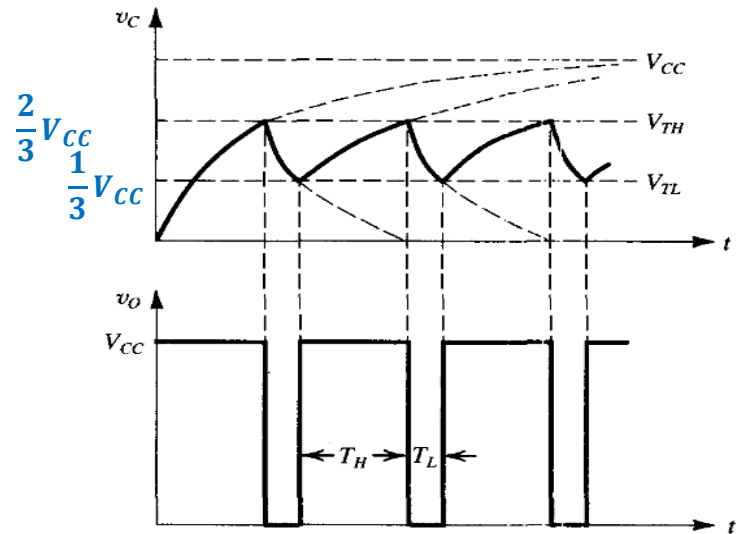

• When $V_C(t) > \frac{2}{3}V_{CC}$



∴ $R = 1$, and $S = 0$

∴ $Q = 0$, and $\bar{Q} = 1$

∴ The transistor turns on

∴ The capacitor starts discharging

$$\tau_d = R_B C$$

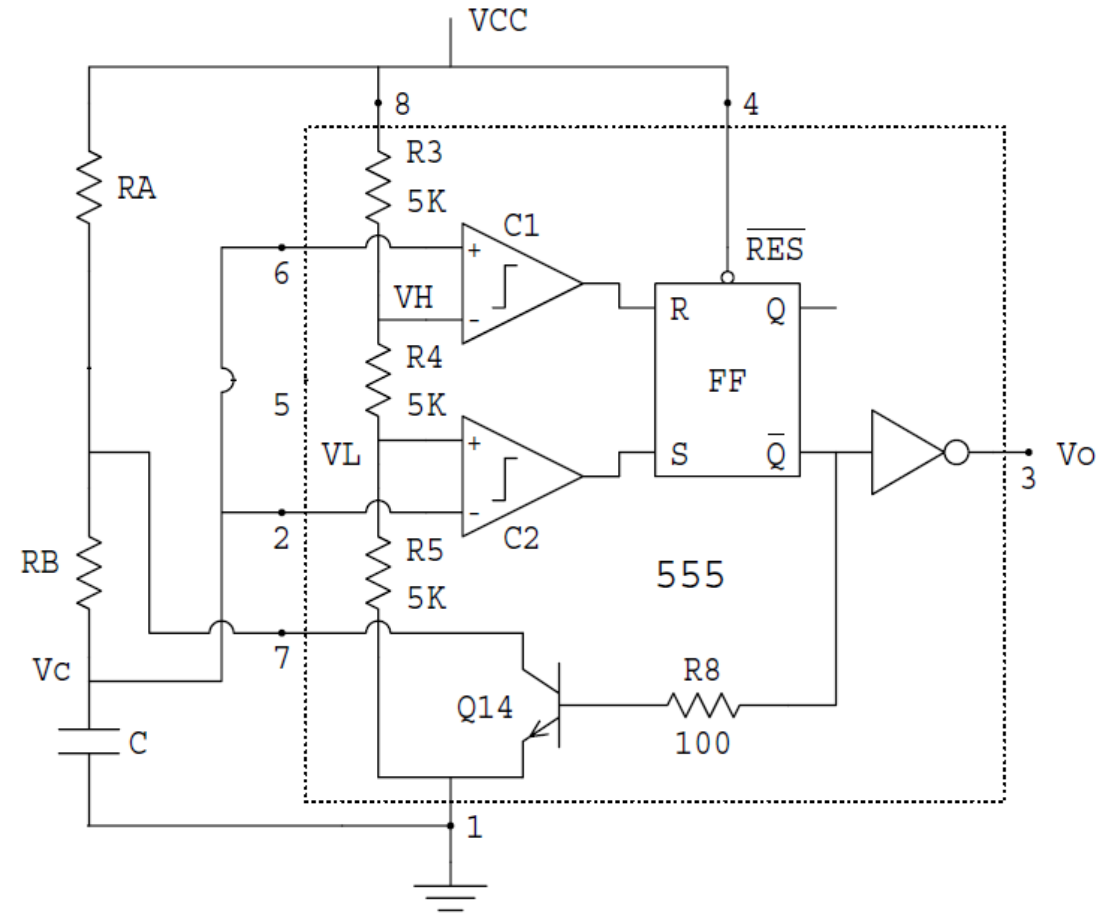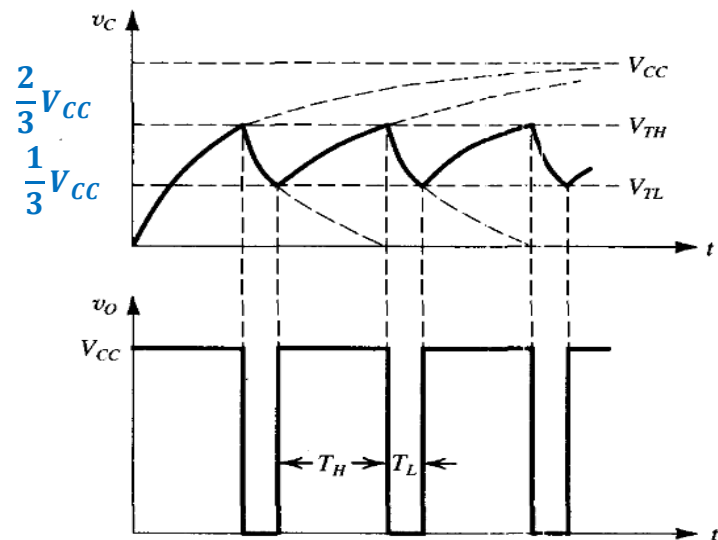



When $V_C(t) < \frac{1}{3}V_{CC}$

$\therefore S = 1$, and $R = 0$

$\therefore Q = 1$, and $\bar{Q} = 0$

\therefore The transistor turn Off



\therefore The capacitor starts charging

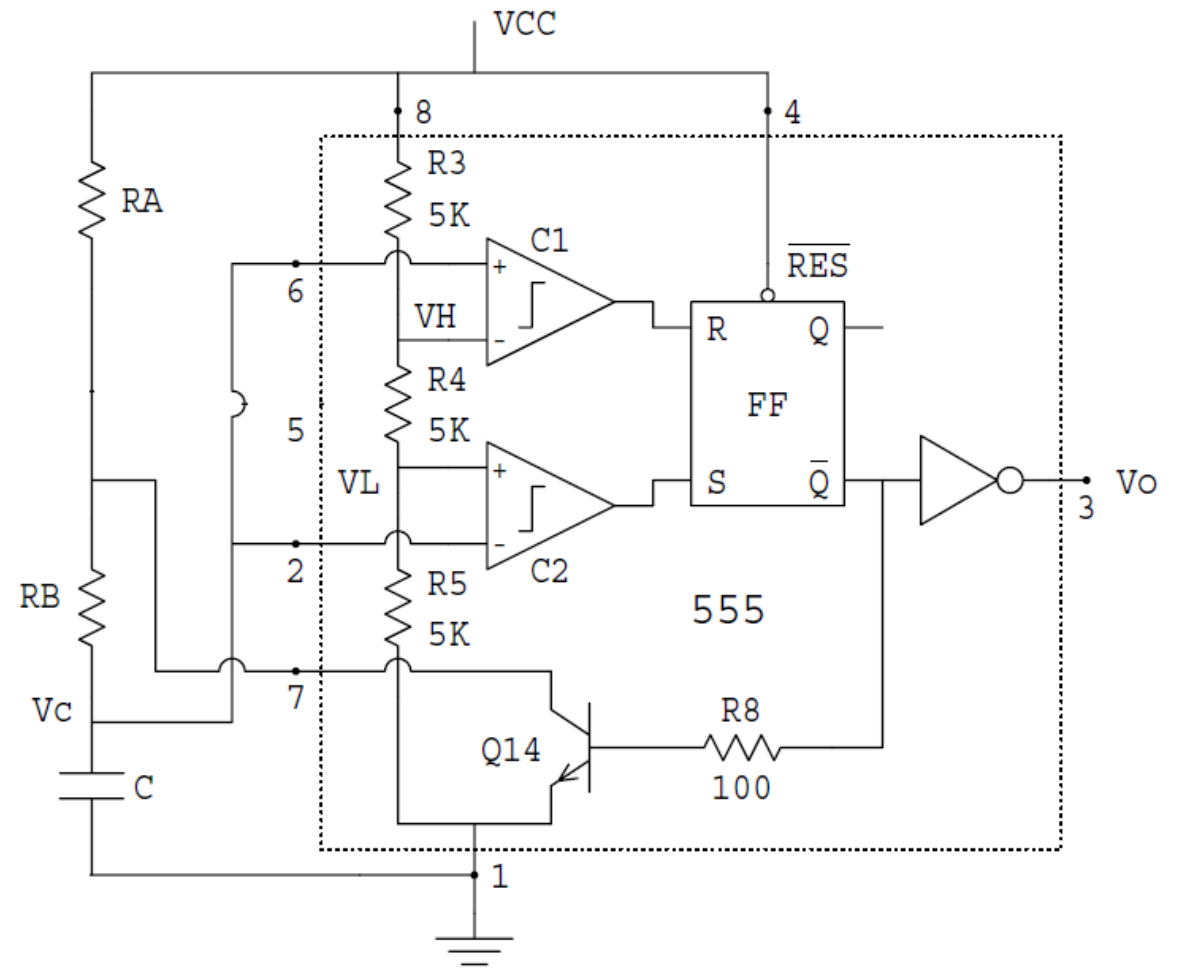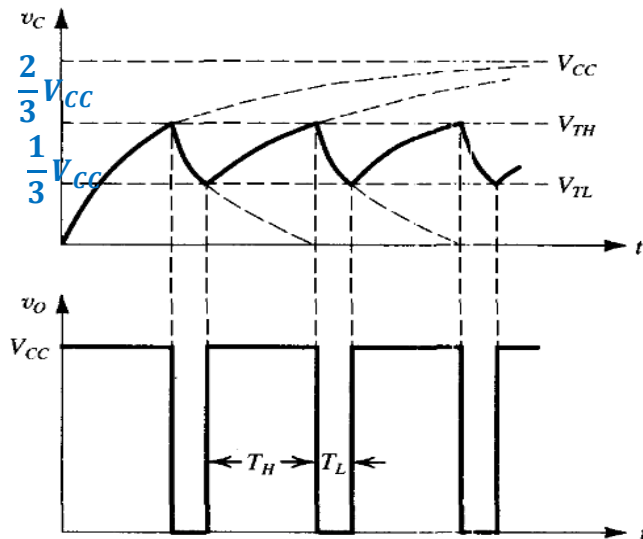

Oscillators

The 555 Timer As an Oscillator.

Operation of the 555 timer oscillator.

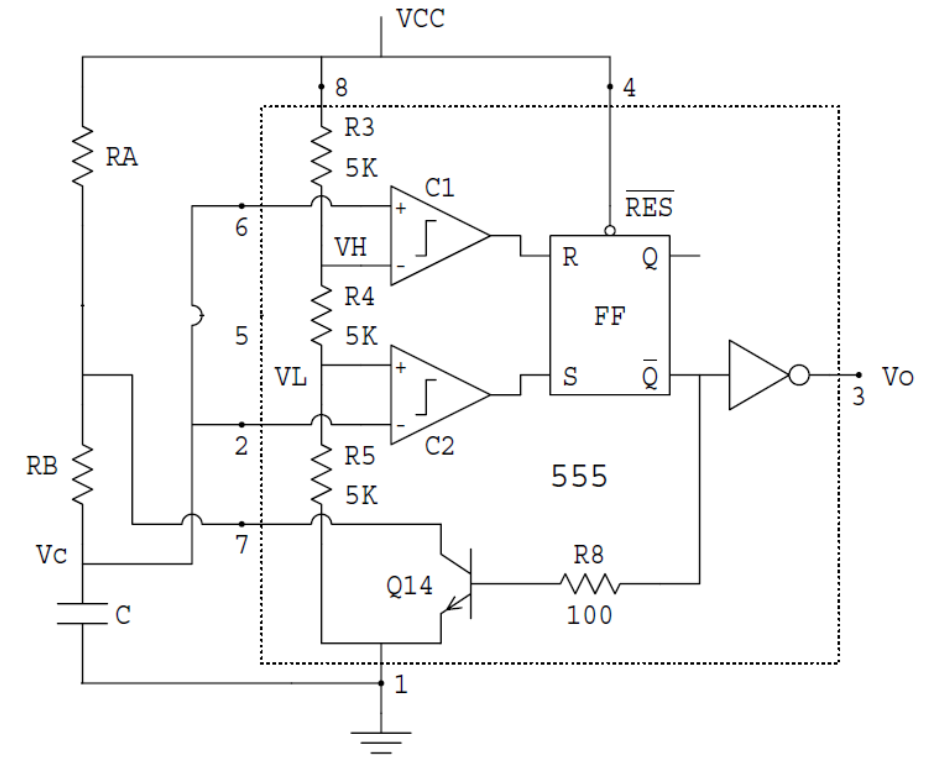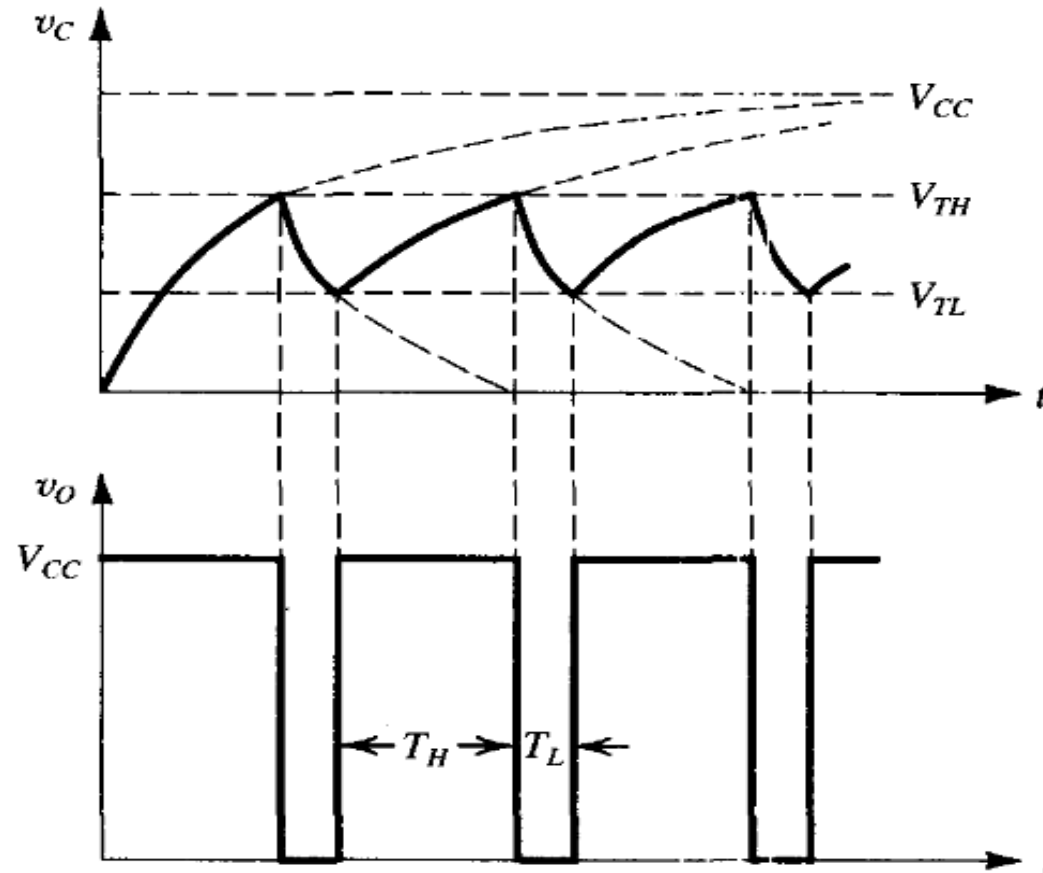

Oscillators

The 555 Timer As an Oscillator.

Operation of the 555 timer oscillator.

1. To find T_C


$$V_c(t) = V_I + (V_f - V_I)(1 - e^{-\frac{t}{\tau}})$$

$$V_c(T_C) = \frac{2}{3}V_{CC} ; \quad V_I = \frac{1}{3}V_{CC} ; \quad V_f = V_{CC}$$

$$\tau_c = (R_A + R_B)C$$

$$V_c(T_C) = \frac{2}{3}V_{CC} = \frac{1}{3}V_{CC} + (V_{CC} - \frac{1}{3}V_{CC})(1 - e^{-\frac{t}{\tau}})$$
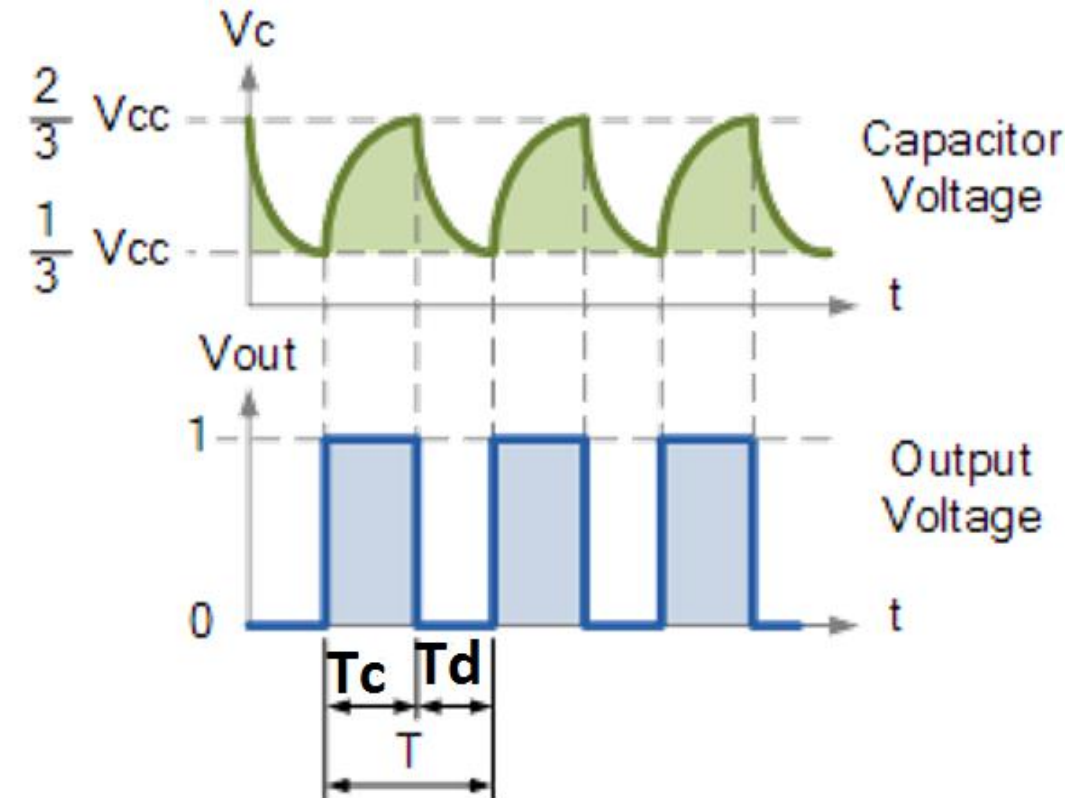
$$T_C = \tau_c \ln 2 = (R_A + R_B)C \ln 2$$



Oscillators

The 555 Timer As an Oscillator.

Operation of the 555 timer oscillator.

2-To find T_d


$$V_c(t) = V_I + (V_f - V_I)(1 - e^{-\frac{t}{\tau}})$$

$$V_c(T_d) = \frac{1}{3}V_{CC} ; \quad V_I = \frac{2}{3}V_{CC} ; \quad V_f = 0$$

$$\tau_d = R_B C$$

$$V_c(T_d) = \frac{1}{3}V_{CC} = \frac{2}{3}V_{CC} (0 - \frac{2}{3}V_{CC}) (1 - e^{-\frac{t}{\tau}})$$
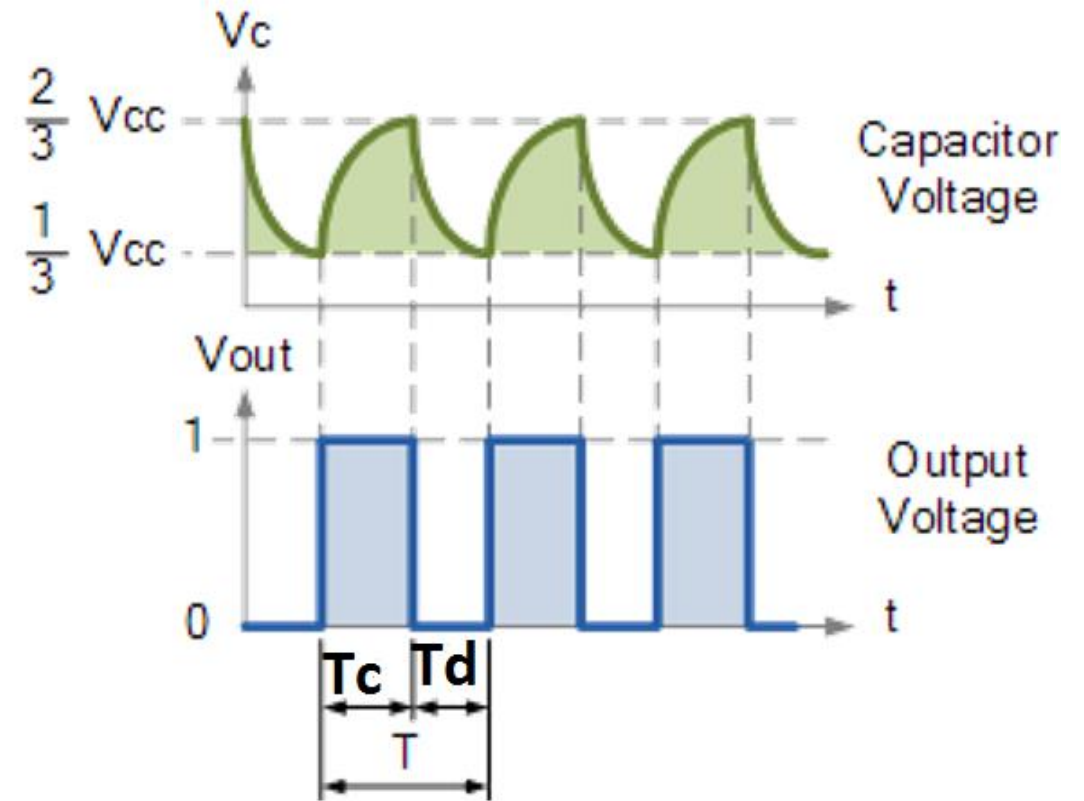
$$\therefore T_d = \tau_d \ln 2 = R_B C \ln 2$$



Oscillators

The 555 Timer As an Oscillator.

Operation of the 555 timer oscillator.

3- To find T

$$T = T_C + T_d = (R_A + 2R_B)C \ln 2$$

$$T = 0.693 (R_A + 2R_B)C$$

4- To find F

$$F = \frac{1}{T} = \frac{1}{0.693 (R_A + 2R_B)C}$$

5- To find Duty cycle

$$\text{Duty cycle} = D = \frac{T_C}{T} = \frac{R_A + R_B}{R_A + 2R_B}$$

Function Generator

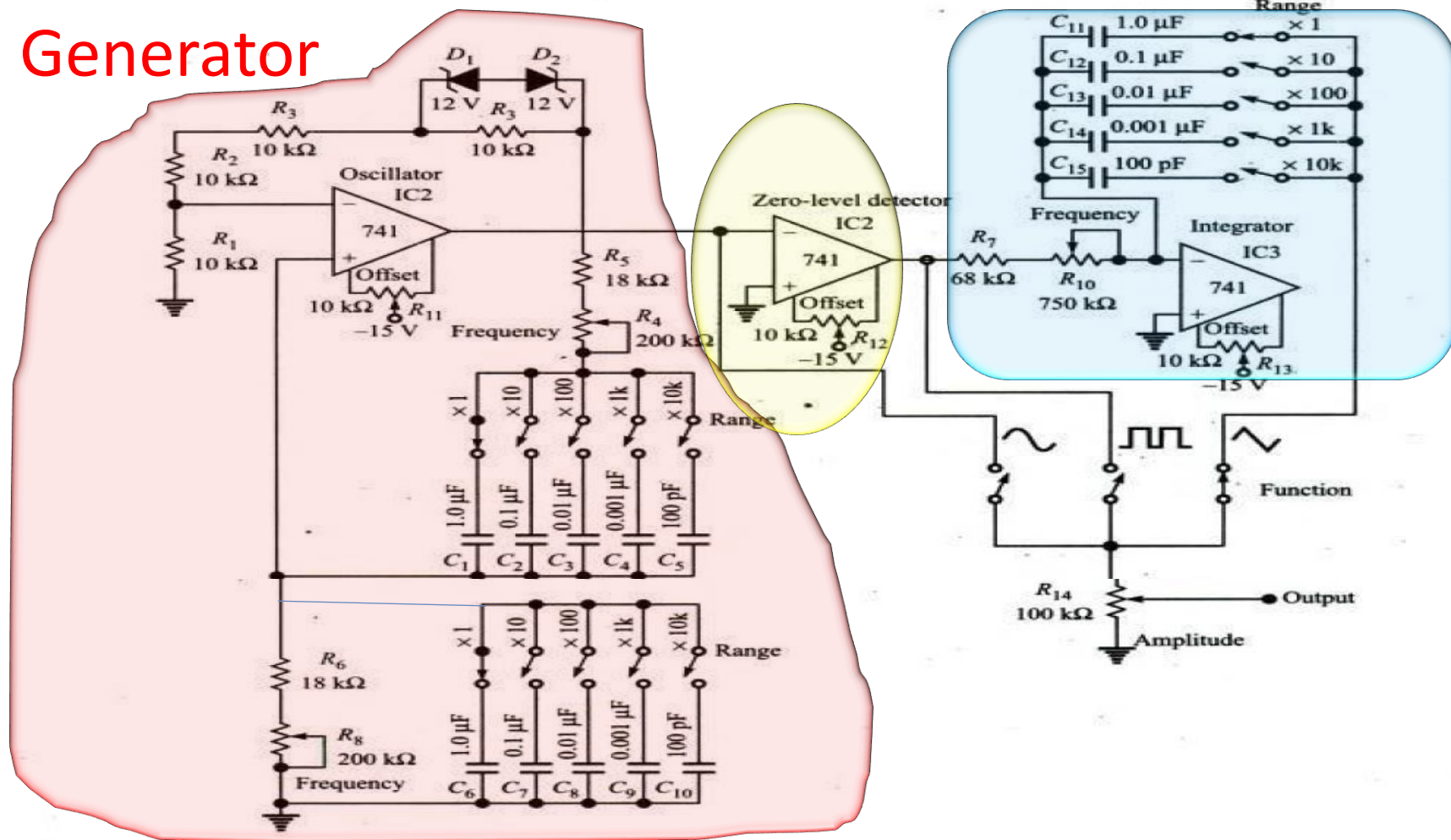


Fig. 16.3 Schematic of the function generator

