

# Negative Feedback

The background features abstract geometric shapes, primarily triangles, in various shades of blue and green. These shapes overlap and intersect, creating a dynamic and modern aesthetic. The colors range from light, airy blues to deeper, more saturated greens and blues.

# Negative Feedback


## Advantages

- 1- Stabilizes the gain of the amplifier against parameters changes in the active devices due to temperature .
- 2- Modifies the input and output impedance in any desired fashion.
- 3- Increases the Bandwidth .



## Disadvantages

- 1- Decreases the gain .
- 2- Oscillation .

# The General Feedback Structure

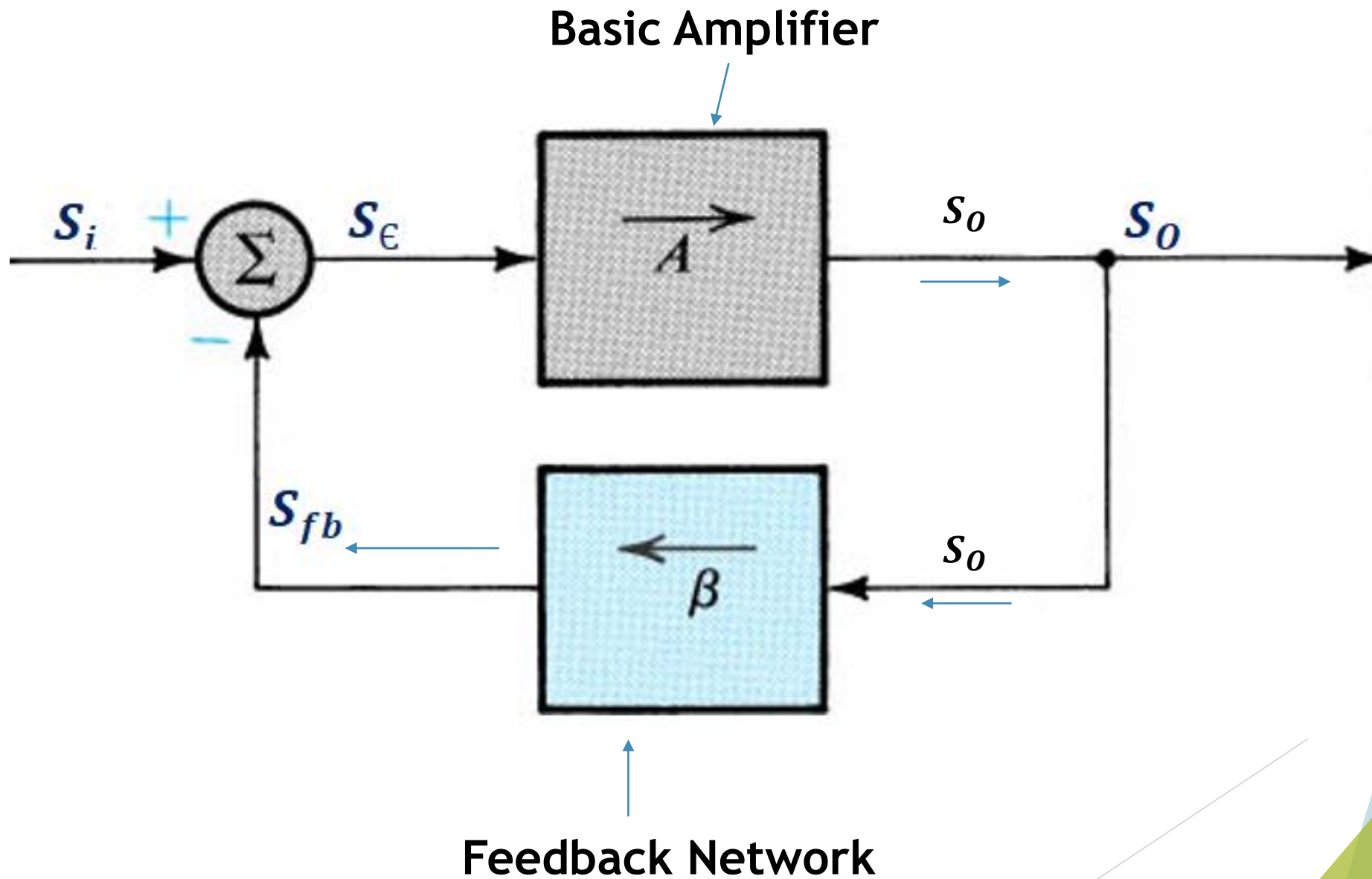

# Example of Feedback Amplifier

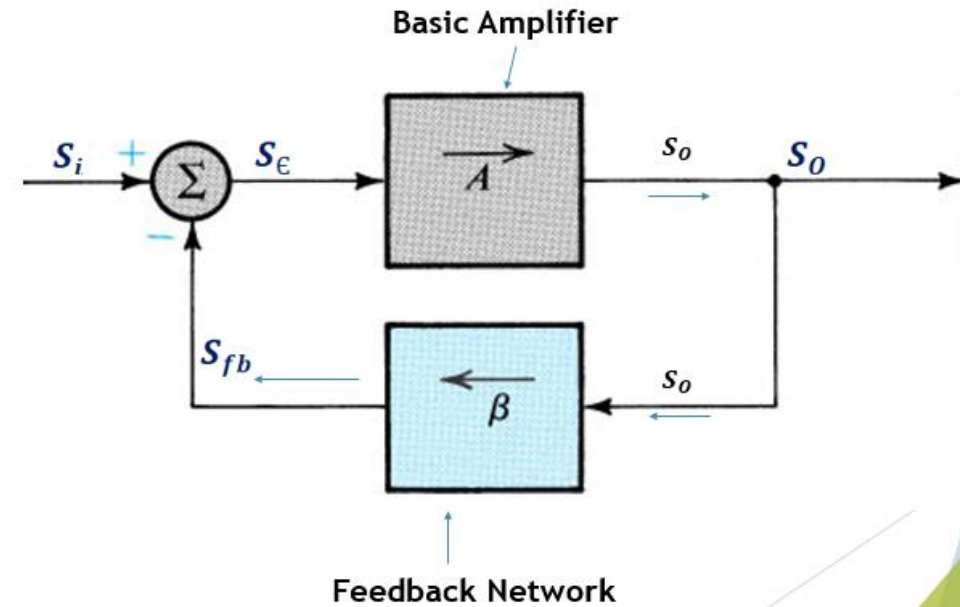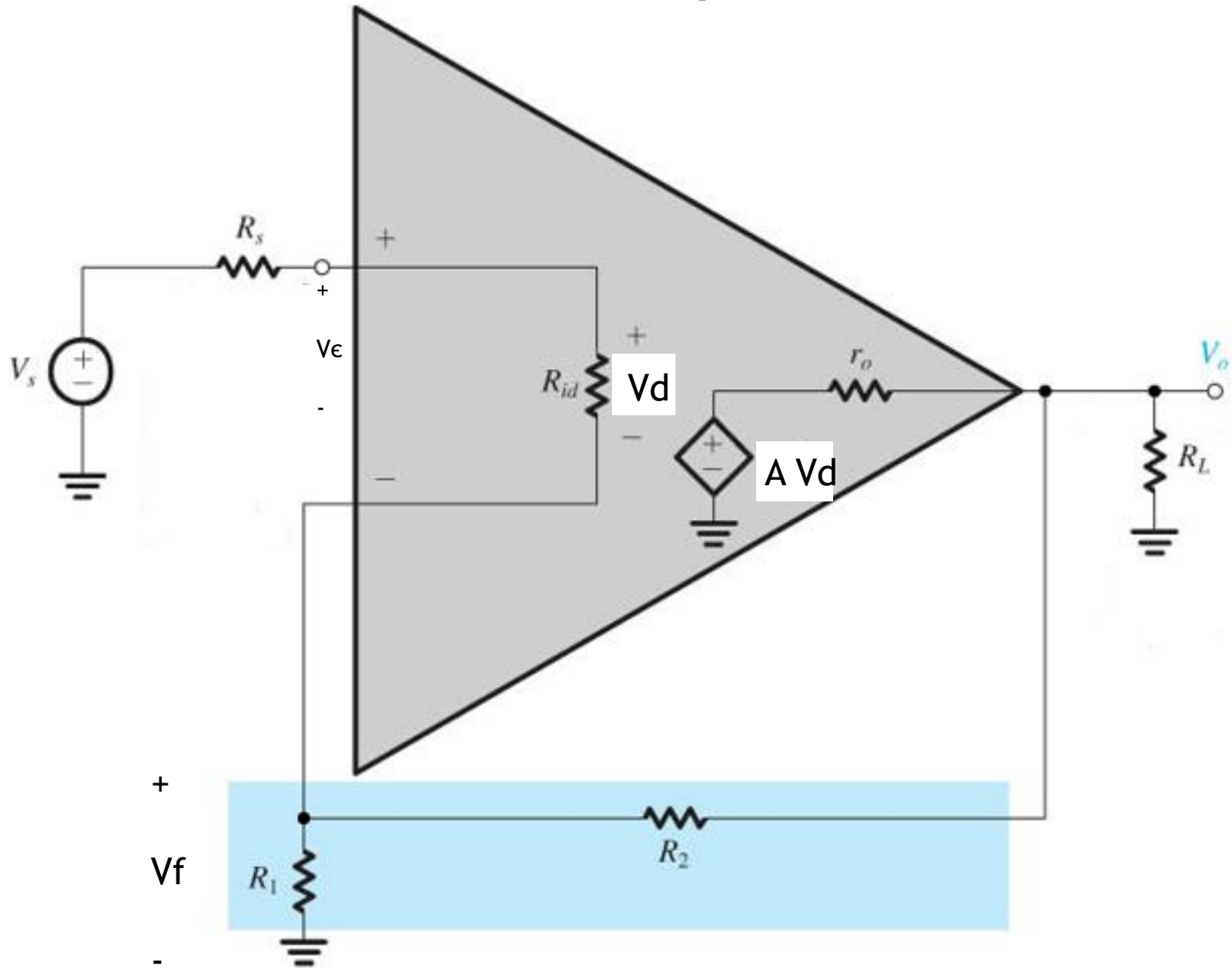

# Negative Feedback

## General Feedback equation

$$S_o = A S_\epsilon$$

$$S_\epsilon = S_i - S_{fb}$$


$$S_{fb} = \beta S_o$$

$$A_f = \frac{S_o}{S_i} = \frac{A}{1 + A\beta}$$

$A\beta \equiv$  Loop gain

If  $A\beta \gg 1$

$$\therefore A_f = \frac{1}{\beta}$$

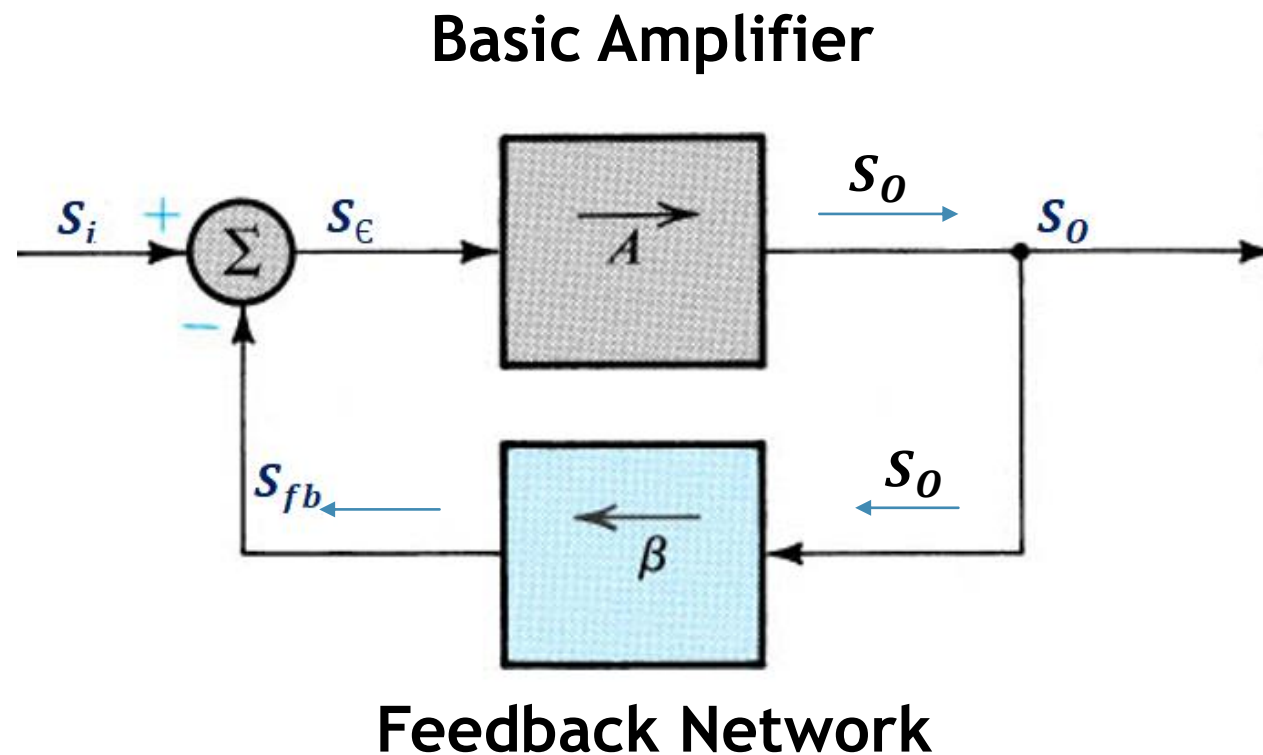

# Negative Feedback

## General Feedback equation

$$S_{\epsilon} = S_i - S_{fb}$$


$$S_{\epsilon} = S_i - \beta S_o$$

$$S_{\epsilon} = S_i - \beta \frac{A}{1+AB} S_i$$

$$S_{\epsilon} = S_i \left(1 - \frac{A\beta}{1+A\beta}\right)$$

If  $A\beta \gg 1$
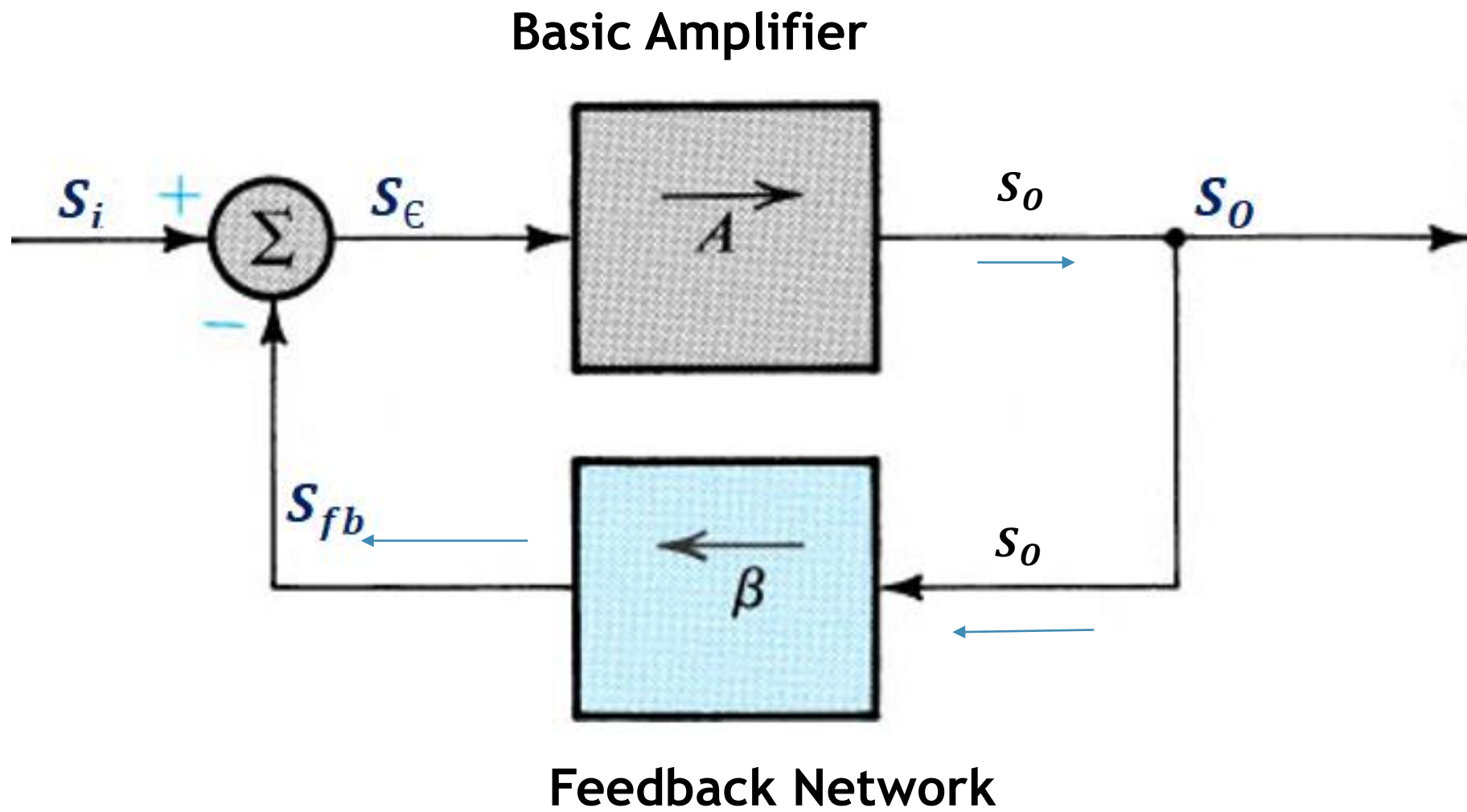
$$S_{\epsilon} \approx S_i \left(1 - \frac{A\beta}{A\beta}\right) = 0$$



# Gain stabilization

let  $A = 10,000$

$\beta = 0.01$

$\therefore A\beta = 100$

$$Af = \frac{A}{1 + A\beta} = 99$$


let  $A = 9000$

$\beta = 0.01$

$\therefore A\beta = 90$

$$Af = \frac{A}{1 + A\beta} = 98.9$$

# Negative Feedback

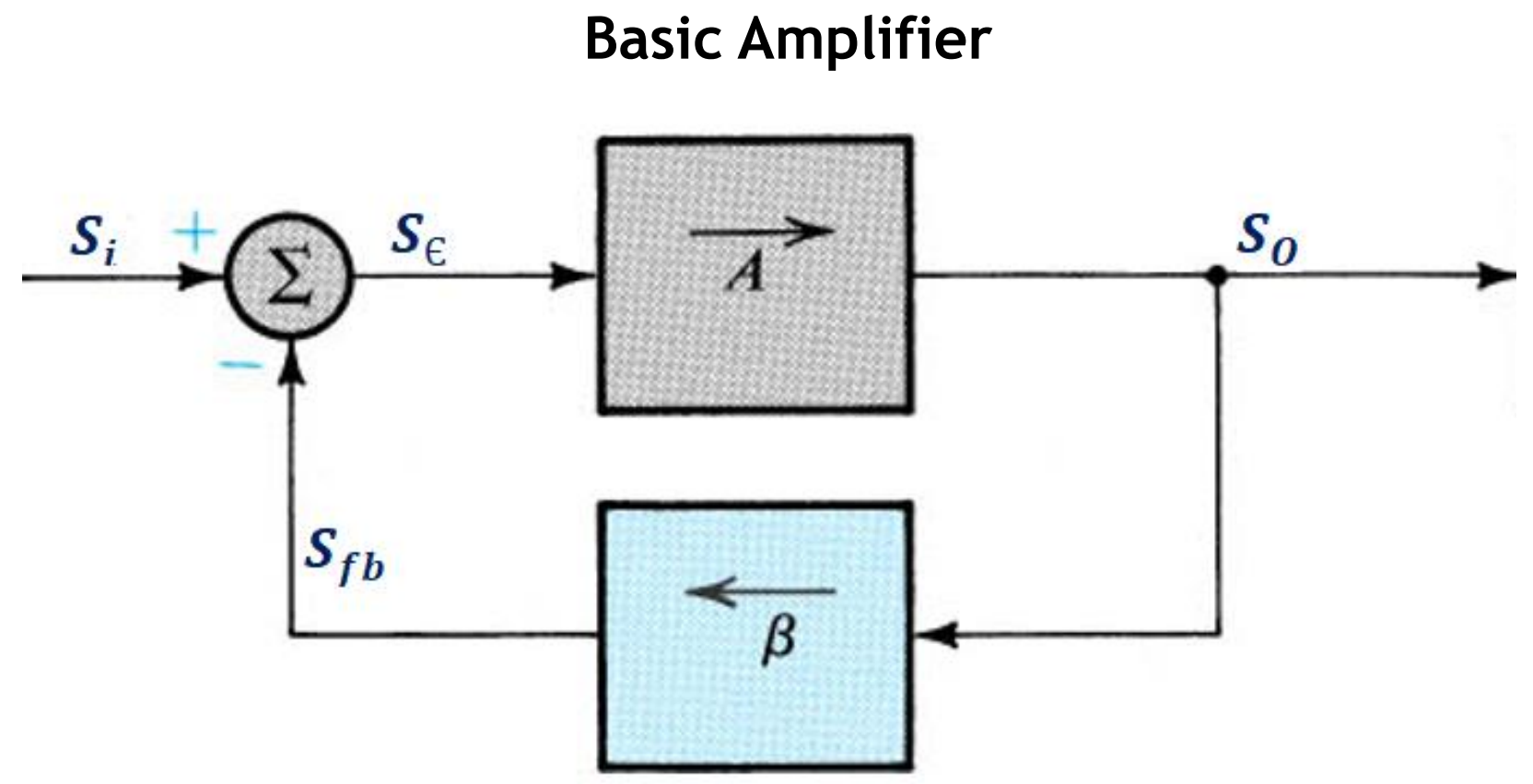

Change in A  $\rightarrow$  change in  $Af$   
10%  $\rightarrow$  0.1%

# Negative Feedback

Increasing the Bandwidth.

At high frequency

$$A(j\omega) = \frac{A_m}{1 + \frac{j\omega}{\omega_2}}$$

$$\therefore \omega_H = \omega_2$$

With Negative Feedback

$$A_f(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)\beta}$$



$$A_f(j\omega) = \frac{A_m}{1 + A_m\beta} \cdot \frac{1}{1 + \frac{j\omega}{\omega_2(1 + A_m\beta)}}$$

$$\therefore \omega_H = \omega_2(1 + A_m\beta)$$



# The Oscillation Problem

1) At mid band

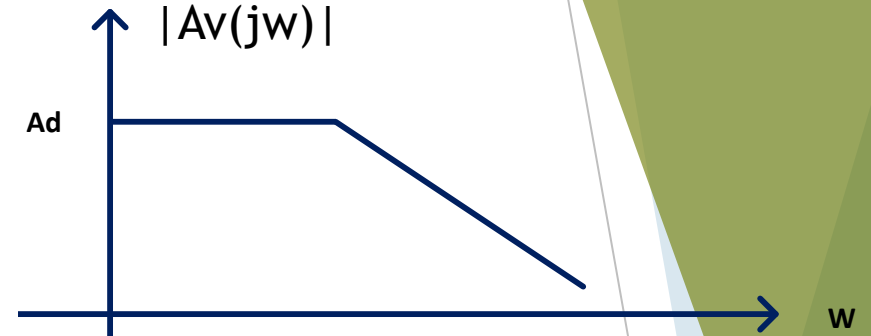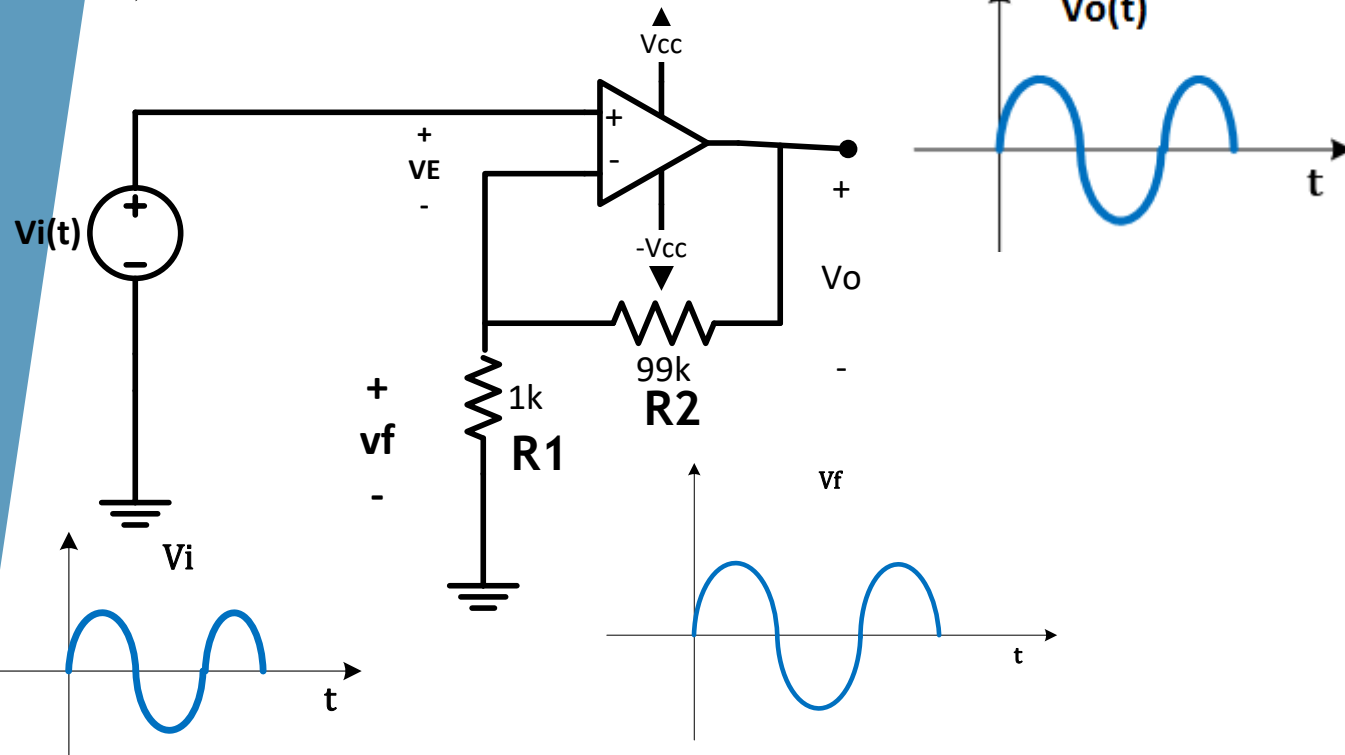

$$V_{\epsilon} = v_i - v_{fb} < v_i$$


**Negative Feedback**

$$v_{fb} = \frac{R_1}{R_1 + R_2} V_o$$


$v_{fb}$  Opposes  $v_i$

# The Oscillation Problem

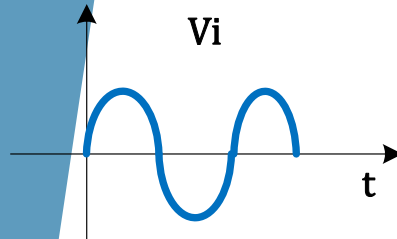2) At High-frequency (phase = 180) at  $\omega_0$




$A = -234$

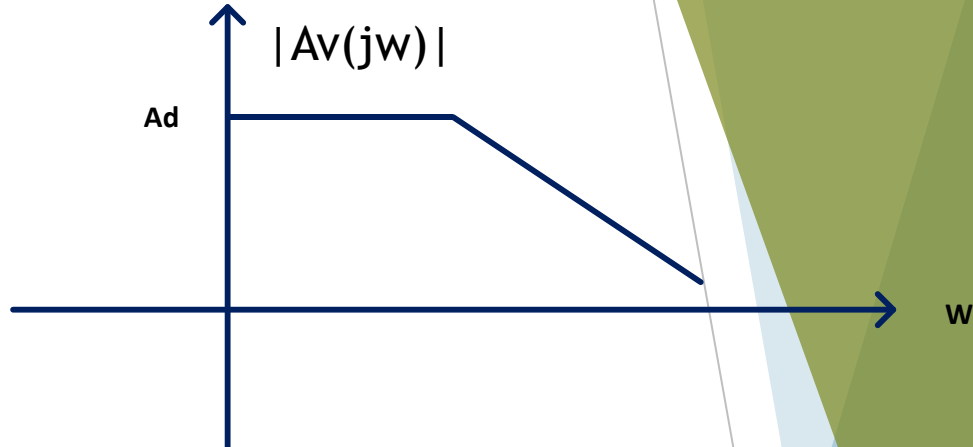

$V_{\epsilon} = v_i - v_{fb} > v_i$

**Positive Feedback**

$v_{fb}$  adds to  $v_i$

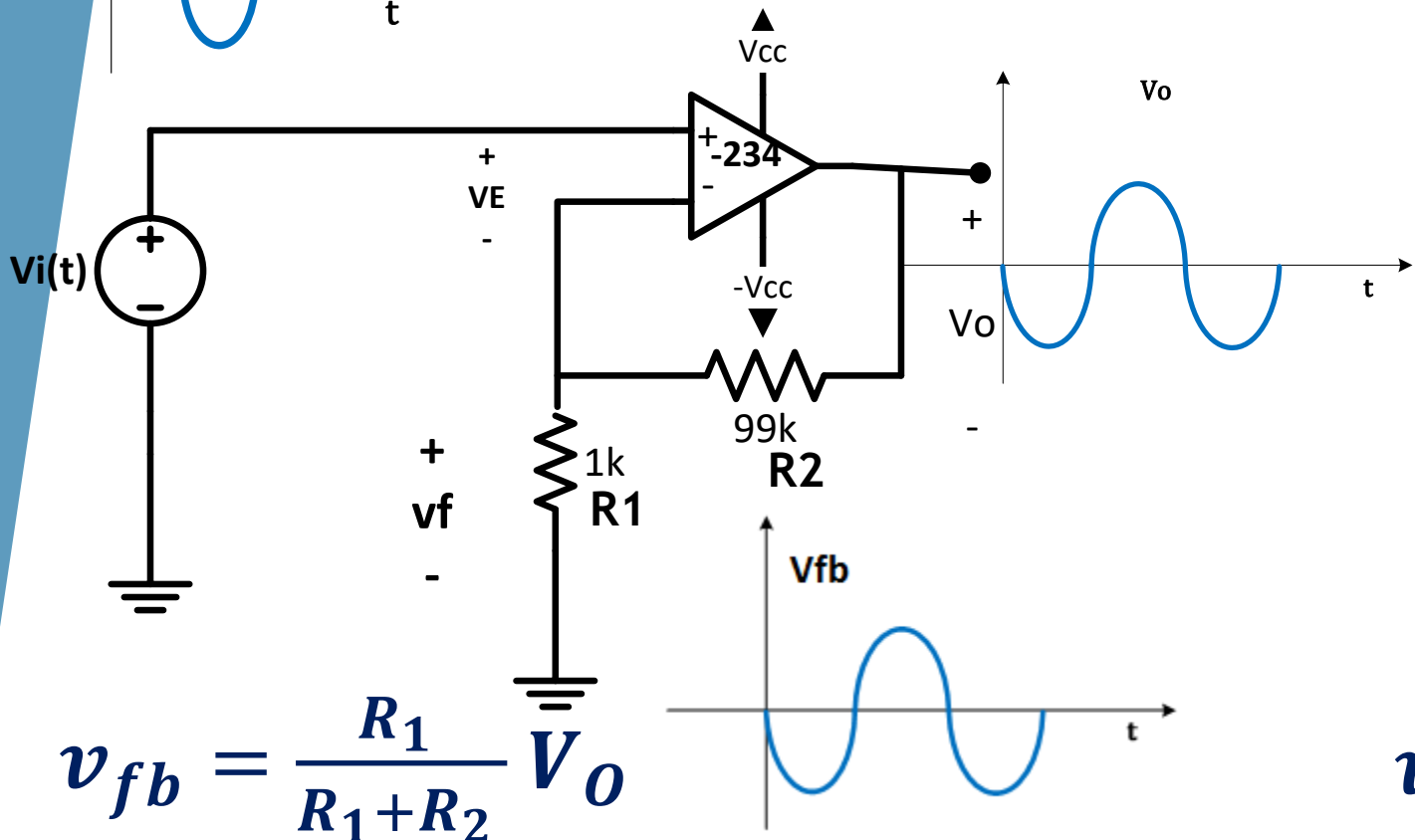

$$v_{fb} = \frac{R_1}{R_1 + R_2} V_o$$

# The Oscillation Problem


$$V_{\epsilon} = v_i - v_{fb}$$

Now let  $v_i = 0$

$$\therefore V_{\epsilon} = -v_{fb}$$

$$V_o = AV_{\epsilon}$$
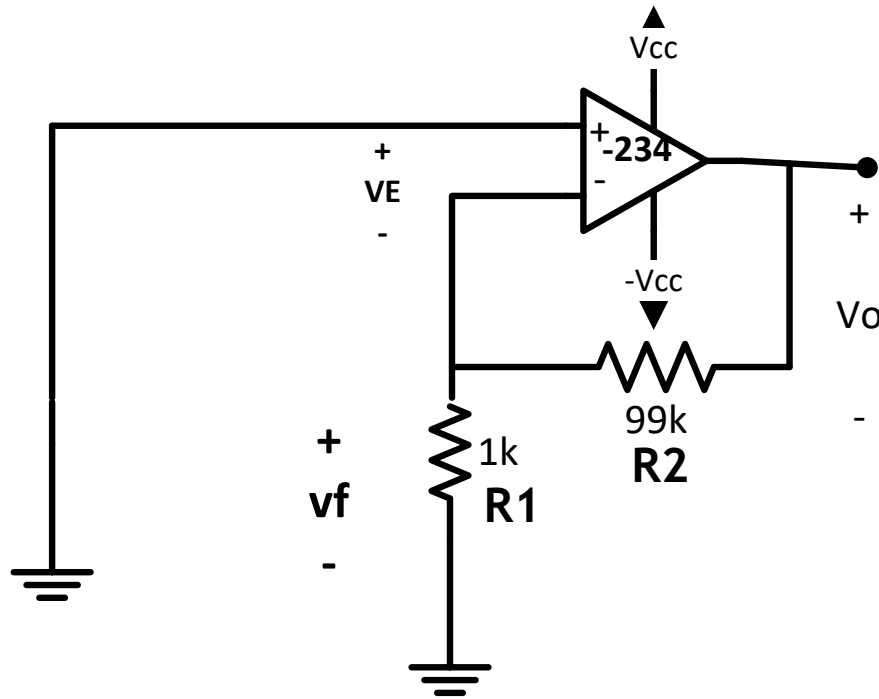
$$v_{fb} = \frac{R_1}{R_1 + R_2} V_o = \frac{1}{100} V_o$$



# The Oscillation Problem

$$A = -234$$

$$V_o = AV_{\epsilon}$$

$$v_{fb} = \frac{R_1}{R_1 + R_2} V_o = \frac{1}{100} V_o$$

1. Let  $V_{\epsilon 1} = 1\text{mV peak}$

$$V_{o1} = -234\text{mV peak}$$

$$V_{fb1} = -2.34\text{mV peak}$$



2.  $V_{\epsilon 2} = -v_{fb1} = 2.34\text{mV peak}$

$$V_{o2} = -548\text{ mV peak}$$

$$V_{fb2} = -5.48\text{ mV peak}$$

3.  $V_{\epsilon 3} = -V_{fb2} = 5.48\text{mV peak}$

$$V_{o3} = 1.282\text{V peak}$$

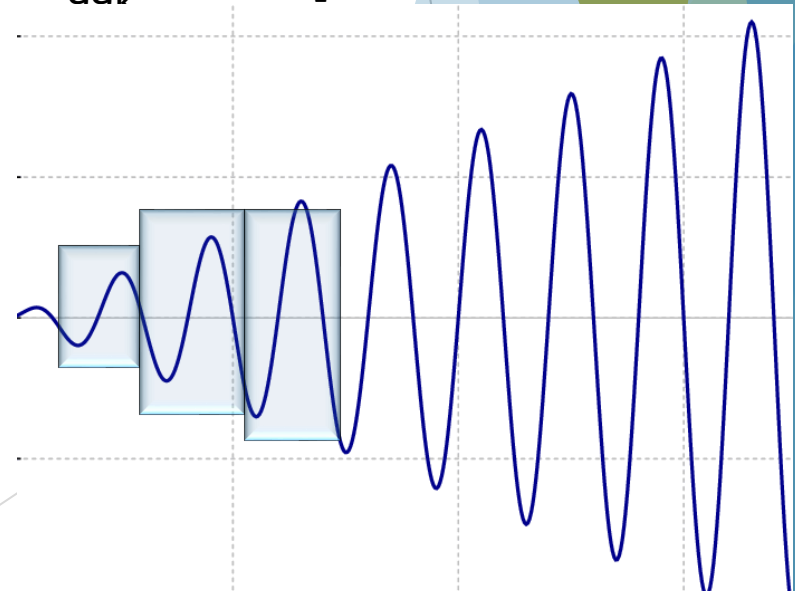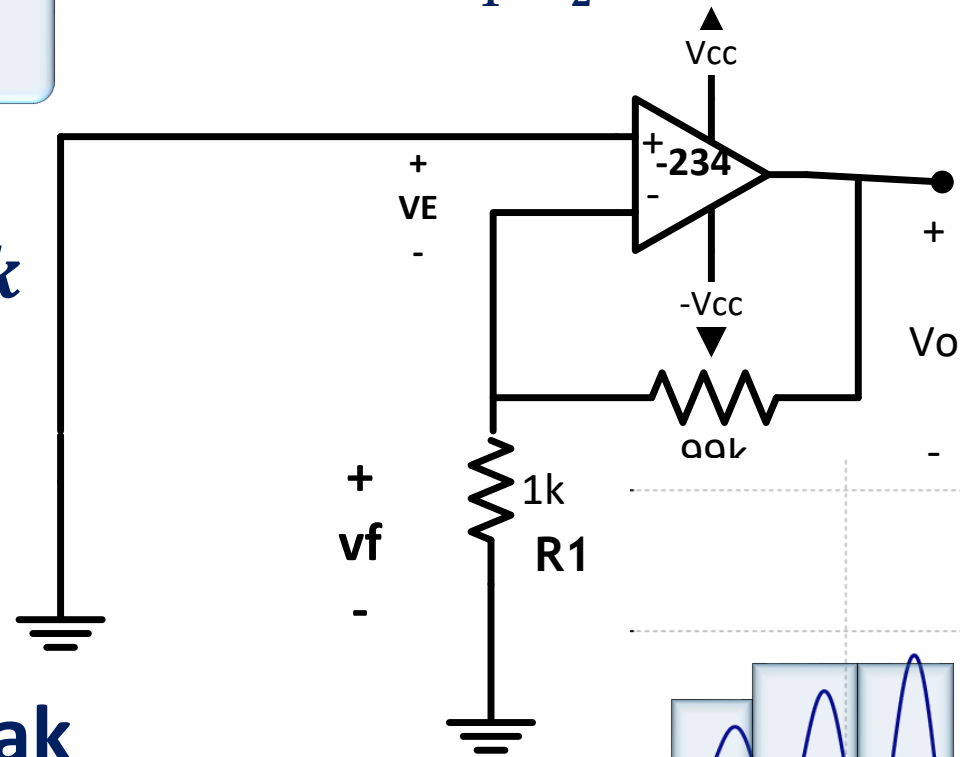

# The Oscillation Problem

$$V_{\epsilon 1} = 1\text{mV peak}$$

$$V_{fb1} = -2.34\text{mV peak}$$


**For Building up voltage**

$$|V_{fb1}| > |V_{\epsilon 1}|$$

$$|\beta V_{o1}| > |V_{\epsilon 1}|$$

$$|A\beta V_{\epsilon 1}| > |V_{\epsilon 1}|$$

$$\therefore |A\beta| > 1$$

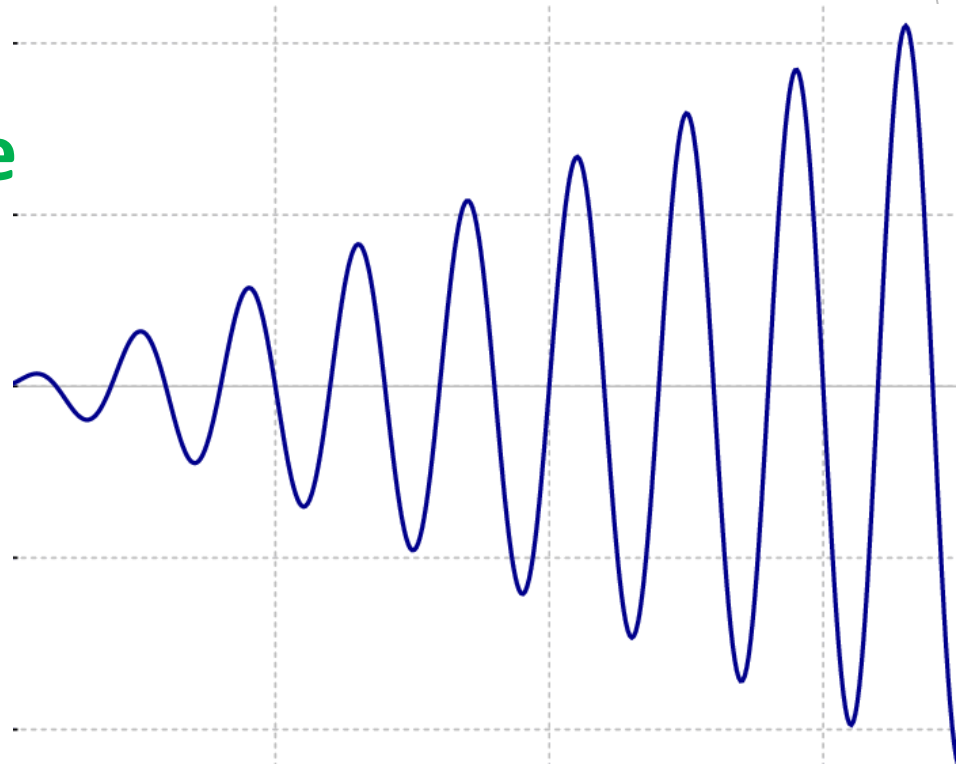

# The Oscillation Problem

1. Let  $A = -100$

$$V_{\epsilon 1} = 100 \text{ mV peak}$$

$$\therefore V_{o1} = -10V \text{ peak}$$

$$V_{fb1} = -100 \text{ mV peak}$$

2.  $V_{\epsilon 2} = -V_{fb} = 100 \text{ mV peak}$



$$V_{o2} = -10V \text{ peak}$$

$$V_{fb2} = -100 \text{ mV peak}$$

The out put signal is sustained

$$|V_{fb1}| = |V_{\epsilon 1}|$$

$$|A\beta| = 1$$

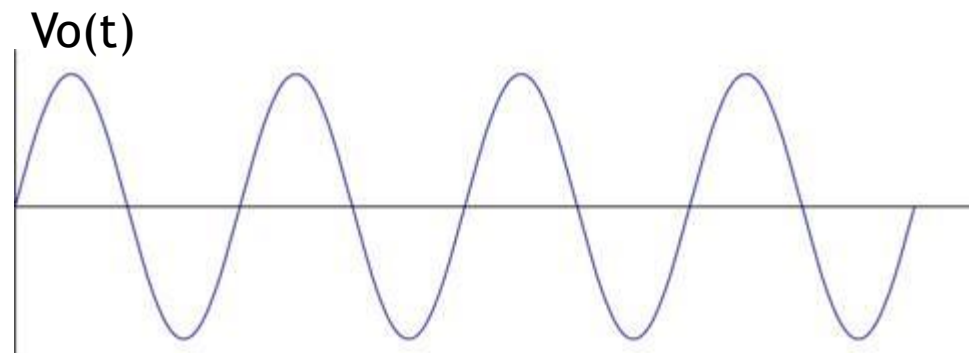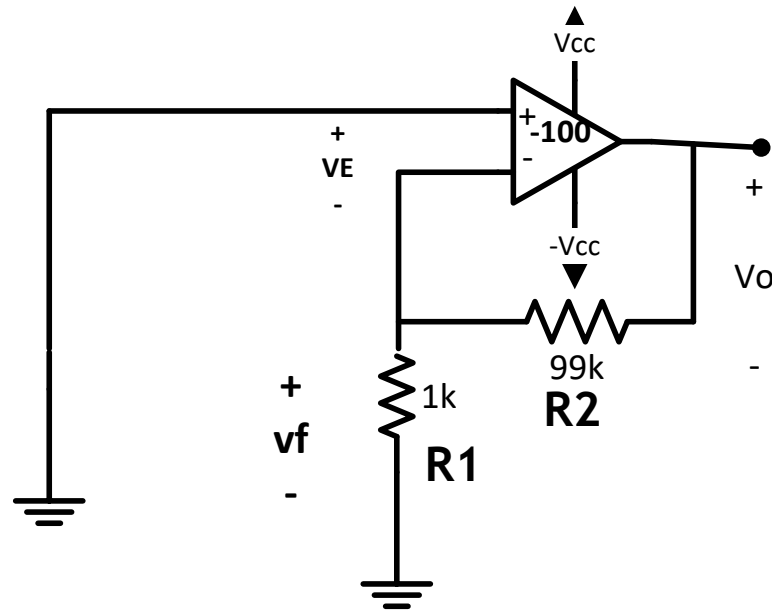

# The Oscillation Problem

Now let change  $R_2 = 299K$

$$\therefore \beta = \frac{1}{300}$$

$$A = -234$$

1.  $V_{\epsilon 1} = 1 \text{ mV peak}$



$$V_{o1} = -234 \text{ mV peak}$$

$$v_{fb1} = -0.78 \text{ mV peak}$$

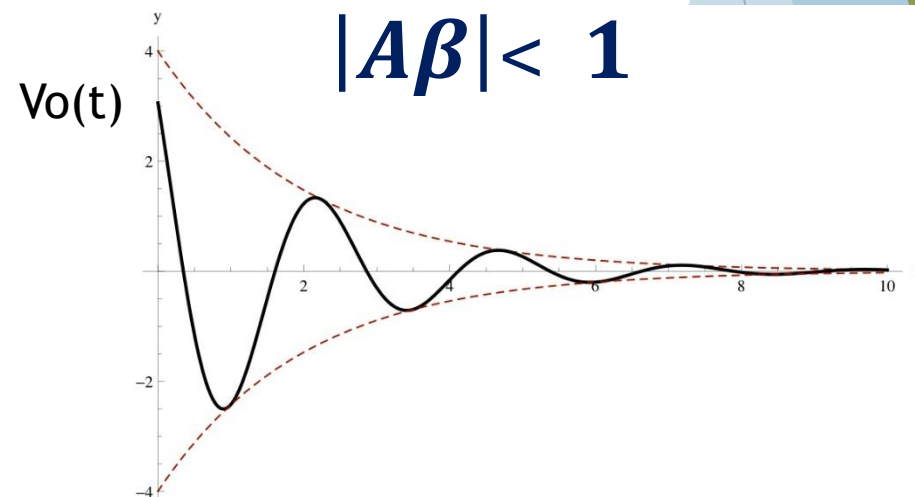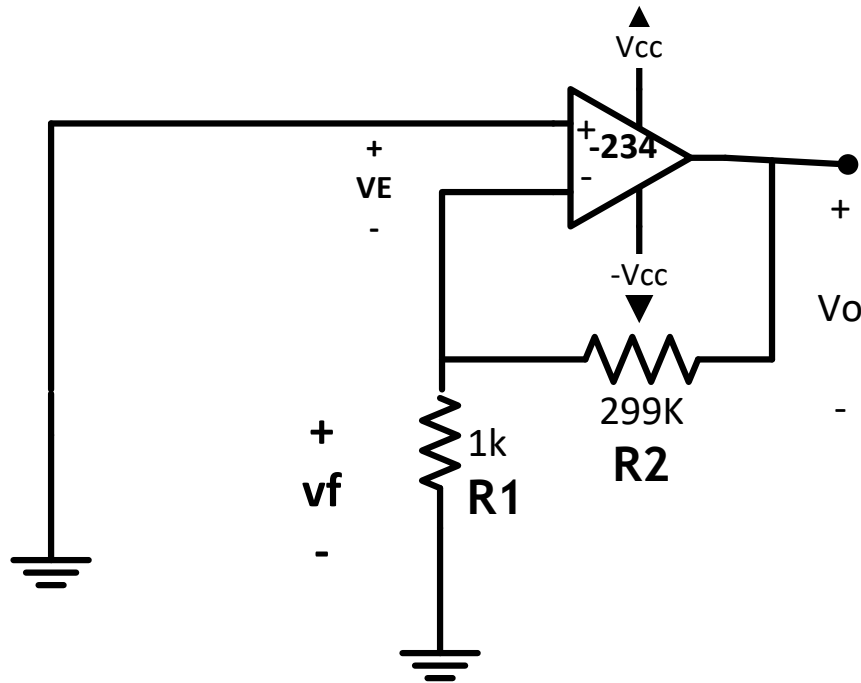
2.  $V_{\epsilon 2} = -v_{fb1} = +0.78 \text{ mV peak}$

$$V_{o2} = -182 \text{ mV peak}$$

$\therefore V_{\epsilon}, V_o, v_{fb}$  are decreasing down



# The Oscillation Problem

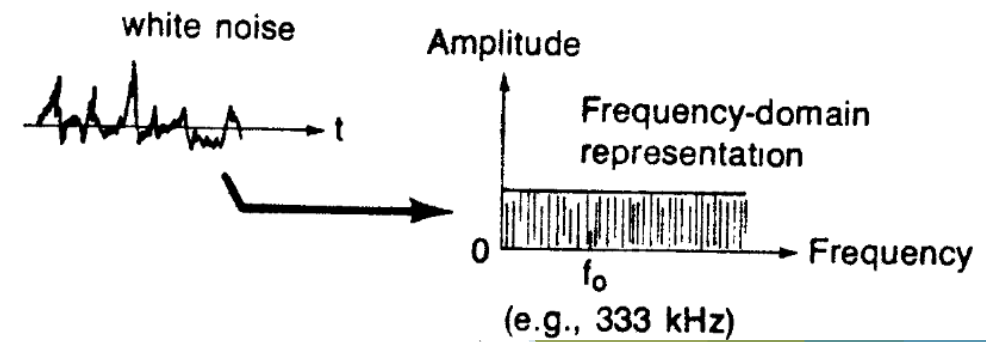

## White noise

- All active and passive devices will generate small levels (typically, nano volts or less ) of white noise.
- White noise are random generation of electrical signal that encompass the frequency spectrum from dc (0Hz) to extremely high (many gaga hertz frequencies).
- Thermal energy will produce a random motion in free electrons . this random electrons motion serves to produce a random current . If this random current exists in a resistor , a random (noise) voltage will be developed a cross the resistor.



