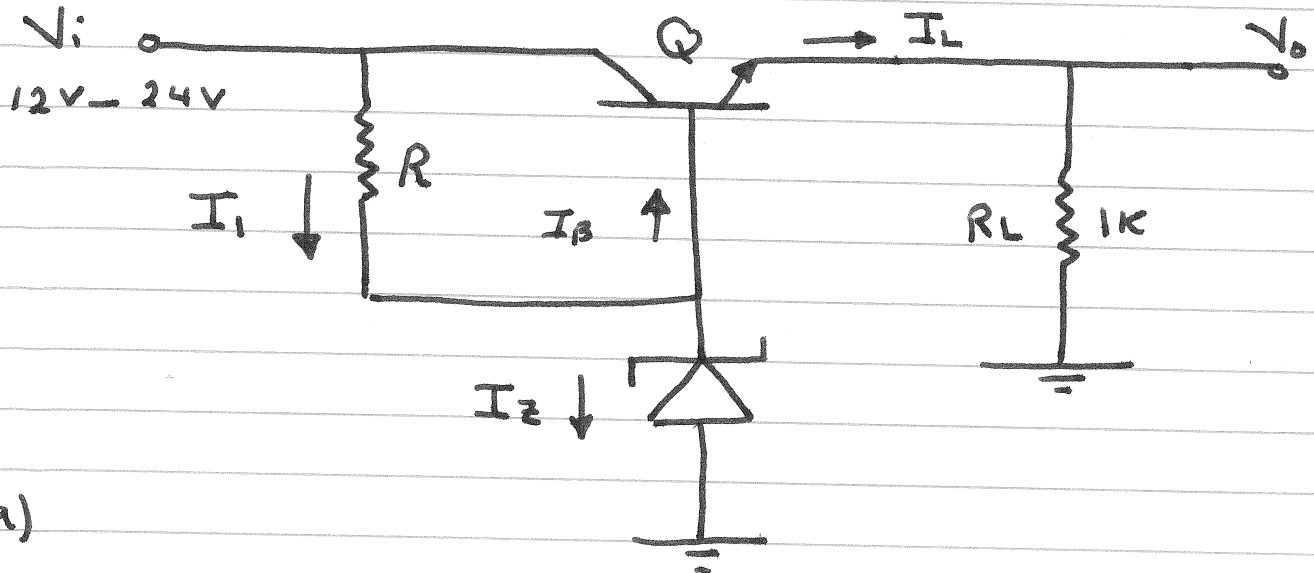


Homework Solutions Voltage Regulators EE338

Problem 1:



a)

$$V_o = V_{EB} + V_z = 9V$$

$$\therefore V_z = V_o - V_{EB} = 9 + 0.7 = 9.7V$$

$$b) I_z = I_1 - I_B \geq 10mA$$

$$I_z = \frac{V_i - V_z}{R} - \frac{I_L}{\beta + 1} \geq 10mA$$

$$\frac{V_i(\min) - V_z}{R} - \frac{V_o}{(1 + \beta)R_L} \geq 10mA$$

$$\therefore R \leq 0.228k\Omega$$

$$\therefore R_{max} = 0.228k\Omega$$

$$c) P_{D,max} = V_z I_z(\max)$$

$$I_z(\max) = I_1(\max) - I_B$$


$$I_1(\max) = \frac{V_i(\max) - V_z}{R} = 62.72 \text{ mA}$$

$$I_B = \frac{I_L}{\beta + 1} = \frac{V_o}{(\beta + 1)R_L} = 0.089 \text{ mA}$$

$$\therefore I_z(\max) = 62.63 \text{ mA}$$

$$\therefore P_{D,\max} = 607.5 \text{ mW}$$

Problem 2 :

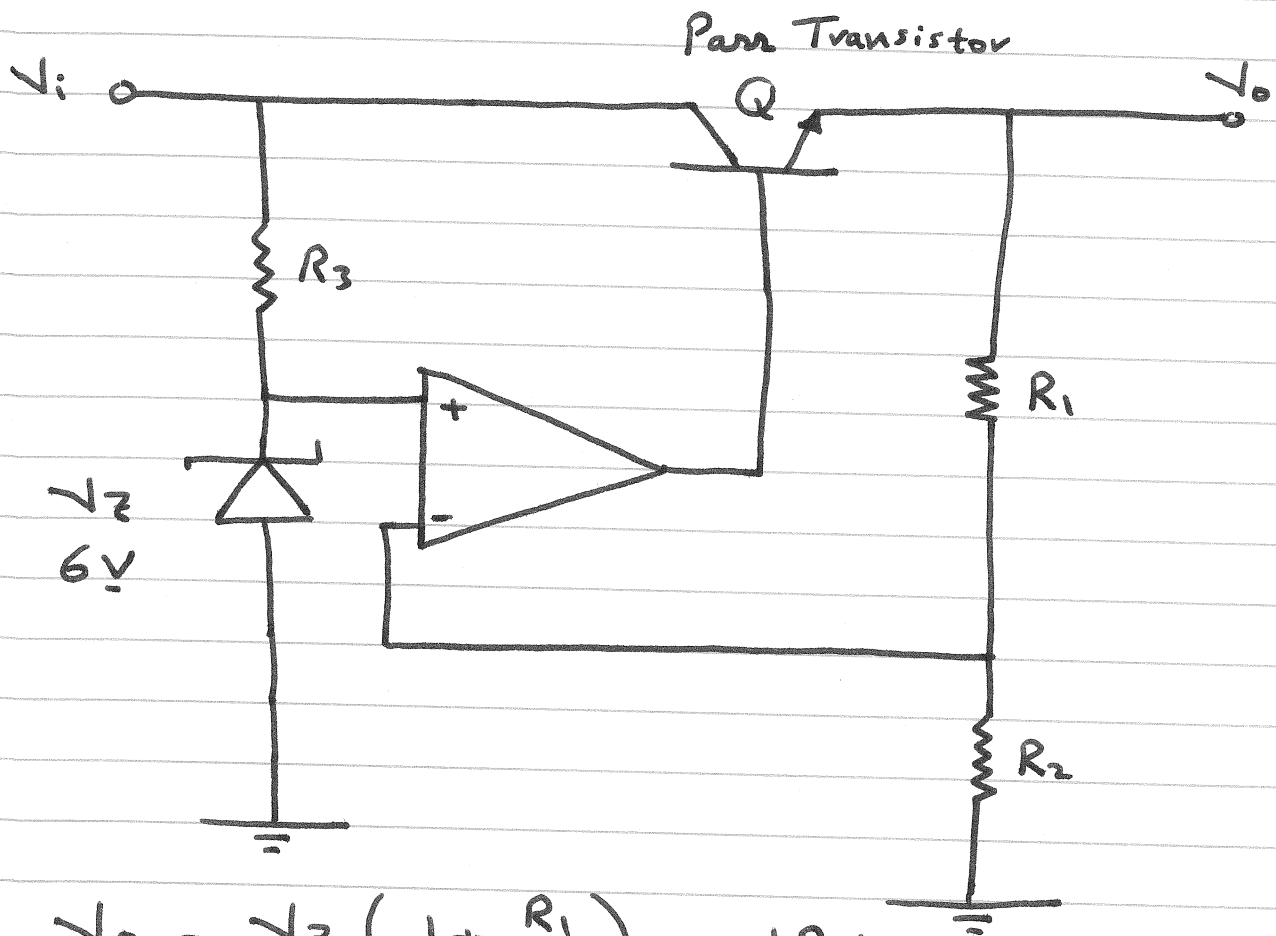

$$V_o = V_z \left(1 + \frac{R_1}{R_2} \right) = 18V$$

$$\therefore \frac{R_1}{R_2} = 2$$

$$\text{Let } R_1 = 20K, \therefore R_2 = 10K$$


$$I_z = \frac{V_i - V_z}{R_3} \geq 20mA$$

$$\therefore \frac{V_i(\min) - V_z}{R_3} \geq 20mA$$

$$\therefore R_3 \leq 0.7K$$

$$\therefore \text{Let } R_3 = 0.5K$$

Problem 3 :

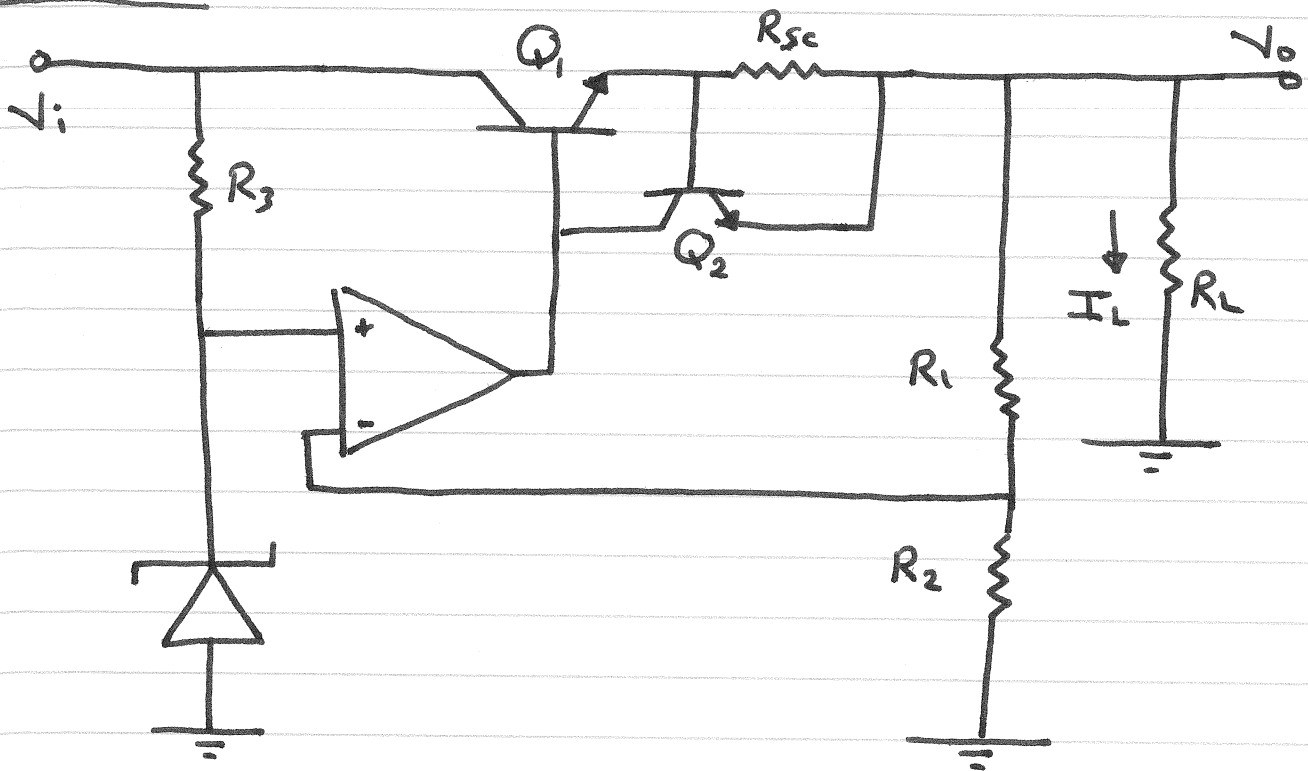

$$a) R_{sc} = \frac{0.7V}{0.5A} = 1.4 \Omega$$

$$b) \text{ When } R_L = 100 \Omega, I_L = \frac{25}{100} = 0.25A$$

$$\text{Since } I_L < I_{L,max}, \therefore V_o = 25V$$


$$c) \text{ When } R_L = 10 \Omega, I_L = \frac{25}{10} = 2.5A$$

Since $I_L > I_{L,max}$; Current Limiting

will occur

$$V_o = I_{L,max} R_L = 5V$$

Problem 4 :

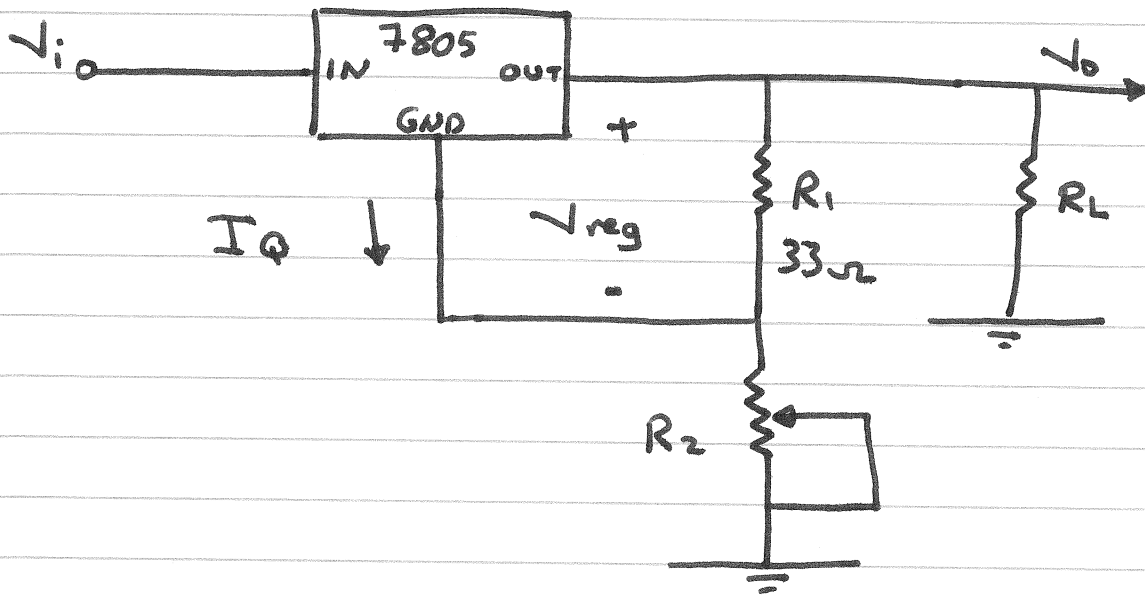

$$a) \quad V_L = V_{reg} \left(1 + \frac{R_2}{R_1} \right) + R_2 I_Q$$


$$V_L = \begin{cases} 5\text{V} & \text{when } R_2 = 0 \\ 21.15\text{V} & \text{when } R_2 = 100\ \Omega \end{cases}$$

$$21.15\text{V} \geq V_L \geq 5\text{V}$$

$$b) \quad \text{When } I_Q = 7\text{mA} \text{ and } R_2 = 100\ \Omega$$

$$V_L = 20.85\text{V}$$

Problem 5 :

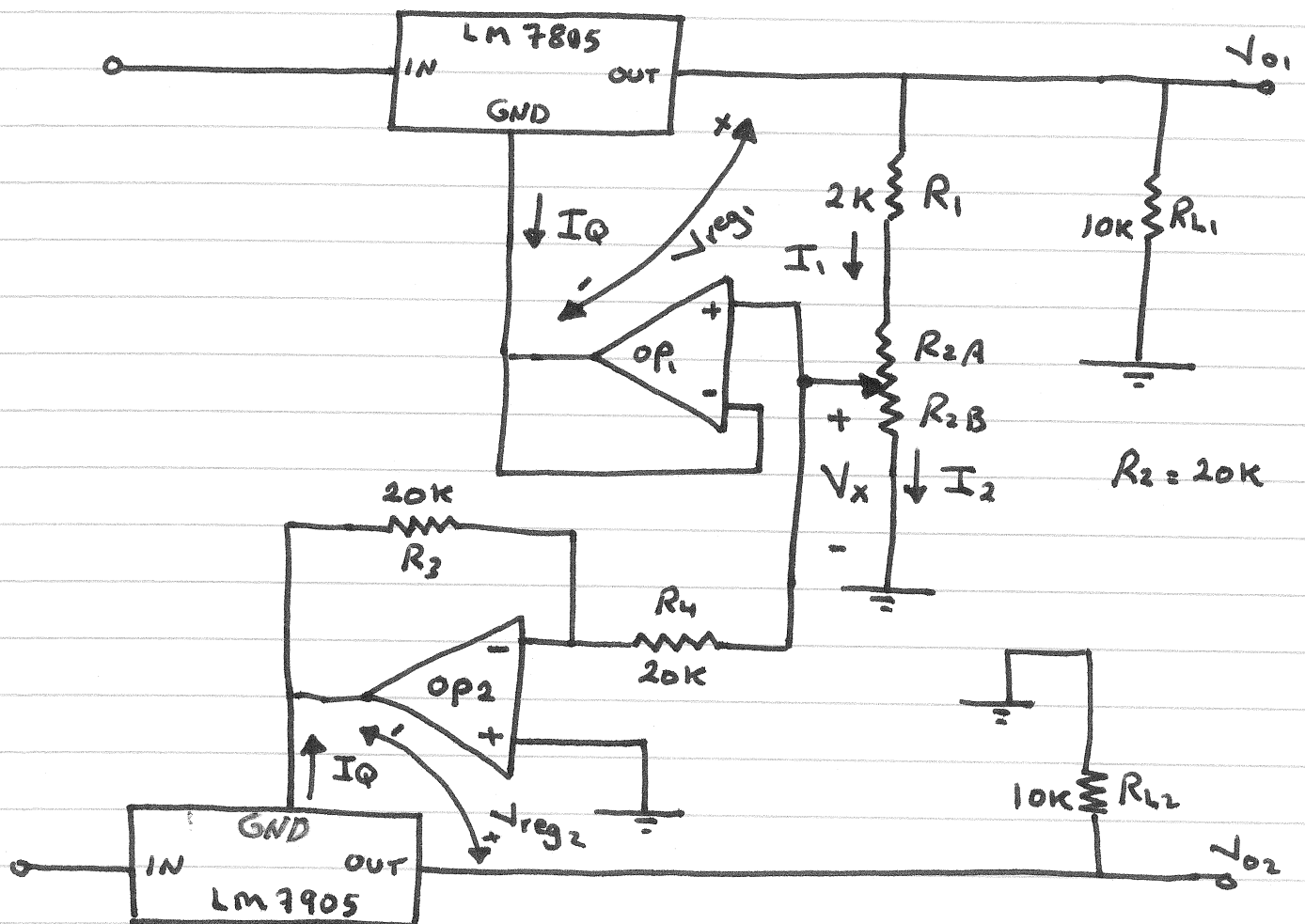

$$I_1 = \frac{V_{reg1}}{R_1 + R_{2A}}$$

$$I_2 = \frac{R_4}{R_4 + R_{2B}} I_1$$

$$V_{o1} = R_1 I_1 + R_{2A} I_1 + R_{2B} I_2$$

$$V_{o1} = V_{reg1} + R_{2B} I_2$$

$$V_{o1} = V_{reg1} + V_{reg1} \frac{R_4 \parallel R_{2B}}{R_1 + R_{2A}}$$

$$V_{o1} = V_{reg1} \left(1 + \frac{R_4 \parallel R_{2B}}{R_1 + R_{2A}} \right)$$

$$V_{o2} = V_{reg_2} + V_{op_2}$$

$$V_{o2} = V_{reg_2} - \frac{R_3}{R_4} V_x$$

$$V_x = R_{2\beta} I_2 = V_{reg_1} \frac{R_4 \parallel R_{2\beta}}{R_1 + R_{2A}}$$

$$V_{reg_1} = -V_{reg_2}$$

$$\therefore V_x = -V_{reg_2} \frac{R_4 \parallel R_{2\beta}}{R_1 + R_{2A}}$$

$$\therefore V_{o2} = V_{reg_2} \left(1 + \frac{R_4 \parallel R_{2\beta}}{R_1 + R_{2A}} \right)$$

$$V_{o1} = V_{reg_1} \left(1 + \frac{R_4 \parallel R_{2\beta}}{R_1 + R_{2A}} \right)$$

a) For $R_{2A} = R_{2\beta} = 10k$

$$V_{o1} = 7.45 \text{ V}$$

$$V_{o2} = -7.45 \text{ V}$$

b) For $R_{2A} = 0\Omega$, and $R_{2\beta} = 20k$

$$V_{o1} = 18.9 \text{ V}$$

$$V_{o2} = -18.9 \text{ V}$$

c) For $R_{2A} = 20k$, and $R_{2\beta} = 0\Omega$

$$V_{o1} = 5 \text{ V}$$

$$V_{o2} = -5 \text{ V}$$