

Analog Electronics

ENEE236


Amplifiers Frequency Response

Instructor
Nasser Ismail


Amplifier Frequency Response

- Audio frequency signals such as speech and music are combination of many different sine waves, occurring simultaneously with different amplitude and frequency in the following range (20Hz-20kHz (audible noise) , other types of signals have their own range.
- In order for the output to be an amplified version of the input, the amplifier must amplify each and every component in the signal by the same amount
- The Bandwidth must cover the entire range of frequency components if considered amplification is to be achieved

Amplifier Frequency Response

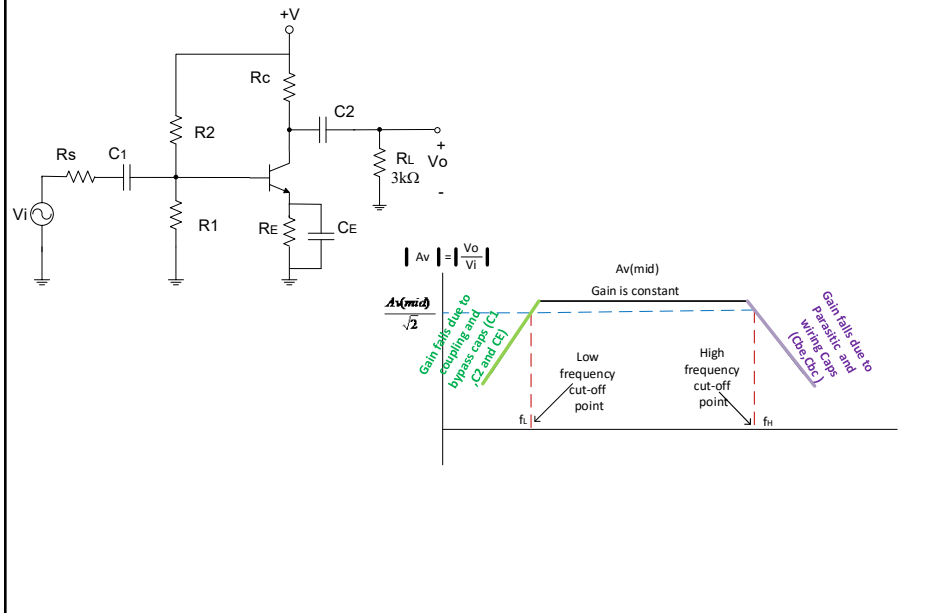

Impedance of a cap

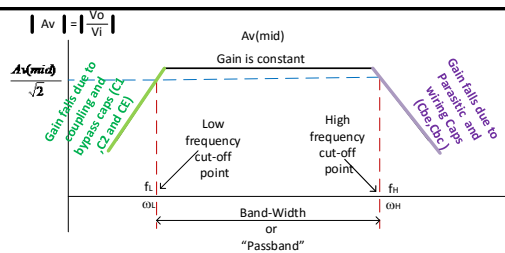

- The impedance of a cap is

$$X_c = \frac{1}{2\pi f C}$$

when $f < f_L$ the coupling caps C_1 and C_2 , and the bypass cap

C_E cannot be considered as short circuit since their impedance is not small enough

when $f > f_H$ the internal caps C_{bc} and C_{be} for a BJT (or C_{gs}

and C_{gd}), cannot be considered as open circuit since their impedance is not high enough


Corner Frequency

we define the corner (break and cut - off) frequency as :

$$|A(j\omega_L)| = \frac{Av(mid)}{\sqrt{2}}$$


$$|A(j\omega_H)| = \frac{Av(mid)}{\sqrt{2}}$$
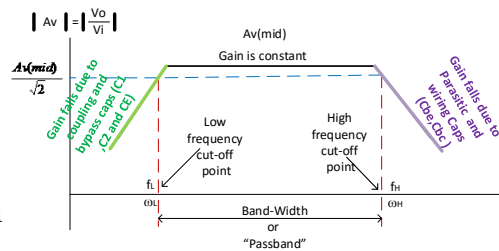
$$\omega_H - \omega_L = BW - \text{Bandwidth}$$



$$\text{Midrange} = \text{midband} \cong 10\omega_L - 0.1\omega_H$$


Corner Frequency

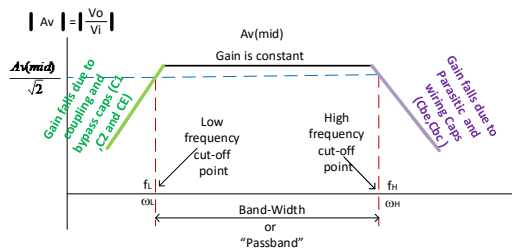

$$\text{Midrange} = \text{midband} \cong 10\omega_L - 0.1\omega_H$$

- This is the range for which the capacitors (C1, C2 and CE) are considered short circuit while the parasitic caps are considered open circuit (this is the range we have considered so far in previous chapters)

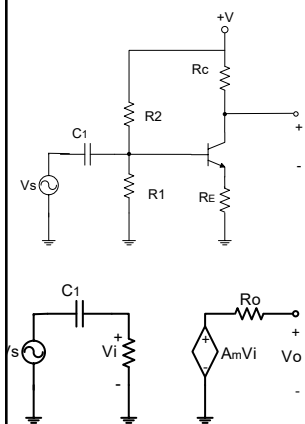Series Capacitance and low frequency response




$$V_o = A_m V_i$$

$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s \rightarrow V_o = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$\frac{V_o}{V_s} = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} = A(j\omega)$$

$$\rightarrow |A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

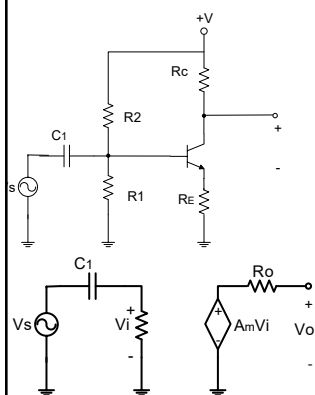Series Capacitance and low frequency response



$$|A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

$$= \frac{A_m}{\sqrt{1 + \left(\frac{\omega_{c1}}{\omega}\right)^2}}$$

where $\omega_{c1} = \frac{1}{R_i C_1}$ is the break frequency due to C_1

For $A_m = 1$

for $\omega = \omega_{c1} \rightarrow 20 \log |A(j\omega)| = 20 \log A_m - 20 \log 0.707 = -3 \text{ dB}$

for $\omega = 0.1 \omega_{c1} \rightarrow 20 \log |A(j\omega)| = -20 \log 10 = -20 \text{ dB} \leftarrow$ High pass filter

Series Capacitance and low frequency response

Note:

- 1) If there is only one cap, we find $\omega_{c1} = \frac{1}{R_{th1} \cdot C1}$ and $\omega_L = \omega_{c1}$
- 2) If there is two caps C1 and C2 with ω_{c1} and ω_{c2} , then

$$A(j\omega) = Am \left(\frac{1}{1 + \left(\frac{\omega_{c1}}{j\omega} \right)} \right) \left(\frac{1}{1 + \left(\frac{\omega_{c2}}{j\omega} \right)} \right)$$

Series Capacitance and low frequency response

in order to find ω_L , we find magnitude of the gain at ω_L

$$|A(j\omega_L)| = \frac{Am}{\sqrt{2}}$$

solving yields

$$\omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{\omega_{c1}^4 + 6\omega_{c1}^2\omega_{c2}^2 + \omega_{c2}^4}}{2}$$

Series Capacitance and low frequency response

1) let $\omega_{c1} = 616$ rad/sec and $\omega_{c2} = 17.86$ rad/sec

here $\omega_{c1} \gg \omega_{c2}$

$\omega_L = 616.5$ rad/sec

2) let $\omega_{c1} = 200$ rad/sec and $\omega_{c2} = 750$ rad/sec

here $\omega_{c2} \gg \omega_{c1}$

$\omega_L = 798$ rad/sec

$$\omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{\omega_{c1}^4 + 6\omega_{c1}^2\omega_{c2}^2 + \omega_{c2}^4}}{2}$$

In both cases and in general


if $\omega_{c1} \gg \omega_{c2}$

$\omega_{c1} < \omega_L < \omega_{c1} + \omega_{c2}$

Biggest $\omega_{c1} < \omega_L < \text{sum of all } \omega_c \text{'s}$

Low Frequency Response Example

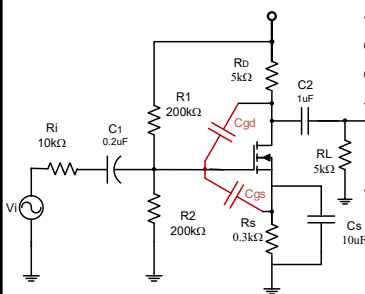
- Calculate the low frequency corner frequencies due to C1, C2, Cs and estimate ω_L ?



-low frequency ac small signal equivalent circuit is constructed (here all high frequency caps Cgs, Cgd are considered as open circuits)

- We consider one capacitor each time , while all other low frequency caps are considered short circuit and its corresponding ω is found

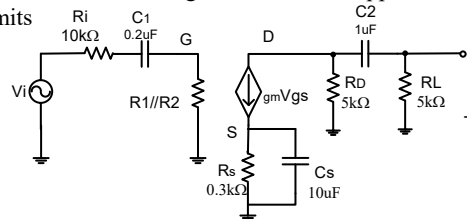- Finally, ω_L is estimated using the formula for upper and lower limits



Effect of each Capacitor at ω_L

- We Calculate the low frequency corner frequencies due to each cap acting alone while all others are considered as short circuit

1) consider C1 (while C2 and Cs are shorted)

$$\omega_{c1} = \frac{1}{C1.Rth1} = 45.45 \text{ rad/sec};$$

Rth1 is the thevenin impedance seen by C1 while all independant sources are set to zero


$$Rth1 = Ri + (R1//R2)$$

2) consider C2 (while C1 and Cs are shorted)

$$\omega_{c2} = \frac{1}{C2.Rth2} = 100 \text{ rad/sec};$$

Rth1 is the thevenin impedance seen by C1

$$Rth2 = R_D + R_L$$

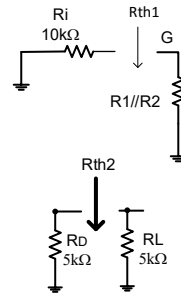

Effect of each Capacitor & ω_L

- We Calculate the low frequency corner frequencies due to cap acting alone while all others are considered as short circuit

3) consider Cs (while C1 and C2 are shorted)

$$\omega_{c3} = \frac{1}{Cs.Rth3} = 1050 \text{ rad/sec};$$



Rth3 is the thevenin impedance seen by Cs

remember $r_{ds} = \infty$

$$Rth3 = R_s // \frac{1}{gm}$$

4) estimation of the ω_L

$$1050 < \omega_L < 1195.5$$

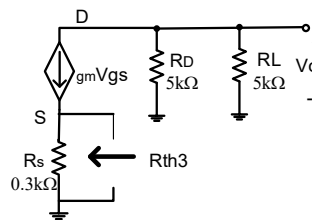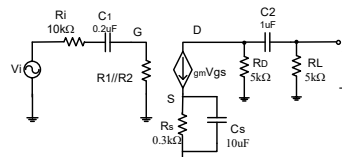

Design of ω_L

- Previous method explained how to estimate value of ω_L in an analysis problem where all capacitor values are given, but what happens if it was desired to design an amplifier with certain ω_L and the task was to find capacitor values ?
- Design criteria to be used is:

$$\omega_{CE} = (0.7 - 0.8)\omega_L$$

$$\omega_{C1} = \omega_{C2} = (0.1 - 0.15)\omega_L$$

C_1, C_2 are input and output coupling capacitors

C_E is bypass capacitor // to R_E emitter stabilizing resistor or R_s source resistor

make sure that $\omega_{CE} + \omega_{C1} + \omega_{C3} = \omega_L$

Shunt Capacitance and High frequency response


$$V_o = A_m V_i$$

$$V_i = \frac{R_i // \frac{1}{j\omega C_A}}{\left(R_i // \frac{1}{j\omega C_A}\right) + R_s} V_s \rightarrow \frac{V_o}{V_s} = A(j\omega)$$

$$A(j\omega) = A_m \frac{R_i // \frac{1}{j\omega C_A}}{\left(R_i // \frac{1}{j\omega C_A}\right) + R_s}$$

$$= A_m \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{1}{1 + j\omega C_A (R_s // R_i)} \right)$$

$$\rightarrow |A(j\omega)| = A_m \frac{R_i}{R_i + R_s} \cdot \frac{1}{\sqrt{1 + [\omega C_A (R_s // R_i)]^2}}$$

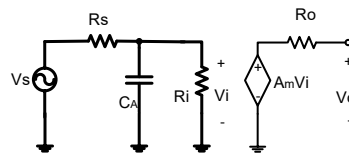

$$\rightarrow |A(j\omega)| = A_v(\text{mid}) \frac{1}{\sqrt{1 + [\omega C_A (R_s // R_i)]^2}}$$


$$\rightarrow |A(j\omega)| = A_v(\text{mid}) \frac{1}{\sqrt{1 + \left[\frac{\omega}{\omega_{c_A}}\right]^2}}$$

$$\rightarrow \text{at } \omega = \omega_H = \omega_{c_A}$$

$$\therefore |A(j\omega_H)| = A_v(\text{mid}) \frac{1}{\sqrt{2}}$$

$$\rightarrow \omega_H C_A (R_s // R_i) = 1$$

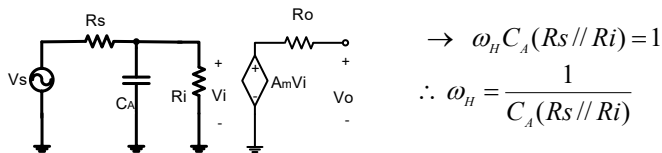
Shunt Capacitance and High frequency response



$$\rightarrow \omega_H C_A (R_s // R_i) = 1$$


$$\therefore \omega_H = \frac{1}{C_A (R_s // R_i)}$$

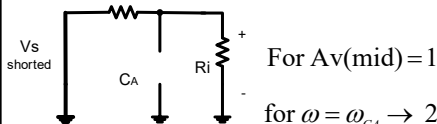where R_{th_A} is thevenin impedance seen by capacitor C_A




For $A_v(\text{mid}) = 1$

for $\omega = \omega_{CA} \rightarrow 20 \log |A(j\omega)| = 20 \log A_v(\text{mid}) - 20 \log 0.707 = -3 \text{ dB}$

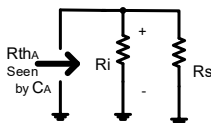

for $\omega = 10\omega_{CA} \rightarrow 20 \log |A(j\omega)| = -20 \log 10 = -20 \text{ dB} \leftarrow \text{low pass filter}$

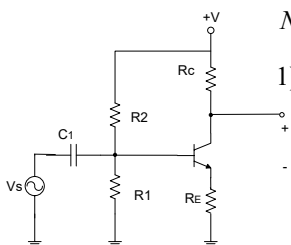Shunt Capacitance and High frequency response



Note:

1) If there is only one cap, we find $\omega_{CA} = \frac{1}{R_{thA} C_1}$ and $\omega_H = \omega_{CA}$

2) If there is two caps C_A and C_B with ω_{CA} and ω_{CB} , then

$$A(j\omega) = A_v(\text{mid}) \frac{1}{1 + \left(\frac{j\omega}{\omega_{CA}}\right)} \frac{1}{1 + \left(\frac{j\omega}{\omega_{CB}}\right)}$$

in order to find ω_H , we find magnitude of the gain at ω_H

$$|A(j\omega_H)| = \frac{A_v(\text{mid})}{\sqrt{2}} = \frac{A_v(\text{mid})}{\left[1 + \left(\frac{j\omega}{\omega_{CA}}\right)\right] \left[1 + \left(\frac{j\omega}{\omega_{CB}}\right)\right]}$$

Shunt Capacitance and High frequency response

By solving for the magnitude of the gain $A(j\omega)$ at $\omega = \omega_H$
yields for an approximation for the lower and upper limit to estimate ω_H
for $\omega_{CA} \gg \omega_{CB}$


$$\longrightarrow \frac{1}{\frac{1}{\omega_{CA}} + \frac{1}{\omega_{CB}}} < \omega_H < \omega_{CB}$$

$$\frac{\omega_{CA} \cdot \omega_{CB}}{\omega_{CA} + \omega_{CB}} < \omega_H < \omega_{CB}$$

lower limit $< \omega_H < \text{Smallest } \omega$

High Frequency Response Example

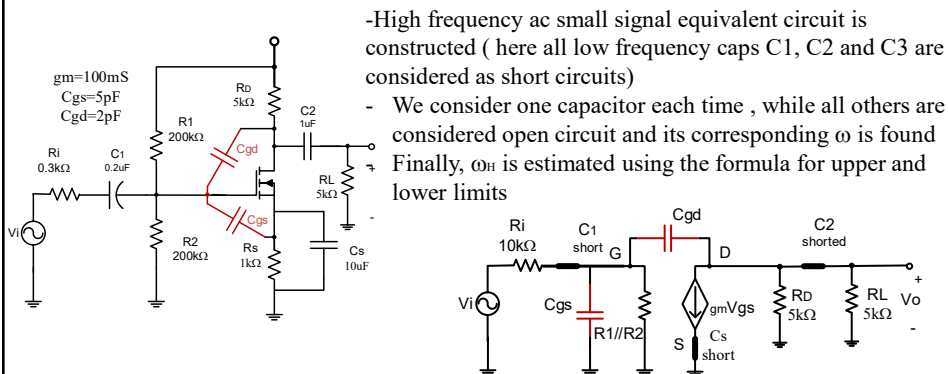- Calculate the high frequency corner frequencies due to C_{gs}, C_{gd} and estimate ω_H ?



Effect of each Capacitor & ω_H

- We Calculate the high frequency corner frequencies due to each high frequency cap acting alone while all others are considered as open circuit


1) Consider C_{gs} (while C_{gs} is open , C_1, C_2 & C_s are shorted)

$$\omega_{C_{gs}} = \frac{1}{C_{gs}.R_{gs}}$$

R_{gs} is the thevenin impedance seen by C_{gs}

$$R_{gs} = R_1 // R_2 // R_i$$

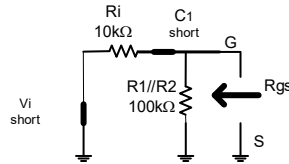
$$\omega_{C_{gs}} = 668.45 \text{ Mrad/sec;}$$



Effect of each Capacitor & ω_H


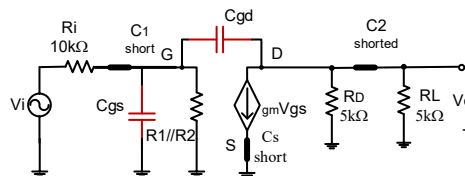
2) Consider C_{gd} (while C_{gs} is open , C_1, C_2 & C_s are shorted)

$$\omega_{C_{gd}} = \frac{1}{C_{gd}.R_{gd}}$$



Effect of Capacitor Cgd

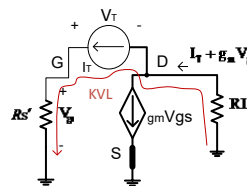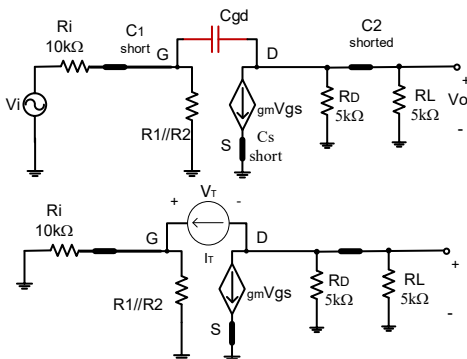- Calculation of Rgd is done through test current /voltage method



KVL :

$$RL'(I_T + g_m V_{gs}) + I_T R_{s'} = V_T$$

$$\text{but } V_{gs} = V_g - V_s = R_{s'} I_T$$

substituting yeilds

$$RL'(I_T + g_m R_{s'} I_T) + I_T R_{s'} = V_T$$

$$R_{gd} = \frac{V_T}{I_T} = RL' + R_{s'} + g_m RL' R_{s'}$$

$$RL' = R_D // R_L \text{ and } R_{s'} = R_i // R_1 // R_2$$

Effect of each Capacitor & ω_H

Now

$$\omega_{C_{gd}} = \frac{1}{C_{gd} \cdot R_{gd}} = 48.54 \text{ Mrad/sec;}$$





3) Estimation of the ω_H

$$\frac{(\omega_{gd} \cdot \omega_{gs})}{(\omega_{gd} + \omega_{gs})} < \omega_H < 48.45$$

$$45.25 < \omega_H < 48.45$$

Effect of each Capacitor & ω_H

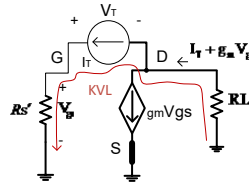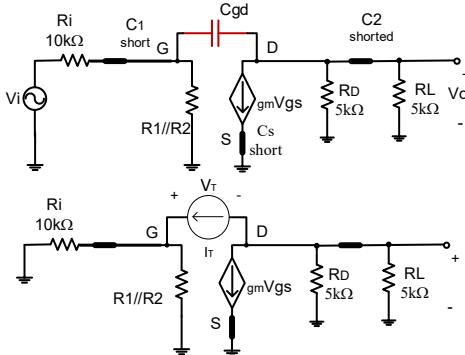- Calculation of R_{gd} is done through
- test current /voltage method



$$\text{KVL : } RL'(I_T + g_m V_{gs}) + I_T R_s' = V_T$$

$$\text{but } V_{gs} = V_g - V_s = R_s' I_T$$

substituting yields


$$RL'(I_T + g_m R_s' I_T) + I_T R_s' = V_T$$

$$R_{gd} = \frac{V_T}{I_T} = RL' + R_s' + g_m RL' R_s'$$

$$RL' = R_D // R_L \quad \text{and} \quad R_s' = R_i // R_1 // R_2$$

BJT High Frequency Response

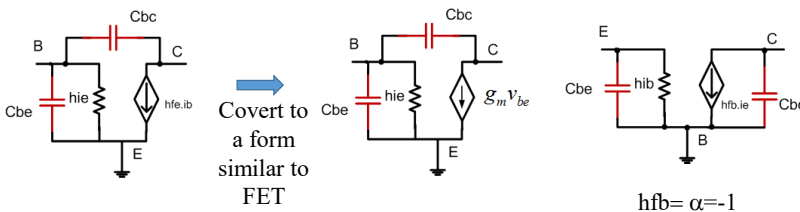- Capacitors C_{be} and C_{bc}
- CE and CC model



CB model

$$h_{fb} = \alpha = -1$$

$$h_{fe} i_b = h_{fe} \frac{v_{be}}{h_{ie}} = g_m v_{be}$$

where

$$\frac{h_{fe}}{h_{ie}} = g_m$$

CE Example:


- Estimate the high corner frequency for the following BJT amplifier

1) Effect of Cbe (Cbc is considered open) High Frequency Small Signal equivalent Circuit

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{be}}$$

where R_{be} is the thevenin impedance seen by C_{be}

$$R_{be} = ((Ri // Rth) + rb) // hie$$


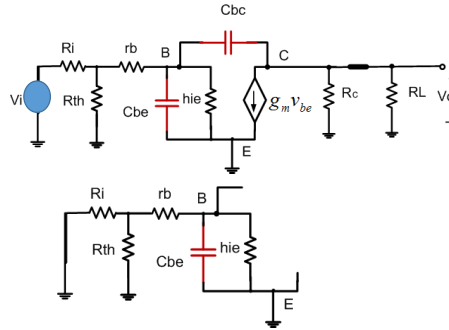


CE Example:

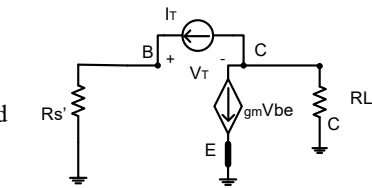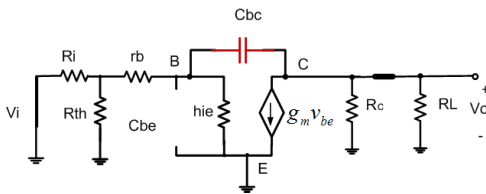2) Effect of Cbc (Cbe is considered open)

$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}}$$

where R_{bc} is the thevenin impedance seen by C_{bc} and it is found by V_T/I_T method



$$RL'(I_T + g_m V_{bc}) + I_T R_s' = V_T$$

$$\text{but } V_{bc} = V_b - V_c = R_s' I_T$$

substituting yields

$$RL'(I_T + g_m R_s' I_T) + I_T R_s' = V_T$$

$$R_{bc} = \frac{V_T}{I_T} = RL' + R_s' + g_m RL' R_s'$$

$$R_s' = (Ri // Rth + rb) // hie$$

CE Example:

- Given the following values in previous example

$$g_m = 33.5 \text{ mS}$$

$$h_{ie} = 8.77 \text{ k}\Omega$$

$$h_{fe} = 294$$

$$R_s = 1 \text{ k}\Omega, R_1 // R_2 = 16.67 \text{ k}\Omega$$

$$r_b = 20 \Omega; C_{bc} = 1.8 \text{ pF}; C_{be} = 17.25 \text{ pF}$$

$$R_c = 5 \text{ k}\Omega; R_L = 2 \text{ k}\Omega$$

calculate :

$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}} = 66.7 \text{ Mrad/sec}$$

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{bc}} = 12.67 \text{ Mrad/sec}$$


Estimate ω_H

$$\frac{(\omega_{be} \cdot \omega_{bc})}{(\omega_{be} + \omega_{bc})} < \omega_H < \omega_{be}$$

$$10.65 < \omega_H < 12.67$$

Miller Theorem (another method to solve previous example)

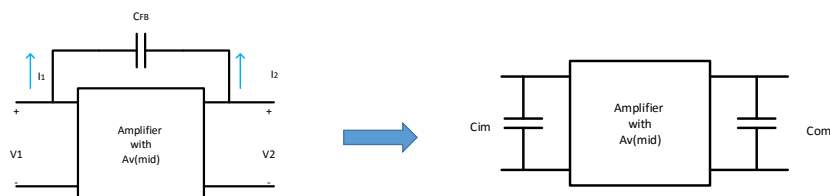- Miller theorem is used to simplify the analysis of inverting amplifiers only at high frequencies
- The feedback capacitor C_{bc} or C_{gd} is decomposed into two capacitors, one at the input C_{im} and one at the output C_{om} , whose values are found using the following formulas:



Input Miller Capacitance

$$C_{IM} = C_{FB} \left[1 - A_v(\text{mid}) \right]$$

Output Miller Capacitance

$$C_{OM} = C_{FB} \left[1 - \frac{1}{A_v(\text{mid})} \right]$$

CE Example using Miller Theorem:

- Estimate the high corner frequency for the following BJT amplifier using miller theorem

- Calculate $A_v(\text{mid}) = \frac{V_y}{V_x}$

- Calculate $C_{IM} = C_{FB} [1 - A_v(\text{mid})]$


$C_{FB} = C_{BC}$

- Calculate $C_{OM} = C_{FB} \left[1 + \frac{1}{A_v(\text{mid})} \right]$

- Calculate $\omega_{IM} = \frac{1}{(C_{IM} + C_{be})R_{be}}$

- Calculate $\omega_{OM} = \frac{1}{C_{OM}R_{ce}}$

- Estimate ω_L

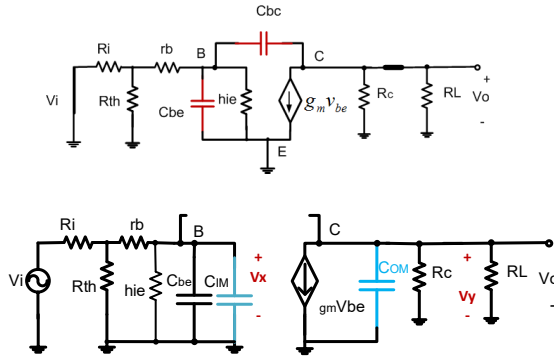

CB Example :

- Estimate the high corner frequency ω_H for the following BJT amplifier

1) Effect of C_{be} (C_{bc} is considered open)

$\omega_{be} = \frac{1}{C_{be} \cdot R_{be}}$; where R_{be} is the thevenin


impedance seen by C_{be}

$R_{be} = ((R_s // R_E)) // h_{ib}$

2) Effect of C_{bc}

$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}}$;

where $R_{bc} = R_L // R_C$

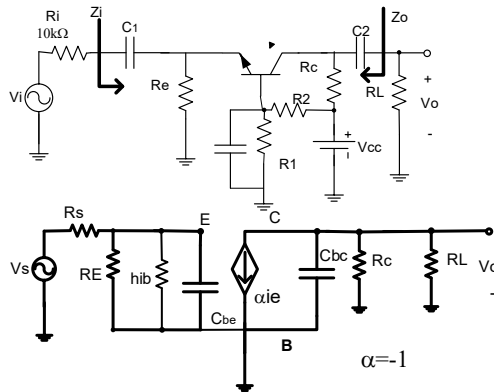

Homework : Amplifier Frequency Response

- Estimate the value of **low** and **high** frequency corner frequencies and calculate the mid-range voltage gain of the following amplifier

Important

