



Electrical and Computer Engineering Department

Power Electronics-ENEE 3305

An Assignment on Power Supply Design Using Rectifiers and Voltage Regulators

Fall 2017

Student's name: Anas Abdelhalim Tomaizeh

Student's number: 1152325

Assign. #2

Dc Power Supply

Dr. M. Adu-Khaizaran




Abstract:

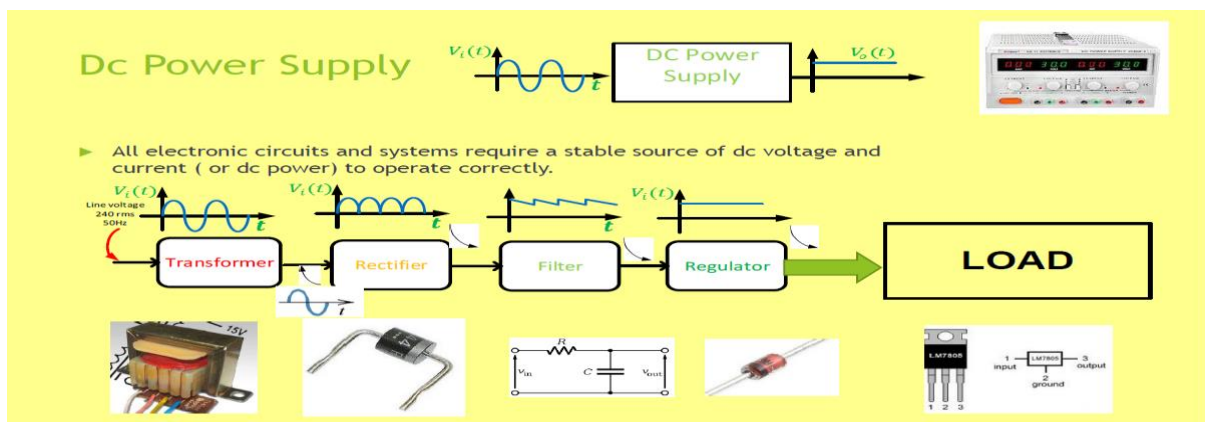- **1) The aim of this assignment** is to design a three phase full wave rectifier to convert the Ac voltage(380VRMS) to the DC voltage(12 Volt and 15A) and is connected to the regulator via a step down transformer.
 - 2) To show the design steps of the step-down transformer, the capacitor at the input of the linear regulator, and the linear regulator.
 - 3) Show the Orcad circuit and its simulations.
- The methods used: in this assignment we use orcad simulation.

➤ Theory:

- A group of circuits that convert the supply standard ac voltage (220 V, 50 Hz) provided by the wall outlet to constant dc voltage



Calculation:

from the question: $V_1=12V$ and $I_1=15A \gg \gg$ so, $R_1 = \frac{12}{15} = 0.8$

Assume $\Delta V=20V$

$$\triangleright \Delta V = \frac{I}{C \cdot 6 \cdot f}$$

$$20 = \frac{15}{C \cdot 6 \cdot 50}$$

$$\text{So, } C = 2500\mu$$

$$\triangleright V_m = \frac{\Delta V}{2} + 16 = 26V$$

To find the turns ratio:

$$\frac{310}{26} = 12$$

$$\triangleright V_o = \left(1 + \frac{R_2}{R_1}\right) \cdot V_z$$

Assume $V_z=6V$ olt.

$$\gg 12 = 6 + 6 \frac{R_2}{R_1}$$

$$R_2 = R_1 \gg = R$$


Hence, assume $R=100K$.

\triangleright the attenuation ripple:


$$\triangleright 65 = 20 \log(\Delta V_{in} / \Delta V_o)$$

$$\triangleright 65 = 20 \log(20 / \Delta V_o)$$

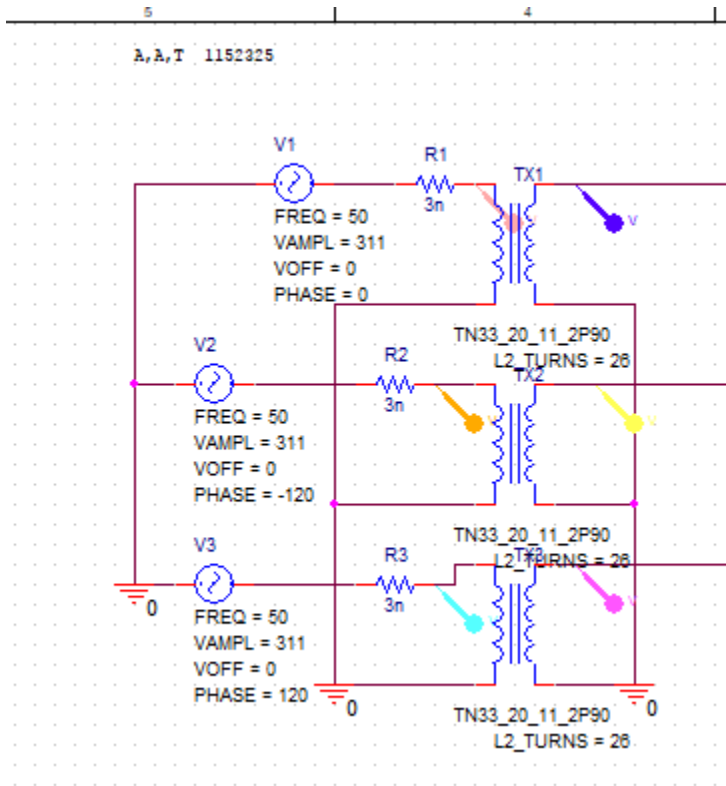
Stage one the input and output voltages from the transformer:



The result:

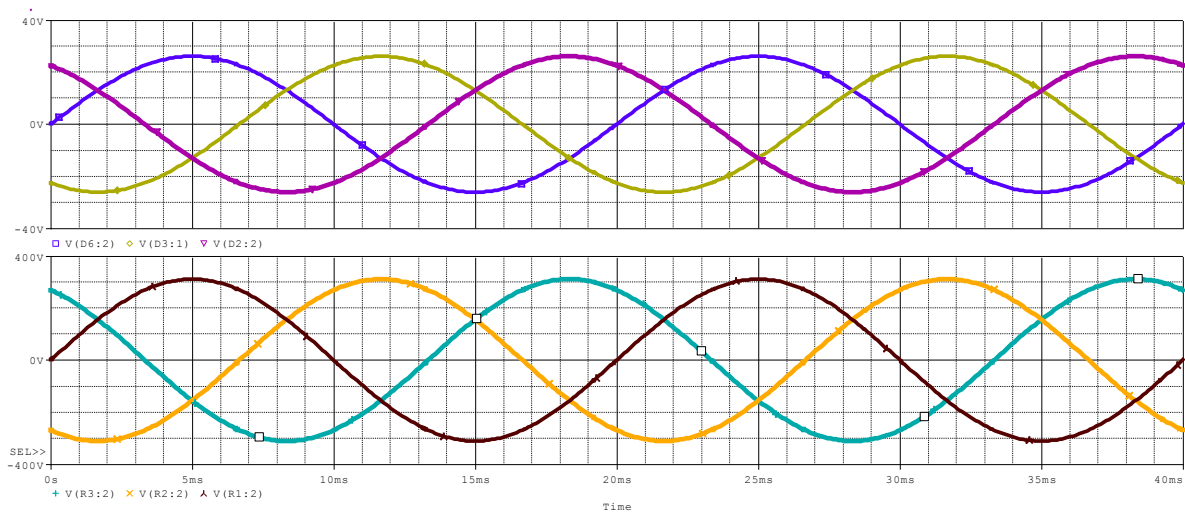



Current in the secondary

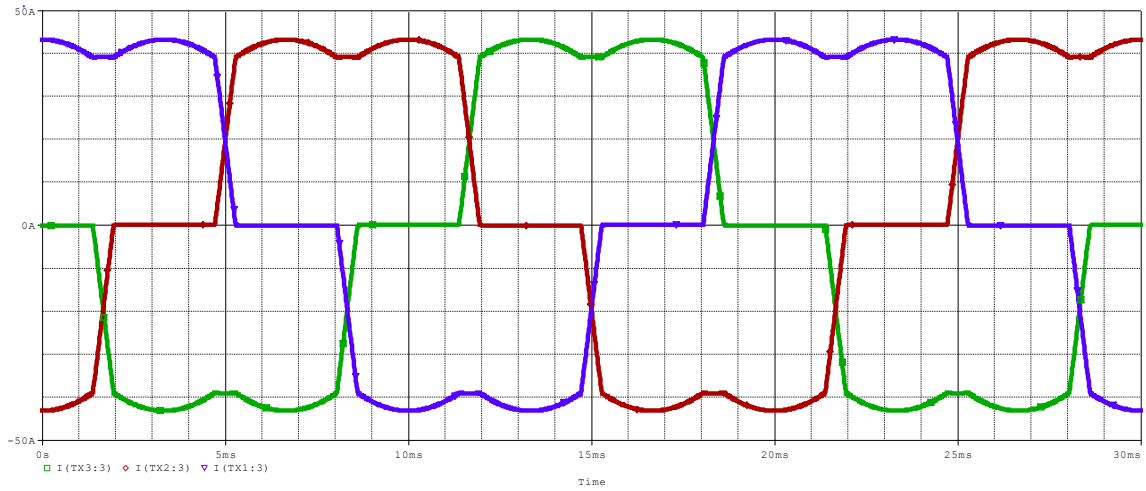


The output from the capacitor:

Circuit diagram:

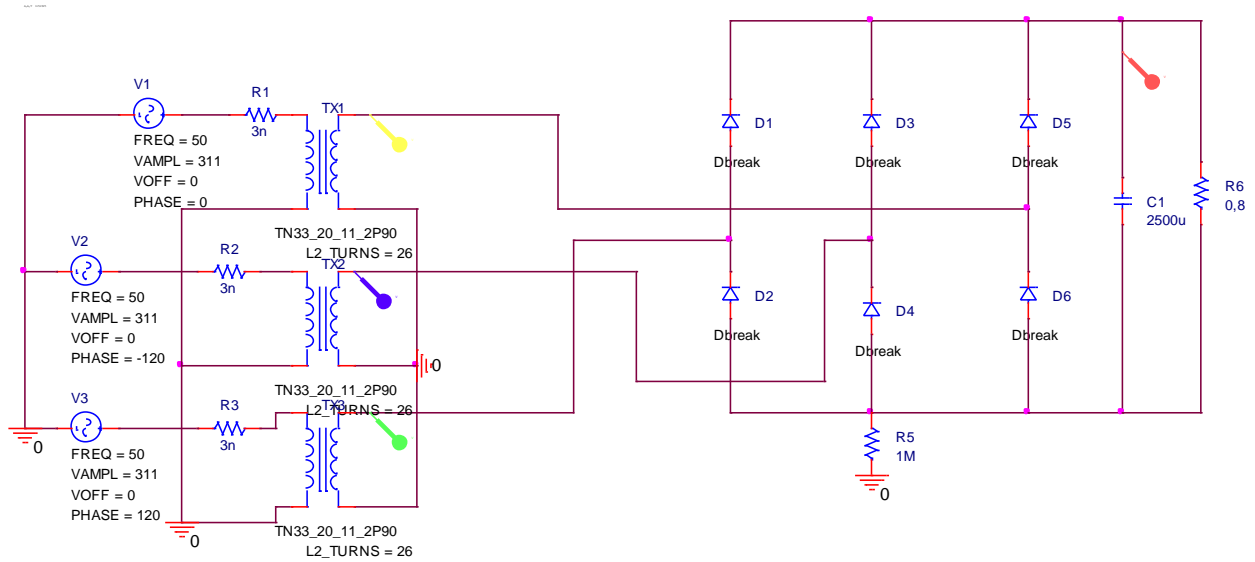


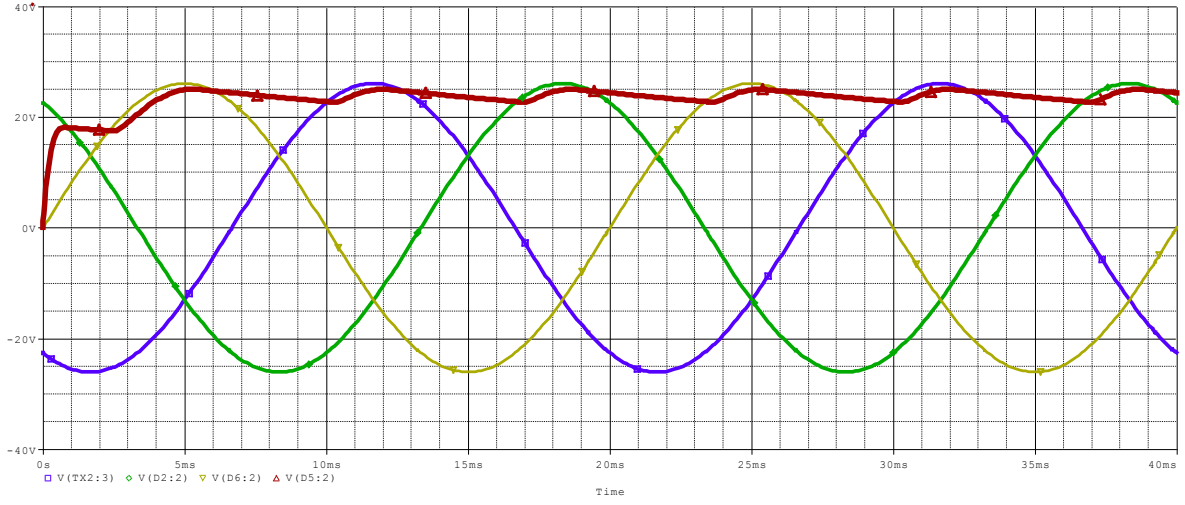

Current at the capacitor:

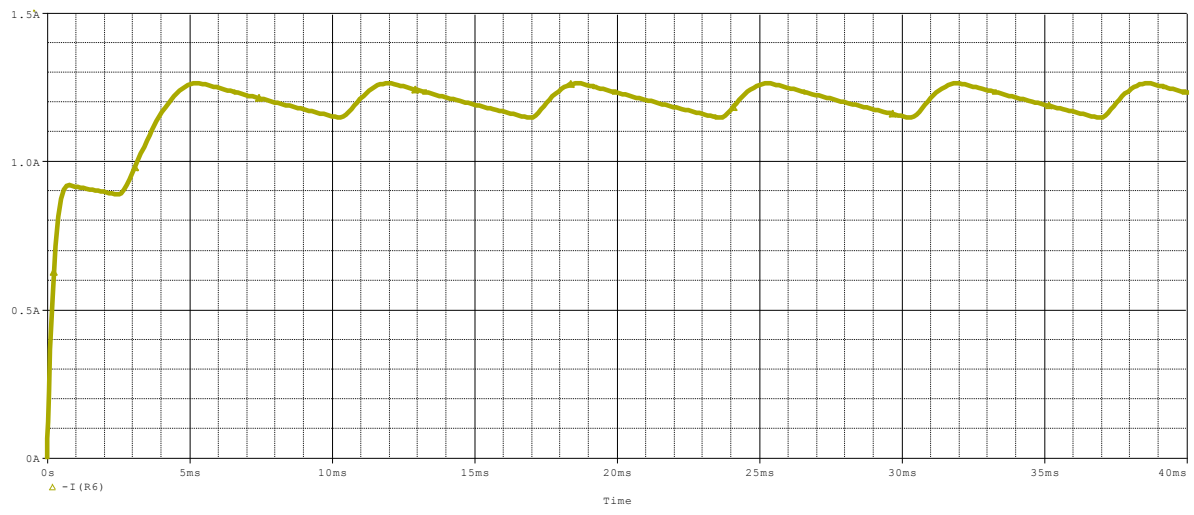


The output from the regulator:

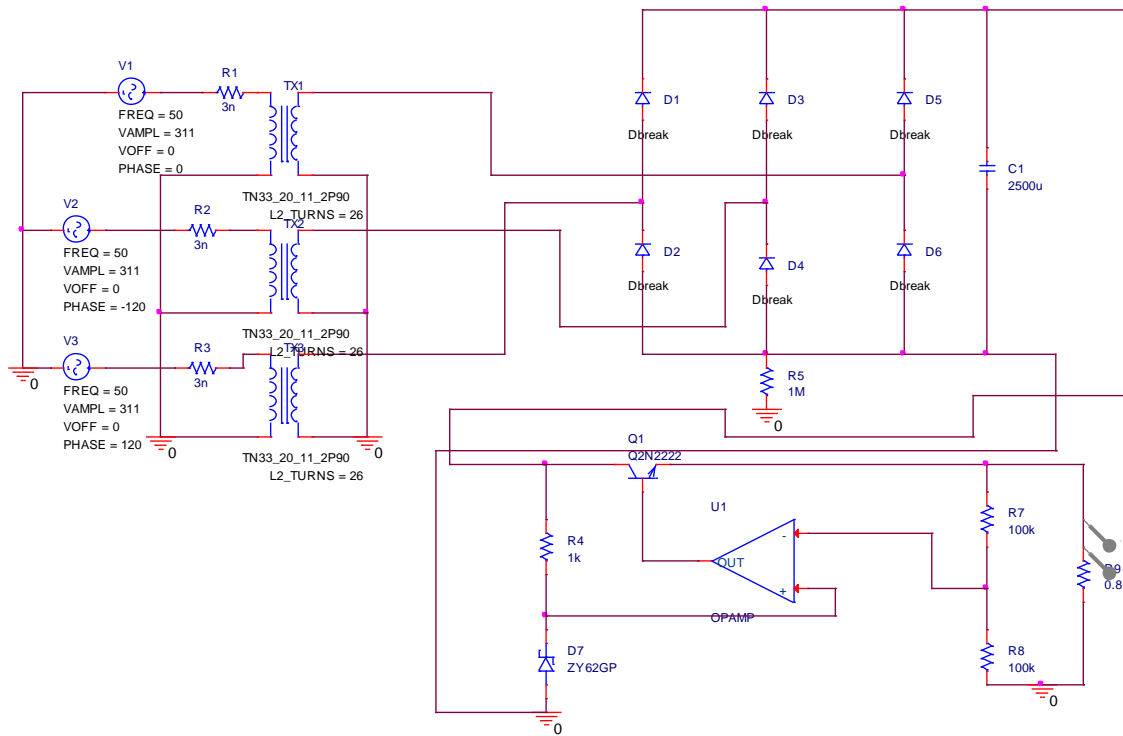

<Title>		
A	<Doc>	<Rev Code>
Monday, November 27, 2017		1 1

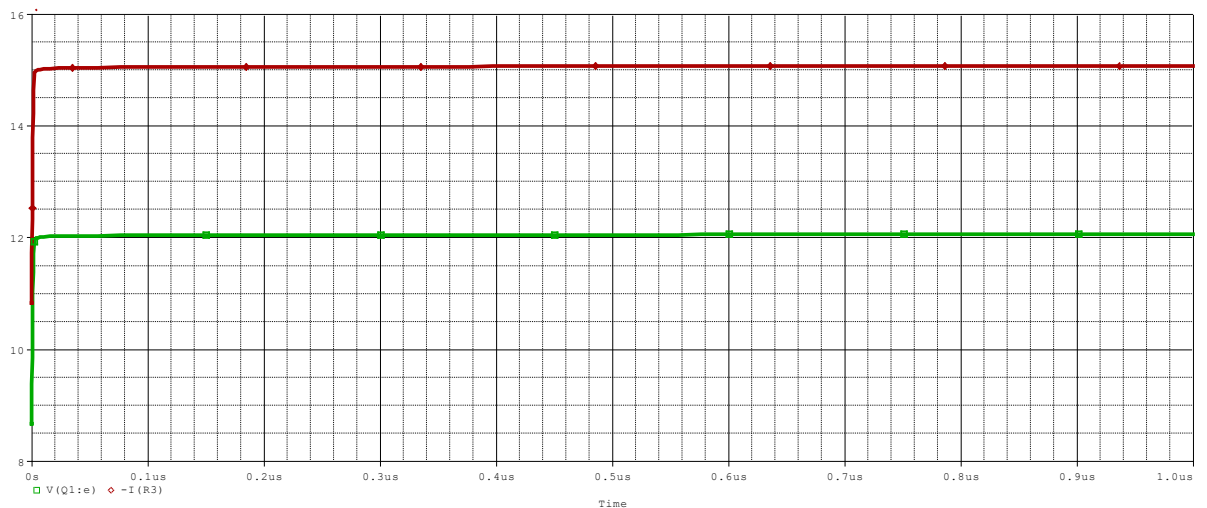The final output from the DC power supply:



Conclusion:

Not That: The aim of DC power supply is to get a DC current and voltages at the output, this operation must be pass from many stages, when I design the DC power supply I take with the intonation the minimum coast for the components and the minimum size of the DC voltages.

The practical design maybe different from the practical project since that the voltage drop at the component in orcad is zero "IDEAL CASE" but in practical we find the voltage drop at the component.

The main error and problem we face in this assignment is the orcad cannot graph the currents at different nodes.

Try to solveASSI. Use MATLAB Simulink. >>.



