



Electrical and Computer Engineering Department
Power Electronics ENEE 3305
An Assignment on Power Devices Switching
Fall 2017

1. A chopper circuit supplying a highly inductive load and having an IGBT **(BSM200GA120D)** as a switch, has the following parameters: $I_o=25A$ (use a current source of 25A to represent the RL load), $V_d=400V$, $f_s=15kHz$, $L_s=700nH$ and $t_{on}=30\mu s$. Assume linear voltage and current falls and rises during switching to:
 - i) calculate the conduction and the switching power losses if $t_c(on) = 400ns$, $t_c(off)=600ns$, assuming that $V_{on}=2.5V$ using the appropriate derived formulas
 - ii) In ORCAD/PSPICE, simulate a chopper circuit implementing an IGBT (BSM150GB50D) as a switch to supply a highly inductive load which has the following parameters: $I_o=25A$, $V_d=400V$, $f_s=15kHz$, $L_s=700nH$ and $t_{on}=30\mu s$. In the results, show the turn-on and turn-off transitions (magnified) for the voltage, current and power losses in the IGBT.
 - iii) calculate the average power losses in the IGBT
2. If the chopper circuit is now supplying a purely resistive load of 15 Ohms (no parallel diode) and implementing the IGBT model. Assume linear voltage and current falls and rises during switching to:
 - a) calculate the conduction and the switching power losses if $V_d=400V$, $f_s=15kHz$, $t_{on}=30\mu s$, $t_c(on) = 400ns$, $t_c(off)=600ns$, $L_s=700nH$ and $V_{on}=2.5V$ using the appropriate derived formulas
 - b) simulate the circuit in 2) using ORCAD/PSPICE and plot the magnified turn-on and turn off transitions of the voltage, current and power loss in the IGBT.
 - c) calculate the average power losses in the IGBT

The assignment is due to on Tuesday 24/10/2016.