



Electrical and Computer Engineering Department
Power Electronics ENEE 3305
An Assignment on Power Devices Switching
Fall 2017

Student's name: Anas Abdelhalim Tomaizeh

Student's number: 1152325

Assign. #1

Power device switching

Dr. M. Adu-Khaizaran



Abstract:

The aim of this assignment is to implement IGBT in a chopper circuit, and to simulate it using ORCAD to graph the voltage, current and power characteristics.

Theory:

- **Insulated Gate Bipolar Transistor (IGBTs):**

- The circuit symbol of IGBT is shown in the Fig. 1-a below, and i-v characteristic is shown in the Fig. 1-b below.

Fig. 1-a:


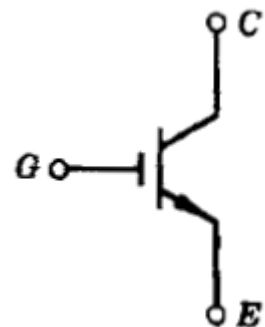


Fig. 1-b

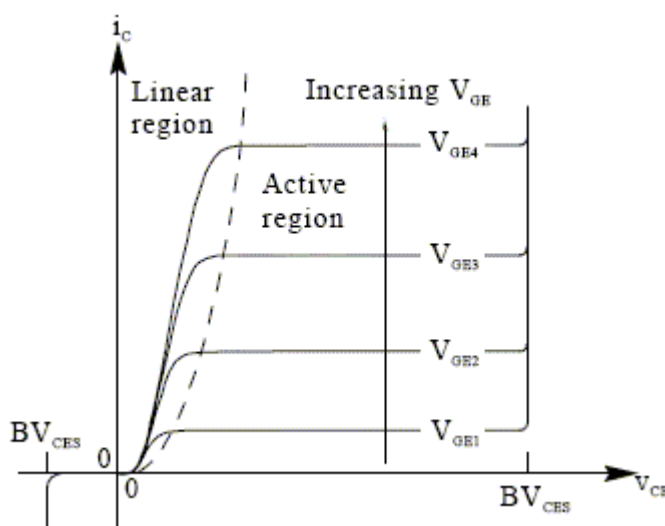

- Some advantages of IGBT:

- 1) Is better than MOSFET and BJT.
- 2) High input impedance so, it is required only a small amount of energy to switch the device.
- 3) IGBT have turn-on turn-off on the order of $1\mu s$.

➤ Some applications of IGBT:

IGBT is finding increasing application in medium power application for example, DC motor and AC motor drives and power supply.

● **Snubber Circuit:**

The aim of the snubber circuit is to reduce the electrical stress placed on the device during switching.

✓ **More function of snubber circuit:**

1. Limiting voltages applied to devices during turn-off transients.
2. Limiting device currents during turn-on transients.
3. Limiting the rate of rise (di/dt) of currents through devices at device turn-on.
4. Limiting the rate of rise (dv/dt) of voltages across devices during device turn-off.
or during reapplied forward blocking voltages (e.g., SCRs during the forward blocking state).
5. Shaping of the switching trajectory of the device as it turns on and off.

From the circuit topology perspective, there are three broad classes of snubber circuit:

1. Unpolarized series R-C snubbers used to protect diodes and thyristors by limiting the maximum voltage and dv/dt at reverse recovery.
2. Polarized R-C snubbers. These snubbers are used to shape the turn-off portion of

the switching trajectory of controllable switches, to clamp voltages applied to the

devices to safe levels, or to limit dv/dt during device turn-off.

3. Polarized L-R snubbers. These snubbers are used to shape the turn-on switching

trajectory of controllable switches and/or to limit dI/dt during device turn-on.

- ✓ **Freewheeling diode:** when turn-on the switch the result is stored energy in the inductor, this energy will be dissipated in the form spark, so use a Freewheeling diode across the load to provide an alternative path for the current when the switch is off.

Calculation:

Part one: high inductive load:

1) the average power losses during conduction in the IGBT

$$P_{on} = V_{on} * I_o * T_{on} * F_s \\ = 2.5 * 25 * 30\mu * 15K = 28.125 \text{ watt}$$

2) The total average power losses during switching in the switch is:

$$P_s = 1/2 * F_s * V_d * I_o * (T_{c(on)} + T_{c(off)}) \\ = 0.5 * 15K * 400 * 25 * 1000 * 10^{-9} = 75 \text{ watt.}$$

Part two: resistive load:


1) The average conduction power loss is:

$$P_{on} = V_{on} \cdot I_o \cdot F_s \cdot T_{on} \\ = 2.5 \cdot (400 - 2.5/15) \cdot 15K \cdot 30 \cdot 10^{-6} = 29.8125 \text{ watt.}$$

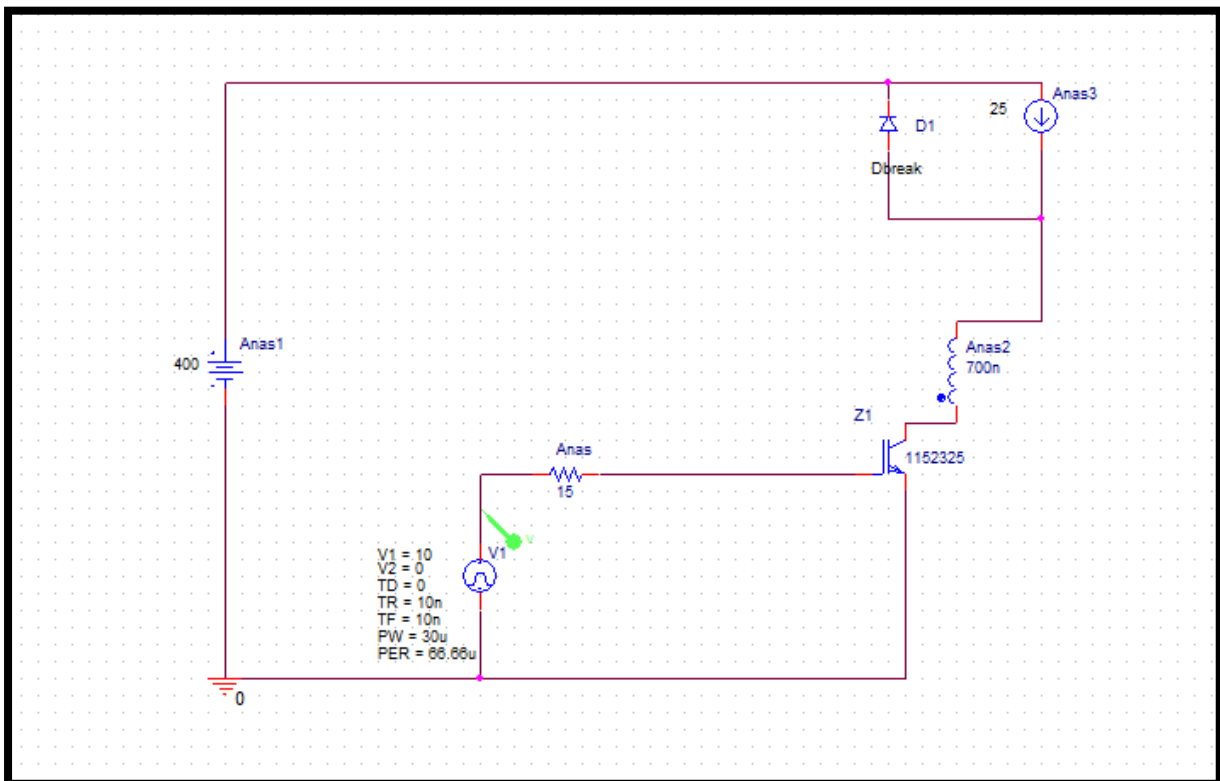
2) Total average switching power loss with resistive load is:

$$P_s = 1/6 \cdot F_s \cdot V_{dc} \cdot I_o \cdot (T_{c'on} + T_{c'off}) \\ = 1/6 \cdot 15K \cdot 400 \cdot (400 - 2.5/15) \cdot (1000 \cdot 10^{-9}) = 26.5 \text{ watt.}$$


For high inductive load: **Circuit diagram:**



V-Pulse

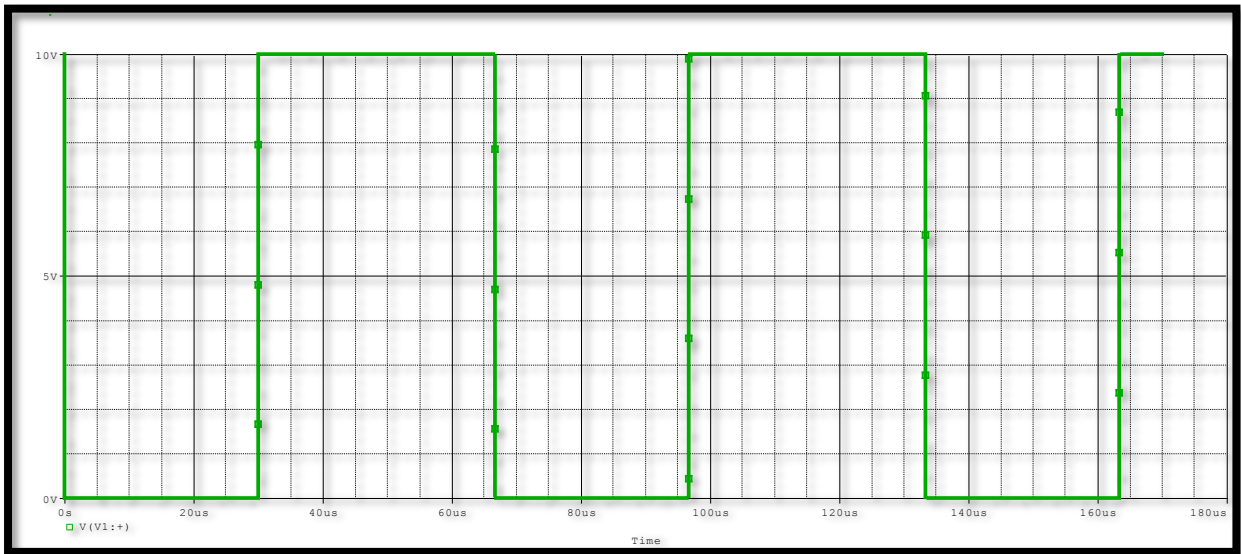


The results:

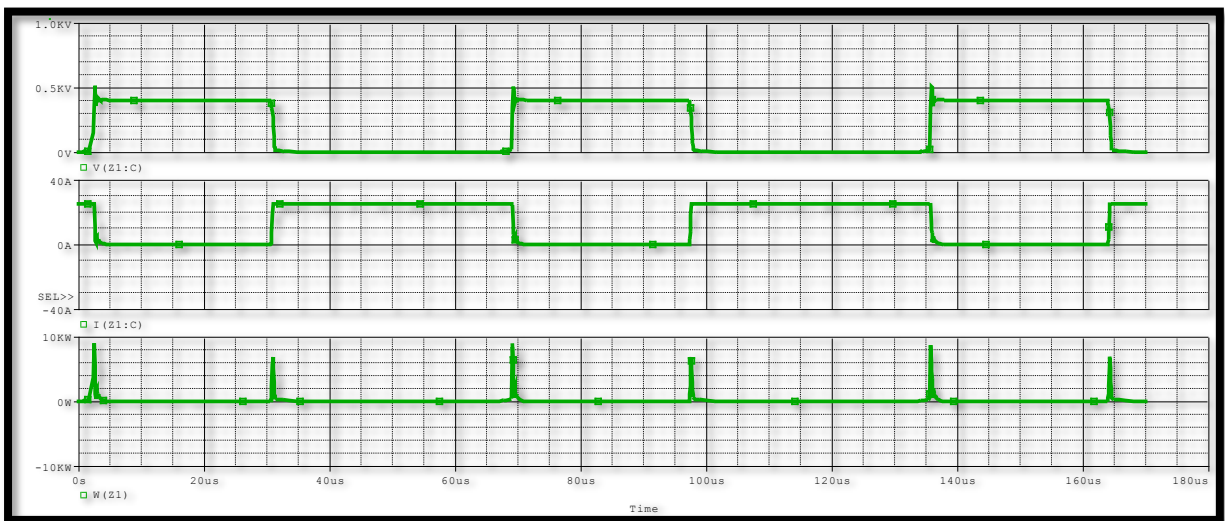


For resistive load:

Circuit diagram:

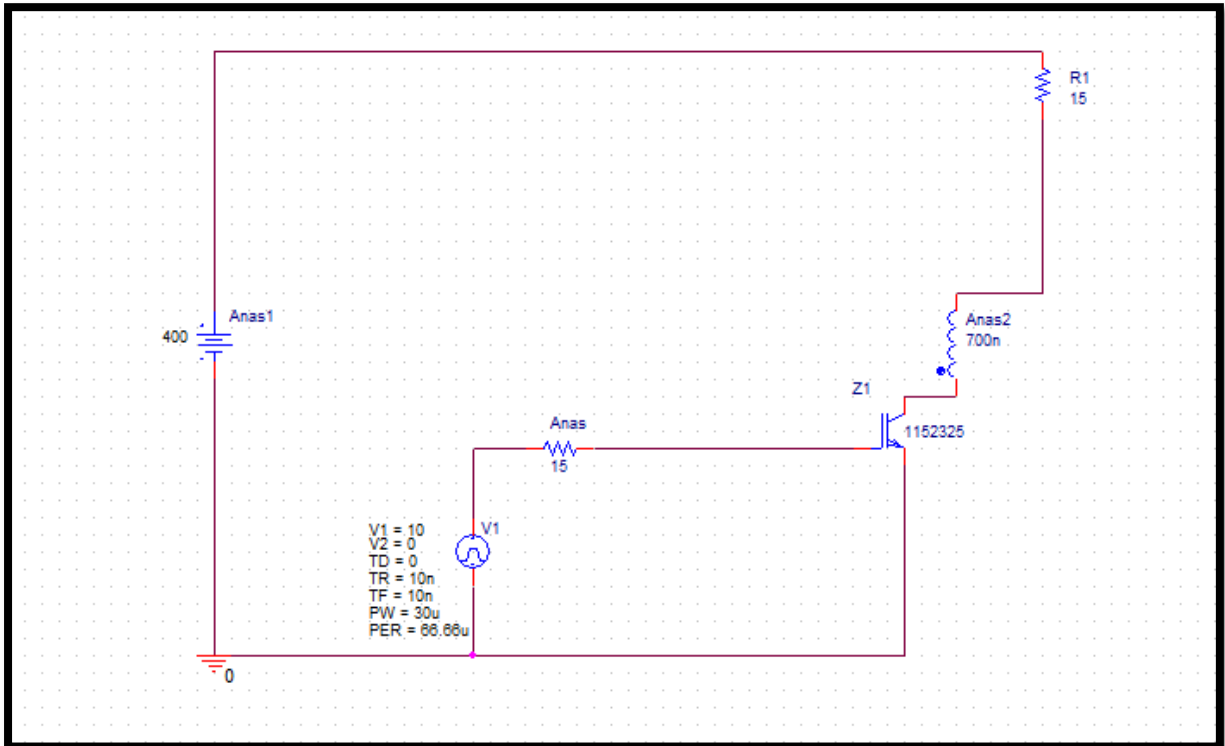


The result:

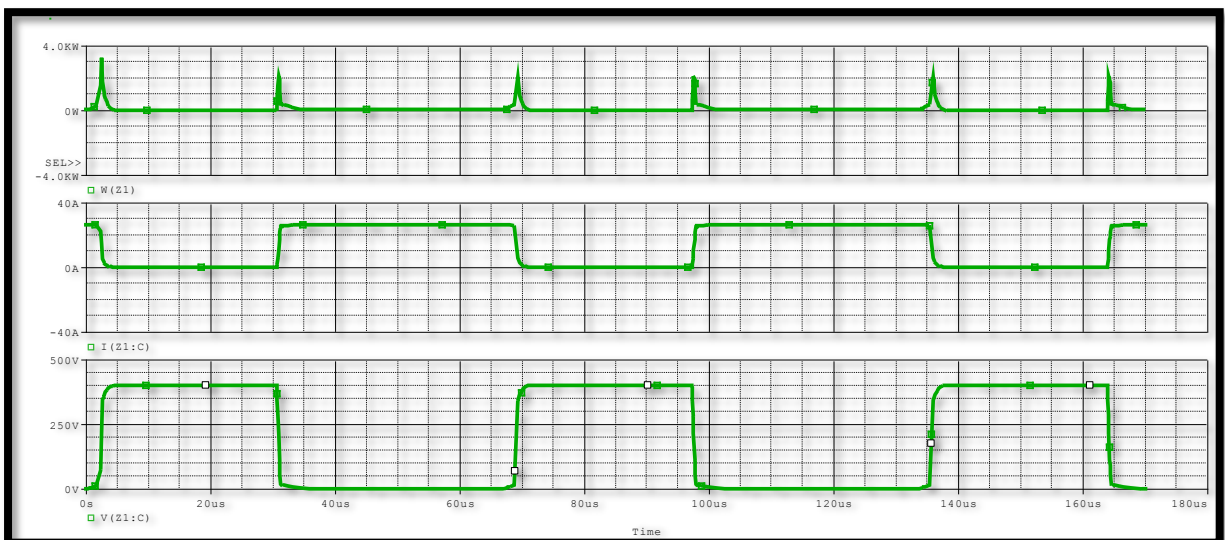

Conclusion:


Zoom for part one: high inductive load:

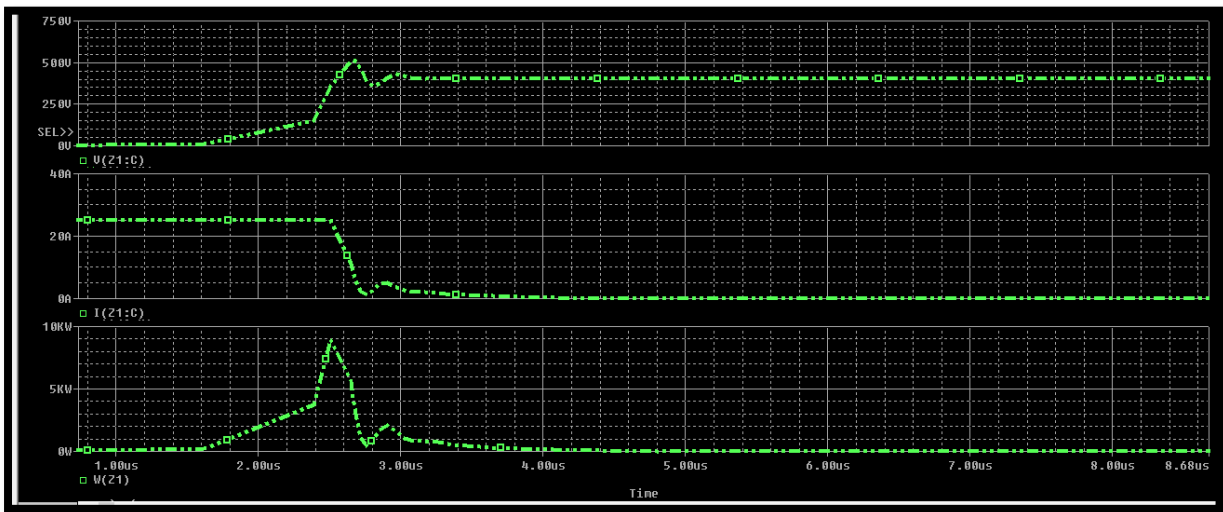

According to the graph 'zoom for part one, shown above' note that:

- There is an over shoot in the voltage curve, since there is a voltage drop across the stray inductance at turn-on state.
- The tail current shown in the current curve, since that the IGBT turns off as an open Base BJT.
- The voltage start increasing when the current is still unchanged, but it is got in a few microsecond, so no need to snubbers' circuit to protect the power electronics device.
- In this case, we use a Freewheeling diode because the inductance load stored the energy when the switch is on, so to protect the device from the spark we use this diode.

Zoom for part two: resistive load:

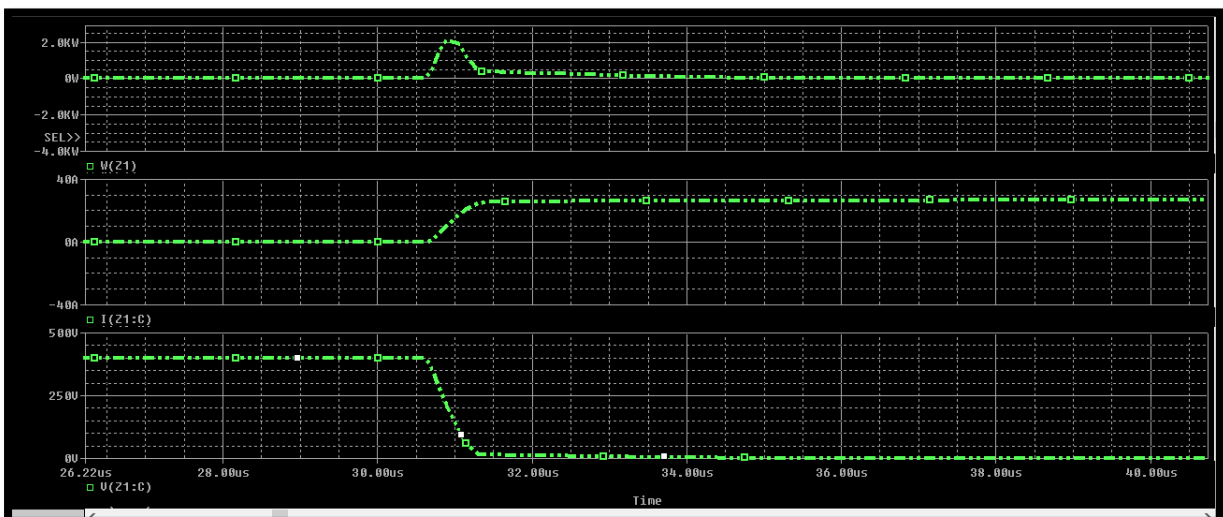

According to the graph 'zoom for part two, shown above' note that:

- The voltage begins increasing when the current starts decreasing at the same time, but it is done in a few microseconds (less than in high inductive load), so no need to snubbers circuit to protect the power electronics device.
- We didn't use a Freewheeling diode in this case because no energy is stored in the resistive load.

NOTE THAT: The error in simulation: the power dissipated in IGBT in the ideal case is equal: $V_d \cdot I_o = 400 \cdot 25 = 10\text{KW}$ but in the graph the result is about 9KW and that is because the stray inductance which makes an over-shot in the voltage and in the current, also the power dissipated in IGBT when it is connected with resistive load is 1/3 of power dissipated when it is connected with high inductive load.

References:

- 1) Muhammad H. Rashid 'Power Electronics: Circuits, Devices and Applications', 4th edition Prentice Hall 2013.
- 2) Ned Mohan, Tore M. Undeland, and William P. Robbins 'Power Electronics: Converters, Application, and Design', 3rd edition 2003.
- 3) Lecture note, Dr. M. Abu-Khaizaran.

Failer try to solve the assign, use MATLAB SIMULINK.

