
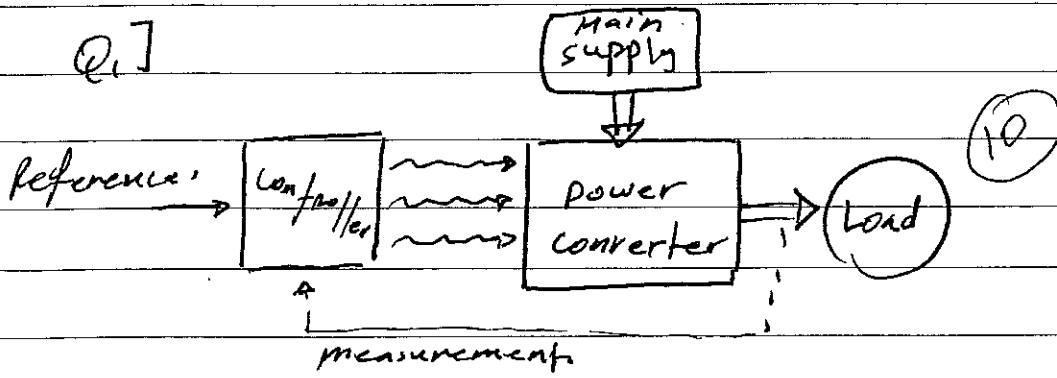


Q1]

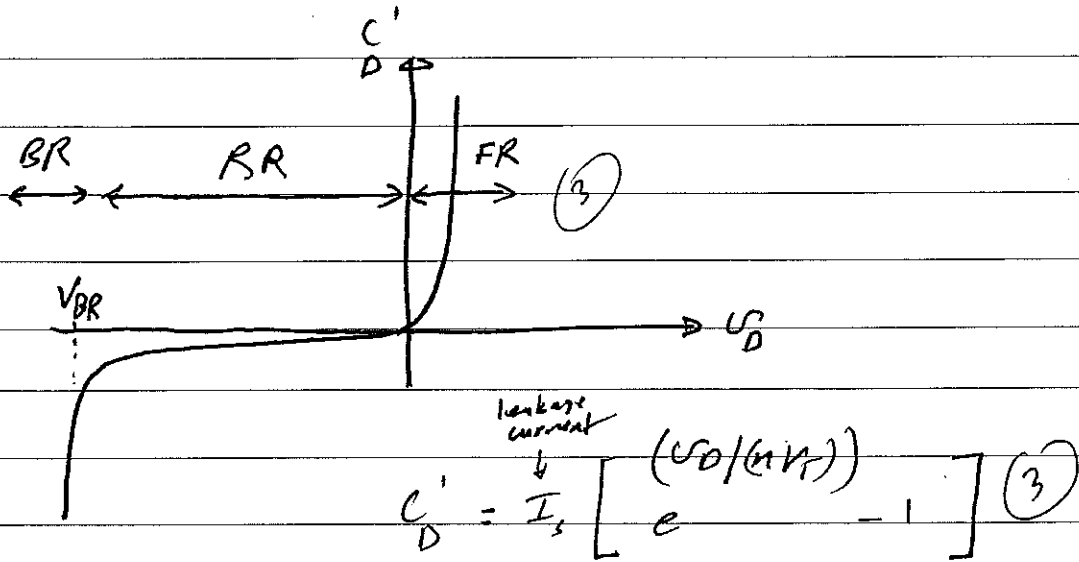

Q2]



$n$ : Ideality factor


$V_T$ : Thermal voltage.

(1) Forward region  $\rightarrow$  D conducts when  $U_D > V_{TD}$ , where  $V_{TD}$  is the threshold voltage or turn on voltage. ( $C_D' \approx I_s e^{\frac{U_D}{nV_T}}$ )

(2) Reverse region  $\rightarrow$  D is non-conducting when  $U_D < 0$  &  $|C_D'| > I_s$   
( $C_D' \approx -I_s$ )

(3) Breakdown region  $\rightarrow$   $U_D$  is high where  $|U_D| > V_{BR}$   
 $C_D'$  increases rapidly. Breakdown voltage

Q2]

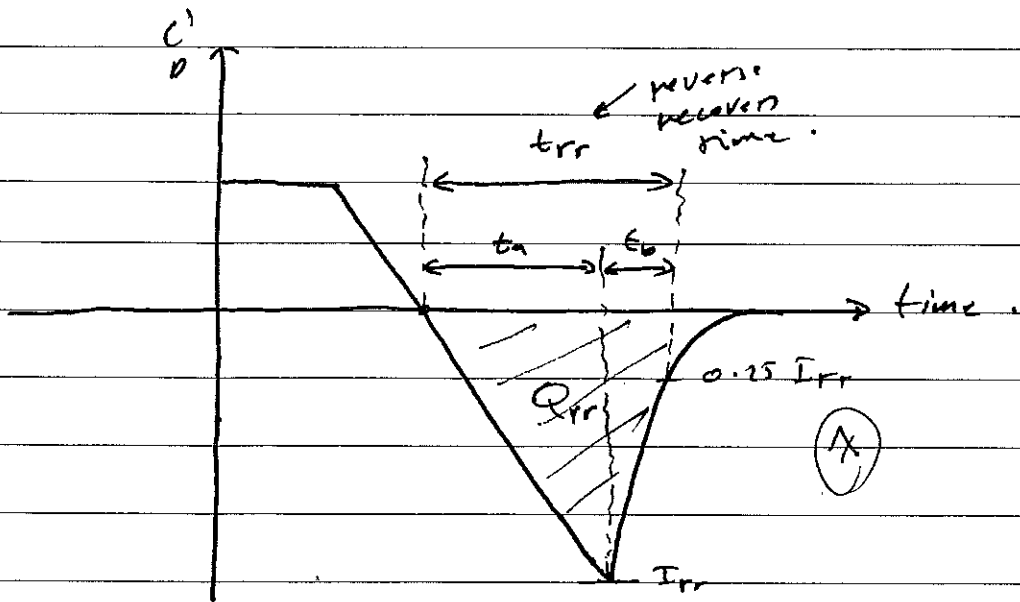


$$\frac{di'}{dt} = \frac{I_{rr}}{t_a} \approx \frac{I_{rr}}{t_{rr}} \Rightarrow t_{rr} = \frac{I_{rr}}{(di'/dt)} \quad (1)$$

$$I_{rr} \Rightarrow Q_{rr} = \frac{1}{2} t_{rr} I_{rr} \Rightarrow I_{rr} = \frac{2Q_{rr}}{t_{rr}} \quad (2)$$

$$(2) \rightarrow (1) \Rightarrow t_{rr} = \sqrt{\frac{2Q_{rr}}{(di'/dt)}}$$

Q4]

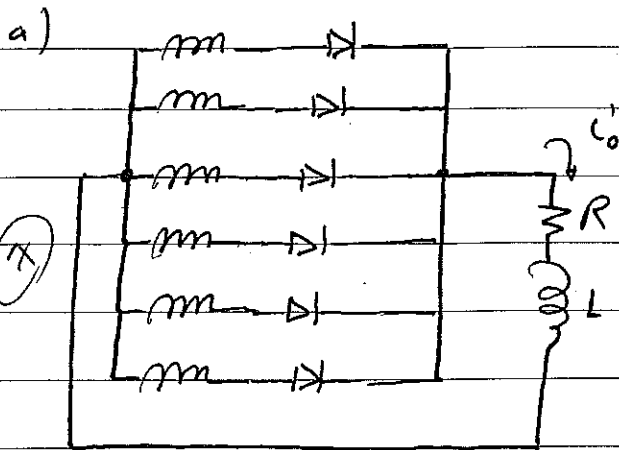

$$e) RF = \frac{I_{AC}}{I_{DC}}$$


$$I_{DC} = \frac{0.955(170)}{200} = 0.81175 A$$

$$I_{AC} = \frac{0.0546 \text{ (X)}}{\sqrt{(200)^2 + (6(170 \times 60)L)^2}} \sqrt{2}$$

$$I_{AC} = \frac{6.563}{\sqrt{40000 + (2262L)^2}}$$

$$p.o.L = \frac{6.563}{0.81175} \sqrt{40000 + (2262L)^2}$$
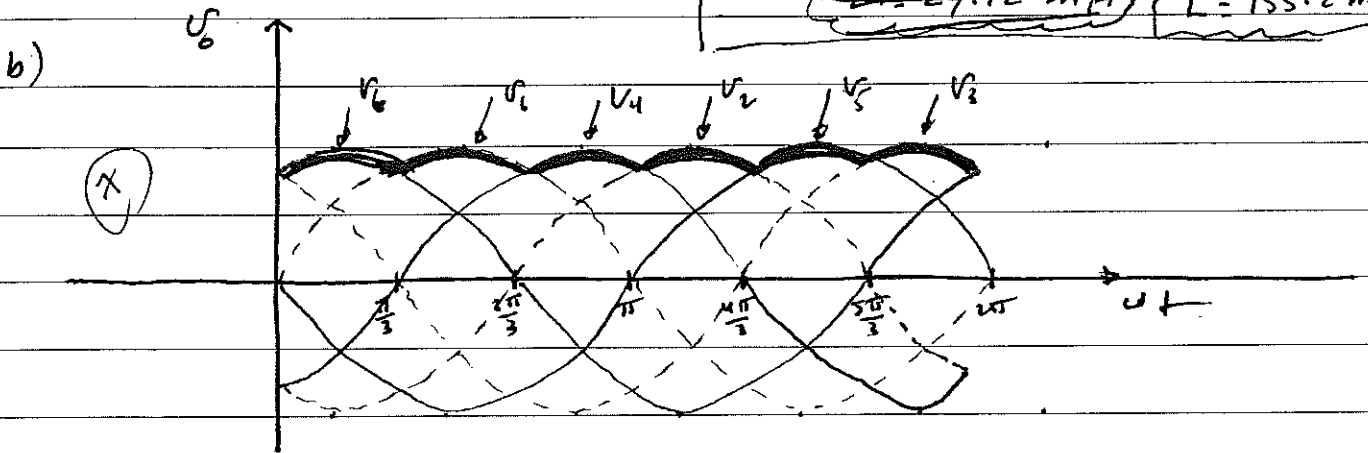
$$\boxed{L = 24.12 \text{ mH}} \quad \boxed{L = 155.2 \text{ mH}}$$



$$c) v_{o,16} = \frac{6}{\pi} \sin\left(\frac{\pi}{6}\right) \left(\frac{2}{3.5}\right) V_m \cos(6\omega t) = 0.0546 V_m \cos(6\omega t)$$

$$\text{(X)} \left\{ \begin{aligned} C_{o1} &= \frac{0.0546 V_m \cos(6\omega t - \tan^{-1}\left(\frac{6\omega L}{R}\right))}{\sqrt{R^2 + (6\omega L)^2}} \end{aligned} \right.$$

$$d) V_{DC} = \frac{6}{\pi} \sin\left(\frac{\pi}{6}\right) V_m = \frac{3}{\pi} V_m = 0.955 V_m$$

$$\text{(X)} V_{RMS} = \sqrt{\frac{2(6)}{2\pi} \int_0^{\pi/6} V_m^2 \cos^2(\omega t) d(\omega t)} = \sqrt{\frac{6}{\pi} \frac{V_m^2}{2} \left(\frac{\pi}{6} + \frac{1}{2} \sin\left(\frac{\pi}{3}\right)\right)}$$

$$V_{RMS} = 0.956 V_m$$

$$FF = \frac{V_{RMS}}{V_{DC}} = \boxed{1.00112} \quad RF = \sqrt{FF^2 - 1} = \boxed{4.74\%}$$

$$1.00088 \text{ or } 4.197\% \text{ or}$$

Q5] a)  $v_a(t) = L \frac{di_a}{dt}$

$$V_m \sin(\omega t) dt = L di_a$$

$$\int_0^{\omega t} V_m \sin(\omega t) d(\omega t) = L \omega \int_{i_a(0)}^{i_a} di_a$$

$$i_a' - i_a(0) = \frac{V_m}{\omega L} [1 - \cos(\omega t)]$$


$$i_a' = -I - \frac{V_m}{\omega L} [\cos(\omega t) - 1]$$

b)  $i_a'(M) = -I = -I - \frac{V_m}{\omega L} [\cos(M) - 1]$

$$M = \cos^{-1} \left[ 1 - \frac{2\omega L I}{V_m} \right]$$

$M = 13.5^\circ$

c)

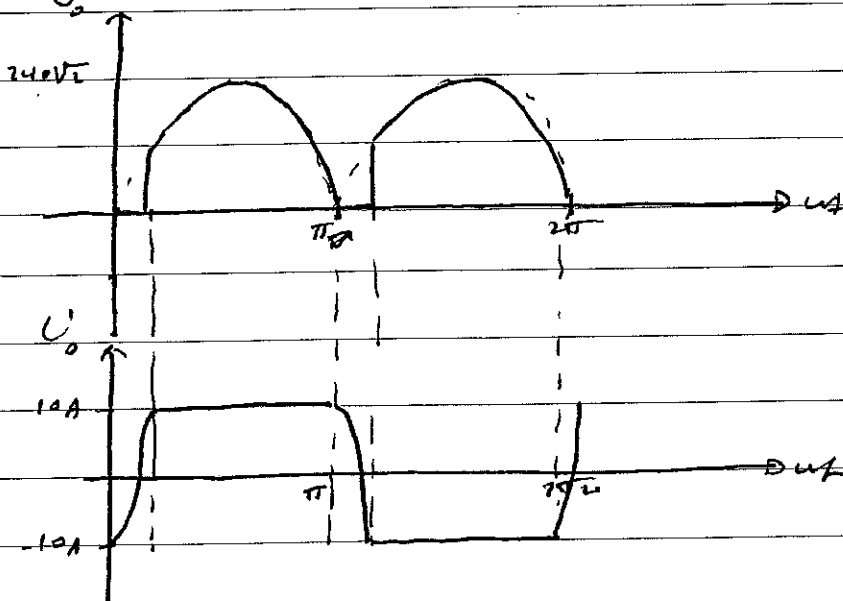

d)  $i_{a1}' = a_1 \cos(\omega t) + b_1 \sin(\omega t)$

$$a_1 = \frac{2}{\pi} \int_0^{\pi} 10 \cos(\omega t) d(\omega t) = 0$$

$$b_1 = \frac{2}{\pi} \int_0^{\pi} 10 \sin(\omega t) d(\omega t) = \frac{20}{\pi} \times 2 = \frac{40}{\pi}$$

$$i_{a1}' = \frac{40}{\pi} \sin(\omega t) \text{ A} = 12.732 \sin(\omega t) \text{ A}$$

$I_{a1} = \frac{40}{\pi} \text{ A}$