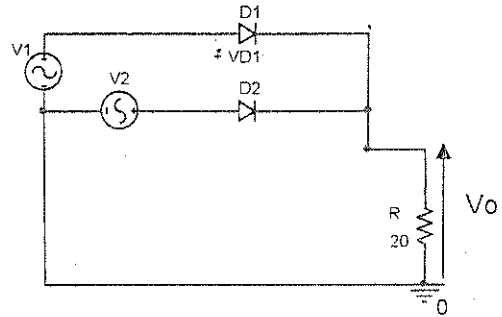


Birzeit University  
Electrical and Computer Engineering Department  
Power Electronics 3305  
Quiz # 2

Student Name: \_\_\_\_\_ ID: \_\_\_\_\_

**Question #1** In the circuit shown below, the  $V_1=8\sin 100\pi t$  V and  $V_2=8\sin(100\pi t-180)$  V, and the diodes are non ideal with a voltage drop of 1V then:

a) Using the waveforms shown, draw the output voltage



b) Calculate the average output voltage


1 diode conducting

~~$V_1 = 8\sin 100\pi t$~~   
 $V_1 = 8\sin \alpha \Rightarrow \alpha = \sin^{-1} \frac{1}{8}$   
 $\alpha = 7.2^\circ$   
 $\alpha = \frac{7.2}{180} \cdot \pi$


$\Rightarrow \alpha = 0.04\pi, \beta = \pi - 0.4\pi = 0.96\pi$  or  $172.8^\circ$

$$V_{dc} = \frac{2}{2\pi} \int_{\alpha}^{\beta} (V_m \sin \omega t - 1) d\omega t$$
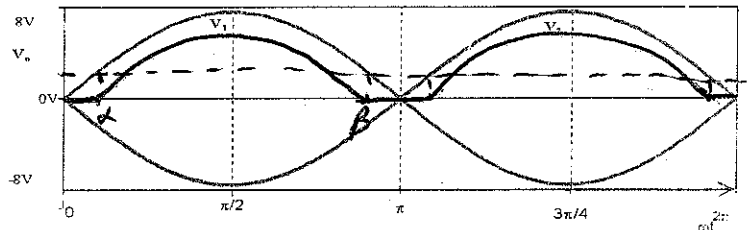
$$= \frac{1}{\pi} \int_{0.04\pi}^{0.96\pi} (8 \sin \omega t - 1) d\omega t$$



c) Plot the voltage across D1

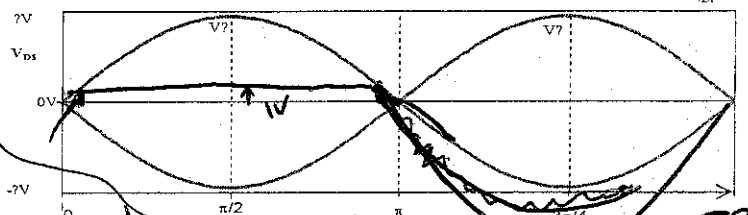


$$= \frac{1}{\pi} \left[ -V_m \cos \omega t \right]_{0.04\pi}^{0.96\pi} - 0.96\pi + 0.04\pi$$

$V_{dc} = V_1 - V_2 + 1$

$$= -\frac{8}{\pi} [\cos 0.96\pi - \cos 0.04\pi] - 0.92\pi$$
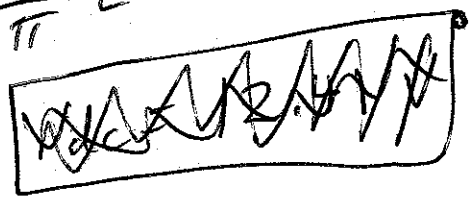
$$= -\frac{8}{\pi} [-0.992 - 0.992] - (2.89) = \frac{-8}{\pi} (-1.984) - 2.89$$




$\Rightarrow V_{dc} = +5.052 - 2.89 = 2.162$   
 $V_{dc} = 2.162 \text{ V} < \frac{2V_m}{\pi}$   
 $V_{dc} = 2.162 < 5.093 \text{ V!}$

Birzeit University  
Electrical and Computer Engineering Department  
Power Electronics 3305  
Quiz# 2

Student Name: \_\_\_\_\_ ID: \_\_\_\_\_

**Question # 1**

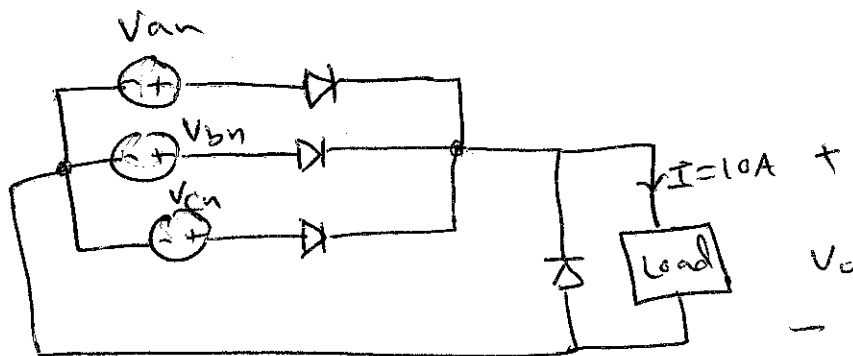- a) Draw the circuit arrangement of a three phase half-wave rectifier supplying a highly Inductive load by 10A.



- b) Assuming ideal diodes, plot the output voltage and calculate its average if  $V_{an} = 314 \sin 100\pi t$  V.

$$V_{dc} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} 314 \sin 100\pi t \, d\omega t$$



$$= \frac{9V_m}{\pi} \sin \frac{\pi}{2} = \frac{3(314)}{\pi} \sin \frac{\pi}{3} = \frac{3(314)}{\pi} \left(\frac{\sqrt{3}}{2}\right) = 259.67V$$

- c) Assuming that a freewheeling diode is connected across the load, plot the input current from Phase a "ia"

