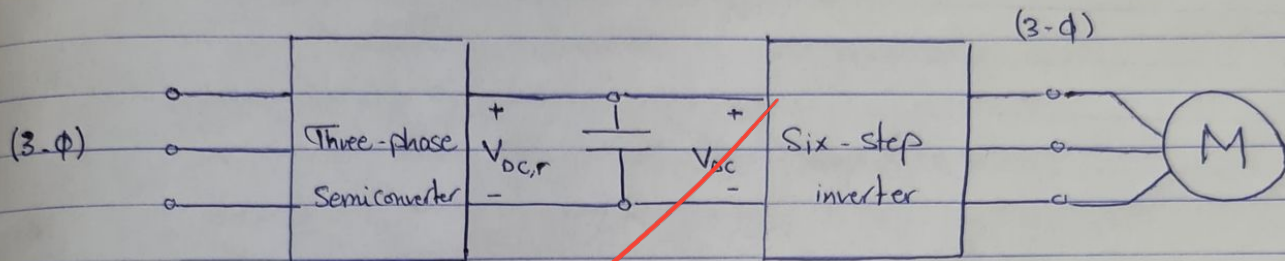


16/20

Name: Yazan Yusef


ID: 1170249

Q1: a) Draw the Drive circuit




- * Where : $V_{DC,r} \Rightarrow$ The DC voltage with ripple.
- $V_{DC} \Rightarrow$ The DC voltage after filtering. [approximately Pure DC]

* The Three-phase semi-converter:

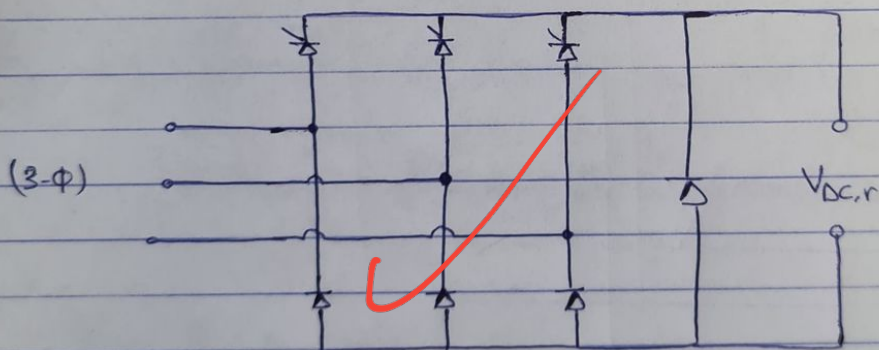

* Six-step inverter:

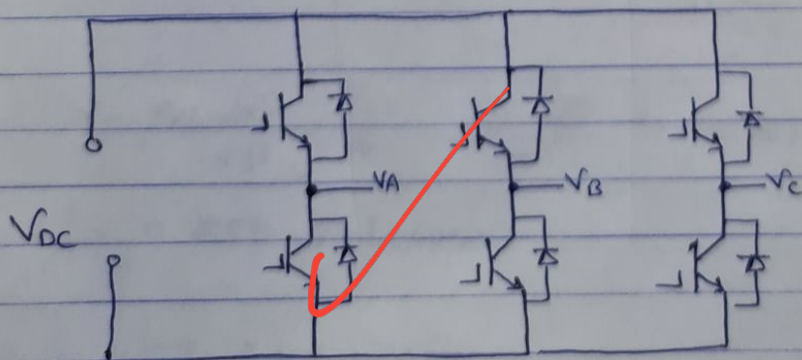

4

Q1: B) Motor operates at 20 Hz, then the firing angle of the controlled rectifier is:

stage 1: input: $V_{L-L} = 420$ volt (rms)
 $f = 50$ Hz

V_{DC} of the rectified signal is:

$$\begin{aligned} V_{DC} &= \frac{3\sqrt{3}}{2\pi} \left(420 \sqrt{\frac{2}{3}} \right) (1 + \cos(\alpha)) \\ &= \frac{1260\sqrt{2}}{2\pi} (1 + \cos(\alpha)) \\ &= \frac{630\sqrt{2}}{\pi} (1 + \cos(\alpha)) \quad \text{--- (1)} \end{aligned}$$

stage 2: The peak of the (line to neutral) Fundamental voltage Harmonic:

$$V_{1, Peak \text{ L-N}} = \frac{2}{\pi} \times \frac{630\sqrt{2}}{\pi} (1 + \cos(\alpha))$$

Since $\frac{V}{f}$ is constant:

$$\frac{V_{L-N}(\text{Nominal})}{f} = \frac{V_{L-N}(\text{Peak})}{f} \rightarrow \frac{440 \left(\frac{\sqrt{2}}{\sqrt{3}} \right)}{50} = \frac{V_{1, Peak \text{ L-N}}}{20}$$

$$\Rightarrow \frac{176\sqrt{2}}{\sqrt{3}} = \frac{2}{\pi} \times \frac{630\sqrt{2}}{\pi} (1 + \cos(\alpha))$$

$$0.7959 = 1 + \cos(\alpha)$$


$$-0.204 = \cos(\alpha)$$

$$\alpha = 101.77^\circ$$

(2)

6

Question 2:

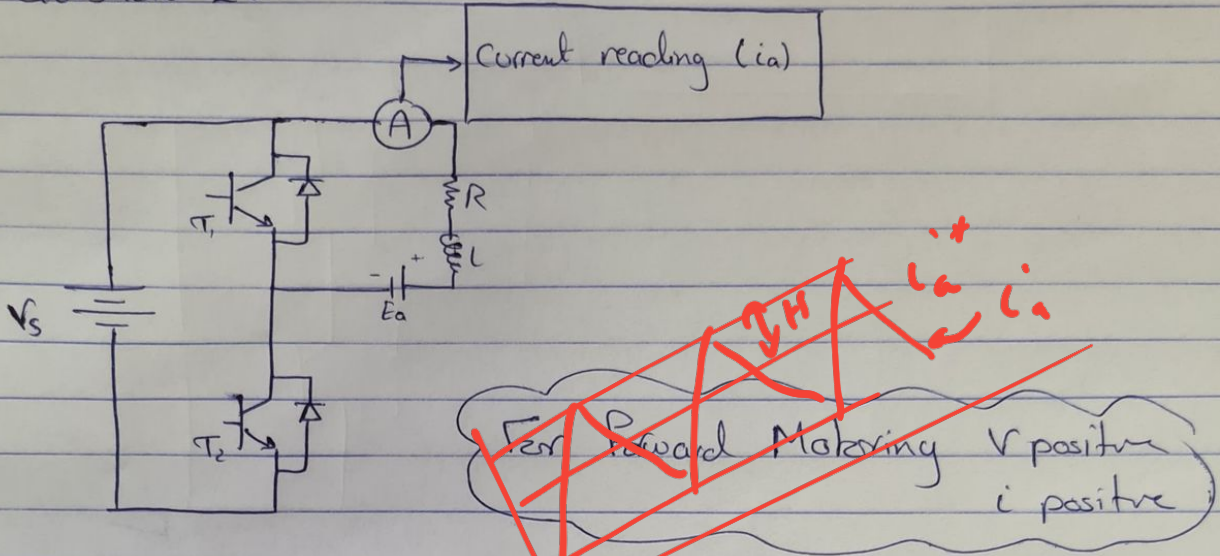

a) Operation & implementation of current controller:


1) Setting a reference current equals to:

$$\frac{V_s - E_a}{\sqrt{R^2 + (\omega L)^2}} = i_a^* \quad \text{"The reference current"}$$


2) define the delta region of oscillation for the current let it be Δi

$$|\Delta i| \Rightarrow \text{For example } 0.01 i_a^*$$

3) Gate control:

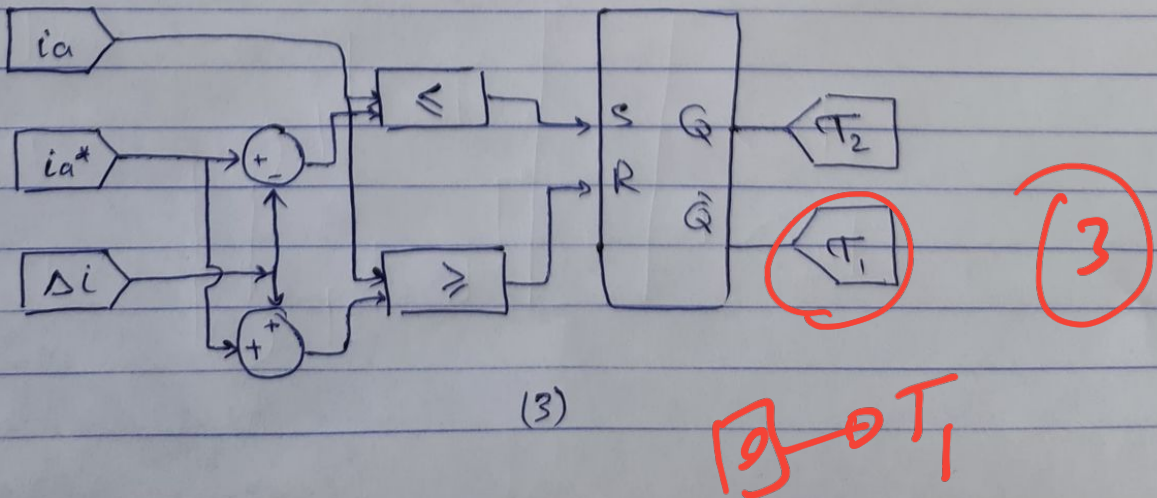


The current sketch

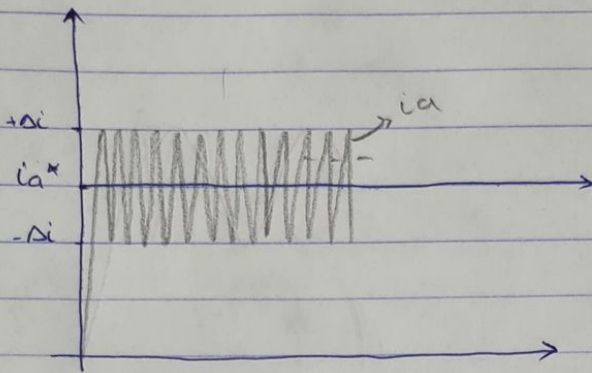

In the period where $i_a < i_a^* - \Delta i \rightarrow T_2$ is on
 " " " " " $i_a > i_a^* + \Delta i \rightarrow T_1$ is on

①

b)

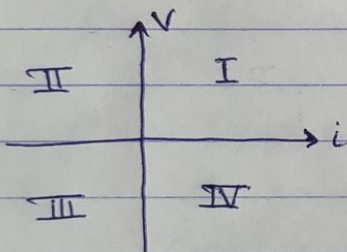

v_a	i_a	Quadrant	T_1	T_2	
v_s	-	IV	0	0	X
v_s	+	I	0	1	✓
0	+	I	0	0	X
0	-	IV	1	0	✓

②