

Electrical and Computer Engineering Department
ENEE5303, Exam 2
Dr. Mahran Quraan

- 1) A 230 V, 500 rpm, 90 A separately excited DC motor has the armature resistance and inductance of 0.115 Ω and 11 mH, respectively. The motor is fed by a four-quadrant chopper. The source voltage is 230 V and the frequency of operation is 400 Hz.
 - i. If the motor operation is required in the fourth quadrant at the rated torque and 300 rpm, calculate the duty cycle.
 - ii. What should be the value of the duty cycle if the motor is working in the third quadrant at 400 rpm and half of the rated torque?

- 2) A DC separately excited motor controlled by a two-quadrant chopper circuit consisting of two IGBTs and two diodes (shown in Fig.1). The motor current is controlled using hysteresis current controller:
 - i. Show, perhaps with the aid of a sketch, the operation and implementation of the current controller to generate the gate drive signals for forward motoring?
 - ii. Draw the control system required for driving the armature circuit of the motor in constant torque region.
 - iii. Complete Table 1 which shows the truth table of current controller where the digital outputs of logic processors are the gate signals of IGBTs T₁, T₂, T₃ and T₄ (1 = high & 0 = low).
 - iv. Derive the transfer function of the speed controller.

Table 1

$\omega_m > 0$	$i_a^* > 0$	$T_P > 0$	Quadrant of operation	Gate signal of IGBT T1	Gate signal of IGBT T2
1	1	1			
1	0	0			
1	0	1			
1	1	0			

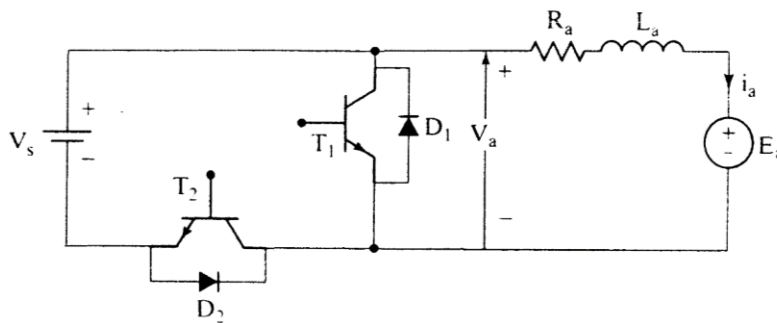


Fig. 1