

Problem 1

$$\textcircled{1} \quad V_{a,r} = R_a I_{a,r} + E_{a,r} = R_a I_{a,r} + K' \omega_{m,r}$$

$$K' = \frac{V_{a,r} - R_a I_{a,r}}{\omega_{m,r}} = \frac{220 - 2(11.6)}{1500 \left(\frac{\pi}{30}\right)}$$

$$K' = 1.25 \left[\frac{V}{r/p} \right]$$

$$\frac{2V_m \cos \alpha}{\pi} = R_a I_{a,r} + K' \omega_m$$

$$\frac{2(230\sqrt{2})}{\pi} \cos \alpha = 2(11.6) + 1.25(1000)$$

solve for α

$$\alpha = 41.8^\circ$$

$$\textcircled{2} \quad \frac{2V_m \cos \alpha}{\pi} = R_a I_{a,r} + K' \omega_m$$

$$\frac{2(230\sqrt{2})}{\pi} \cos \alpha = 2(11.6) + 1.25(-1500)$$

$$\alpha = 147^\circ$$

$$\textcircled{3} \quad \frac{2V_m \cos \alpha}{\pi} = R_a I_{a,r} + K' \omega_m \quad \text{"assume constant flux"}$$

$$\frac{2(230\sqrt{2})}{\pi} \cos(145^\circ) = 2(11.6) + 1.25 \omega_m$$

solve for ω_m

$$\omega_m = -154.3 \text{ r/sec}$$

Problem 2

$$V_{a,r} = R_a I_{a,r} + K' \omega_{m,r}$$

$$I_{a,r} = \frac{V_{a,r} - K' \omega_{m,r}}{R_a} = \frac{230 - 2 \left(1000 \frac{\pi}{30} \right)}{0.4217} = 48.76 \text{ A.}$$

" $\alpha = 0^\circ$ "

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2(240\sqrt{2})}{\pi} \cos(0^\circ) = 216.1 \text{ V} = R_a I_{a,r} + K' \omega_m$$

$$\omega_m = \frac{216.1 - 0.4217(48.76)}{2}$$

$$\omega_m = 97.77 \text{ r/sec} \quad \text{or} \quad n_m = 937.63 \text{ rpm}$$

$$\eta = \frac{P_a}{P_{in}} = \frac{E_a I_{a,r}}{V_a I_{a,r}} = \frac{K' \omega_m}{V_a} = \frac{2(97.77)}{216.1} =$$

$$\eta = 90.44 \%$$

" $\alpha = 20^\circ$ "

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2(240\sqrt{2})}{\pi} \cos 20^\circ = 203 \text{ V} = R_a I_{a,r} + K' \omega_m$$

$$\omega_m = \frac{203 - 0.4217(48.76)}{2} =$$


$$\omega_m = 91.22 \text{ r/sec} \quad \text{or} \quad n_m = 871.08 \text{ rpm}$$

$$\eta = \frac{P_a}{P_{in}} = \frac{K' \omega_m}{V_a} = \frac{2(91.22)}{203} =$$

$$\eta = 89.88 \%$$


Problem 3

$C_a = 1.0 p_u$

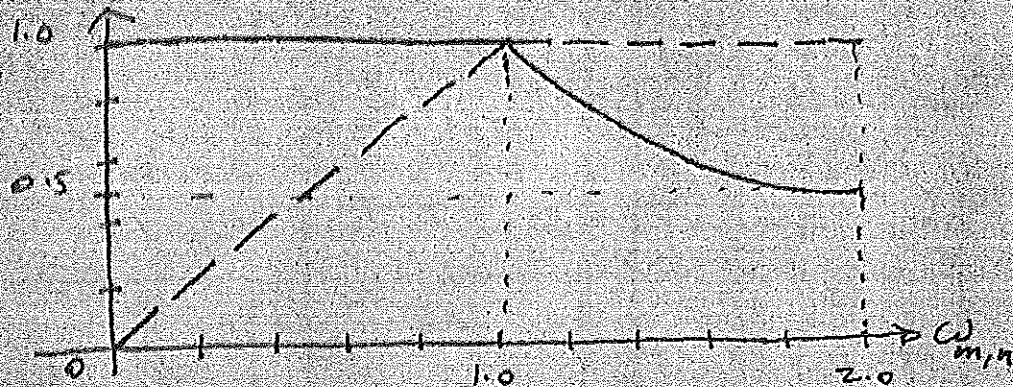

———— $T_{dyn} + A_{dyn}$
 - - - - $P_{dyn} + E_{dyn}$

$C_a = 1.2 p_u$

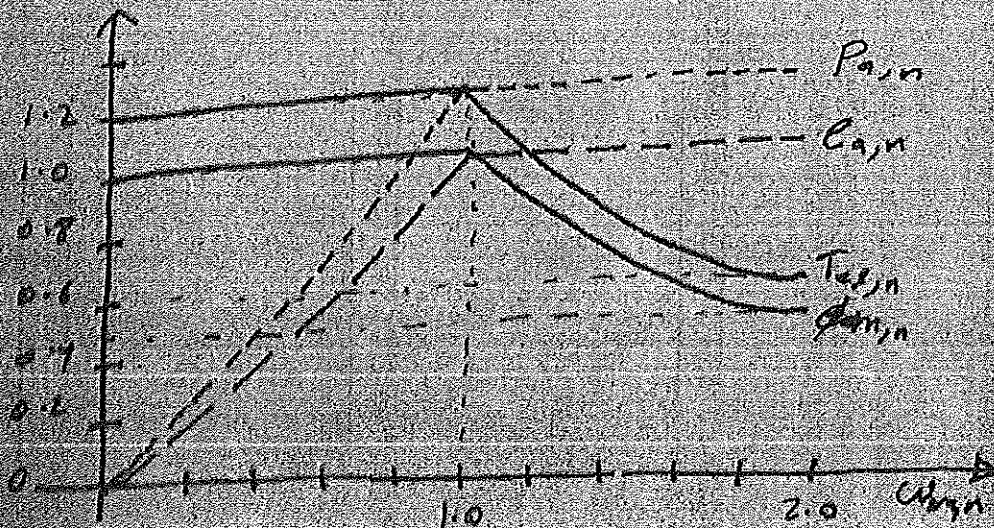

Problem 4

$$\textcircled{1} \quad V_{a,r} = R_a I_{a,r} + k' \omega_{m,r}$$

$$500 = 0.052 I_{a,r} + k' \left(1250 \frac{\pi}{30} \right)$$

$$500 = 0.052 I_{a,r} + 130.9 k' \dots \textcircled{1}$$

$$T_{\text{el},r} = k' I_{a,r} = \frac{P_{a,r}}{\omega_{m,r}} = \frac{250(746)}{130.9}$$

$$k' I_{a,r} = 1424.8 \dots \textcircled{2}$$

$$\text{Solve } \textcircled{1} + \textcircled{2} \Rightarrow k' = 3.6653 \text{ V/(r/sec)}$$

$$I_{a,r} = 388.73 \text{ A}$$


$$\textcircled{2} \quad T_{\text{el}} = k' I_a$$

$$I_a = \frac{V_a - k' \omega_m}{R_a}$$

$$T_{\text{el}} = \frac{k'}{R_a} \left[V_a - k' \omega_m \right]$$

$\frac{3\sqrt{3} V_m \cos \alpha}{\pi}$
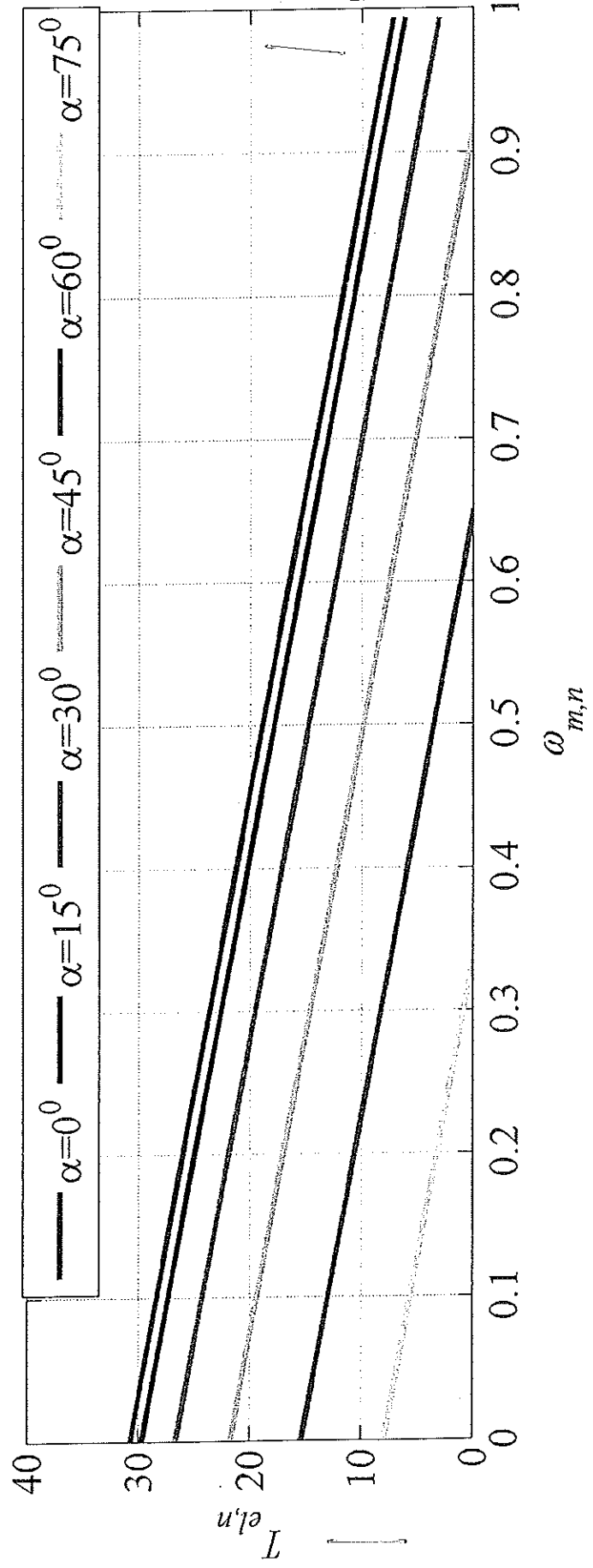
$$T_{\text{el}} = 4378.8 \text{ Wsd} - 258.35 \omega_m$$




$$\textcircled{2.} \quad \frac{3\sqrt{3} V_m}{\pi} \cos \alpha = V_{a,r}$$

$$\frac{3\sqrt{3} \left(\sqrt{\frac{2}{3}} 460 \right)}{\pi} \cos \alpha = 500$$

$$\alpha = 36.4^\circ$$

$$\textcircled{3.} \quad V_a = \frac{3\sqrt{2} \left(\sqrt{\frac{2}{3}} 460 \right)}{\pi} \cos \alpha = 0.088 (153.71) + 7.646 \omega_m$$

$$\alpha = \cos^{-1} \left[0.0218 + 0.0042 \omega_m \right]$$

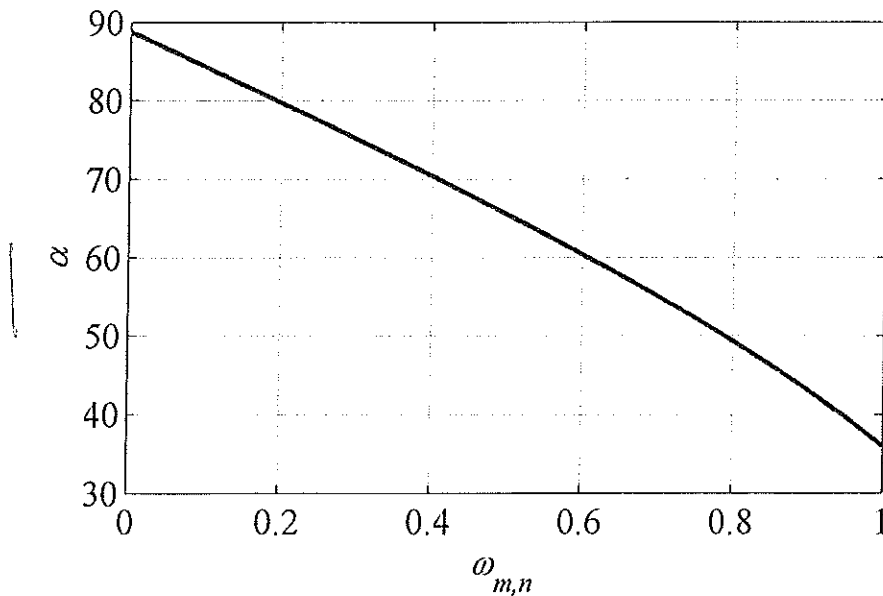

problem 5

speed controller

$$K_1 = 23\omega_n T - B$$

$$K_2 = J\omega_n^2$$

$$\det z = 1/\sqrt{2}$$

$$T = 0.0607, \quad B = 0.0869, \quad \omega_n = 2\pi(5000)$$

$$K_1 = 269.6, \quad K_2 = 5.99 \times 10^5$$

current controller

$$K_1 = 23\omega_n L_a - R_a$$

$$K_2 = \omega_n^2 L_a$$

$$\det z = 1/\sqrt{2}$$

$$R_a = 4\Omega, \quad L_a = 72 \text{ mH}, \quad \omega_n = 2\pi(1000)$$

$$K_1 = 635.8, \quad K_2 = 2.84 \times 10^9$$

flux controller

$$K_1 = 23\omega_n L_f$$

$$K_2 = \omega_n^2 L_f$$

$$\det z = 1/\sqrt{2}$$

$$L_f = 78 \text{ mH}, \quad \omega_n = 2\pi(2000)$$

$$K_1 = 1386.2, \quad K_2 = 1.23 \times 10^7$$

problem 6

$$V_{a1} = R_a I_a + \cancel{E_{a1}}^{A_0} = 0.3(25) = 7.5 \text{ V}$$

$$\omega_m = 0$$

$$V_{a2} = R_a I_a + E_{a2} = 0.3(25) + 60(2000)(0.00167) = 207.9 \text{ V}$$

$$\omega_{m2} = 2000 \left(\frac{\pi}{30} \right)$$

$$\delta_1 = \frac{7.5}{220} = 0.0341$$

$$\delta_2 = \frac{207.9}{220} = 0.943$$

problem 7

$$\eta = \frac{P_{out}}{P_{in}} = 0.785$$

$$\frac{746 \times 1}{P_{in}} = 0.785$$

$$P_{in} = V_{air} I_{air} = 950.32$$

$$I_{air} = \frac{950.32}{10} = 95.032 \text{ A}$$

$$|V_a| = (1.5 I_{air}) R_a = 1.5 (95.032) (0.053) = 7.56 \text{ V}$$

$$\omega_m = 0$$

$$|V_a| = (1.5 I_{air}) R_a + k' \omega_m = 1.5 (95.032) + 0.0191 (0.4) \left(\frac{12500 \pi}{30} \right)$$

$$\omega_m = 0.4$$

$$= 9.56 \text{ V}$$

$$s| = \frac{7.56}{23} = 0.33$$

$$\omega_m = 0.0 \text{ p.u.}$$

$$s| = \frac{9.56}{23} = 0.41$$

$$\omega_m = 0.4 \text{ p.u.}$$