


# Electrical Machine Drive and Special Machines

ENEE5303

# Introduction

- A modern variable speed system has four components:
  1. Power converters or drive circuits
  2. Electric machines
  3. Control system
  4. Load


- A Block diagram of an electric drive

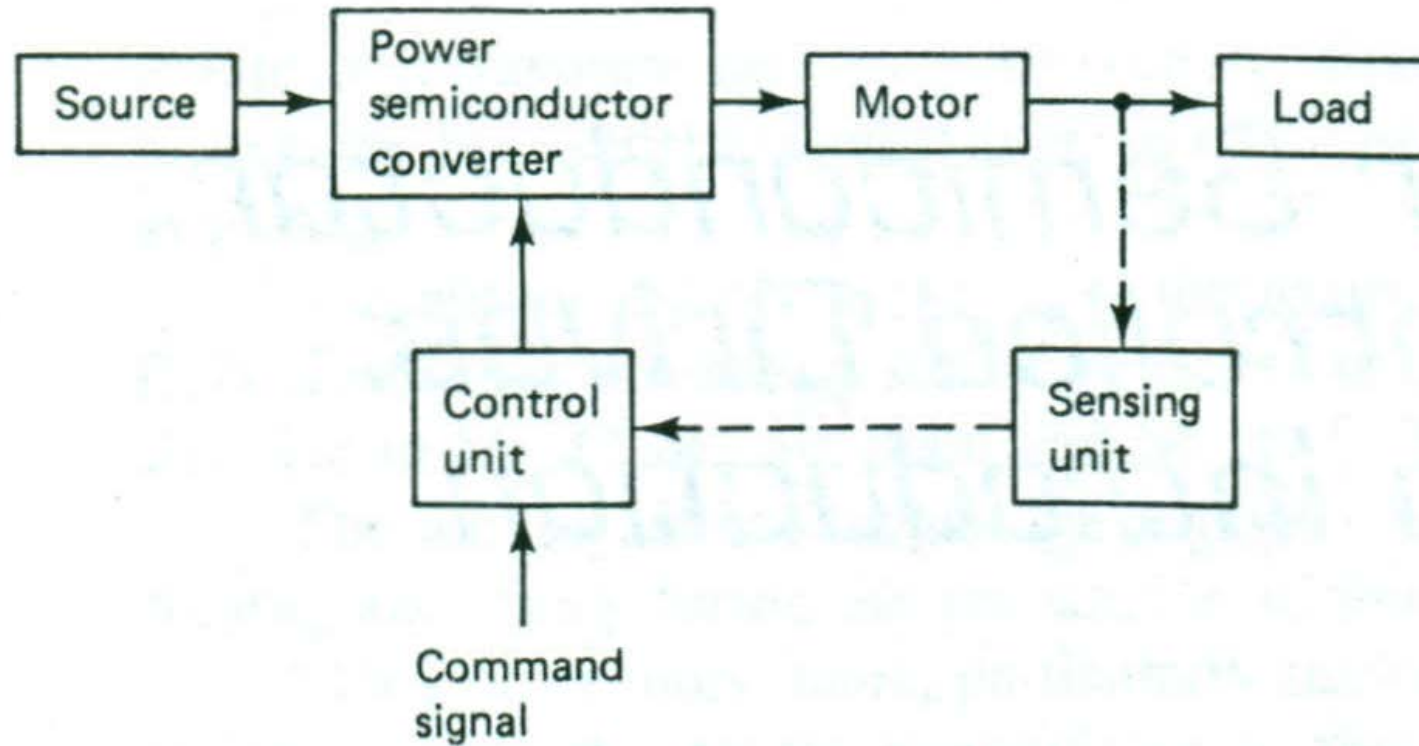

# 1. Power Converters
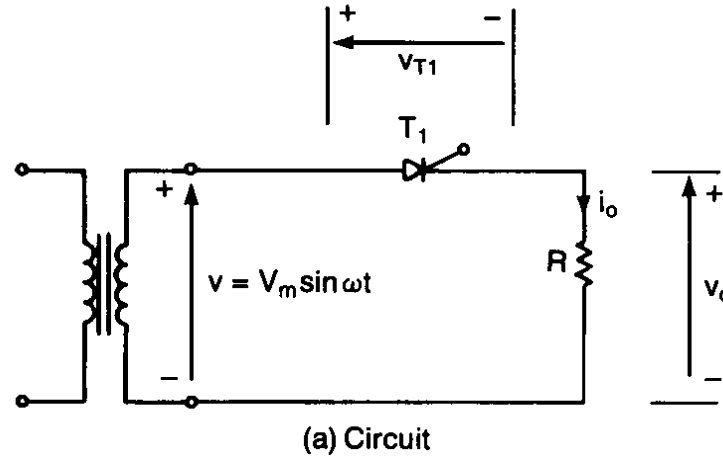
## 1.1 Controlled rectifiers

- Types of controlled rectifiers (single and three-phase)
  - Half-wave
  - Semiconverter
  - Full-wave
  - Dual
- They are fed from 1-phase or 3-phase AC main supply and provide a variable DC output voltage for control of DC motors.
- or sometimes input DC supply to the inverters in the case of AC machines





Single-phase:


Half-wave controlled rectifier

The average DC output voltage is given by:

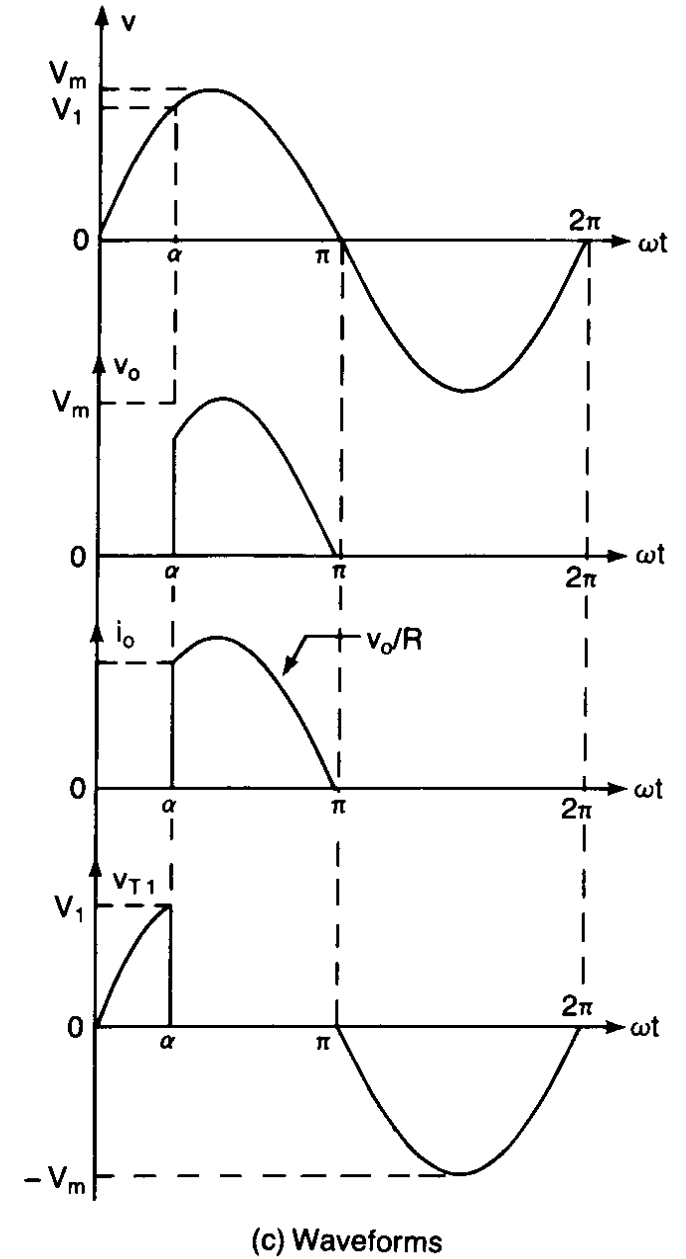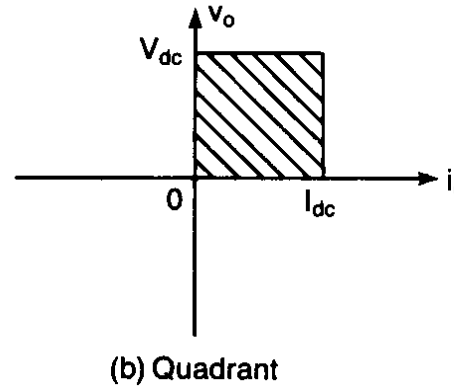
$$V_{DC} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$






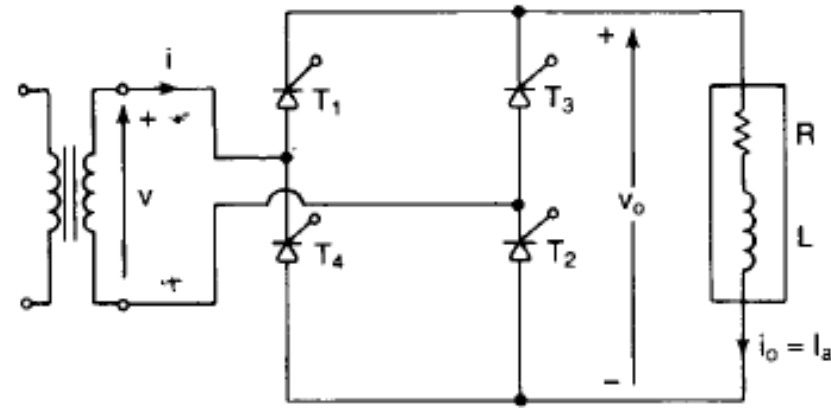

(a) Circuit

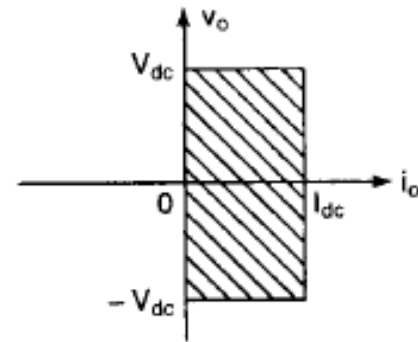

(b) Quadrant

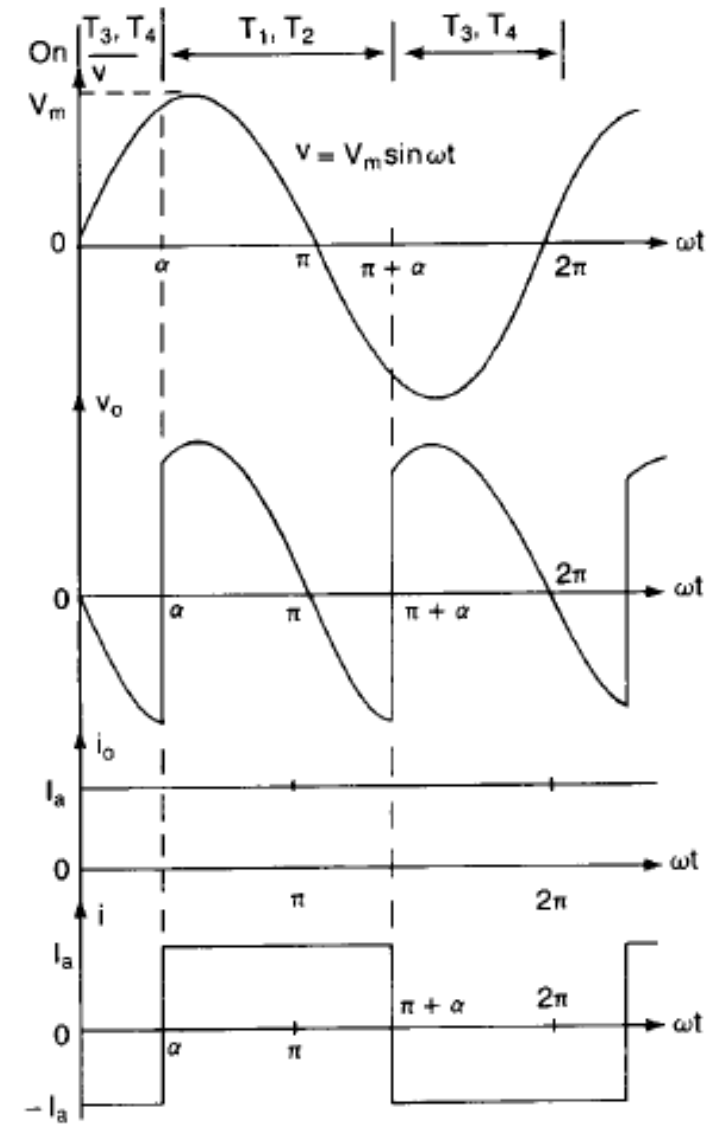

(c) Waveforms

*Single-phase:*

*Full-wave controlled rectifier*


The average DC output voltage is given by:

$$V_{DC} = \frac{2V_m}{\pi} \cos \alpha$$


*Single-phase:  
Dual converter*

The average DC output voltage is given by:

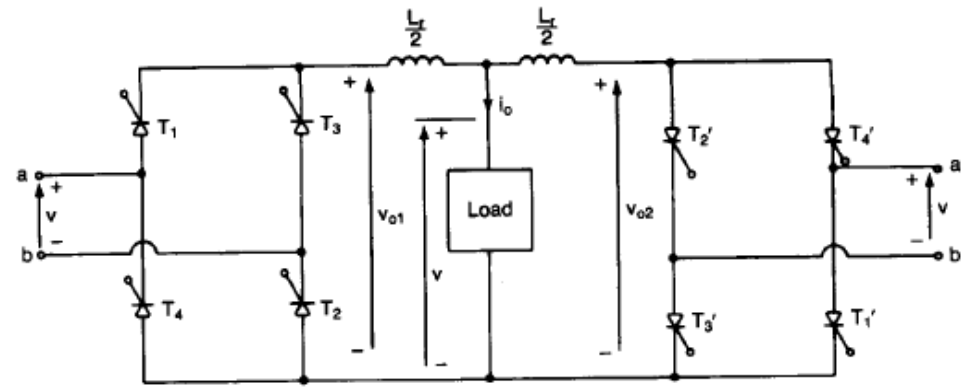
$$V_{DC} = \frac{2V_m}{\pi} \cos \alpha$$



(a) Circuit

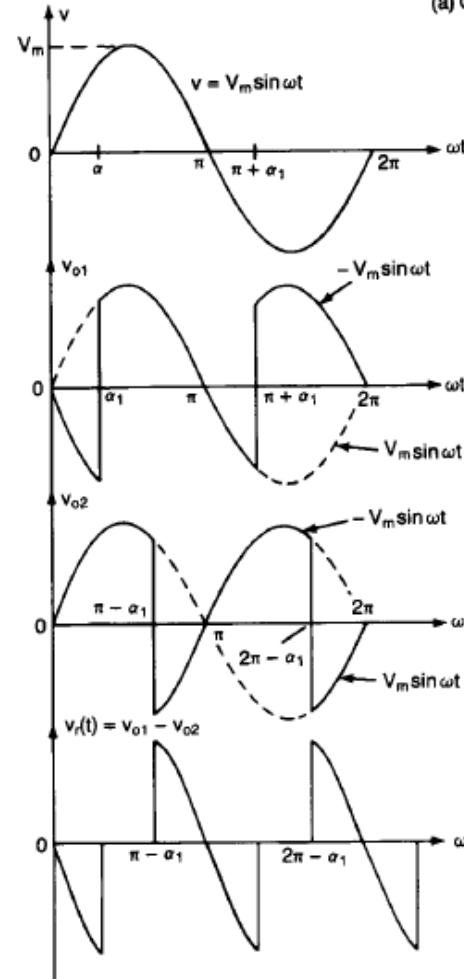


(b) Waveforms

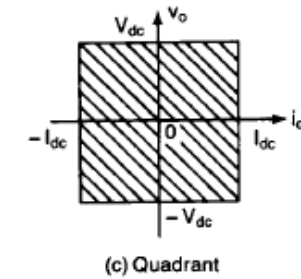

(c) Quadrant



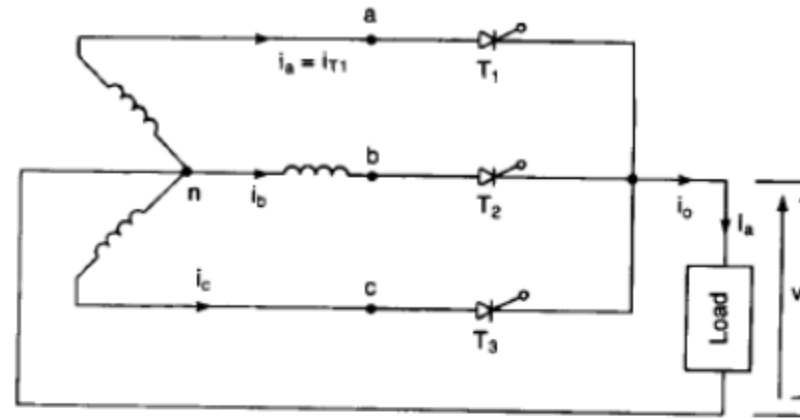


(a) Circuit

Three-phase:


Half-wave controlled rectifier

The average DC output voltage is given by:
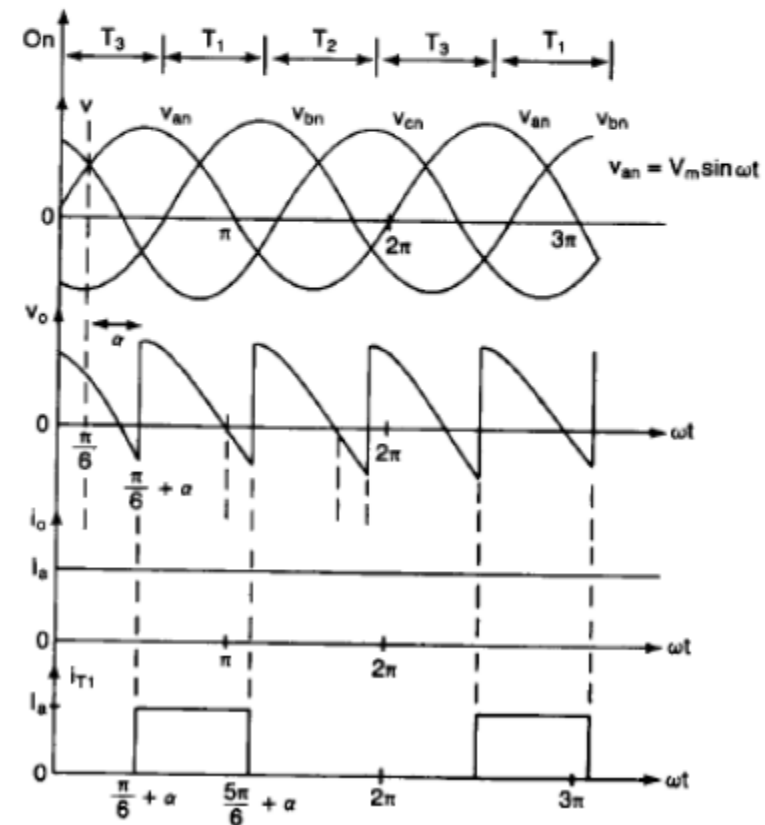
$$V_{DC} = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha$$



(c) For inductive load

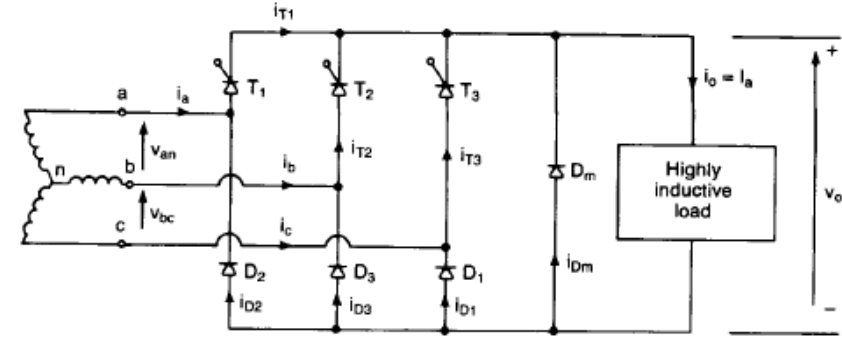


(a) Circuit

Three-phase:


Semiconverter

The average DC output voltage is given by:
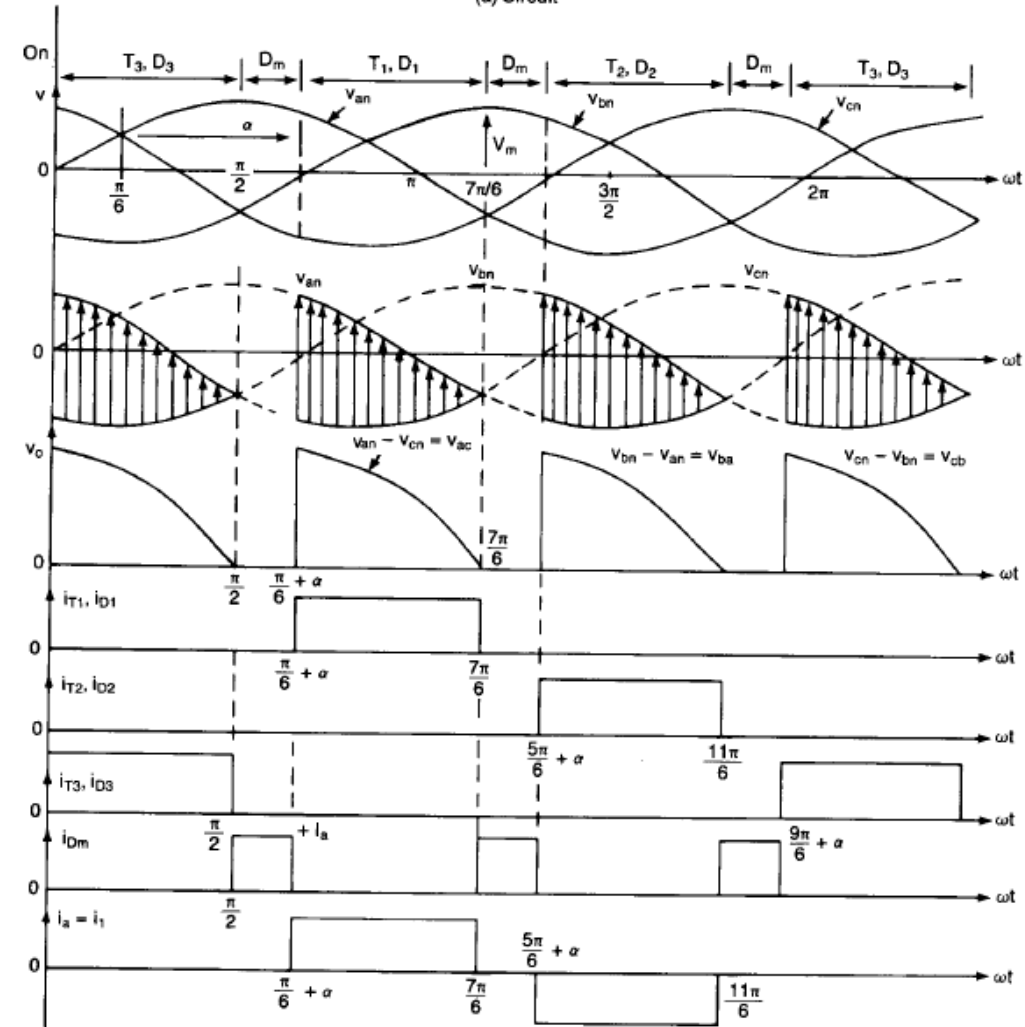
$$V_{DC} = \frac{3\sqrt{3}}{2\pi} V_m (1 + \cos \alpha)$$



(b) Waveforms for  $\alpha = 90^\circ$

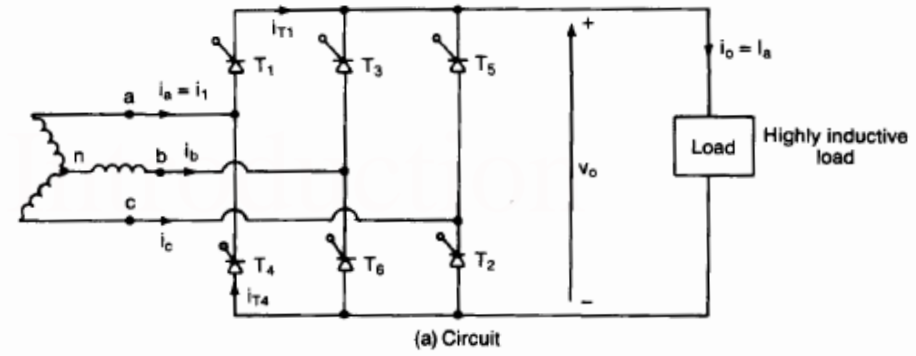



Three-phase:

Full-wave controlled rectifier

The average DC output voltage is given by:
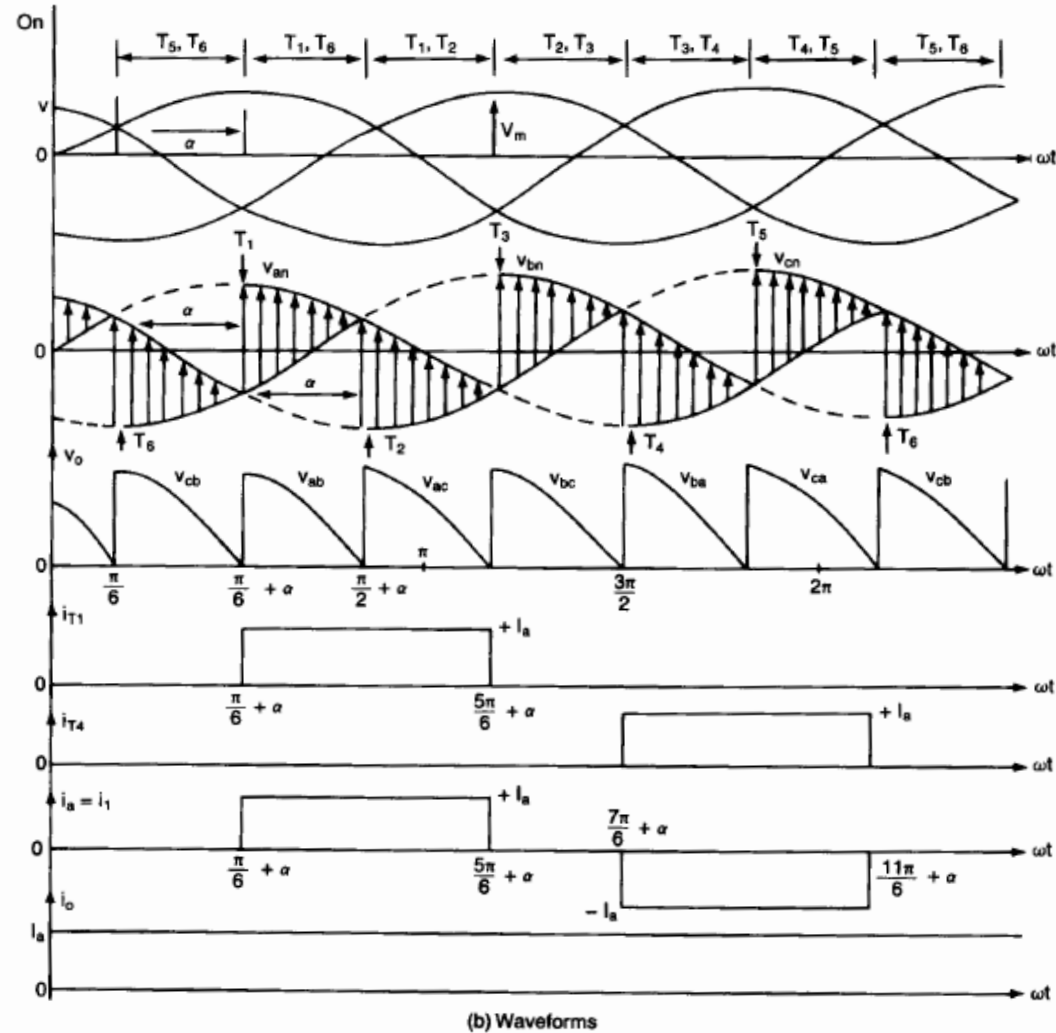
$$V_{DC} = \frac{3\sqrt{3}}{\pi} V_m \cos \alpha$$



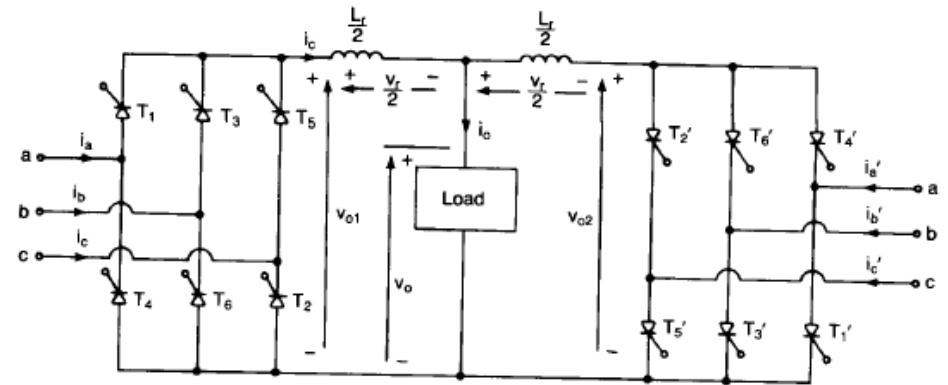


(a) Circuit

Three-phase:

Dual converter

The average DC output voltage is given by:
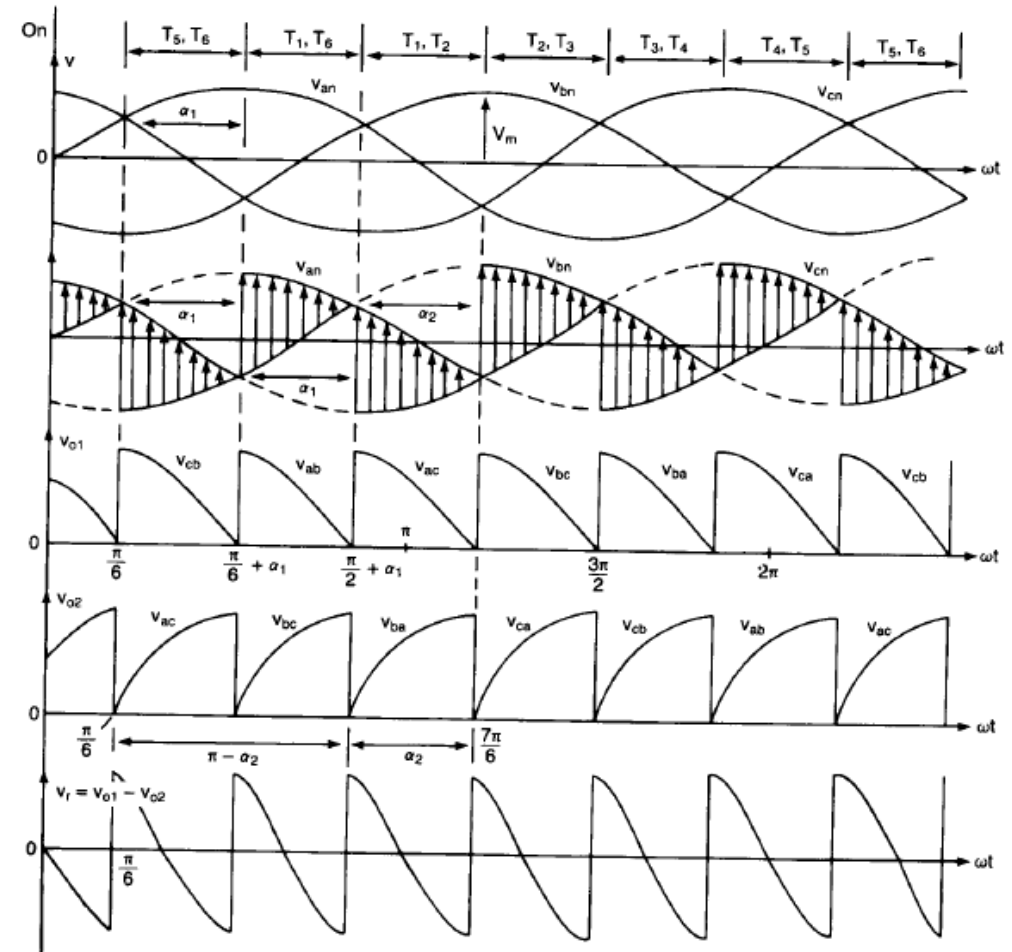
$$V_{DC} = \frac{3\sqrt{3}}{\pi} V_m \cos \alpha$$



(b) Waveforms