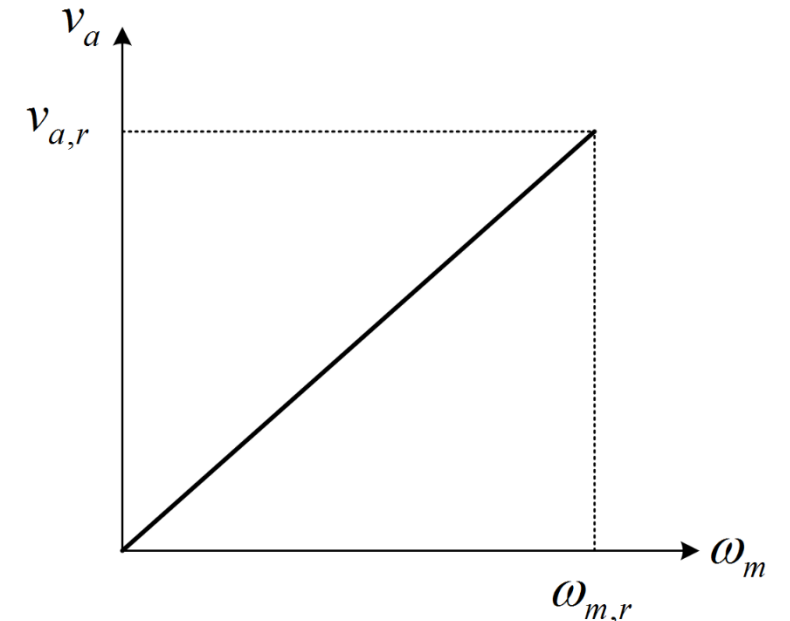


- Principle of DC machine drive

$$v_a = R_a i_a + K \phi_f \omega_m \Rightarrow \omega_m = \frac{v_a - R_a i_a}{K \phi_f}$$


- Armature control: Ideal for speeds lower than motor's rated speed,  $\omega_{m,r}$ .

$$\phi_f = \phi_{f,r} \Rightarrow \omega_m = \frac{v_a - R_a i_a}{K \phi_{f,r}} \approx \frac{v_a}{K \phi_{f,r}} \Rightarrow \omega_m \propto v_a$$



- Field control: Ideal for speeds above than motor's rated speed,  $\omega_{m,r}$ .
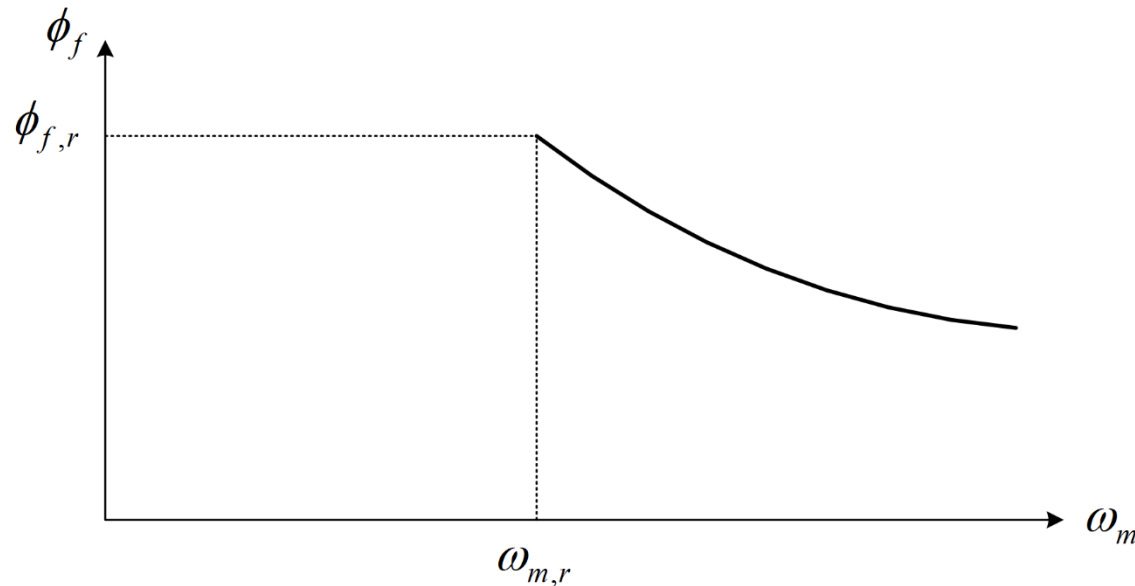
$$v_a = v_{a,r} \Rightarrow \omega_m \approx \frac{v_{a,r}}{K\phi_f} \Rightarrow \phi_f \propto \frac{1}{\omega_m} \Rightarrow \phi_f = \phi_{f,r} \frac{\omega_{m,r}}{\omega_m}$$



- Armature and Field control: Assume that  $i_a = i_{a,r}$

When  $\omega_m \leq \omega_{m,r}$

$$\phi_f = \phi_{f,r}$$

$$T_{el} = K \phi_{f,r} i_{a,r} = \text{Constant}$$

$$P_a = K \phi_{f,r} i_{a,r} \omega_m$$

Constant torque region





When  $\omega_m \geq \omega_{m,r}$

$$\phi_f = \phi_{f,r} \frac{\omega_{m,r}}{\omega_m}$$

$$T_{el} = K \phi_{f,r} \frac{\omega_{m,r}}{\omega_m} i_{a,r}$$

$$P_a = K \phi_{f,r} i_{a,r} \omega_{m,r} = \text{Constant}$$

Constant power region

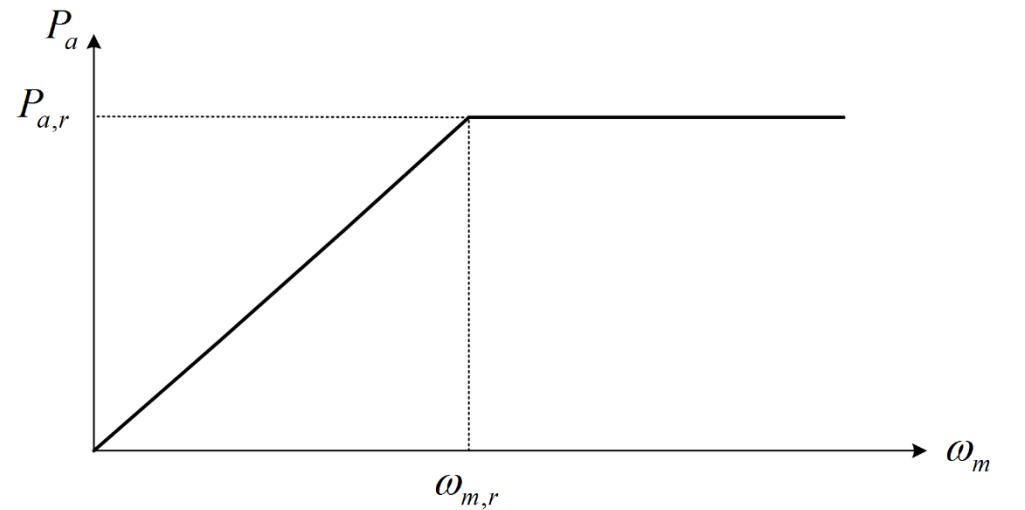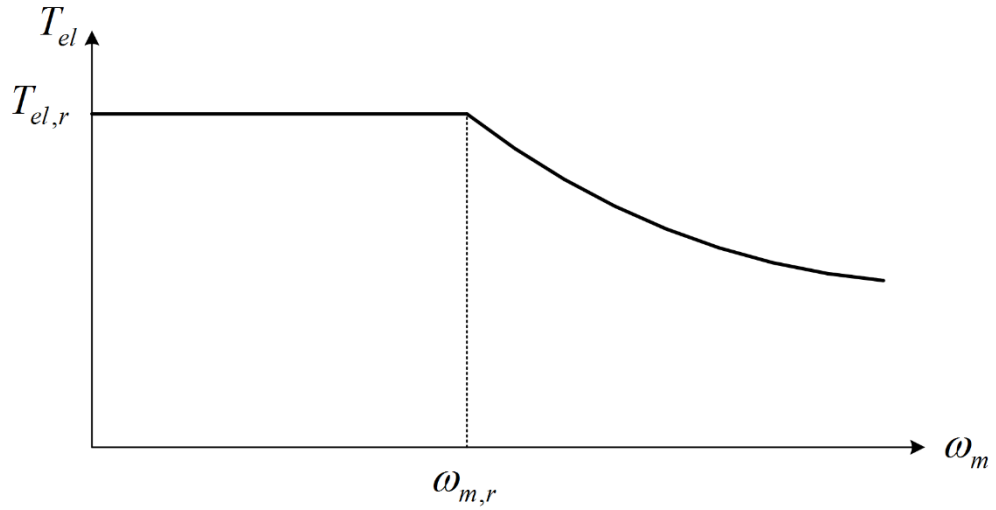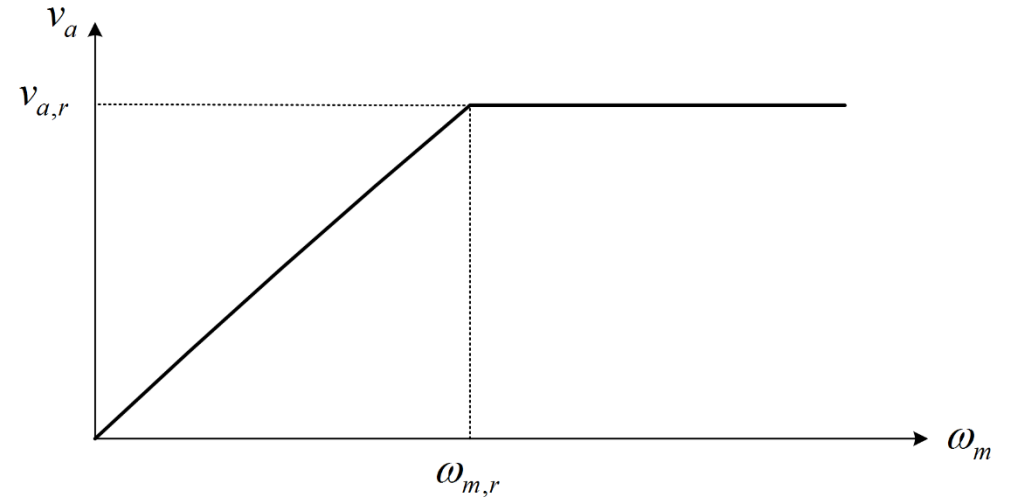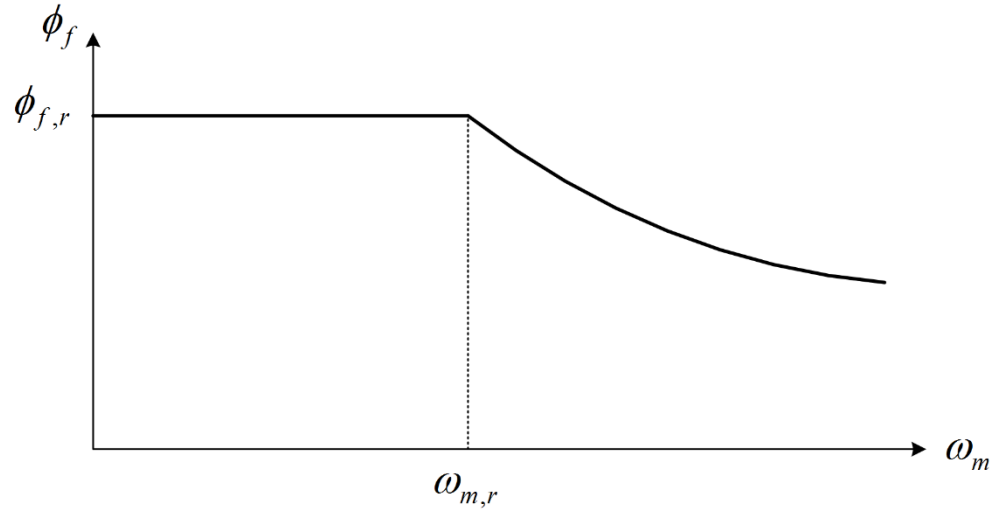

- Braking and 4-quadrant operation

- Braking

The machine is made to work as a generator producing a torque opposite to the motoring torque

$$T_{el} = T_l + J \frac{d\omega_m}{dt}$$

$$\omega_m > 0 \ \& \ (T_{el} - T_l) > 0 \Rightarrow \text{Forward regeneration}$$

$$T_{el} = T_l + J \frac{d\omega_m}{dt} \Rightarrow \Delta t = J \frac{\Delta\omega_m}{T_{el} - T_l}$$

$\Delta t$ : stopping time

Why do we need braking?

1. Reducing  $\Delta t$
2. Achieving quick and smooth stops
3. Achieving accurate stops
4. Holding the speed within safe limit

Braking methods:

1. *Regenerative braking*: generated electrical power is usefully employed
2. *Dynamic braking*: it is an inefficient way of braking
3. *Plugging braking*: it is a highly inefficient way of braking


- 4-quadrant operation

FM: Forward Motoring

FR: Forward Regeneration

RM: Reverse Motoring




RR: Reverse Regeneration

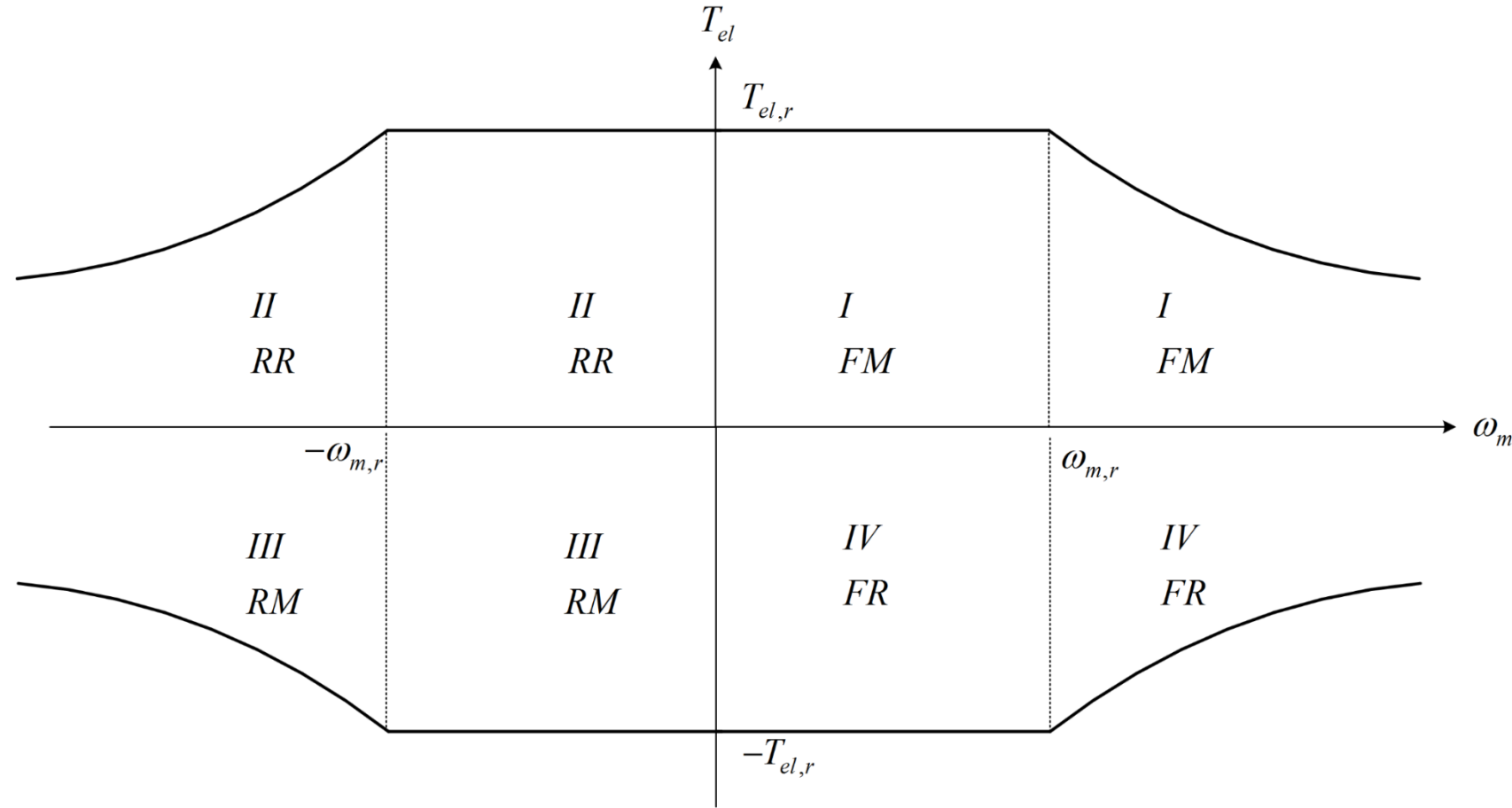


Function	Quadrant	Speed	Torque	Voltage	Current	Power
FM	I	+	+	+	+	+
FR	IV	+	-	+	-	-
RM	III	-	-	-	-	+
RR	II	-	+	-	+	-



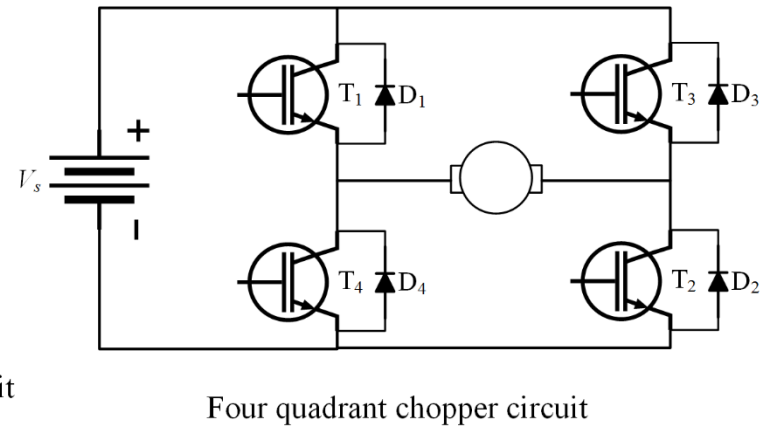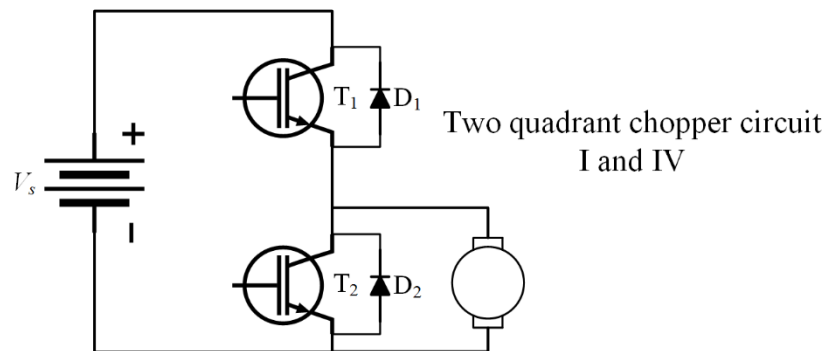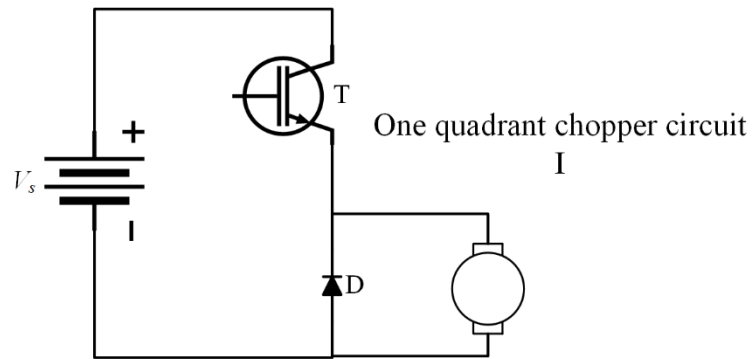- DC machine drive using chopper circuits



## Block diagram of control system

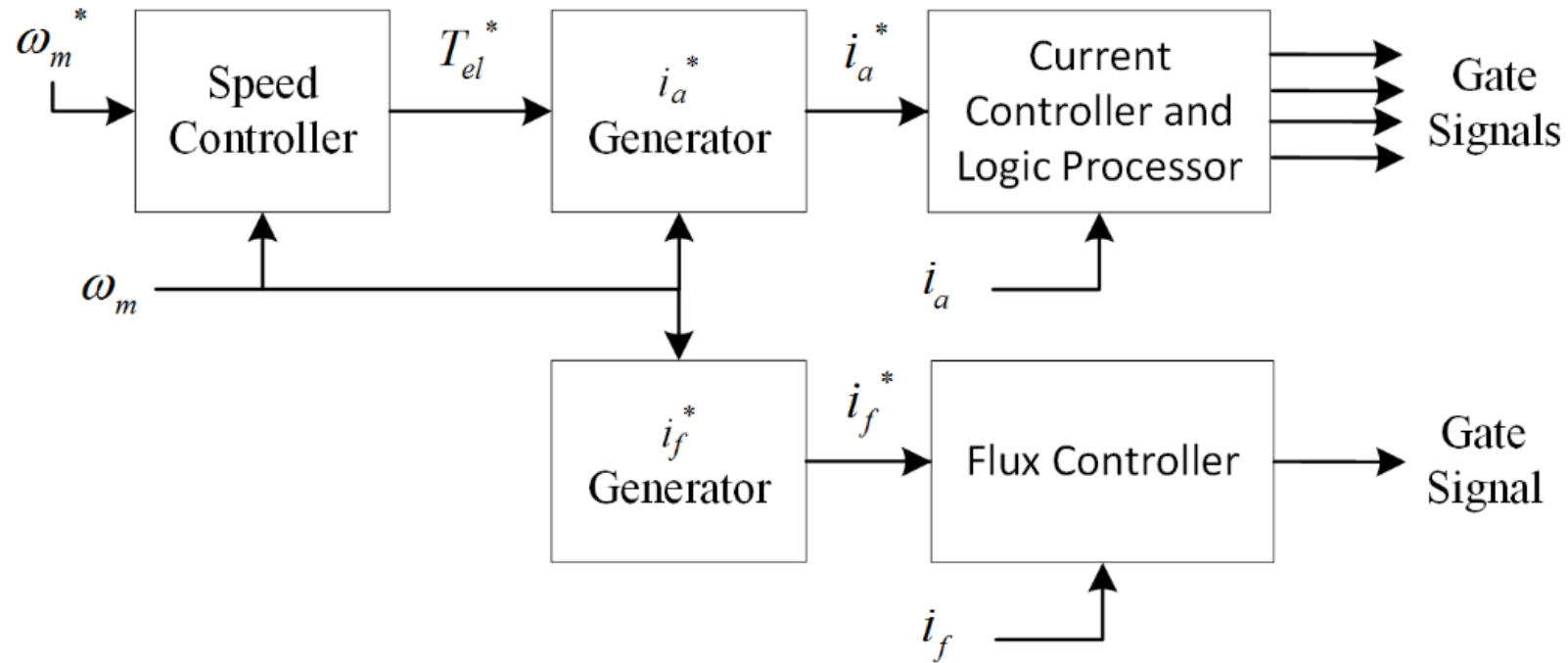

- $i_f^*$  Generator

$$\omega_m \leq \omega_{m,r} \Rightarrow i_f = i_{f,r}$$

$$\omega_m > \omega_{m,r} \Rightarrow i_f = i_{f,r} \frac{\omega_{m,r}}{\omega_m}$$

- $i_a^*$  Generator


$$T_{el} = K \phi_f i_a \Rightarrow i_a^* = \frac{T_{el}^*}{K \phi_f}$$

$$\omega_m \leq \omega_{m,r} \Rightarrow \phi_f = \phi_{f,r} \Rightarrow i_a^* = \frac{1}{K \phi_{f,r}} T_{el}^*$$


$$\omega_m > \omega_{m,r} \Rightarrow \phi_f = \phi_{f,r} \frac{\omega_{m,r}}{\omega_m} \Rightarrow i_a^* = \frac{\omega_m}{K \phi_{f,r} \omega_{m,r}} T_{el}^*$$

- Speed Controller: It is designed using Newton's 2<sup>nd</sup> law
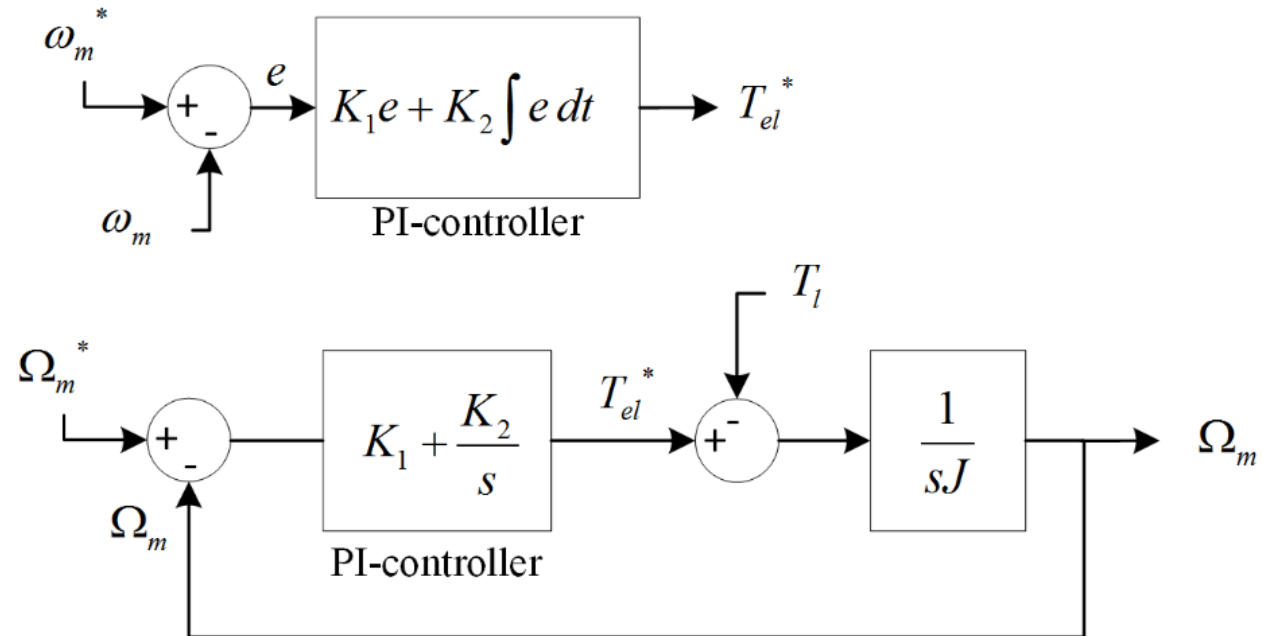
$$T_{el} = T_l + J \frac{d\omega_m}{dt} \xrightarrow{\text{Laplace}} T_{el} = T_l + Js\Omega_m$$



- $T_1: T_l = 0$

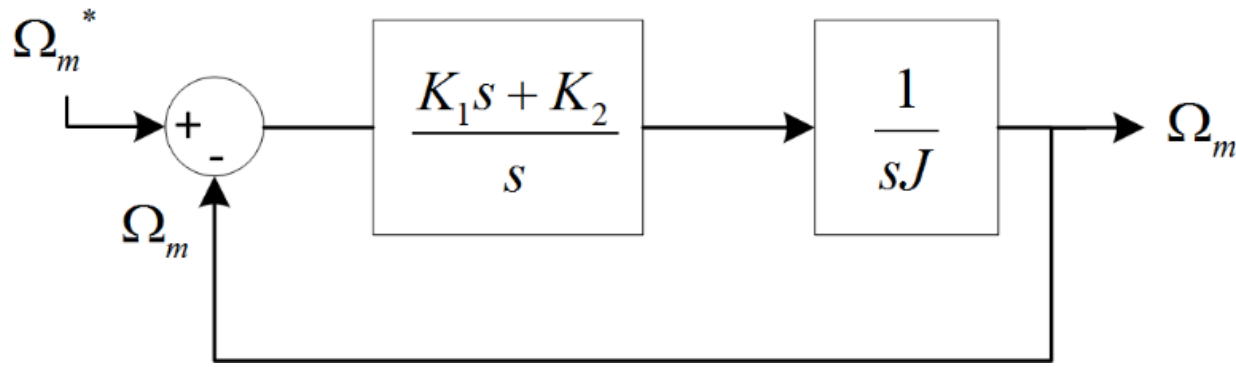

$$T_1 = \frac{G_1}{1 + G_1 H_1};$$

$$G_1 = \frac{K_1 s + K_2}{J s^2}; \quad H_1 = 1$$

$$T_1 = \frac{K_1}{J} \frac{s + \frac{K_2}{K_1}}{\underbrace{s^2 + \frac{K_1}{J}s + \frac{K_2}{J}}_{s^2 + 2\xi\omega_n s + \omega_n^2}};$$


$\xi$ : Damping ratio,  $\omega_n$ : Natural frequency

$\xi < 1 \rightarrow$  Under-damped

$\xi = 1 \rightarrow$  Critically damped

$\xi > 1 \rightarrow$  Over-damped

- $T_2: \Omega_m^* = 0$

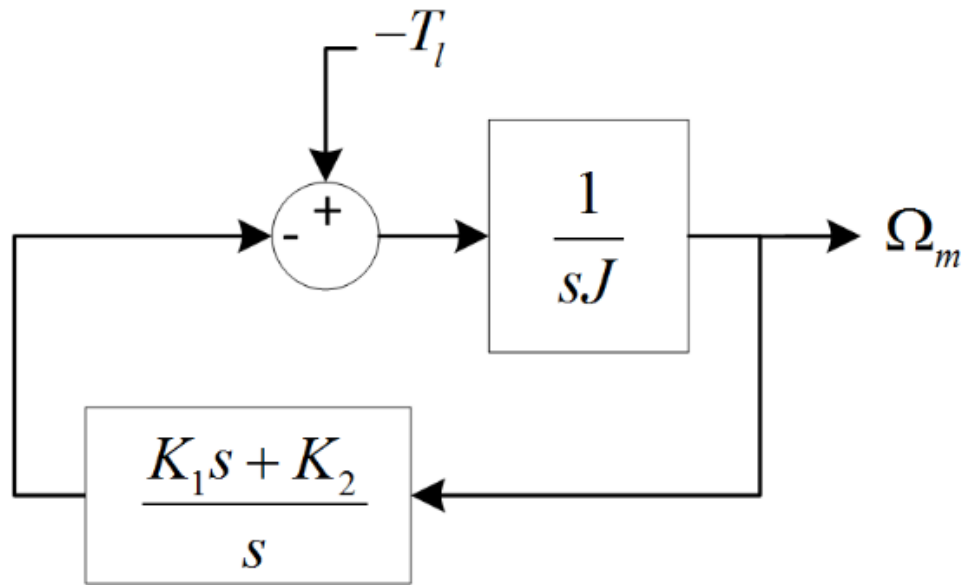

$$T_2 = \frac{-G_2}{1 + G_2H_2};$$

$$G_2 = \frac{1}{Js}; \quad H_2 = \frac{K_1s + K_2}{s}$$

$$T_2 = -\frac{1}{J} \frac{s}{s^2 + \frac{K_1}{J}s + \frac{K_2}{J}};$$


$$\Omega_m = T_1 \Omega_m^* + T_2 T_l$$

$$\omega_{m,ss} = \lim_{s=0} s \Omega_m = \lim_{s=0} s T_1 \Omega_m^* + \lim_{s=0} s T_2 T_l$$

Assume  $\omega_m^* = Au(t)$ ,  $T_l = Bu(t)$


$$\Omega_m^* = \frac{A}{s}, T_l = \frac{B}{s}$$
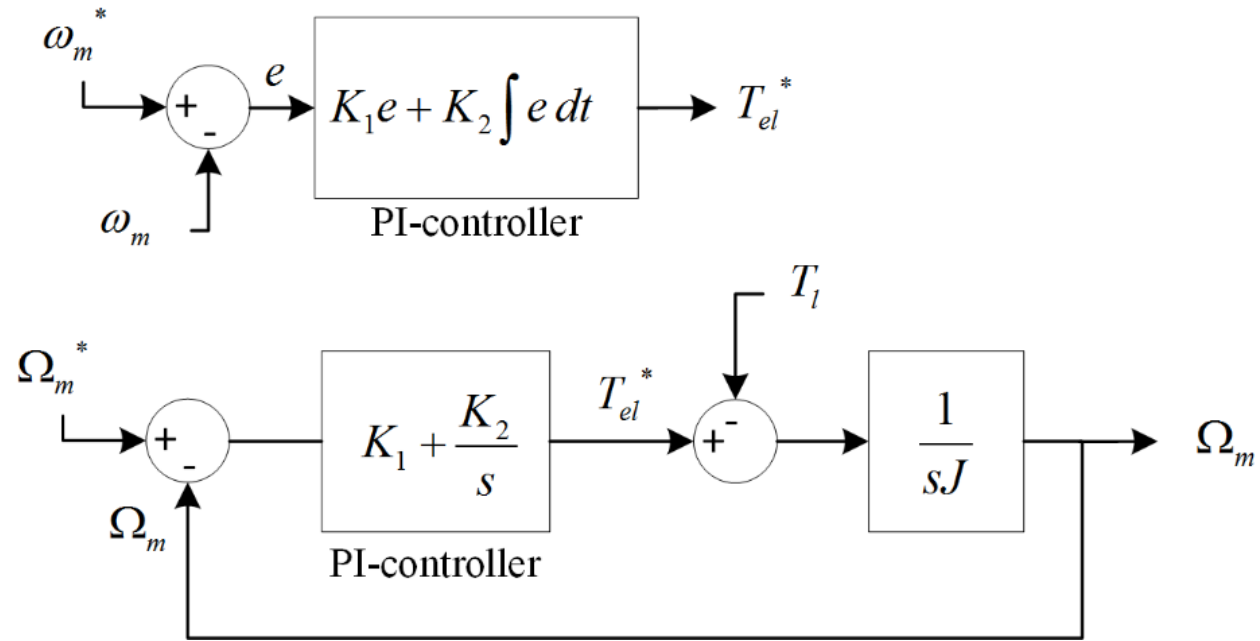
$$\omega_{m,ss} = A \lim_{s=0} T_1 + B \lim_{s=0} T_2 = A$$



- Current Controller and Logic Processor:

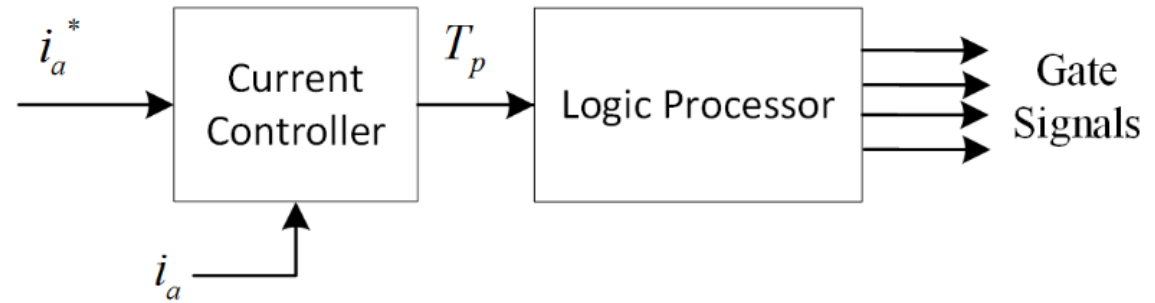- PWM current controller
- Hysteresis current controller



$T_p$  is called the on-time signal

The logic processor determines the quadrant of operation



$$T_p = 1 \rightarrow v_a = \pm V_s$$

$$T_p = 0 \rightarrow v_a = 0$$




- PWM current controller
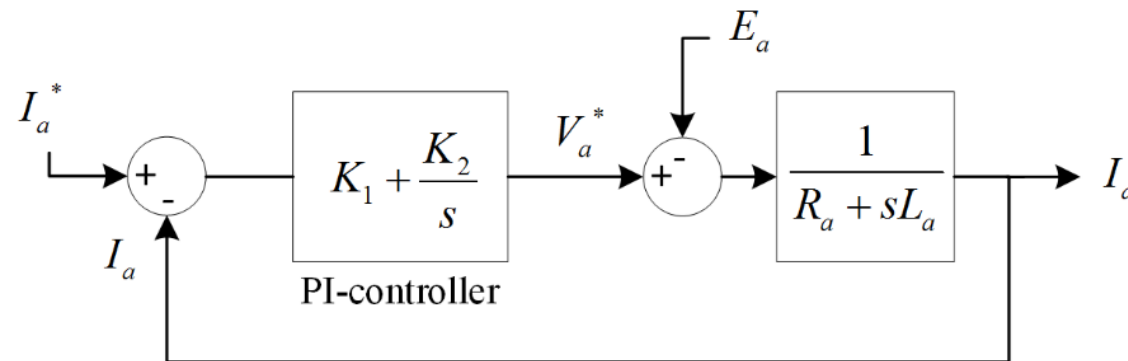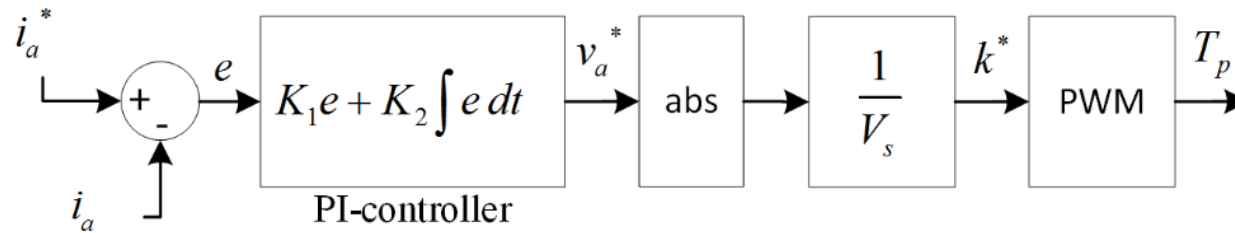
$$v_a = R_a i_a + L_a \frac{di_a}{dt} + e_a \xrightarrow{\text{Laplace}} V_a = (R_a + sL_a) I_a + E_a$$



$$I_a = T_1 I_a^* + T_2 E_a$$

$$T_1: E_a = 0$$

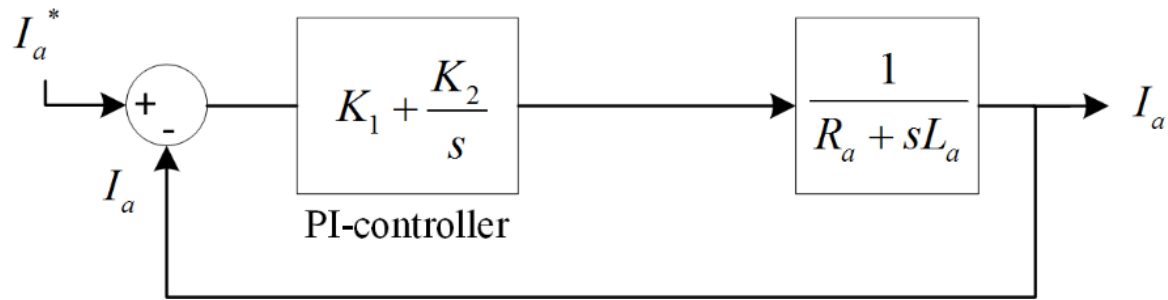

$$T_1 = \frac{G_1}{1 + G_1 H_1};$$

$$G_1 = \frac{K_1 s + K_2}{(R_a + sL_a)s}; \quad H_1 = 1$$

$$T_1 = \frac{K_1}{L_a} \frac{s + \frac{K_2}{K_1}}{\underbrace{s^2 + \left(\frac{K_1 + R_a}{L_a}\right)s + \frac{K_2}{L_a}}_{s^2 + 2\xi\omega_n s + \omega_n^2}};$$


$\xi$ : Damping ratio,  $\omega_n$ : Natural frequency

$\xi < 1 \rightarrow$  Under-damped

$\xi = 1 \rightarrow$  Critically damped

$\xi > 1 \rightarrow$  Over-damped



- Hysteresis current controller

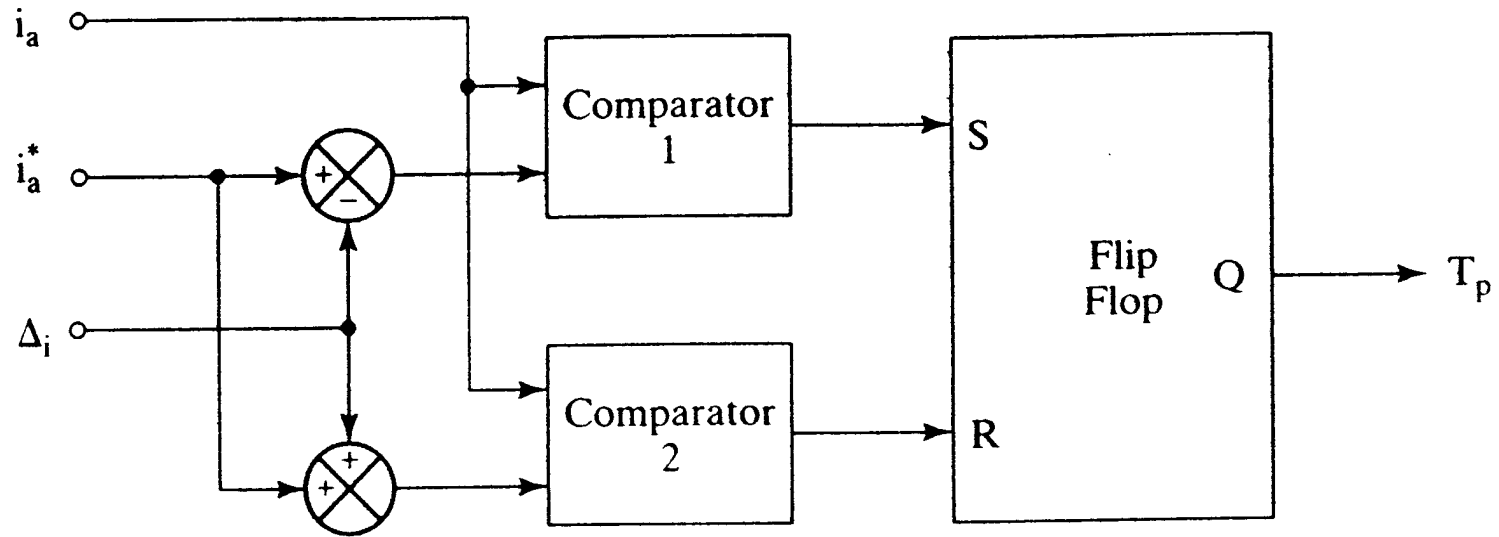

- Flux Controller
  - PWM flux controller
  - Hysteresis flux controller

- PWM flux controller
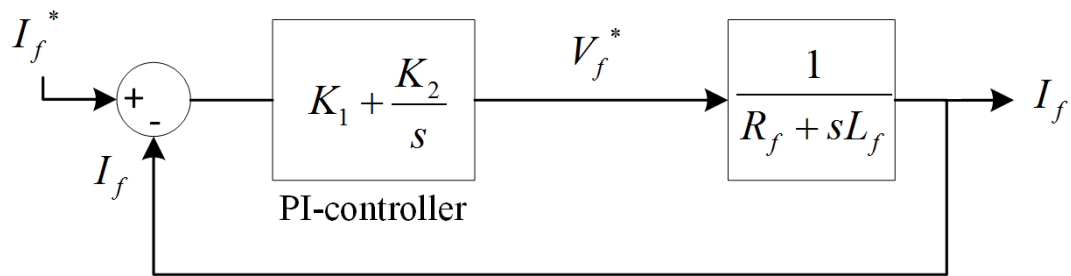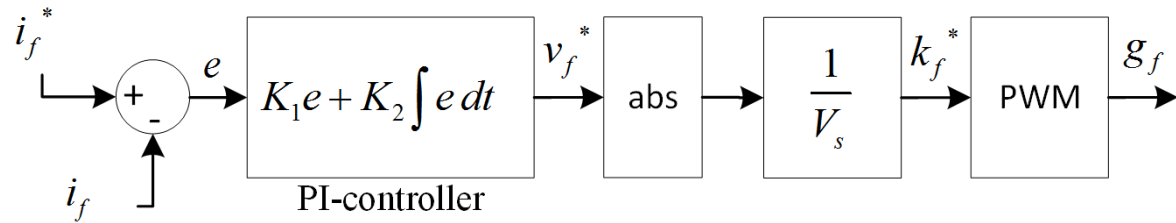
$$v_f = R_f i_f + L_f \frac{di_f}{dt} \xrightarrow{\text{Laplace}} V_f = (R_f + sL_f) I_f$$



$$T = \frac{G}{1 + GH};$$

$$G = \frac{K_1 s + K_2}{(R_f + sL_f)s}; \quad H = 1$$

$$T = \frac{K_1}{L_f} \frac{s + \frac{K_2}{K_1}}{s^2 + \left( \frac{K_1 + R_f}{L_f} \right) s + \frac{K_2}{L_f}};$$

$$s^2 + 2\xi\omega_n s + \omega_n^2$$