

Block diagram and transfer function



$$V_a = R_a \dot{C}_a + L_a \frac{d\dot{C}_a}{dt} + e_a$$

$$e_a = k \phi_f \omega_m = k' \omega_m$$

$$T_{ex} = k \phi_f C_a \dot{C}_a = k' C_a \dot{C}_a$$

$$T_{ex} = T_d + J \frac{d\omega_m}{dt}$$

t-domain

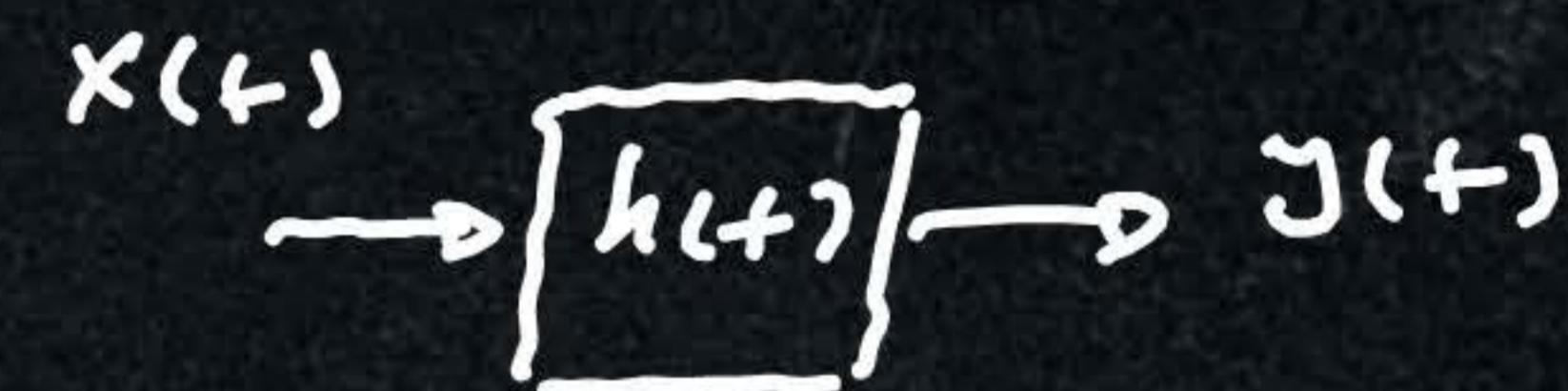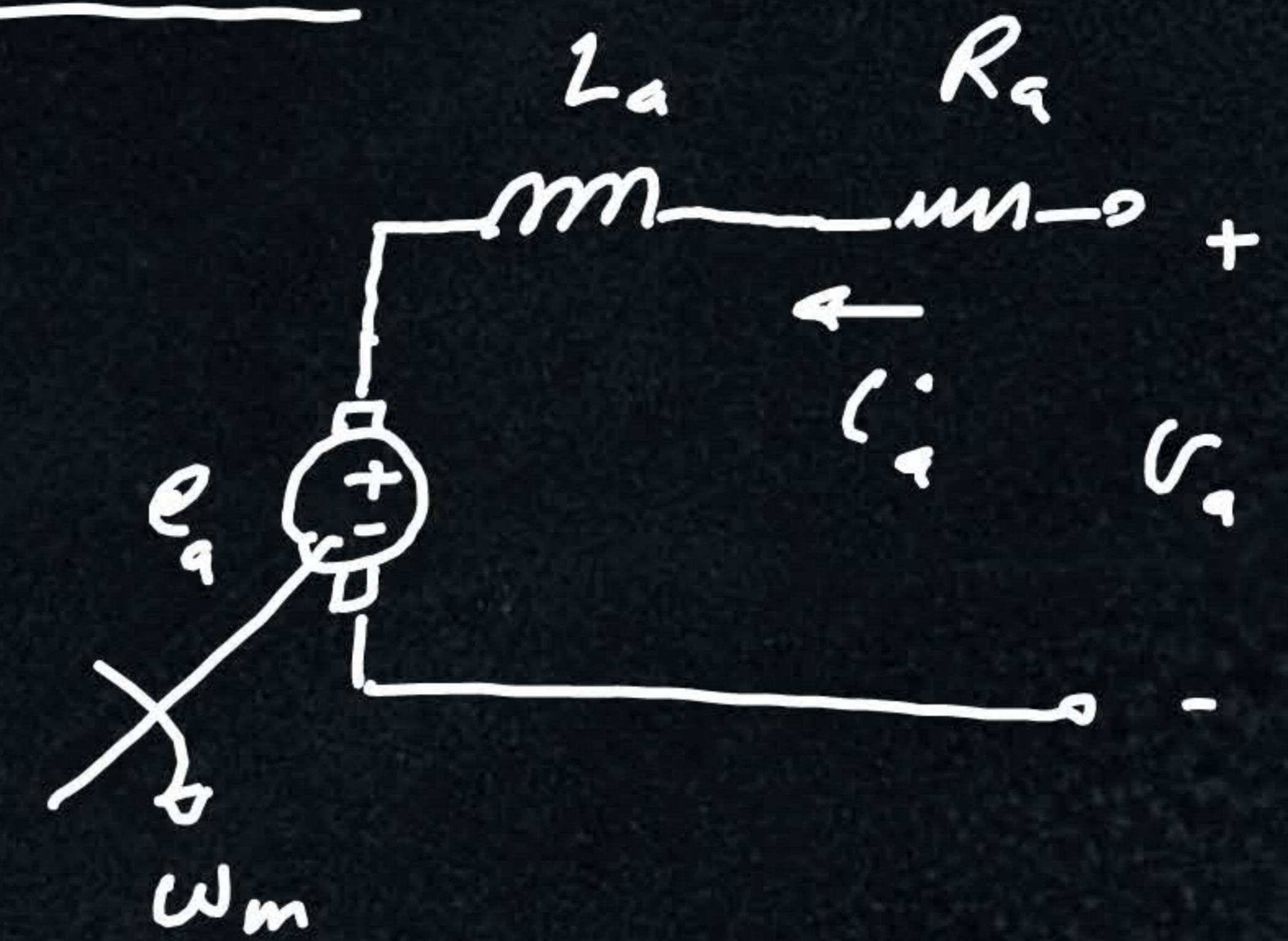

$$y(t) = x(t) \otimes h(t)$$

$$Y(s) = H(s) X(s)$$

Transfer
Function

$$V_a = R_a I_a + L_a \frac{dI_a}{dt} + E_a \xrightarrow{\mathcal{L}} V_a = (R_a + sL_a) I_a + E_a$$


$$E_a = k' \omega_m$$

$$\bar{T}_{qf} = k' l_a$$

$$T_{qf} = T_d + J \frac{d\omega_m}{dt}$$

$$\begin{aligned} & \xrightarrow{\mathcal{L}} E_a = k' \omega_m \\ & \xrightarrow{\mathcal{L}} \bar{T}_{qf} = k' I_a \end{aligned}$$
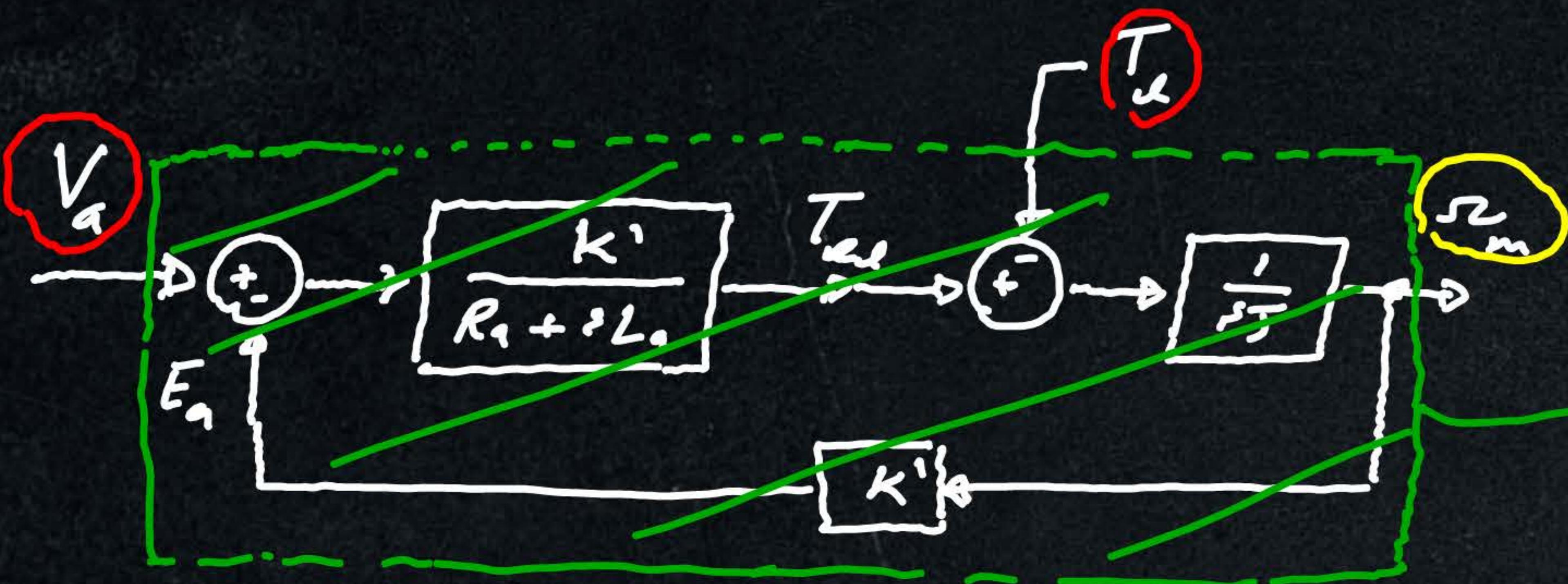
$$\xrightarrow{\mathcal{L}} T_{qf} = T_d + f J \omega_m$$



Block diagram
of DC machine
"constant flux"


Linear system

$$a_0 y + a_1 \frac{dy}{dt} + a_2 \frac{d^2y}{dt^2} + \dots + a_n \frac{dy^{(n)}}{dt^{(n)}} = b_0 x(t)$$

$y_1 \leftarrow x_1$
 $y_2 \leftarrow x_2$
 $y_3 \leftarrow x_3$
 $y_4 \leftarrow x_4$
 $y_5 \leftarrow x_5$

a_0, a_1, \dots, a_n are constants.

x : input , y = output

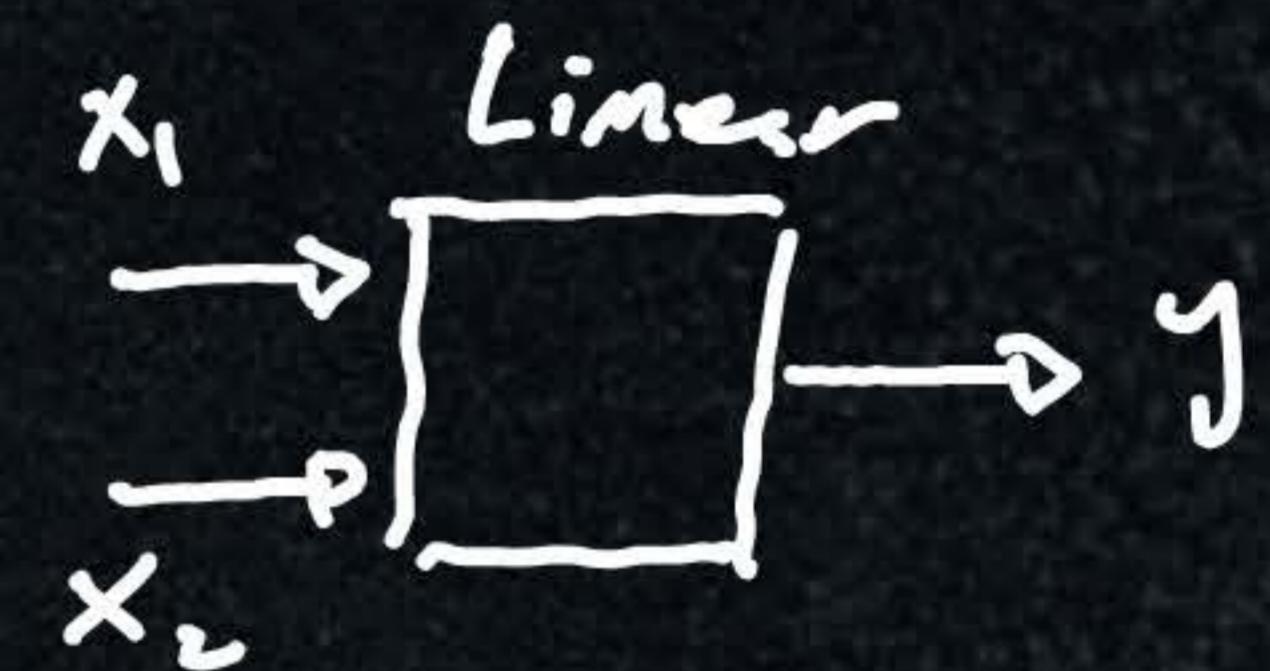

$$\frac{Y(s)}{X(s)} = H(s) = \text{Transfer Function}$$

$$\begin{aligned} y_1 &\leftarrow x_1 \\ y_2 &\leftarrow x_2 \end{aligned}$$


$$a_0 y + a_1 \frac{dy}{dt} = b_0 x$$

$$a_0 y_1 + a_1 \frac{dy_1}{dt} = b_0 x_1$$

$$a_0 y_2 + a_1 \frac{dy_2}{dt} = b_0 x_2$$

$$y_1 + y_2 \leftarrow x_1 + x_2$$
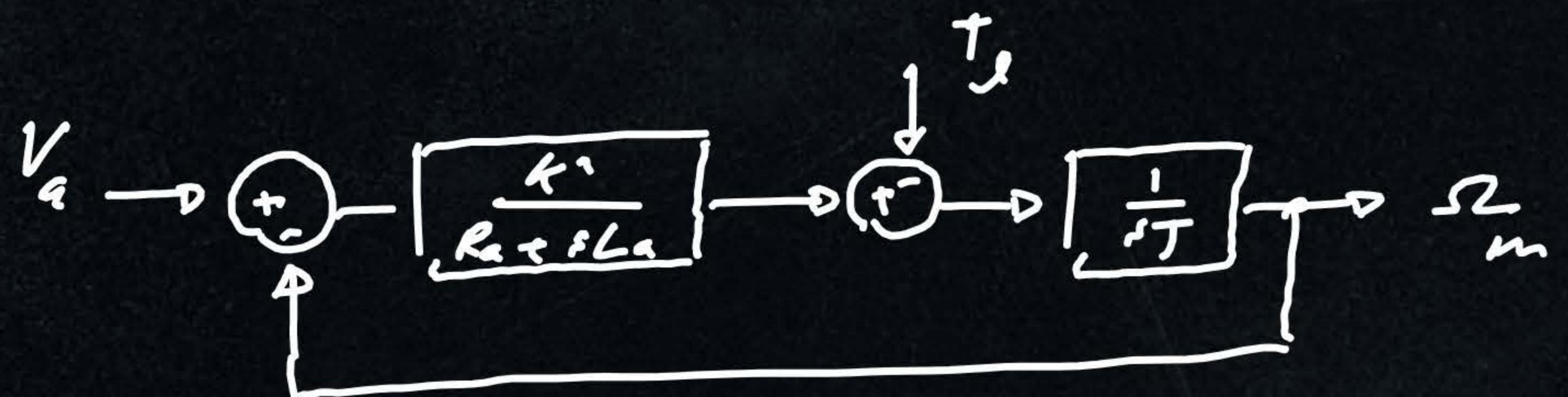
$$\begin{aligned} &a_0(y_1 + y_2) + a_1 \frac{d(y_1 + y_2)}{dt} \\ &= b_0(x_1 + x_2) \end{aligned}$$



$$R_m = R_{m_1} + R_{m_2}; \quad R_{m_1} = T_1 V_a \quad \text{when } T_2 = 0$$


$$R_{m_2} = T_2 T_L \quad \text{when } V_a = 0$$

$$R_m = T_1 V_a + T_2 T_L.$$

where $T_1 = \frac{R_m}{V_a} \mid T_L = 0$

$$T_2 = \frac{R_m}{T_L} \mid V_a = 0$$

Closed loop system

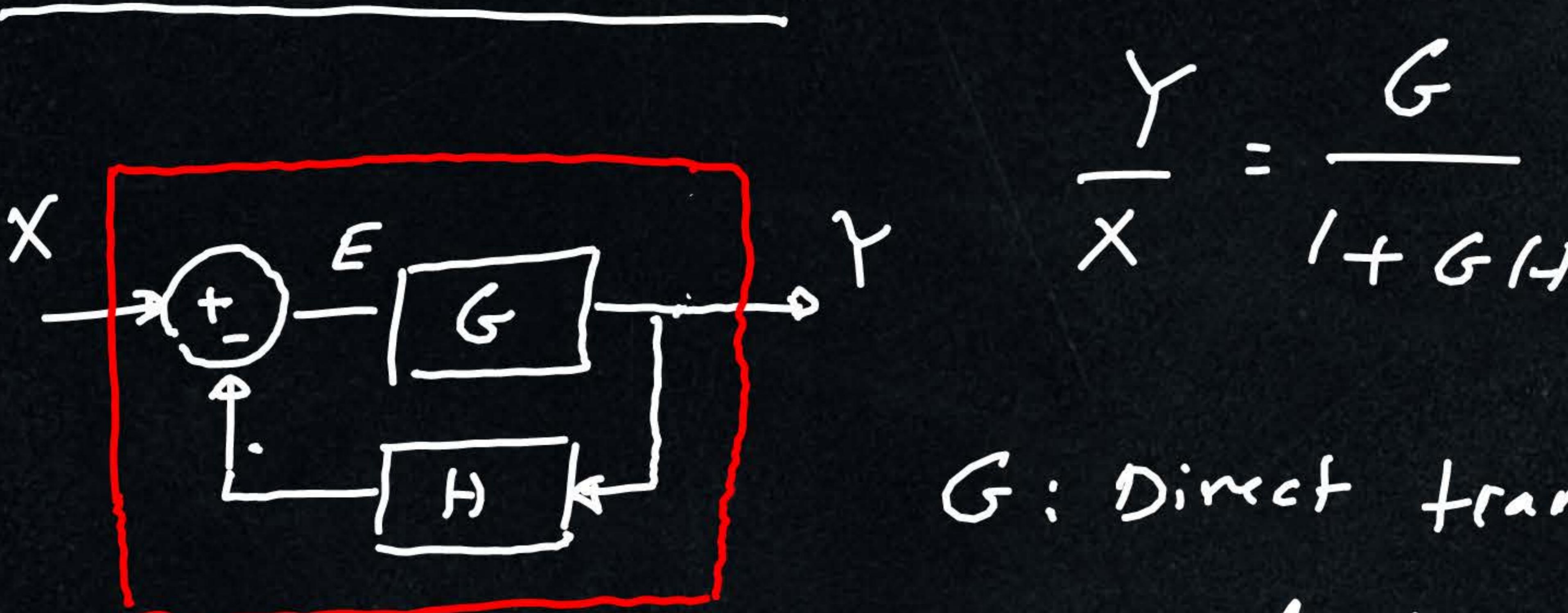

$$\frac{Y}{X} = \frac{G}{1+GH}$$

G : Direct transfer function


H : Feedback transfer function

$$Y = G E = G(X - HY)$$

$$Y = GX - GHY \Rightarrow Y(1 + GH) = GX$$

$$\frac{Y}{X} = \frac{G}{1+GH}$$
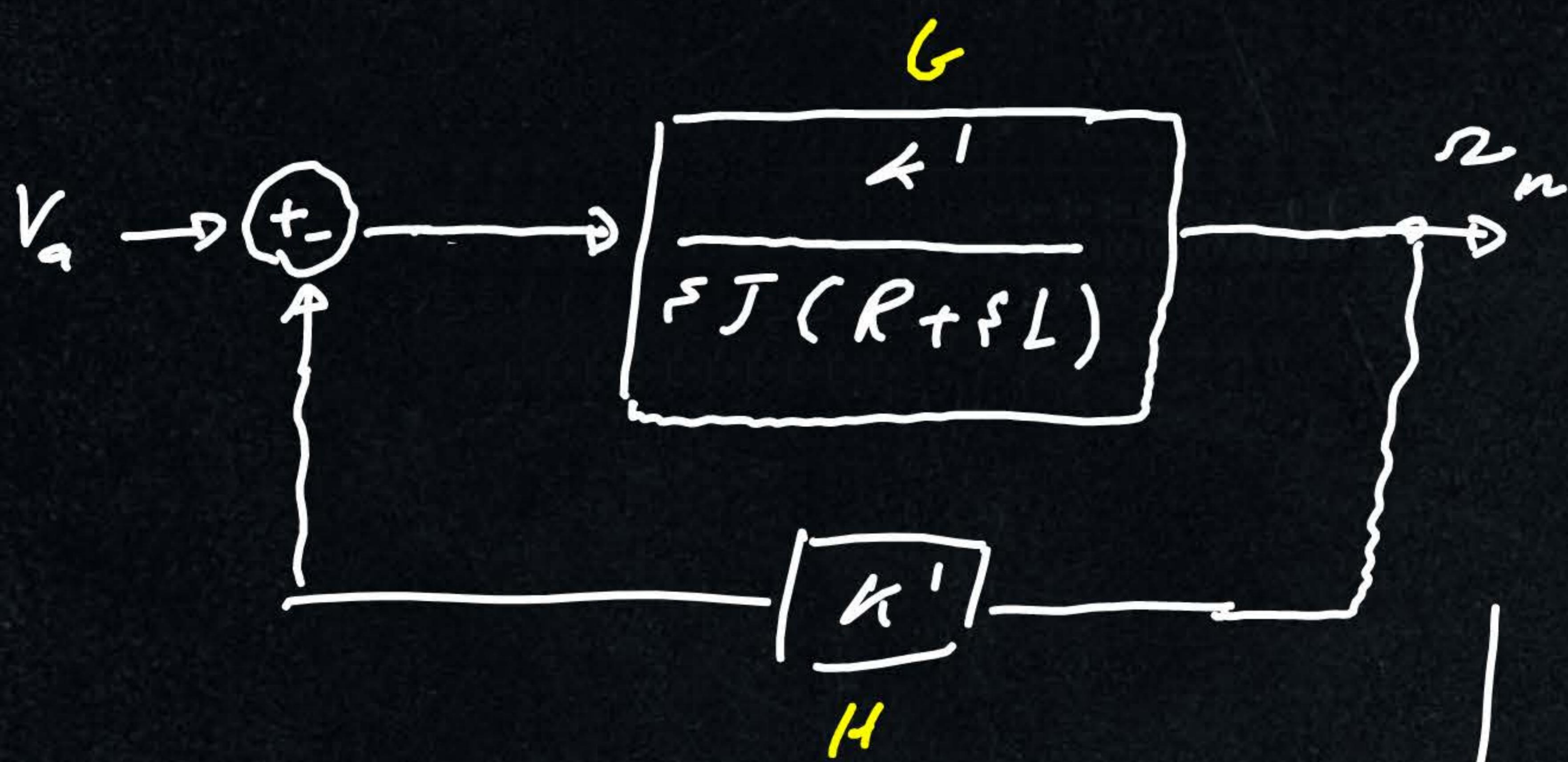
$$T_I = \frac{G}{1+GH} \text{ where } T_I = 0$$



$$T_I = \frac{G}{1+GH} ; \quad G = \frac{k'}{sT(R + sL)}$$




$$H = k'$$

$$T_I = \frac{\frac{k'}{sT(R + sL)}}{1 + \frac{k'^2}{sT(R + sL)}}$$

$$T_I = \frac{k'}{sT(R + sL) + k'^2}$$

$$T_I = \frac{k'}{JLs^2 + JRs + k'^2}$$
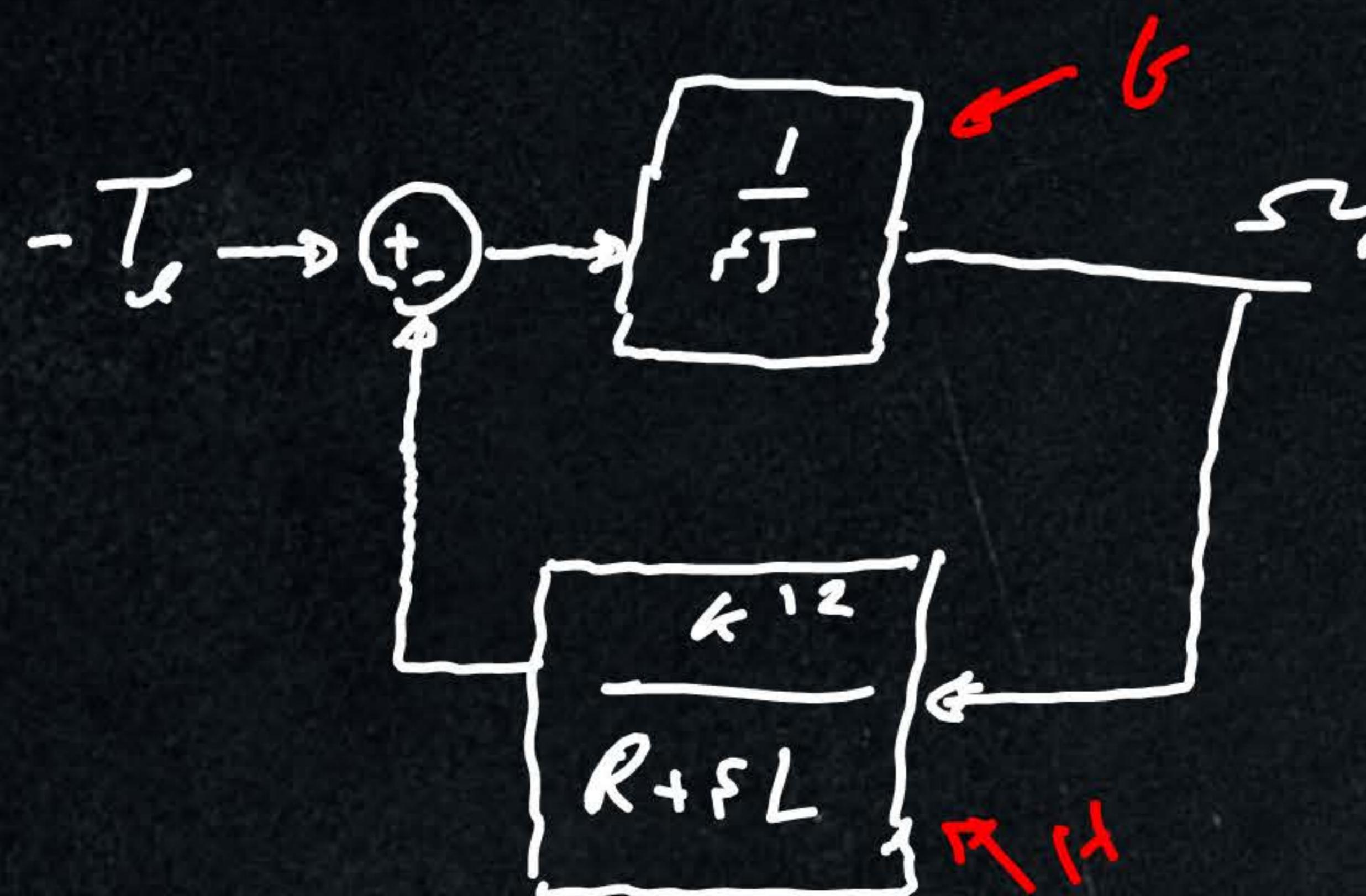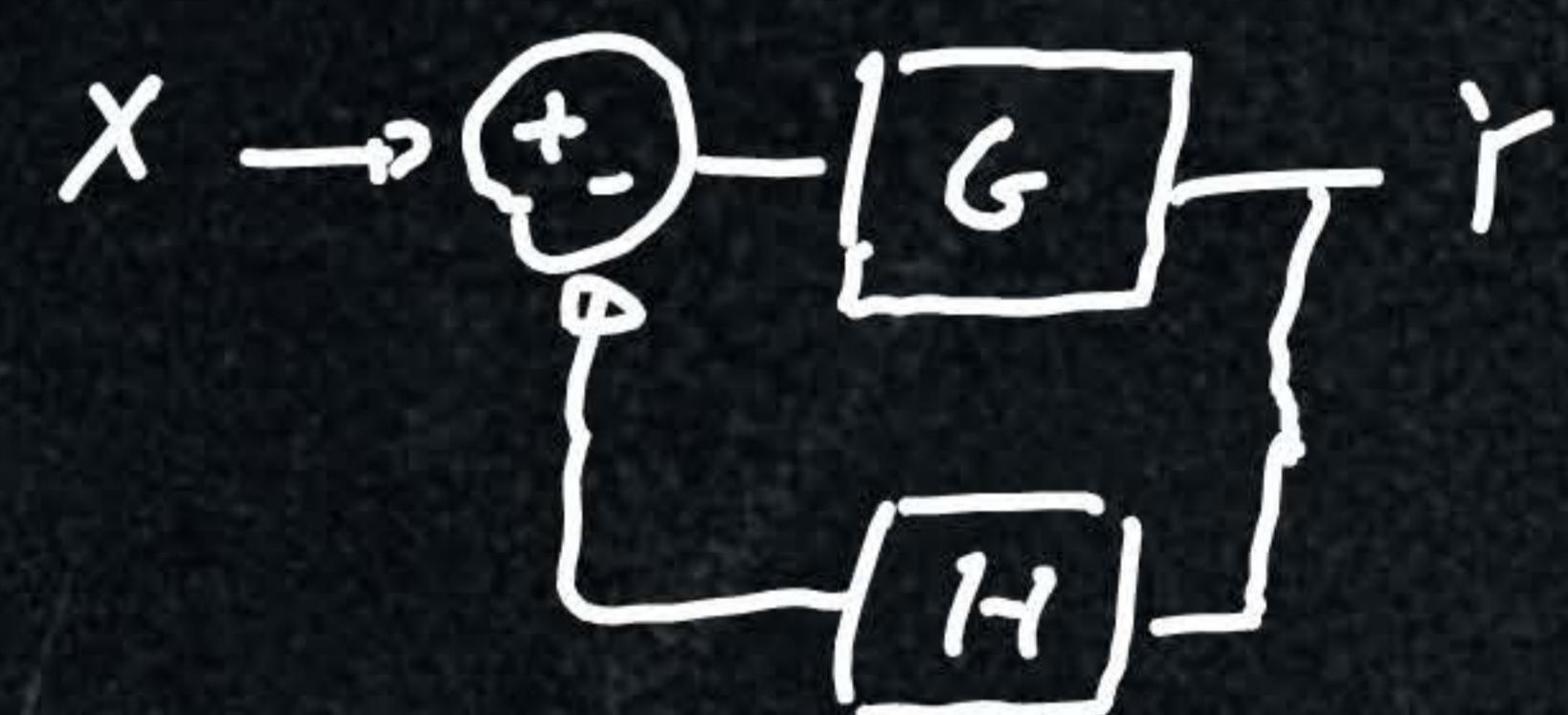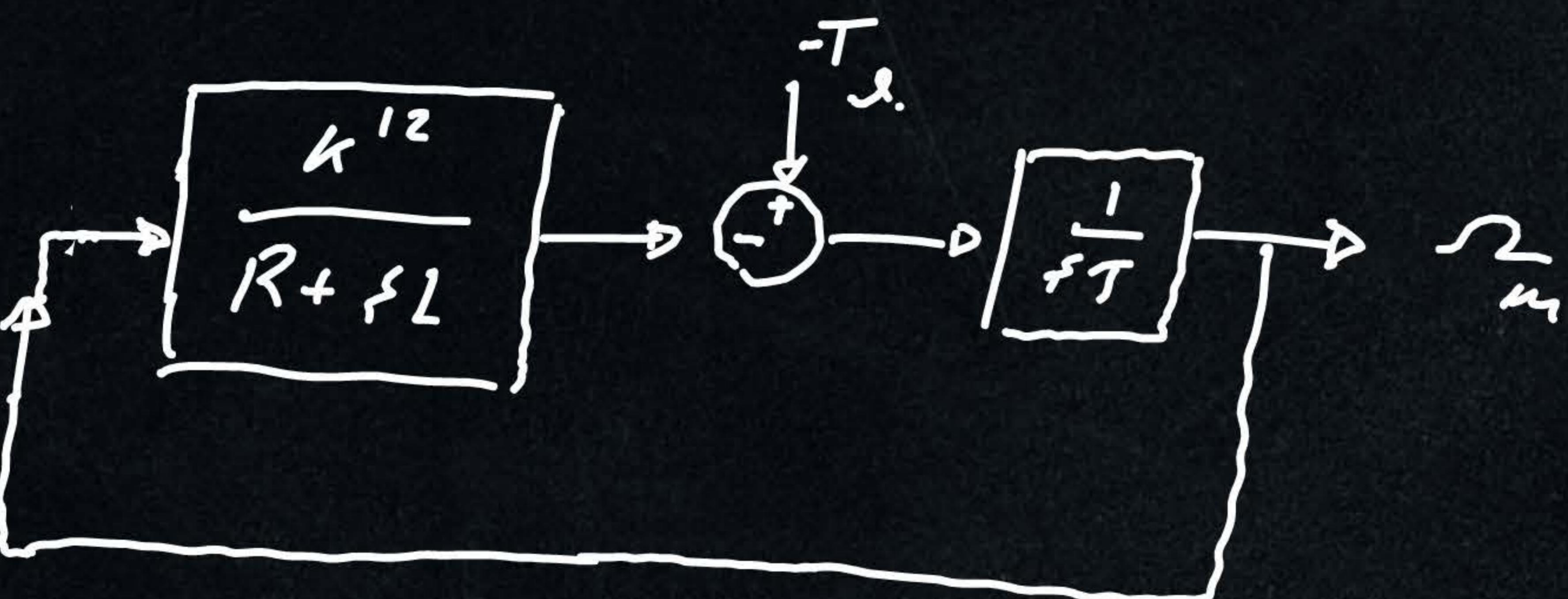
$$T_2 = \frac{S_m}{T_x} \text{ when } V_a = 0$$



$$T_2 = \frac{S_m}{T_x} = \frac{-G}{1 + GH}$$

$$G = \frac{1}{fT} ; H = \frac{k'^2}{R + fL}$$


Separately excited DC motor

$$V_a = R_a l_a + e_a ; \quad e_a = K \phi_q w_m \Rightarrow V_a = R_a l_a + K \phi_q w_m \quad \dots \textcircled{1}$$

$$T_{el} = K \phi_q l_a \Rightarrow l_a = \frac{T_{el}}{K \phi_q} \quad \dots \textcircled{2}$$

$$\textcircled{2} \rightarrow \textcircled{1} \Rightarrow V_a = \frac{R_a}{K \phi_q} T_{el} + K \phi_q w_m$$
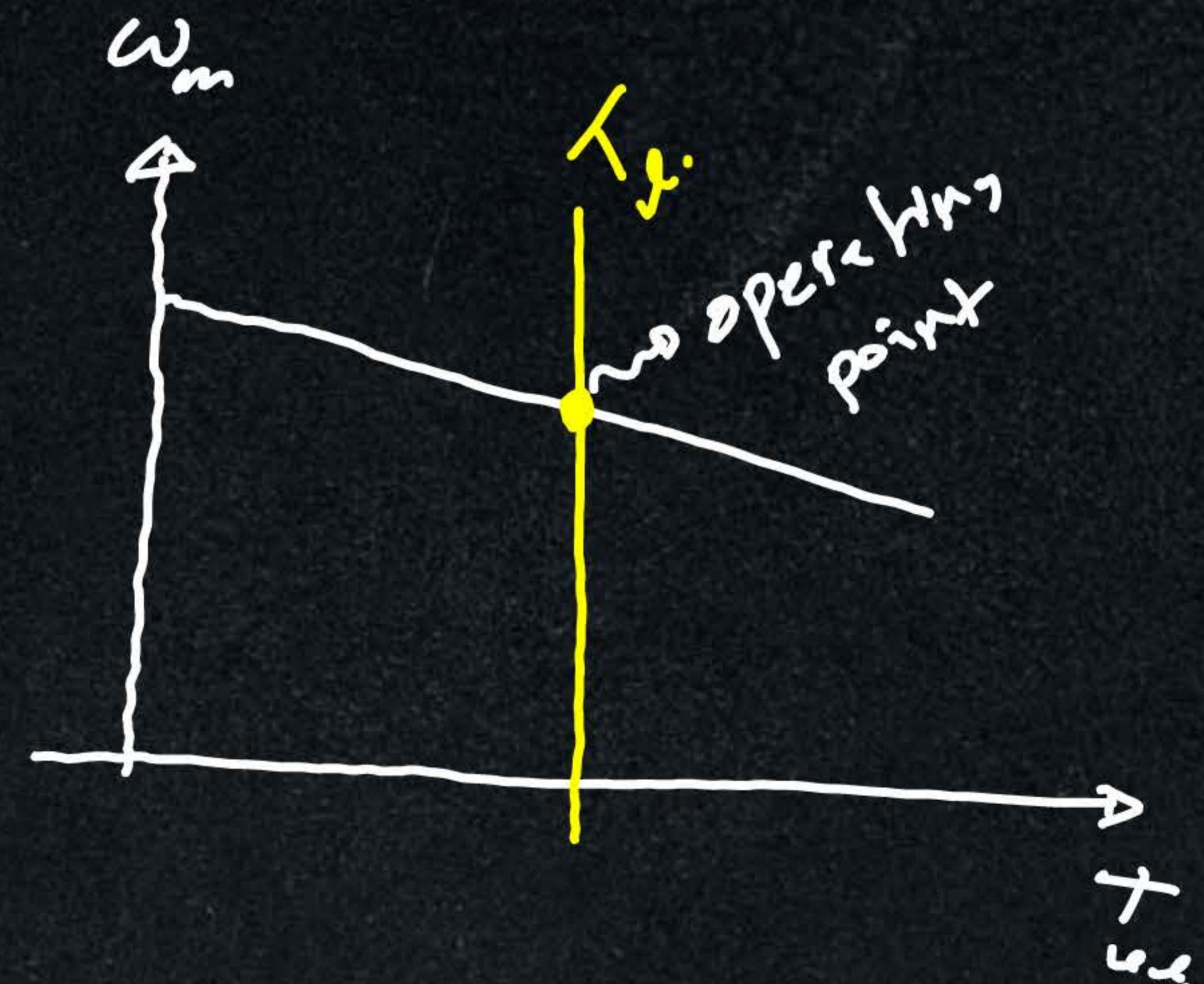
$$\omega_m = \frac{V_a}{K \phi_q} - \frac{R_a}{(K \phi_q)^2} T_{el}$$




Separately excited DC motor

$$V_a = R_a l_a + e_a ; \quad e_a = K \phi_q w_m \Rightarrow V_a = R_a l_a + K \phi_q w_m \quad \dots \textcircled{1}$$

$$T_{el} = K \phi_q l_a \Rightarrow l_a = \frac{T_{el}}{K \phi_q} \quad \dots \textcircled{2}$$

$$\textcircled{2} \rightarrow \textcircled{1} \Rightarrow V_a = \frac{R_a}{K \phi_q} T_{el} + K \phi_q w_m$$

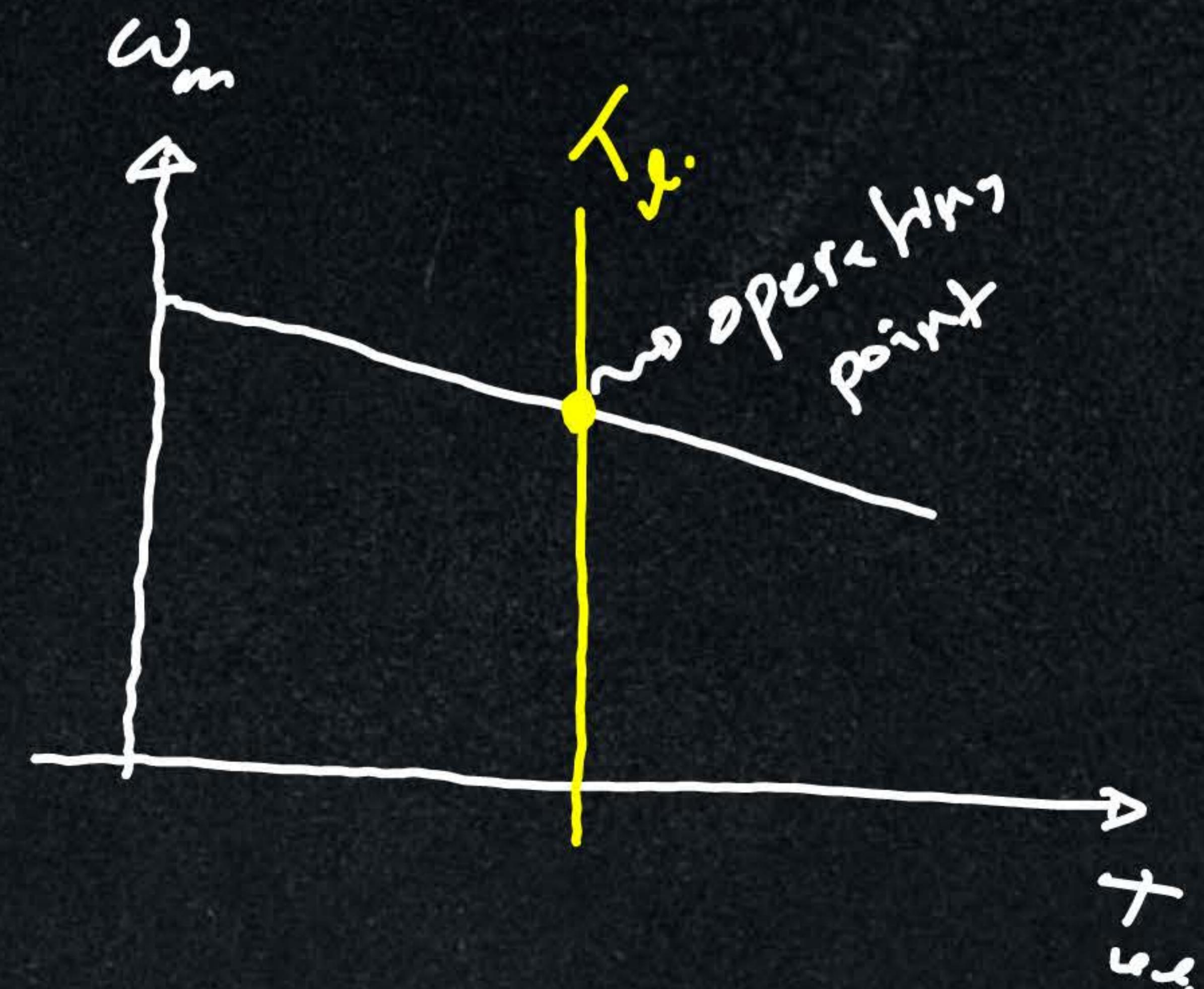
$$\omega_m = \frac{V_a}{K \phi_q} - \frac{R_a}{(K \phi_q)^2} T_{el}$$



Methods of speed control


$$\omega_m = \frac{V_q}{k\phi_L} - \frac{R_q}{(k\phi_L)^2} T_{dL}$$

- V_q control

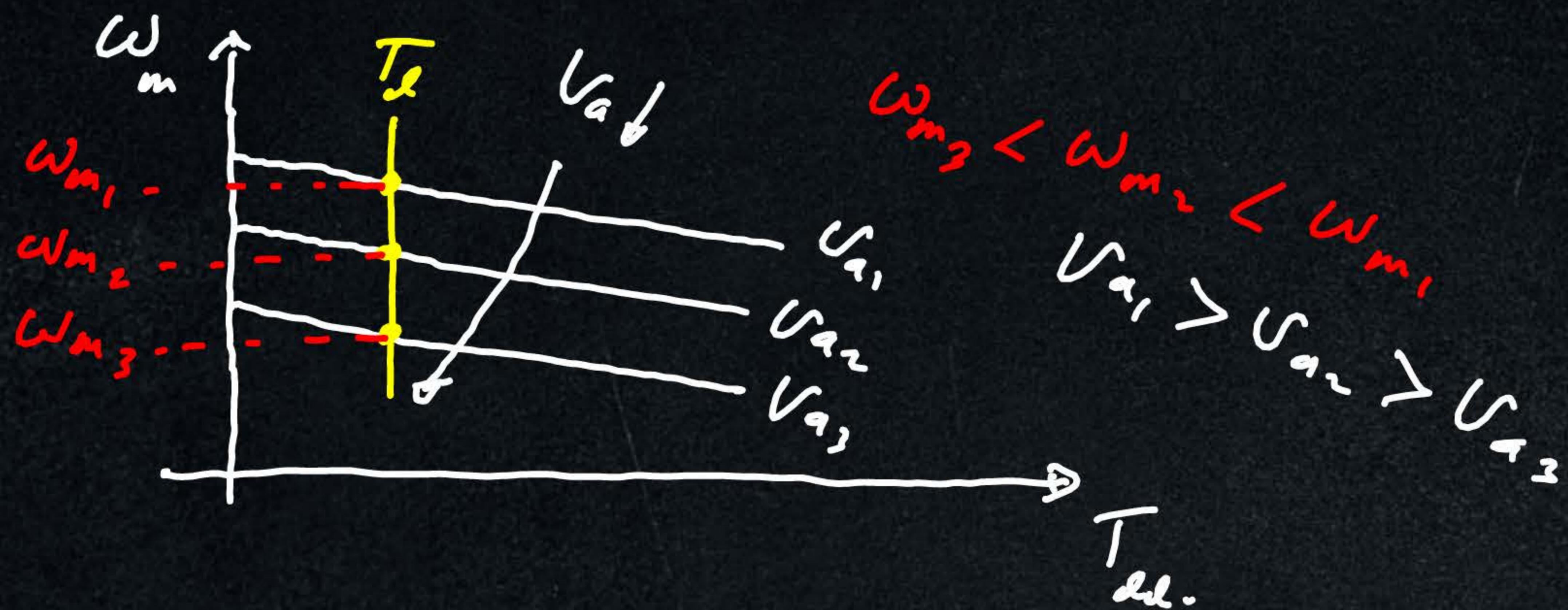

- R_a control
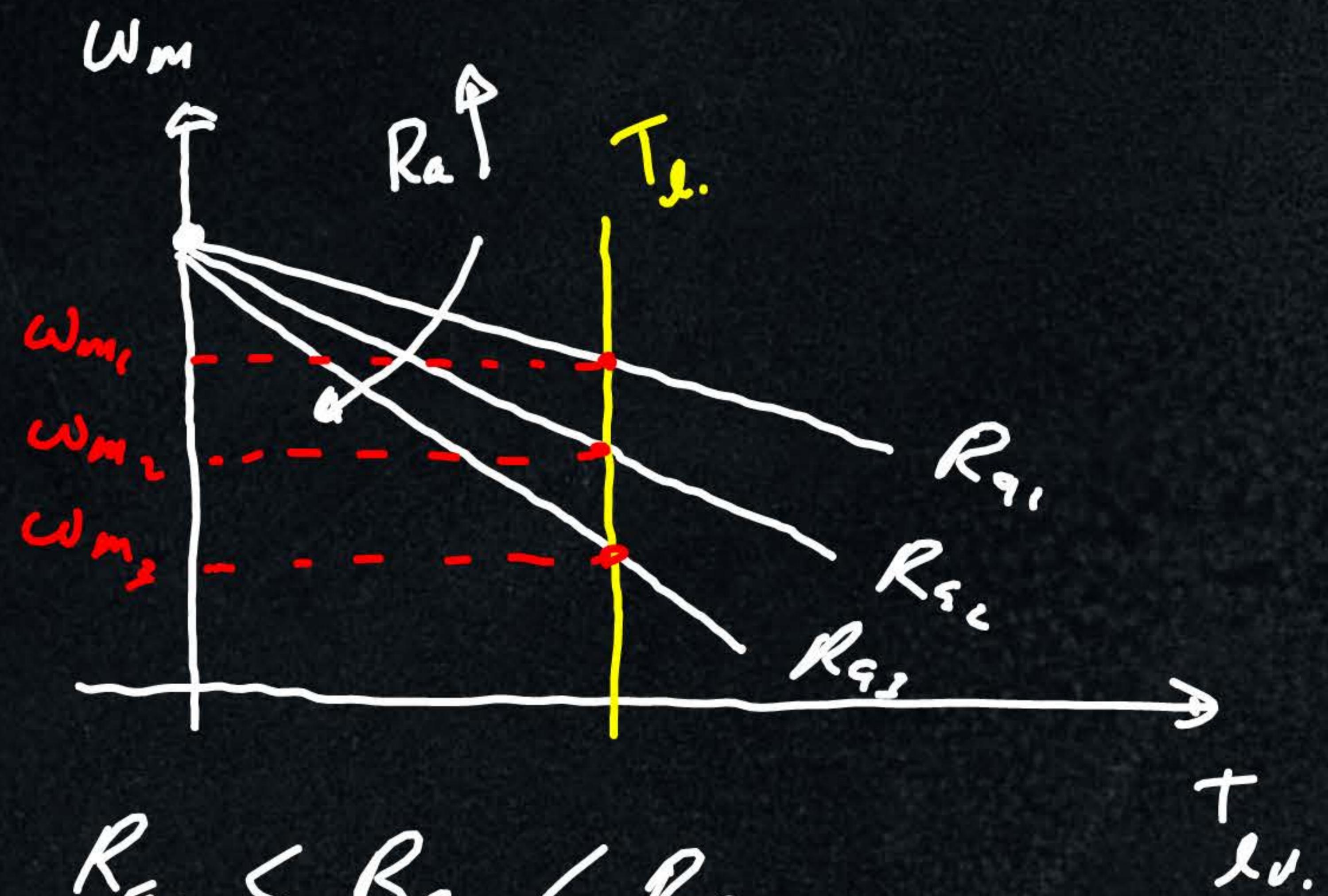
$$\omega_m = \frac{V_g}{K\phi_L} - \frac{R_a}{(K\phi_L)^2} T_{LL}$$



$$R_{q_1} < R_{q_2} < R_{q_3}$$

$$\omega_{m_1} > \omega_{m_2} > \omega_{m_3}$$

$$R_a \uparrow \Rightarrow \omega_m \downarrow$$

Torque-speed equation "shunt & separately excited DC motors"


$$V_a = R_a \dot{I}_a + e_a ; \quad e_a = K \phi_y \omega_m$$

$$V_a = R_a \dot{I}_a + K \phi_y \omega_m \dots \textcircled{1}$$

$$T_{eq} = K \phi_y \dot{I}_a \Rightarrow \dot{I}_a = \frac{T_{eq}}{K \phi_y} \dots \textcircled{2}$$

$$\textcircled{2} \rightarrow \textcircled{1} \Rightarrow V_a = \frac{R_a}{K \phi_y} T_{eq} + K \phi_y \omega_m$$

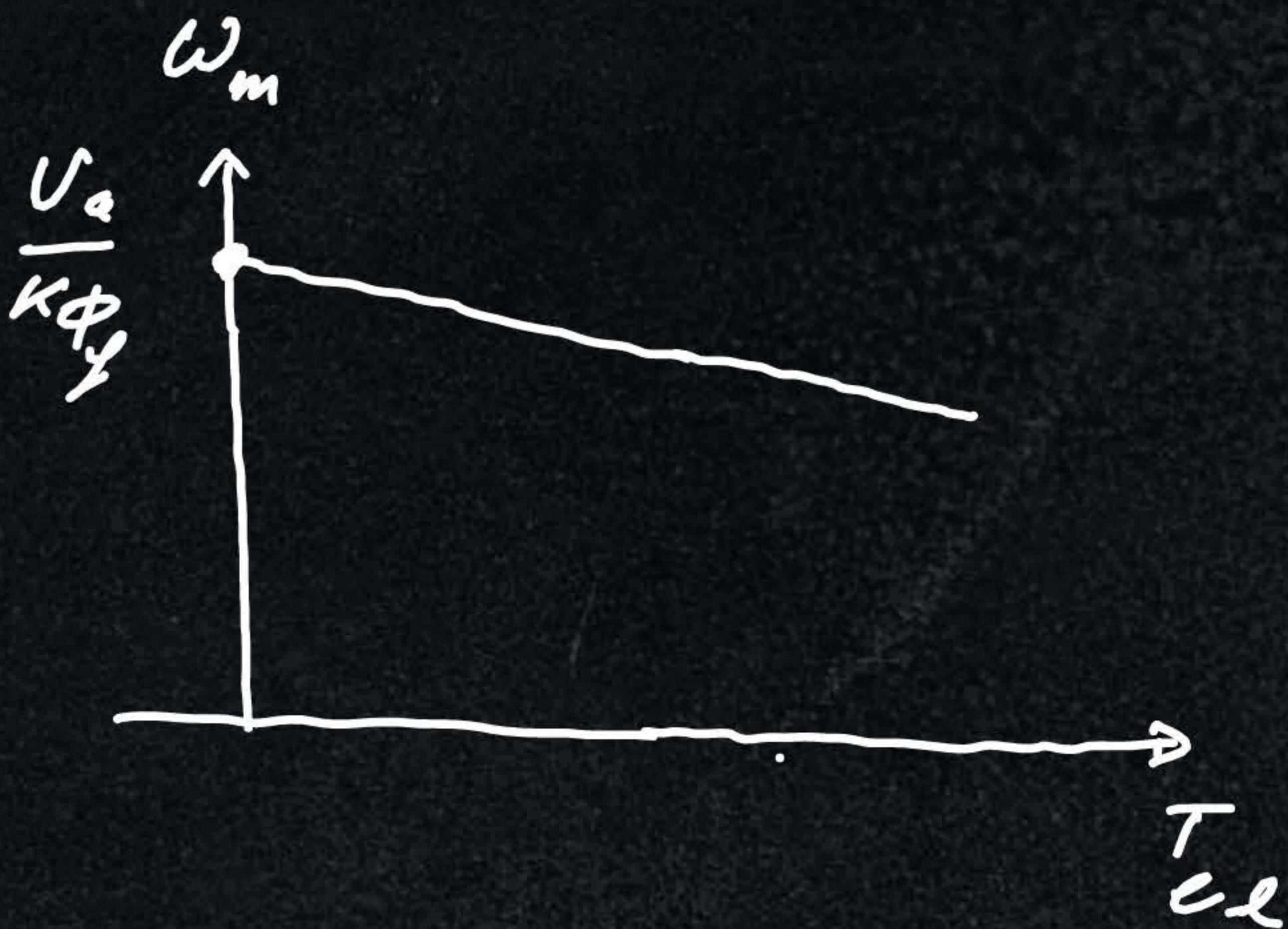
$$\boxed{\omega_m = \frac{V_a}{K \phi_y} - \frac{R_a}{(K \phi_y)^2} T_{eq}}$$




$$\omega_m = \frac{V_a}{K\phi_y} - \frac{R_a}{(K\phi_y)^2} T_{el.}$$

Methods of speed control :-

1) V_a control.

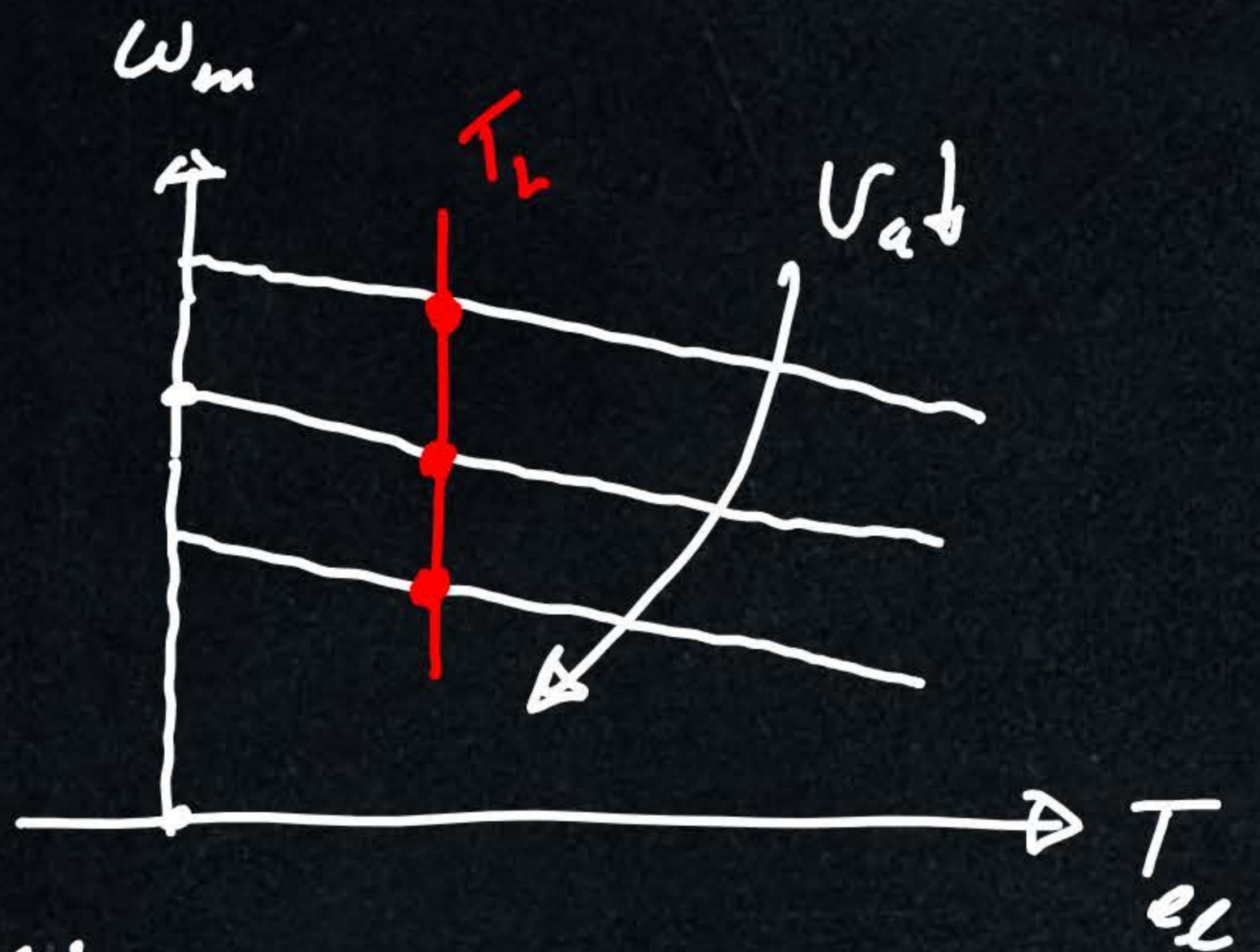

2) R_a control

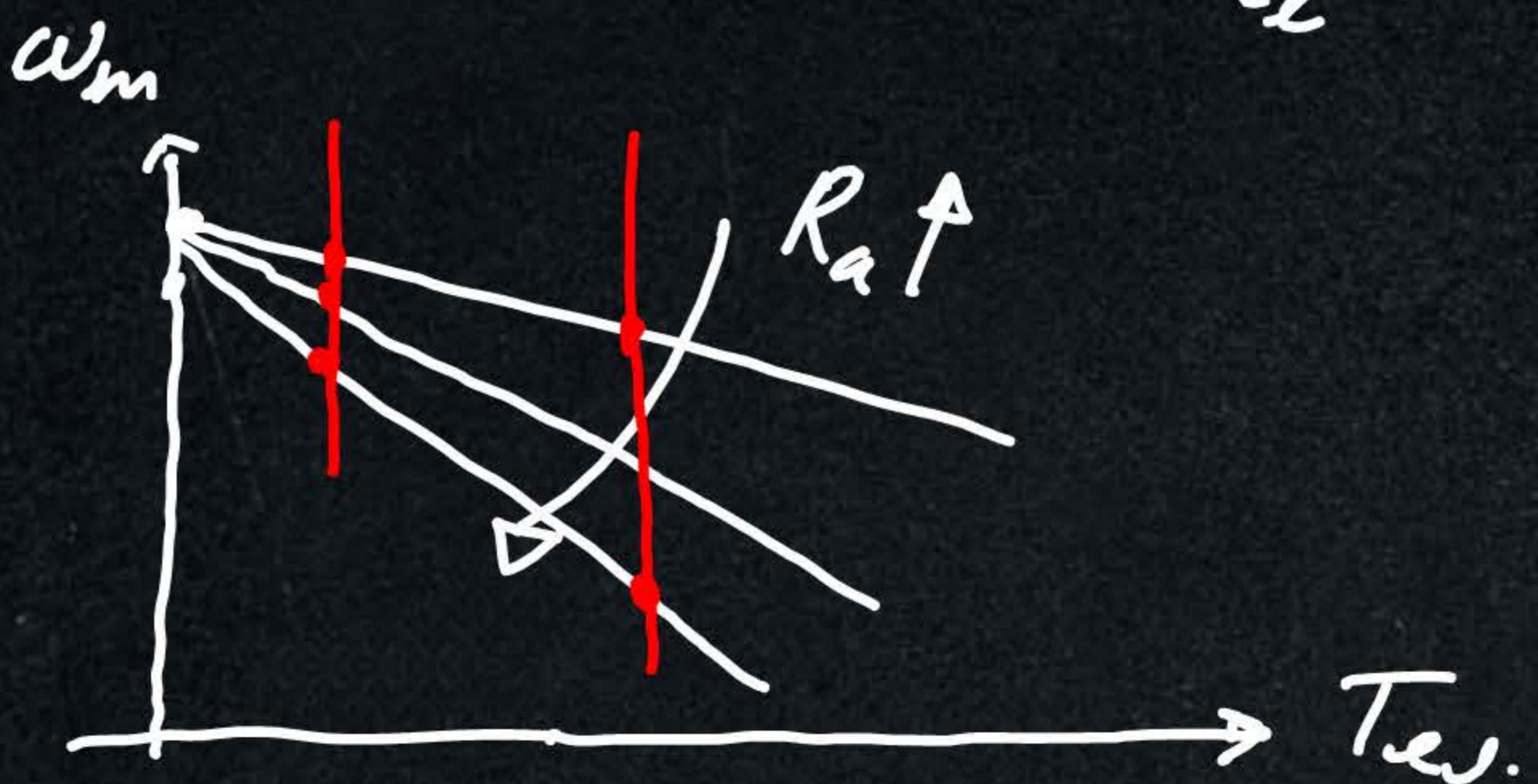


Torque-speed equation (series DC motor)

$$V_L = (R_f + R_a) \dot{C}_a + K\dot{\phi} w_m$$

$$\dot{\phi} = C_i \dot{C}_a'$$

$$\dot{C}_a = \dot{C}_a'$$
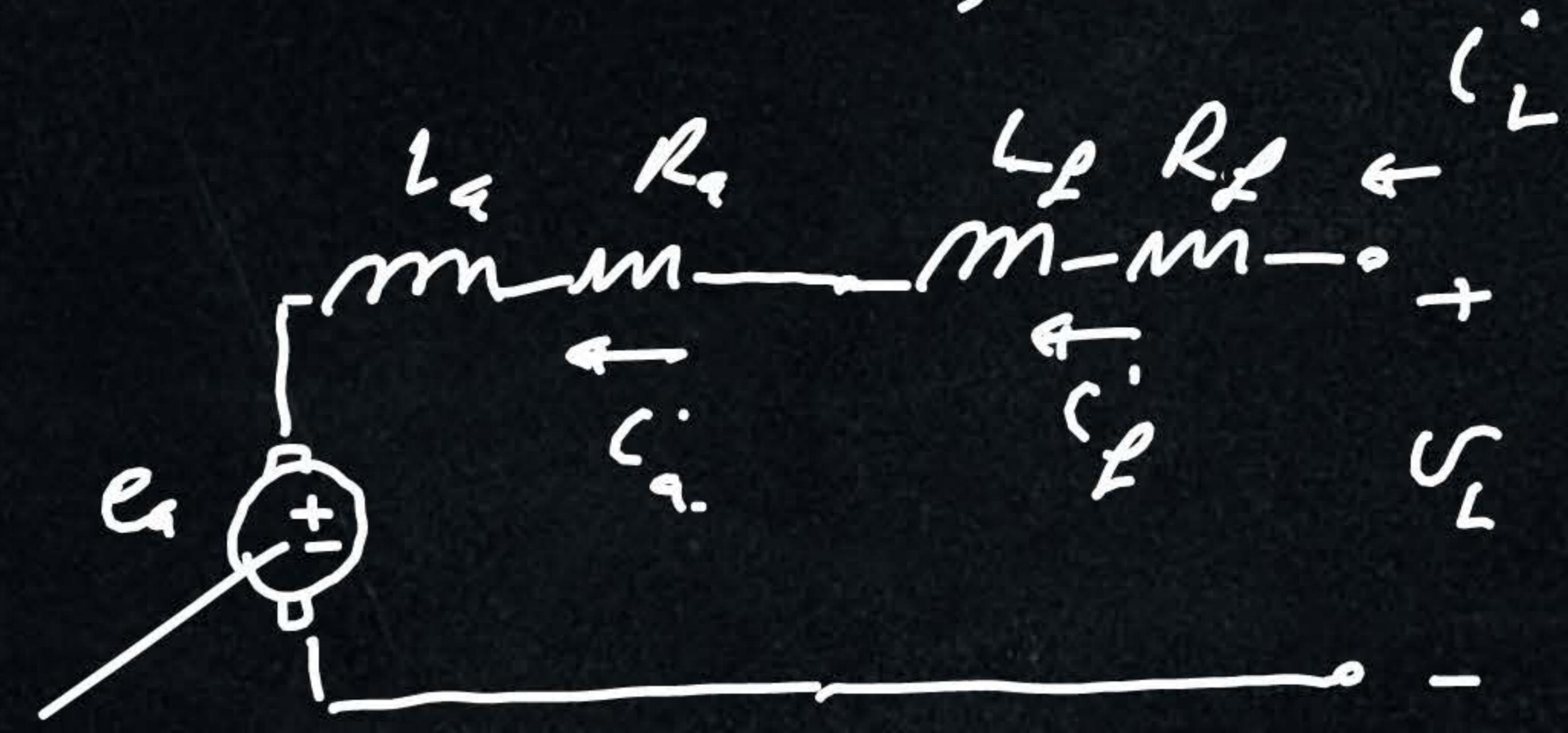
$$\underline{\dot{\phi}} = C_i \dot{C}_a$$




$$V_L = (R_f + R_a) \dot{C}_a' + K_C \dot{C}_a' w_m \quad \dots \textcircled{1}$$

$$T_{ed} = K\dot{\phi} \dot{C}_a' = K_C \dot{C}_a'^2 \Rightarrow \dot{C}_a' = \sqrt{\frac{T_{ed}}{K_C}} \quad \dots \textcircled{2}$$


$$\textcircled{2} \rightarrow \textcircled{1} \Rightarrow V_L = \frac{(R_f + R_a)}{\sqrt{K_C}} \overbrace{N \sqrt{T_{ed}}} + \underbrace{\sqrt{K_C} \sqrt{T_{ed}} w_m}_{w_m = \frac{V_L}{\sqrt{K_C}} \frac{1}{\sqrt{T_{ed}}} - \frac{(R_f + R_a)}{K_C}}$$
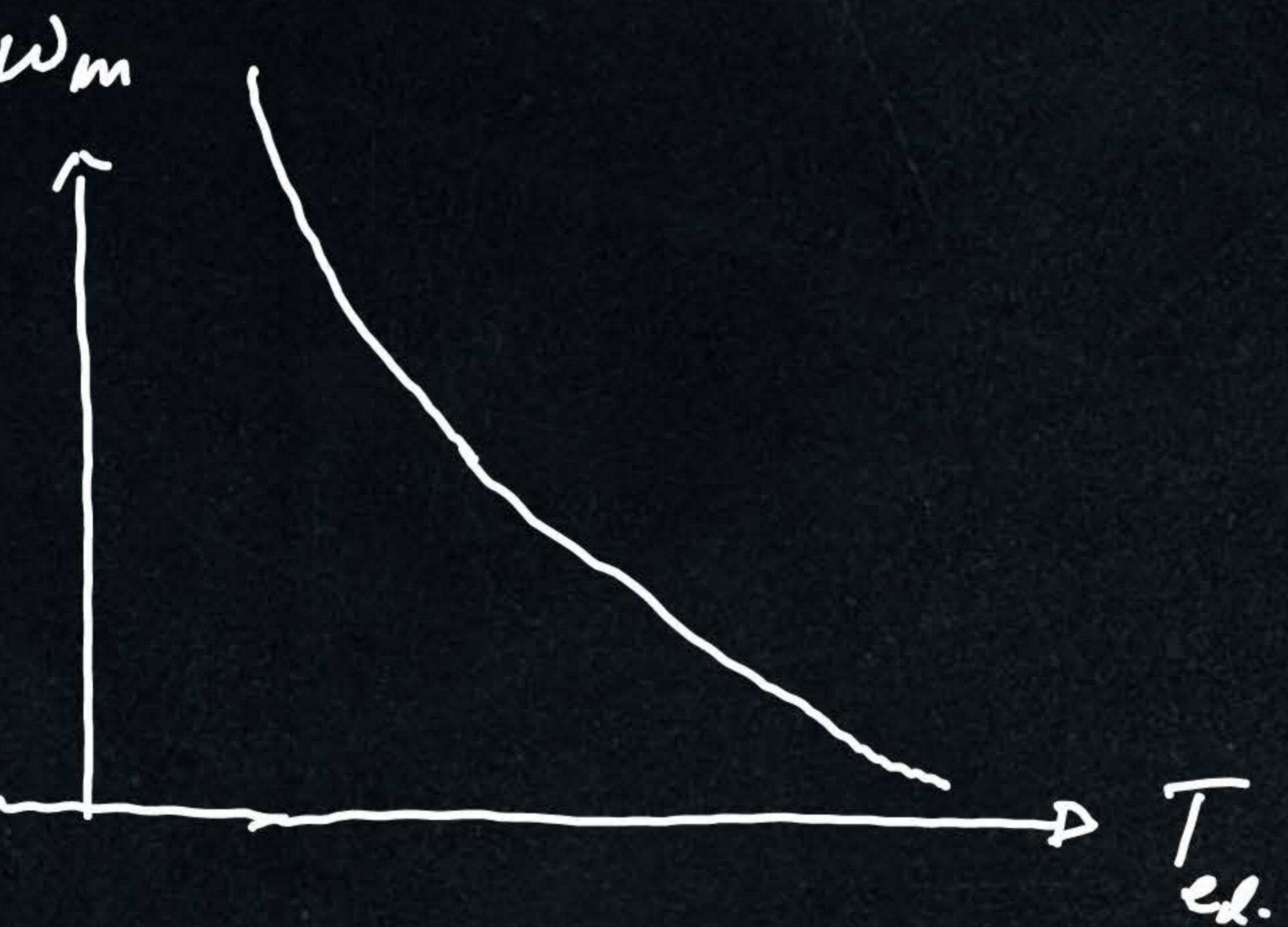
$$\omega_m = \frac{V_t}{N\kappa C} \frac{1}{\sqrt{T_{ex}}} - \frac{R_a + R_p}{\kappa C}$$



Field control "series DC motor"

(Field diverting resistor method)

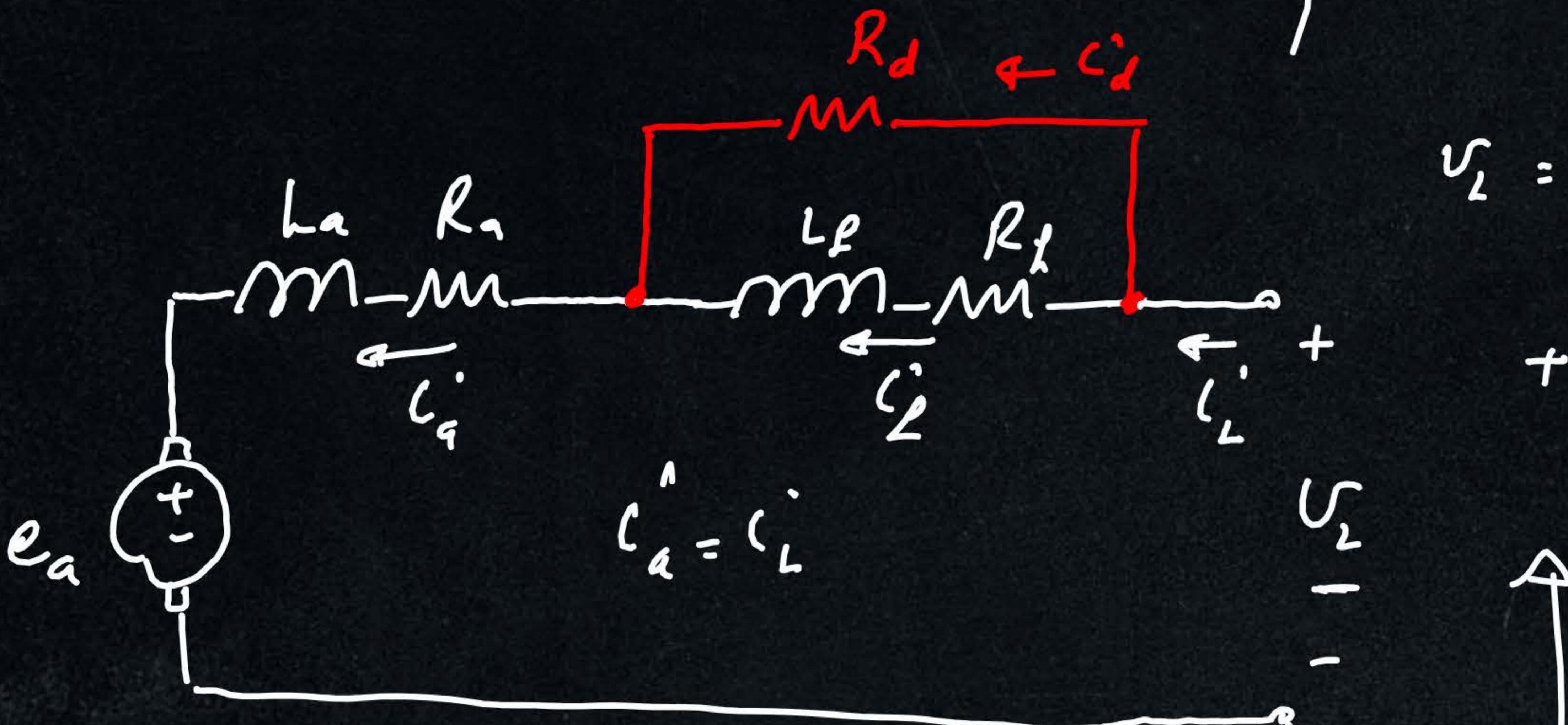

$$U_L = R_a i_L + \frac{R_f R_d}{R_f + R_d} i_L + K \phi_f \omega_m$$

$$\phi_f = C_i^f = C \frac{R_d}{R_d + R_f} i_L$$

$$U_L = R_a i_L + \frac{R_f R_d}{R_f + R_d} i_L + K C \frac{R_d}{R_d + R_f} i_L \omega_m$$

$$R_d \uparrow \Rightarrow C_f \uparrow$$

$$\Rightarrow \phi_f \uparrow \Rightarrow \omega_m \downarrow$$



$\rightarrow T_{e,L}$

Ex :- A separately excited DC motor used to drive a fan whose torque is proportional to ω_m^2 . When the armature circuit is connected across 200 V, it takes armature current of 16 A and the motor runs at speed of 1000 rpm. If the speed of the motor is to be reduced to 750 rpm, calculate the required voltage and the current drawn by the motor. ($R_a = 0.5 \Omega$) .



$$V_{a_1} = R_a I_{a_1} + E_{a_1}$$

$$200 = 0.5(16) + E_{a_1} \Rightarrow E_{a_1} = 192 \text{ V}$$

$$E_{a_2} = 144.36 \text{ V}$$

$$\frac{E_{a_2}}{E_{a_1}} = \frac{n_2}{n_1} = \frac{750}{1000} = \frac{E_{a_2}}{192}$$

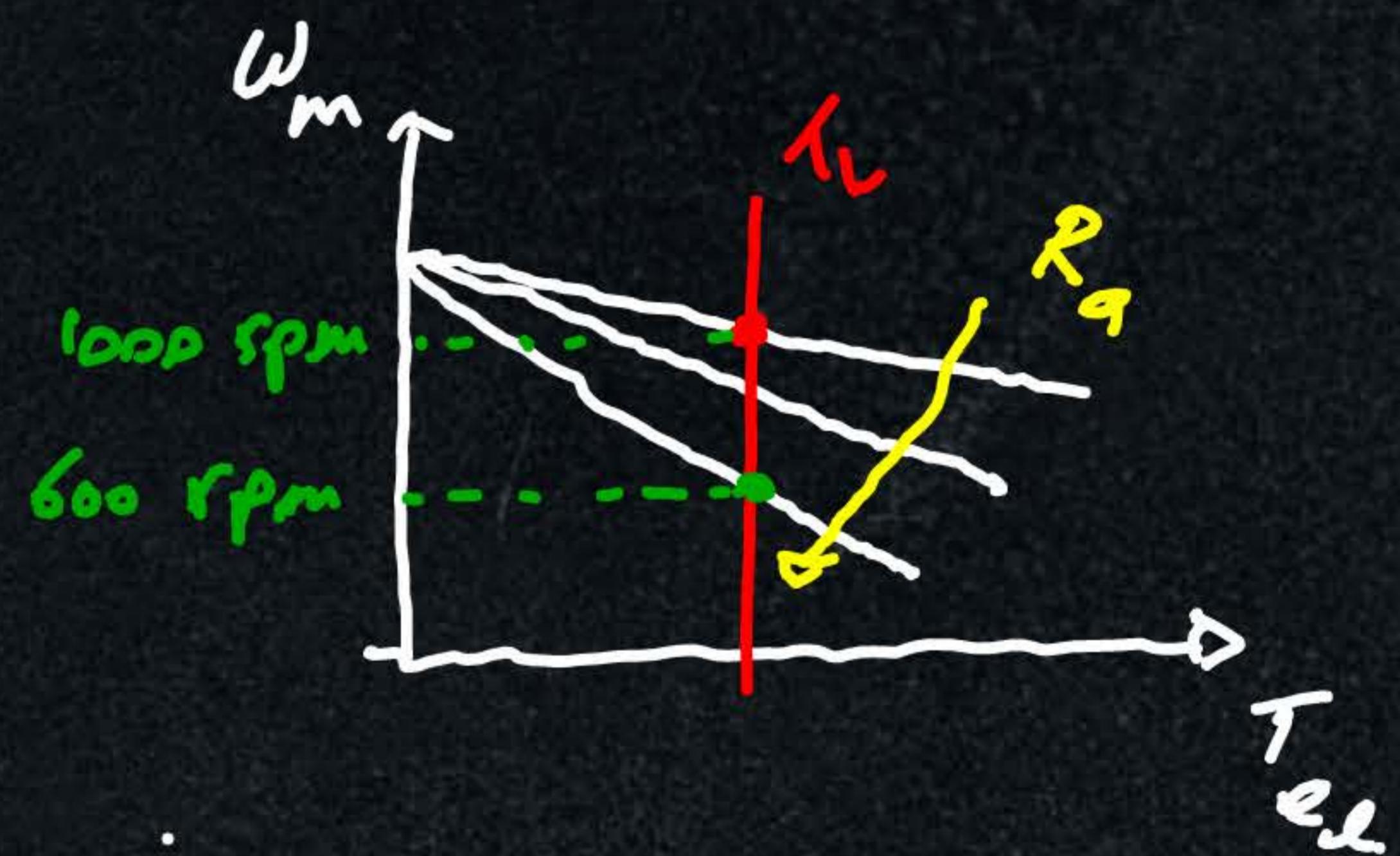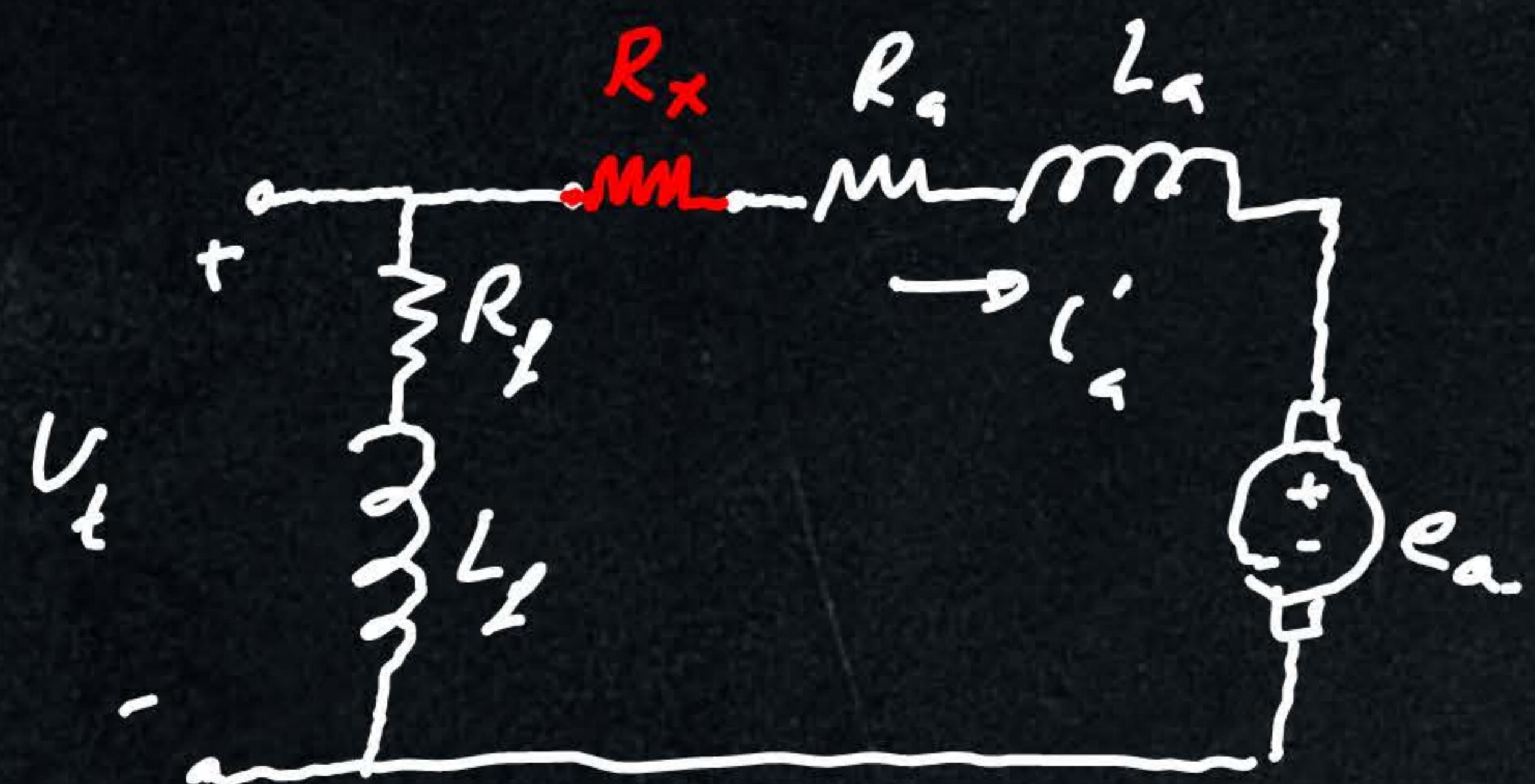Ex:- A 240 V DC shunt motor has an armature resistance of 0.2 Ω. When the armature current is 40 A, the speed is 1000 rpm. (a) Find additional resistance, R_x , to be connected in series with armature to reduce the speed to 600 rpm. Assume the armature current remains the same.




Ex:- A 240 V DC shunt motor has an armature resistance of 0.2 Ω. When the armature current is 40 A, the speed is 1000 rpm. (a) Find additional resistance, R_x , to be connected in series with armature to reduce the speed to 600 rpm. Assume the armature current remains the same.

$$V_a = (R_a + R_x) i_a + e_{a2}$$

$$240 = (0.2 + R_x) 40 + e_{a2}$$

$$e_{a2} = 232 - 40 R_x$$

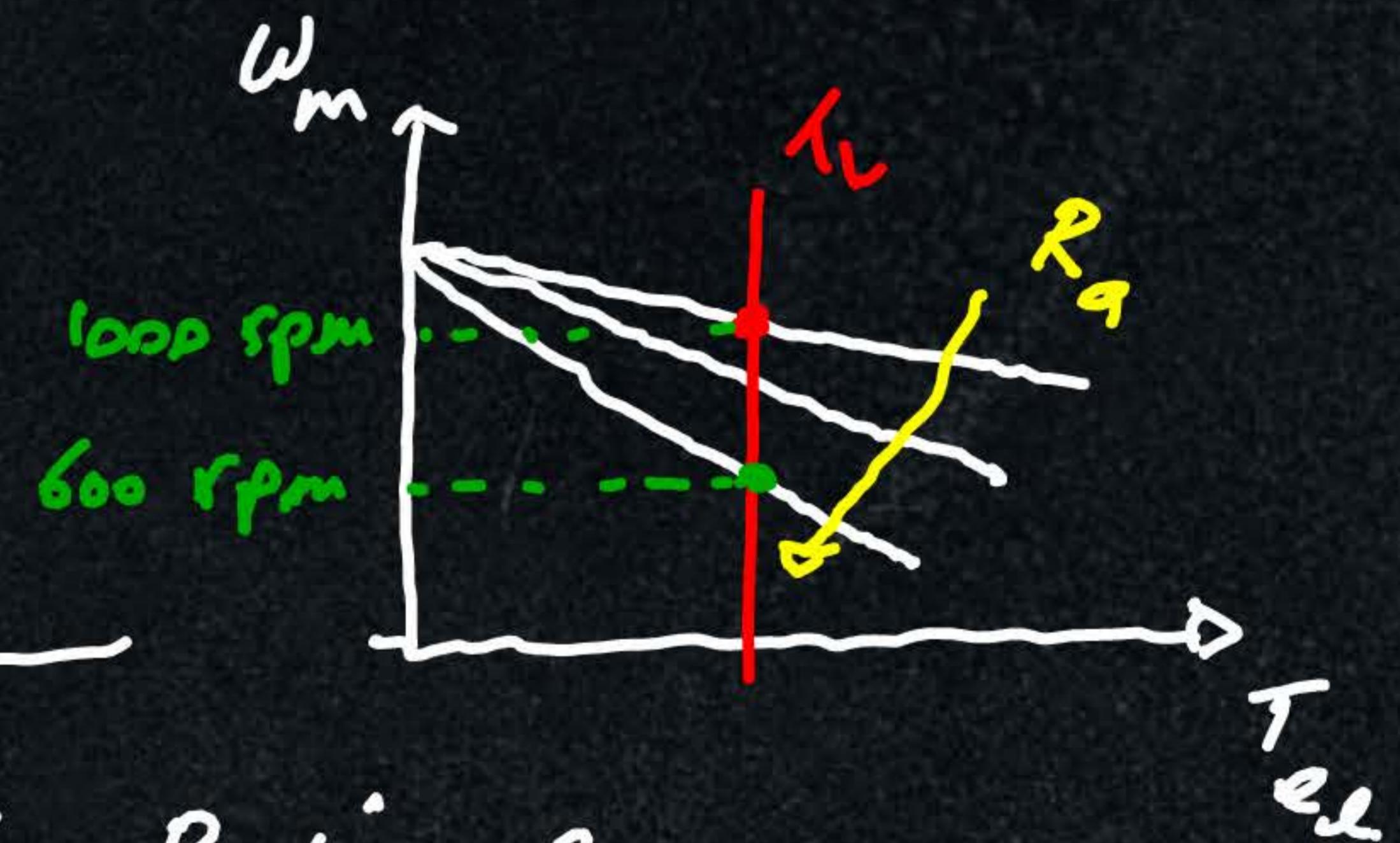

$$V_a = R_a i_a + e_{a1}$$

$$240 = 0.2 (40) + e_{a1}$$

$$e_{a1} = 240 - 8 \Rightarrow e_{a1} = 232 \text{ V}$$

$$e_{a_1} = 232 \text{ V}$$

$$e_{a_2} = \frac{n_2}{n_1} = \frac{600}{1000} = \frac{232 - 40R_x}{232}$$

$$e_{a_2} = 232 - 40 R_x$$

solve for $R_x \Rightarrow$

$$R_x = 2.325 \Omega$$


(b) If the current decreases to 20 A (with resistance R_x connected) find the new speed of the motor.

$$e_{a_1} = 232 \text{ V}$$

$$e_{a_2} = V_t - (R_a + R_x) i_a$$

$$= 240 - (0.2 + 2.325)(20) = 189.5 \text{ V}$$
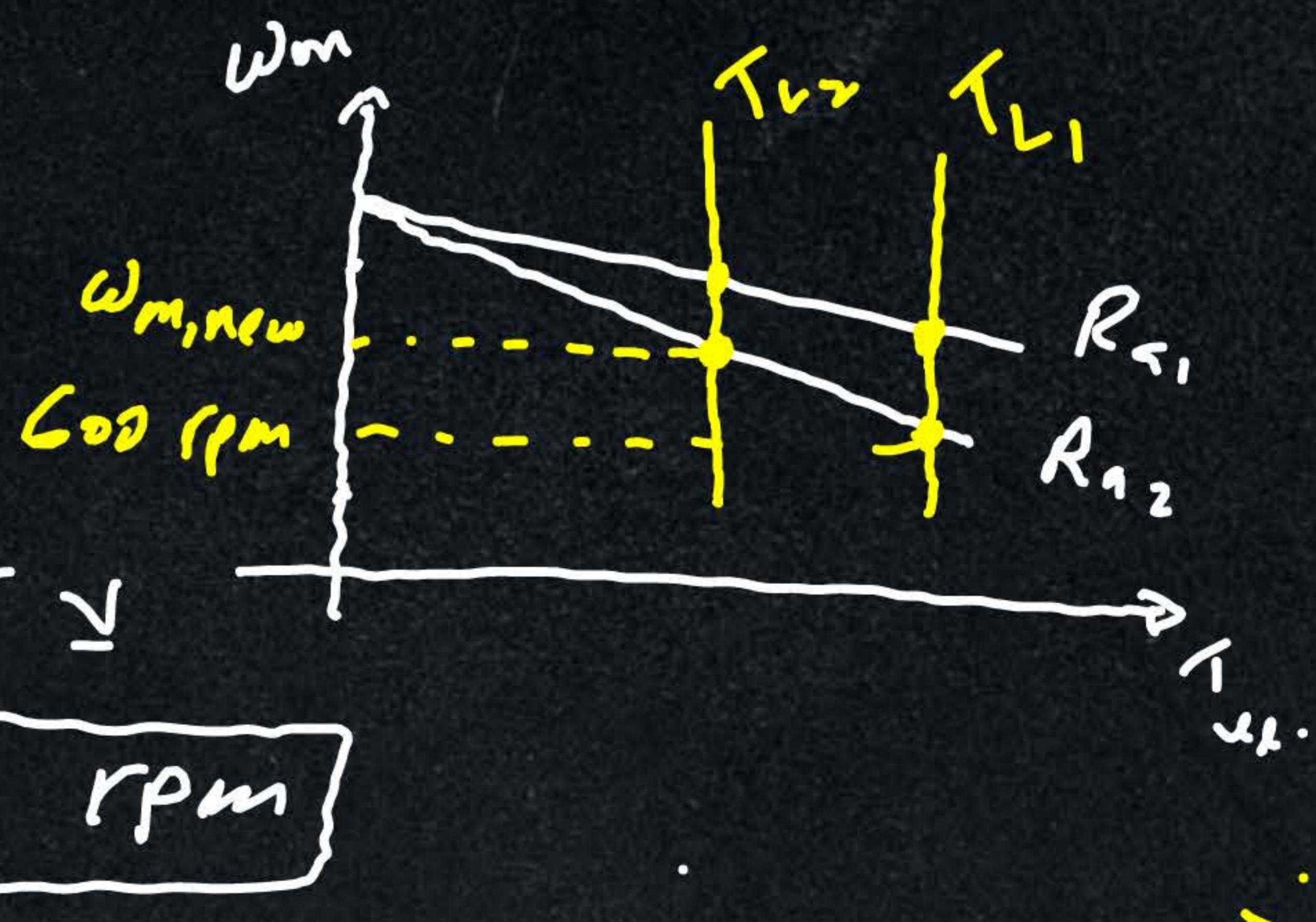
$$\frac{e_{a_2}}{e_{a_1}} = \frac{n_2}{1000} = \frac{189.5}{232} \Rightarrow n_2 : 803 \text{ rpm}$$



$$e_{a_1} = 232 \text{ V}$$

$$e_{a_2} = \frac{n_2}{n_1} = \frac{600}{1000} = \frac{232 - 40R_x}{232}$$

$$e_{a_2} = 232 - 40 R_x$$

solve for $R_x \Rightarrow R_x = 2.325 \Omega$


(b) If the current decreases to 20 A (with resistance R_x connected) find the new speed of the motor.

$$e_{a_1} = 232 \text{ V}$$

$$e_{a_2} = V_t - (R_a + R_x) I_a$$

$$= 240 - (0.2 + 2.325)(20) = 189.5 \text{ V}$$
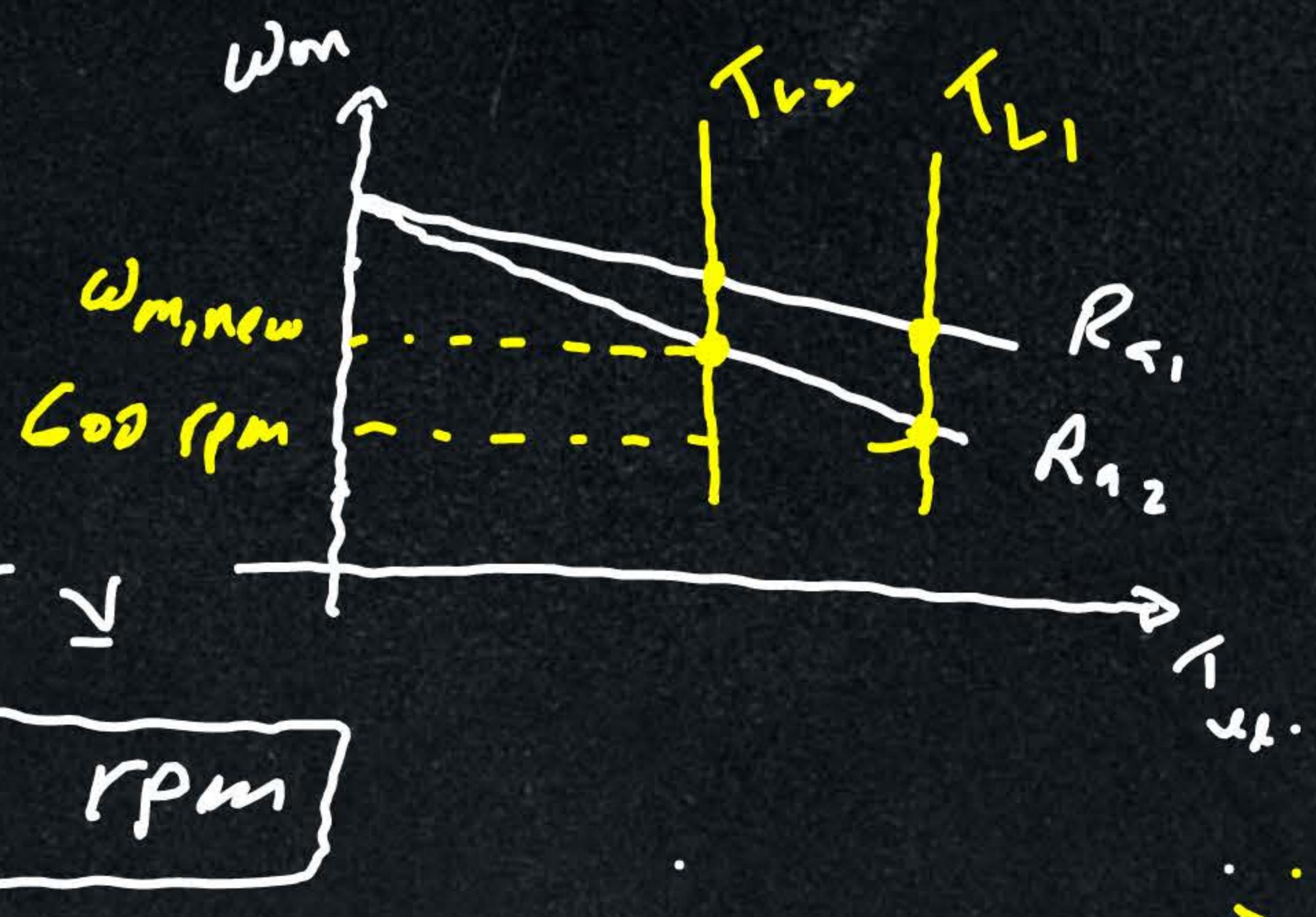
$$\frac{e_{a_2}}{e_{a_1}} = \frac{n_2}{1000} = \frac{189.5}{232} \Rightarrow n_2 : 803 \text{ rpm}$$



Principle of DC machine drive

$$y = \frac{x}{z}$$


KVL in the armature circuit

$$V_a = R_a i_a + K\phi_L \omega_m \Rightarrow \omega_m = \frac{V_a - R_a i_a}{K\phi_L}$$


Armature control: Ideal for speeds lower than $\omega_{m,r}$, ϕ_L

$$\phi_L = \phi_{L,r} \Rightarrow \omega_m = \frac{V_a - R_a i_a}{K\phi_{L,r}} \approx \frac{V_a}{K\phi_{L,r}}$$

$$\Rightarrow \omega_m \propto V_a$$

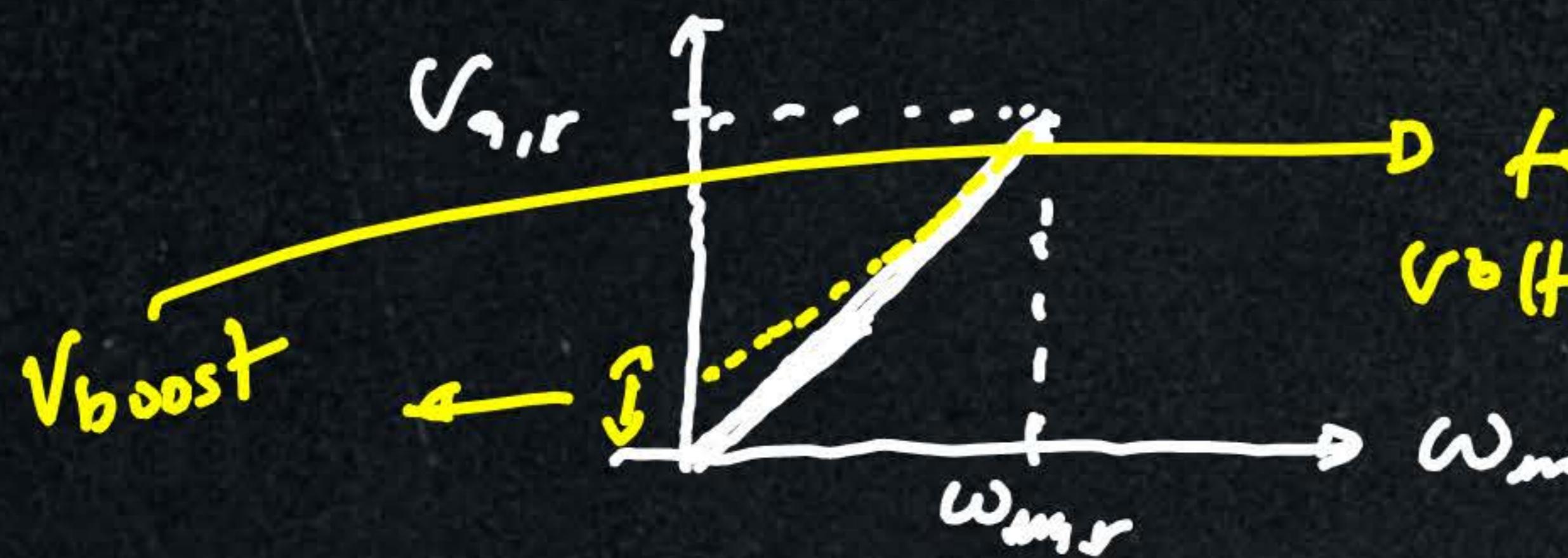

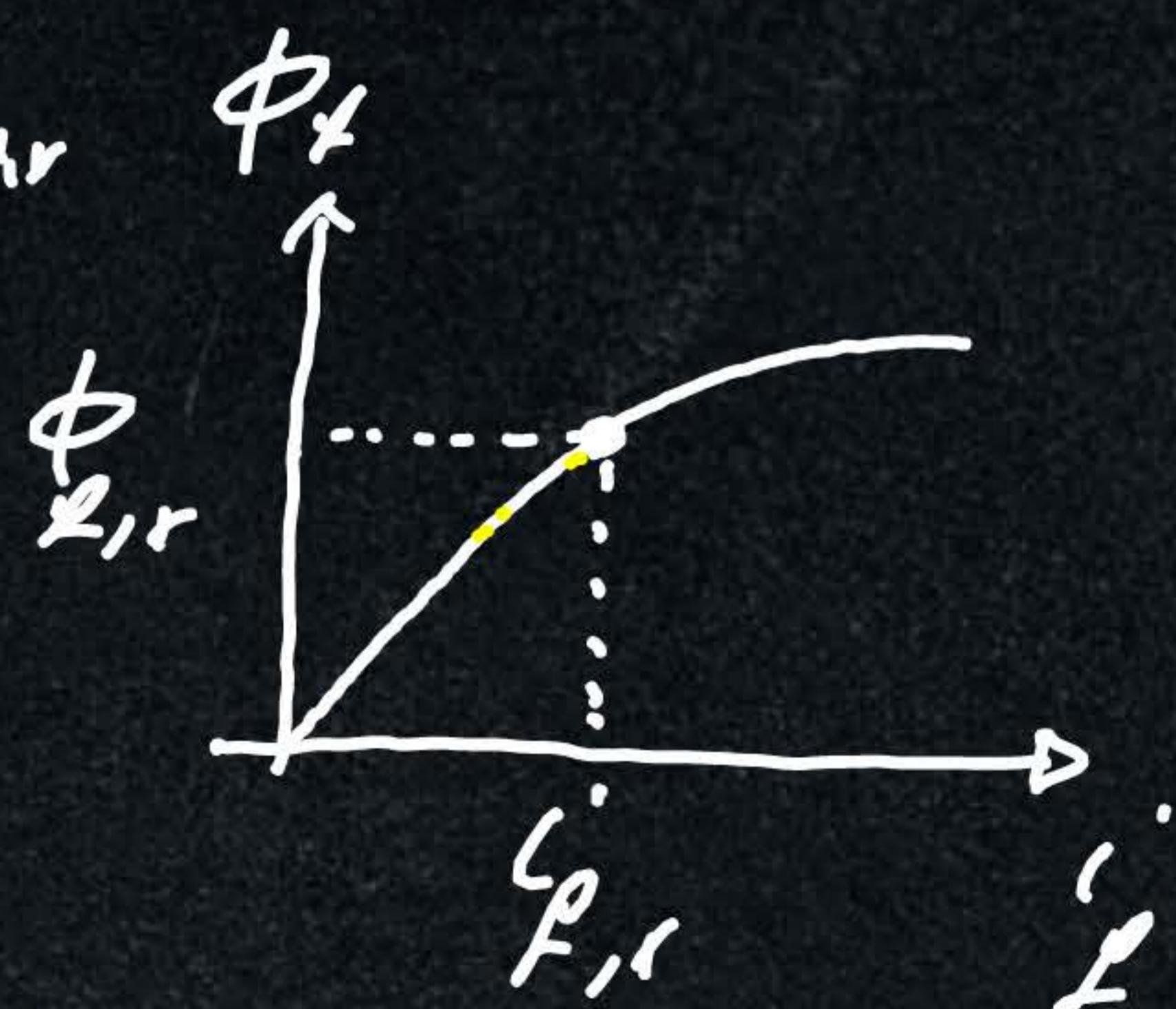to compensate the voltage drop across R_a .




Field control

$$V_a = V_{a,r} \Rightarrow \omega_m = \frac{V_{a,r}}{K\phi_L} \Rightarrow \phi_L \propto \frac{1}{\omega_m} \Rightarrow \phi_L = \phi_{L,r} \cdot \frac{\omega_{m,r}}{\omega_m}$$

$$\phi_L \omega_m = A$$

$$\phi_{L,r} \omega_{m,r} = \phi_L \omega_m \Rightarrow \phi_L = \phi_{L,r} \frac{\omega_{m,r}}{\omega_m}$$

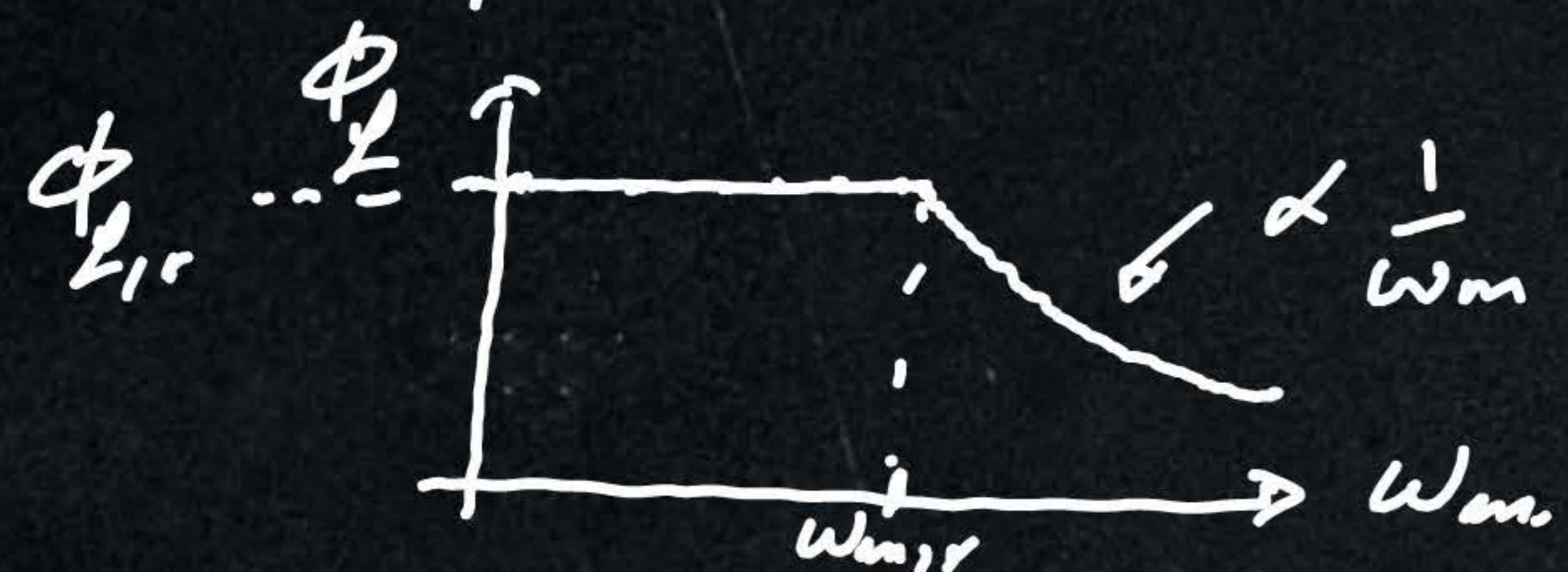Ideal for speeds above than $\omega_{m,r}$



Armature and field control

Assume that $i_a = i_{a,r} = \text{Rated current}$

$$\omega_m \leq \omega_{m,r}$$

$$\phi_f = \phi_{f,r}$$

$$V_a \propto \omega_m$$

$$T_{el} = K \phi_f i_{a,r} = \text{constant} = T_{el,r}$$

$$P_a = T_{el} \omega_m = T_{el,r} \omega_m \Rightarrow P_a \propto \omega_m$$

Armature control
mode

"constant
torque region"

$$\omega_m > \omega_{m,r}$$

2 kW

$$V_a = V_{a,r}$$


$$\phi_f = \phi_{f,r} \frac{\omega_{m,r}}{\omega_m}$$

$$\begin{aligned} T_{el} &= K \phi_f C_{a,r} = \frac{K \phi_{f,r} \omega_{m,r} C_{a,r}}{\omega_m} \\ &= T_{el,r} \cdot \frac{\omega_{m,r}}{\omega_m} = T_{el,r} \cdot \frac{1}{\omega_m} \end{aligned}$$



Field control
mode

constant power
region.
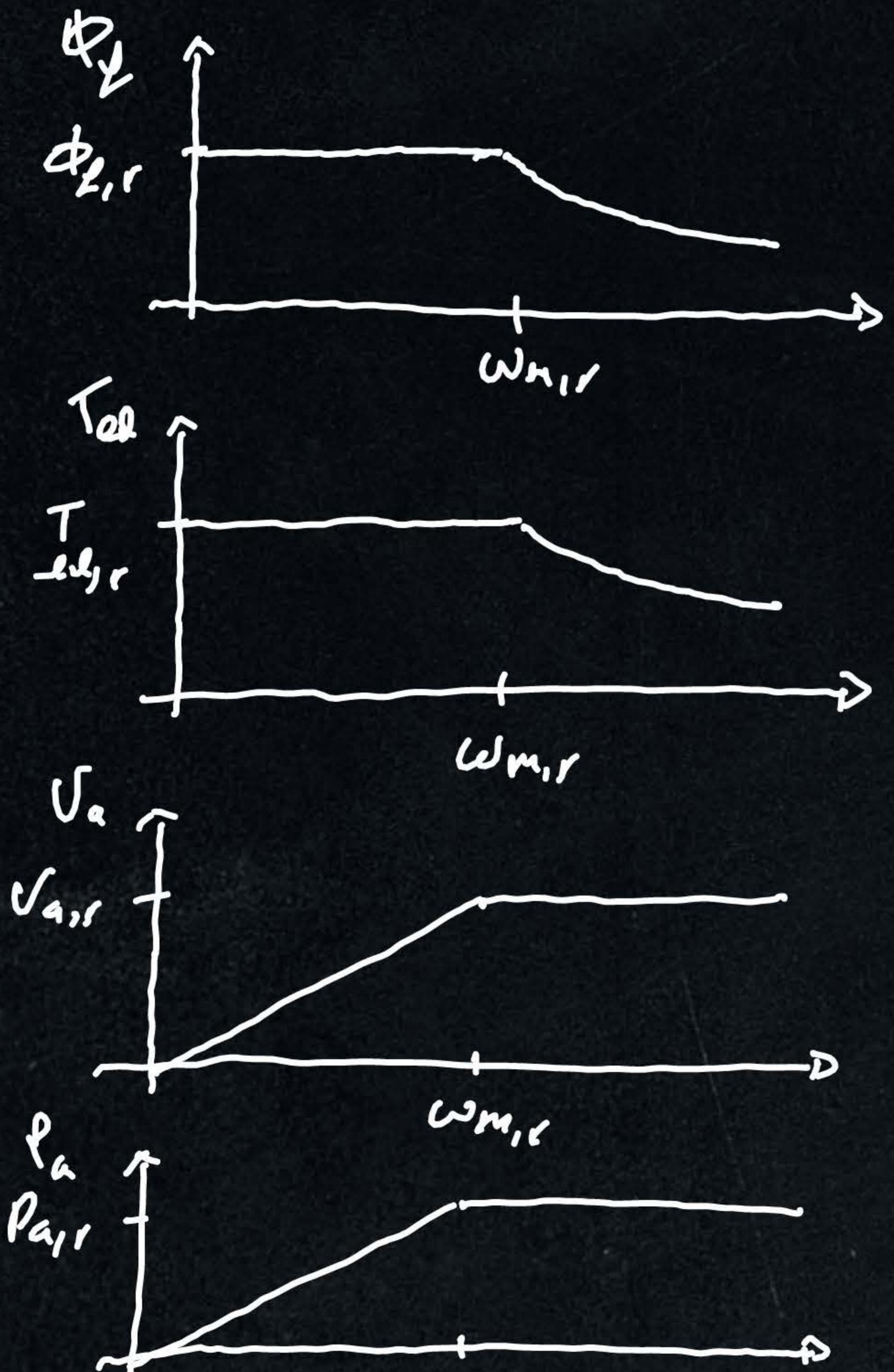
$$\begin{aligned} P_a &= T_{el} \omega_m = T_{el,r} \frac{\omega_{m,r}}{\omega_m} \cdot \omega_m \\ &= T_{el,r} \omega_{m,r} = P_{a,r} \end{aligned}$$




Control system of DC Machine Drive

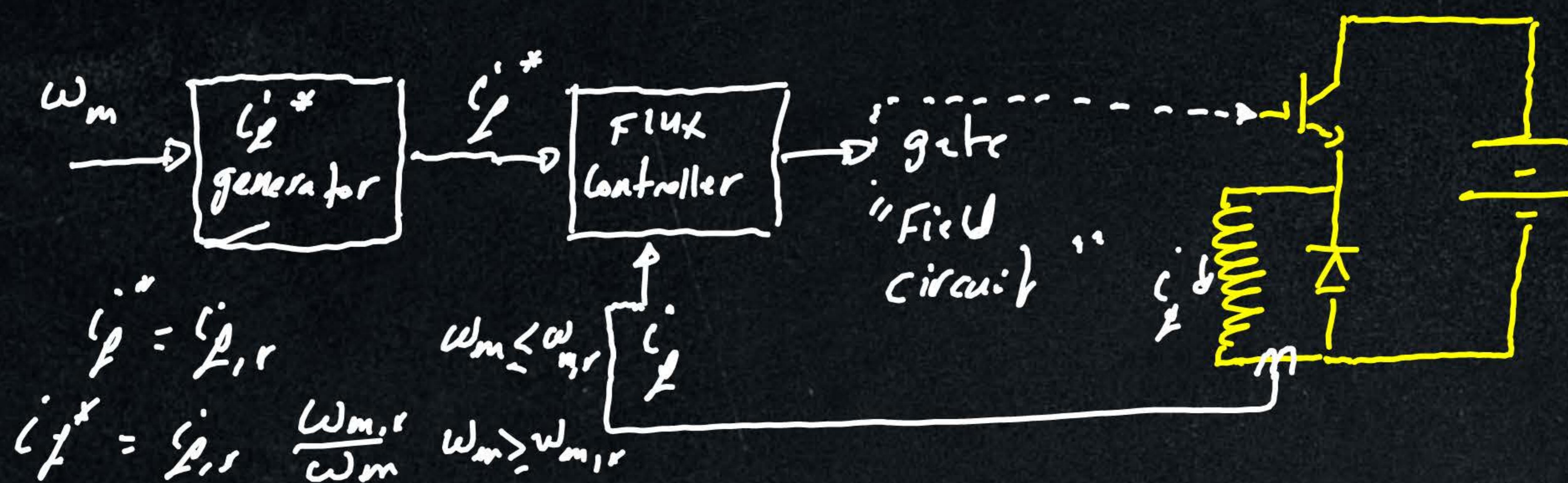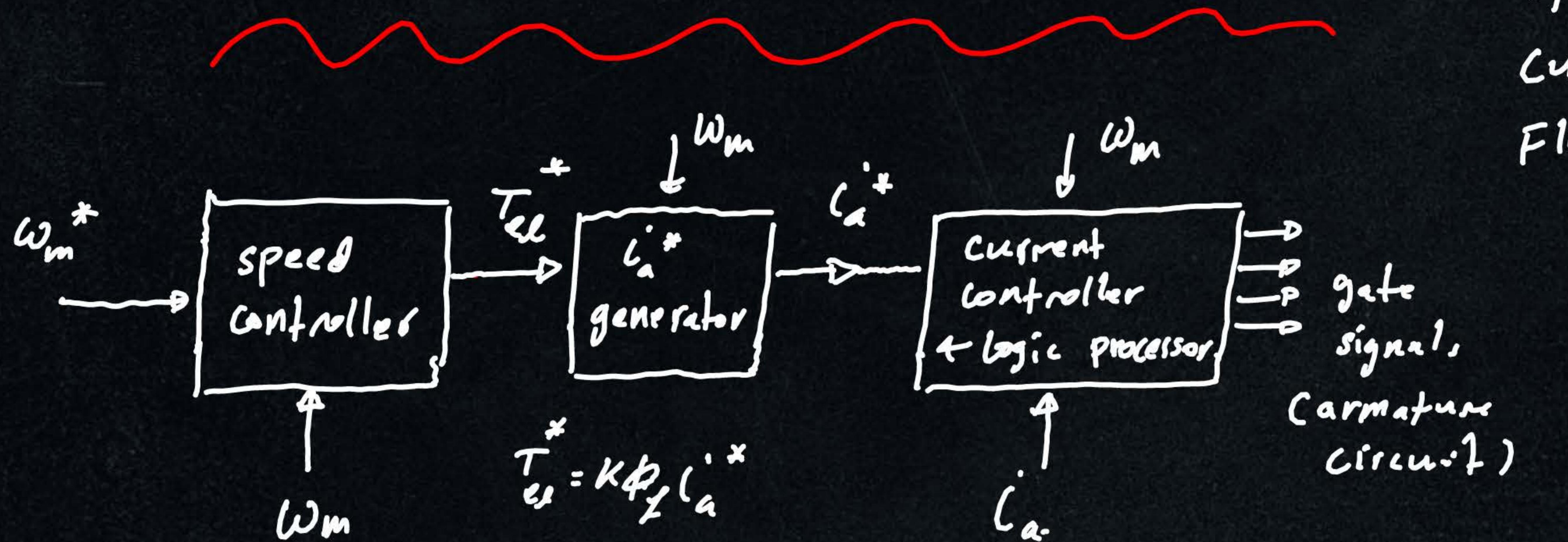


speed controller
current controller
Flux controller
* to reference

gate
signals,
(carmature
circuit)

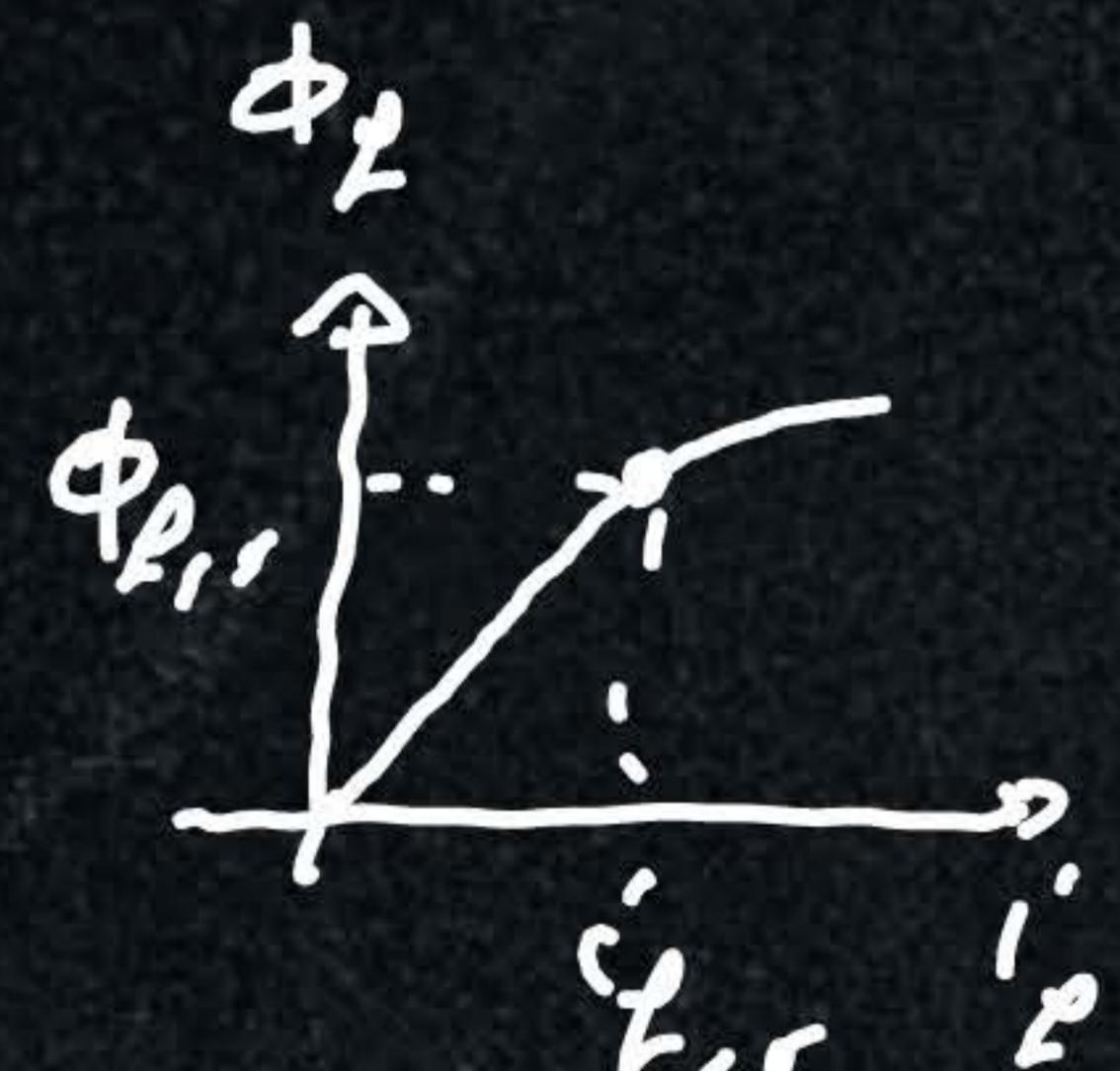

\dot{i}_a^* Generator

$$T_{el} = K\phi_f \dot{i}_a$$

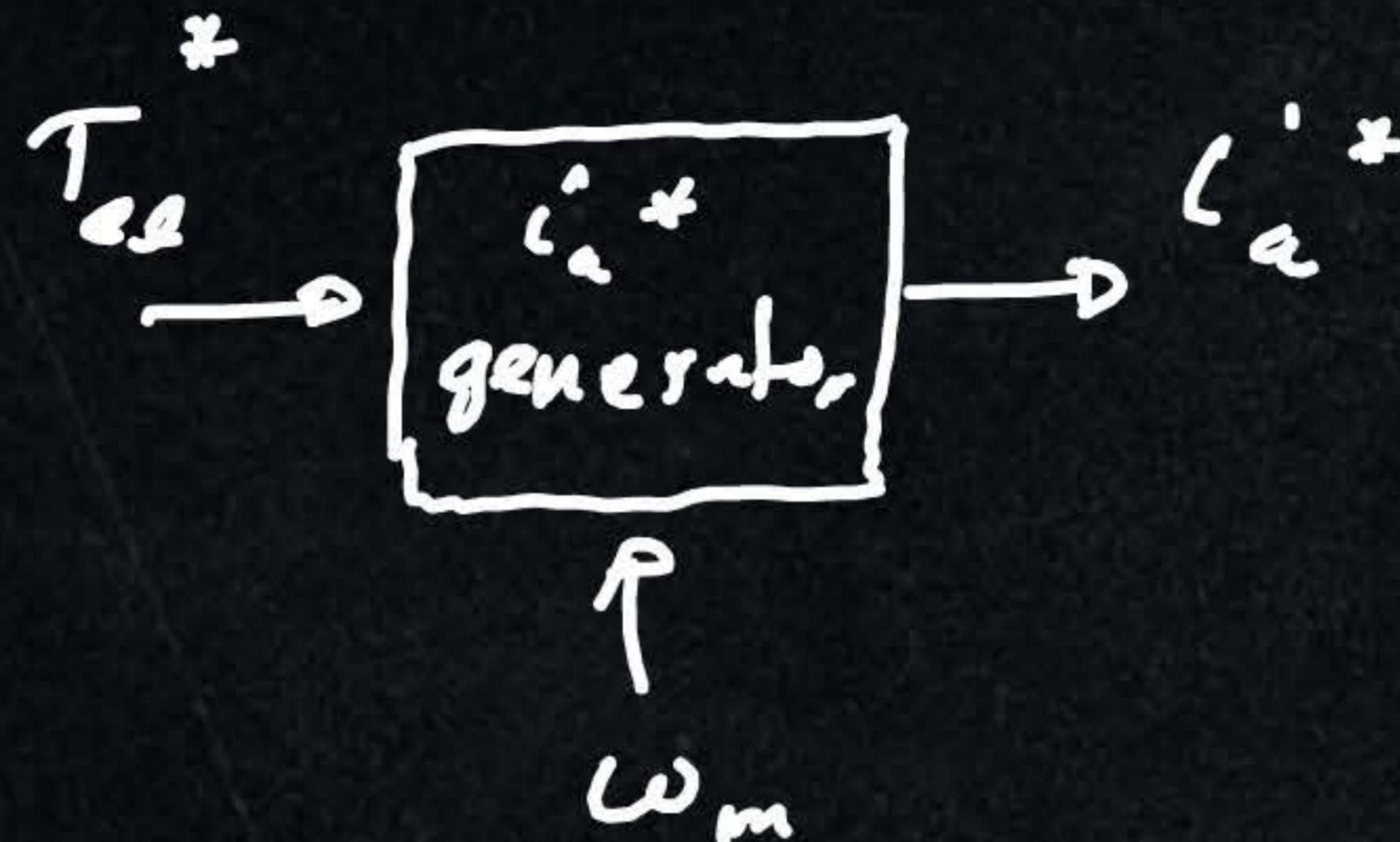


$$\omega_m \leq \omega_{m,r} \rightarrow \dot{i}_a^* = \frac{T_{el}^*}{K\phi_{f,r}}$$

$$\omega_m > \omega_{m,r} \rightarrow \dot{i}_a^* = \frac{T_{el} \omega_m}{K\phi_{f,r} \omega_{m,r}}$$

\dot{i}_p^* Generator
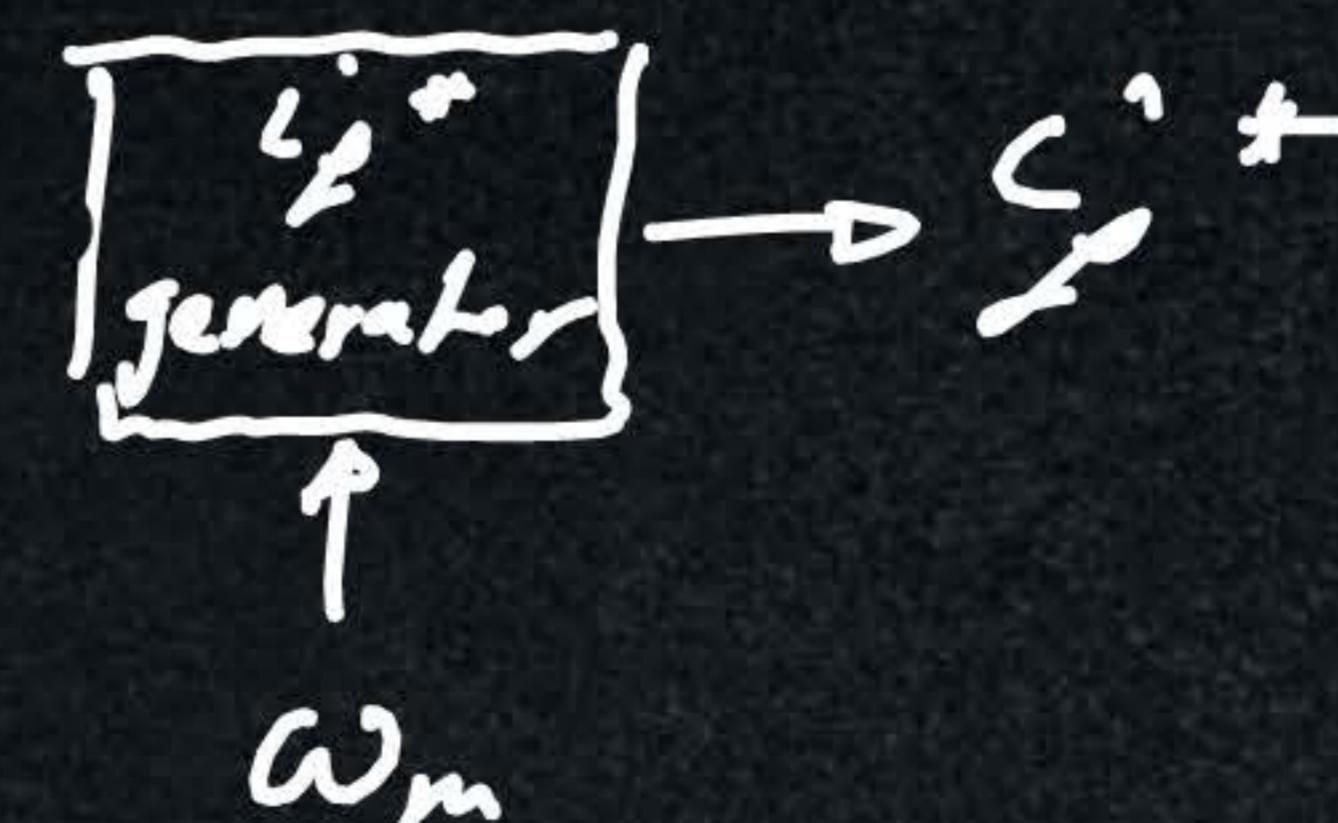
$$\omega_m \leq \omega_{m,r} \Rightarrow \dot{i}_p^* = \dot{i}_{p,r}$$




$$\omega_m > \omega_{m,r} \Rightarrow \dot{i}_p^* = \dot{i}_{p,r} \frac{\omega_{m,r}}{\omega_m}$$

Speed Controller


It is designed using Newton's 2nd law:-
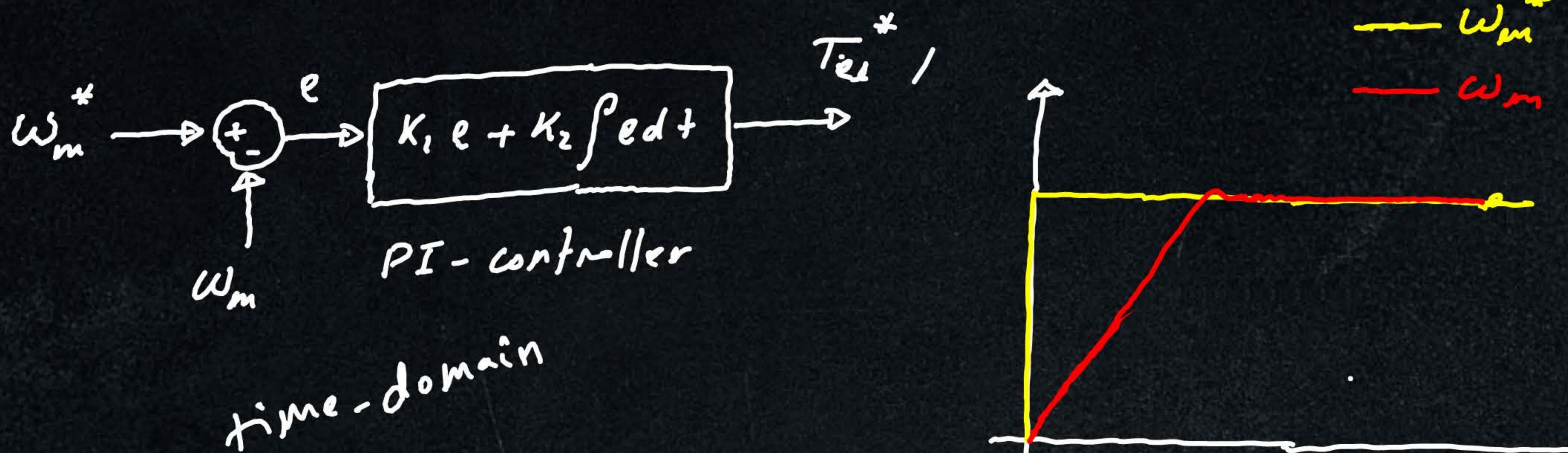
$$T_{ee} - T_d = J \frac{d\omega_m}{dt}$$



Design of speed controller in μ -domain

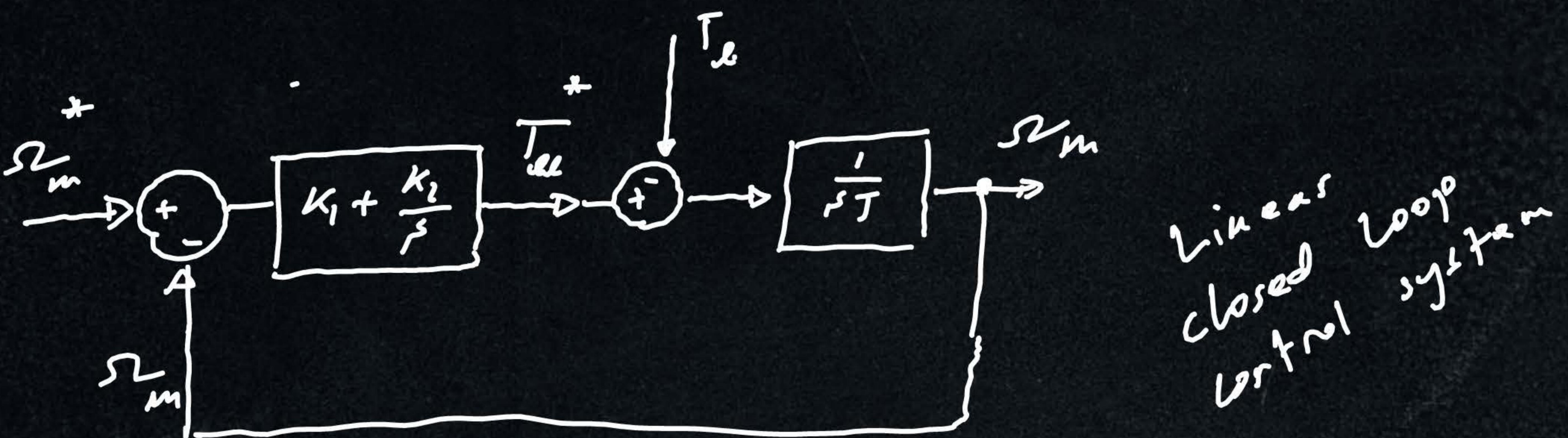
$$T_{ee} = T_L + T \frac{d\omega_m}{dt} \xrightarrow{\text{Laplace}} T_{ee} = T_L + \mu T \omega_m$$



$$\omega_m = T_f \omega_m^* + T_2 T_L$$

$$\omega_{m,ss} : \omega_m(t \rightarrow \infty) = \omega_m^* ??$$

$$T_1 : T_L = 0$$

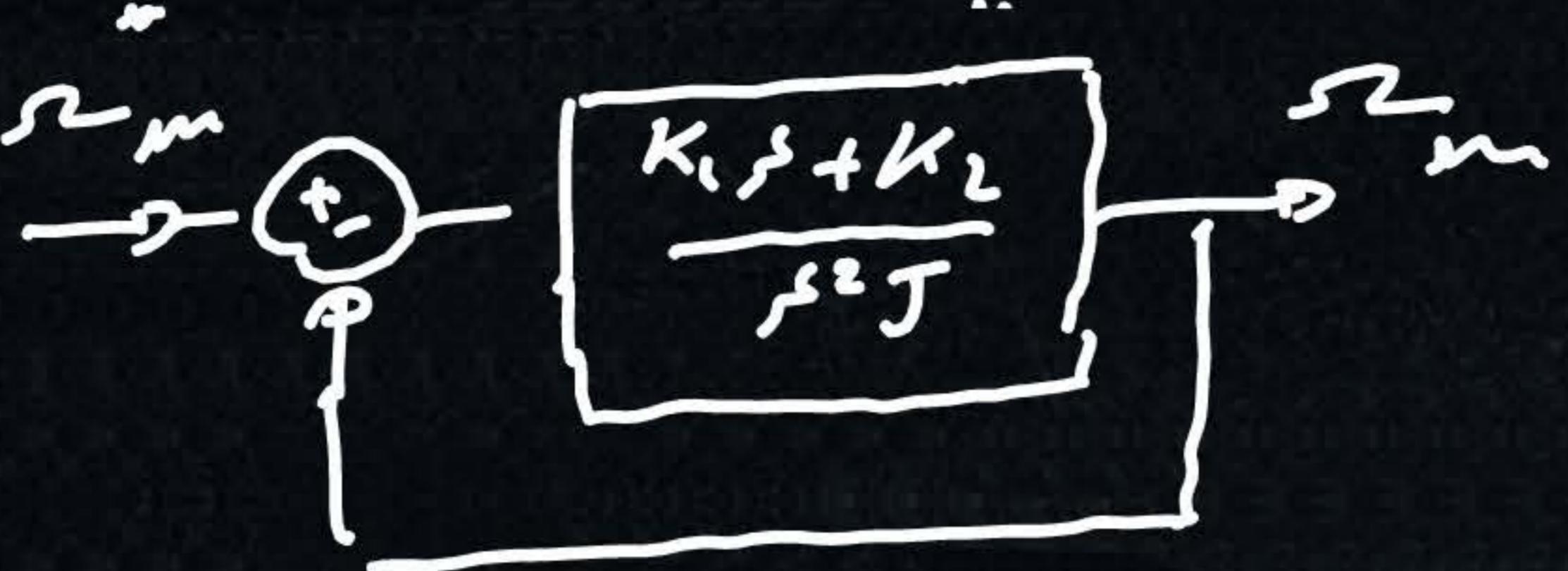

$$T_1 = \left. \frac{u_m}{u_m^*} \right| = \frac{G}{1 + GH}; \quad G = \frac{K_1 s + K_2}{s^2 J}$$

$$T_L = 0$$

$$H = 1$$

$$T_1 = \frac{\frac{K_1 s + K_2}{s^2 J}}{1 + \frac{K_1 s + K_2}{s^2 J}} = \frac{K_1 s + K_2}{s^2 J + K_1 s + K_2} = \frac{K_1}{J} \left[\frac{s + K_2 / K_1}{s^2 + \frac{K_1}{J} s + \frac{K_2}{J}} \right]$$

$s^2 + 2\zeta \omega_n^2 s + \omega_n^2$


ζ : damping ration


ω_n : Natural frequency

$\zeta < 1$ Under-damped



$\zeta = 1$ critically-damped

$\zeta > 1$ over-damped

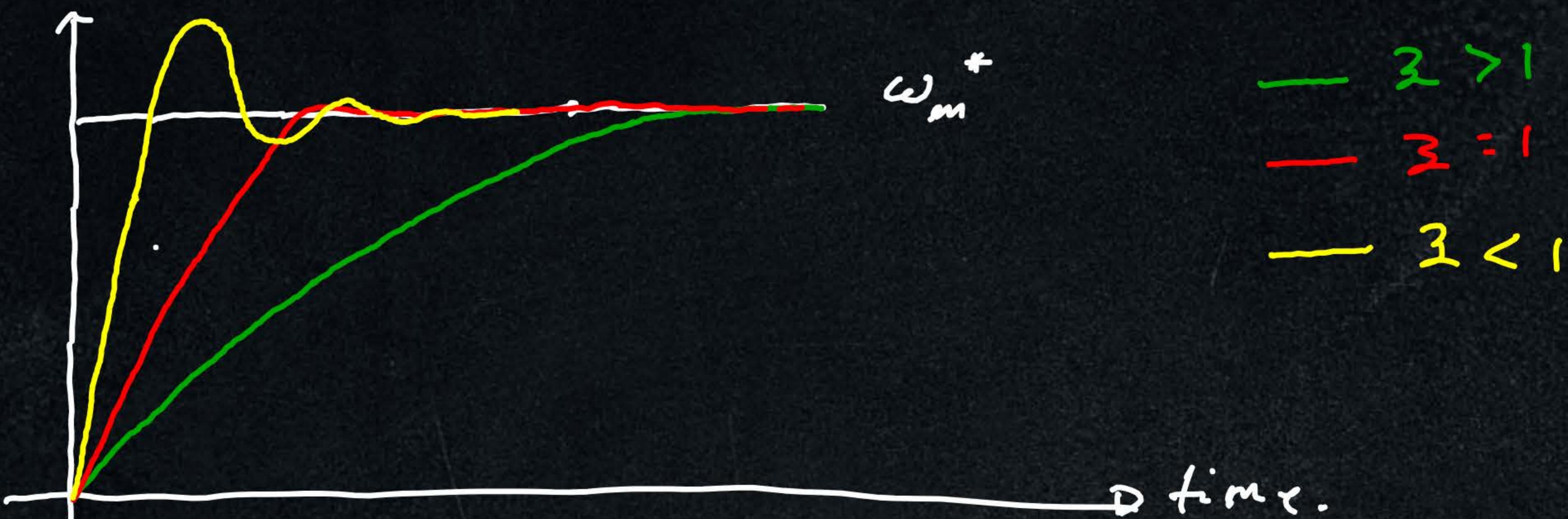

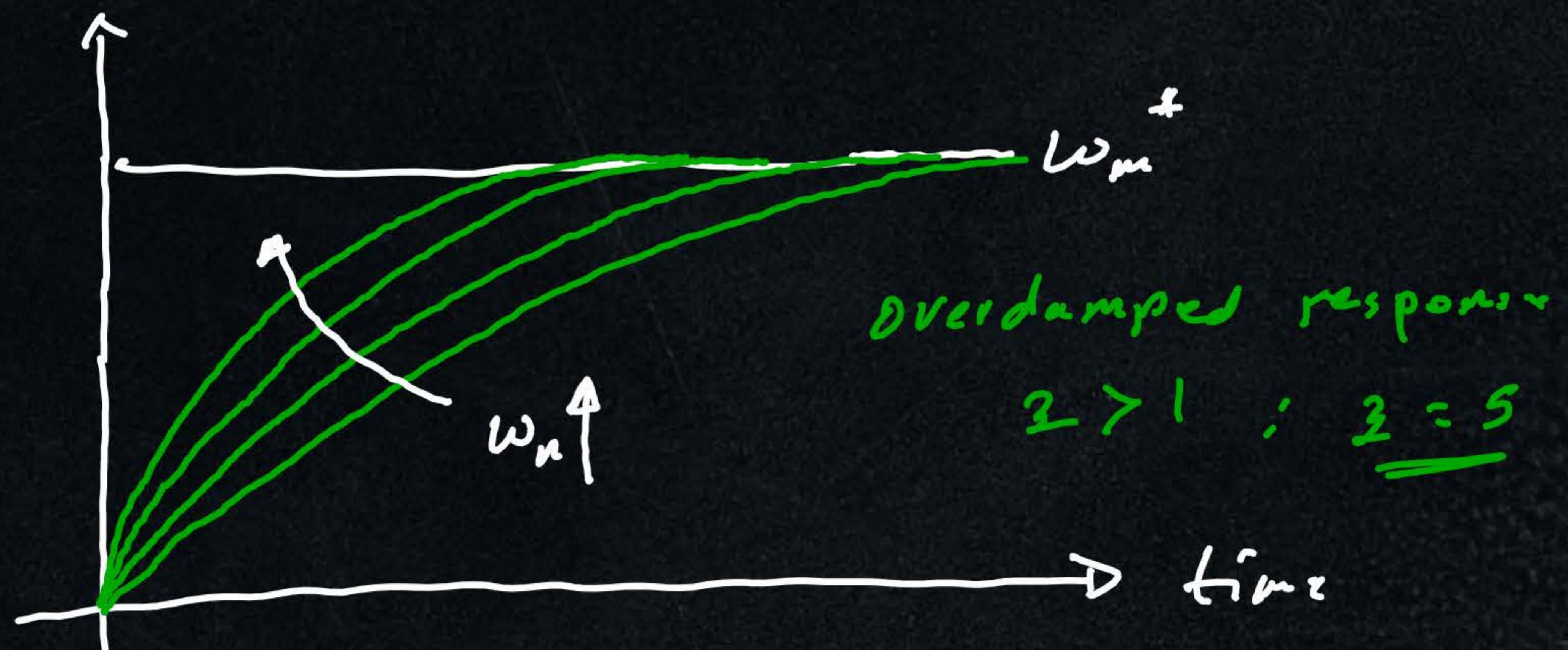
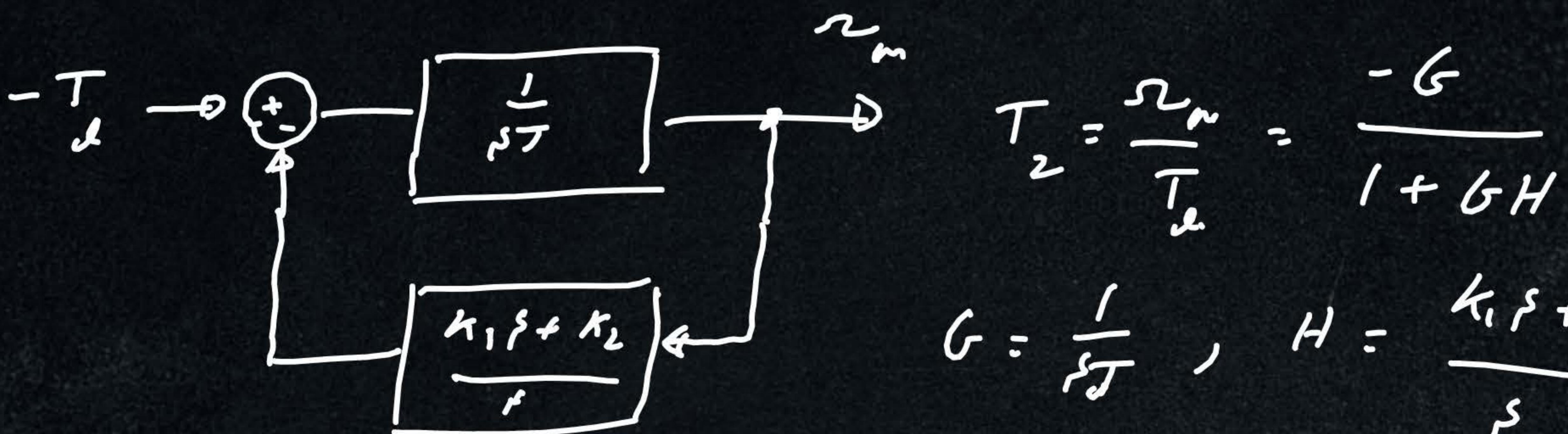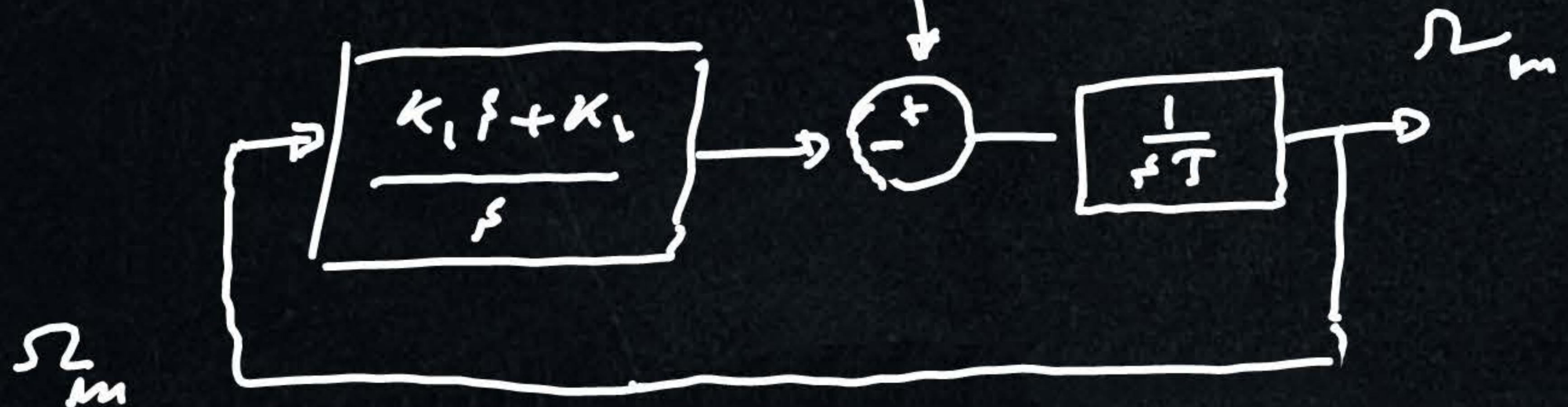
$$T_2: \dot{r}_m^* = 0 ; \quad T_2 = \frac{\dot{r}_m^*}{T_d} \mid \dot{r}_m^* = 0 = -T_d$$



$$T_2 = \frac{r_m}{T_d} = \frac{-G}{1 + GH}$$

$$G = \frac{1}{sT}, \quad H = \frac{K_1 s + K_2}{s}$$

$$T_2 = - \left[\frac{\frac{1}{sT}}{1 + \frac{K_1 s + K_2}{sT}} \right] = \frac{-s}{s^2 T + K_1 s + R_L} = -\frac{1}{T} \frac{s}{s^2 + \frac{K_1}{T} s + \frac{R_L}{T}}$$