

# DC Machine Drive

Theory of operation  
of DC Motor



Electro-magnet force:

$$F_e = i_a \vec{l} \times \vec{B}$$


Electro-magnet torque:

$$T_{el} = \vec{r} \times \vec{F}_e$$
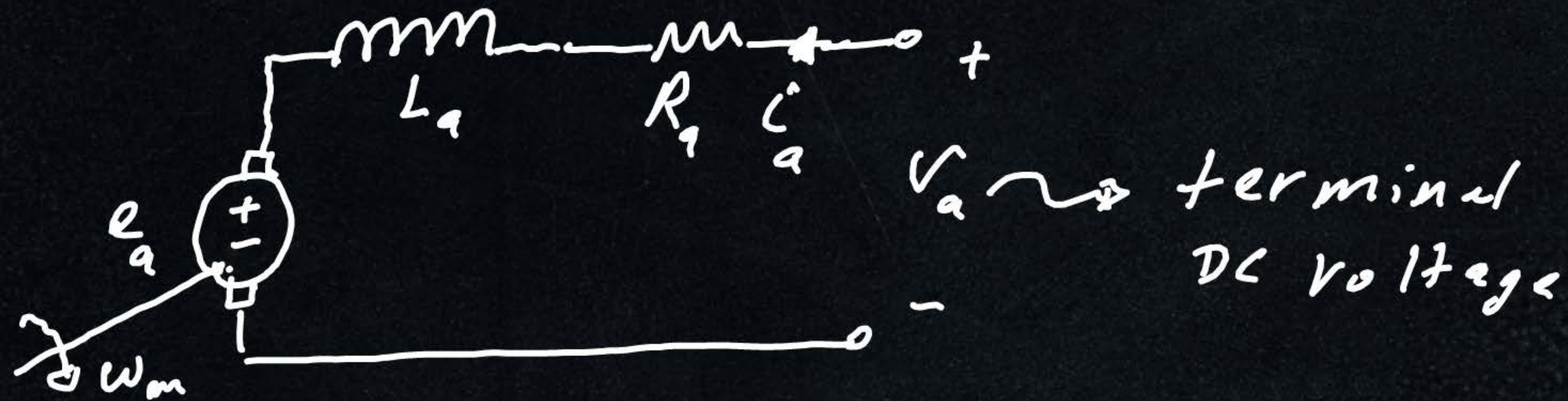
## operation of DC motor

- x The electric current,  $I_a$ , passes through the armature winding via a commutator.
- x When  $I_a$  passes through the armature winding in a magnetic field, a magnetic force,  $F_e$ , is induced ( $\vec{F}_e = I_a \vec{l} \times \vec{B}$ ).
- x The magnetic force produces a torque, which turns the DC motor.

Equivalent circuit of DC motor armature :-



$R_a$  &  $L_a$  are the resistance  
& self-inductance of armature  
winding

$e_a$ : Back emf voltage or induced voltage


$$e_a = K \phi \omega_m$$

induced voltage  $\mathcal{E}_a = k \phi \omega_m$  rotor's speed


constant depends on the machine structure

flux  $\phi$  machine's

$\phi_f = L_f i_f$

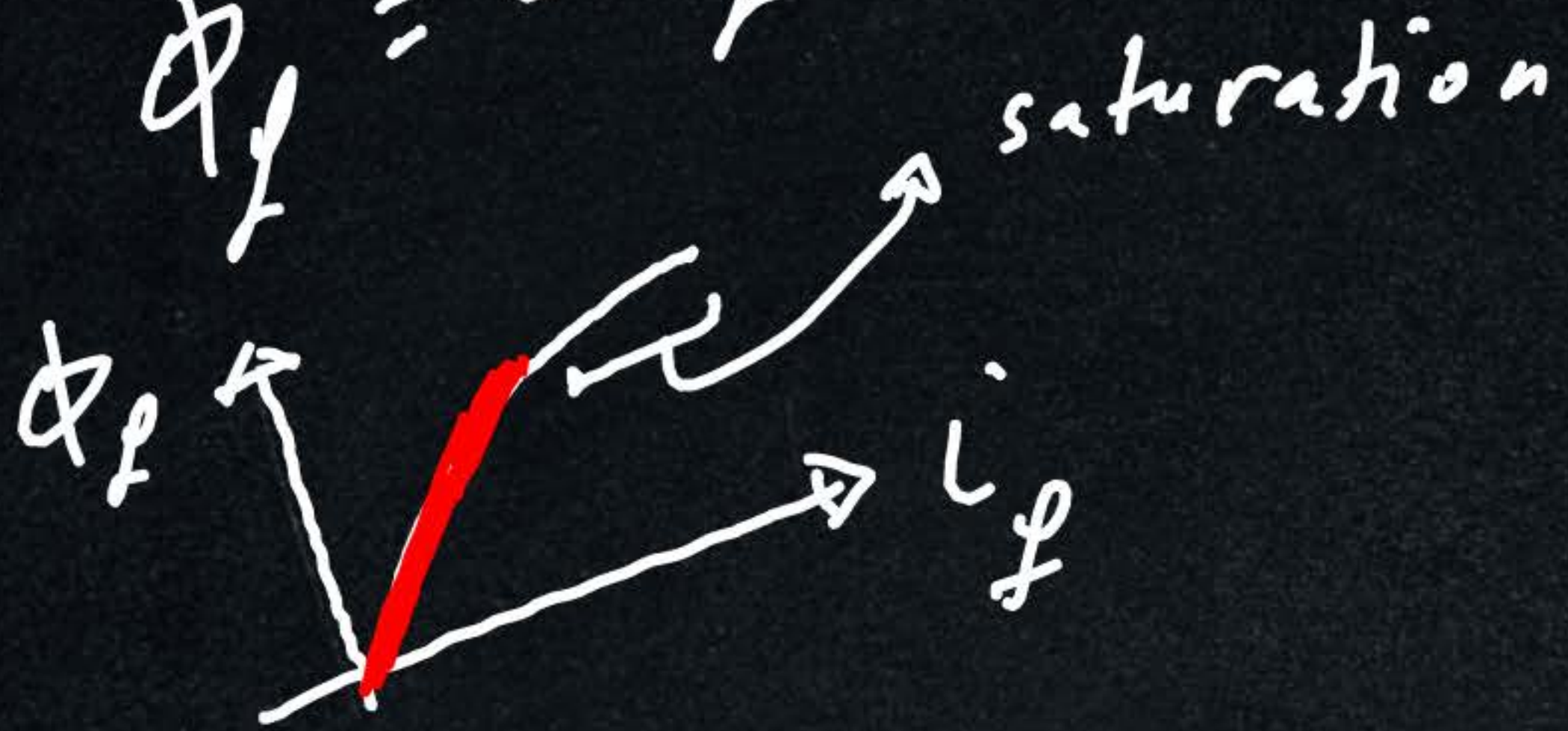

# Torque Equation

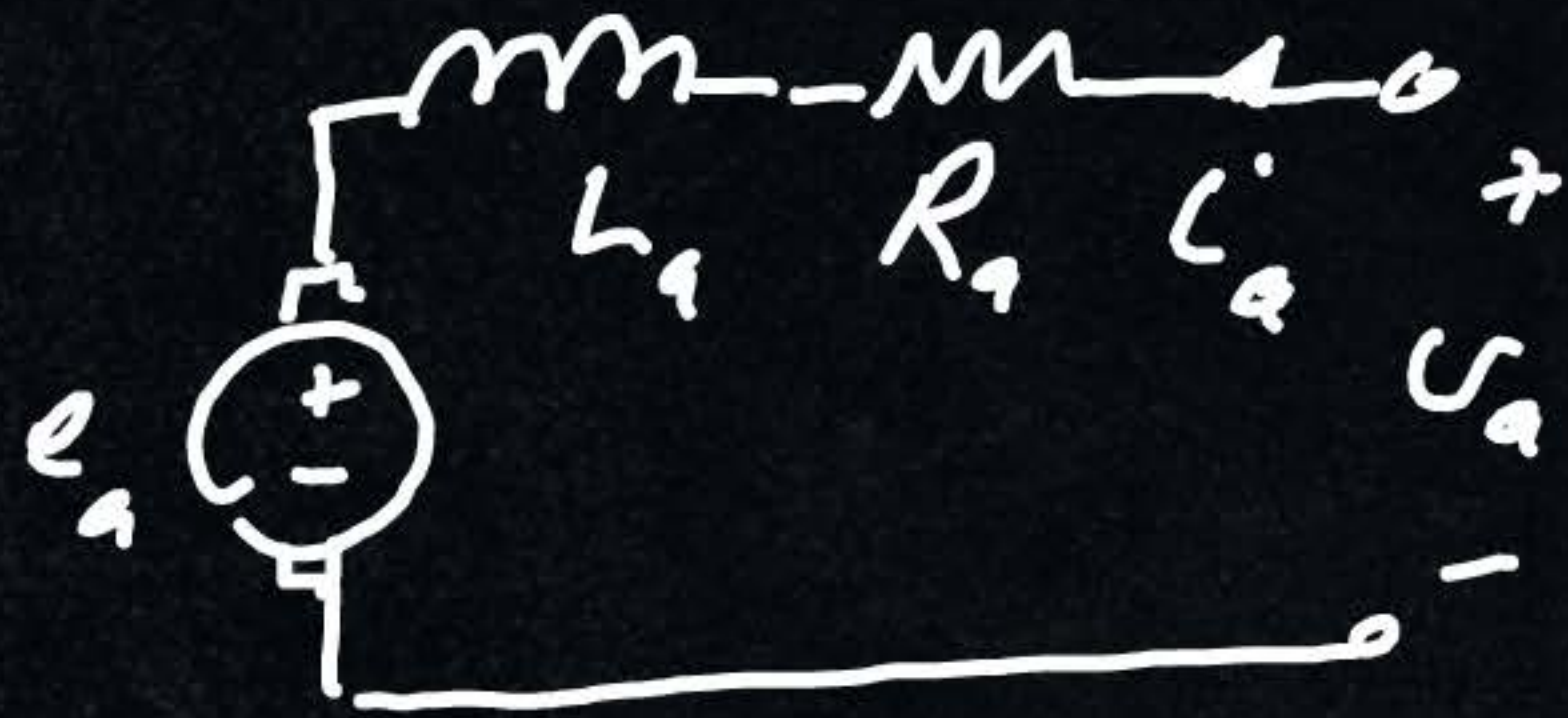

KVL in the armature circuit :-

$$V_a = R_a i_a + L_a \frac{di_a}{dt} + e_a$$

under SS condition

$$\rightarrow \frac{di_a}{dt} = 0$$

$$\Rightarrow V_a = R_a i_a + e_a$$

$$V_a = R_a i_a + e_a$$

$$V_a i_a = R_a i_a^2 + e_a i_a$$

$\underbrace{V_a i_a}$   
↓  
Total  
input  
power

$\underbrace{R_a i_a^2}$   
↓  
Armature  
copper  
losses

$\underbrace{e_a i_a}$   
↓  
Air-gap power

"Effective power  
that has been  
transformed to  
mechanical power"

$$P_a = e_a i_a = (k \phi \omega_m) i_a$$

$$P_a = e_a \dot{L}_a = (k \phi_p \omega_m) \dot{L}_a$$

$$P_a = T_{rel} \omega_m$$

$$T_{rel} \omega_m = (k \phi_p \omega_m) \dot{L}_a$$

$$T_{rel} = k \phi_p \dot{L}_a$$

# Machine Equations (time-domain)

$$V_a = R_a I_a + L_a \frac{dI_a}{dt} + E_a$$

$$E_a = k \phi_f \omega_m = k' \omega_m \text{ "constant flux"}$$

$$T_{el} = k \phi_f I_a = k' I_a \text{ "constant flux"}$$

$$T_{el} = T_L + J \frac{d\omega_m}{dt} \text{ "Newton's 2<sup>nd</sup> Law"}$$

$$V_a \xrightarrow{L} V_a$$



## Machine Equations (s-domain)

$$V_a = (R_a + sL_a) I_a + E_a$$


$$E_a = k' \Omega_m$$

$$T_{el} = k' I_a$$

$$T_{el} = T_L + (sJ) \Omega_m.$$


$$V_a = (R_a + sL_a) I_a + E_a, \quad E_a = k' \omega_m$$
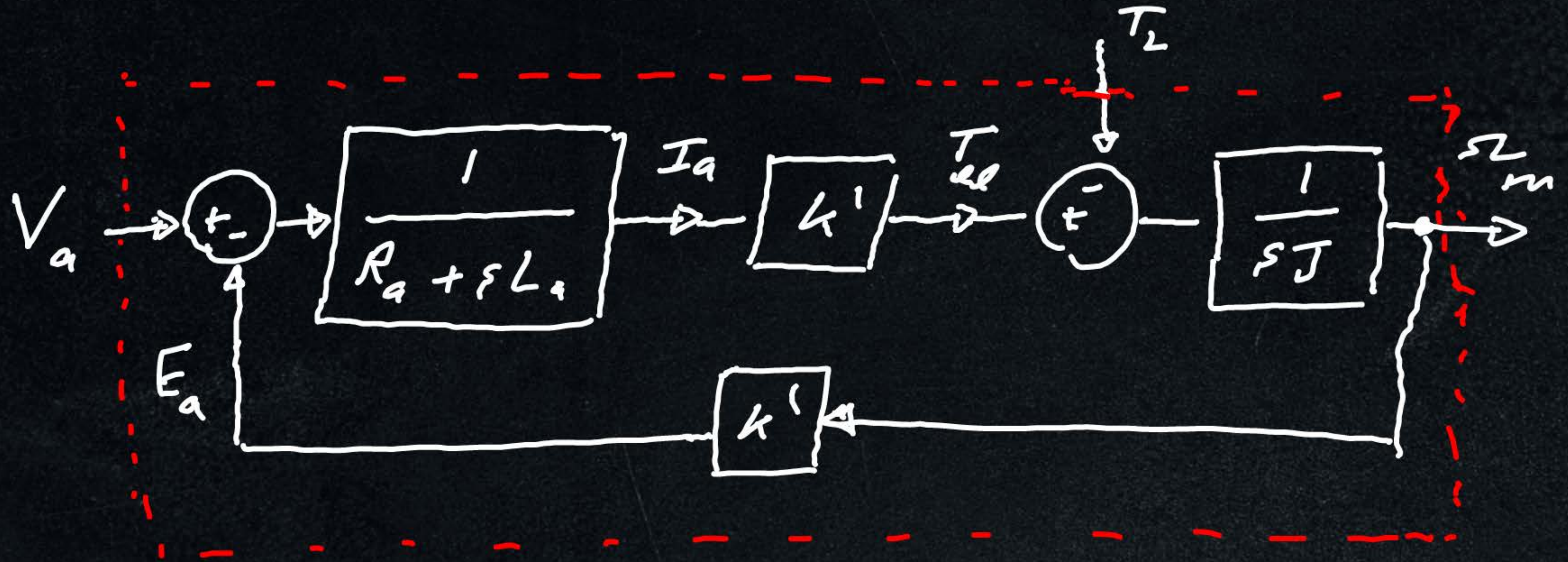
$$T_{el} = k' I_a, \quad T_{el} = T_L + sJ \omega_m$$



Block Diagram of DC Motor

# Block Diagram and Transfer Function

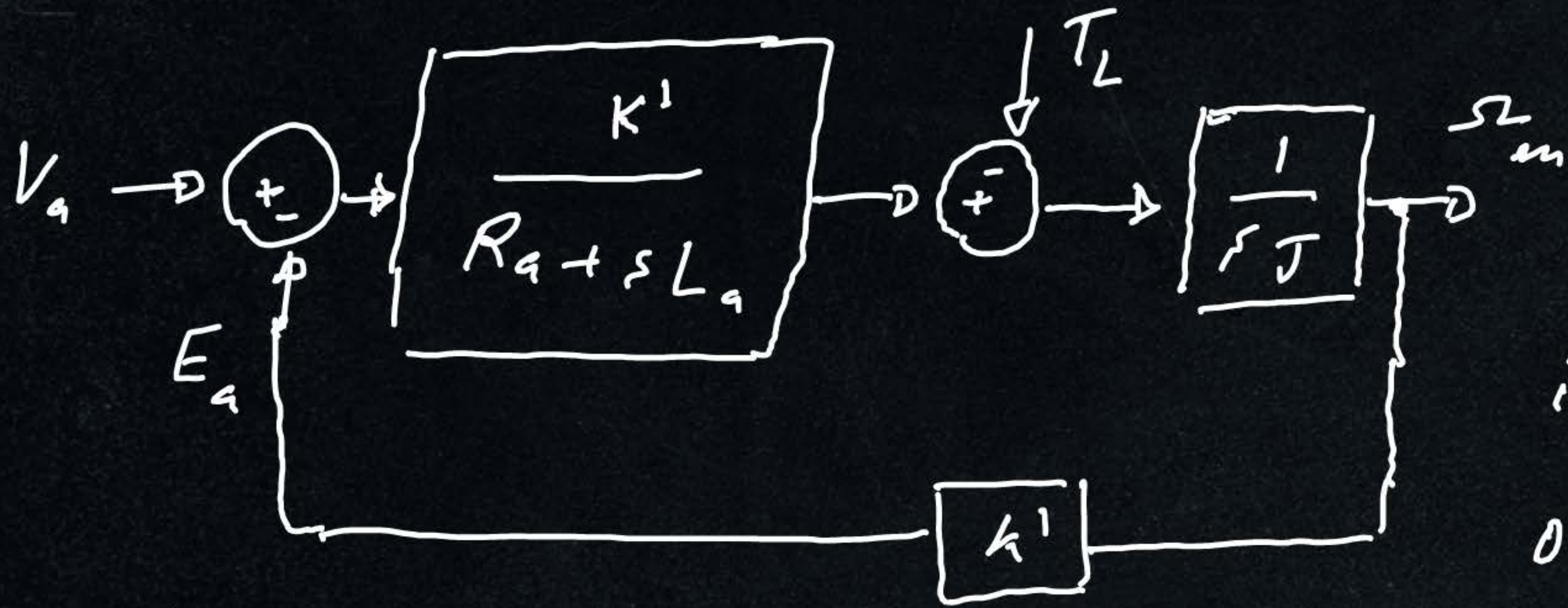


Linear system

inputs:  $V_a, T_L$   
output =  $\omega_m$

$$\omega_m = T_1 V_a + T_2 T_L$$

where  $T_1 = \omega_m / V_a$  when  $T_L = 0$   
 $T_2 = \omega_m / T_L$  when  $V_a = 0$

# Closed loop system

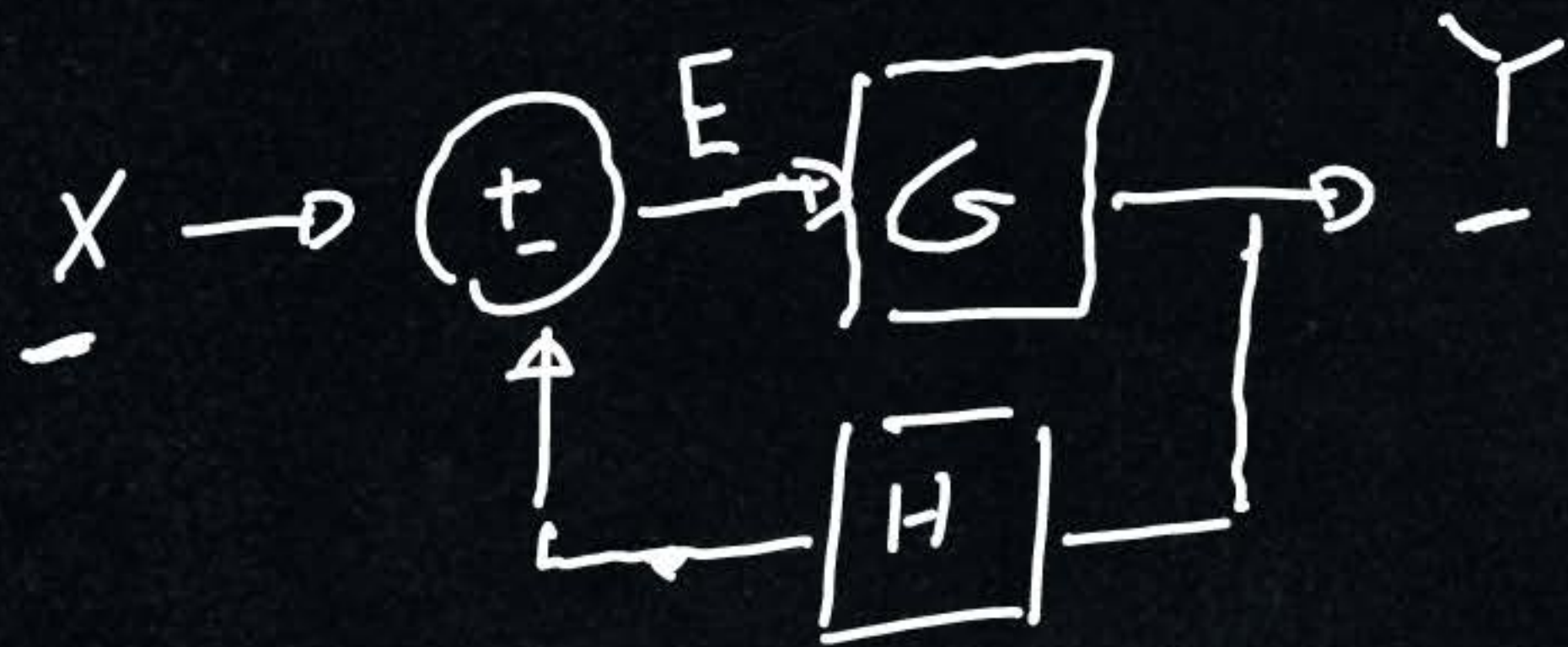

$G$ : Direct transfer function

$H$ : Feedback transfer function

$$Y = GE = G(X - HY)$$


$$Y = GX - GHY$$

$$\Rightarrow \frac{Y}{X} = \frac{G}{1 + GH}$$

$T_1$  ??

$T_2 = 0$

$G$

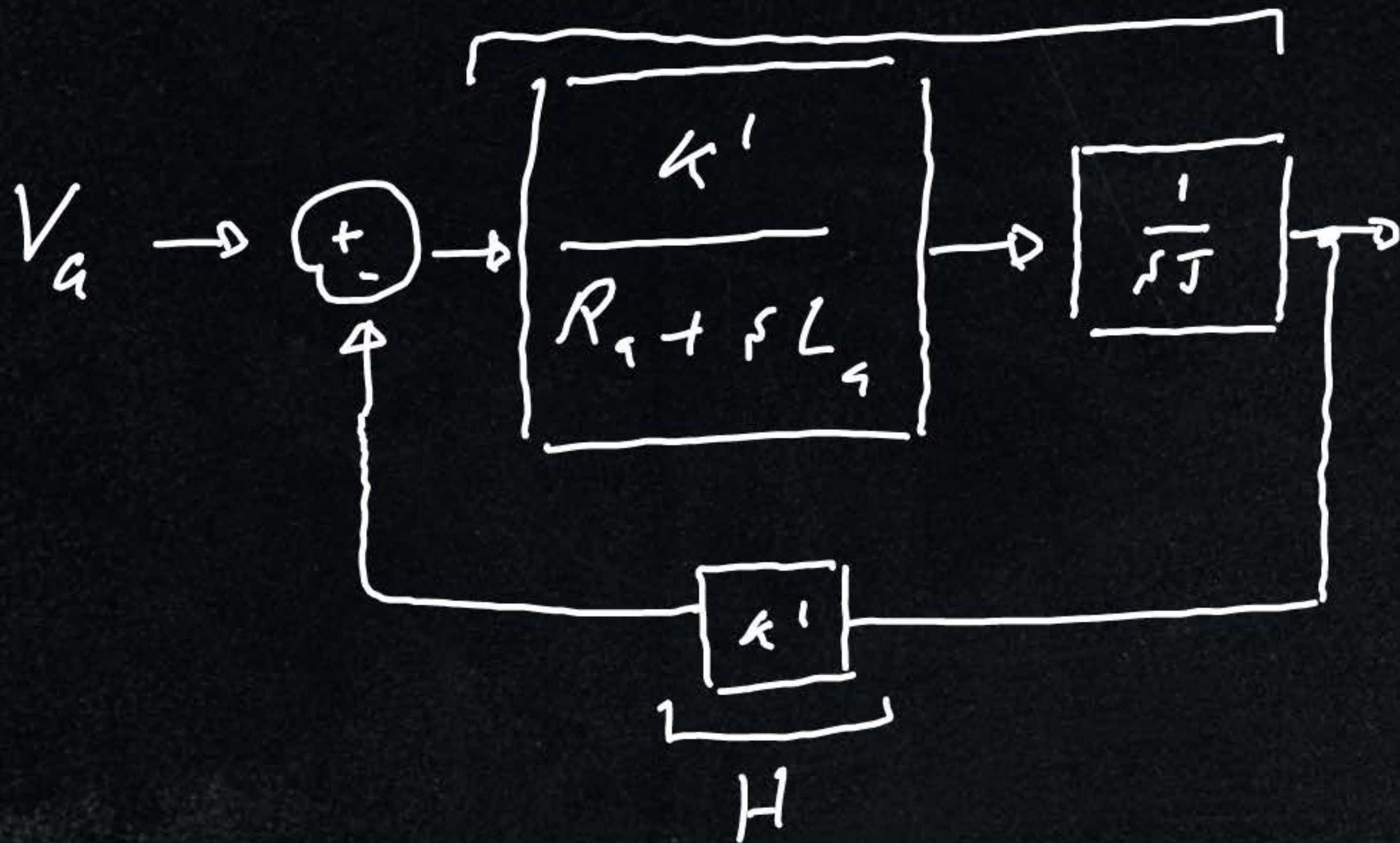


$\Omega_m$

$$G = \frac{k'}{sJ [R_a + sL_a]}$$


$$H = k'$$

$$T_1 = \frac{\Omega_m}{V_a} = \frac{G}{1 + GH}$$

$T_2$  ??  $V_a = 0$

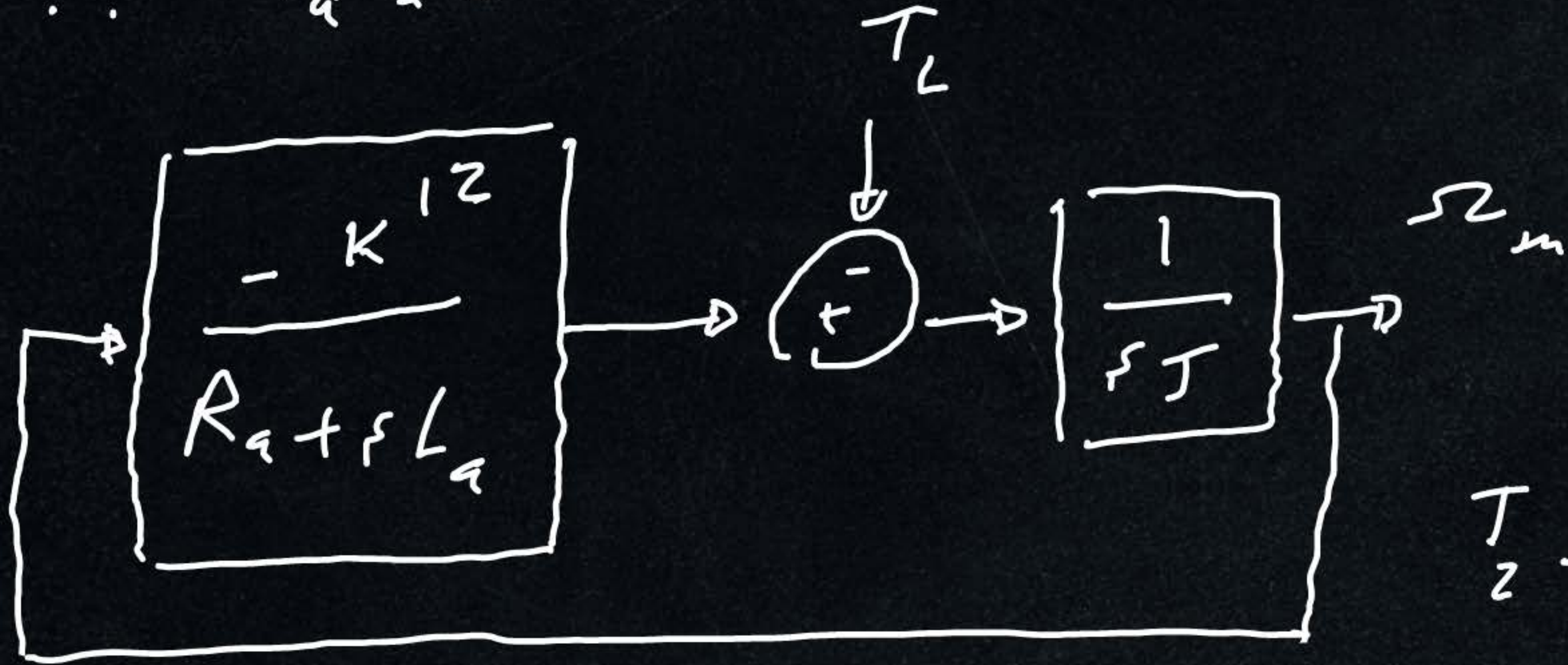
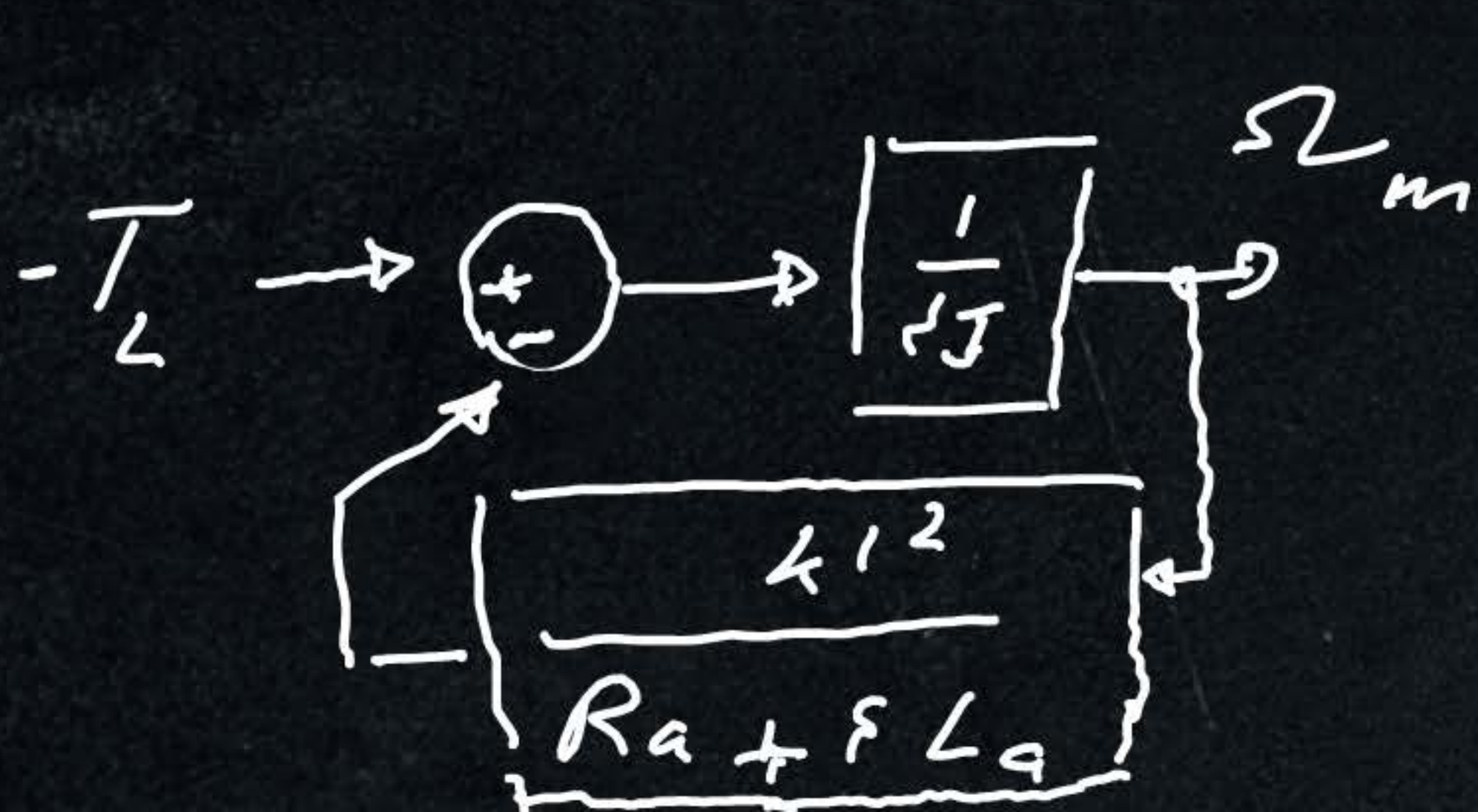
$$T_2 = \frac{-G}{1 + GH} = \frac{\Omega_m}{T_L}$$



$$G = \frac{1}{sJ}$$

$$H = \frac{k'2}{R_a + fL_a}$$


$$\Omega_m = T_1 V_a + T_2 T_L$$

## Field Excitation

- separately excited DC machine
- Shunt excited DC machine
- Series excited DC machine
- Compound DC machine
- permanent magnet DC machine (PMDC)


# Steady state speed-torque relations

① Separately & shunt

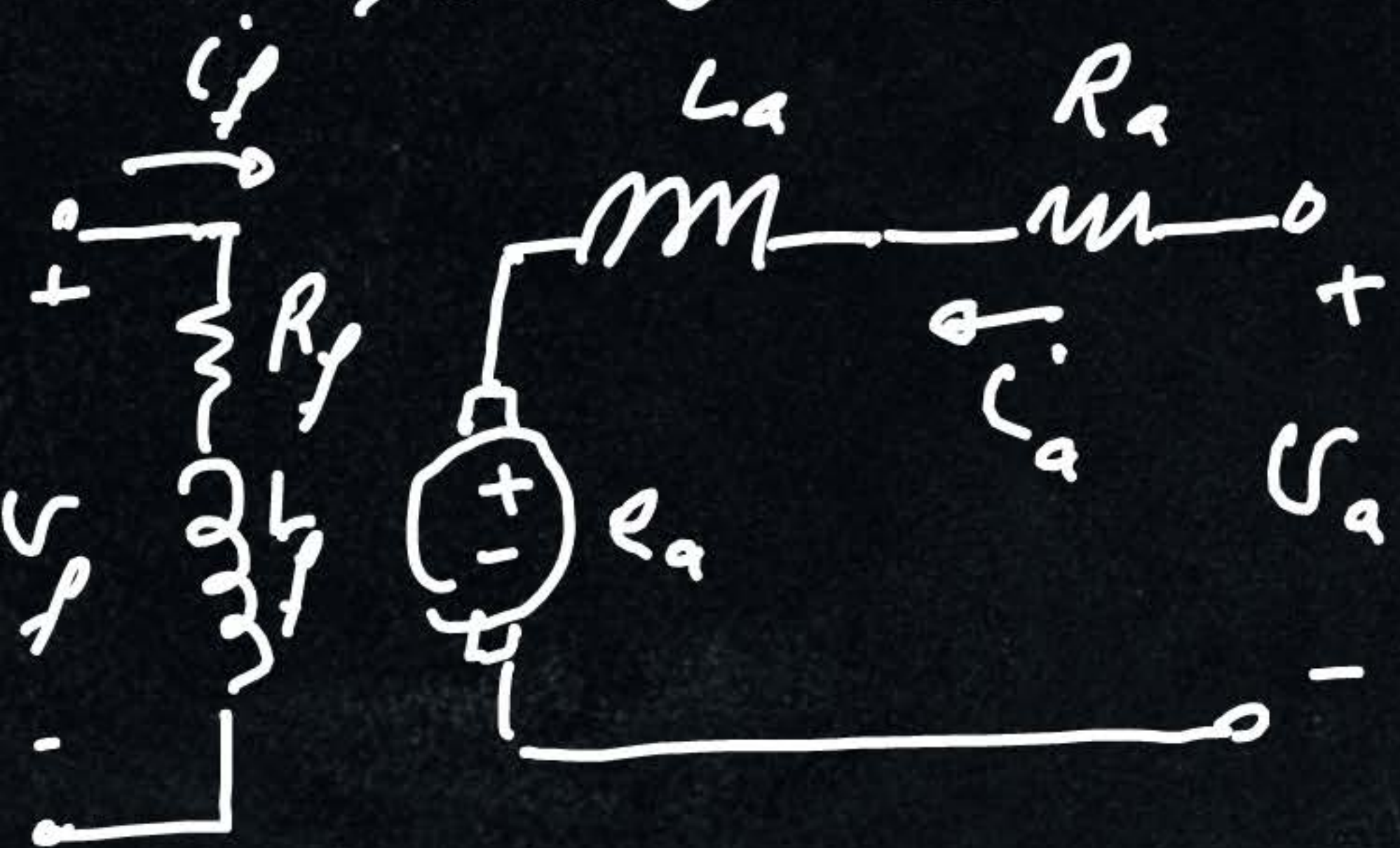

Field      armature

separately

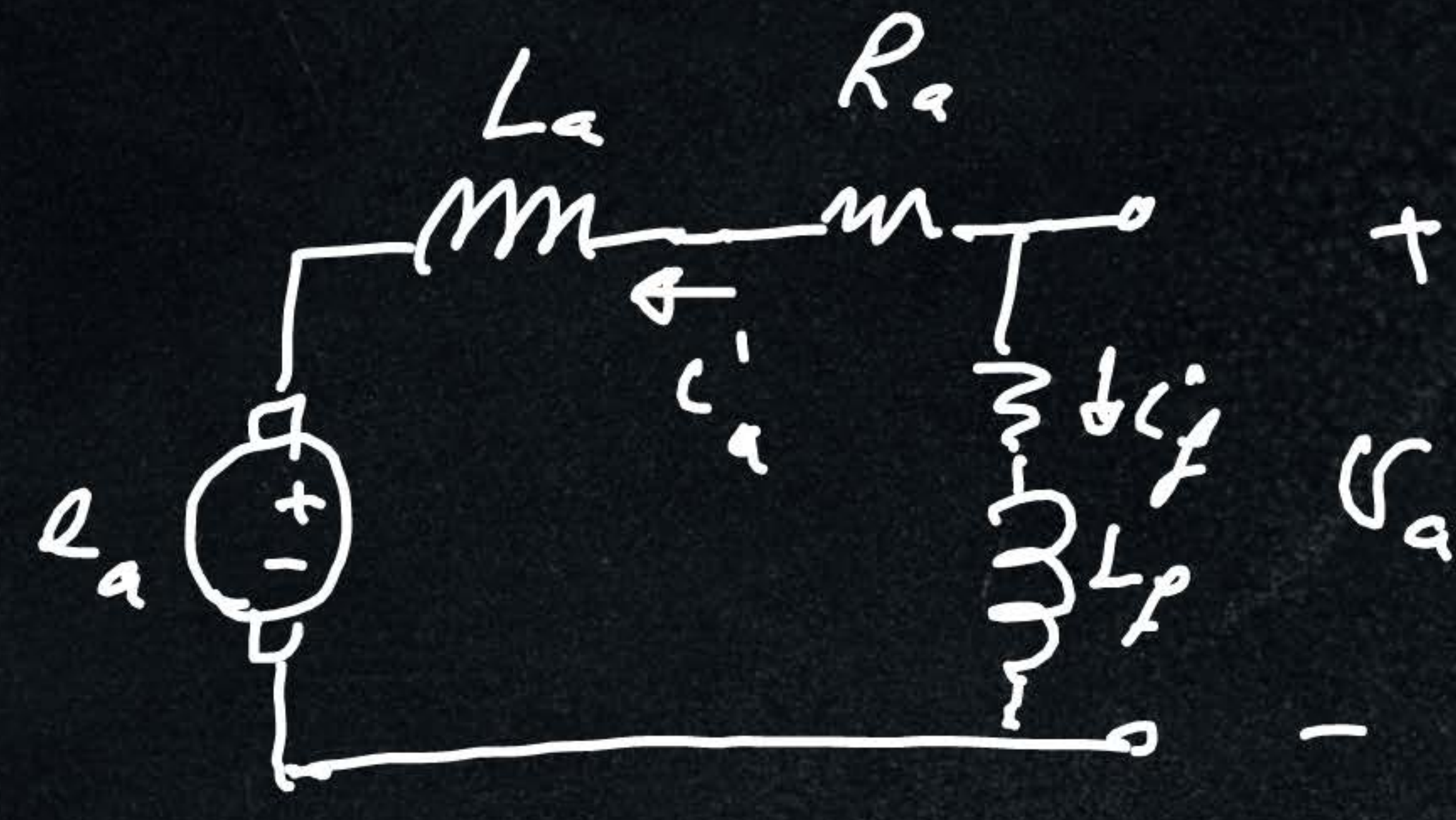

shunt




$$V_a = R_a I_a + k\phi_f \omega_m \text{ --- (1)}$$

$$T_{el} = k\phi_f I_a \Rightarrow I_a = \frac{T_{el}}{k\phi_f} \text{ --- (2)}$$

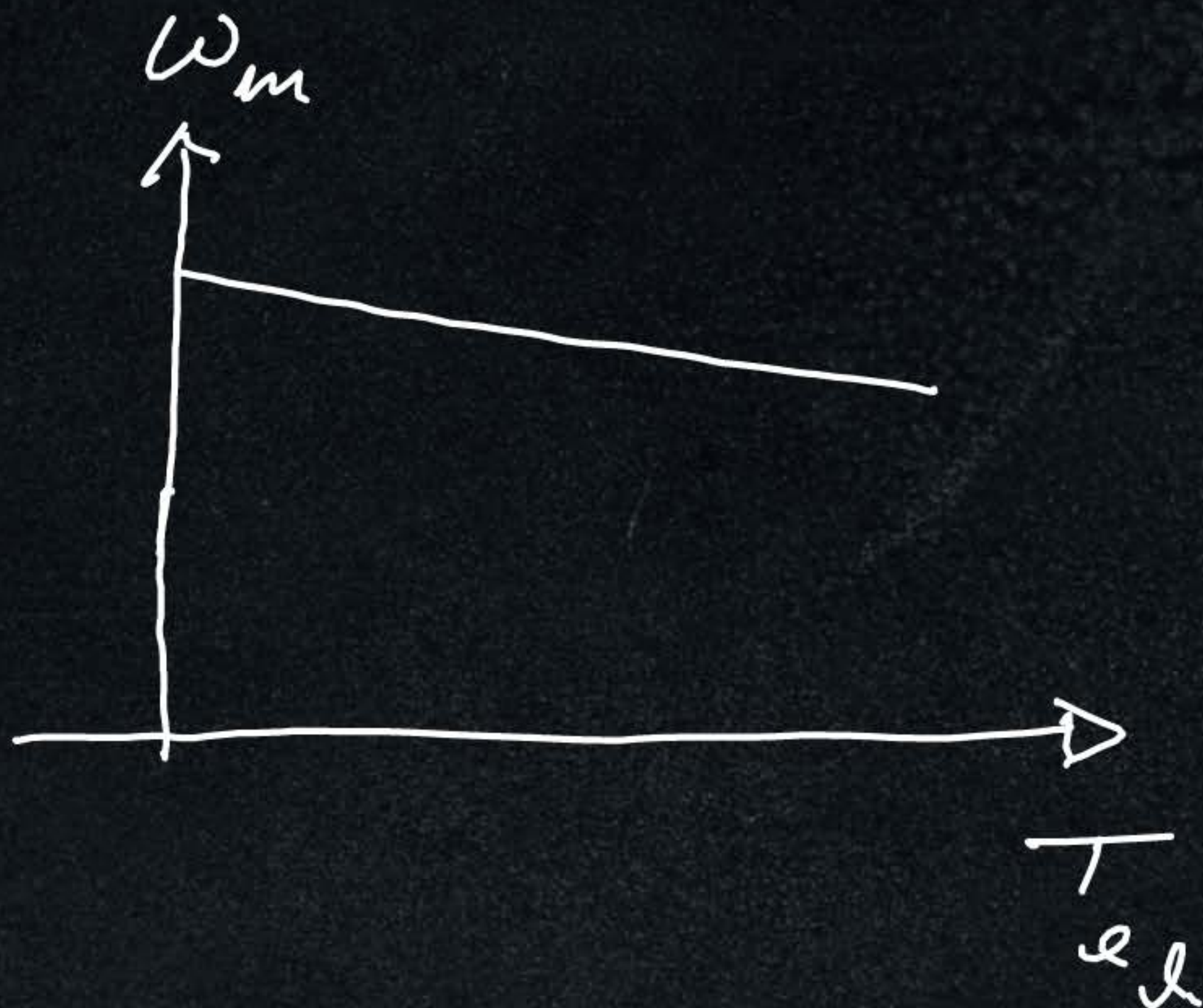(2)  $\rightarrow$  (1)


$$V_a = \frac{R_a}{k\phi_f} T_{el} + k\phi_f \omega_m$$

$$\omega_m = \frac{V_a}{k\phi_f} - \frac{R_a}{(k\phi_f)^2} T_{el}$$




# Methods of speed control

1)  $V_a$  control

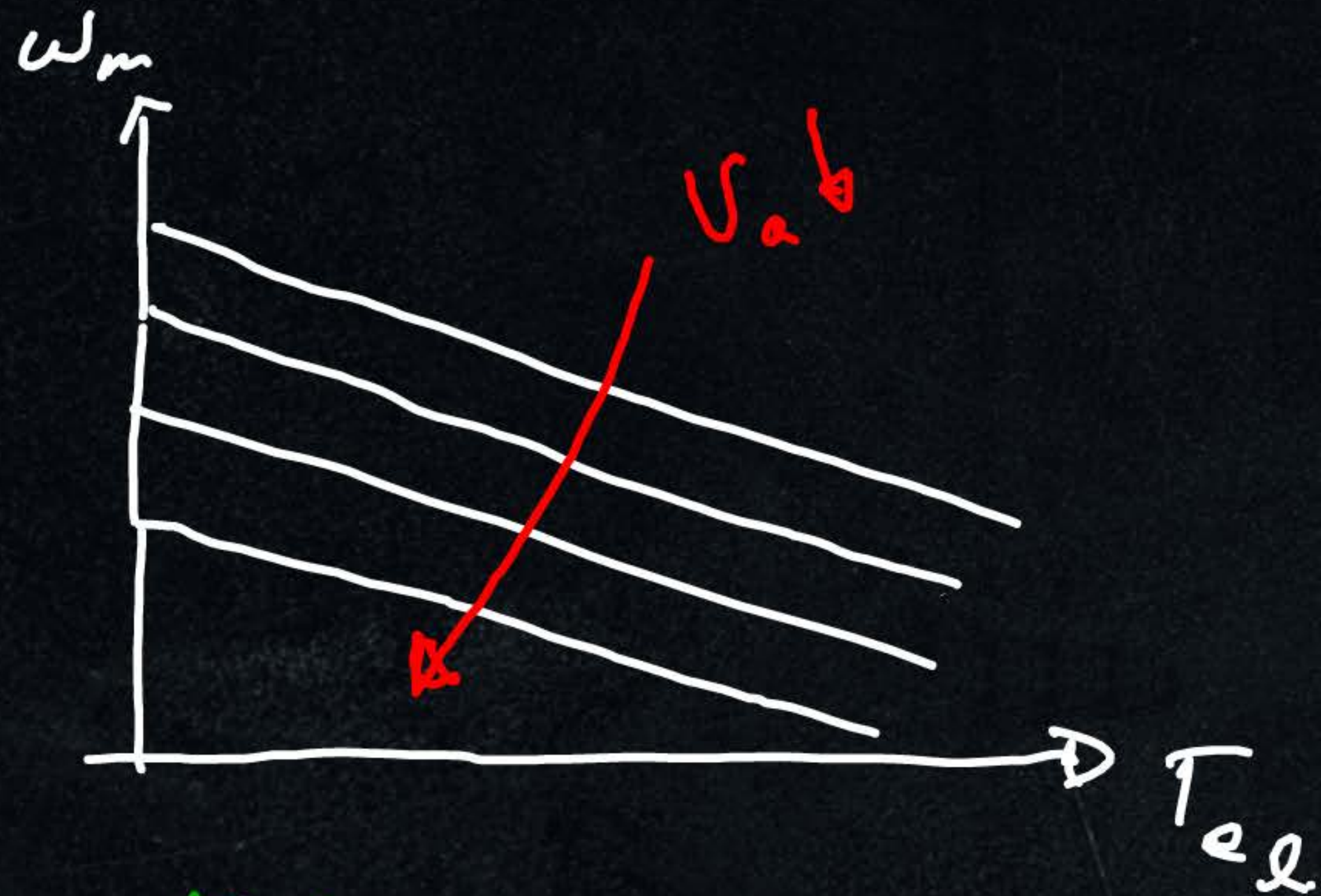


$V_a \downarrow \Rightarrow \omega_m \downarrow$

2)  $R_a$  control

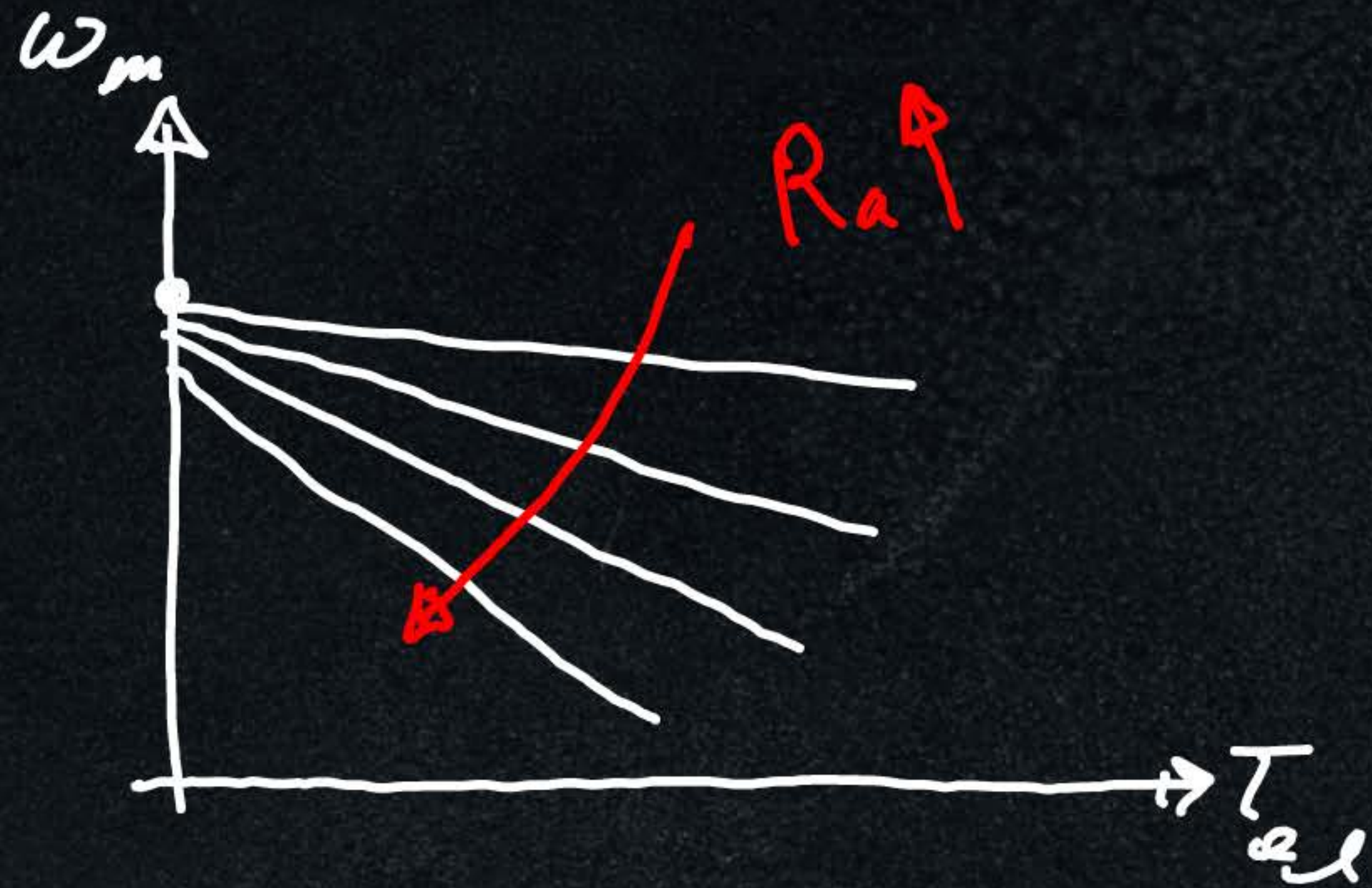

$R_a \uparrow \Rightarrow \omega_m \downarrow$

## ② Series

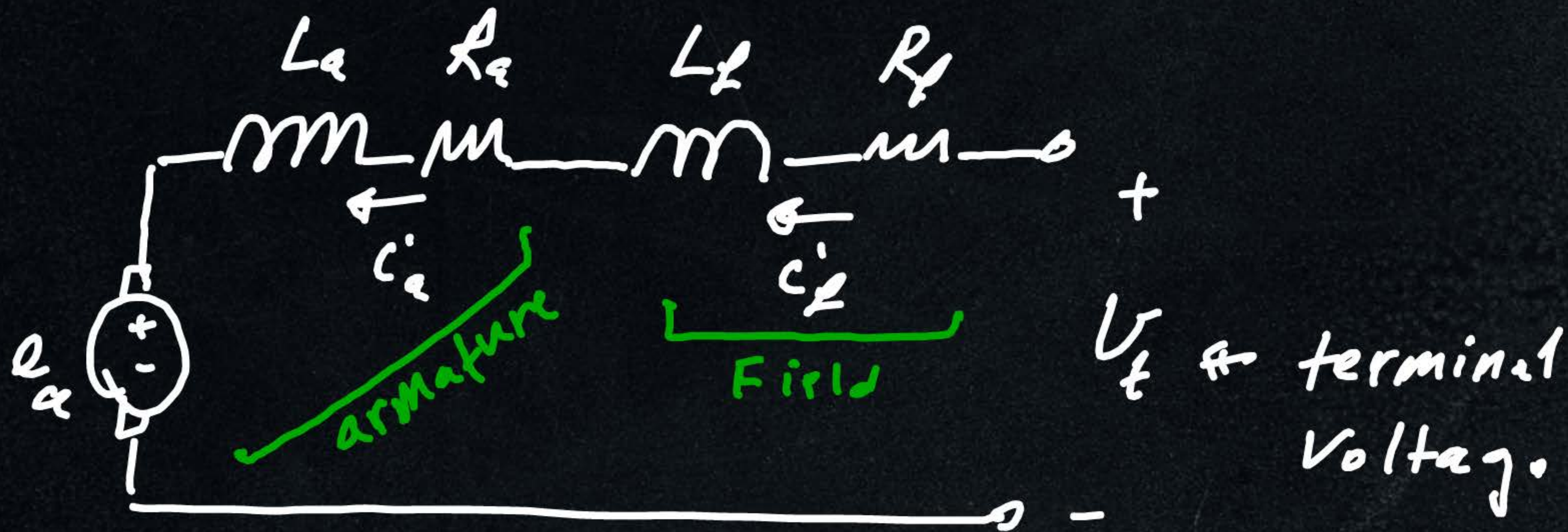

$$i_a = i_f$$

$$V_t = R i_a + k \phi_f \omega_m$$

where  $R = R_f + R_a$ ,  $\phi_f = C L_f$


$$V_t = R i_a + k C L_a \omega_m \quad \text{--- (1)}$$

$$T_{el} = k \phi_f i_a = k C L_a i_a^2$$

$$\Rightarrow i_a = \sqrt{T_{el}} / \sqrt{k C} \quad \text{--- (2)}$$


$$\text{(2)} \rightarrow \text{(1)} \quad V_t = \frac{R}{\sqrt{k C}} \sqrt{T_{el}} + \sqrt{k C} \sqrt{T_{el}} \omega_m$$
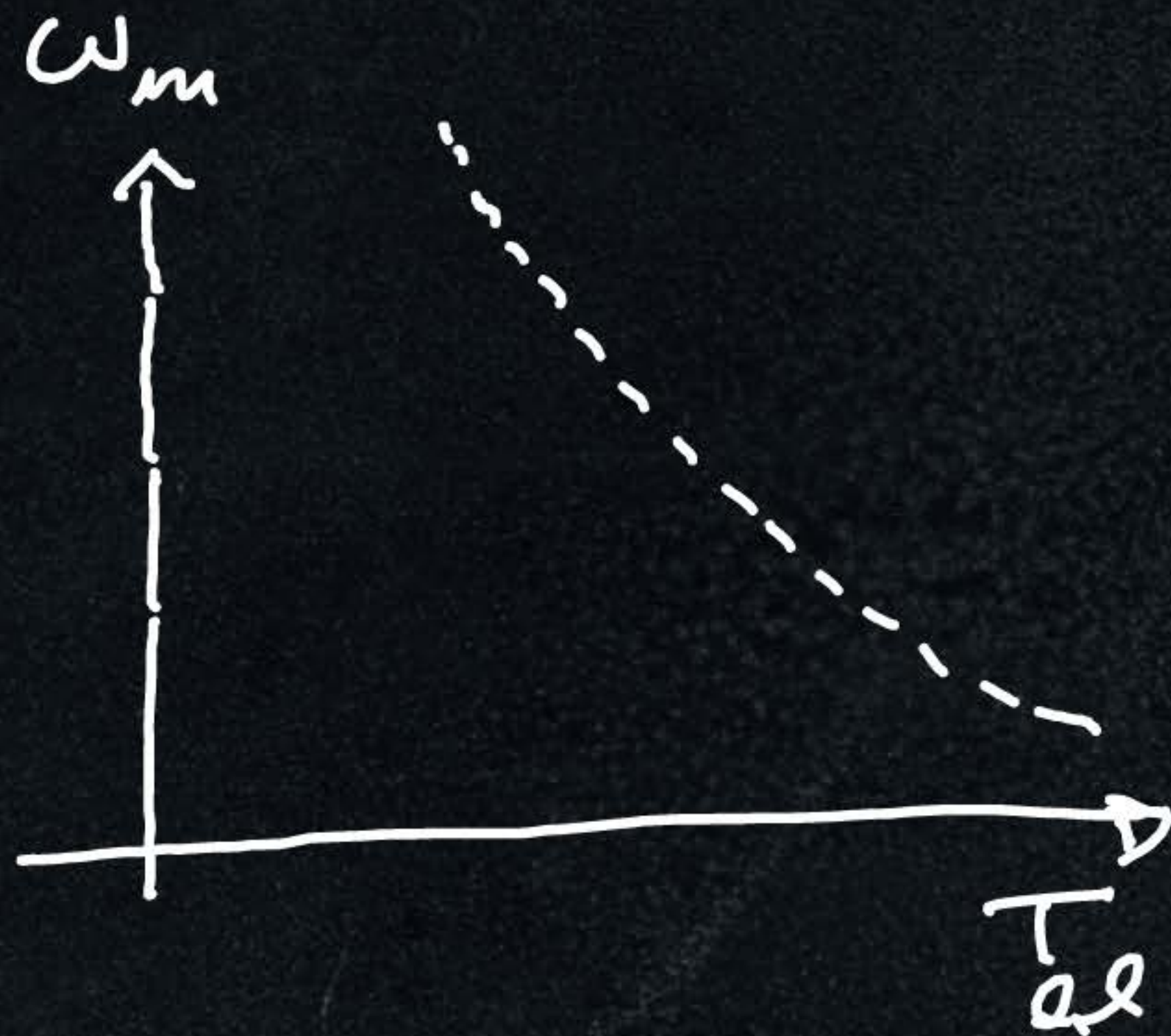
$$\Rightarrow \omega_m = \frac{V_t}{\sqrt{k C}} \cdot \frac{1}{\sqrt{T_{el}}} - \frac{R}{k C}$$




# Methods of speed control

1)  $V_t$  control

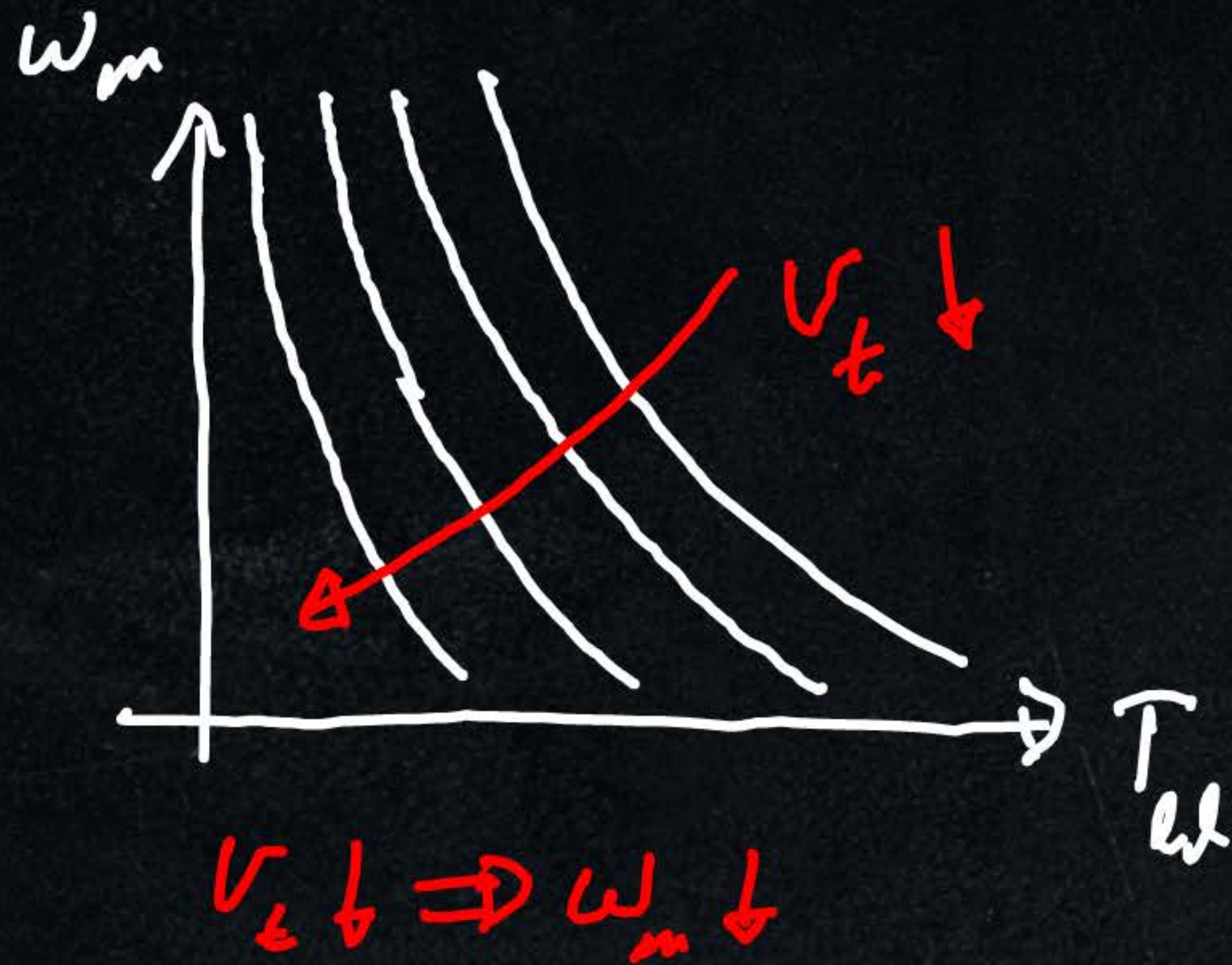

2) R control

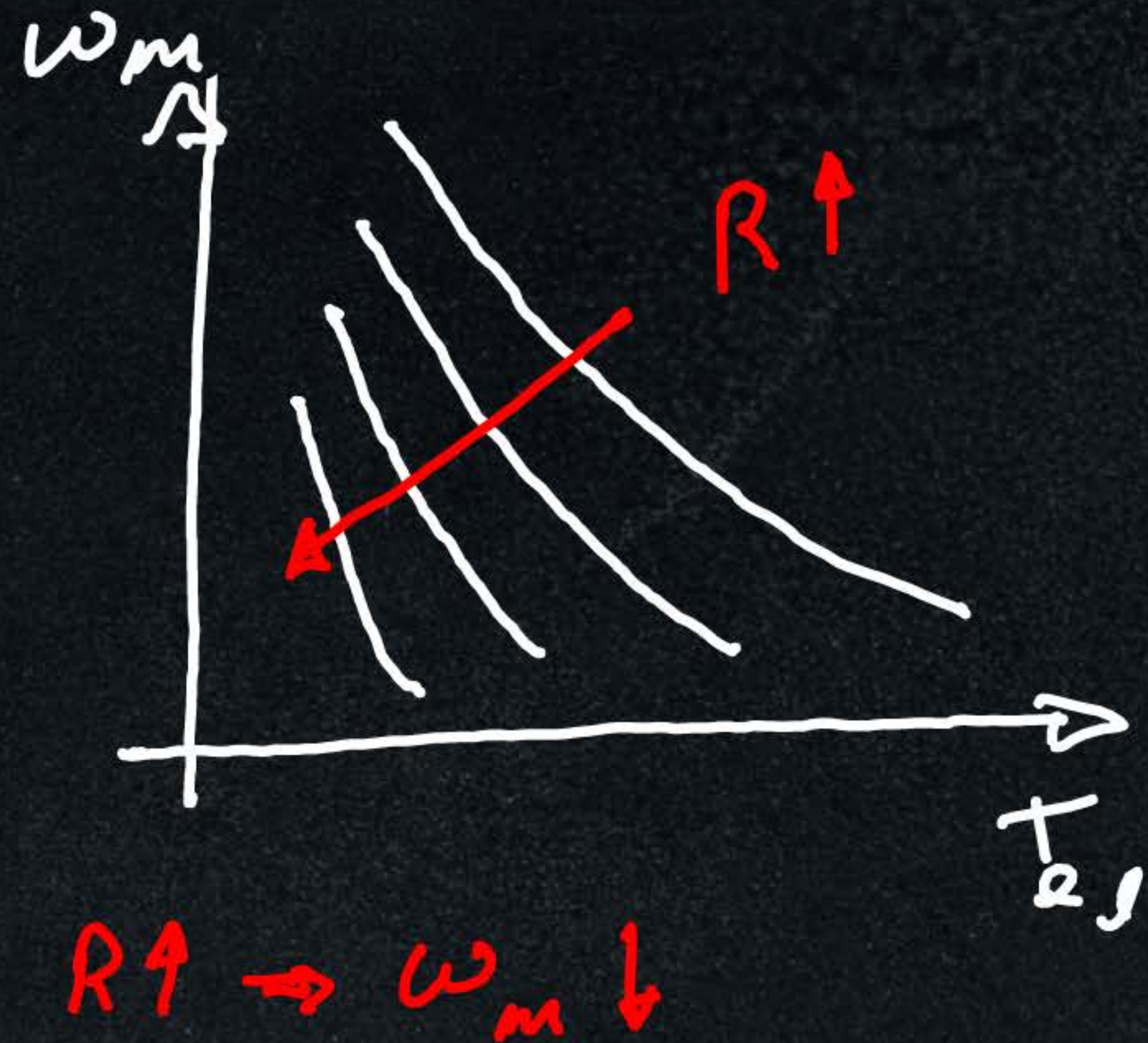


# Principle of DC Machine Drive

$$V_a = R_a I_a + k\phi_f \omega_m \Rightarrow \omega_m = \frac{V_a - R_a I_a}{k\phi_f} \approx \frac{V_a}{k\phi_f}$$

Armature control

↳ Ideal for speeds lower than  $\omega_{m,r}$ .
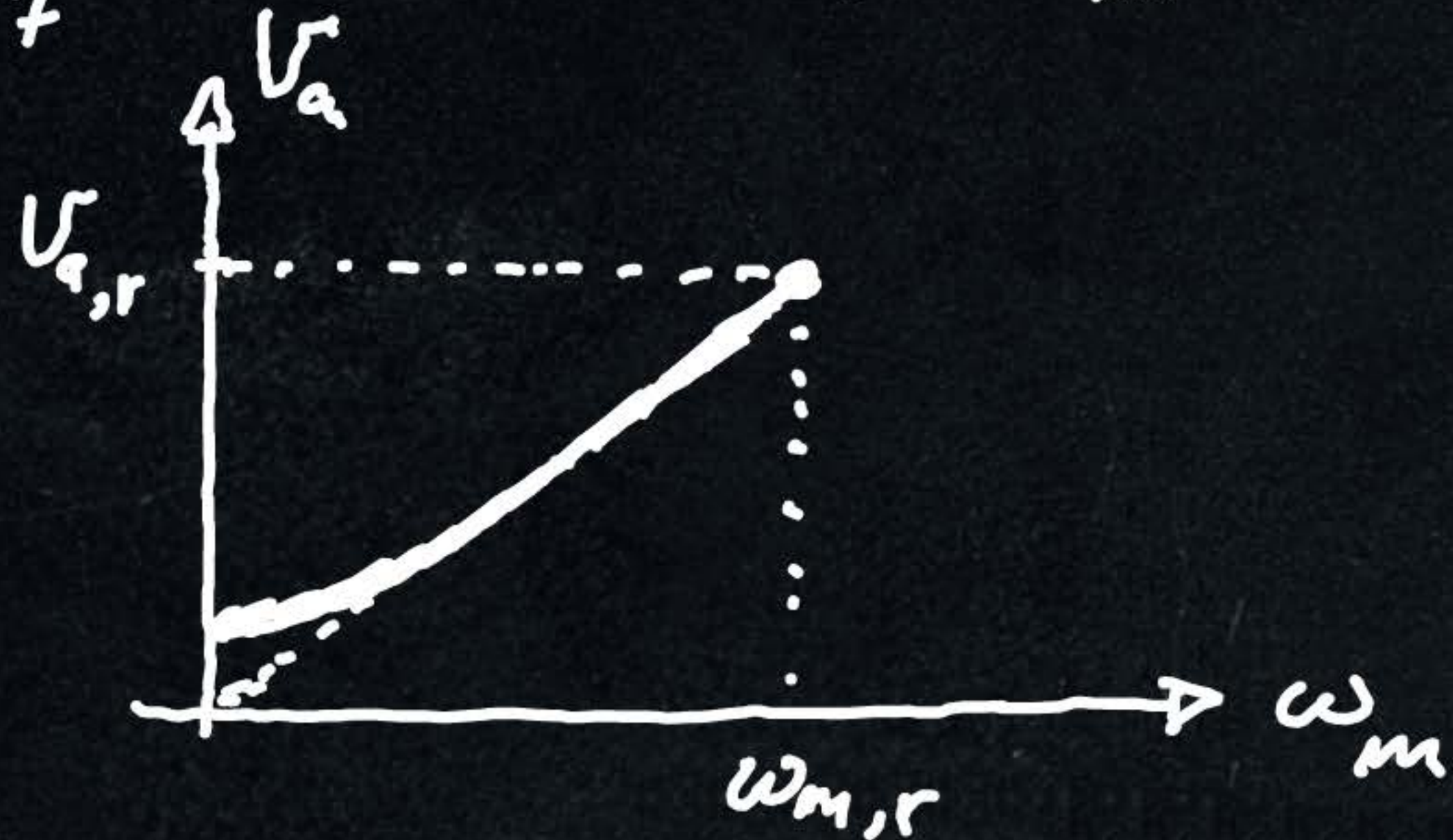
$$\phi_f = \text{constant} \Rightarrow \omega_m \propto V_a$$



$\omega_{m,r}$ : Rated speed


$V_{a,r}$ : Rated voltage

# Field control

↳ Ideal for speeds above  $\omega_{m,r}$

$$V_e = V_{a,r} \Rightarrow \omega_m = \frac{V_{a,r}}{k\phi_f} \Rightarrow \phi_f \propto \frac{1}{\omega_m}$$
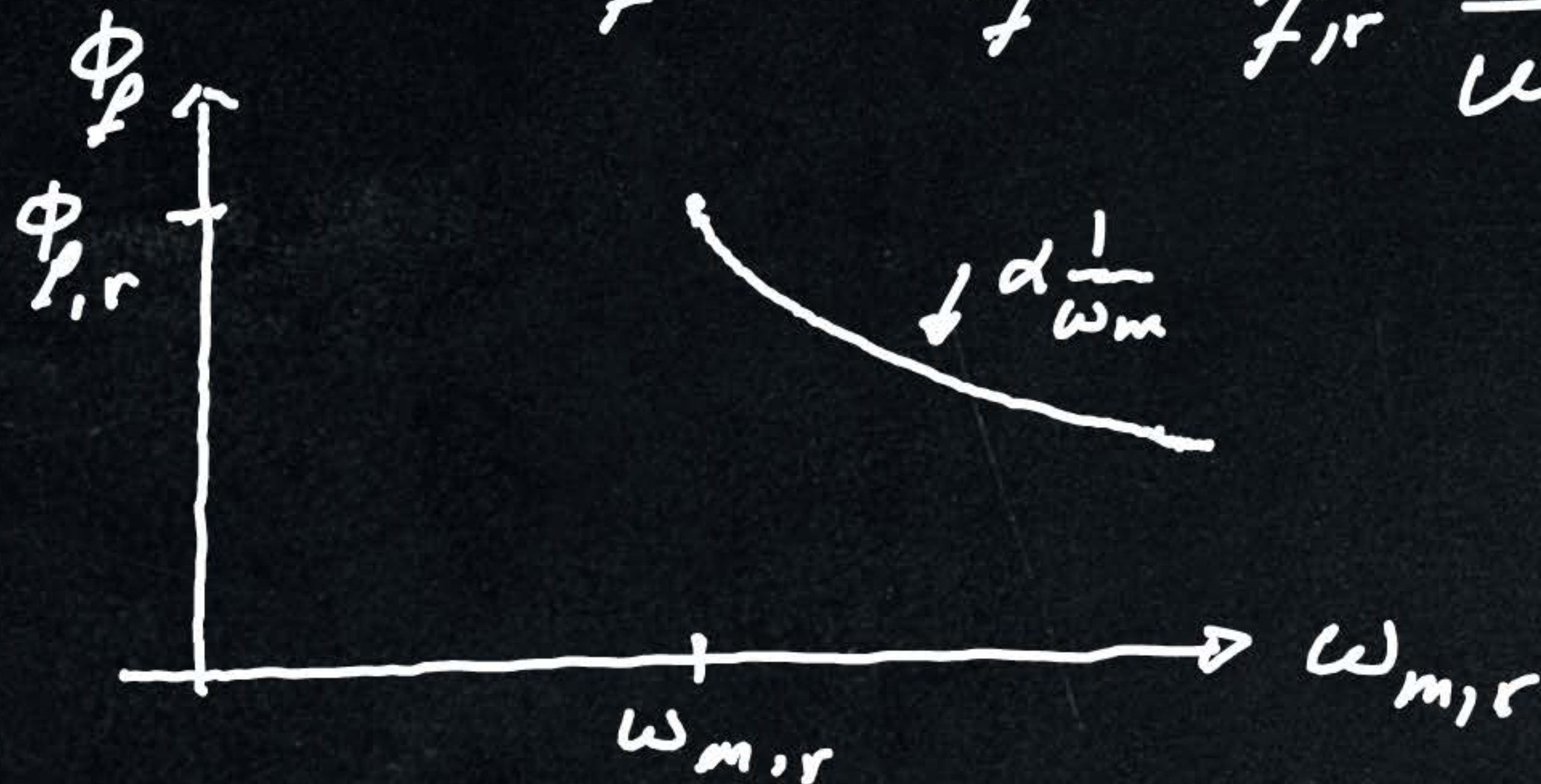
$$\omega_m \uparrow \Rightarrow \phi_f \downarrow \quad \phi_f = \phi_{f,r} \frac{\omega_{m,r}}{\omega_m}$$



$\phi_{f,r}$  : Rated flux  
 $\omega_{m,r}$  : Rated speed

# Armature and field control

$$\omega_m \leq \omega_{m,r} \Rightarrow \Phi_f = \Phi_{f,r} \quad \& \quad U_a = R_a I_a' + k \Phi_f \omega_m$$

Assume  $I_a' = I_{a,r}$  where  $I_{a,r}$  is the rated current

$$T_{el} = k \Phi_{f,r} I_{a,r} = \text{constant}$$

$$P_a = T_{el} \omega_m \propto \omega_m$$

constant torque region







$$\omega_m \geq \omega_{m,r} \Rightarrow \phi_f = \phi_{f,r} \frac{\omega_{m,r}}{\omega_m} + U_a = U_{a,r}$$

Assume  $L'_a = L'_{a,r}$

$$T_{el} = k \phi_f L'_a = k \phi_{f,r} L'_{a,r} \frac{\omega_{m,r}}{\omega_m} \propto \frac{1}{\omega_m}$$

$$P_a = T_{el} \omega_m = k \phi_{f,r} L'_{a,r} \omega_{m,r} = \text{constant}$$

constant power region

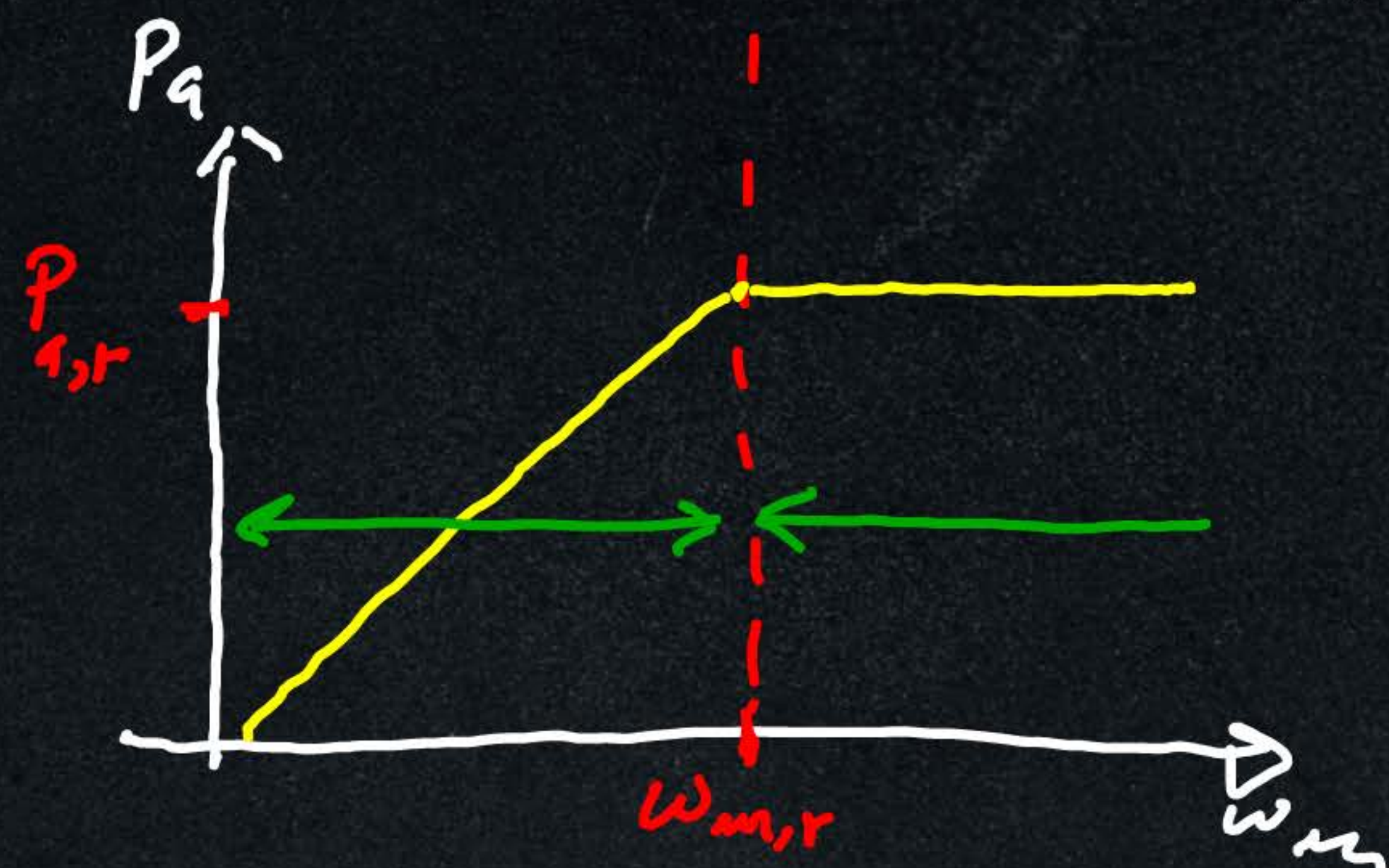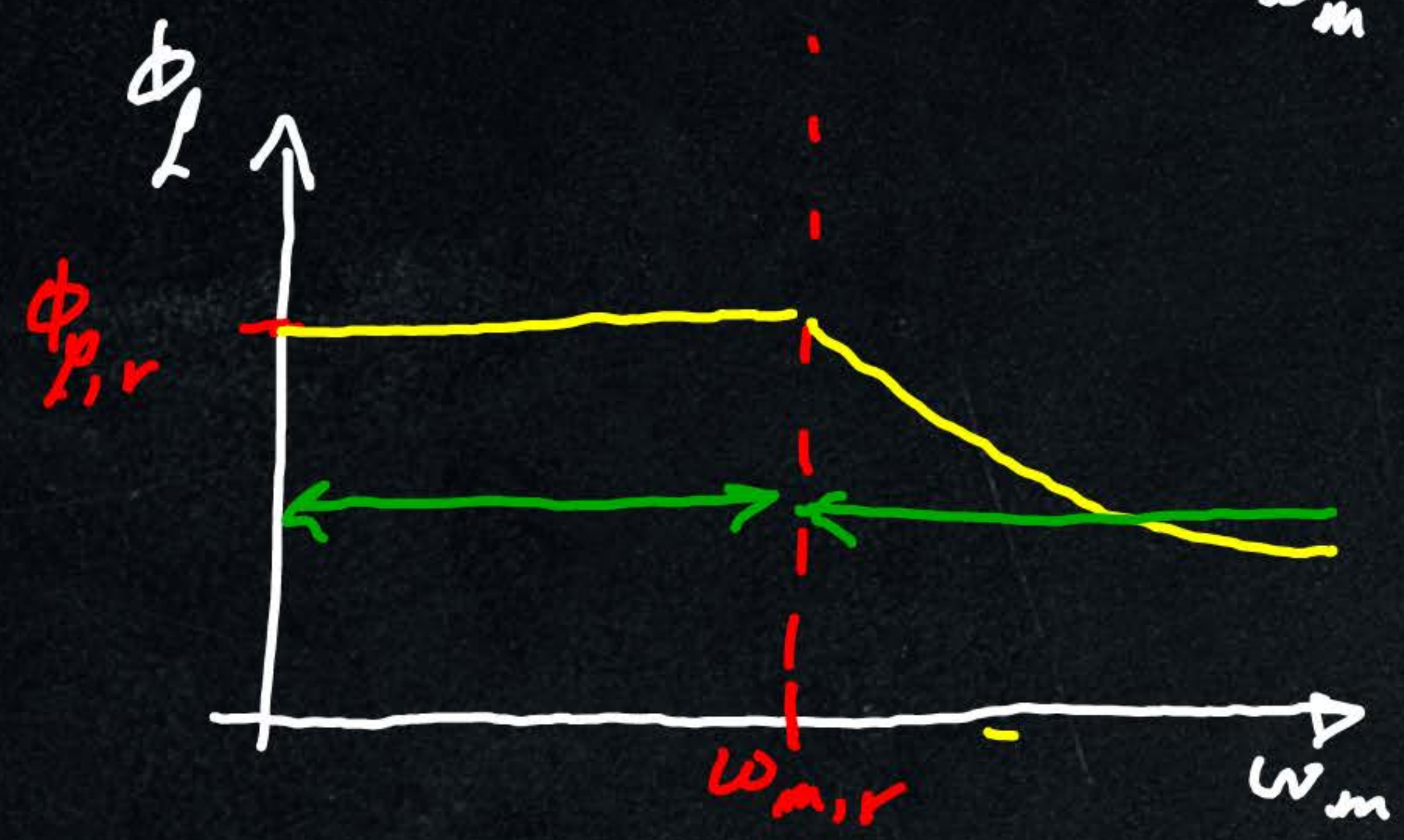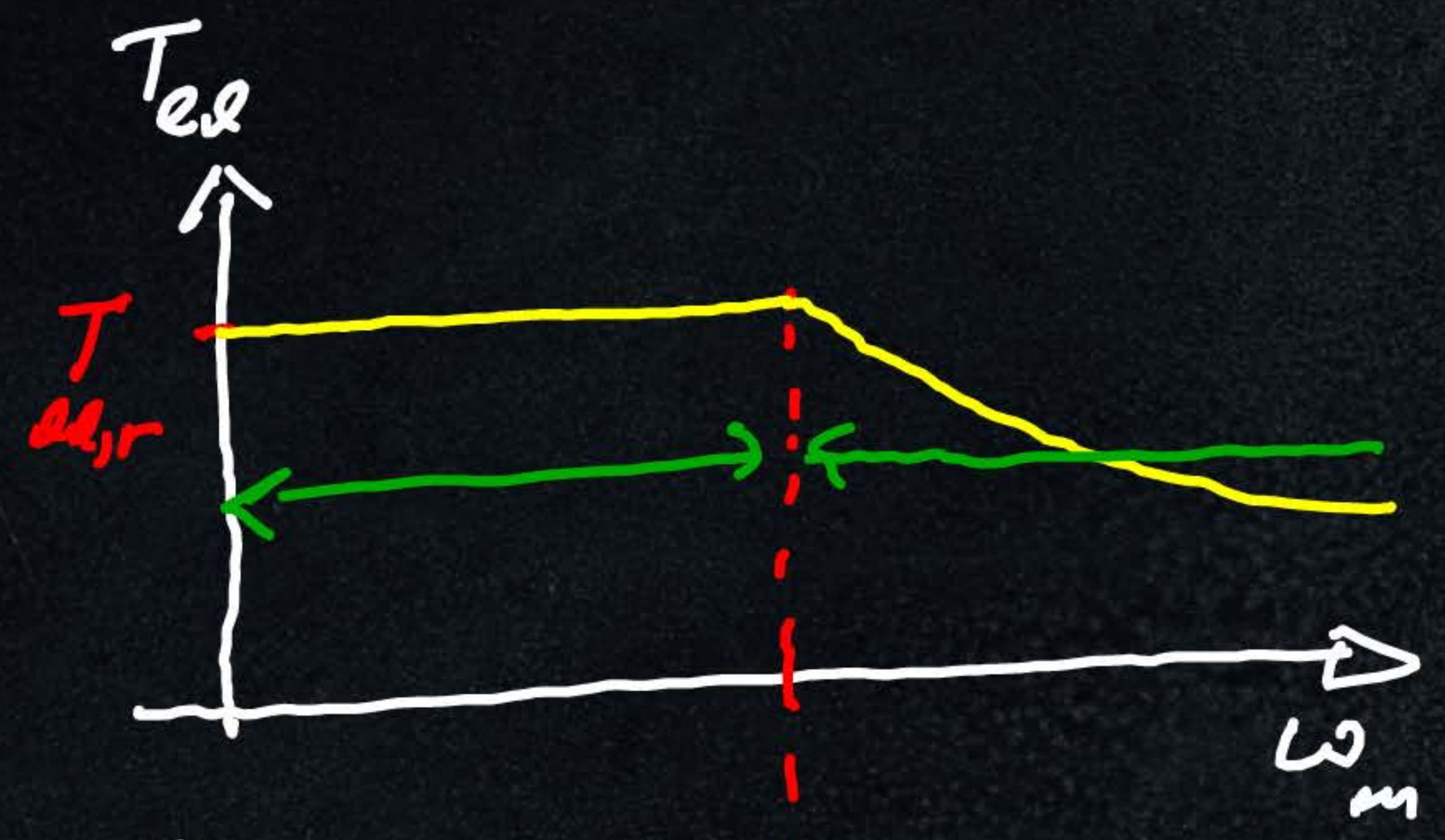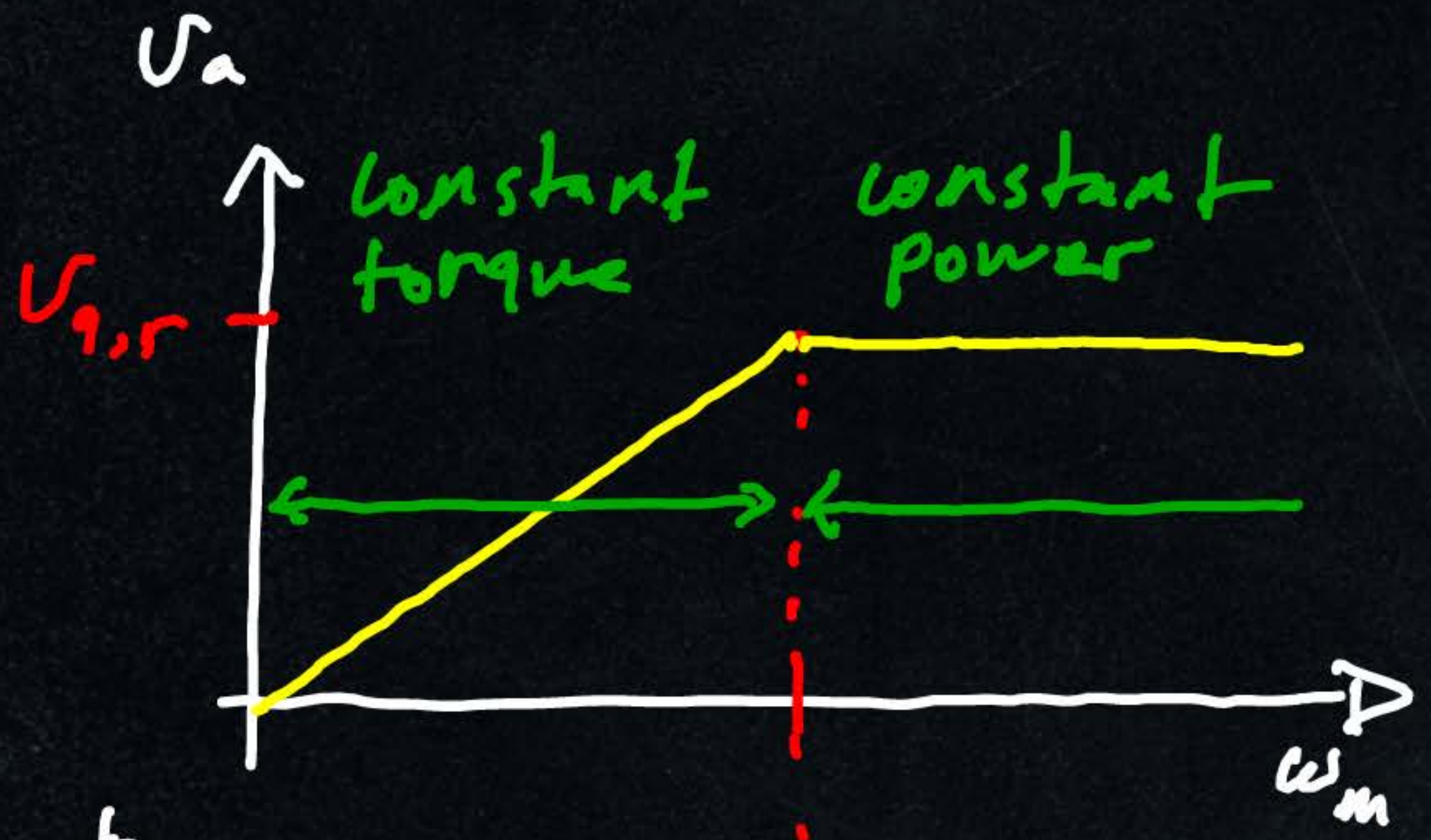

# Braking and Four-Quadrant operation

## Braking

The machine is made to work as a generator producing a negative torque

$$T_{e1} - T_L = J \frac{d\omega_m}{dt}$$

$\omega_m > 0$  +  $(T_{e1} - T_L) < 0 \Rightarrow$  machine acts as a generator

$$T_{el} - T_L = J_{tot} \frac{d\omega_m}{dt} \Rightarrow \Delta t = \frac{J_{tot}}{T_{el} - T_L} \Delta \omega_m$$

$\Delta t$  : Stopping time



why do we need braking?

- 1) Reducing  $\Delta t$
- 2) Achieving quick and smooth stops
- 3) Achieving accurate stops
- 4) Holding the speed within safe limit

# Braking methods
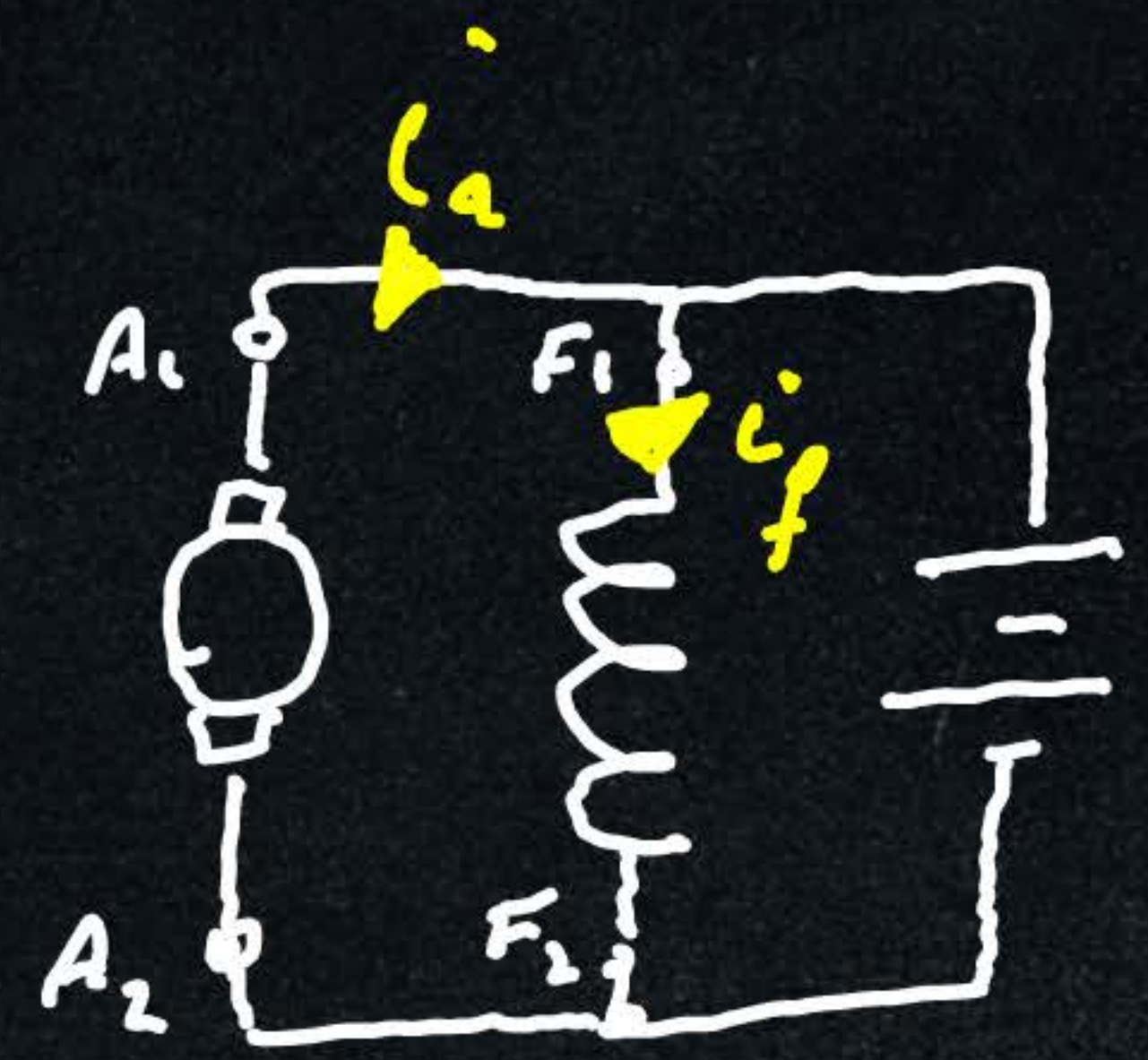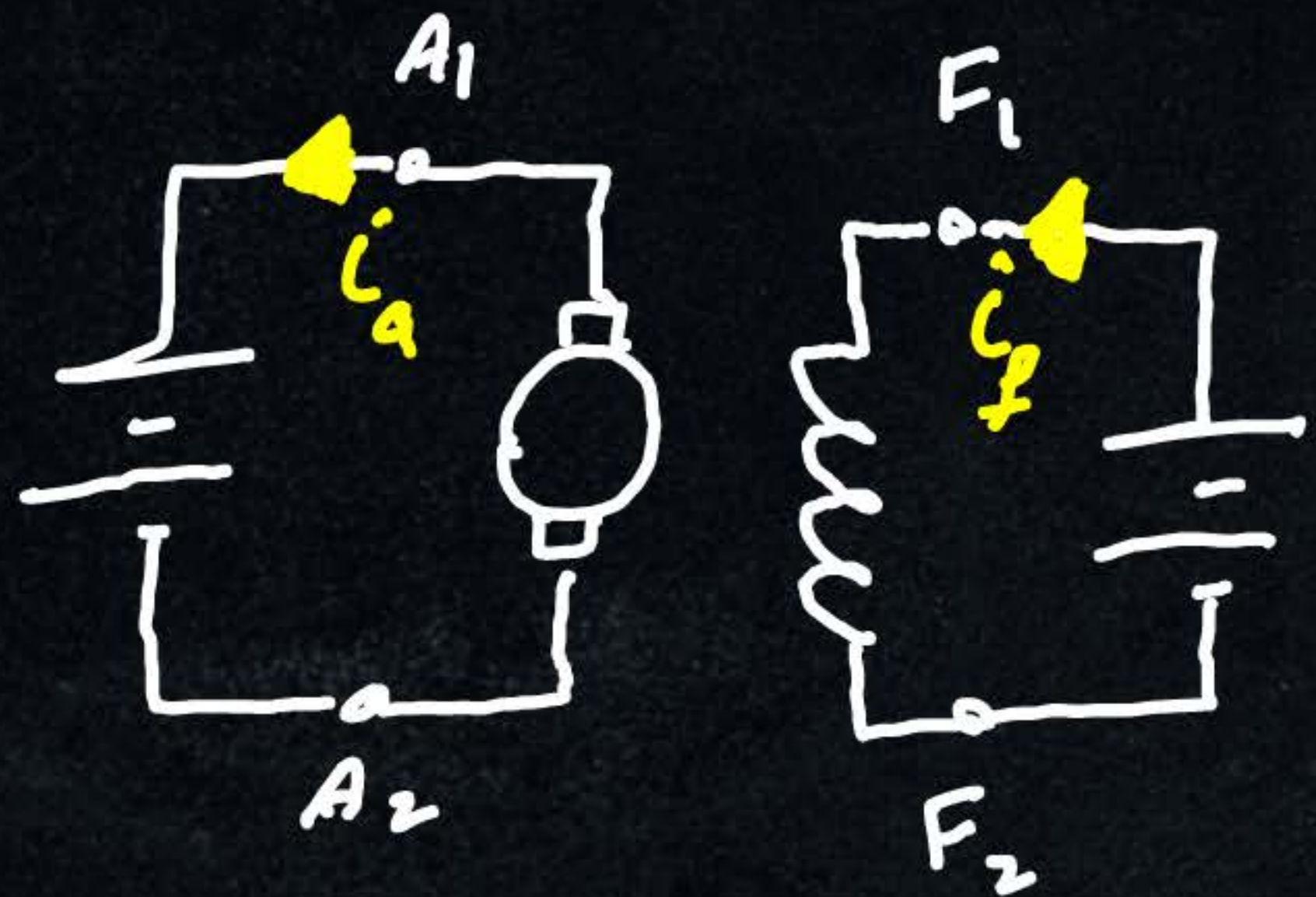
## ① Regenerative braking


Generated electrical power is usefully employed.




separately

shunt.

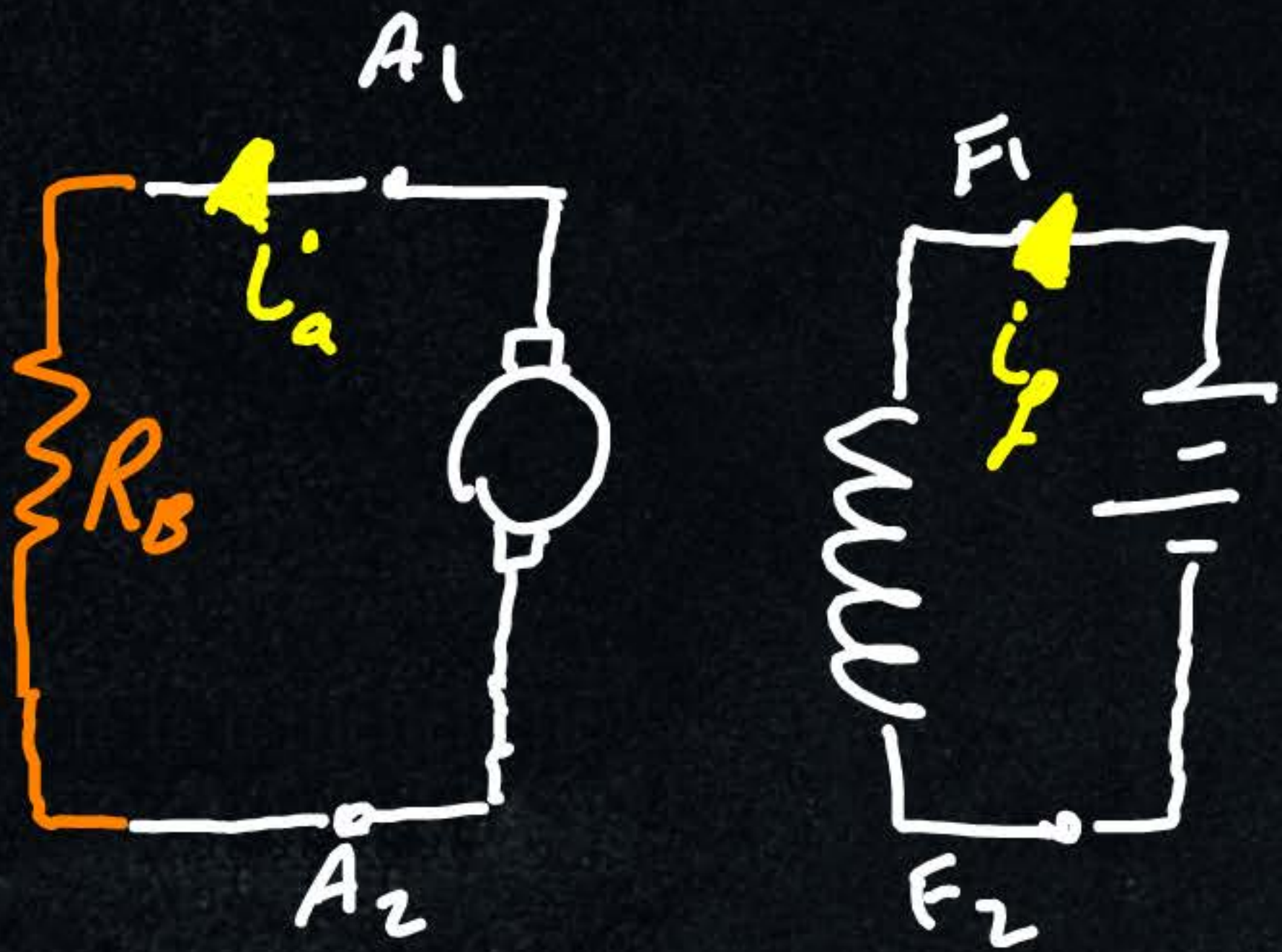② Dynamic braking  $\rightarrow$  It is an inefficient method of braking.




separately

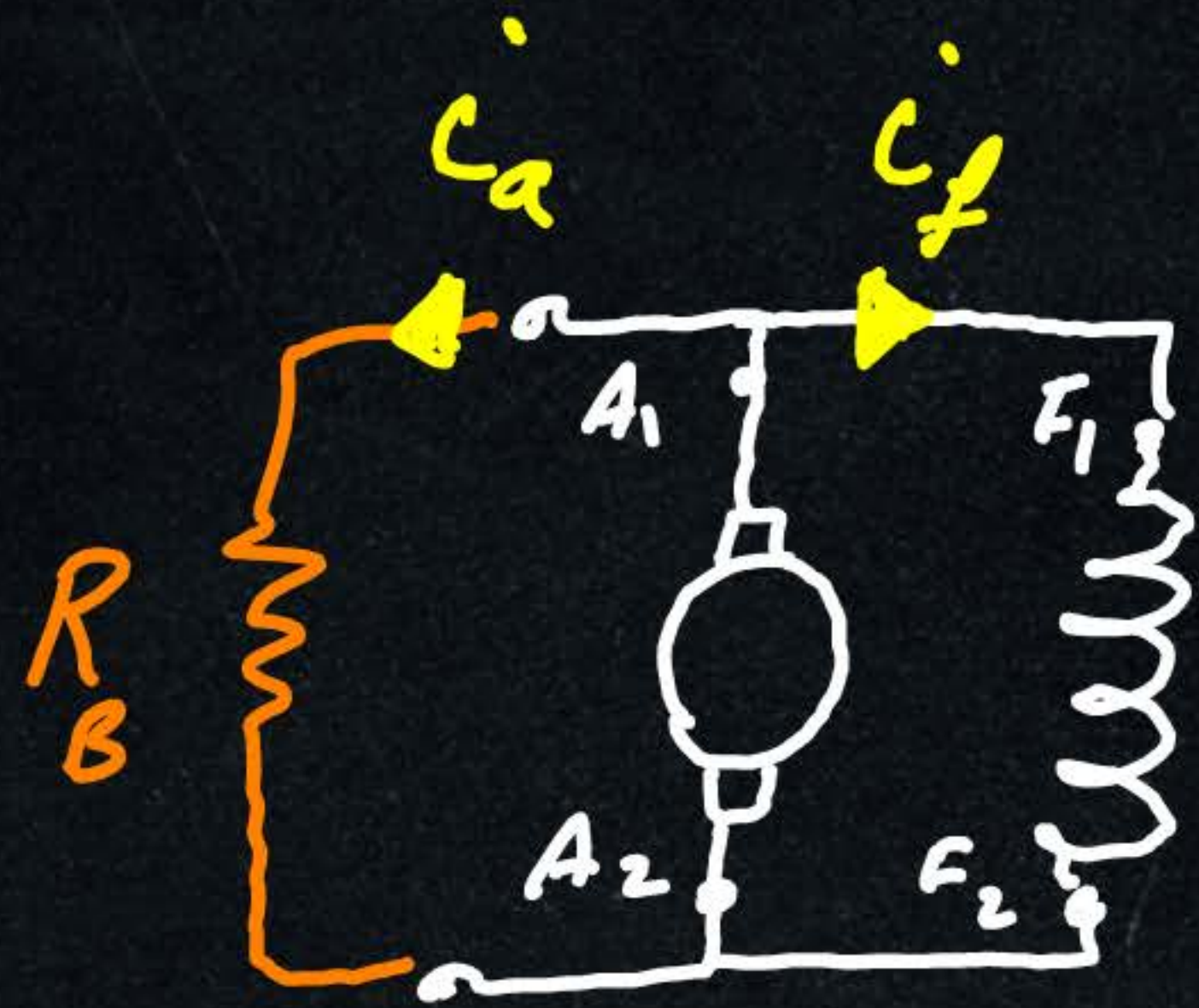

shunt

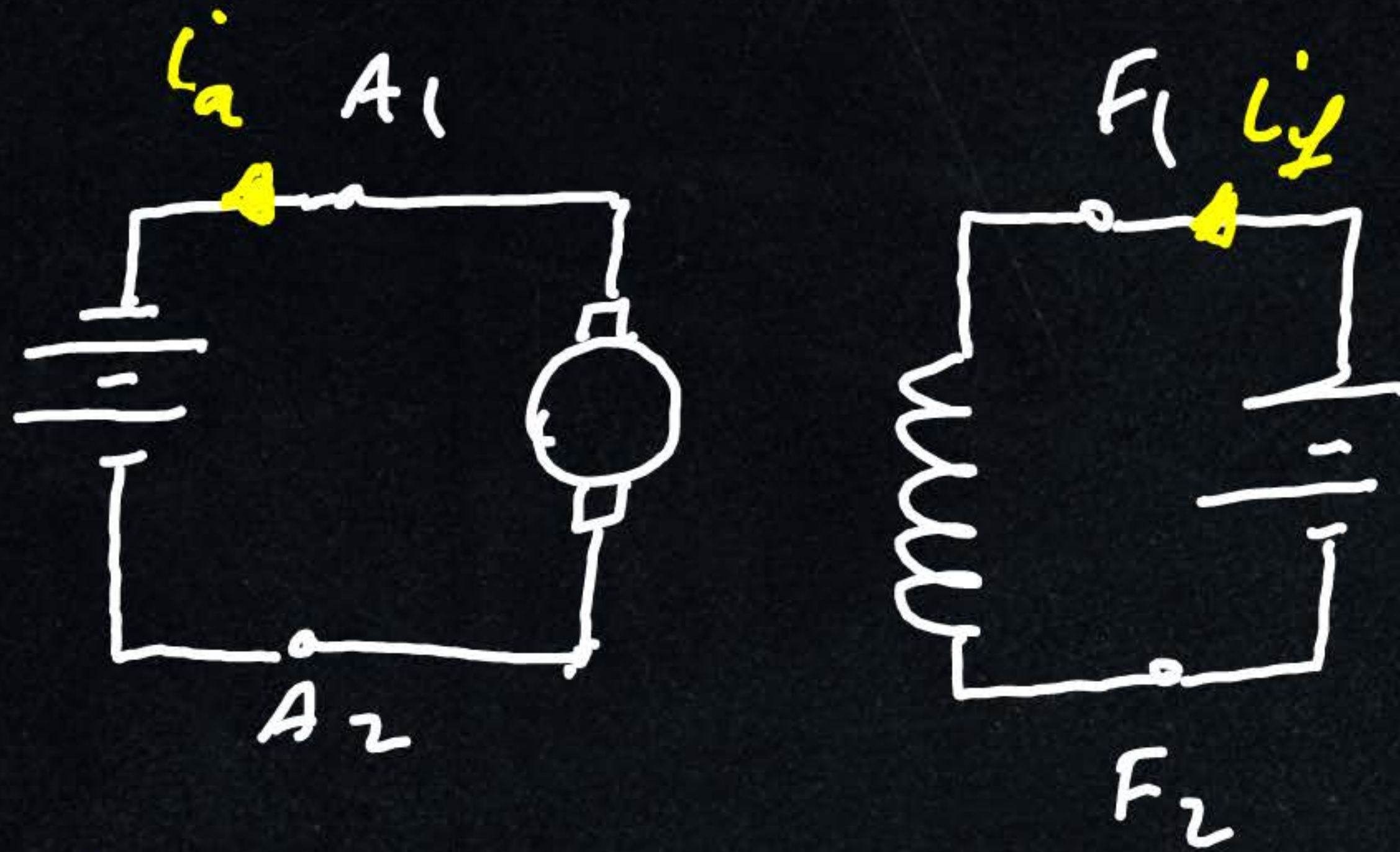
③ plugging braking  $\rightarrow$  It is a highly inefficient method.



separately
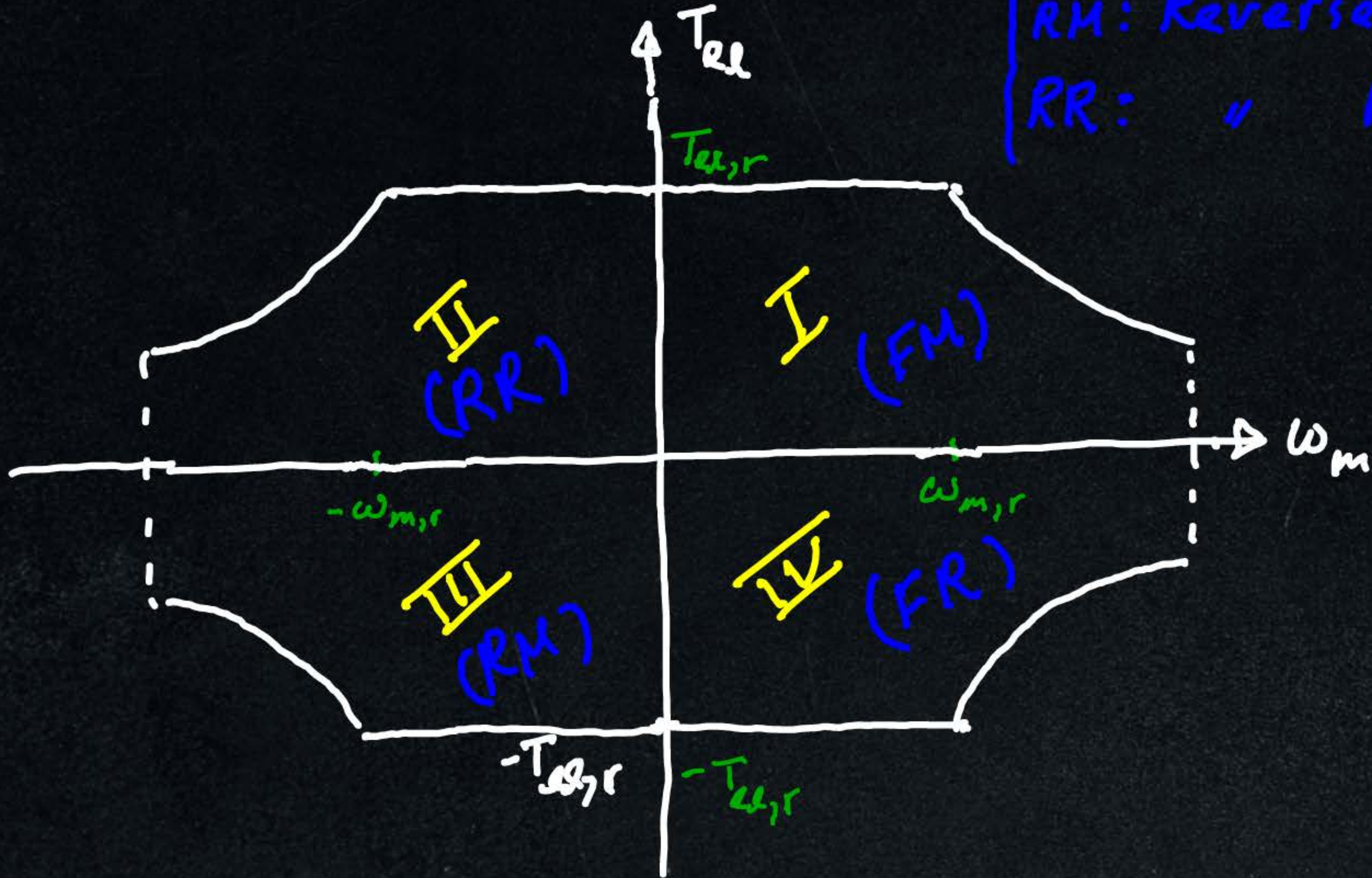
# Four-Quadrant Operation






EM: Forward Motoring  
FR: " Regeneration  
RM: Reverse Motoring  
RR: " Regeneration





Function	Quadrant	$\omega_m$	$T_{el}$	$V_a$	$C_a$	$P_a$
FM	I	+	+	+	+	+
FR	IV	+	-	+	-	-
RM	III	-	-	-	-	+
RR	II	-	+	-	+	-



# Chopper Controlled DC Motor Drive

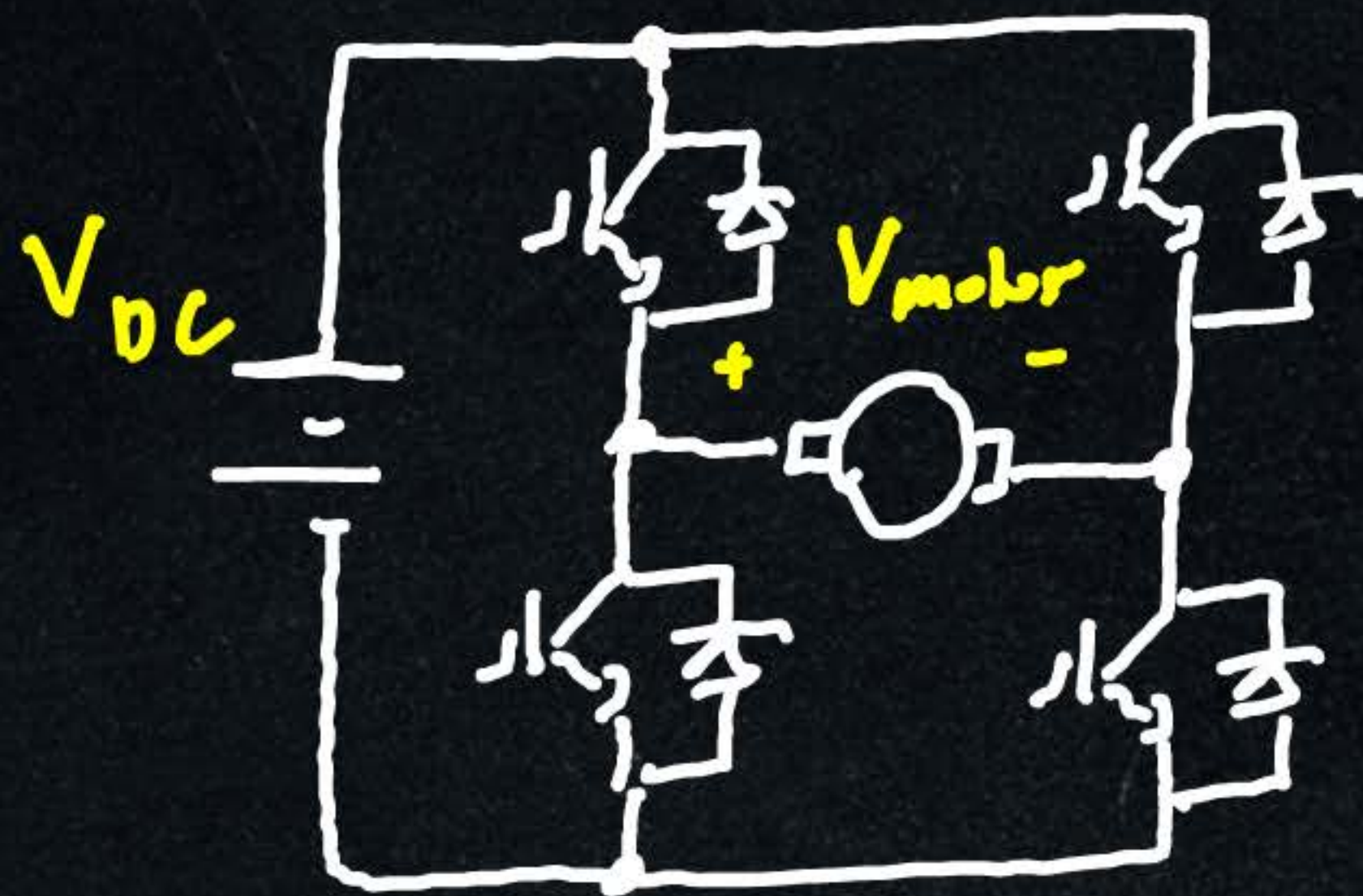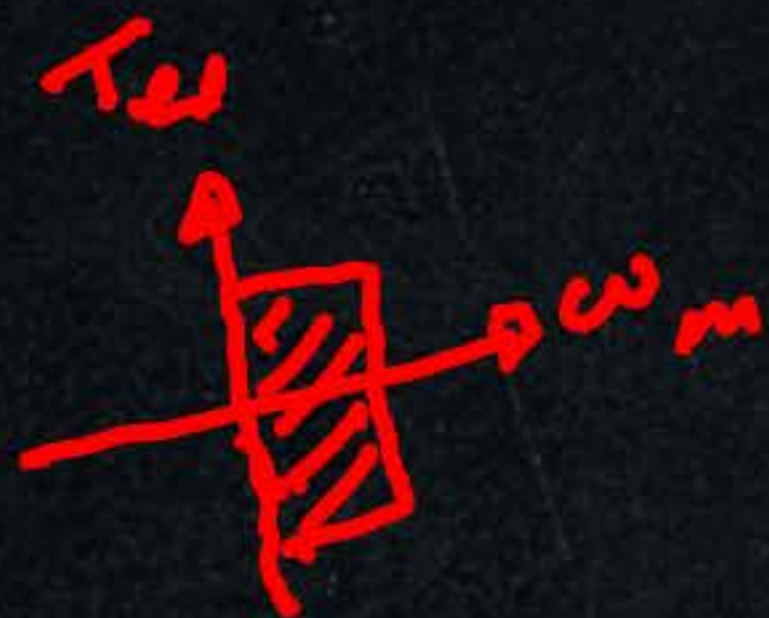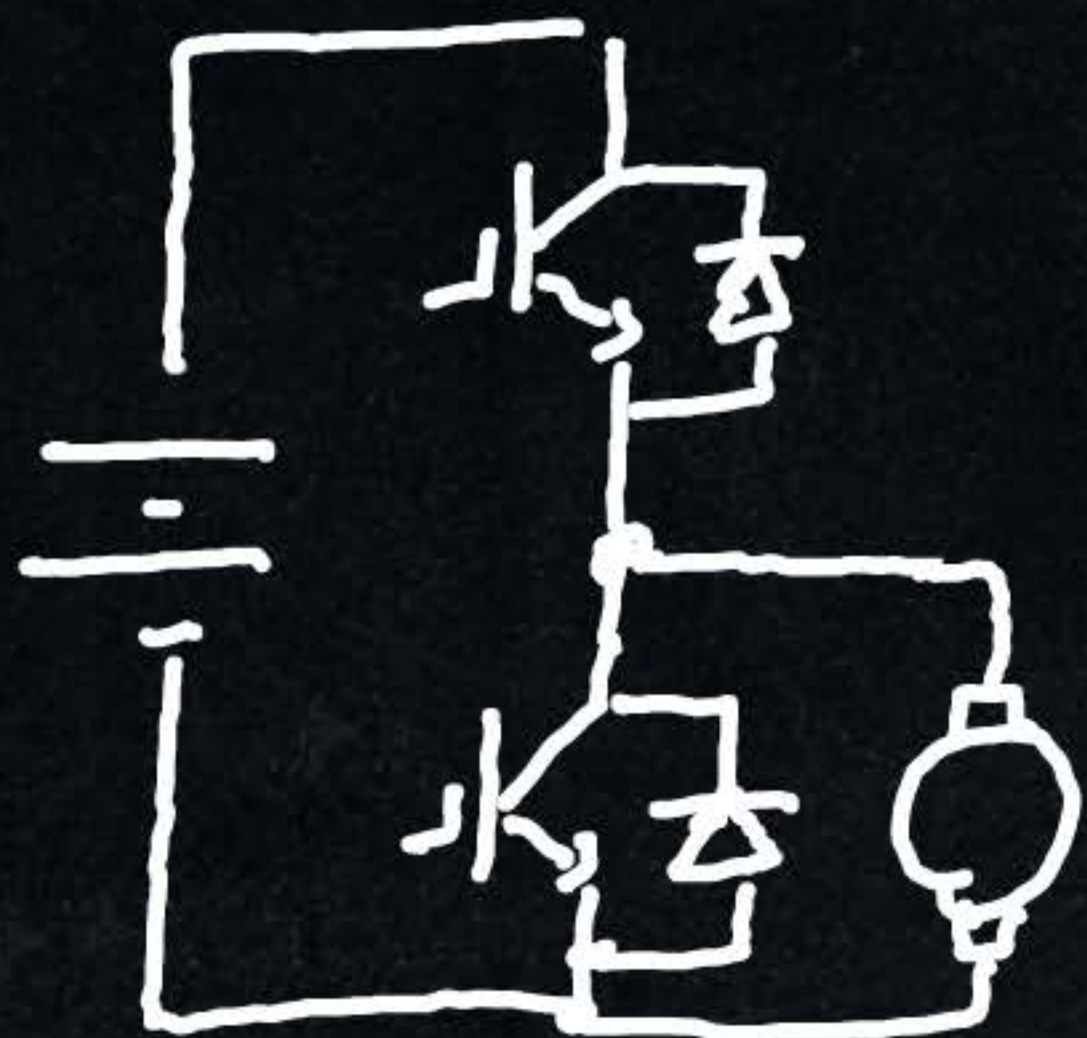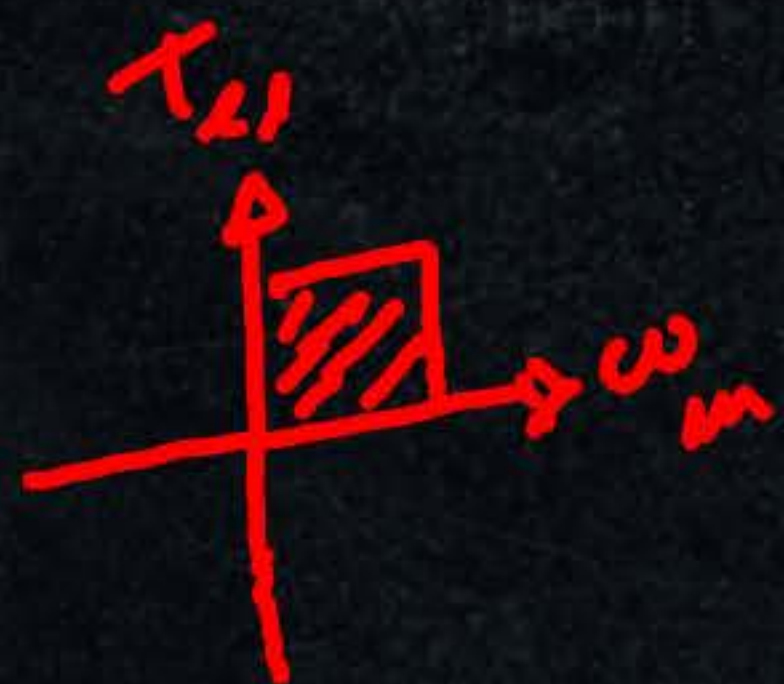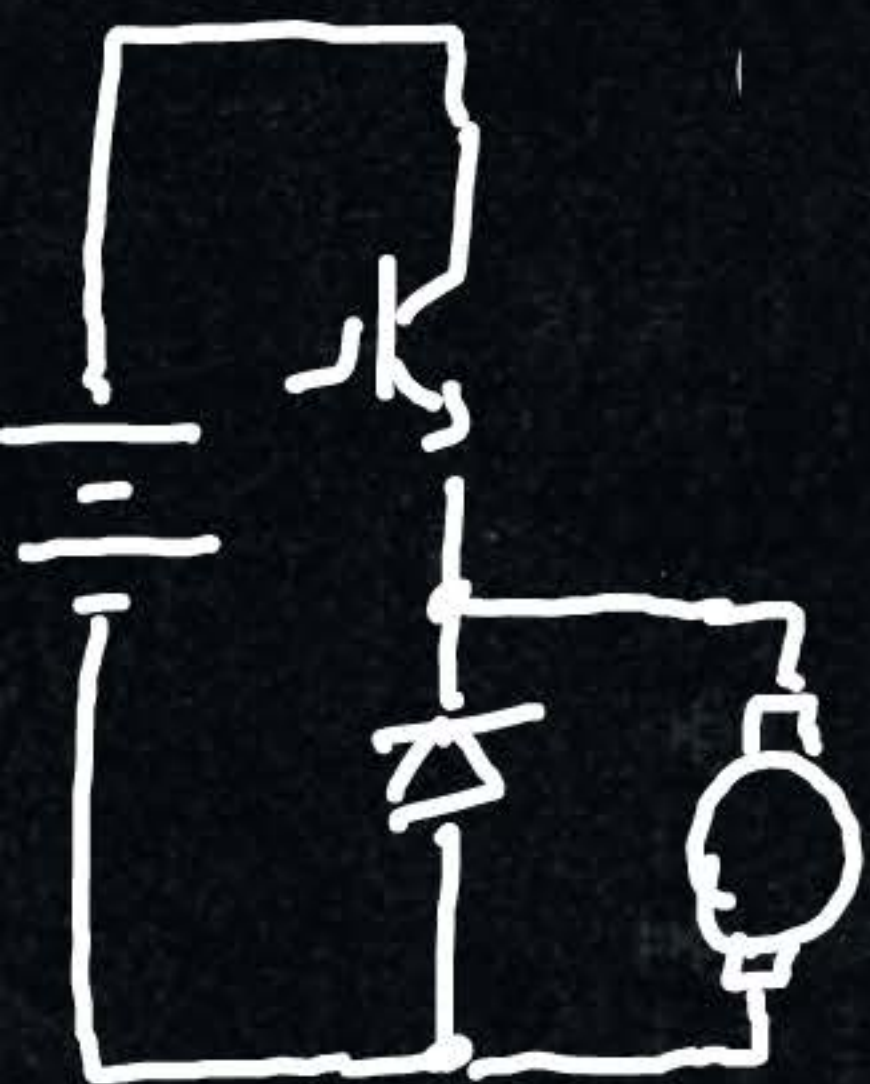

$$0 \leq \delta \leq 1$$


$$V_{motor} = \delta V_{DC}; \delta: \text{Duty cycle}$$

# 4 quadrant chopper

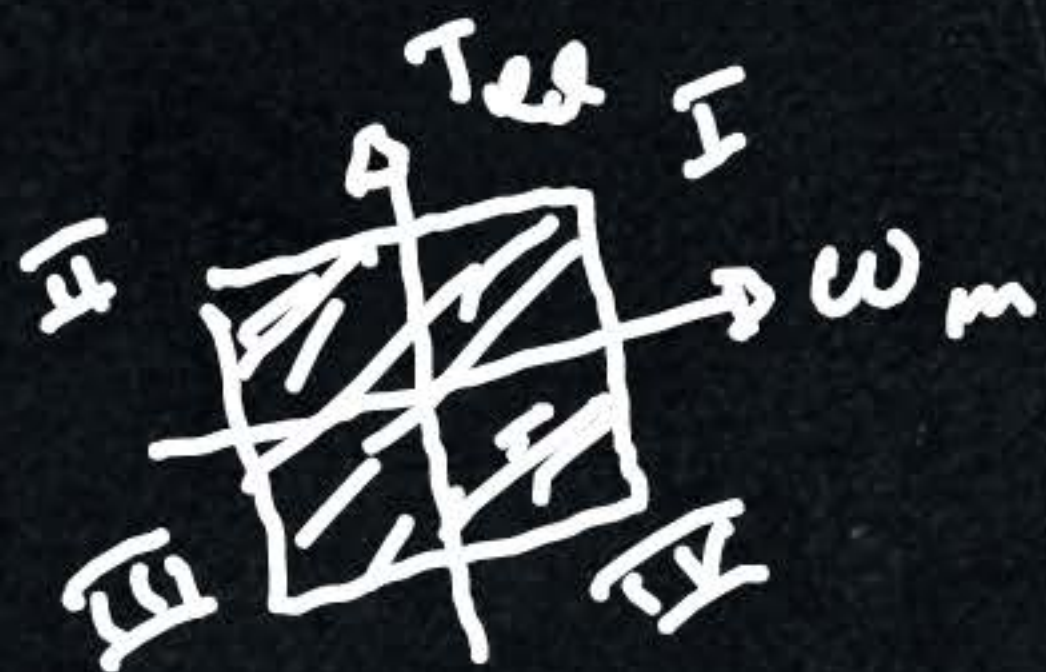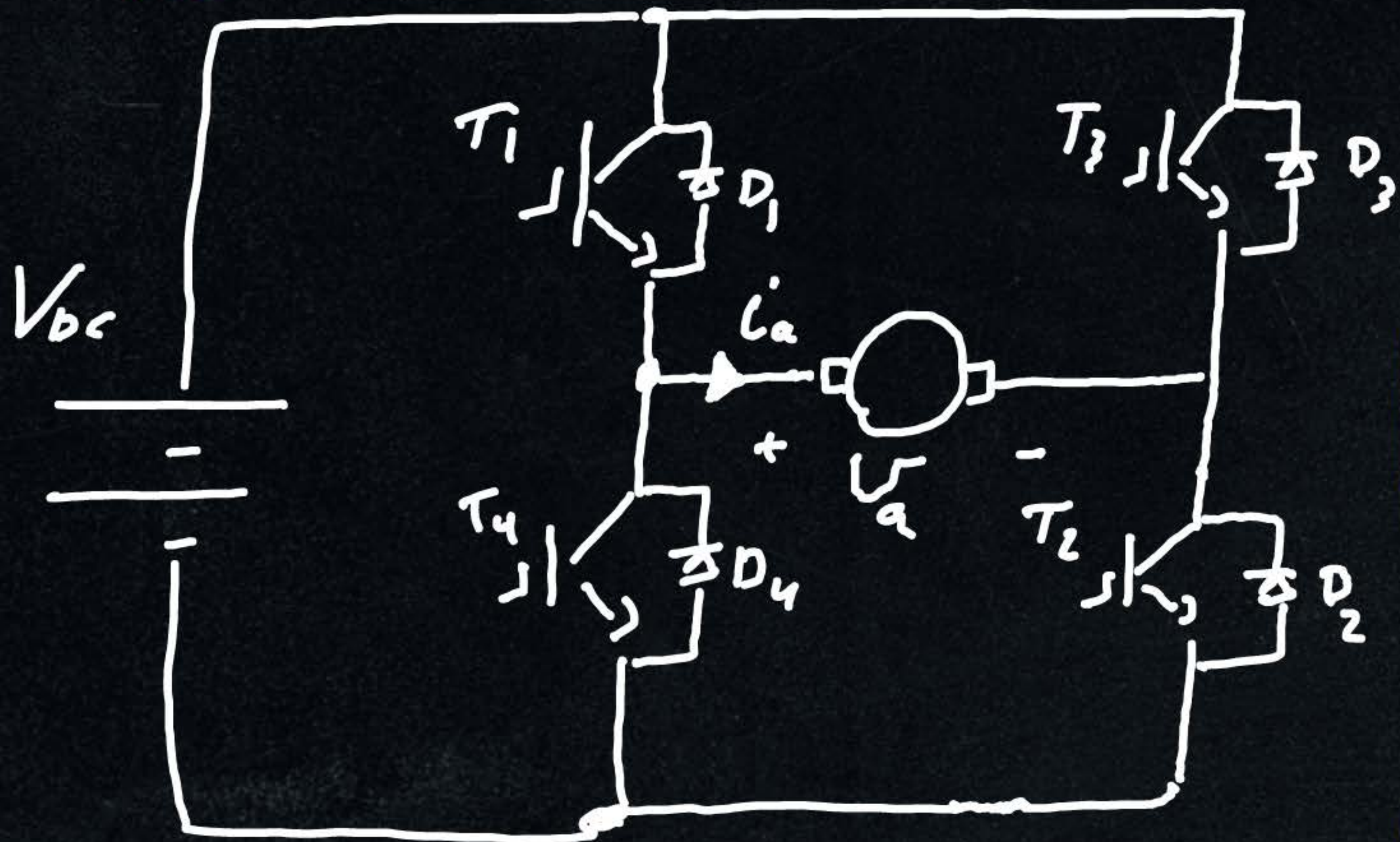


	Conducting Devices	$V_a$	$i_a$	$V_a i_a$
I	$T_1 T_2$	+	+	$V_{DC}$
I	$T_1 D_3$ or $T_2 D_4$	0	+	0
II	$D_3 D_4$	-	+	$-V_{DC}$
II	$T_1 D_3$ or $T_2 D_4$	0	+	0
III	$T_3 T_4$	-	-	$-V_{DC}$
III	$T_3 D_1$ or $T_4 D_2$	0	-	0
IV	$D_1 D_2$	+	-	$V_{DC}$
IV	$T_3 D_1$ or $T_4 D_2$	0	-	0

# 2 quadrant chopper

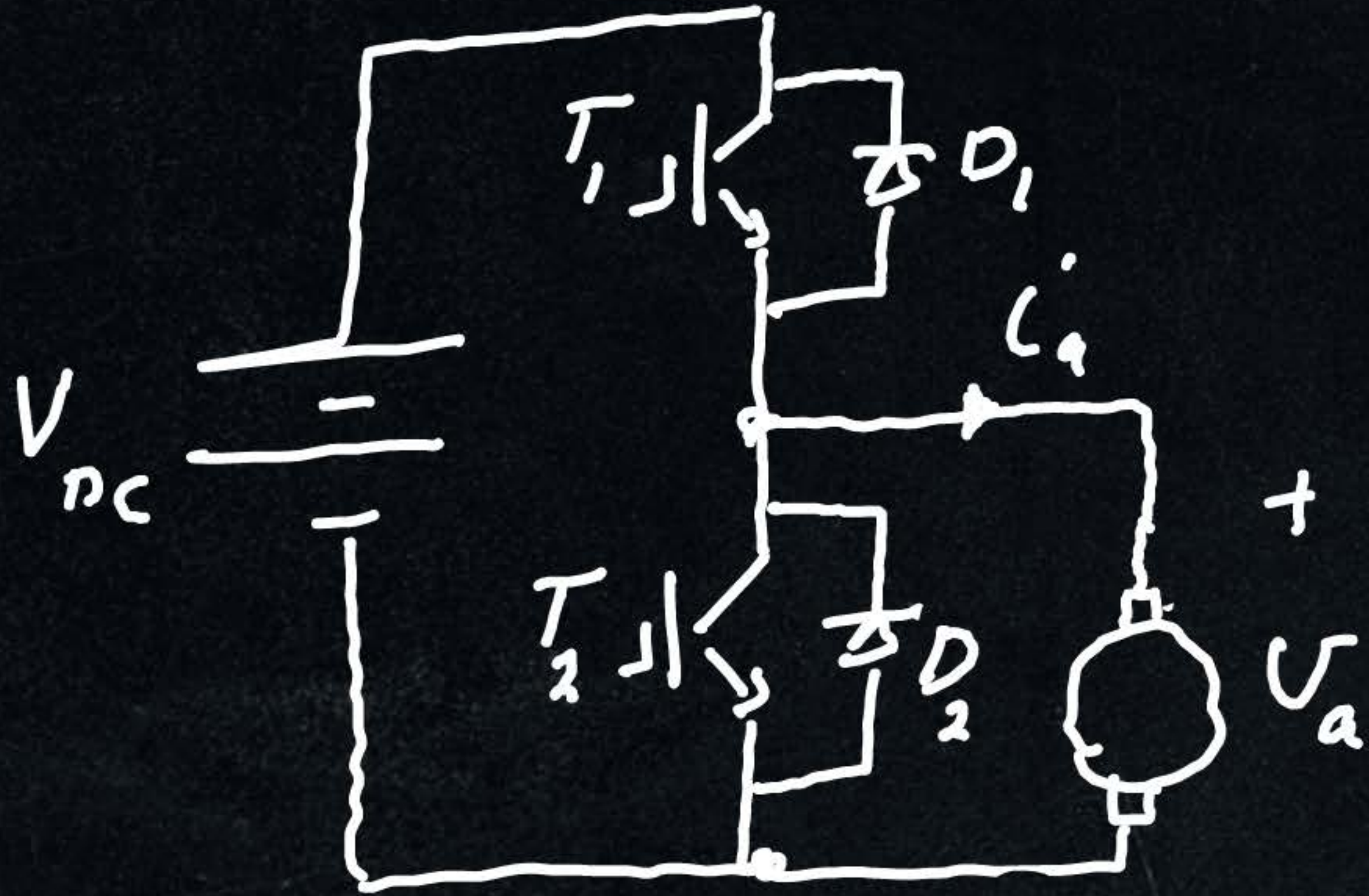


Q	Conducting Devices	$V_a$	$I_a$	$V_a$
I	$T_1$	+	+	$V_{oc}$
I	$D_2$	0	+	0
IV	$T_2$	0	-	0
IV	$D_1$	+	-	$V_{oc}$

# 1 quadrant chopper


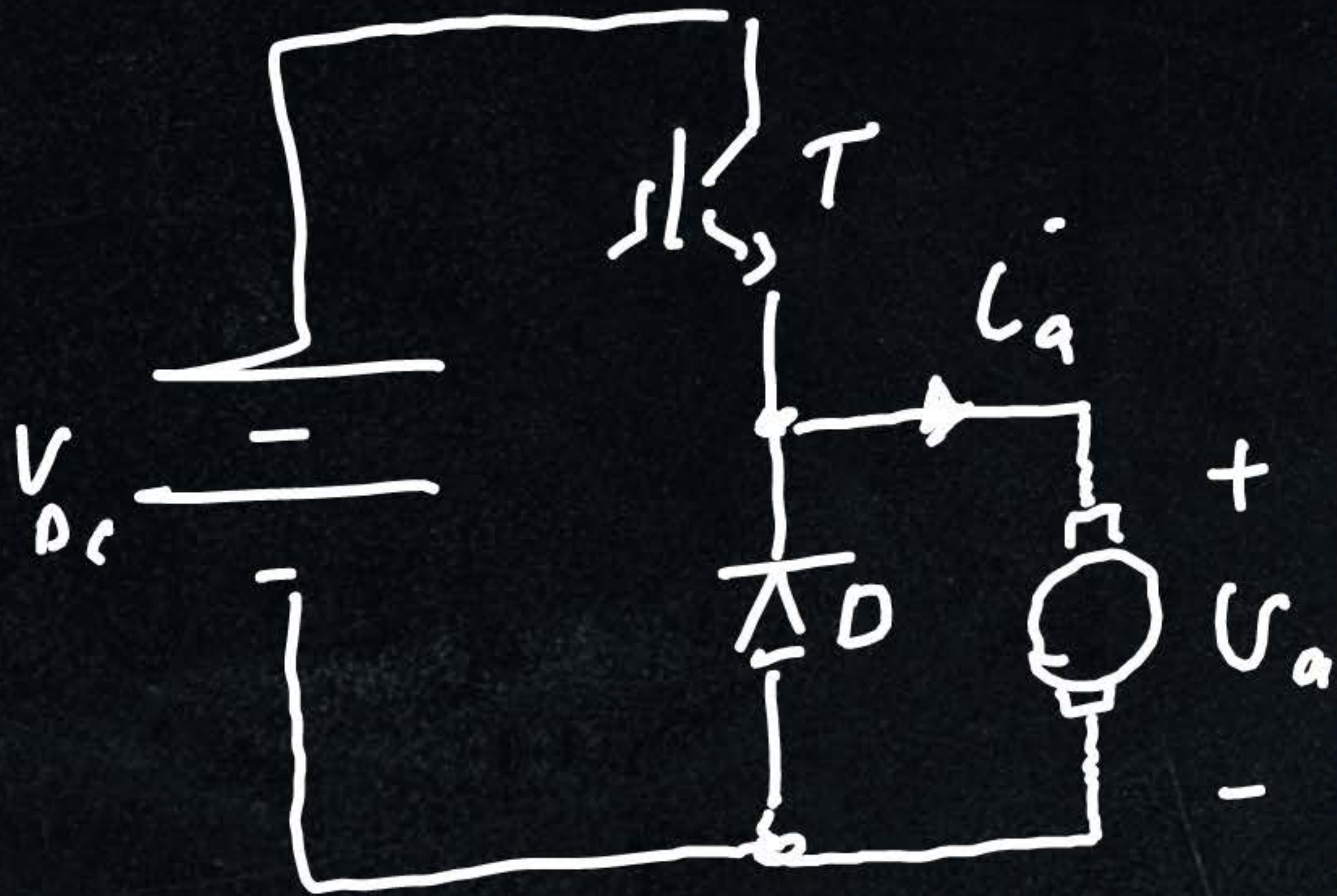


Q	conducting Devices	$U_a$	$i_a$	$U_a$
I	T	+	+	$V_{dc}$
I	D	0	+	0

# Block Diagram of Control system

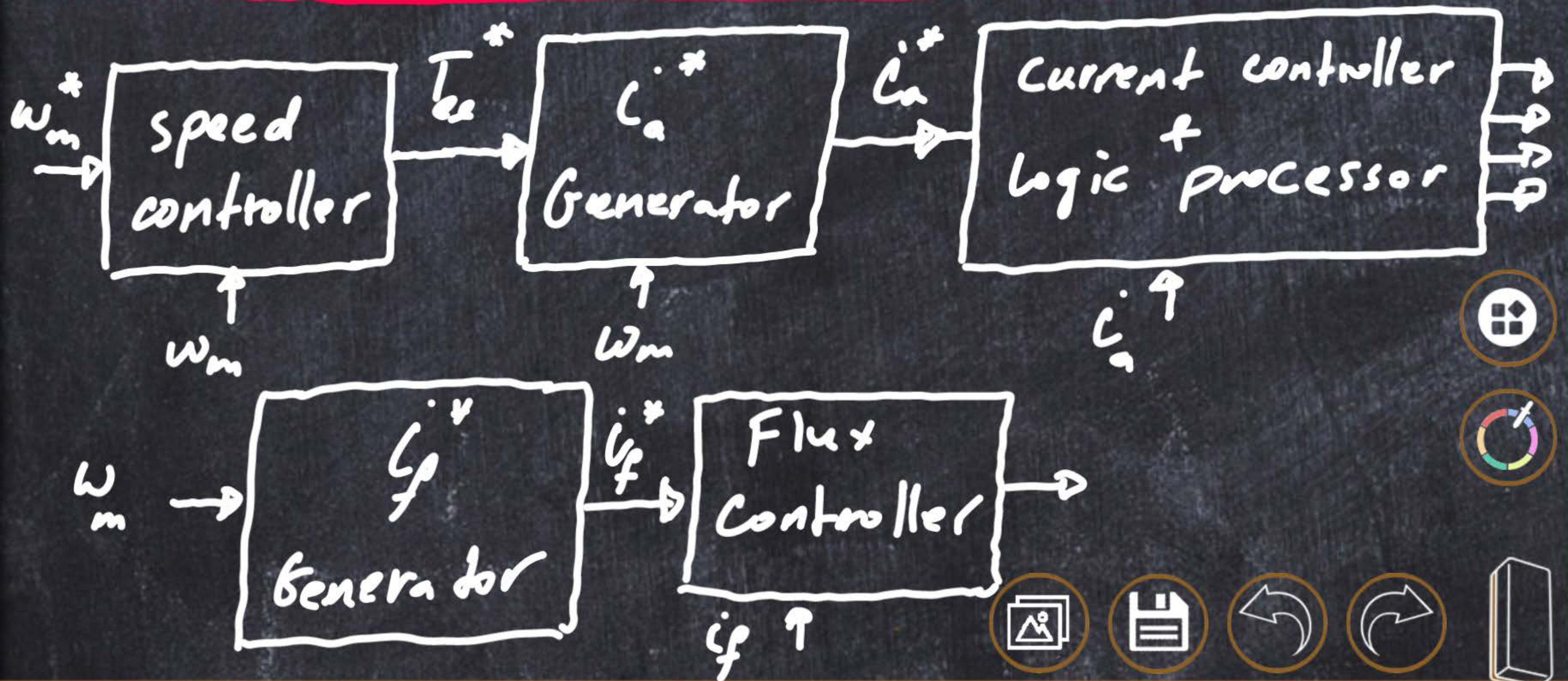

# Block Diagram of Control System

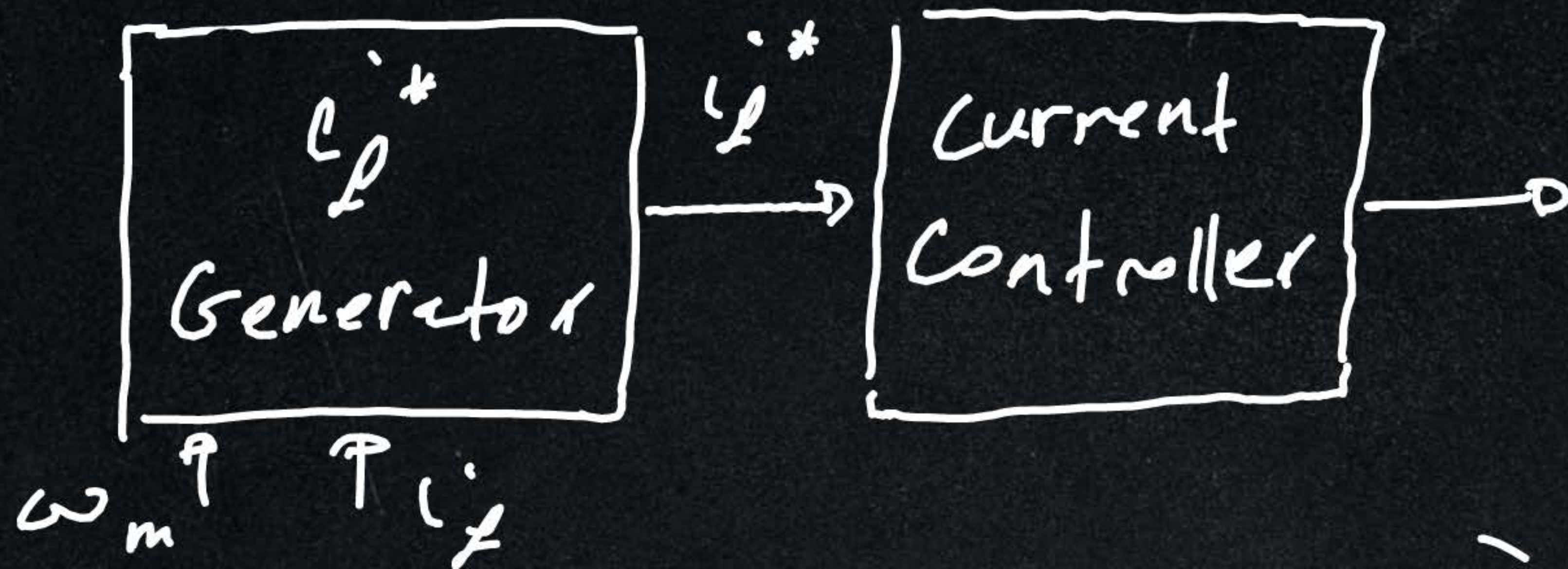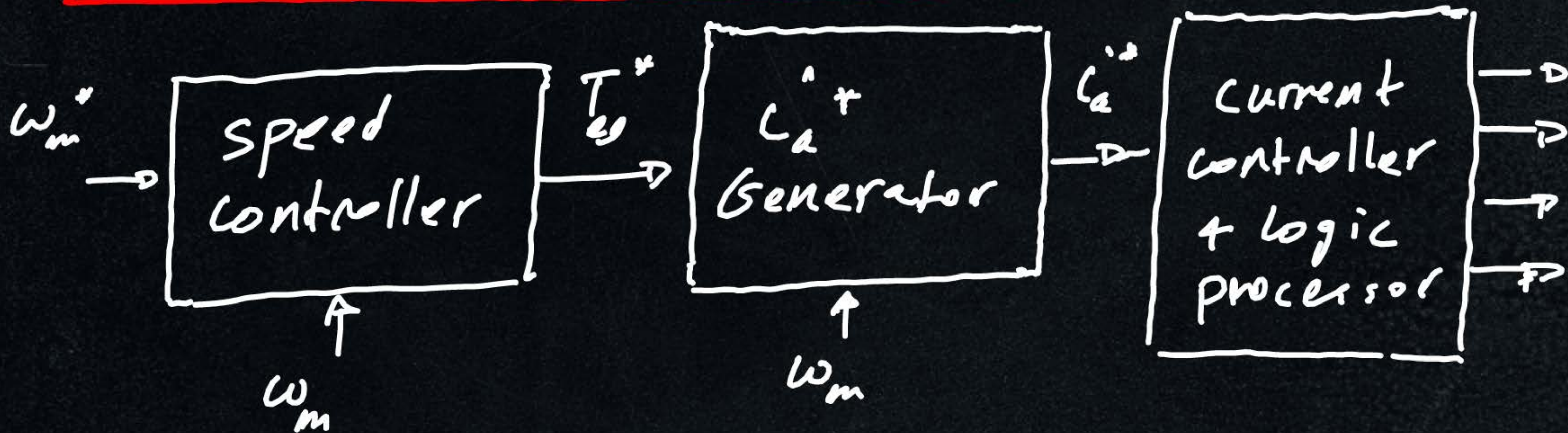


# $L_f^*$ Generator

If  $\omega_m \leq \omega_{m,r}$

$$L_f^* = L_{f,r} = \frac{\Phi_{f,r}}{C}$$

If  $\omega_m > \omega_{m,r}$
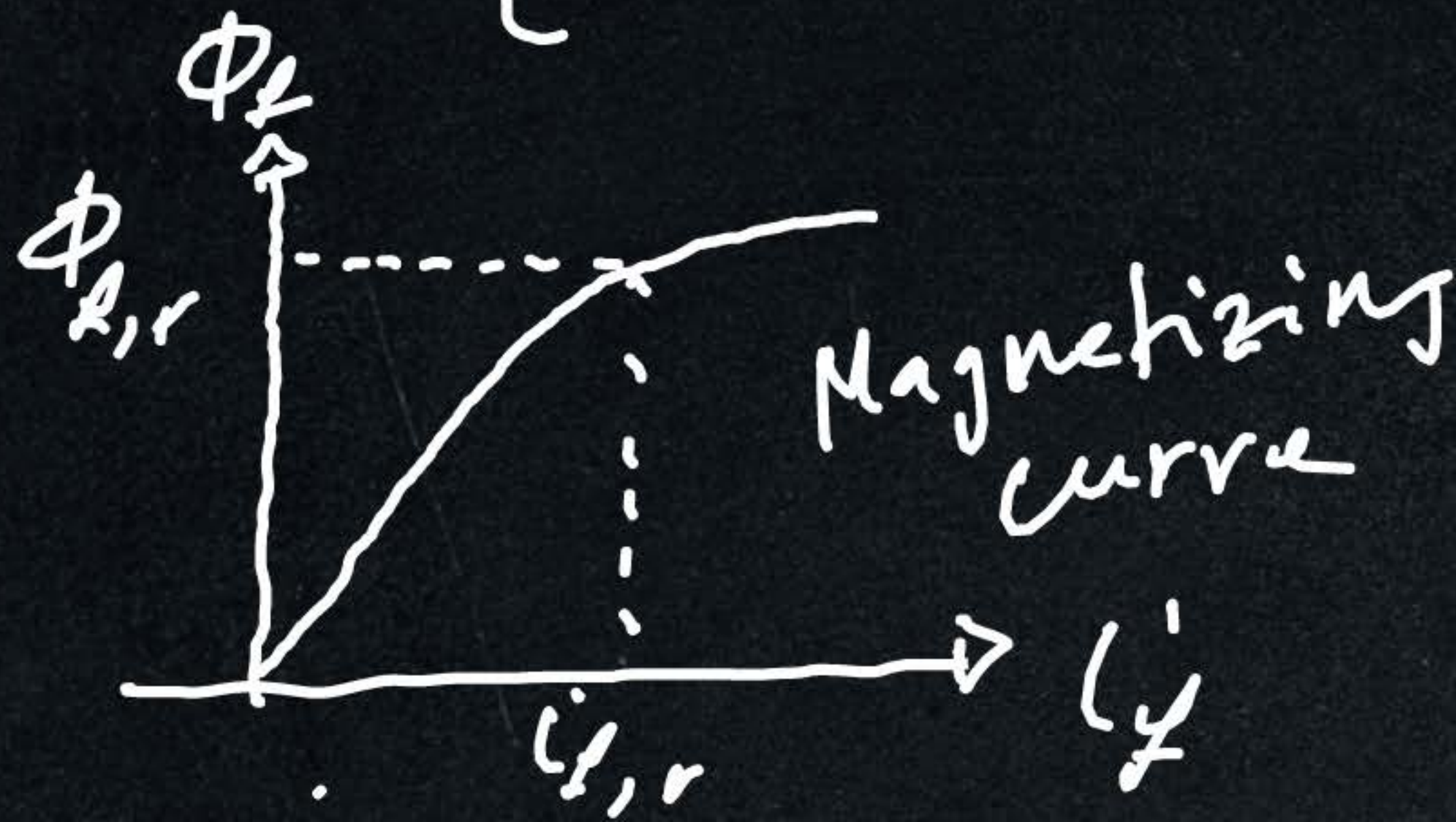
$$L_f^* = L_{f,r} \frac{\omega_{m,r}}{\omega_m}$$





# $C_a^*$ Generator

$$T_{el}^* = k \Phi_f C_a^* \Rightarrow C_a^* = \frac{T_{el}^*}{k \Phi_f}$$

If  $\omega_m \leq \omega_{m,r}$

$$C_a^* = \frac{1}{k \Phi_{f,r}} T_{el}^*$$


If  $\omega_m > \omega_{m,r}$

$$C_a^* = \frac{\omega_m}{k \Phi_{f,r} \omega_{m,r}} T_{el}^*$$
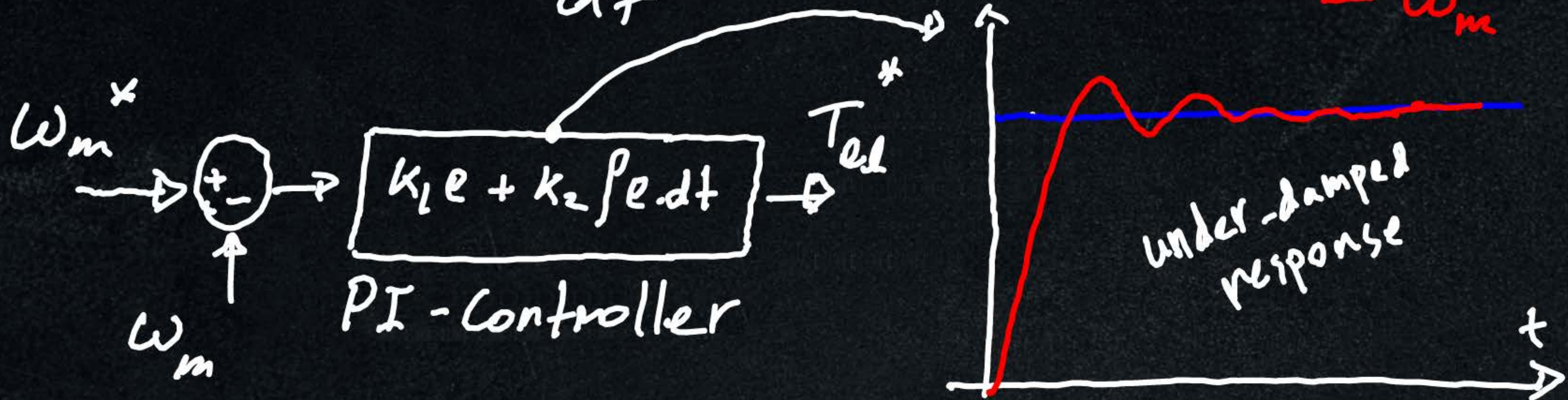
# speed controller


It is designed using Newton's 2<sup>nd</sup> Law:

$$T_{el} = T_L + J \frac{d\omega_m}{dt}$$


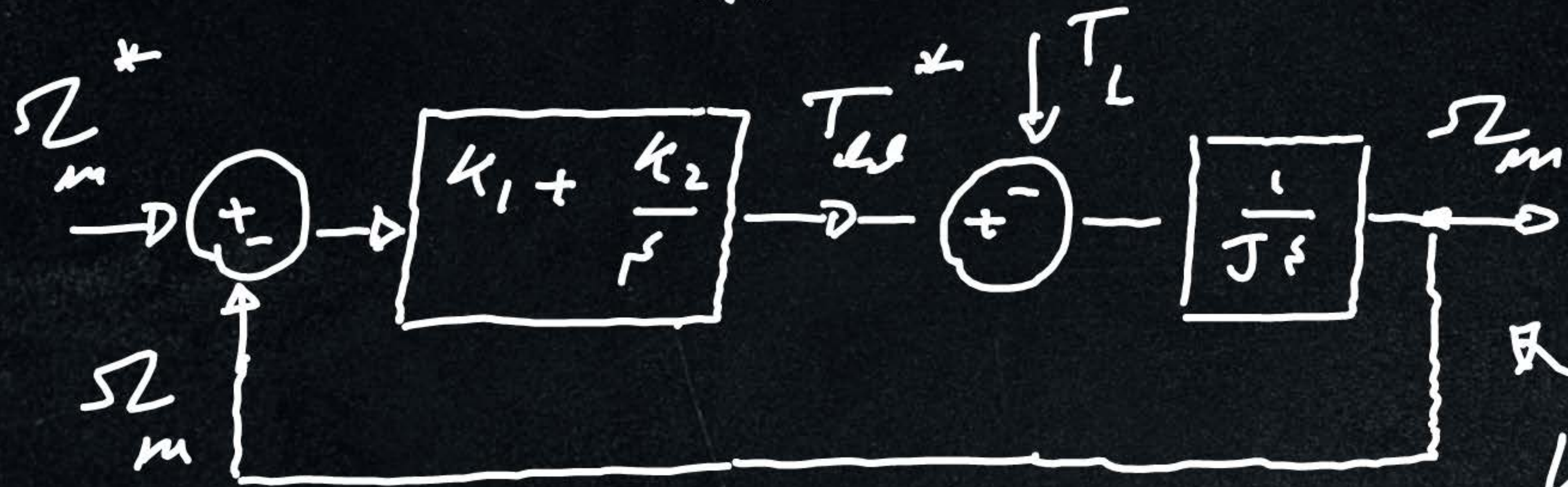
# Design of speed controller in s-domain

$$T_{eq} = T_L + J \frac{dw_m}{dt} \xrightarrow{\mathcal{L}} T_{eq} = T_L + s J \omega_m$$



↻ Closed loop control system

# Transfer Function

$$\Omega_m = T_1 \Omega_m^* + T_2 T_L$$


$$T_1 = \frac{\Omega_m}{\Omega_m^*} \quad \text{when } T_L = 0$$

$$T_2 = \frac{\Omega_m}{T_L} \quad \text{when } \Omega_m^* = 0$$

superposition

"Linear system"

$T_1$ ??

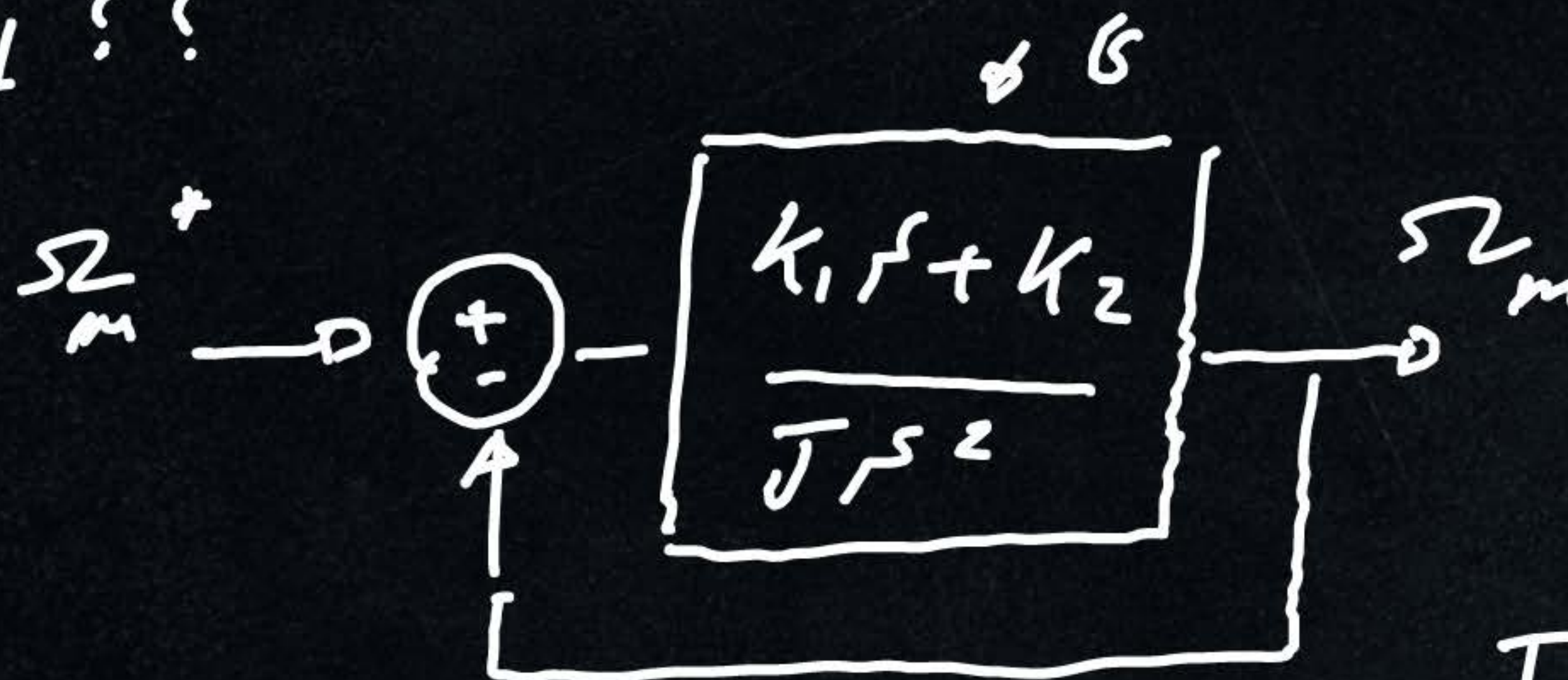

$$T_1 = \frac{G}{1+G}$$

$$T_1 = \frac{(k_1 s + k_2) / (J s^2)}{1 + [(k_1 s + k_2) / (J s^2)]}$$

$$T_1 = \frac{k_1 s + k_2}{J s^2 + k_1 s + k_2} = \frac{k_1}{J} \left[ \frac{s + k_2/k_1}{s^2 + \left(\frac{k_1}{J}\right) s + \left(\frac{k_2}{J}\right)} \right]$$


In general  $T_1 = k \frac{s + a}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

$\zeta$ : Damping ratio,  $\omega_n$ : Natural frequency


$\zeta < 1$  underdamped

$\zeta = 1$  critically damped

$\zeta > 1$  overdamped

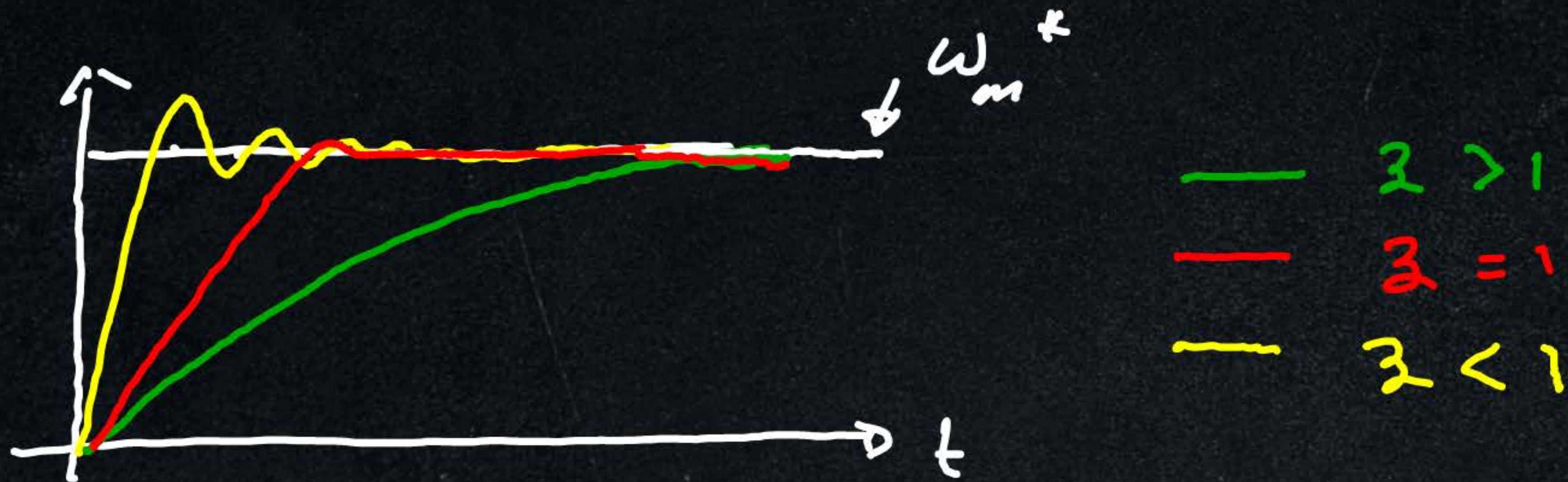

$T_2$  ??

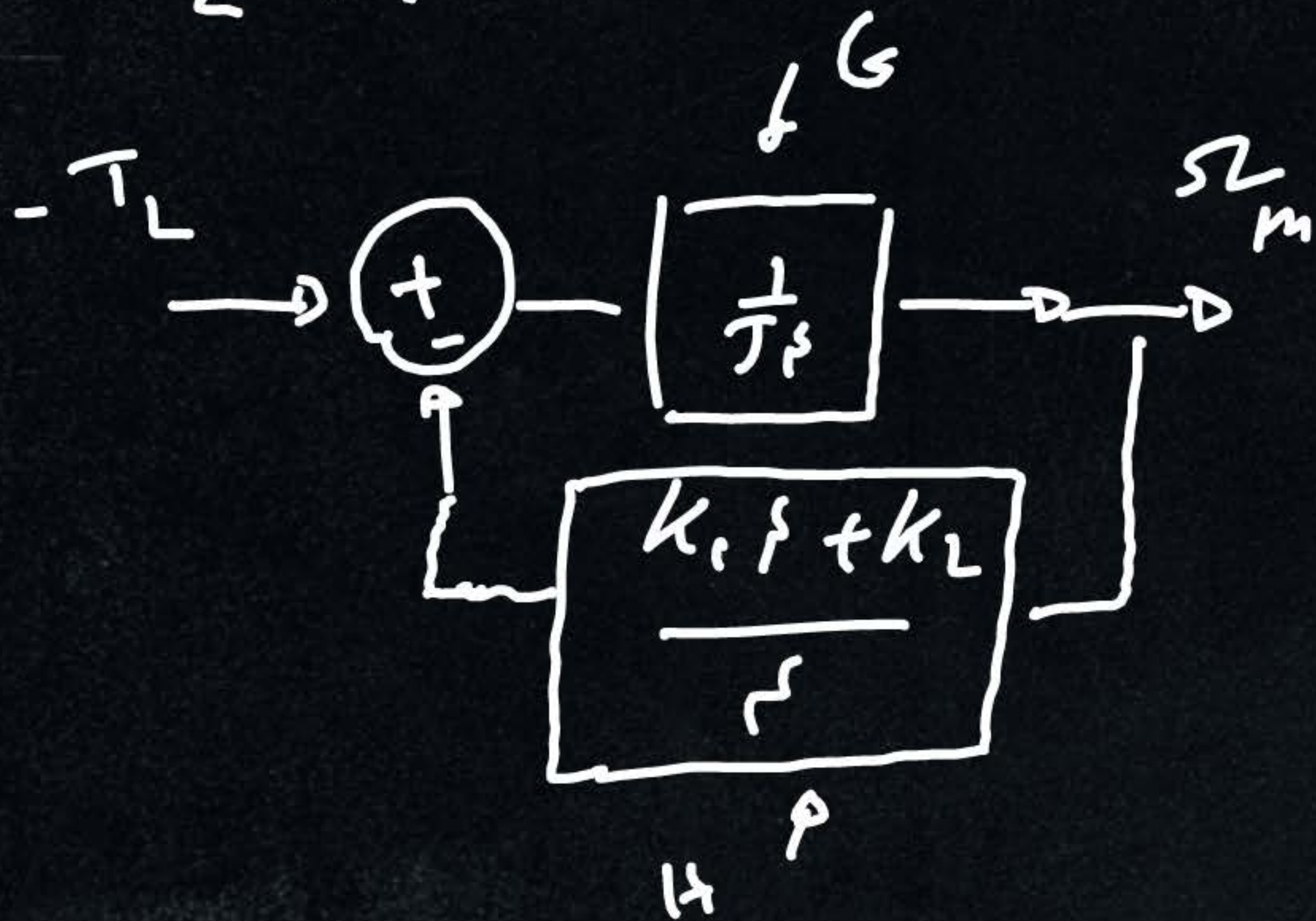

$$T_2 = \frac{-G}{1 + GH}$$

$$T_2 = \frac{-1/Jp}{1 + \frac{k_1 p + k_2}{Jp^2}}$$

$$T_2 = \frac{-p}{Jp^2 + k_1 p + k_2} = \frac{-1}{J} \left[ \frac{p}{p^2 + \left(\frac{k_1}{J}\right)p + \left(\frac{k_2}{J}\right)} \right]$$

$$\Omega_m = T_1 \Omega_m^* + T_2 T_L$$

$$T_1 = \frac{k_1}{J} \left[ \frac{s + \frac{k_2}{k_1}}{s^2 + \frac{k_1}{J}s + \frac{k_2}{J}} \right], \quad T_2 = \frac{-1}{J} \left[ \frac{s}{s^2 + \frac{k_1}{J}s + \frac{k_2}{J}} \right]$$

$$W_{m,ss} = \lim_{t \rightarrow \infty} \omega_m(t) = \lim_{s \rightarrow 0} s \Omega_m = \lim_{s \rightarrow 0} s T_1 \Omega_m^* + \lim_{s \rightarrow 0} s T_2 T_L$$


Assume  $\omega_m^* = A u(t)$  &  $T_L = B u(t)$

$$\xrightarrow{\mathcal{L}} \Omega_m^* = A/s \quad \& \quad T_L = B/s$$



$$\omega_{m,ss} = \lim_{s \rightarrow 0} \frac{s}{T_1} \frac{A}{s} + \lim_{s \rightarrow 0} \frac{s}{T_2} \frac{B}{s}$$

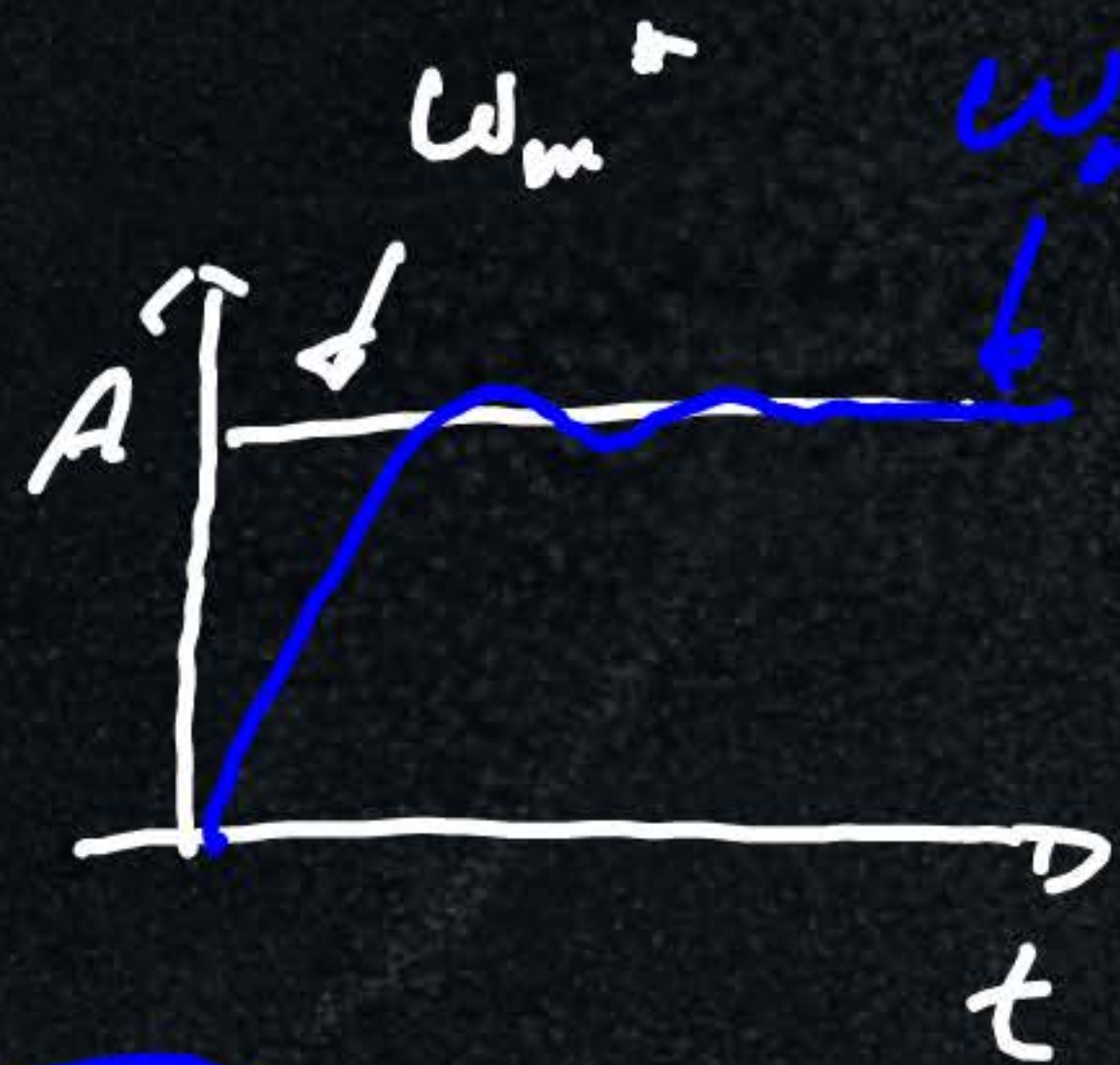
$$\omega_{m,ss} = A \lim_{s \rightarrow 0} T_1 + B \lim_{s \rightarrow 0} T_2$$



$\omega_{m,ss} = A \rightarrow$  zero ss error
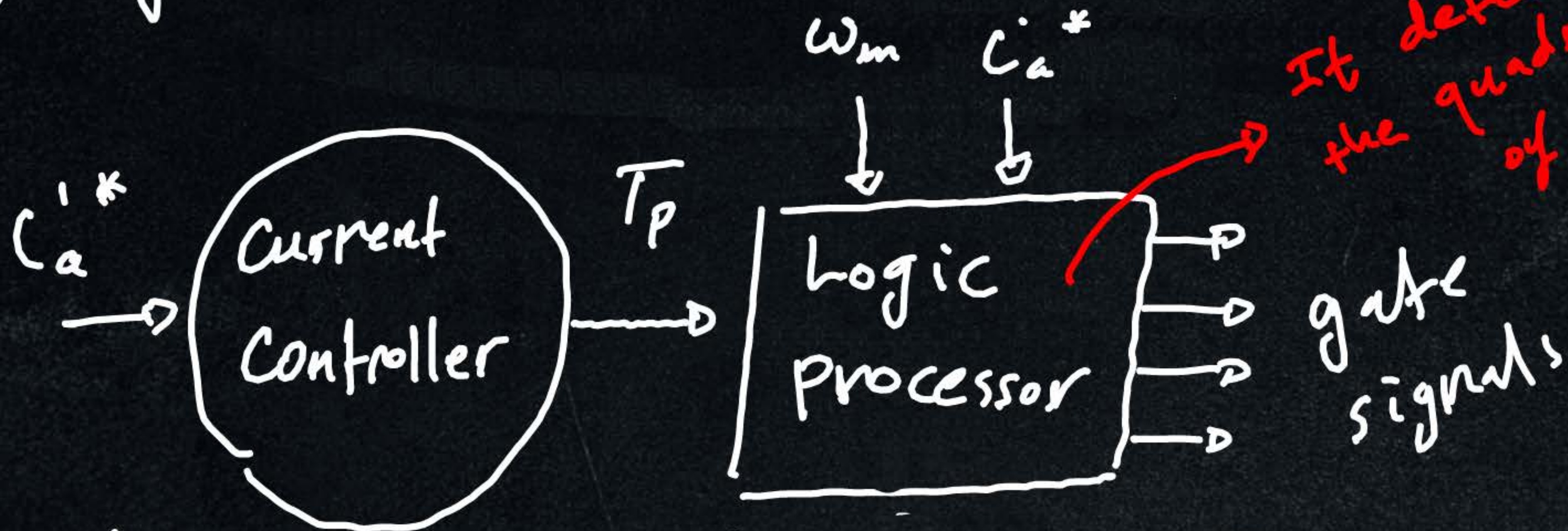
# Current Controller & Logic Processor

- ① PWM Current Controller
- ② Hysteresis Current Controller




It determines the quadrant of operation

$T_p$ : On-time signal .  $T_p = 1 \quad V_a = \pm U_{DC}$   
 $T_p = 0 \quad V_a = 0$

# Table of logic processor

Q	$T_P$	$T_1$	$T_2$	$T_3$	$T_4$
H	1	1	1	0	0
H	0	1	0	0	0
H	1	0	0	0	0
H	0	1	0	0	0
H	1	0	0	1	1
H	0	0	0	1	0
H	1	0	0	0	0
L	0	0	0	1	0

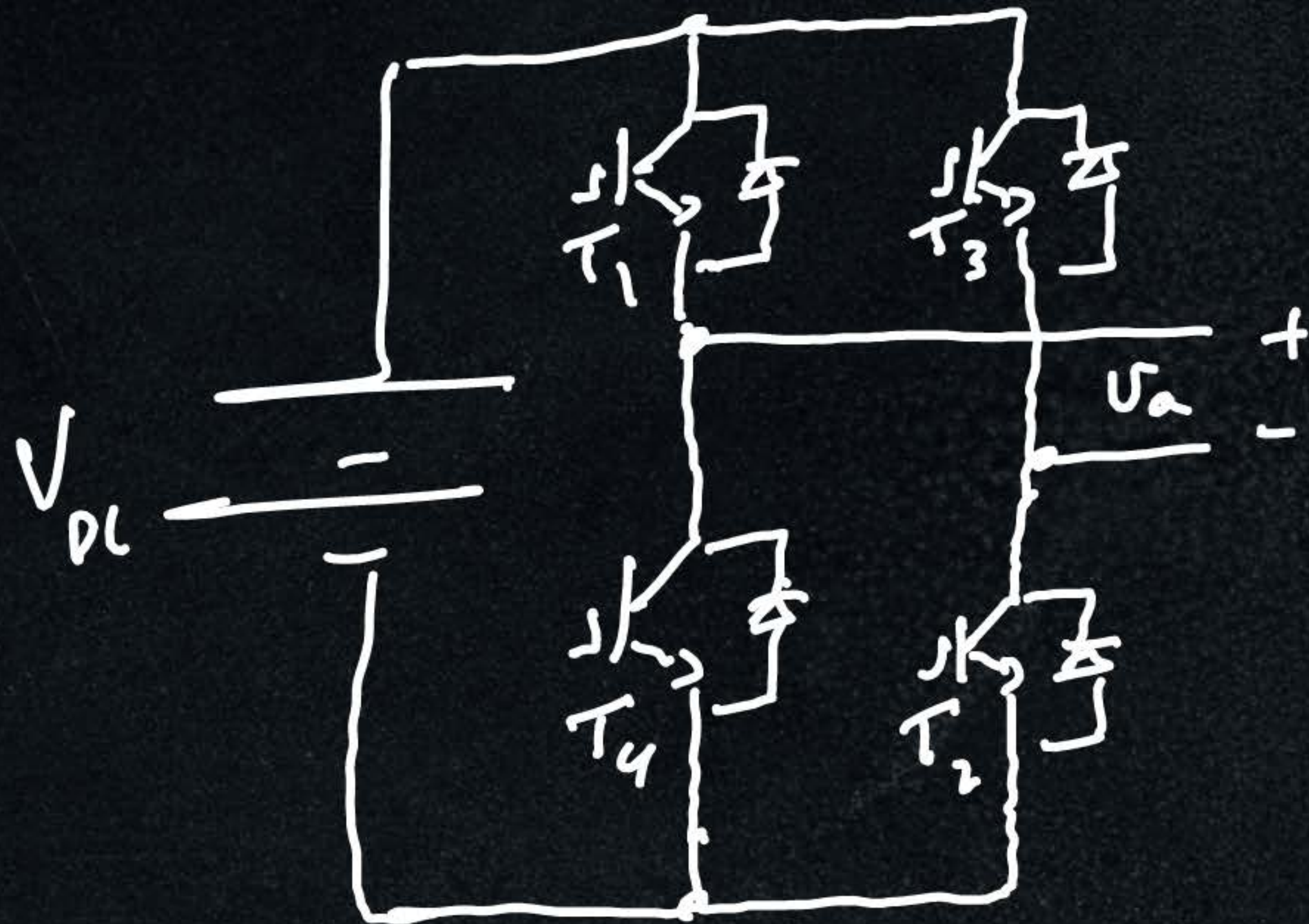


1: ON  
0: OFF

# Table of Logic processor

## Two-quadrant chopper



Q	$T_P$	$T_1$	$T_2$
I	1	1	0
H	0	0	0
$\frac{1}{2}I$	1	0	0
$\frac{1}{2}H$	0	0	1

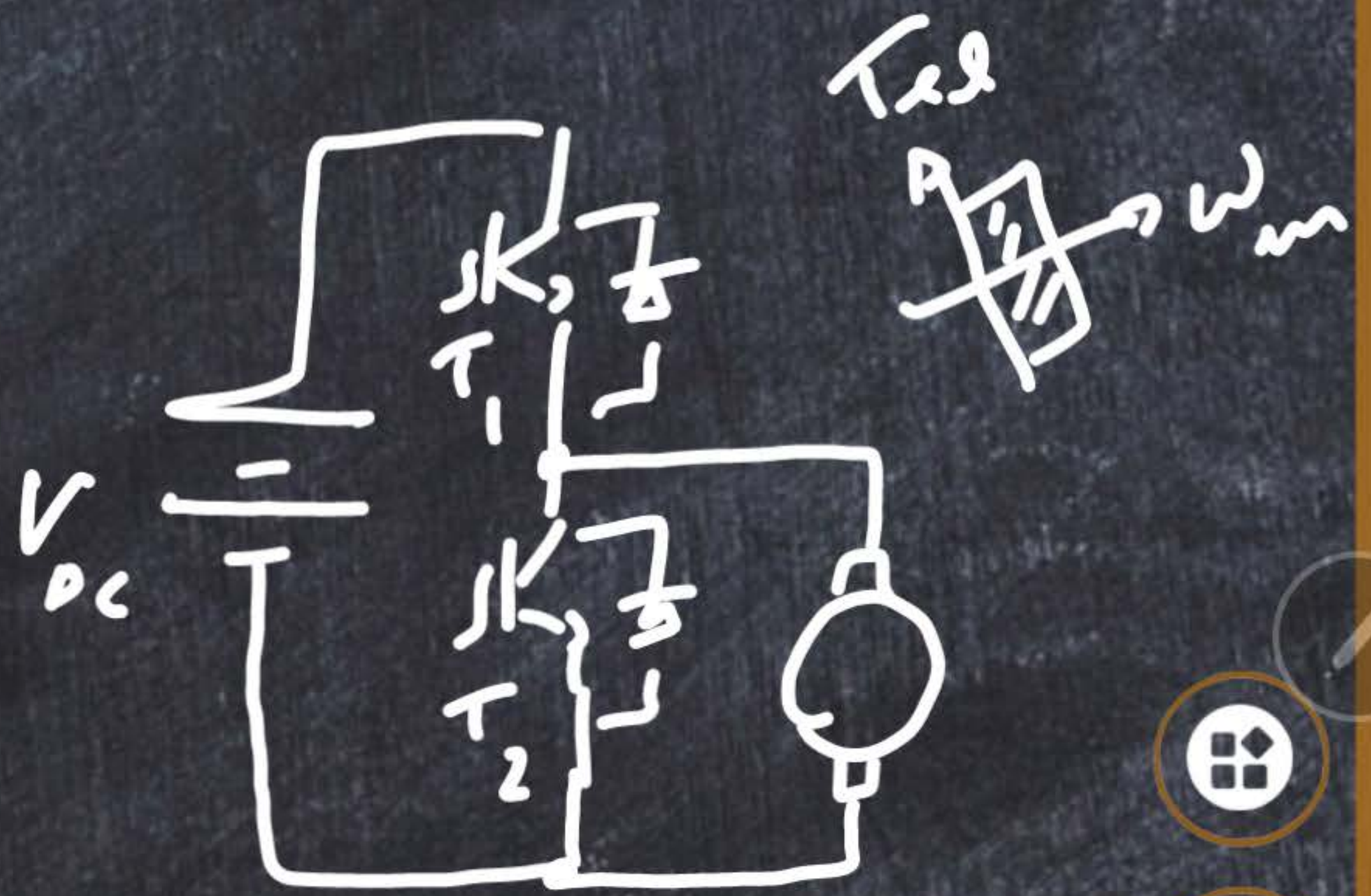


# Table of logic processor

## One-quadrant chopper

$\phi$	$T_p$	$T_i$
1	1	1
1	0	0

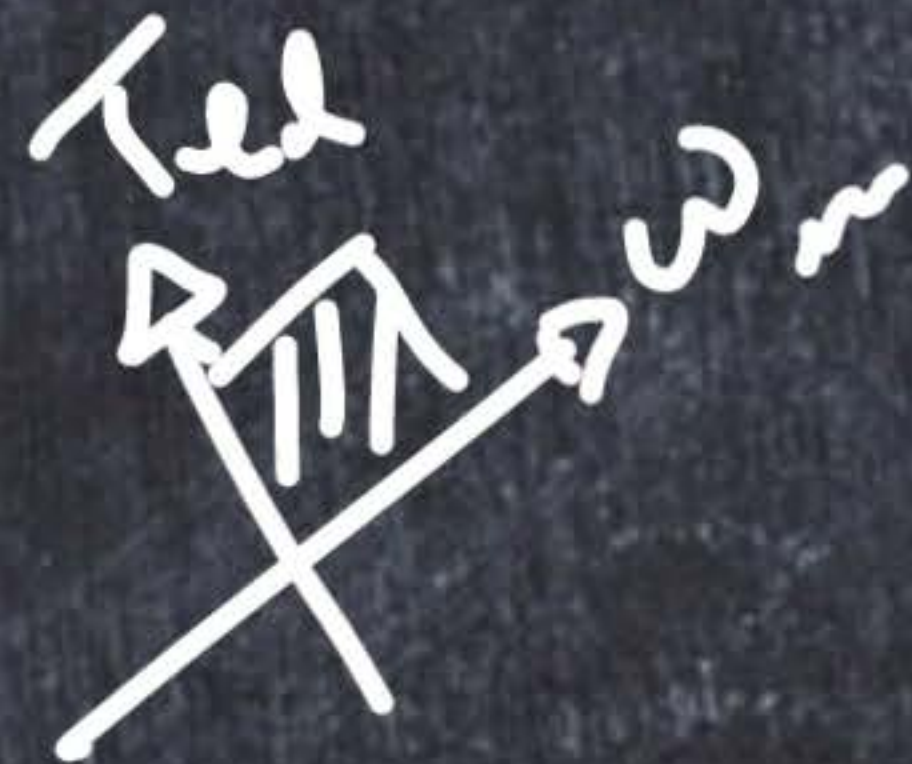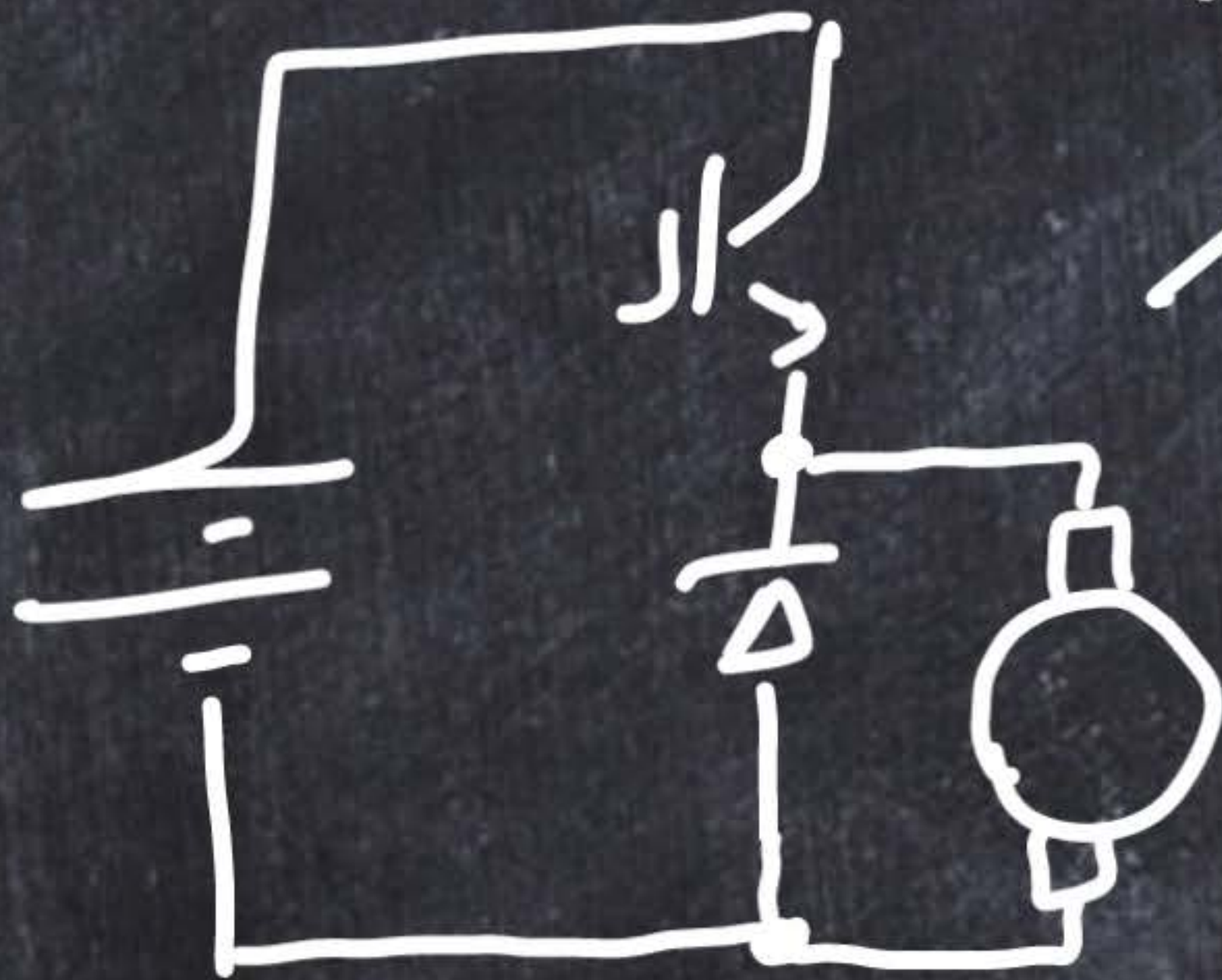

# ① PWM current controller

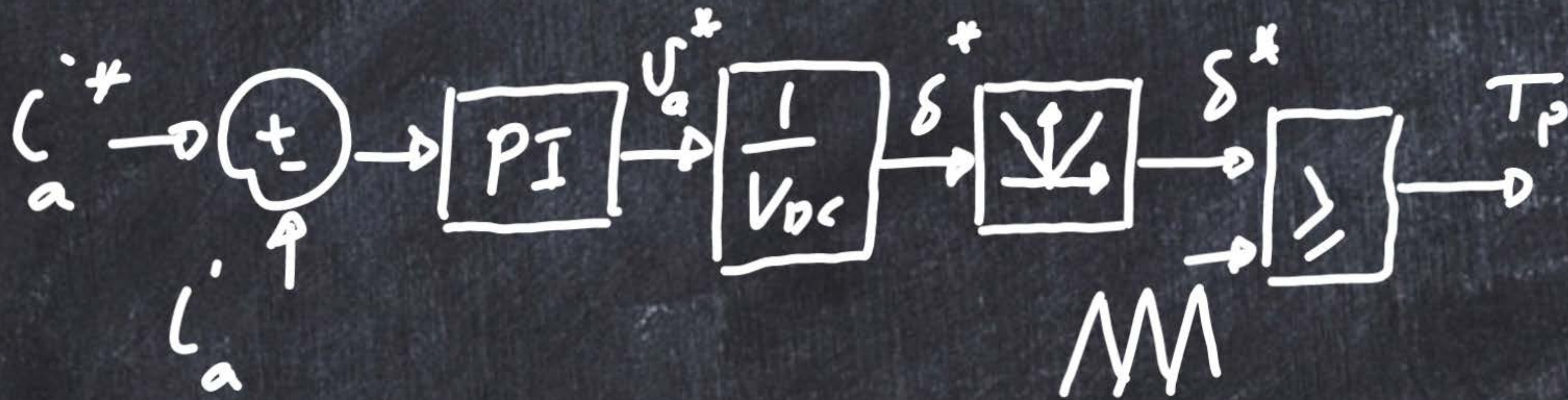

Implementation of PWM CC



## Design of PWM CC

It is designed by using the KVL equation in the armature circuit:


$$V_a = R_a I_a + L_a \frac{dI_a}{dt} + E_a$$

$\xrightarrow{L}$

$$V_a = (R_a + f L_a) I_a + E_a$$



# Block diagram in $s$ -domain

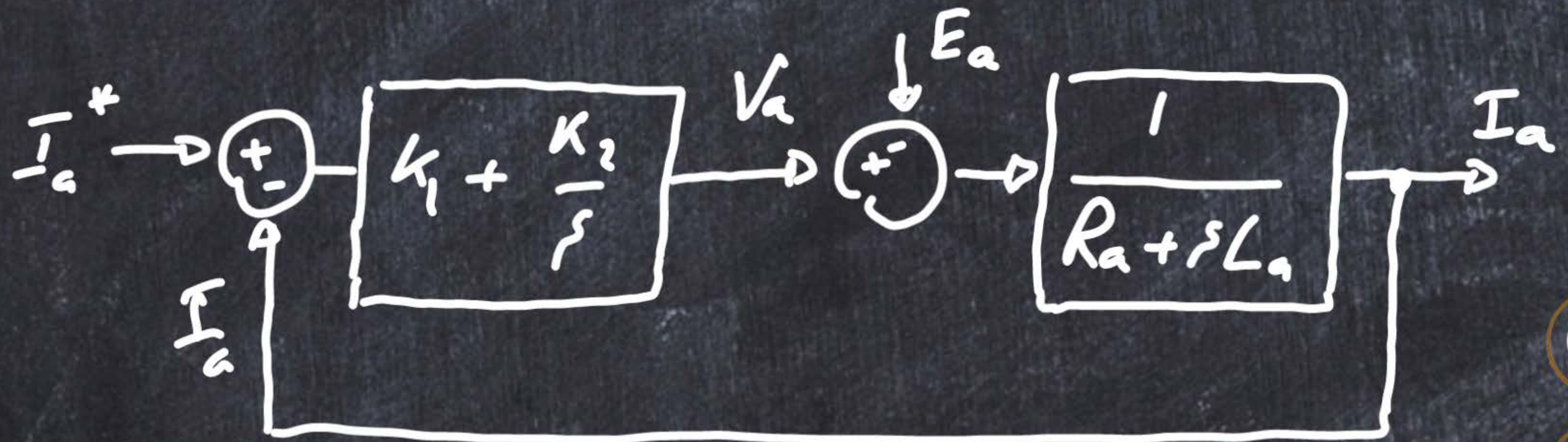

$$I_a = T_1 I_a^* + T_2 E_a$$





# Transfer function

$$I_a = T_1 I_a^* + T_2 E_a$$

$$T_1 = \frac{I_a}{I_a^*} \Big|_{E_a=0} = \frac{G}{1+G} ; G = \frac{k_1 s + k_2}{s[R_a + sL_a]}$$

$$T_1 = \frac{(k_1 s + k_2) / (s(R_a + sL_a))}{1 + (k_1 s + k_2) / (s(R_a + sL_a))}$$



$$T_I = \frac{k_1 s + k_2}{k_1 s + k_2 + s^2 L_a + R_a s} = \frac{k_1 s + k_2}{s^2 L_a + (k_1 + R_a) s + k_2}$$

$$T_I = \frac{k_1}{L_a} \left( \frac{s + k_2/k_1}{s^2 + [(k_1 + R_a)/L_a] s + k_2/L_a} \right)$$


$$s^2 + 2\zeta\omega_n s + \omega_n^2$$

$$k_1 = 2\zeta\omega_n L_a - R_a$$

$$k_2 = \omega_n^2 L_a$$



## ② Hysteresis current controller

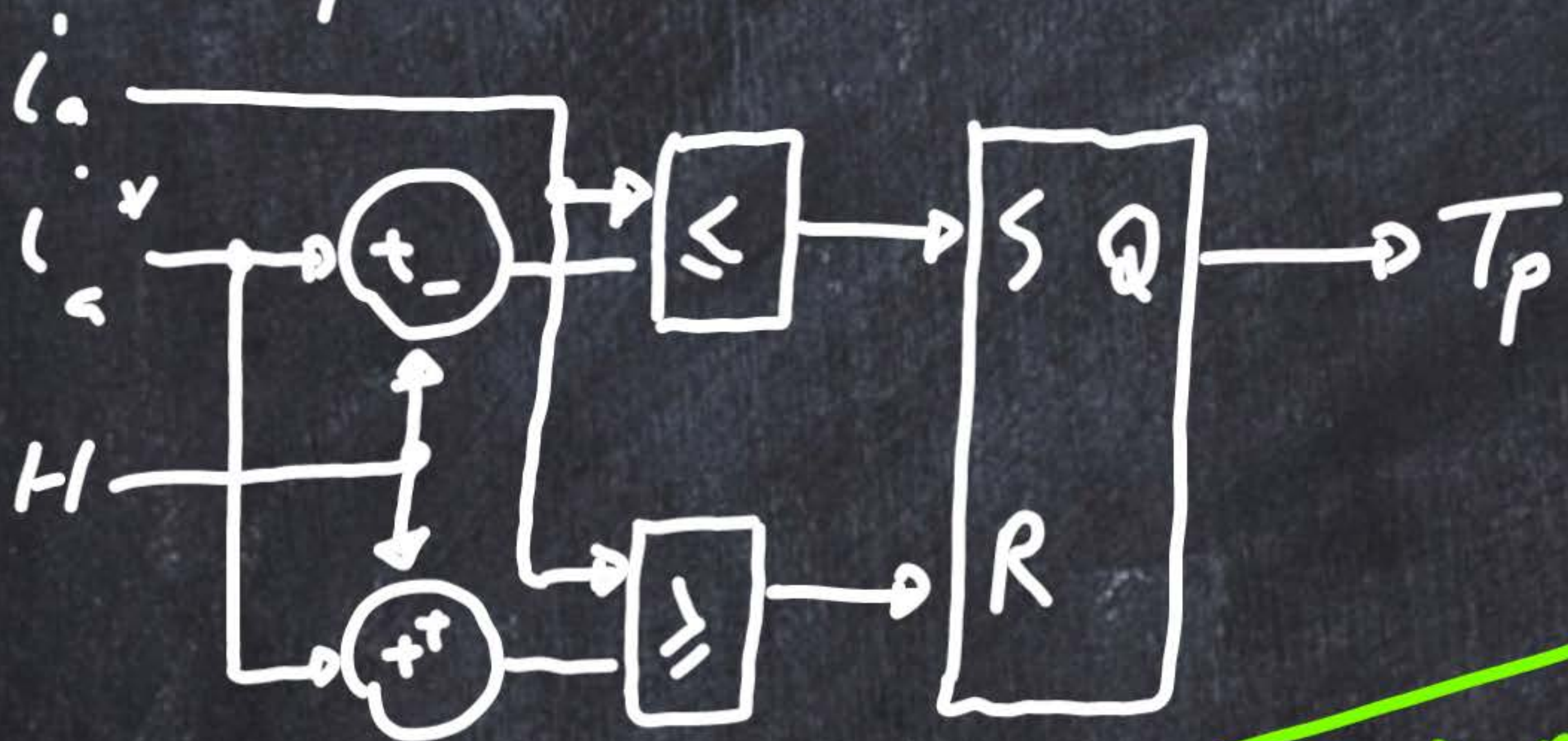


Implementation  
of HCC



# Flux Controller


① PWM CC

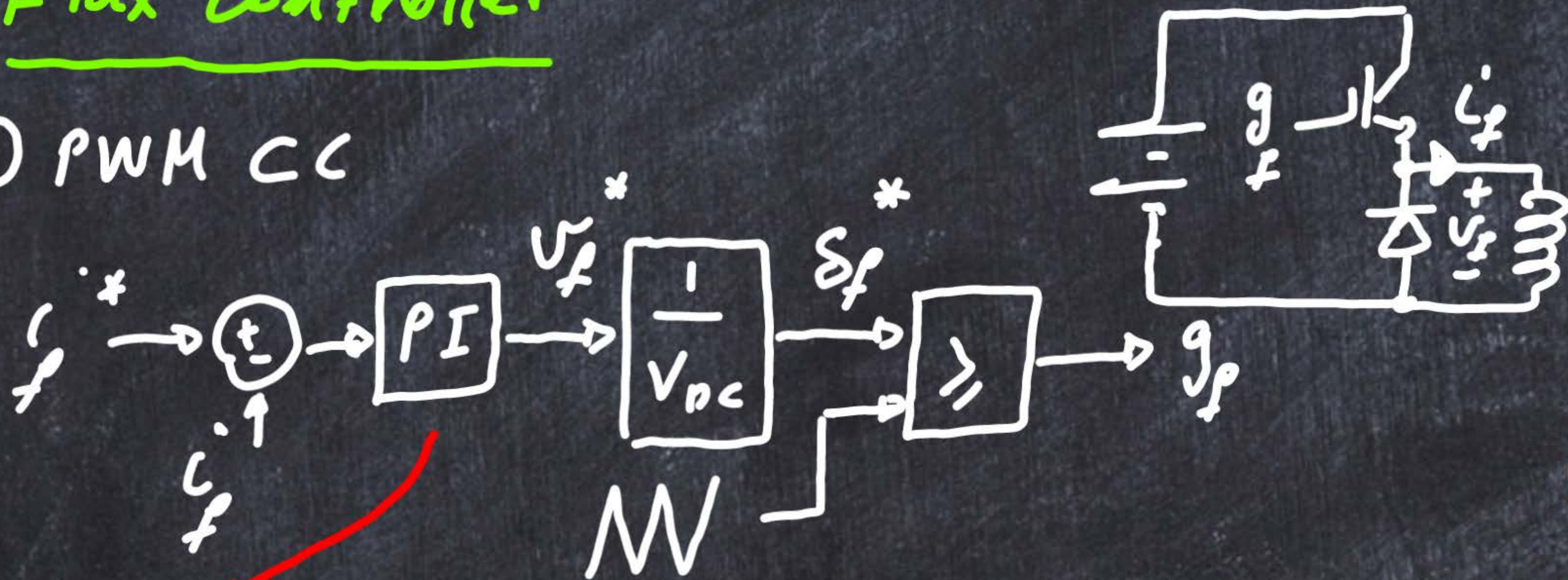

It is designed using the KVL equation in the field circuit.


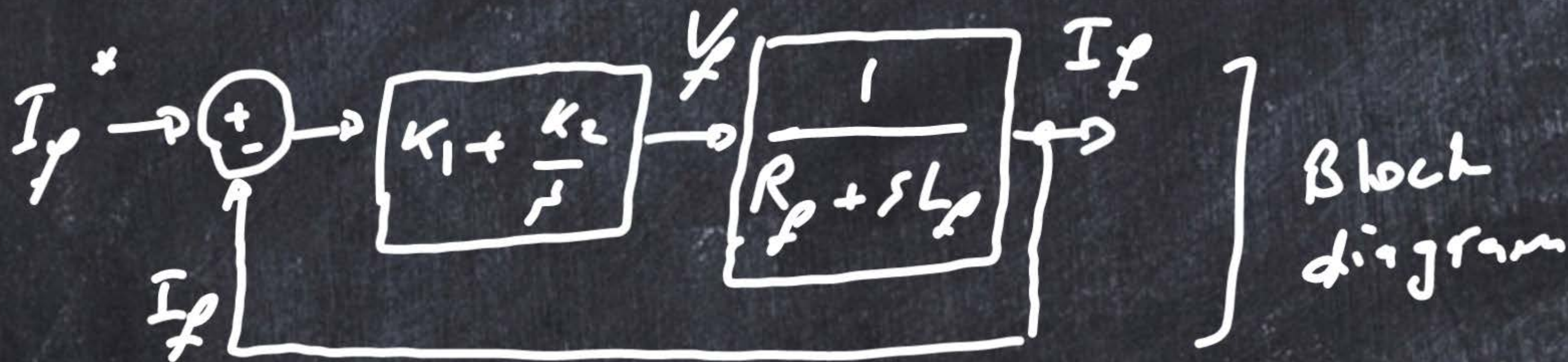
$$V_f = R_f + L \frac{di_f}{dt} \xrightarrow{\mathcal{L}} V_f = (R_f + sL_f) I_f$$



$$I_f = T I_p^* ; T = \frac{G}{1+G} ; G = \frac{k_1 s + k_2}{s [R_f + sL_f]}$$



$$T = \frac{k_1 s + k_2}{k_1 s + k_2 + R_p s + s^2 L_f}$$

$$T = \frac{k_1}{L_f} \left[ \frac{s + \frac{k_2}{k_1}}{s^2 + \left( \frac{k_1 + R_p}{L_f} \right) s + \frac{k_2}{L_f}} \right]$$


$$s^2 + 2\zeta\omega_n s + \omega_n^2$$

$$k_1 = 2\zeta\omega_n L_f - R_p$$

$$k_2 = \omega_n^2 L_f$$



## ② Hysteresis CC

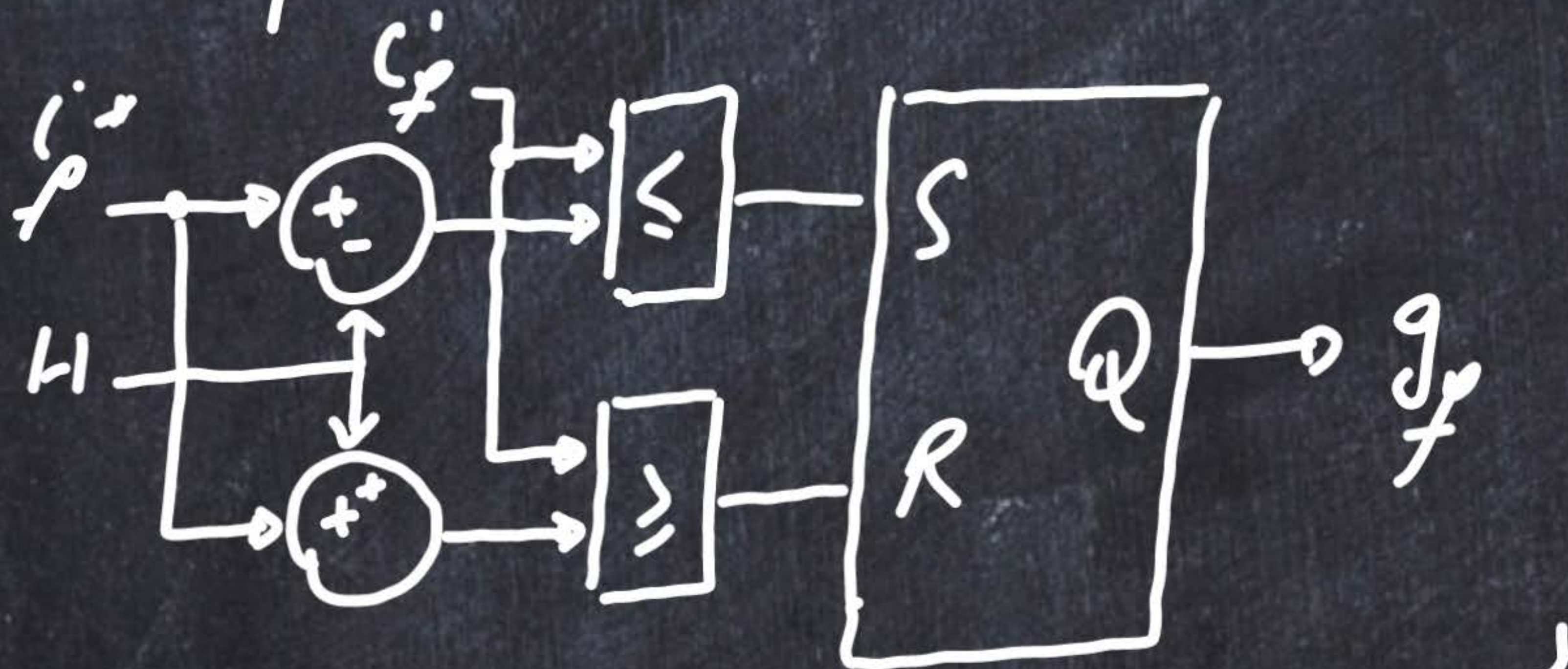

Implementation



# DC Motor Drive with Controlled Rectifiers

## ① Single-phase Controlled Rectifiers

1.1) Half-Wave

1.2) Semiconverter


1.3) Full-Wave

1.4) Dual Converter






# Line Diagram

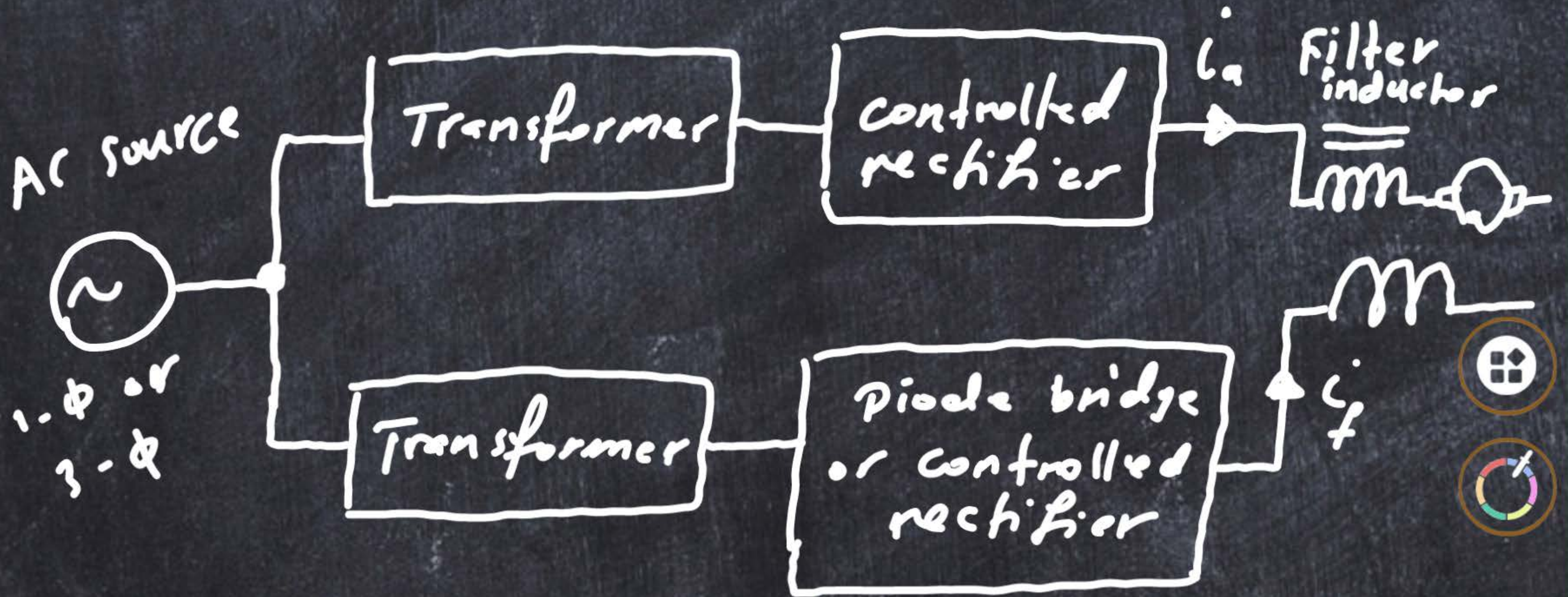

# 1.1) Half wave

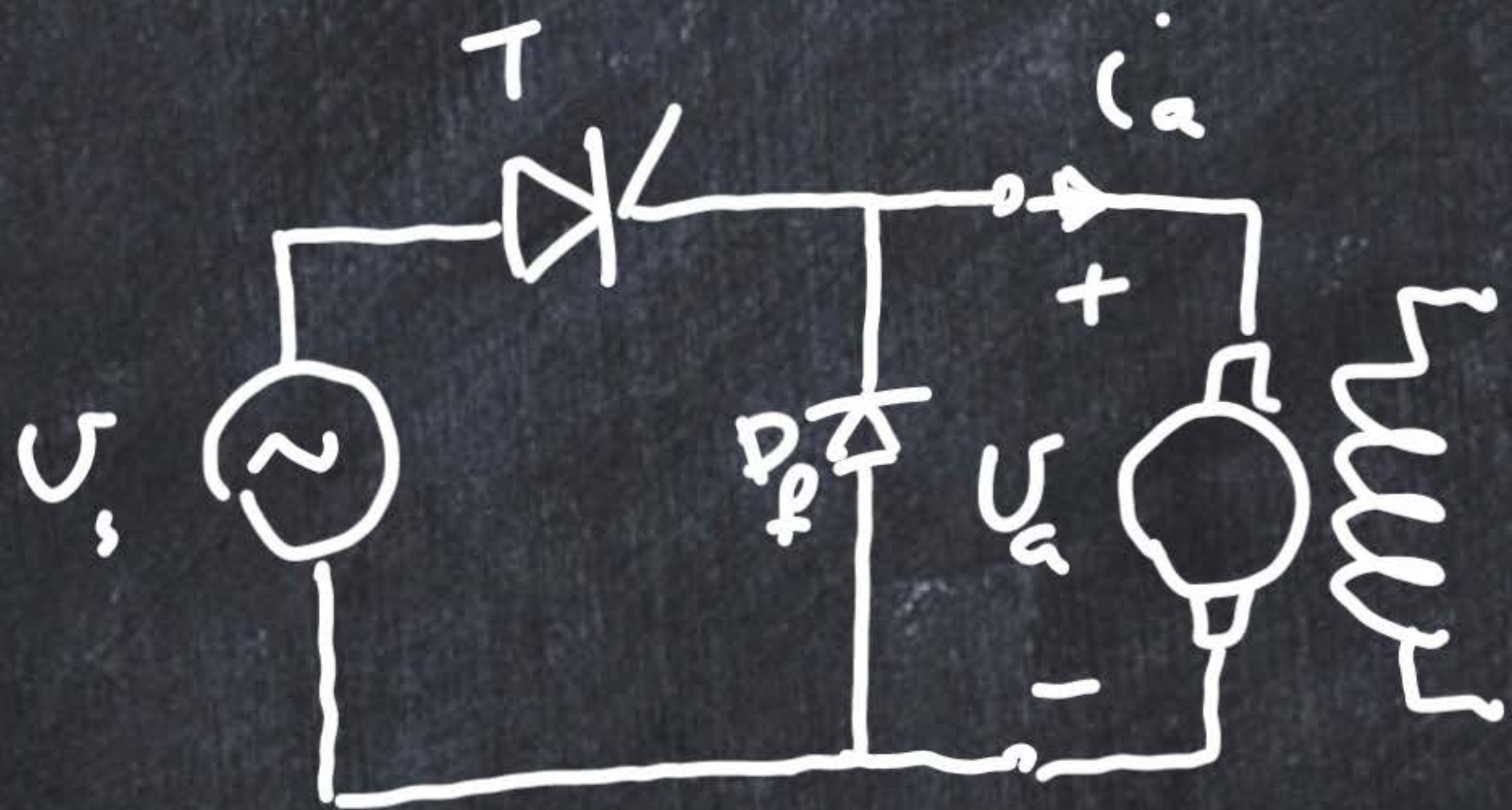

$$U_s = V_m \sin(\omega t)$$



1.1) Half-wave

$$V_a = \frac{1}{2\pi} \int_0^{\pi} v_a d(\omega t)$$

$$V_a = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{2\pi} \left[ \cos \omega t \right]_{\alpha}^{\pi}$$

$$V_a = \frac{V_m}{2\pi} (1 + \cos \alpha)$$



## 1.2) Semi converter

$$V_a = \frac{1}{2\pi} \int_0^{2\pi} v_a d(\omega t) = \frac{2}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t$$

$$V_a = \frac{V_m}{\pi} \cos(\omega t) \Big|_{\alpha}^{\pi}$$

$$V_a = \frac{V_m}{\pi} (1 + \cos \alpha)$$



1.3) Full-wave  
 $2\pi$

$$V_a = \frac{1}{2\pi} \int_0^{2\pi} V_a d(\omega t) = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin(\omega t) d\omega t$$

$$V_a = \frac{V_m}{\pi} \cos \omega t \Big|_{\pi+\alpha}^{\alpha}$$


$$V_a = \frac{2V_m}{\pi} \cos \alpha$$




Half




Semi

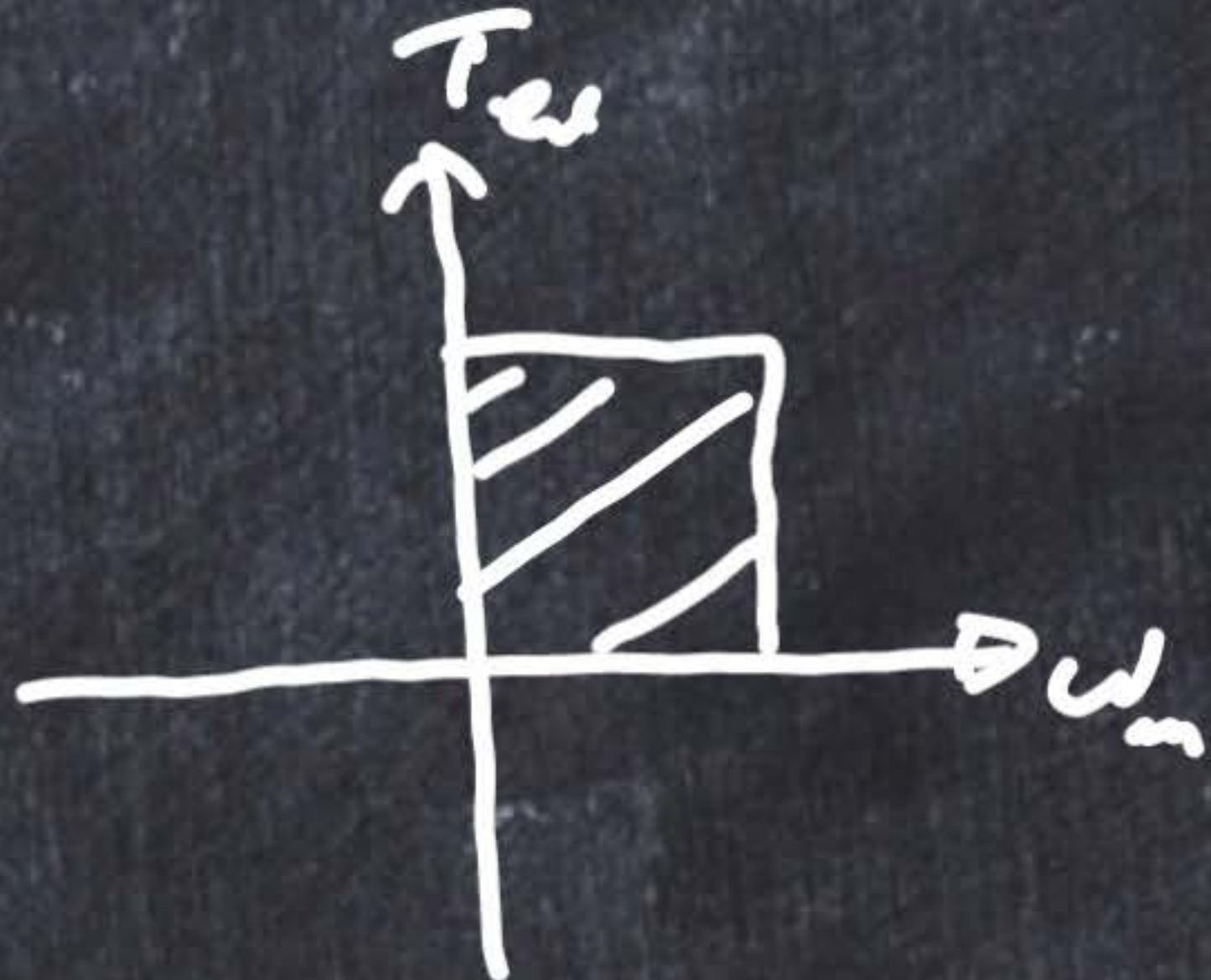


Full

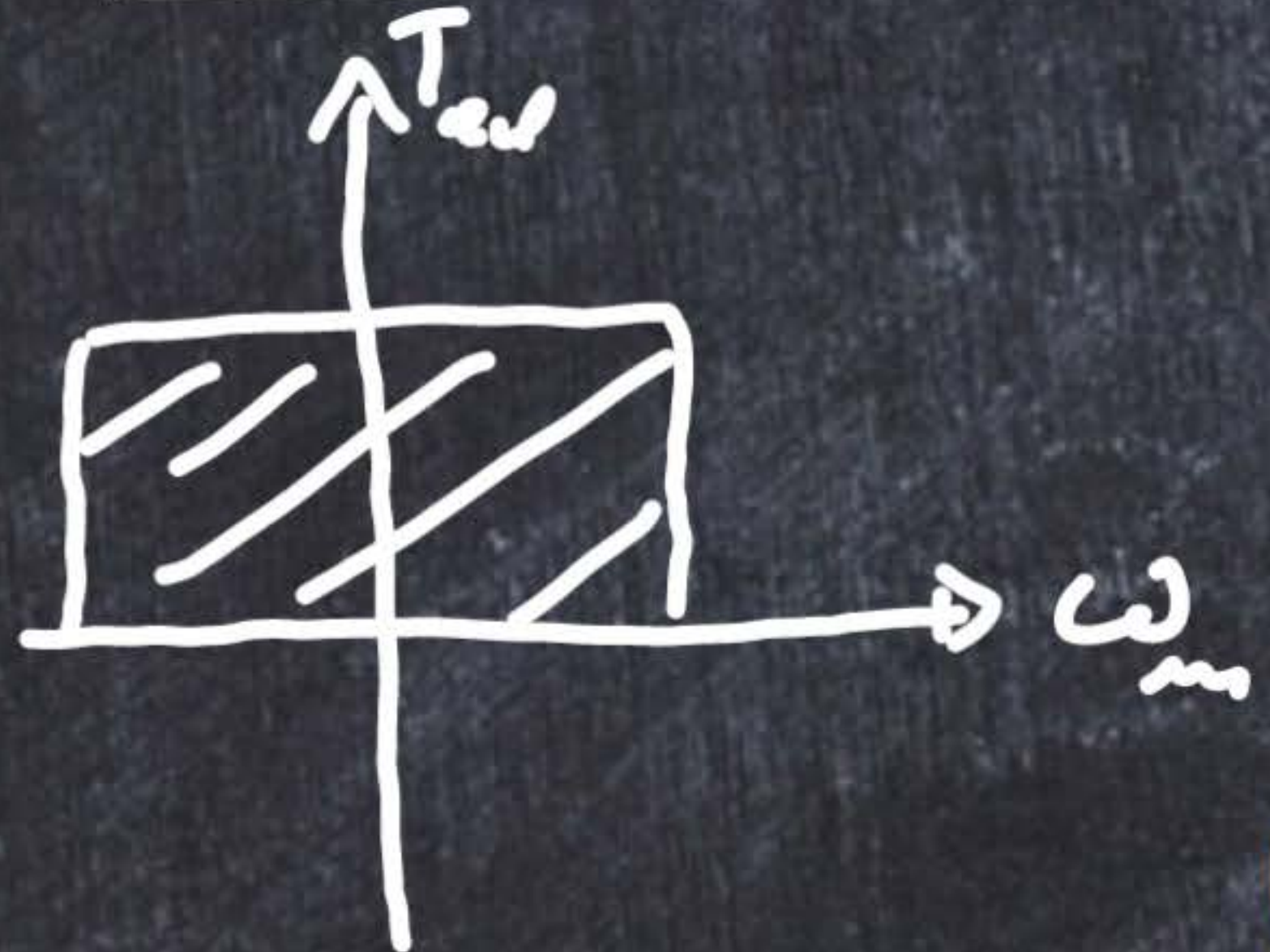


Half

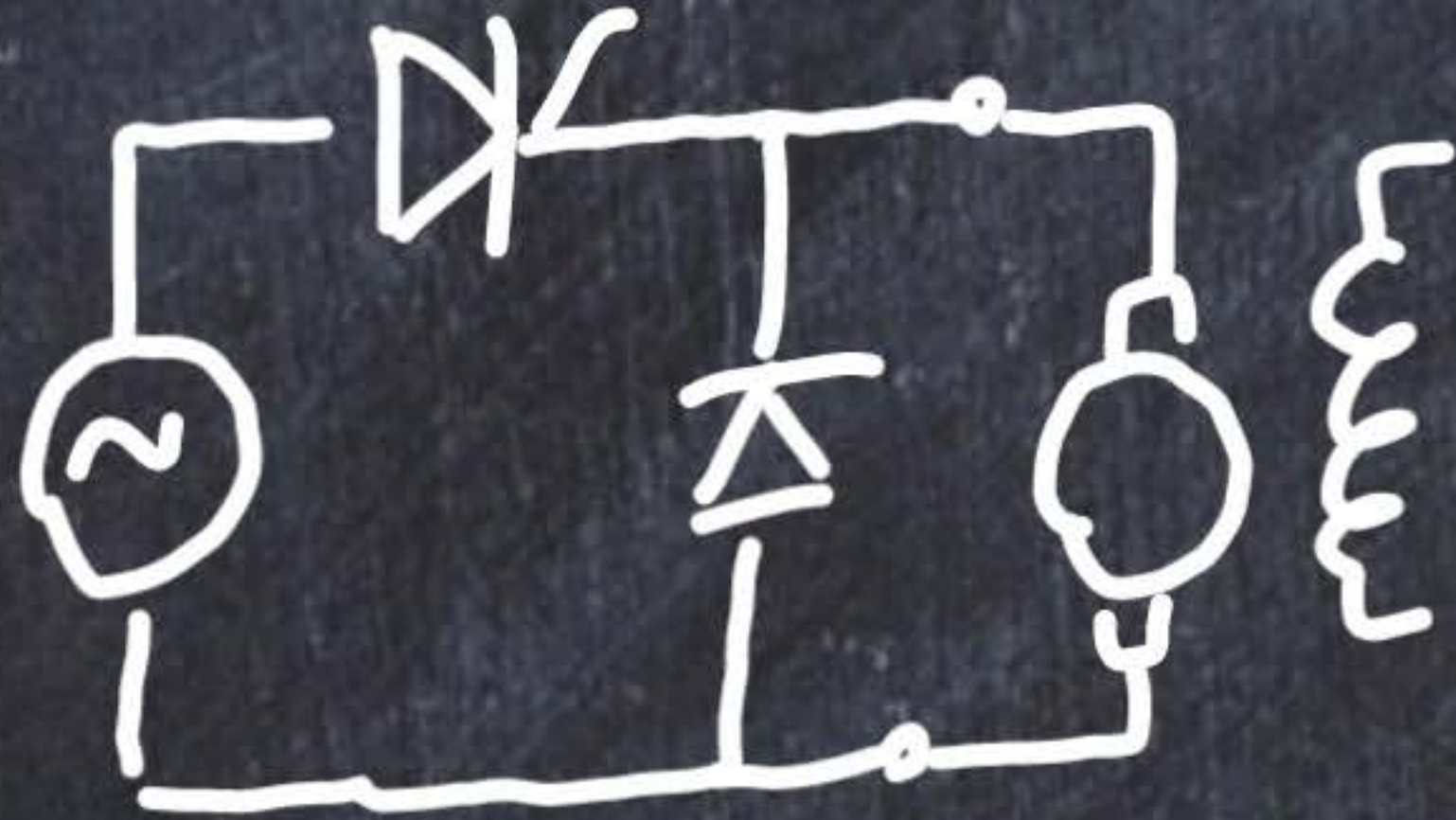

Semi

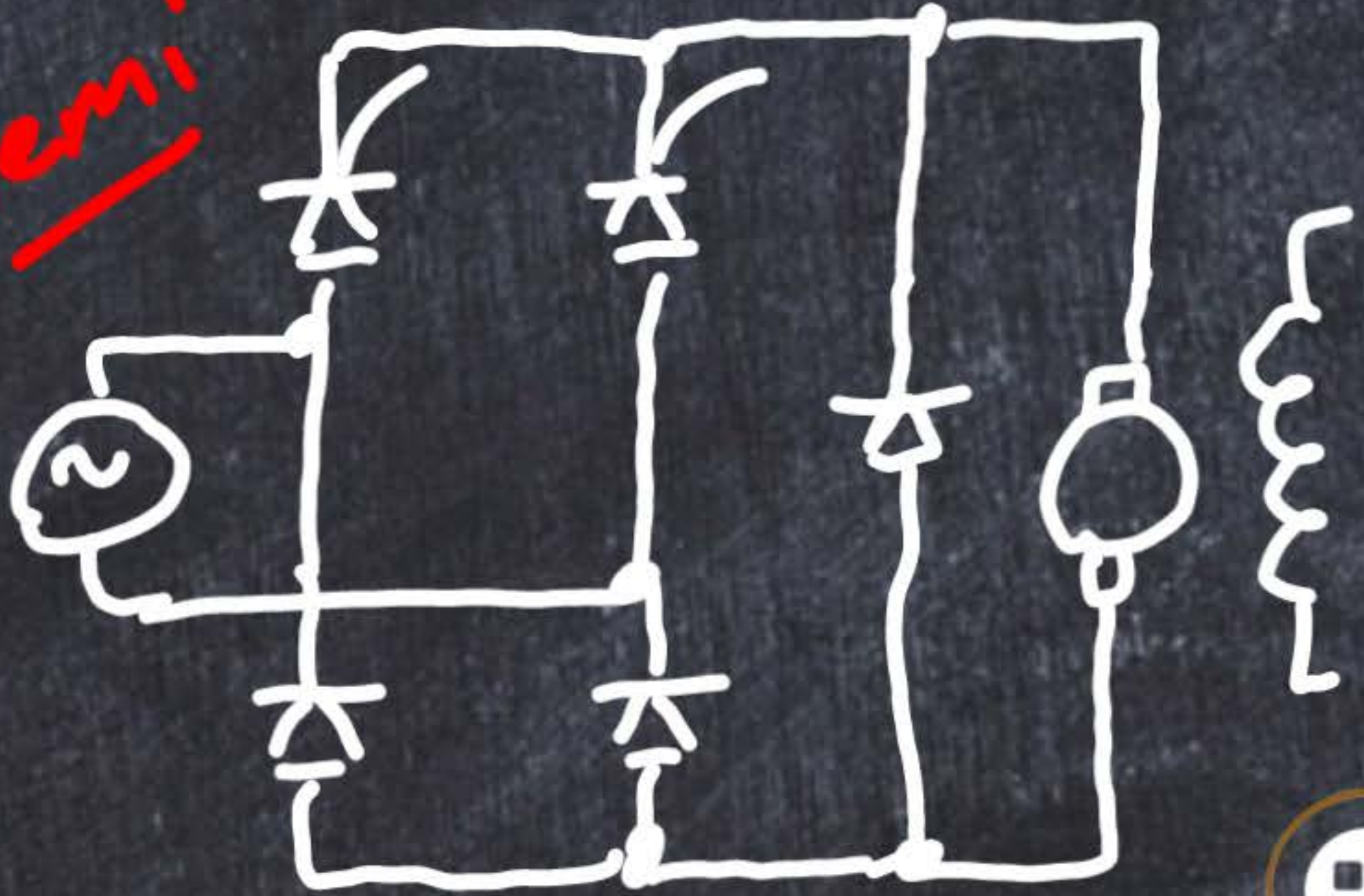

Full

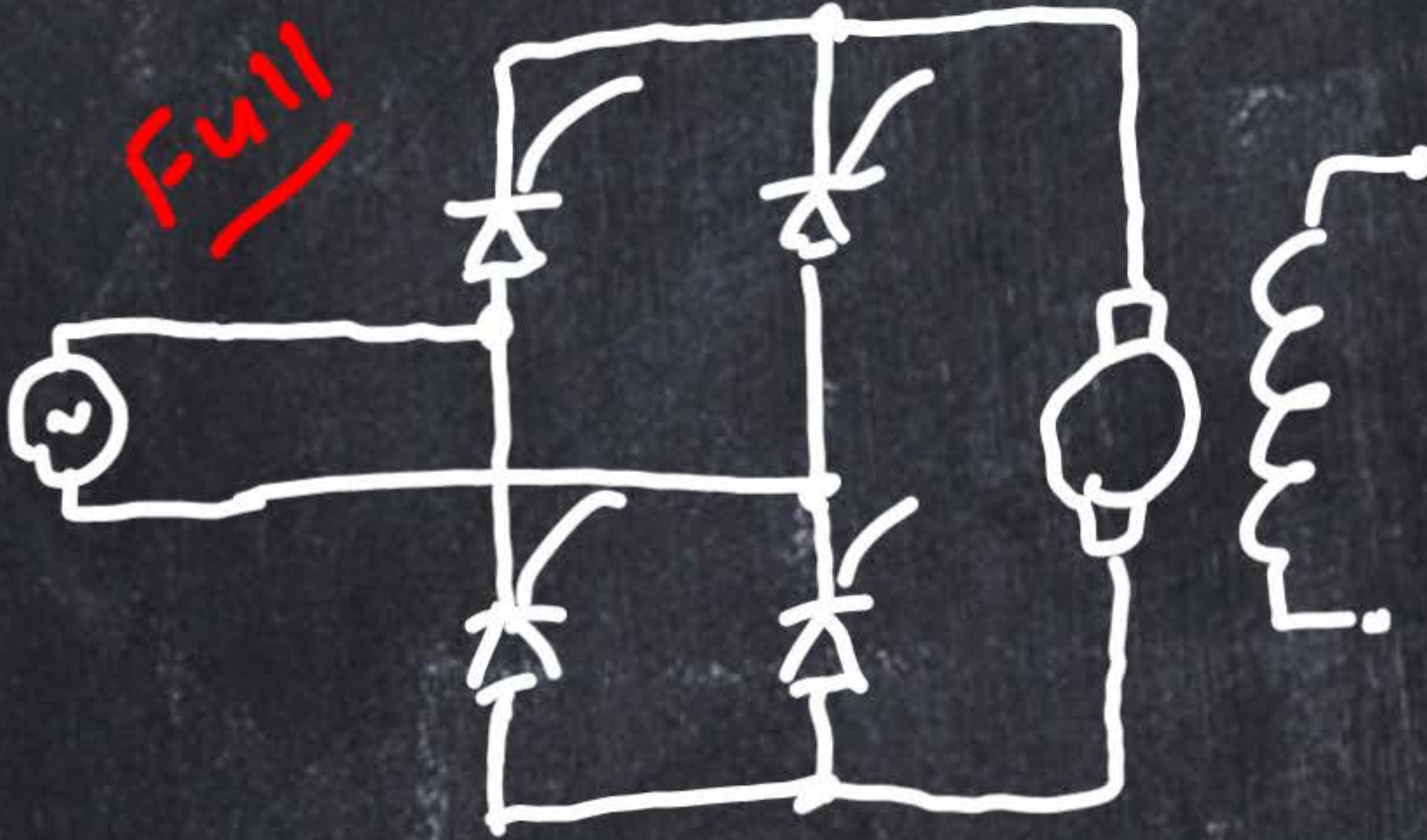

## ② Three-phase controlled rectifiers

2.1) Half wave

2.2) semi converter


2.3) Full wave

2.4) Dual converter





## 2.1) Half wave

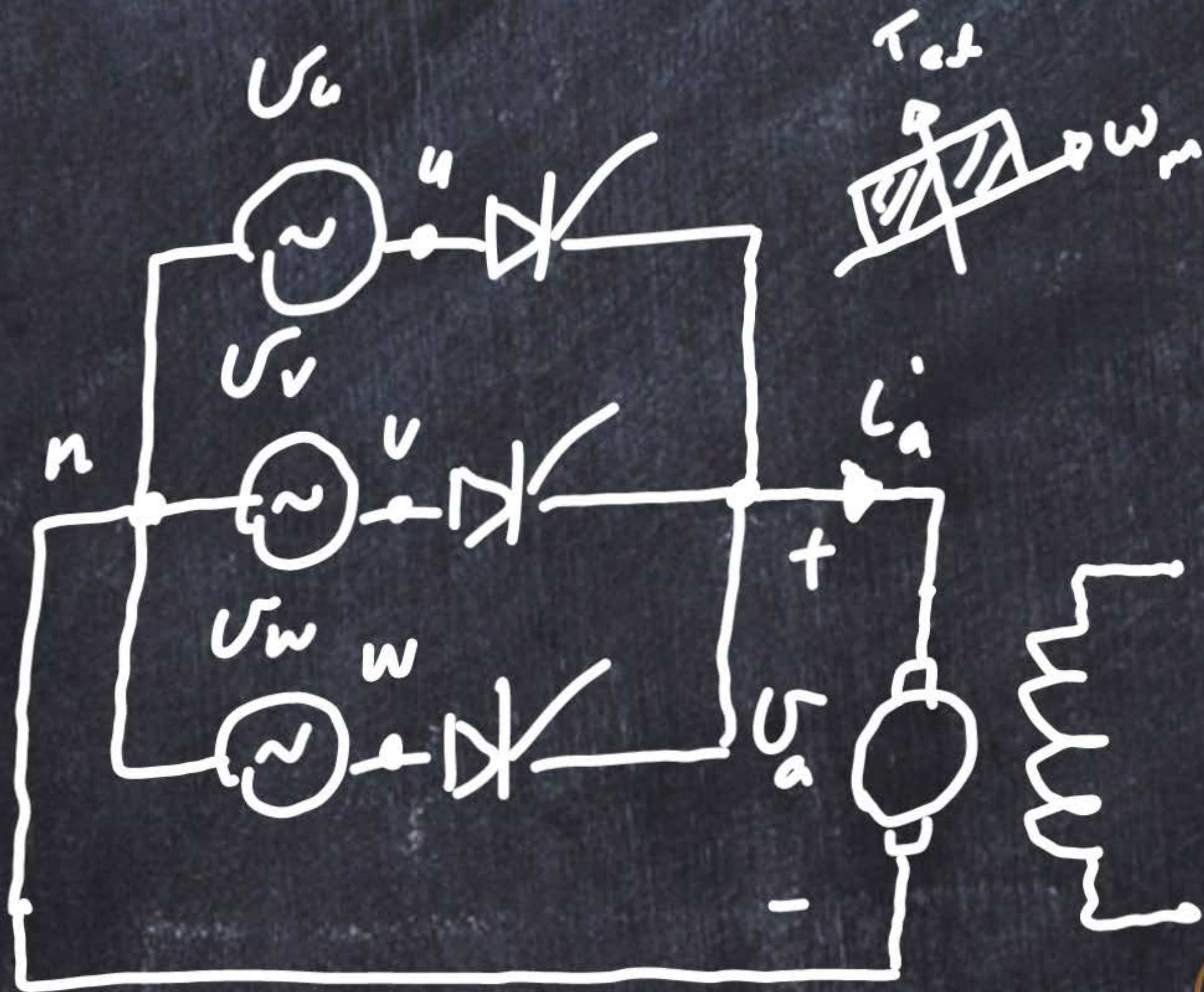

$$\begin{aligned} U_u &= V_m \sin(\omega t) \\ U_v &= V_m \sin(\omega t - \frac{2\pi}{3}) \\ U_w &= V_m \sin(\omega t + \frac{2\pi}{3}) \end{aligned}$$

phase voltages



$$V_a = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin(\omega t) d(\omega t)$$

$$= -\frac{3V_m}{2\pi} \cos(\omega t) \Big|_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha}$$

$$= \frac{3V_m}{2\pi} \left[ \cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\frac{5\pi}{6} + \alpha\right) \right]$$



$$V_a = \frac{3V_m}{2\pi} \left[ \left( \cos \frac{\pi}{6} \cos \alpha - \sin \frac{\pi}{6} \sin \alpha \right) - \left( \cos \frac{5\pi}{6} \cos \alpha - \sin \frac{5\pi}{6} \sin \alpha \right) \right]$$

$$V_a = \frac{3V_m}{2\pi} \left[ \left( \frac{\sqrt{3}}{2} \cos \alpha - \frac{1}{2} \sin \alpha \right) - \left( -\frac{\sqrt{3}}{2} \cos \alpha - \frac{1}{2} \sin \alpha \right) \right]$$

$$V_a = \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

$$-\frac{3\sqrt{3}V_m}{2\pi} \leq V_a \leq \frac{3\sqrt{3}V_m}{2\pi}$$



$$V_a = \frac{3}{2\pi} \left[ \int_{\frac{\pi}{6} + \alpha}^{\pi/2} V_{uv} d\omega t + \int_{\frac{\pi}{2}}^{\frac{5\pi}{6} + \alpha} V_{uw} d\omega t \right] \left| \begin{array}{l} V_{uv} \\ V_{vw} \\ V_{wu} \end{array} \right.$$


$$V_{uv} = \sqrt{3} V_m \sin(\omega t + 30^\circ)$$

$$V_{uw} = -\sqrt{3} V_m \sin(\omega t + 30^\circ + 120^\circ)$$



$$V_a = \frac{3\sqrt{3} V_m}{2\pi} (1 + \cos\alpha)$$



# 2.3) Full-wave

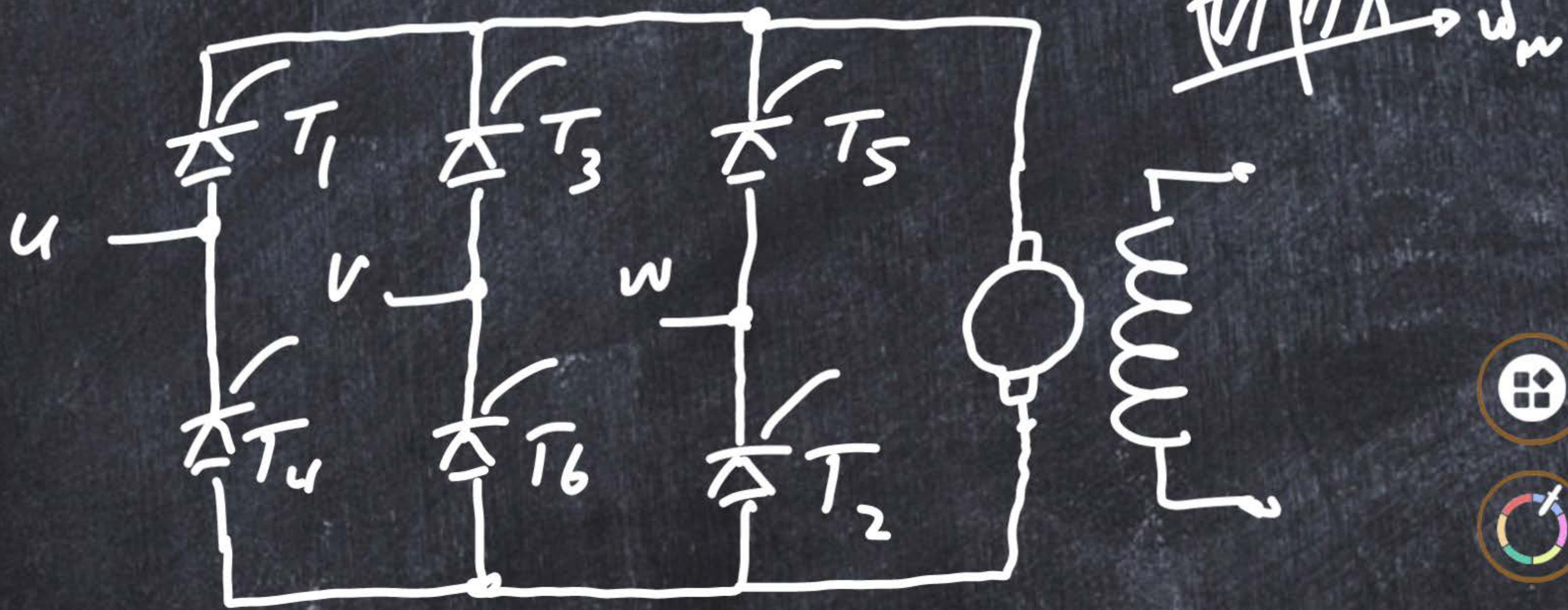

# 2.2) Semi-converter

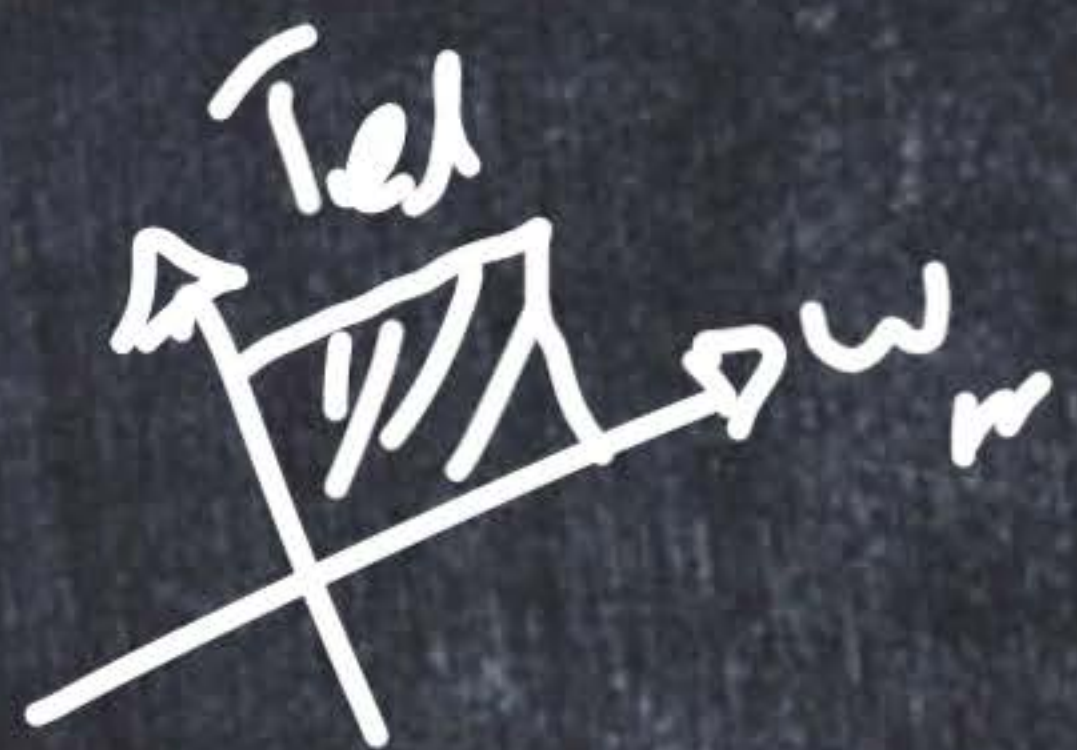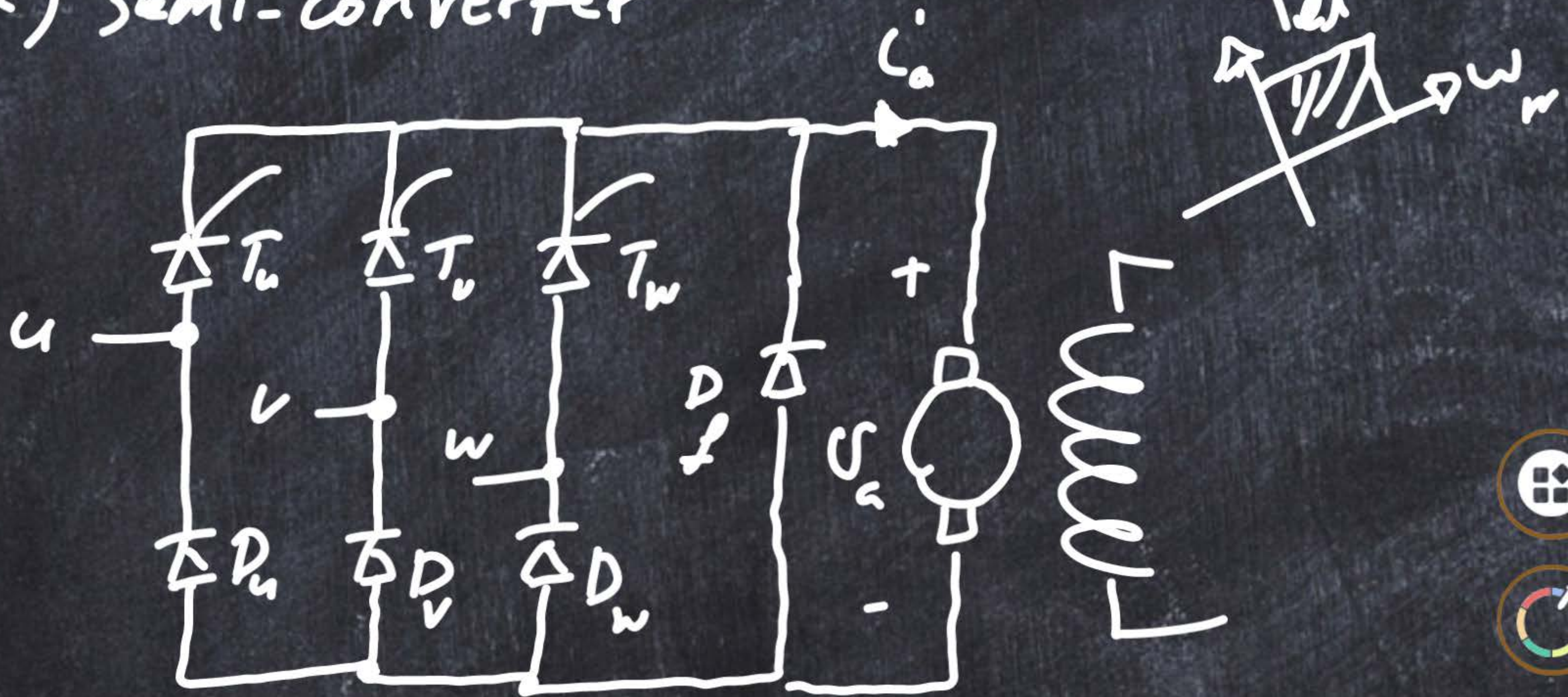

$$V_a = \frac{6}{2\pi} \int_{\frac{\pi}{2} + \alpha}^{\frac{3\pi}{2} + \alpha} U_{uv} d\omega t \quad ; \quad U_{uv} = \sqrt{3} V_m \sin(\omega t + 30^\circ)$$

$$V_a = \frac{3\sqrt{3} V_m}{\pi} \cos \alpha$$



1- $\phi$

Circuit	$V_a$
Half	$\frac{V_m}{2\pi} (1 + \cos \alpha)$
Semi	$\frac{V_m}{\pi} (1 + \cos \alpha)$
Full	$\frac{2V_m}{\pi} \cos \alpha$






3- $\phi$


Circuit	$V_a$
Half	$\frac{3\sqrt{3} V_m}{2\pi} \cos \alpha$
Semi	$\frac{3\sqrt{3} V_m}{2\pi} (1 + \cos \alpha)$
Full	$\frac{3\sqrt{3} V_m}{\pi} \cos \alpha$



# Control system "Armature circuit"

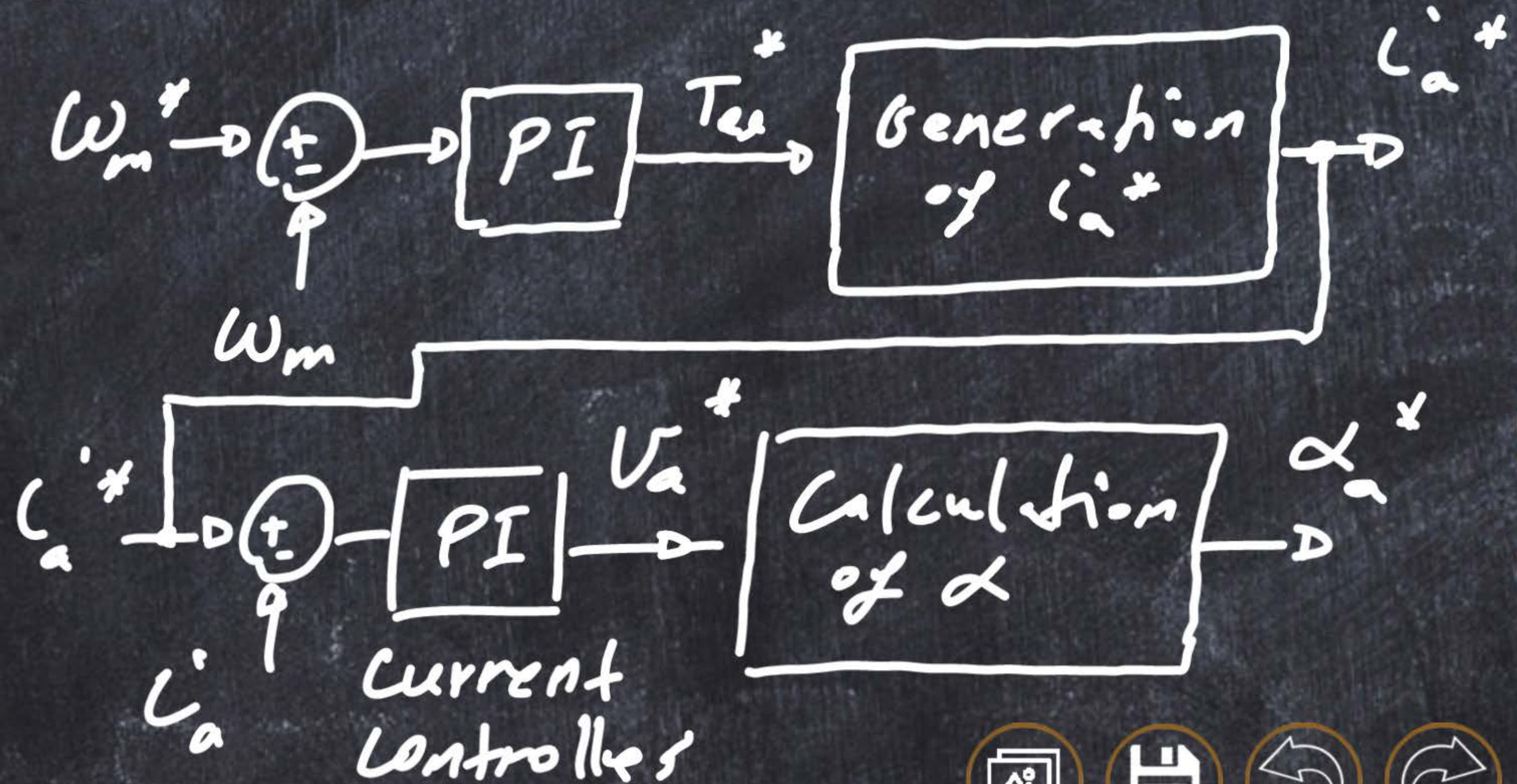


# Control System "Field Circuit"

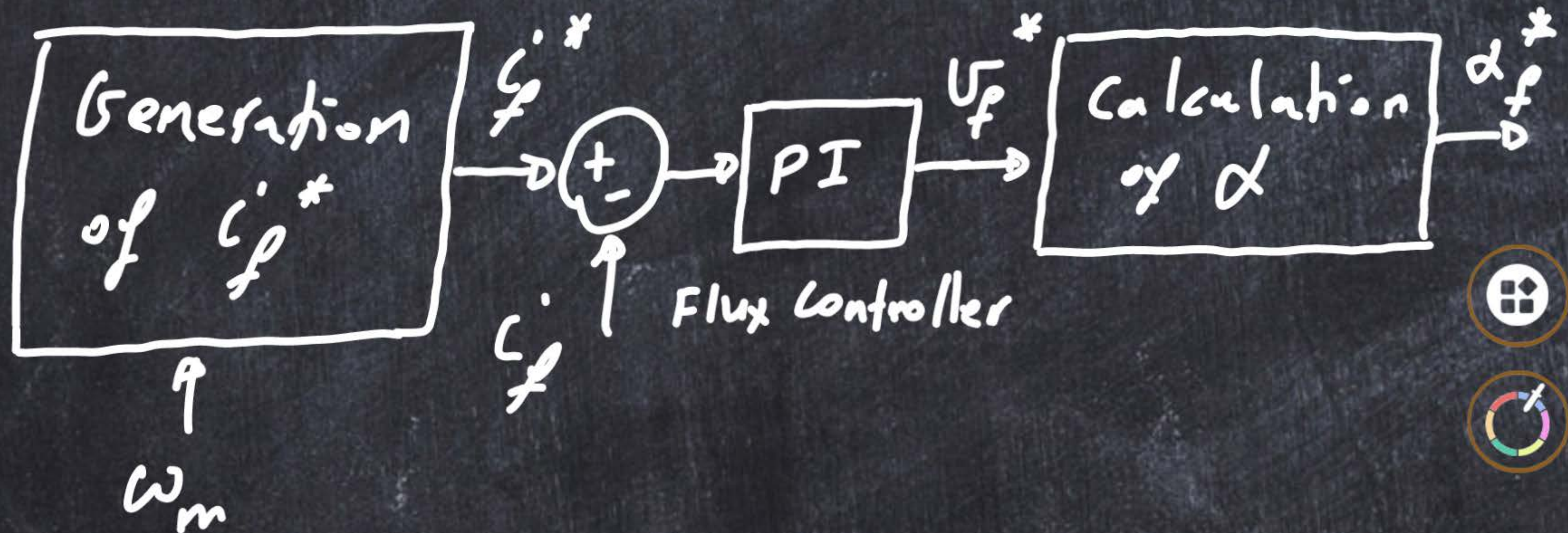

# Dual Converter

- The controlled rectifier is voltage reversible, but not current reversible.
- To obtain 4-quadrant operation, it is necessary to have two converters operating back-to-back or in anti-parallel.
- The converter can be controlled in 2 ways:
  - circulating current method
  - Non-circulating current method

# Circulating current scheme

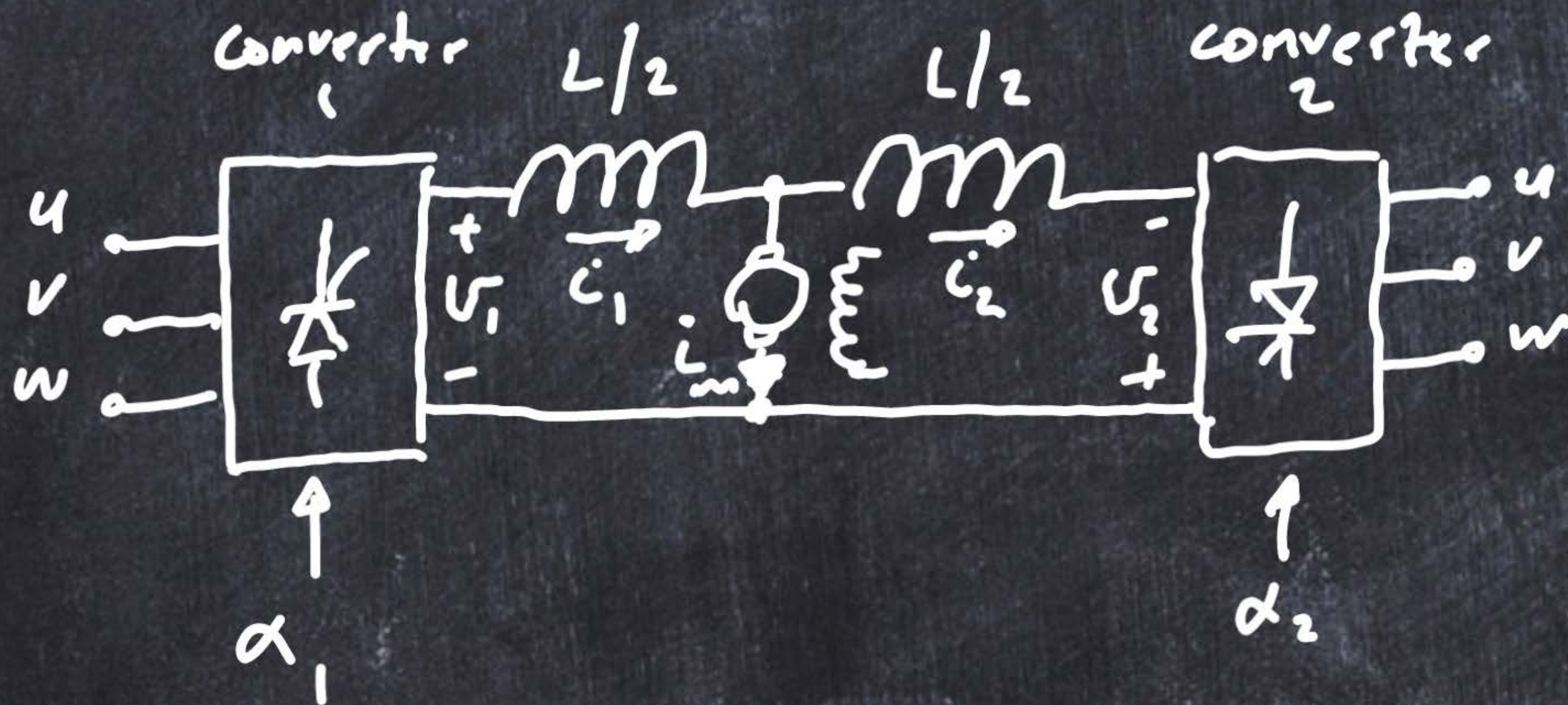

- The converters are controlled to produce the same DC voltage across the motor terminals:

$$-v_1 + \frac{L}{2} \frac{di_1'}{dt} + \frac{L}{2} \frac{di_2'}{dt} - v_2 = 0$$

$$-V_1 - V_2 = 0 \quad V_1 = \frac{1}{T} \int_0^T v_1 dt, \quad V_2 = \frac{1}{T} \int_0^T v_2 dt$$

$$V_1 + V_2 = 0$$



$$\cos \alpha_1 + \cos \alpha_2 = 0$$

$$\cos \alpha_1 = -\cos \alpha_2 = \cos(\pi - \alpha_2)$$

$$\Rightarrow \alpha_1 = \pi - \alpha_2$$

or

$$\boxed{\alpha_1 + \alpha_2 = \pi}$$



$$L'_{cir} = L'_{cir, DC} + L'_{cir, AC}$$

$$L'_{cir, DC} = 0 \quad \text{since} \quad V_1 = V_2$$

$$L'_{cir, AC} \neq 0 \quad \text{since} \quad U_1 \neq U_2$$

Note:  $L'_{cir}$  flows only in one direction.





-  $i_{cir, AC}$  is limited by using buffer inductor,  $L$ .

- KVL in the loop:  $V_1 + V_2 = \frac{L}{2} \frac{di_1}{dt} + \frac{L}{2} \frac{di_2}{dt}$

$$i_1 = i_m + i_{cir, AC}$$

$$i_2 = i_{cir, AC}$$

$$i_1 = i_{cir, AC}$$

$$i_2 = i_m + i_{cir, AC}$$



$$V_1 + V_2 = L \frac{di_{cir, AC}}{dt} \Rightarrow L i_{cir, AC} = \frac{1}{L} \int (V_1 + V_2) dt$$

$i_{cir, AC}$

Discontinuous



$$0 \leq \alpha_1 \leq \frac{\pi}{3}$$

$i_{cir, AC}$

Continuous



$$\frac{\pi}{3} \leq \alpha_1 \leq \frac{2\pi}{3}$$

3- $\phi$  half-wave



→ In order for the combination to respond rapidly to control signals, it is necessary for SCR<sub>1</sub> to be in continuous conduction.

This can be achieved by making  $\alpha_1 + \alpha_2$  is very slightly less than  $\pi$ , which effectively creates  $C_{cir,DC}$  component, causing  $C_{cir}$  to be all the time continuous.




The main disadvantage of this scheme is the use of inductors, which are larger and more expensive.





# Non-circulating current scheme

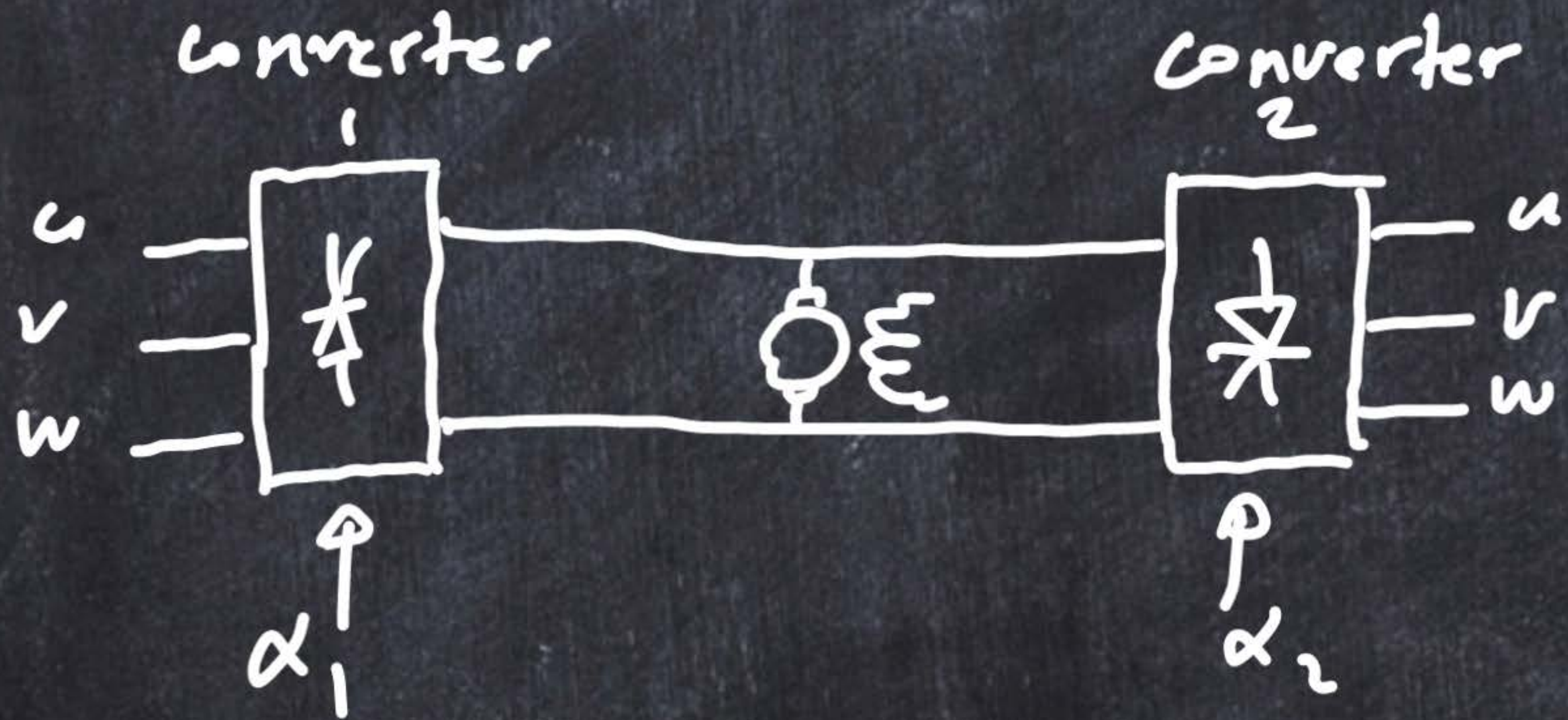---



→ In this scheme, only one converter receives firing pulses at a time.

$T_{er}$	$C_m$	$C_1 =$	$C_2 =$	Converter 1	Converter 2
	+	$C_m$	0	ON	OFF
	-	0	$C_m$	OFF	ON

