

Relay + Programmable Logic Controllers

1) RLC


2) PLC

① RLC


- prior to the widespread use of PLCs in process control and automation, hardwired relay control systems were used.
- Control of motors such as starting, stopping, reversing the direction, sequence starting, etc can be achieved by designing suitable control circuits using relays, contactors, push buttons, etc

Relay :- It is an electromagnet switch that has a coil and a set of associate contacts.

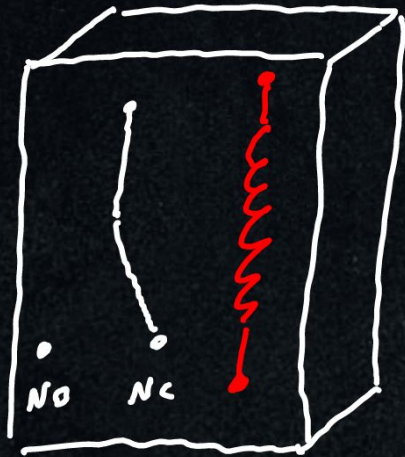→ Contacts can be either normally open or normally closed. "Auxiliary contacts"



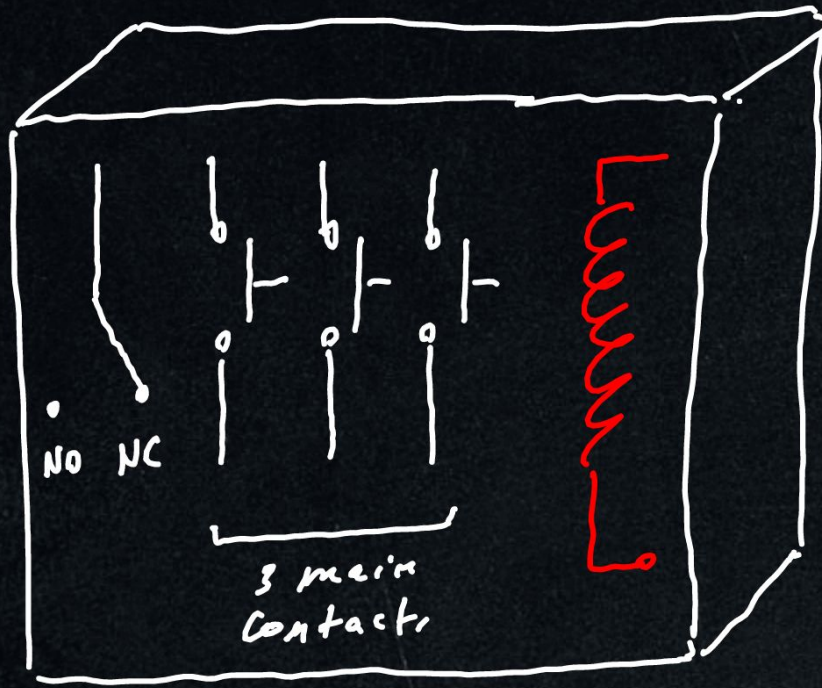Contactor :- It is an electromagnet switch that has a coil and 3 main contacts with a few auxiliary contacts.




- Relay symbols
- Relay coil
 - ||- Normally open
 - ∩- Normally closed


Line Diagram

Example,


1) start / stop DC motor

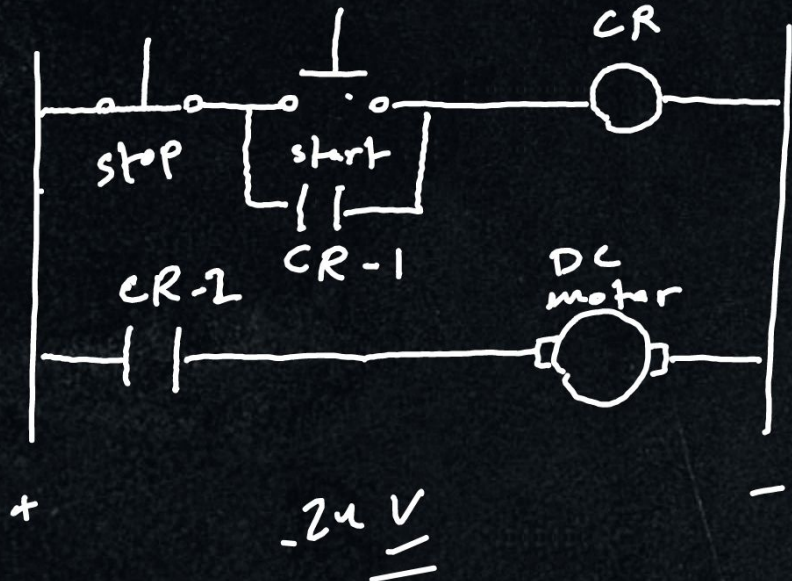


2) Relay controlling two pilot lights

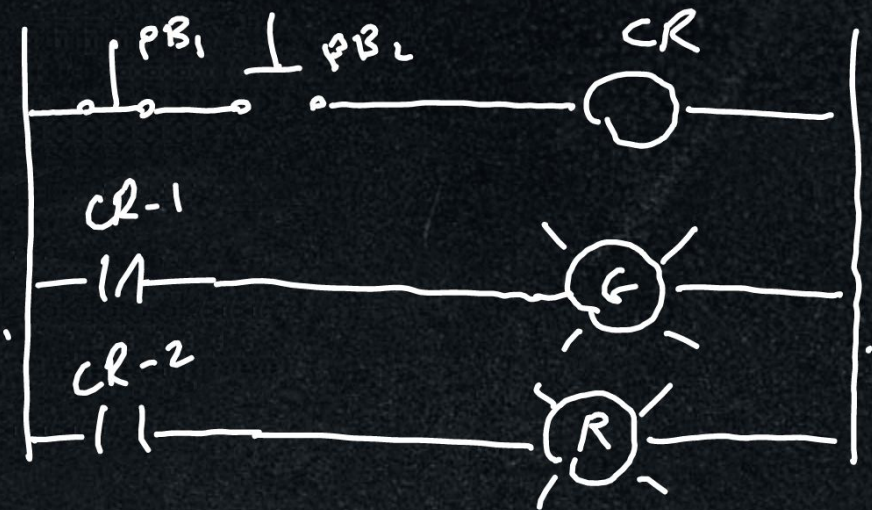

3) AND logic $y = AB$

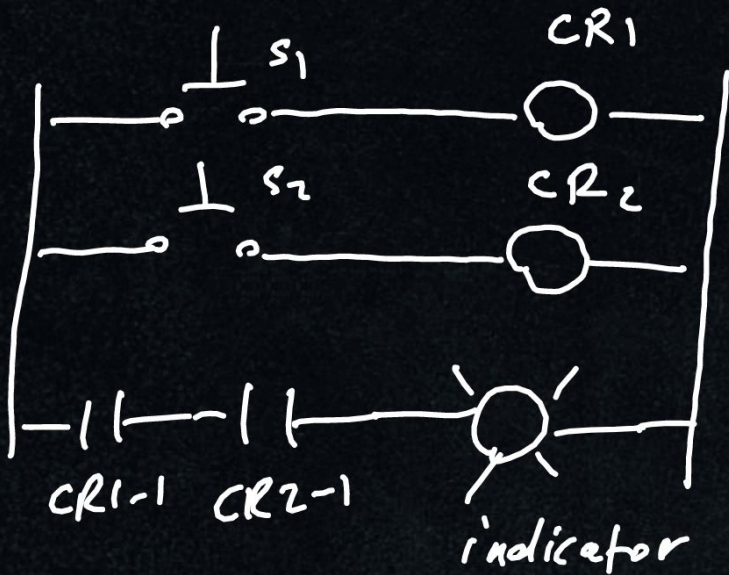


4) OR logic $y = A+B$

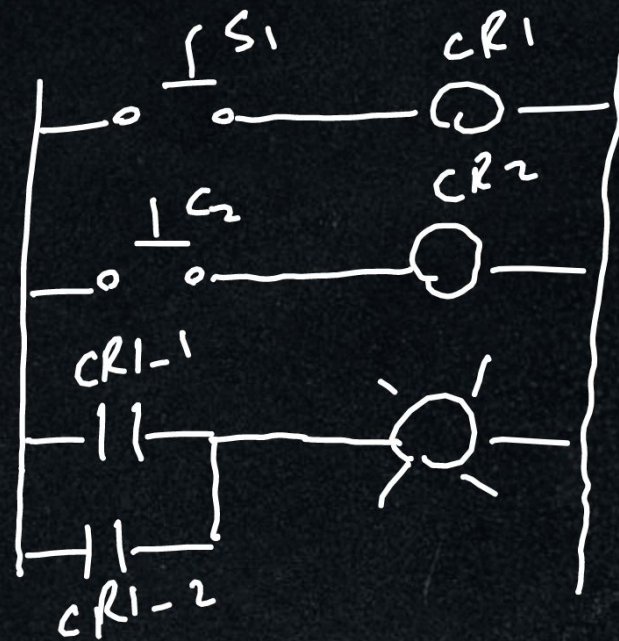


5) XOR $y = AB' + A'B$

5)

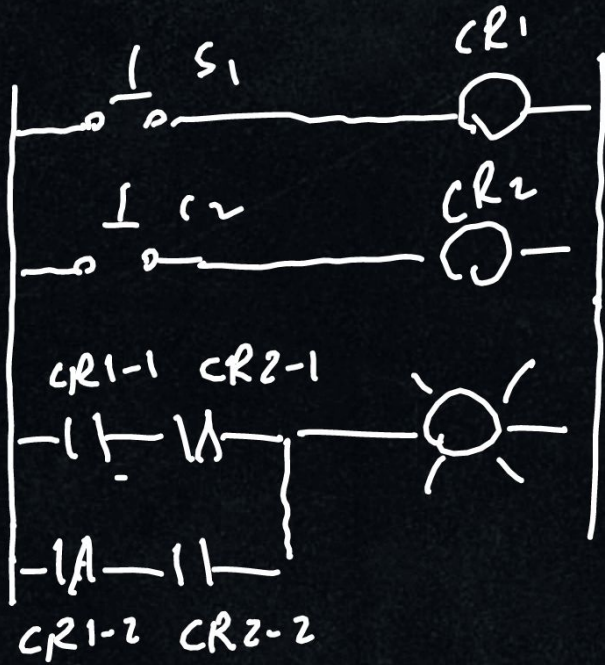


$$y = \underbrace{A B^{\prime}}_{\text{AND}} + \underbrace{A^{\prime} B}_{\text{AND}} \\ \text{OR}$$

6) Start/stop of 3- ϕ Motor


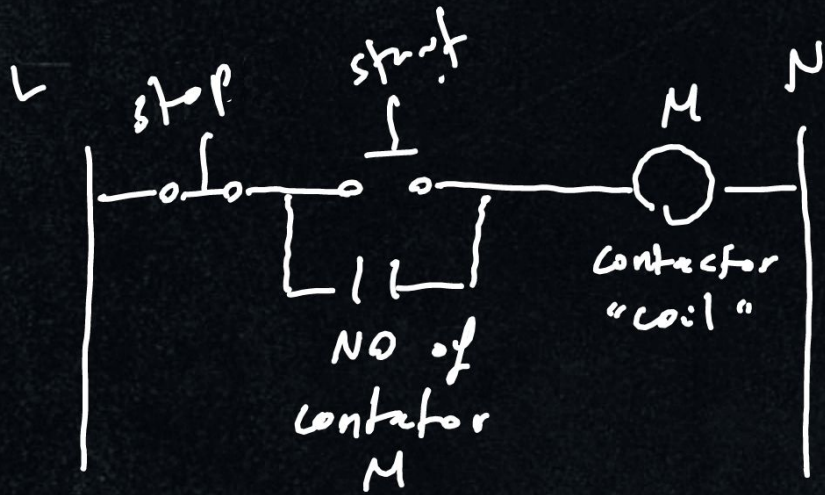


Control Circuit

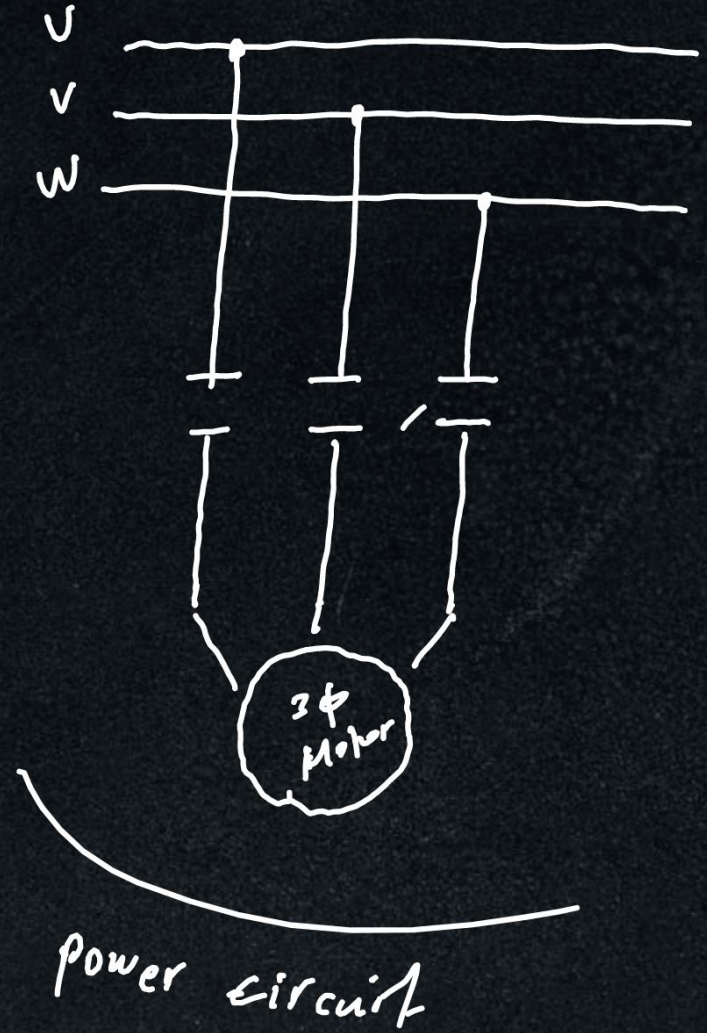


power circuit

7) Reversing the direction of 3 ϕ motor

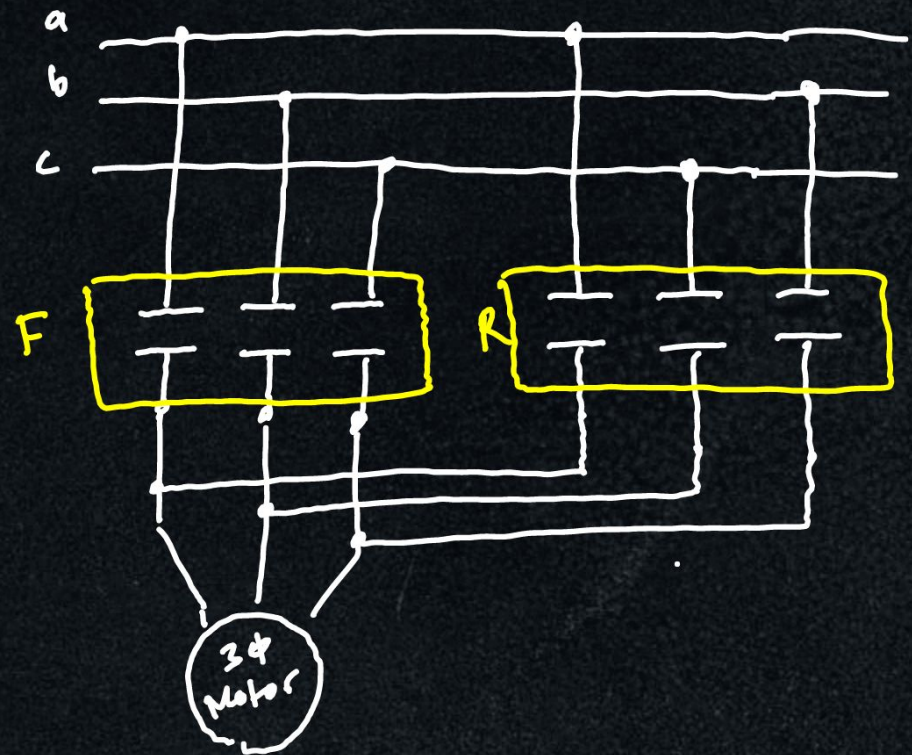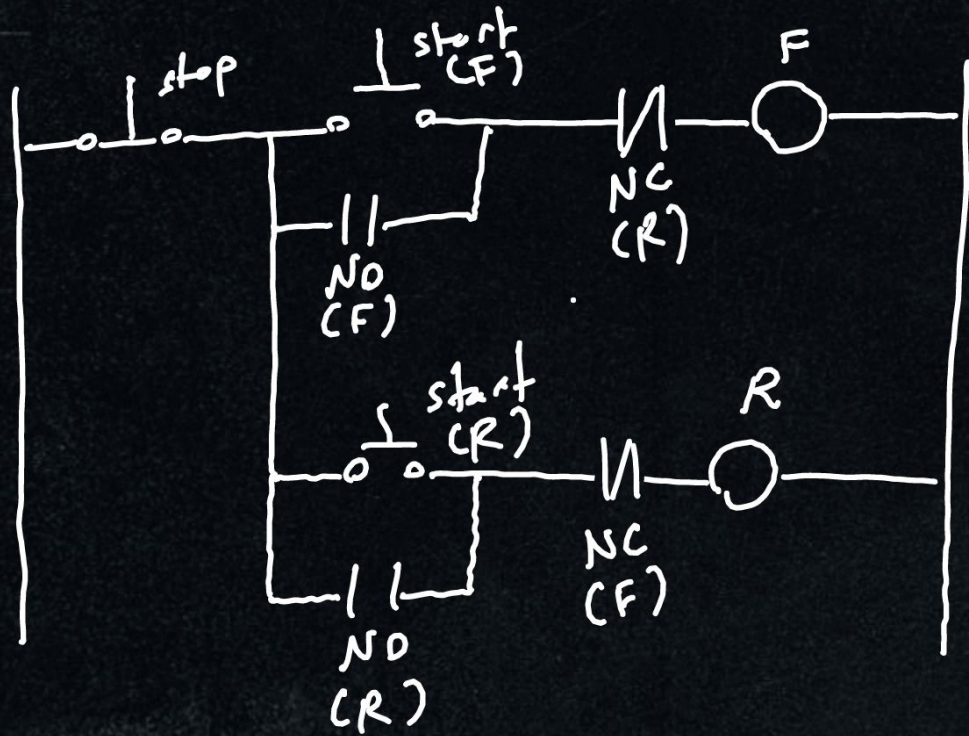

② PLC

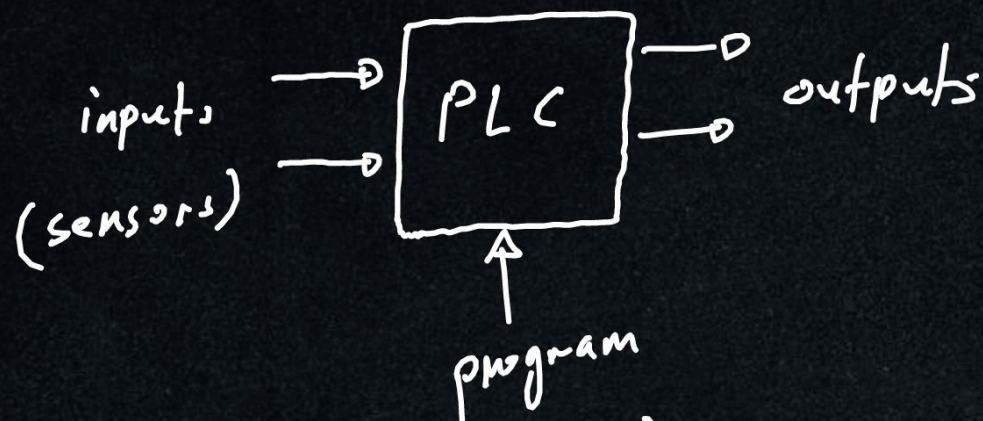
• It is a special form of microprocessor-based controller that uses memory to store instructions.



Advantages (Compared to RLC)

- 1) Can easily implemented changes "implemented in software"
- 2) More reliable
- 3) More compact
- 4) require less maintenance
- 5) can operate faster

Block Diagram

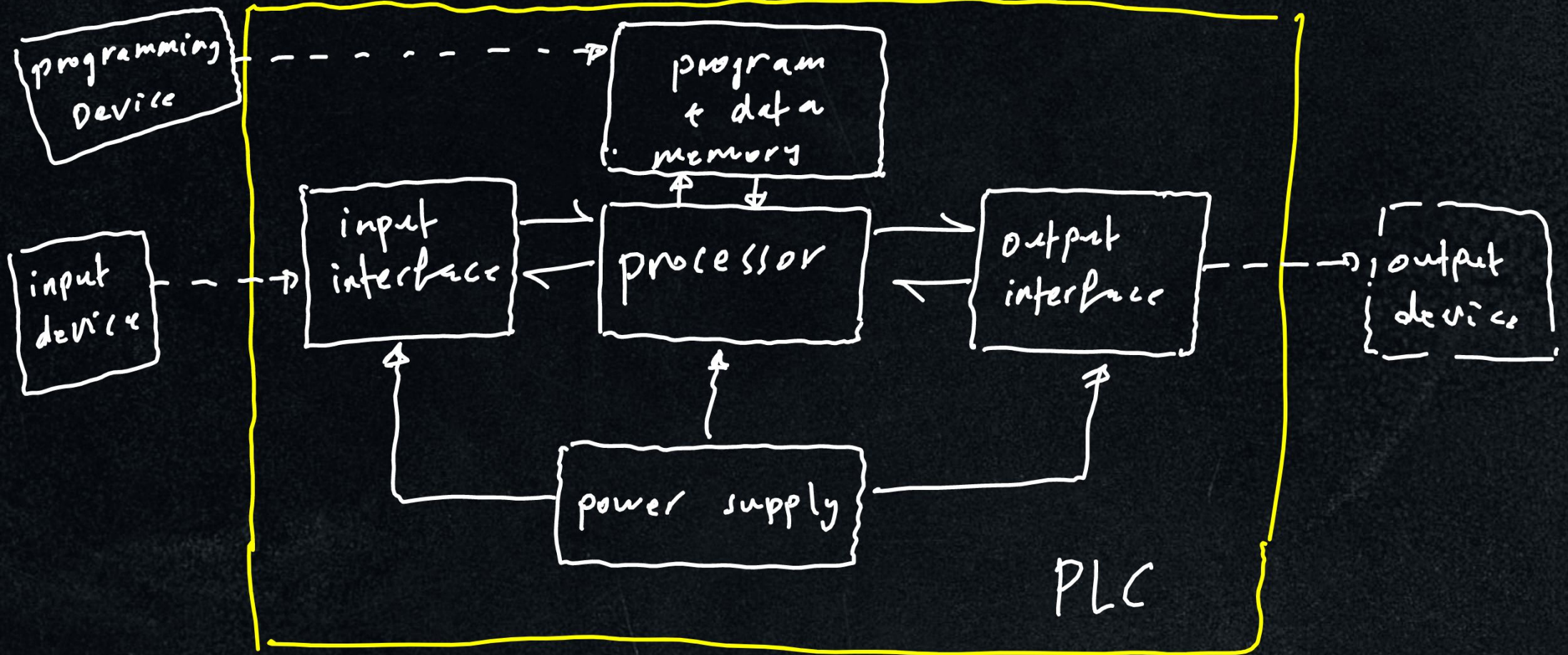

PLCs :-

- * Mitsubishi
- * Siemens
- * Toshiba
- * Allen-Bradley
- * Schneider

Programming Languages

- Ladder diagrams (LAD)
- Instruction lists (IL)
- Function block diagram (FBD)
- structured text (ST)
- Sequential function charts (SFC)

I/O Addresses

- The PLC has to be able to identify each input and output. It does this by allocating addresses to each input + output.
- This is likely to be just a number prefixed by a letter to indicate whether it is an input or output.
- Mitsubishi



24 inputs X400 - X427 in octal format

X400, X401, X402, X403, X404, X405, X406, X407, X410,

16 outputs Y430 - Y447

• Siemens

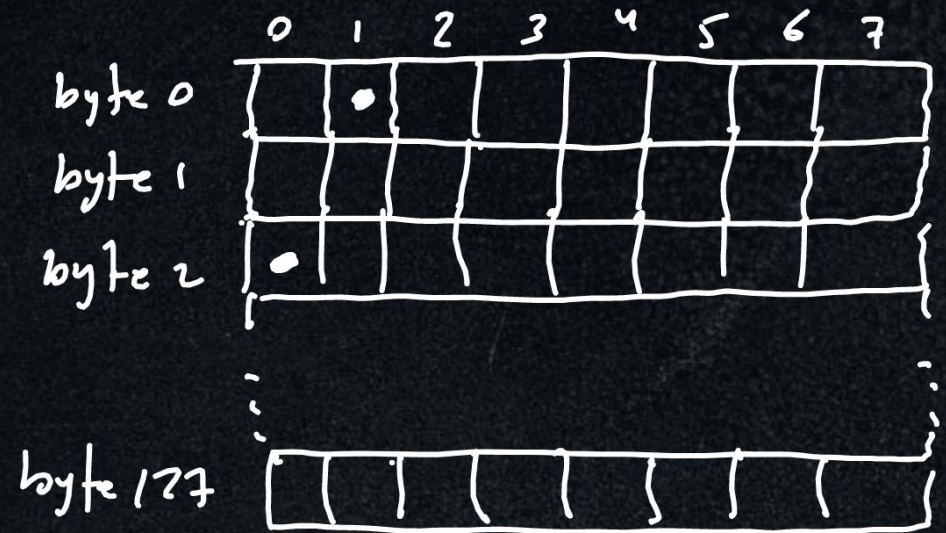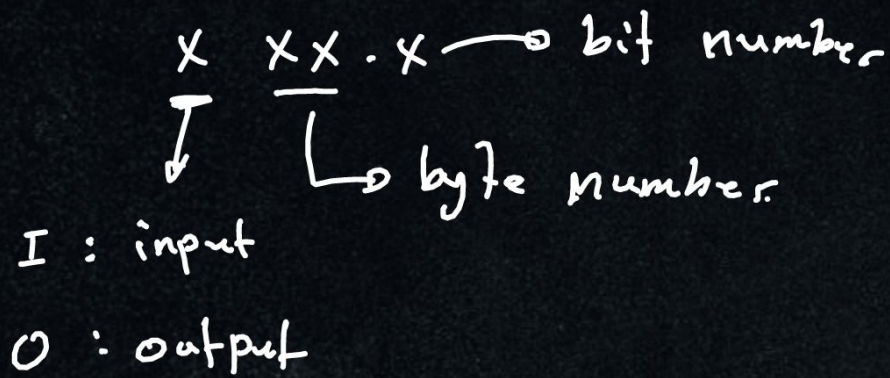The digital I/O is arranged into groups of 8 bits, called a byte. A signal is identified by its bit number (0-7) and its byte number (0-127)




EX :-

I 0.1 input at bit 1 in byte 0

O 2.0 output at bit 0 in byte 2

Logic Functions (LAD)

1) AND $O = AB$


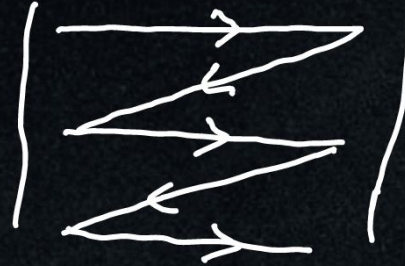


<u>A</u>	<u>B</u>	<u>O</u>
0	0	0
0	1	0
1	0	0
1	1	1






Mitsubishi

Siemens

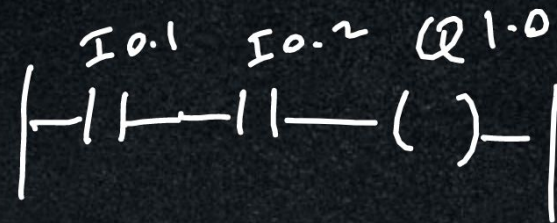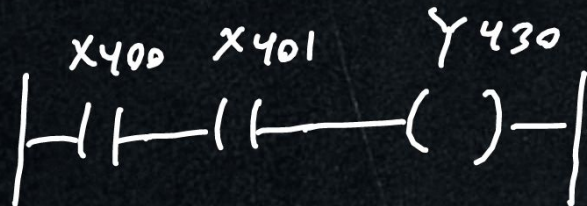



2) OR $O = A + B$

A	B	O
0	0	0
0	1	1
1	0	1
1	1	1

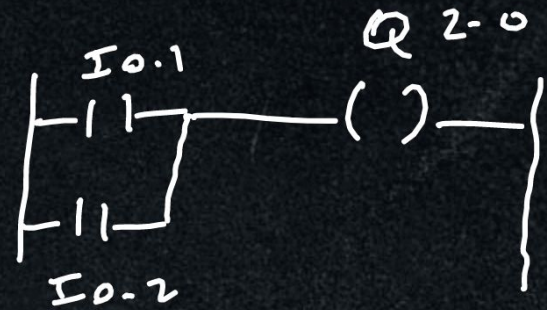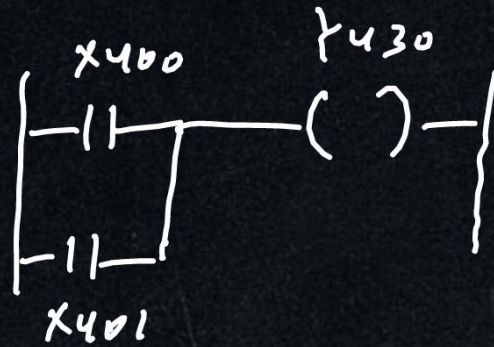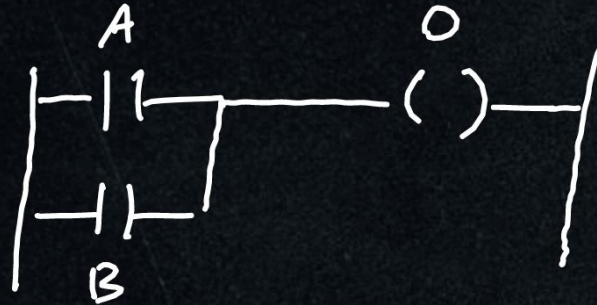


3) NOT $Q = A'$

<u>A</u>	<u>Q</u>
0	1
1	0

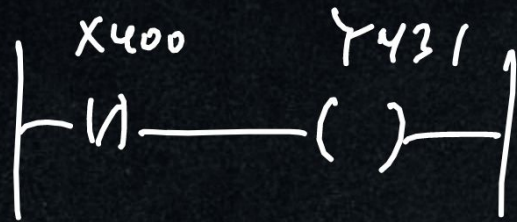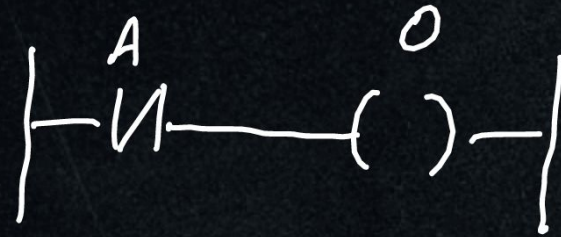


4) NAND $O = (AB)' = A' + B'$

<u>A</u>	<u>B</u>	<u>O</u>
0	0	1
0	1	1
1	0	1
1	1	0

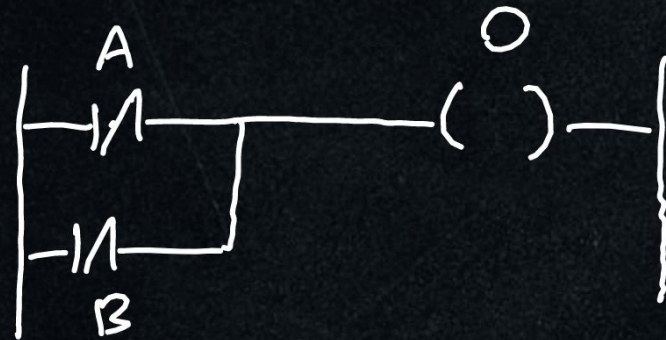




5) NOR $O = (A+B)' = A'B'$

<u>A</u>	<u>B</u>	<u>O</u>
0	0	1
0	1	0
1	0	0
1	1	0

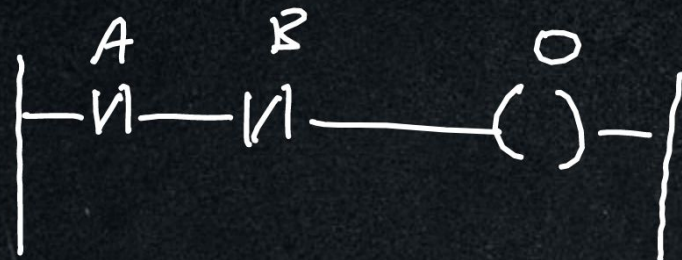

6) XOR $O = AB' + A'B$



A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

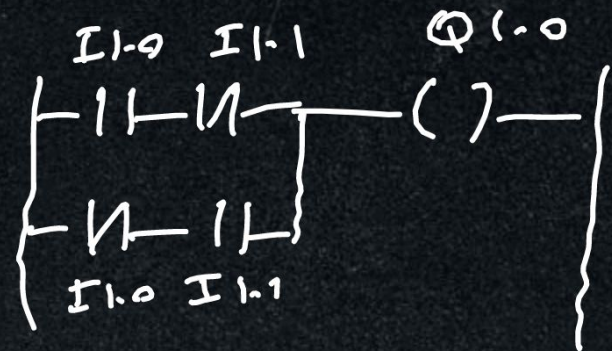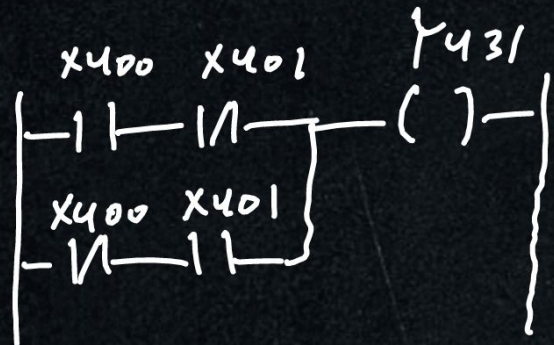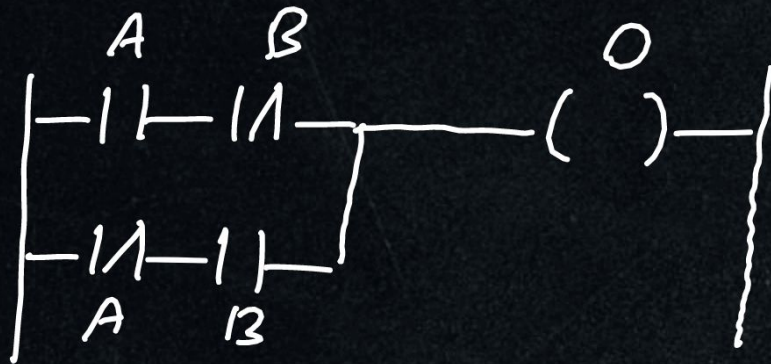

Logic Functions (FBD)

Functions	FBD
AND	
OR	
NOT	
NAND	
NOR	
XOR	

EX :-

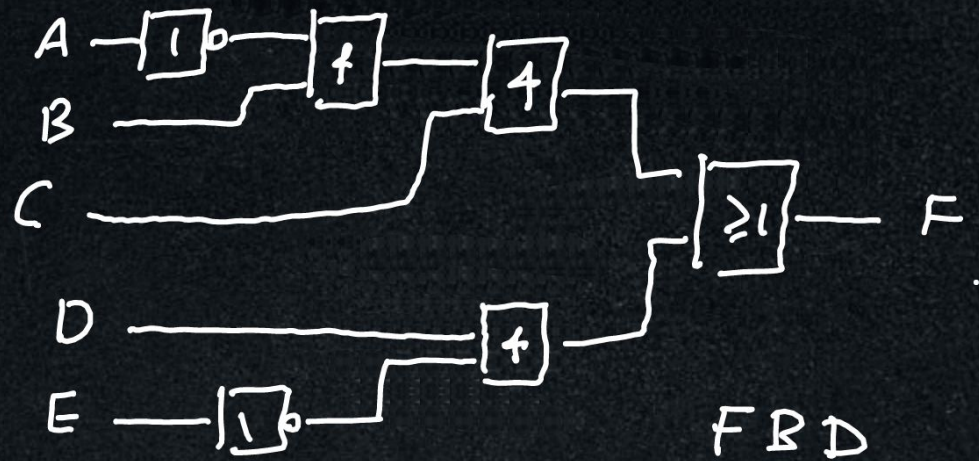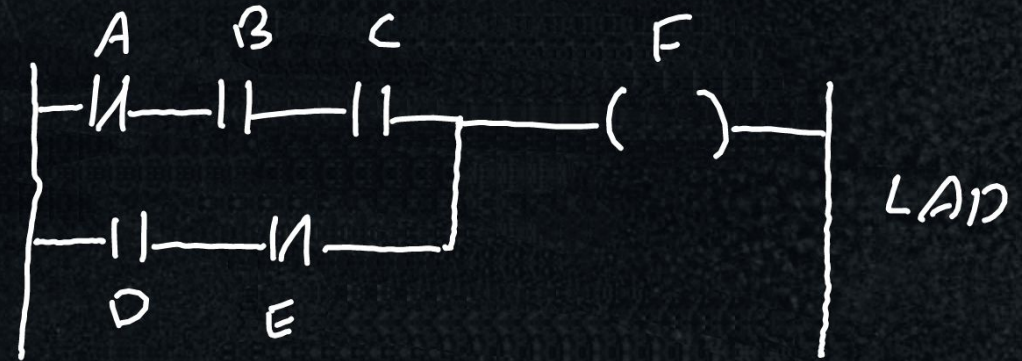

$$F = A'BC + DE'$$

IL programming



Mitsubishi

Siemens

LD	A	start a rung with open contacts
LDI	AN	" " " " closed "
AND	A	series element with open contacts
ANI	AN	" " " " closed "
OR	O	parallel " " open "
ORI	ON	" " " " closed "
OUT	=	An output .

Logic Function, (IL)

1) OR

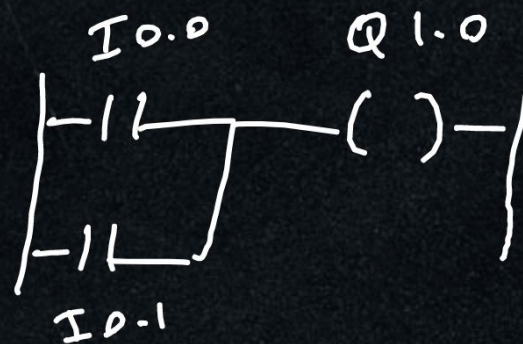
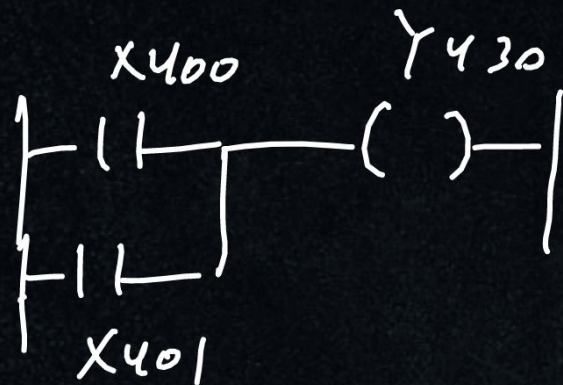


```
LD X400  
OR X401  
OUT Y430
```

```
A I0.0  
Q I0.1  
= Q1.0
```

Logic Function, (IL)


1) OR

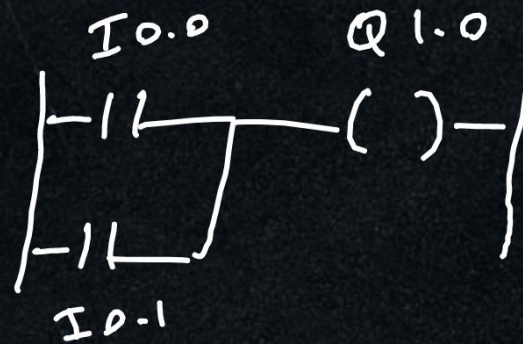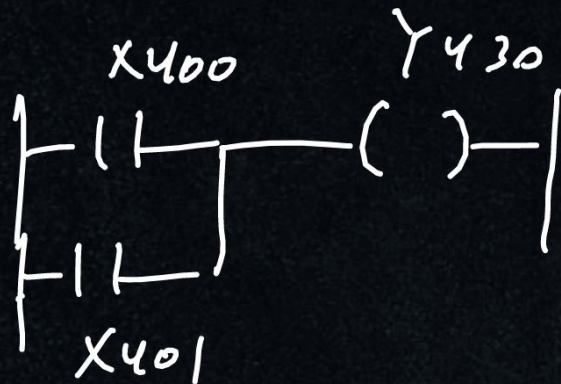


```
LD X400  
OR X401  
OUT Y430
```

```
A I0.0  
Q I0.1  
= Q1.0
```

2) AND

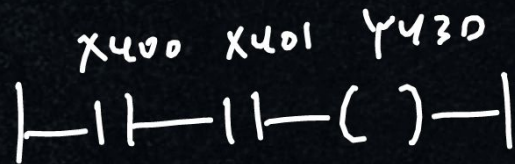


LD X400
AND X401
OUT Y430

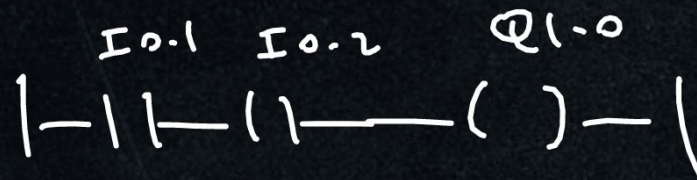


A I 0.1
A I 0.2
= Q 1.0

3) NOR $O = (A+B)' = A'B'$


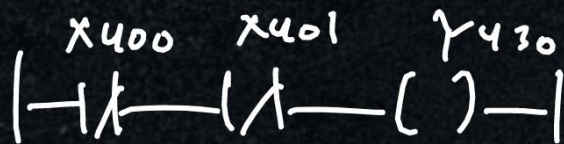


LDI X400
ANI X401
OUT Y430

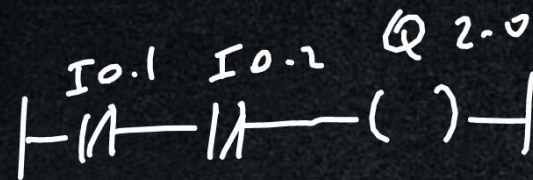

AN I 0.1
AN I 0.2
= Q 2.0

4) XOR $O = AB' + A'B$

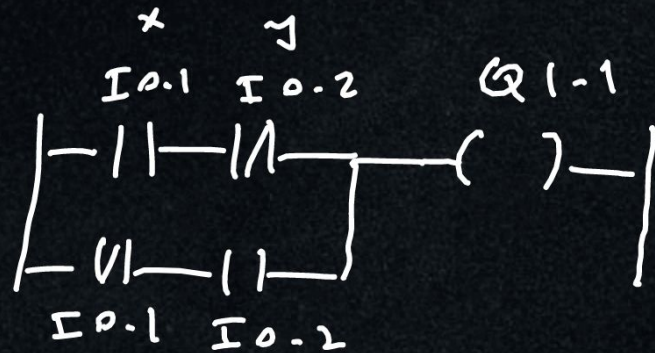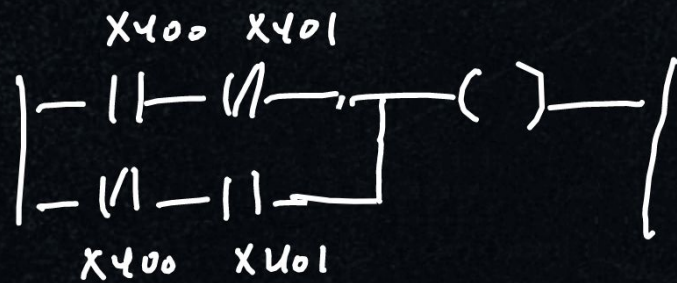


```
LD X400
ANI X401
LDI X400
AND X401

ORB

OUT Y430
```

```
A (
  A I0.1
  AN I0.2
)
O (
  AN I0.1
  A I0.2
)
= Q1.1
```


Internal Relay



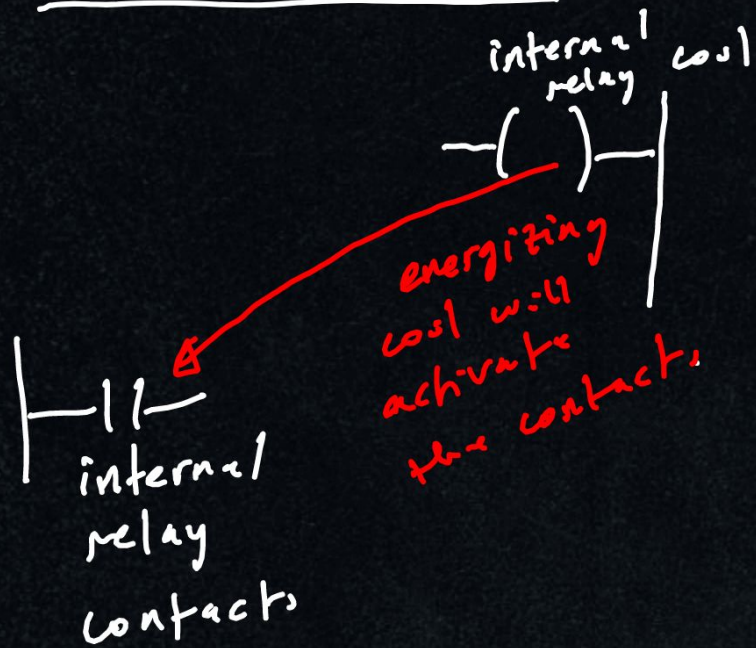


Addresses :-


Mitsubishi M100, M101, M102, ...

Siemens F0.0, F0.1, F0.2, ...

EX

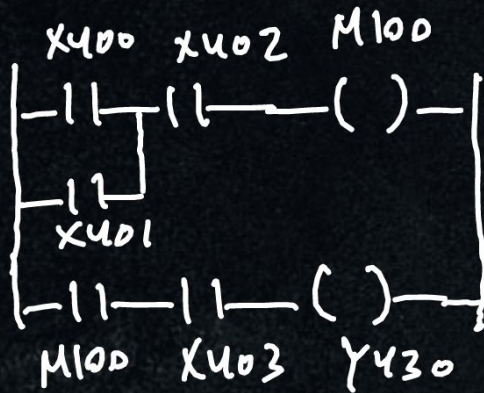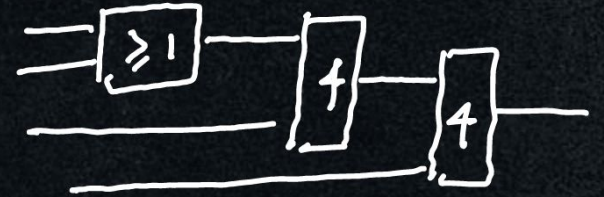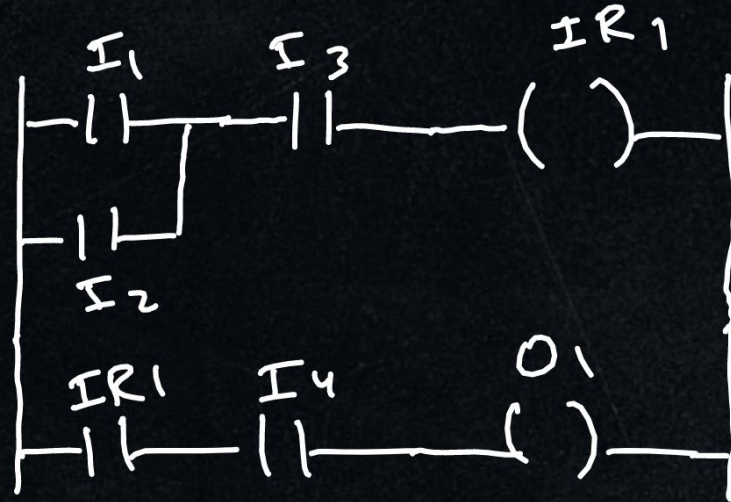

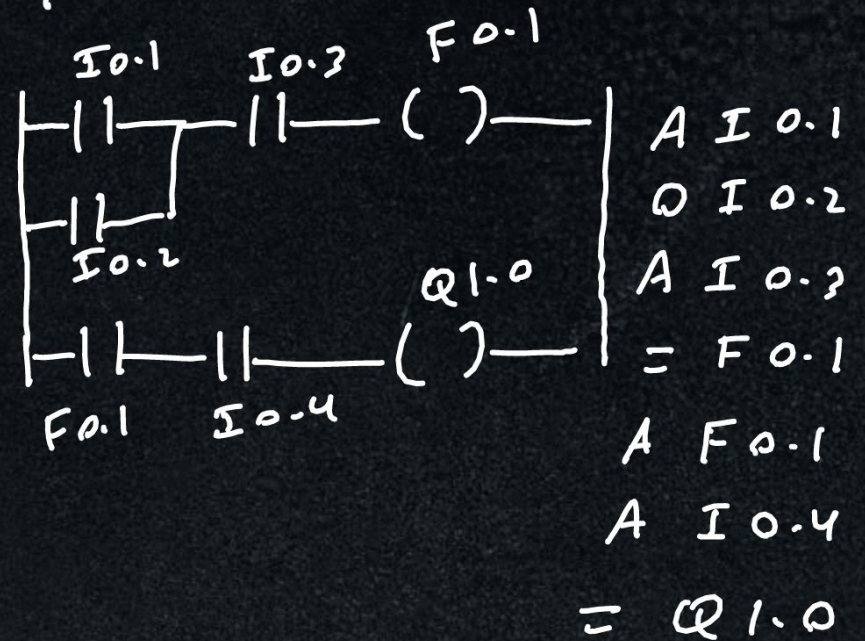
```
LD X400
OR X401
AND X402
OUT M100
LD M100
AND X403
OUT Y430
```




```
A I0.1
O I0.2
A I0.3
= F0.1
A F0.1
A I0.4
= Q1.0
```

Set and Reset

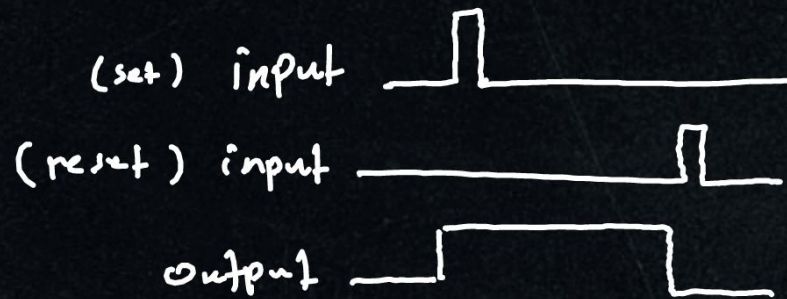


Mitsubishi

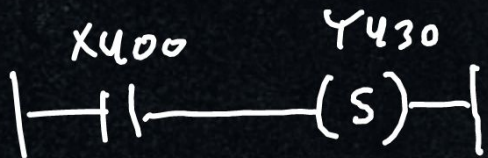

```
LD X400
S Y430
```

```
LD X401
R Y430
```

Siemens

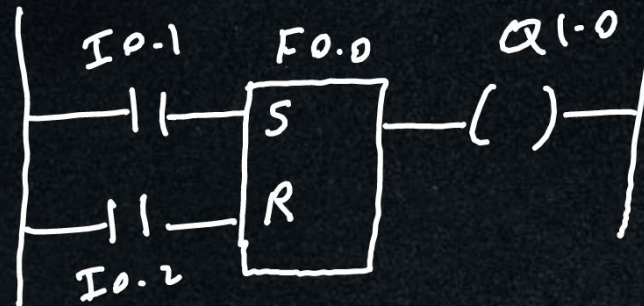


```
A I0.1
S F0.0
A I0.2
R F0.0
```

```
A F0.0
= Q1.0
```


Timers

Types of timers


1) ON-delay timer

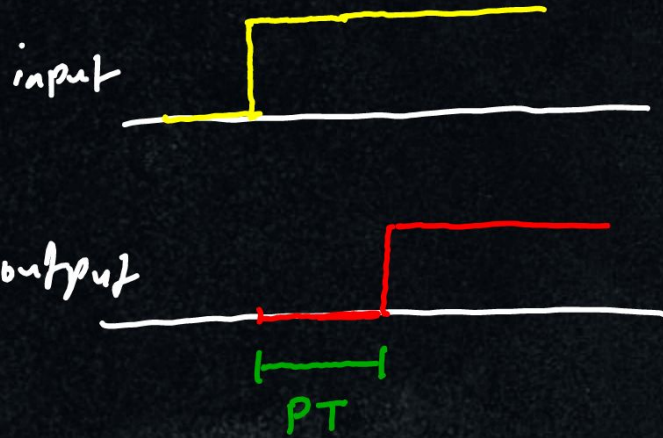

2) OFF-delay timer

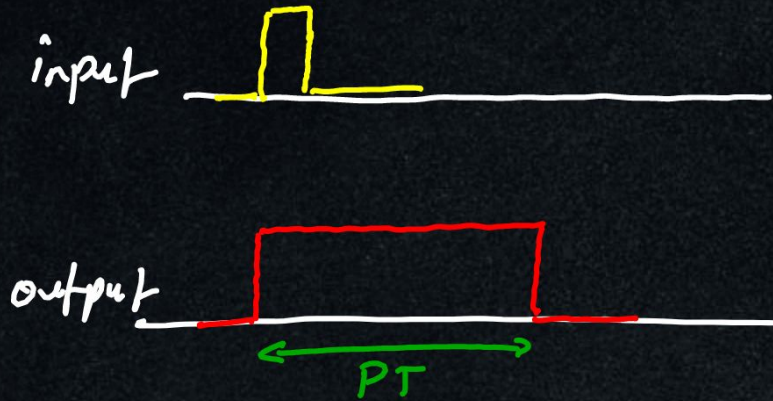


3) pulse timer

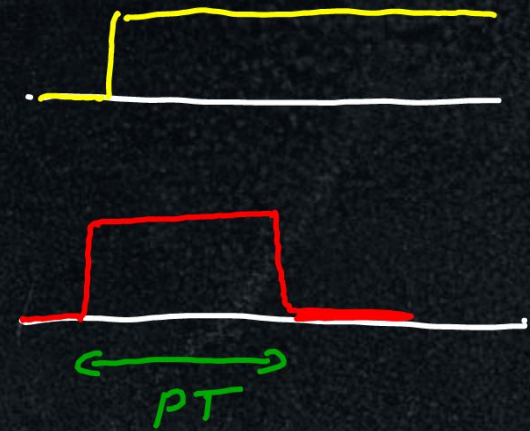


Timers

Types of timers


1) ON-delay timer

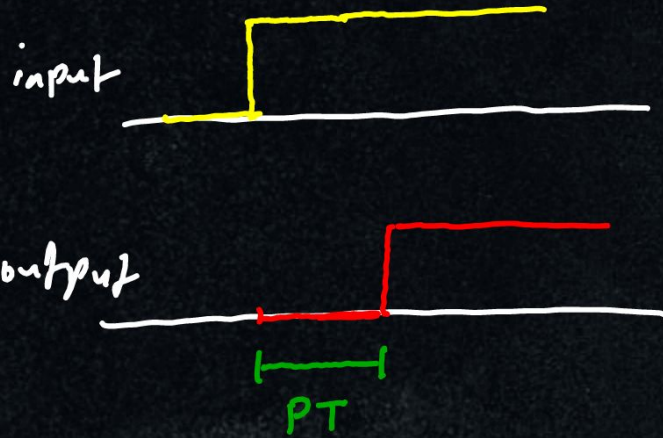

2) OFF-delay timer

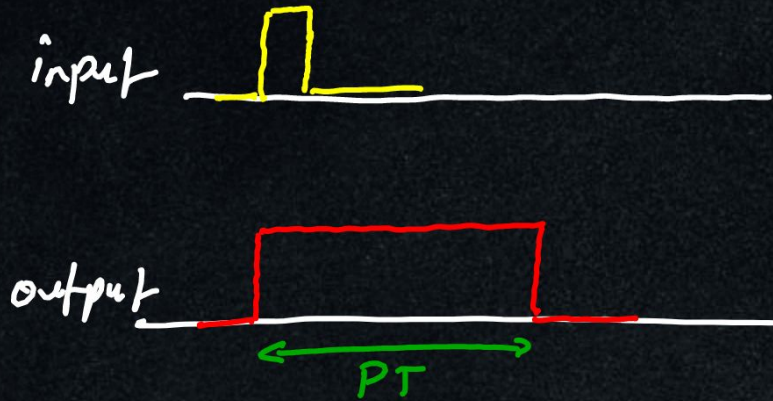


3) pulse timer

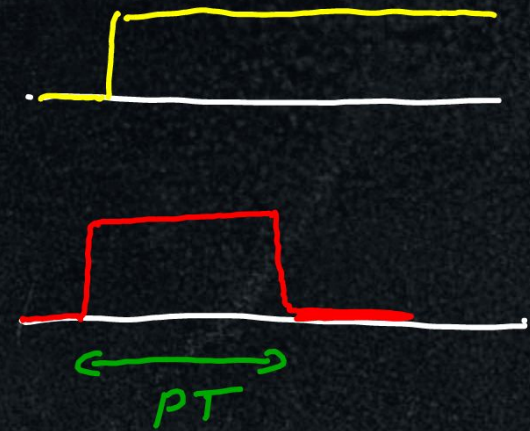

Timers

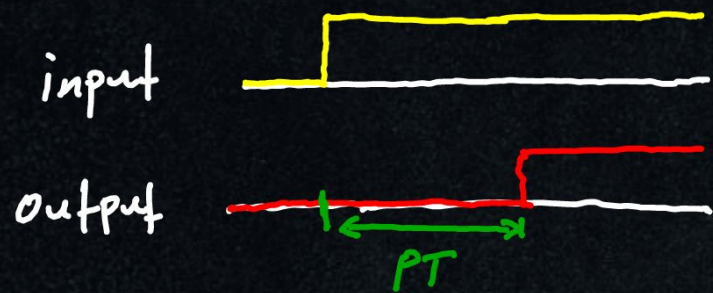- ON delay timer
- OFF delay timer
- pulse timer



ON-delay timer

PT: preset time

Mitsubishi

$PT = n * \text{time base of PLC}$

↓
is real integer

10 ms
100 ms
1 sec
10 sec
100 sec

$K5 \Rightarrow PT = 5 \text{ sec}$ time base = 1 sec

$K4 \Rightarrow PT = 4 \text{ sec}$ time base = 1 sec

Siemens

$KT \text{ xxx}.x$

000 0 → 10 ms
001 1 → 100 ms
 2 → 1 sec
 ⋮
999

$KT 5.1$

$PT = 5 * 100 \text{ msec} = 500 \text{ ms}$

$KT = 7.2$

$PT = 7 * 1 \text{ sec} = 7 \text{ sec}$


Addresses

Mitsubishi: T450, T451, ...


Siemens: T0, T1, T2, ...

① ON-delay timer


Mitsubishi:

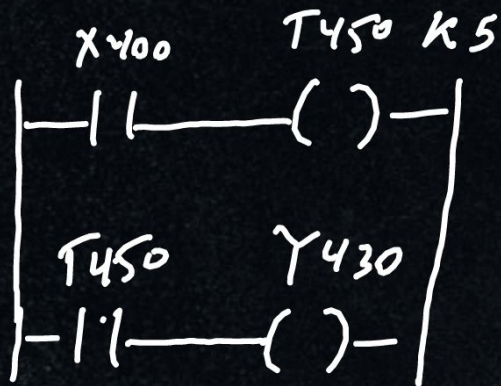
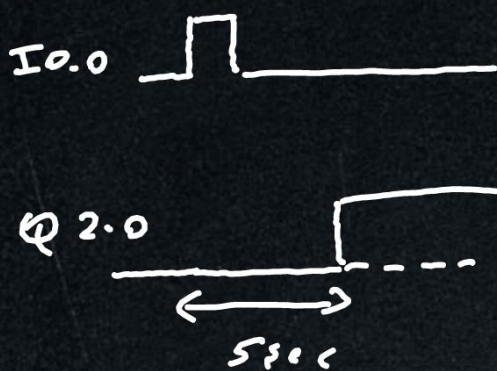
```
LD X400
OUT T450
K5
LD T450
OUT Y430
```






Siemens:

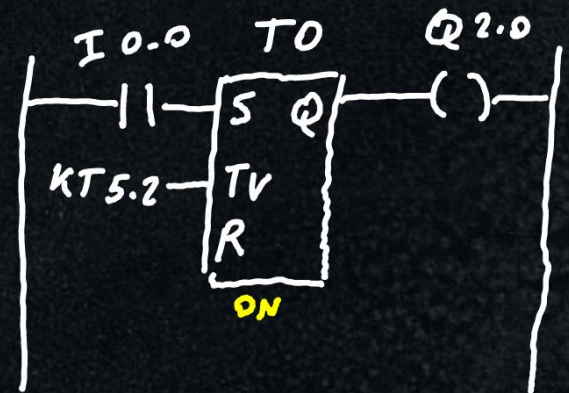

```
AI 0.0
SR T0
LKT 5.2
ATO
= Q2.0
```



② OFF delay timer

timer → Co.1 ←
 ↘ contact.

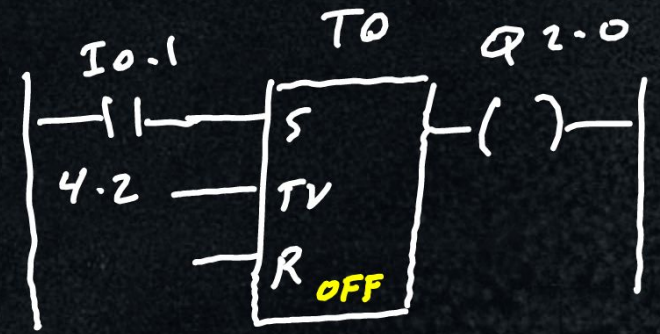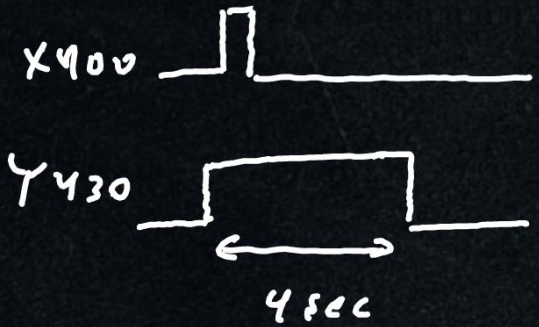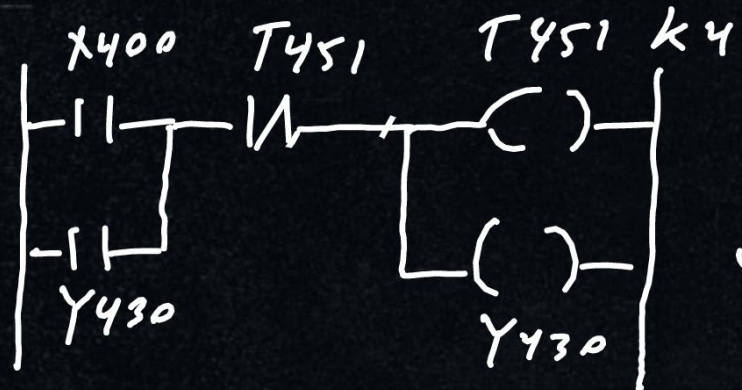
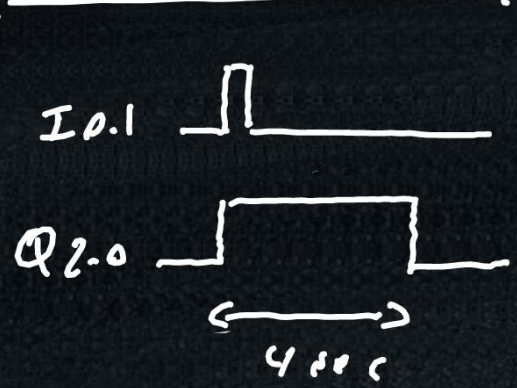


A I 0.1
 S R T0
 L K T 4.2
 A T0
 = Q 2.0

```
LD X400
OR Y430
ANI T451
OUT T451
    K4
LD X400
OR Y430
ANI T451
OUT Y430
```



EX :- ON/OFF cycle

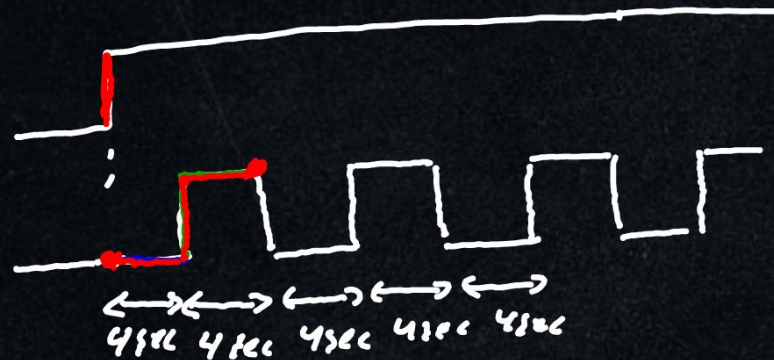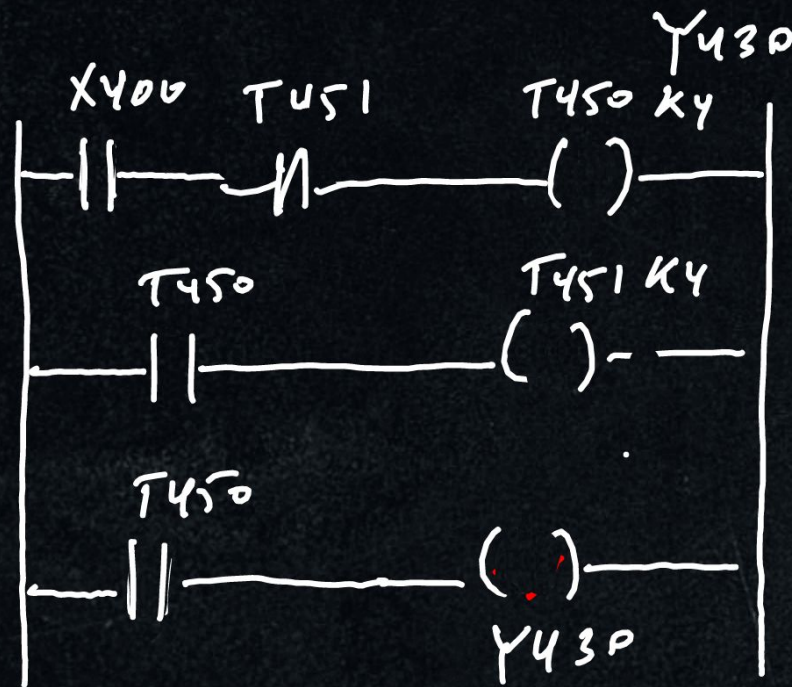


```

LD X400
ANI T451
OUT T450
    K4
LD T450
OUT T451
    K4
LD T450
OUT Y430
  
```

EX:- $\gamma \rightarrow \Delta$ starter of induction motor


$$I_{\gamma} = \frac{\text{phase voltage}}{R}$$

$$I_{\gamma} = \frac{V/\sqrt{3}}{R}$$

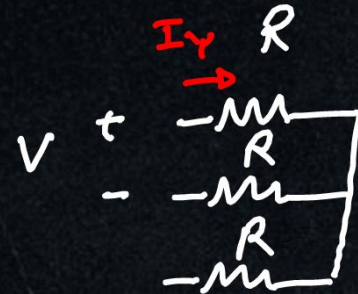


$$I_{\Delta} = \frac{\text{phase voltage}}{R}$$



$$I_{\Delta} = \frac{V}{R}$$

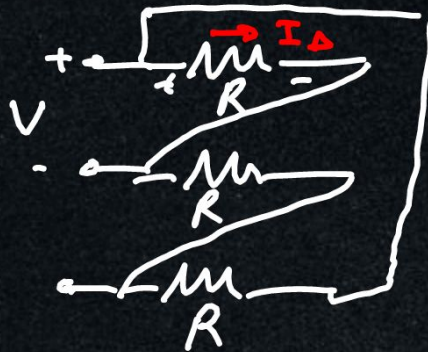


$$\frac{I_{\gamma}}{I_{\Delta}} = \frac{1}{\sqrt{3}} \Rightarrow I_{\gamma} = \frac{1}{\sqrt{3}} I_{\Delta}$$
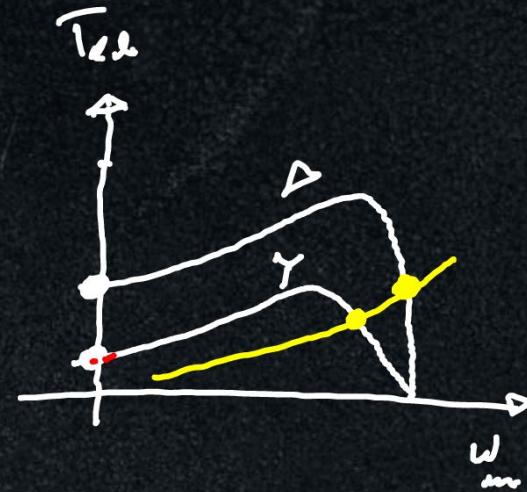
$$T_{\text{del } \gamma} = \frac{1}{3} T_{\text{del } \Delta}$$



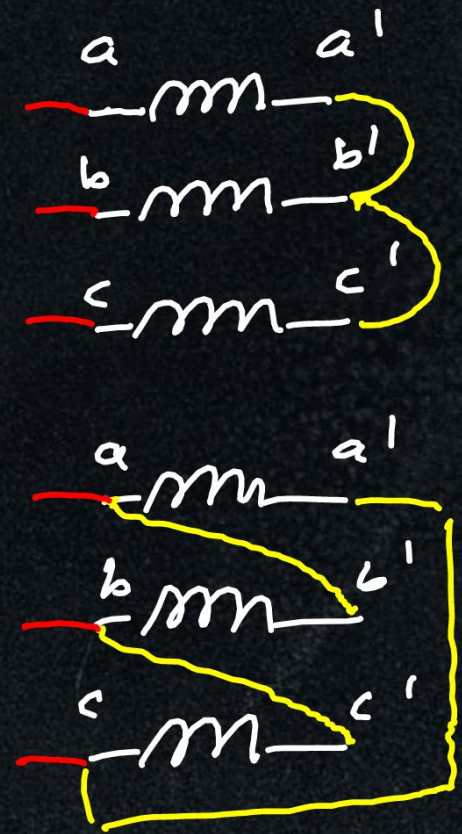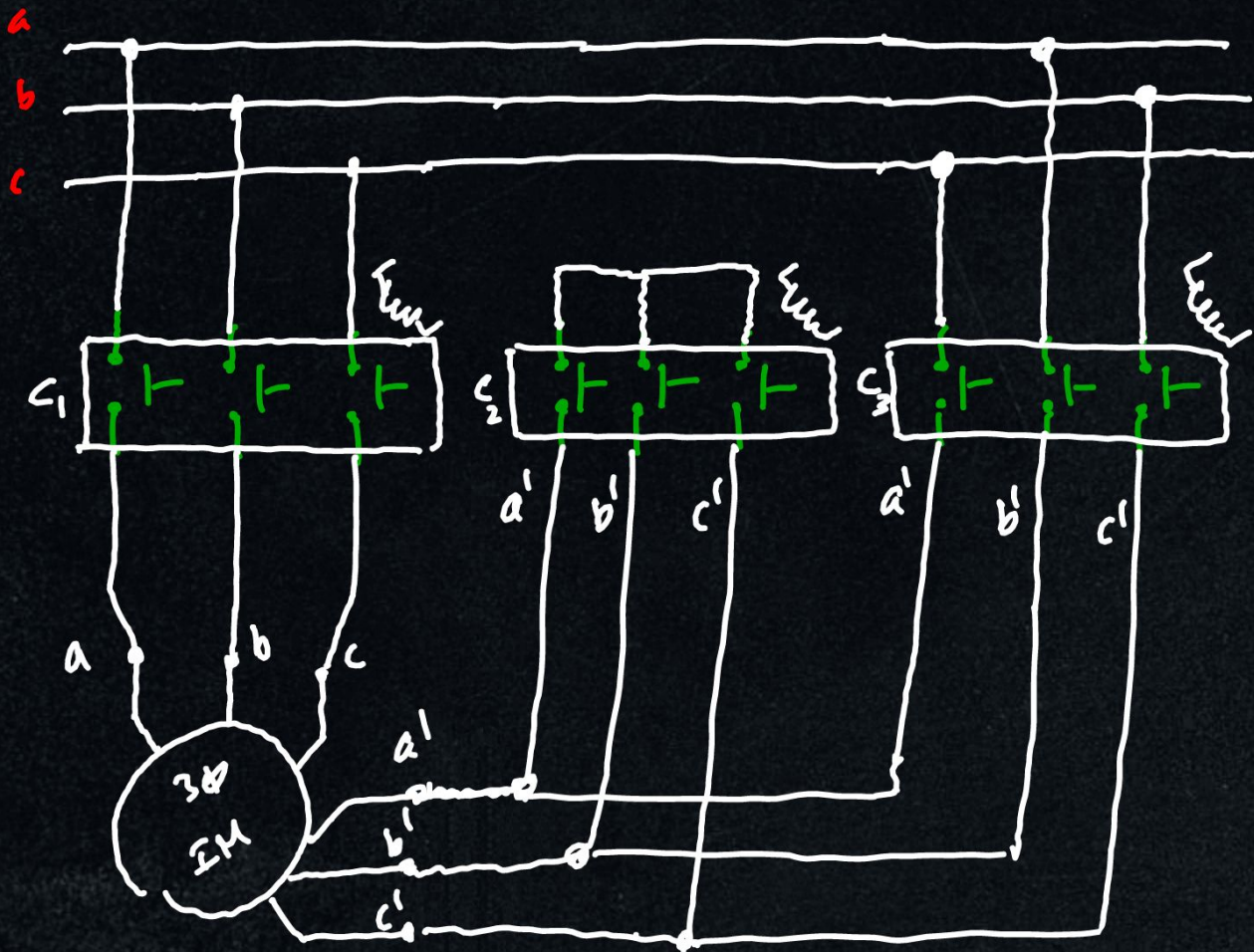

power circuit

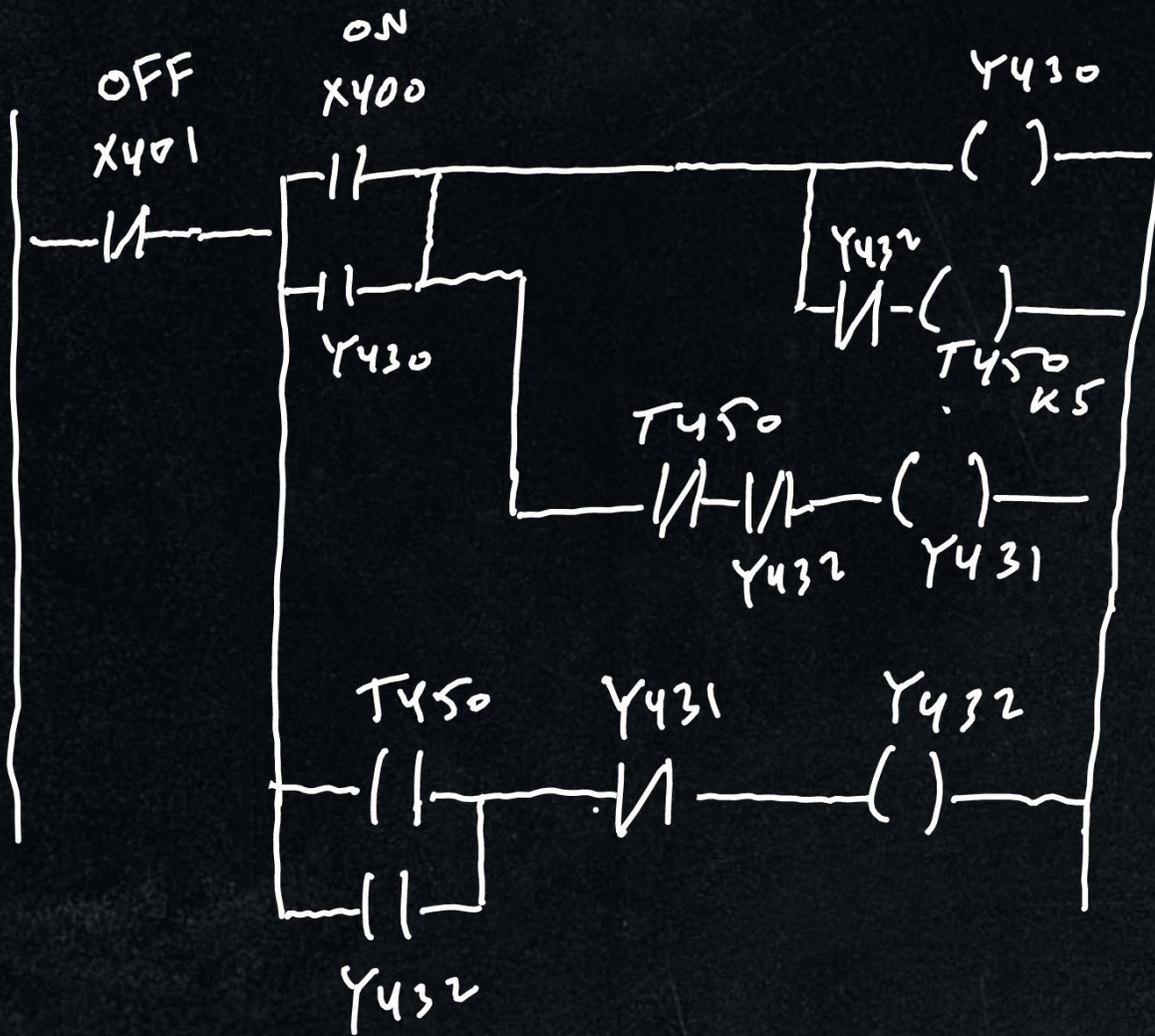


- C₁ Y430
- C₂ Y431
- C₃ Y432

Counters

Up-counter → Count from zero up to the preset value

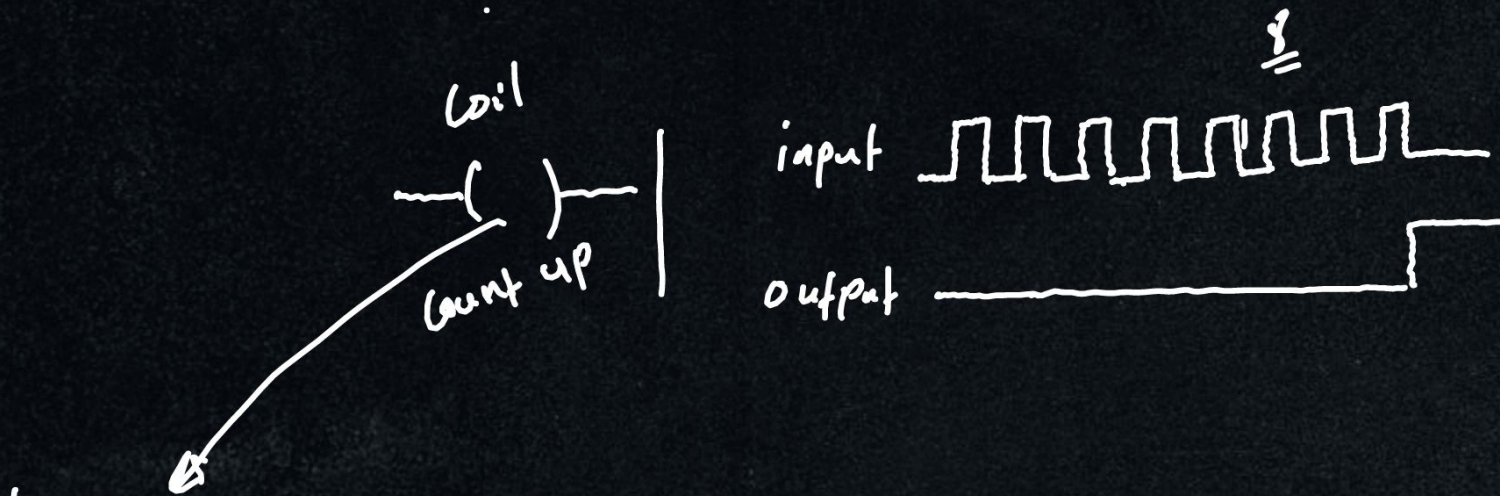Down-counter → Count from preset value to zero



50


Activated when set count is reached after counting from zero

Addresses

Mitsubishi C460, C461, ...


Siemens C0, C1, C2, ...

Mitsubishi

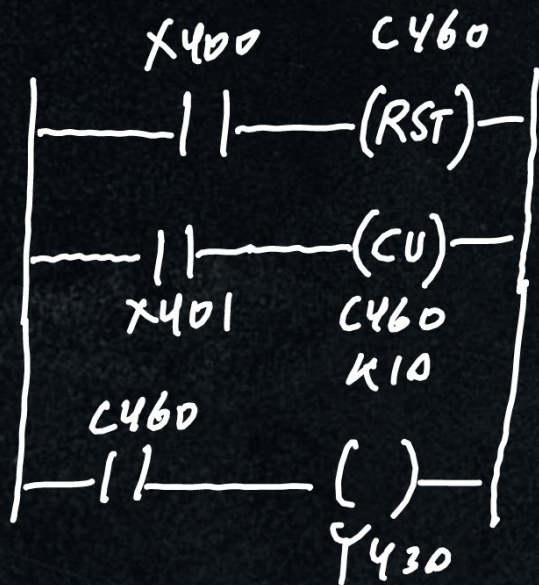


```
LD X400
RST C460
LD X401
CU C460
K10
LD C460
OUT Y430
```

Siemens

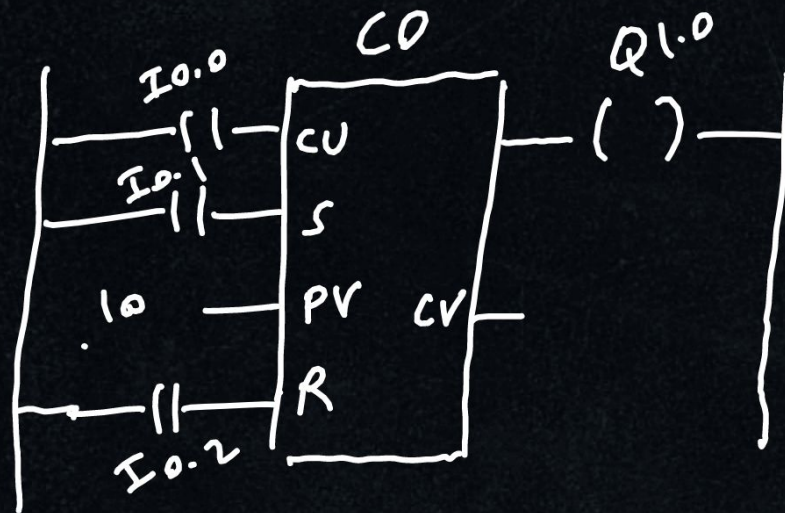


```
A I 0.0
CU CO
A I 0.1
S CO
LKC IO
A I 0.2
R CO
A CO
= Q 1.0
```

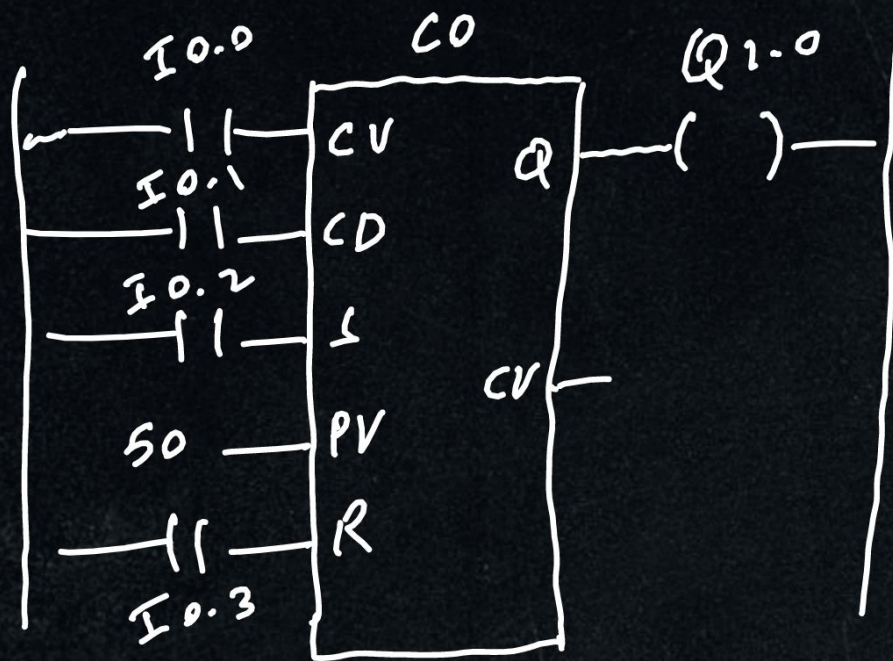
EX :- Design a counter that counts the cars entering a park or leaving it, and gives a message if the park is full.




A I 0.0
 CV CO
 A I 0.1
 CD CO
 A I 0.2
 S CO
 LK S0
 A I 0.3
 R CO
 A CO
 = Q 2.0

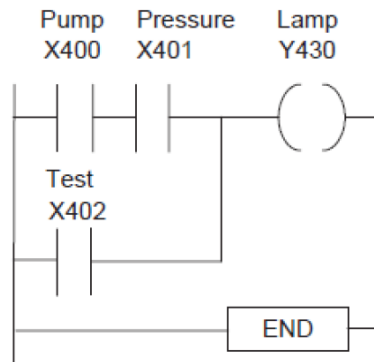
1. Devise a ladder program to switch on a signal lamp if a pump is running and the pressure is satisfactory, or if the lamp test switch is closed.



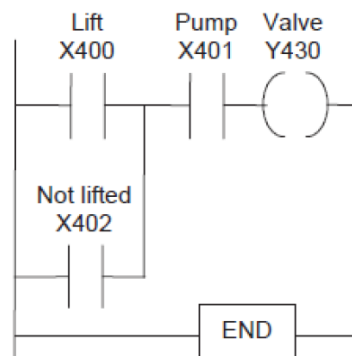
2. Consider a valve which is to be operated to lift a load when a pump is running and either the lift switch is operated or a switch operated indicating that the load has not already been lifted and is at the bottom of its lift channel.



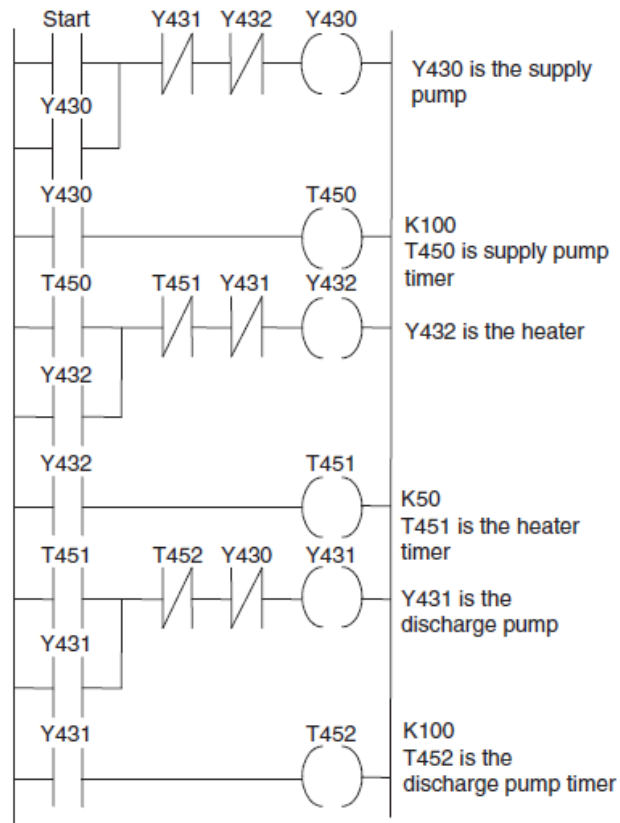
3. This problem is essentially part of the domestic washing-machine program. Devise a ladder program to switch on a pump for 100 s. It is then to be switched off and a heater switched on for 50 s. Then the heater is to be switched off and another pump is to be used to empty the water.




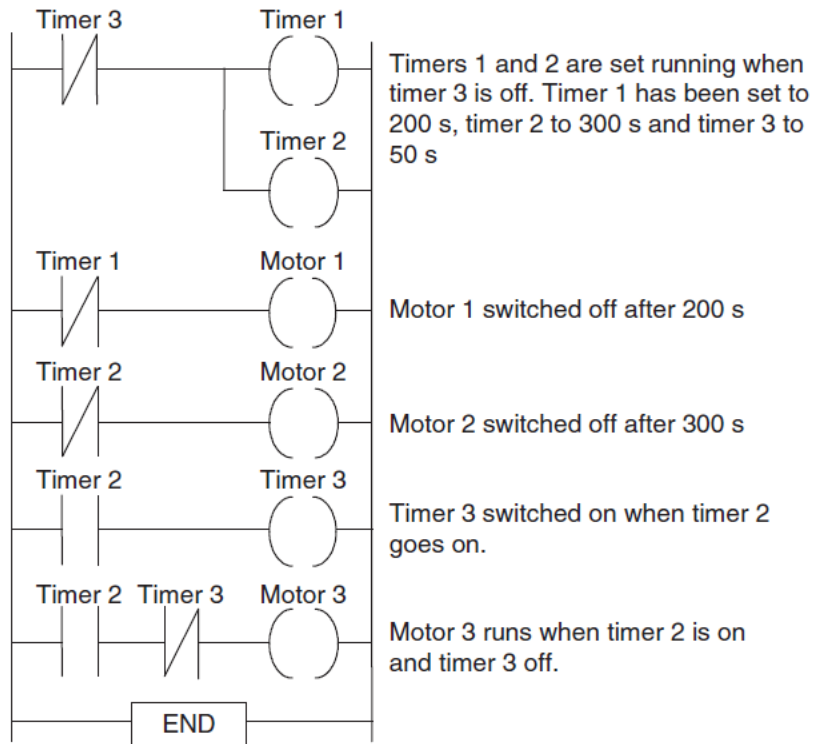
4. Write a ladder program that will switch on two motors when the start switch is operated, then switch off one motor after 200 s and the other motor after a further 100 s. When both motors have been switched off, a third motor is to be switched on for 50 s. The cycle is then to repeat itself unless a stop switch has been activated.



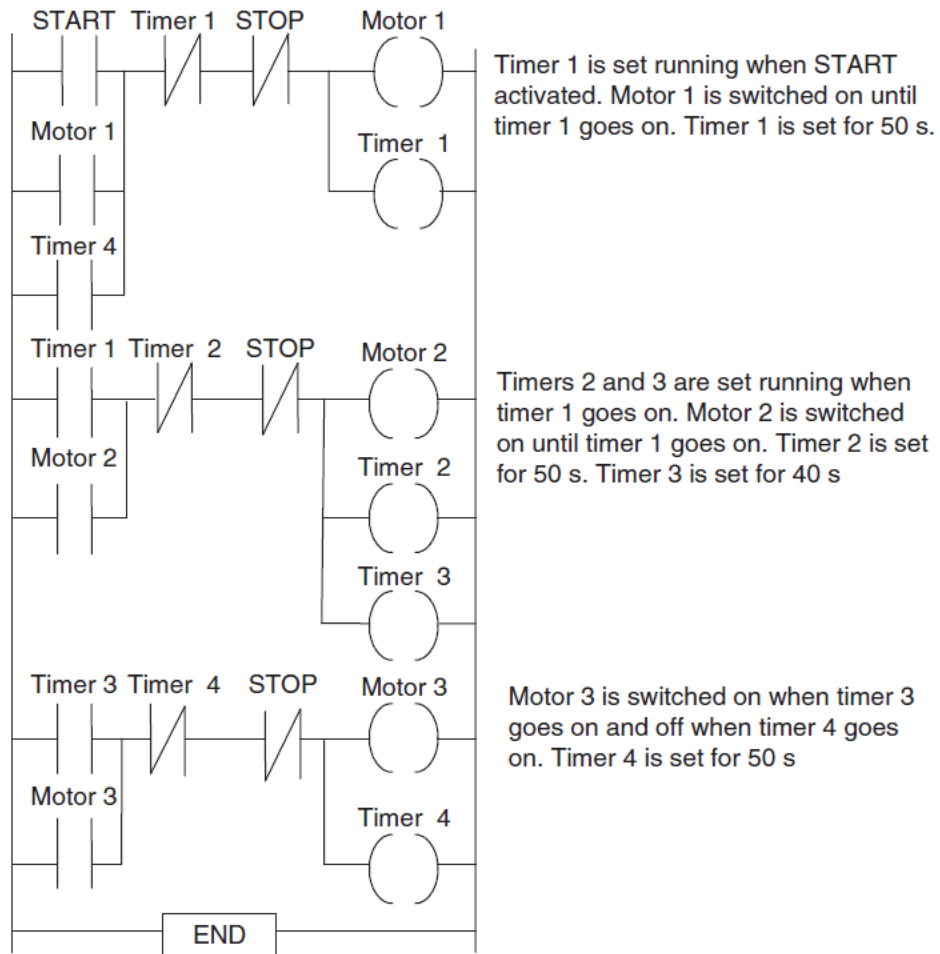5. Write a ladder program to switch on a motor when the start switch is momentarily activated, with the motor remaining on for 50 s. At the end of that time a second motor is to be switched on for a further 50 s. A third motor is to be switched on 10 s before the second motor switches off and is to remain on for 50 s. The cycle is then to repeat itself unless a stop switch has been activated.



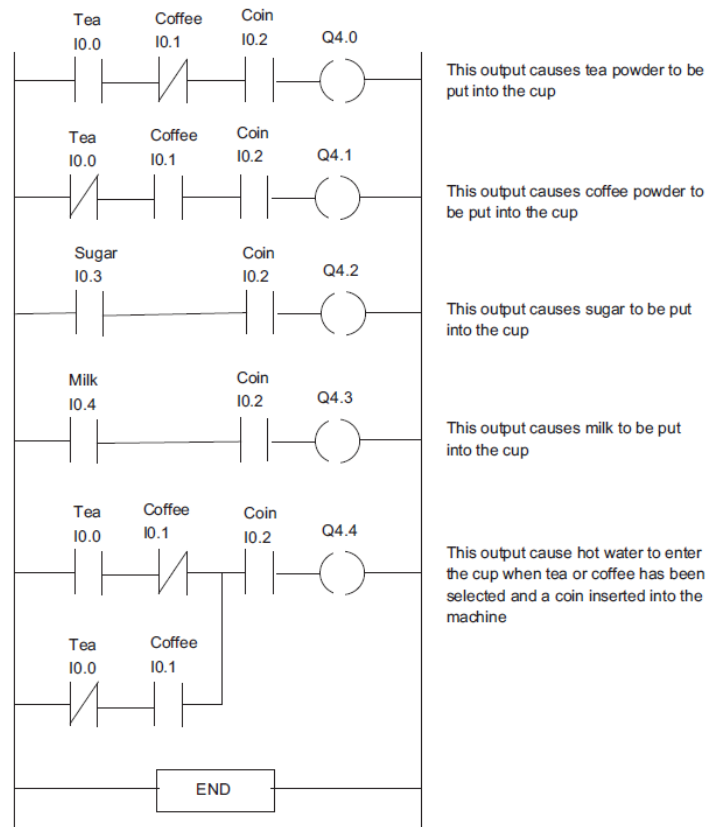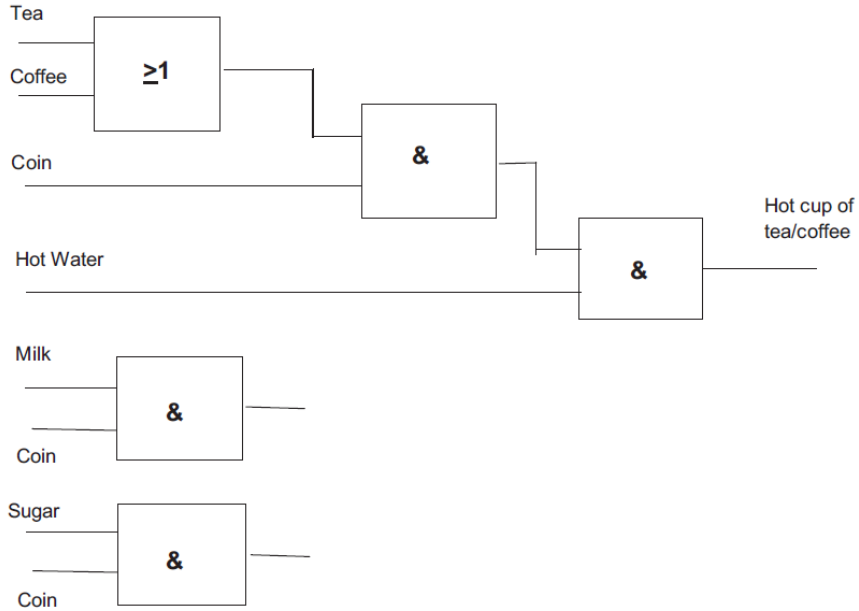6. Write a FBD and ladder programs for drinks machine that allows the selection of tea or coffee, milk or no milk, sugar or no sugar, and will supply the required hot drink on the insertion of a coin.



7. Consider the problem of the control of a machine which is required to direct 6 tins along one path for packaging in a box and then 12 tins along another path for packaging in another box. A deflector plate might be controlled by a photocell sensor which gives an output every time a tin passes it. Thus the number of pulses from the sensor has to be counted and used to control the deflector.

