

Relay + Programmable Logic Controllers


- 1) RLC
- 2) PLC

① RLC


- prior to the widespread use of PLCs in process control and automation, hardwired relay control systems were used.
- Control of motors such as starting, stopping, reversing the direction, sequence starting, etc can be achieved by designing suitable control circuits using relays, contactors, push buttons, etc.

Relay: It is an electromagnet switch that has a coil and a set of associated contacts.

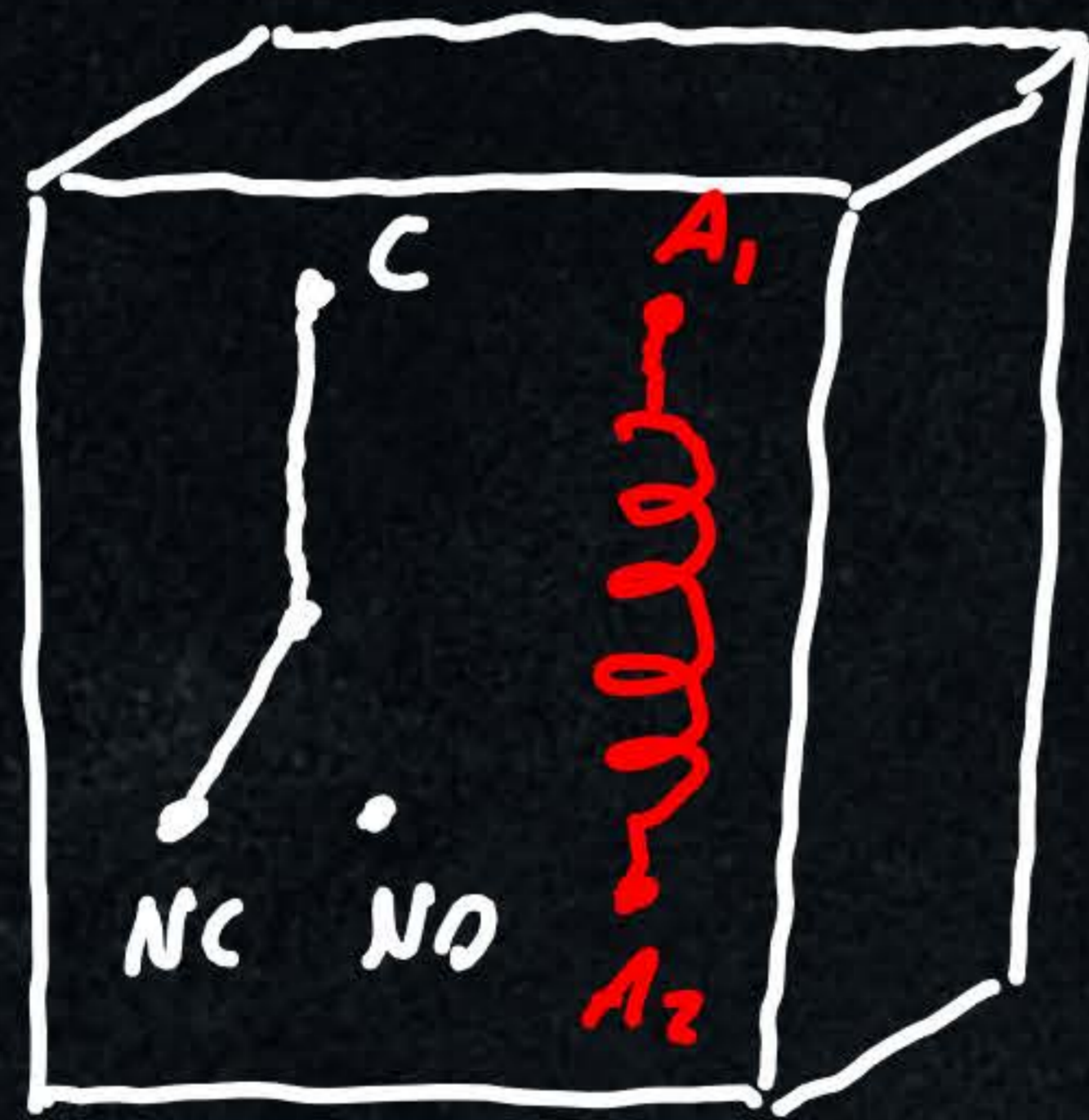→ Contacts can be either normally open or normally closed. (Auxiliary contacts)



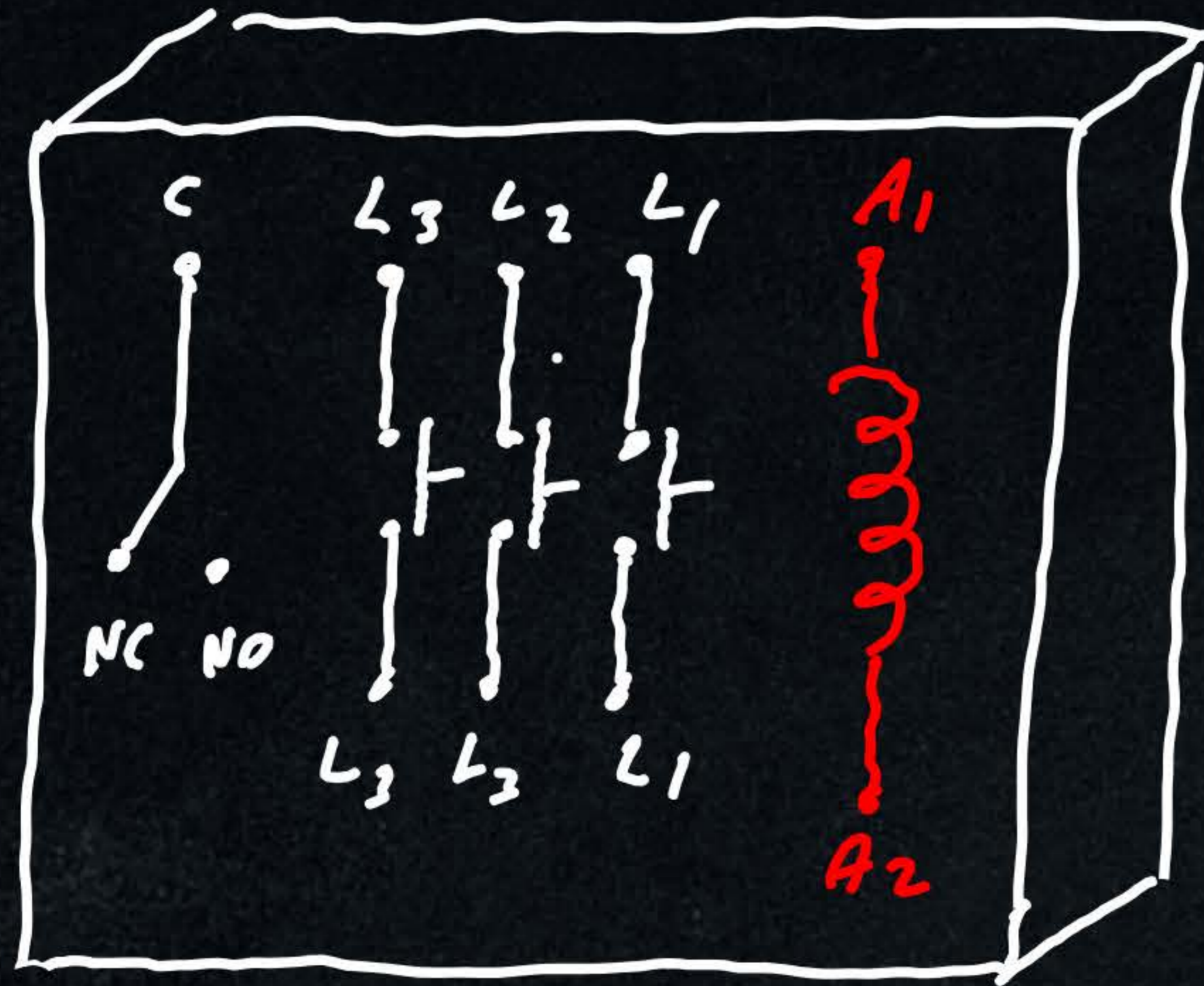Contactor :- It is an electromagnet switch that has a coil and three main contacts with a few auxiliary contacts




Relay symbols



Relay coil



Normally open contact

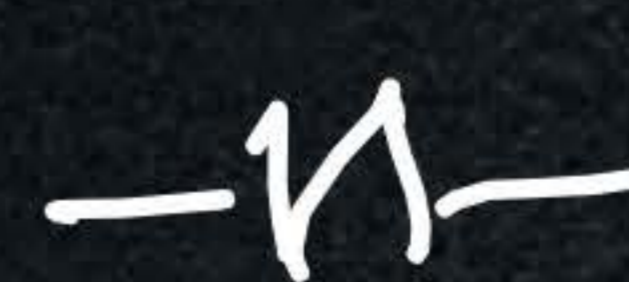


Normally closed contact


Line Diagram

Examples


① AND logic

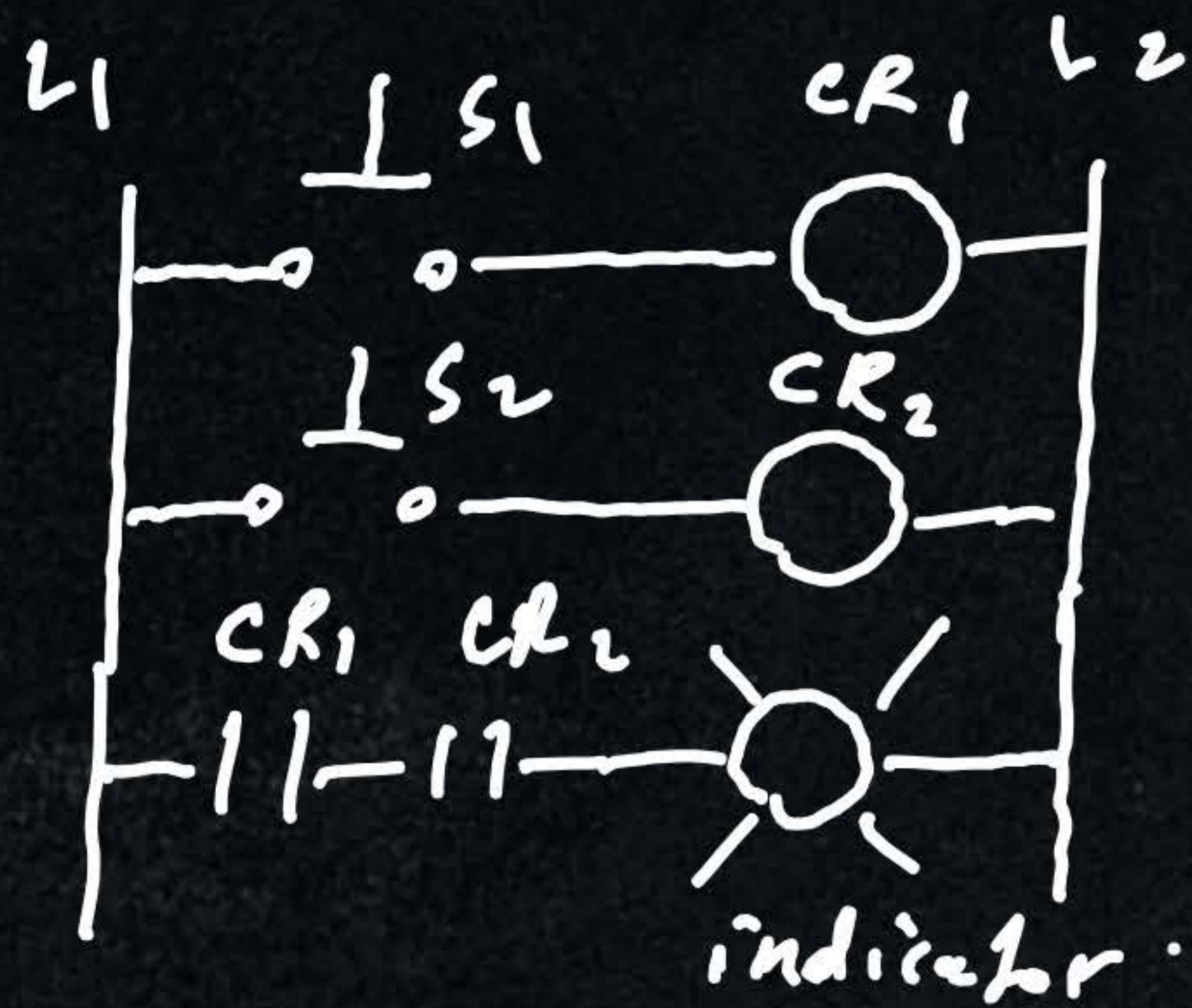


② OR logic

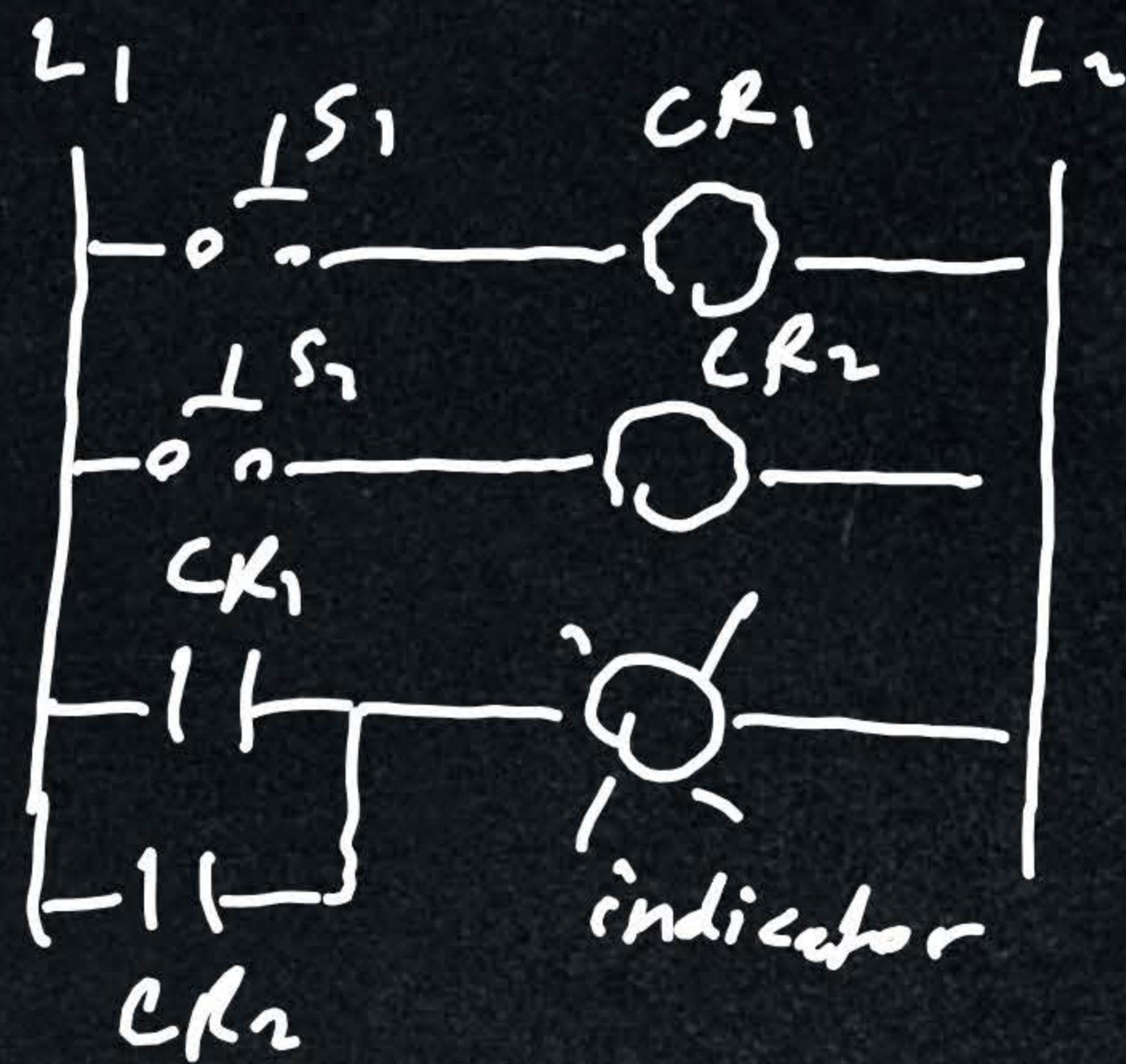



3) start / stop DC Motor

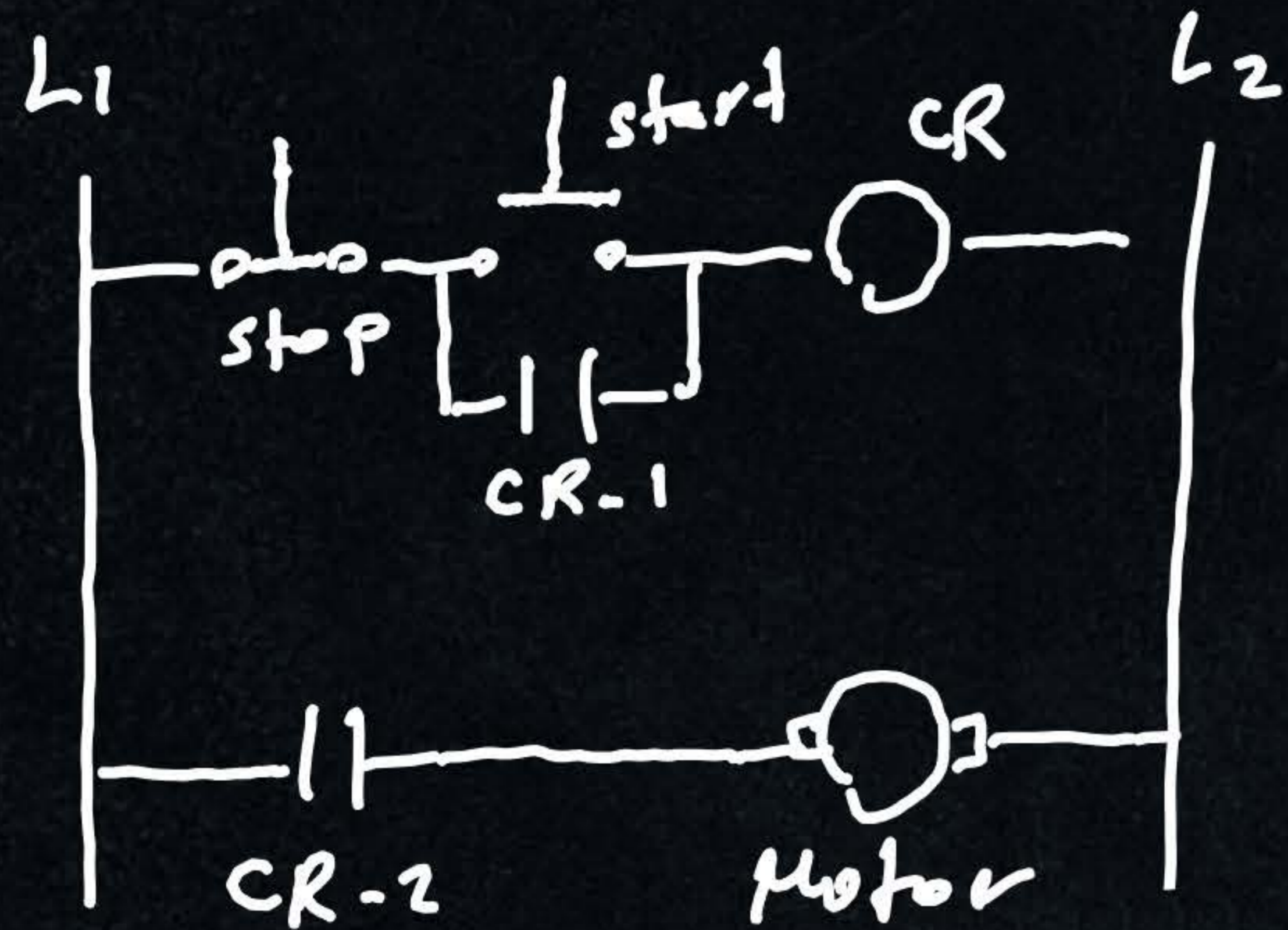



4) Relay controlling two pilot lights,

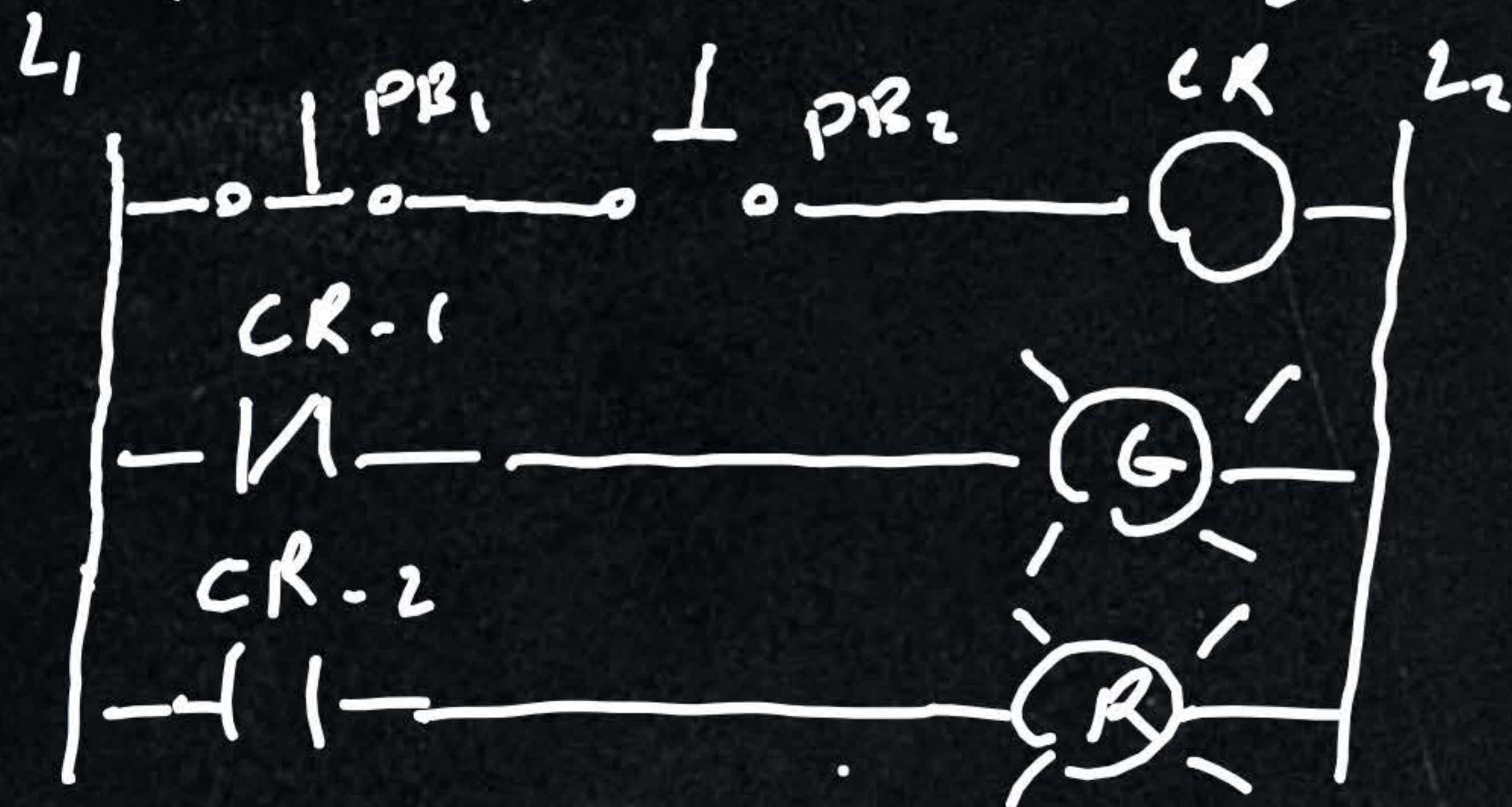



5) Start / stop of 3- ϕ Motor

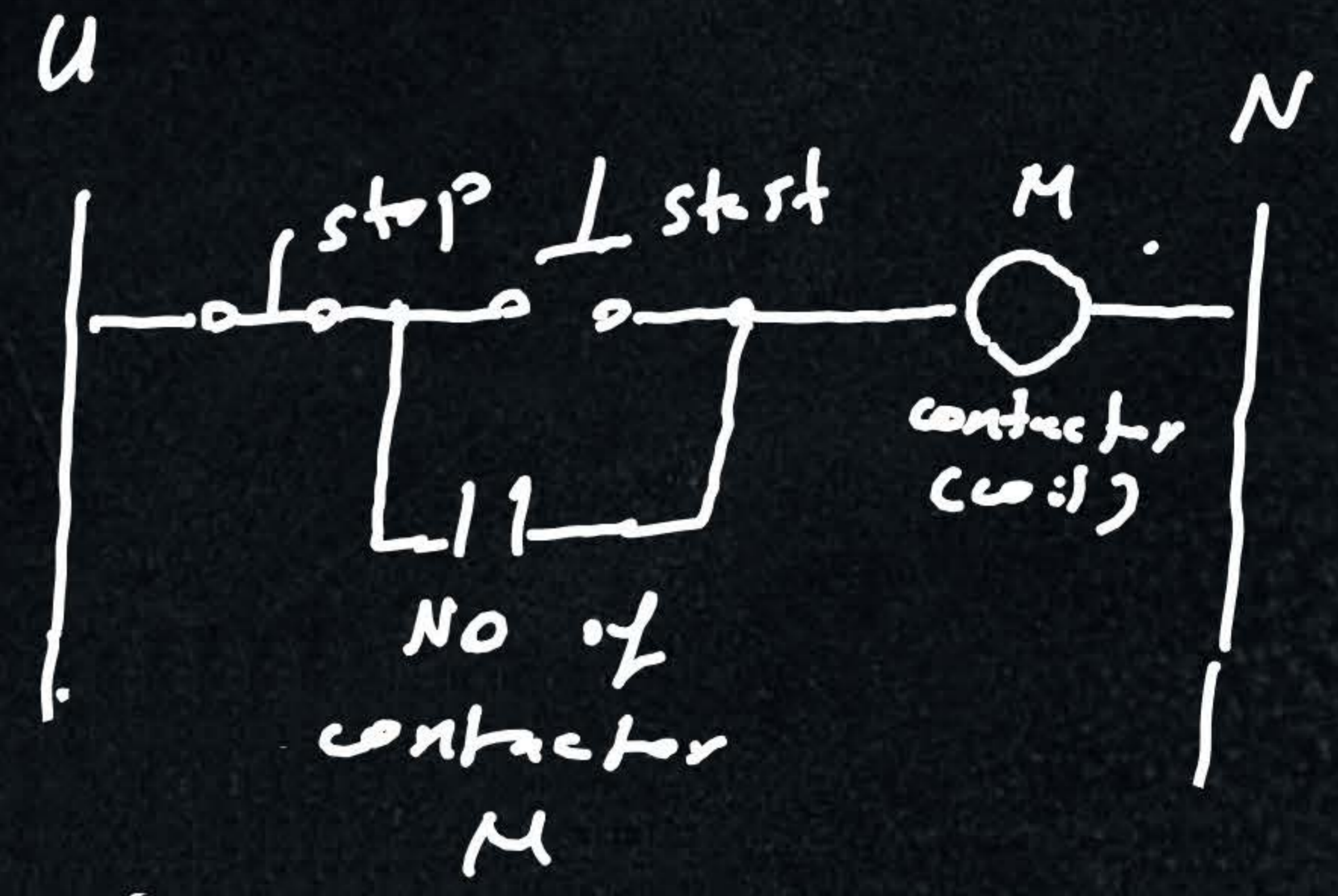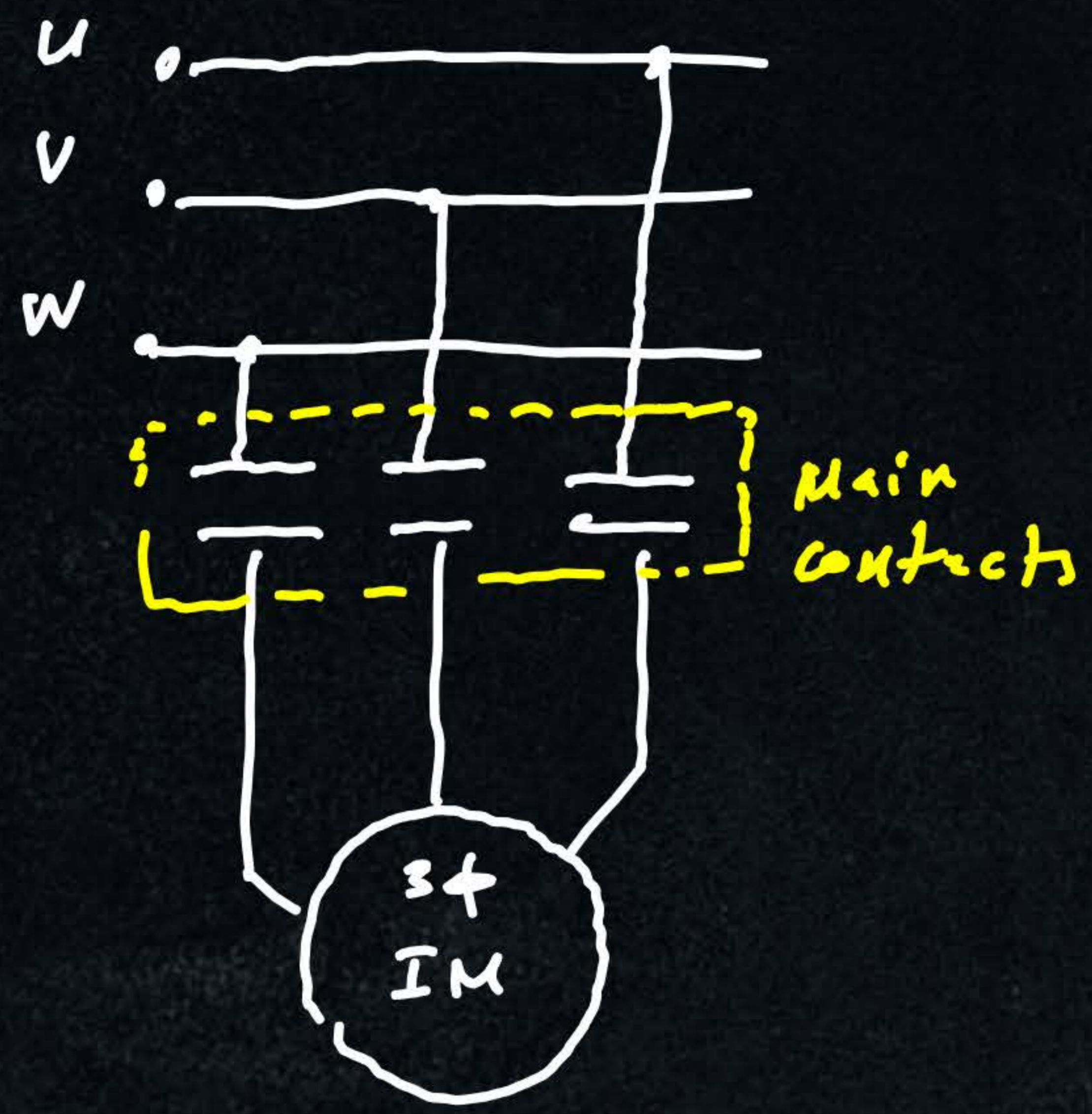

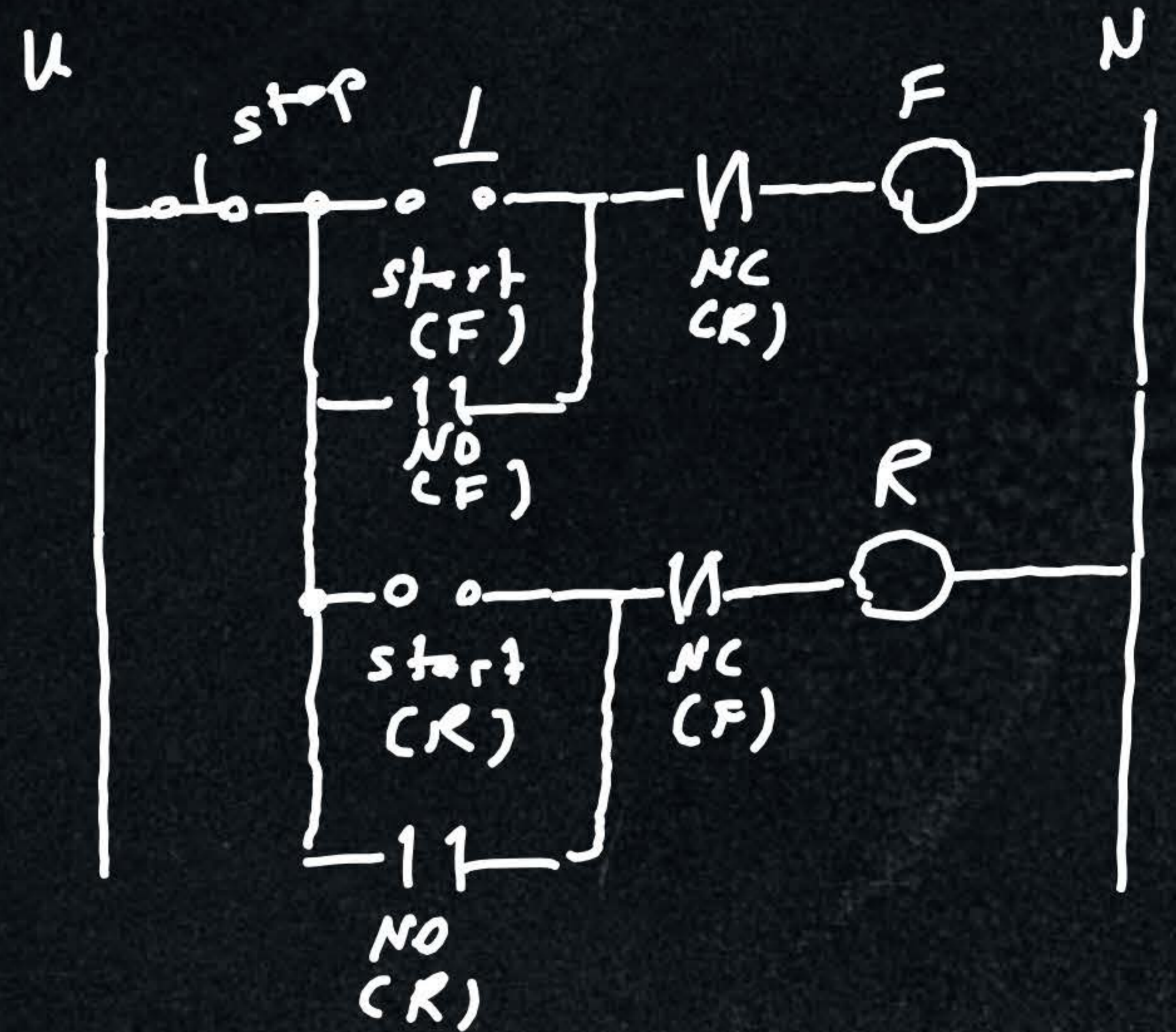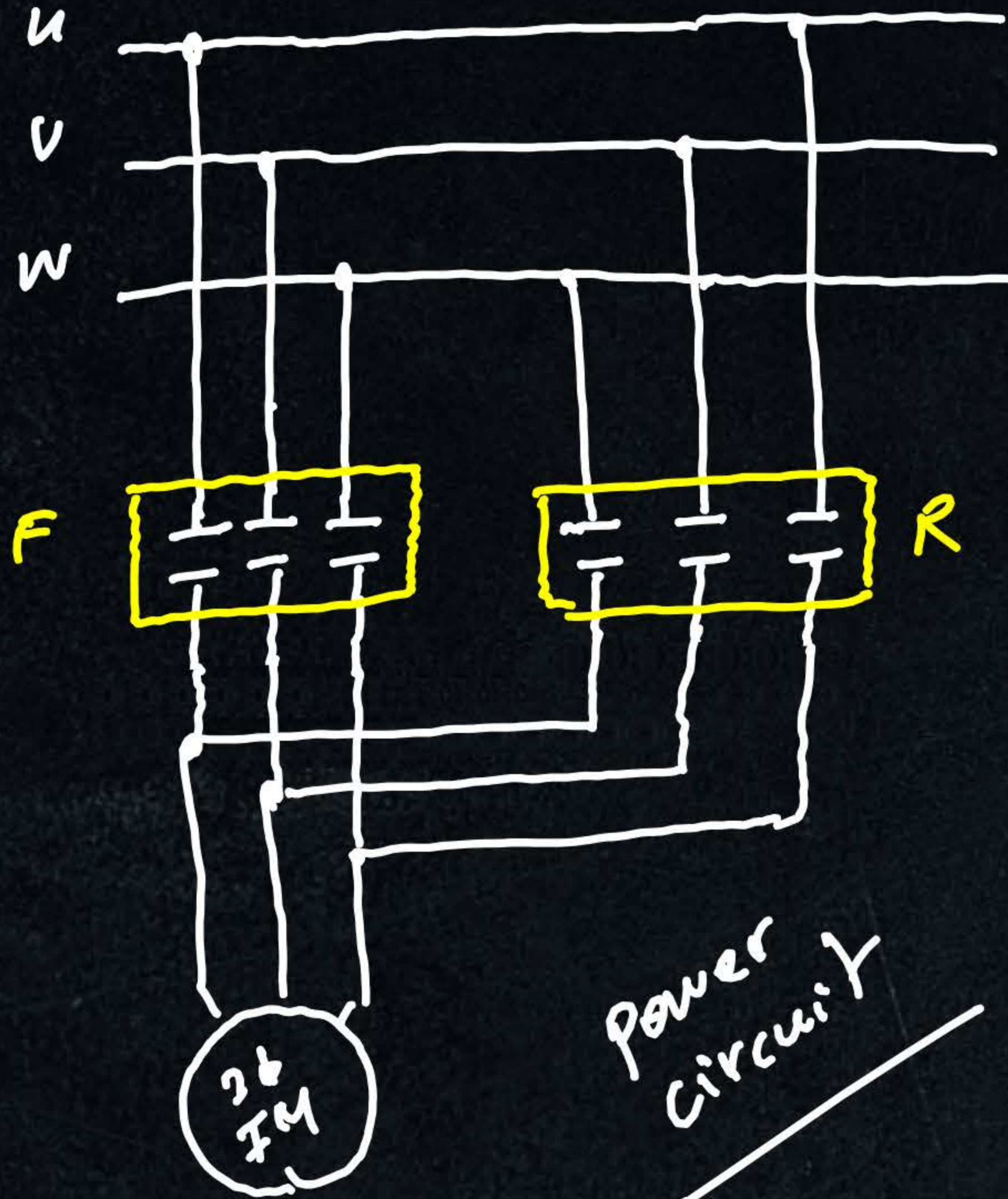6) Reversing the direction of 3 ϕ motor + start/stop




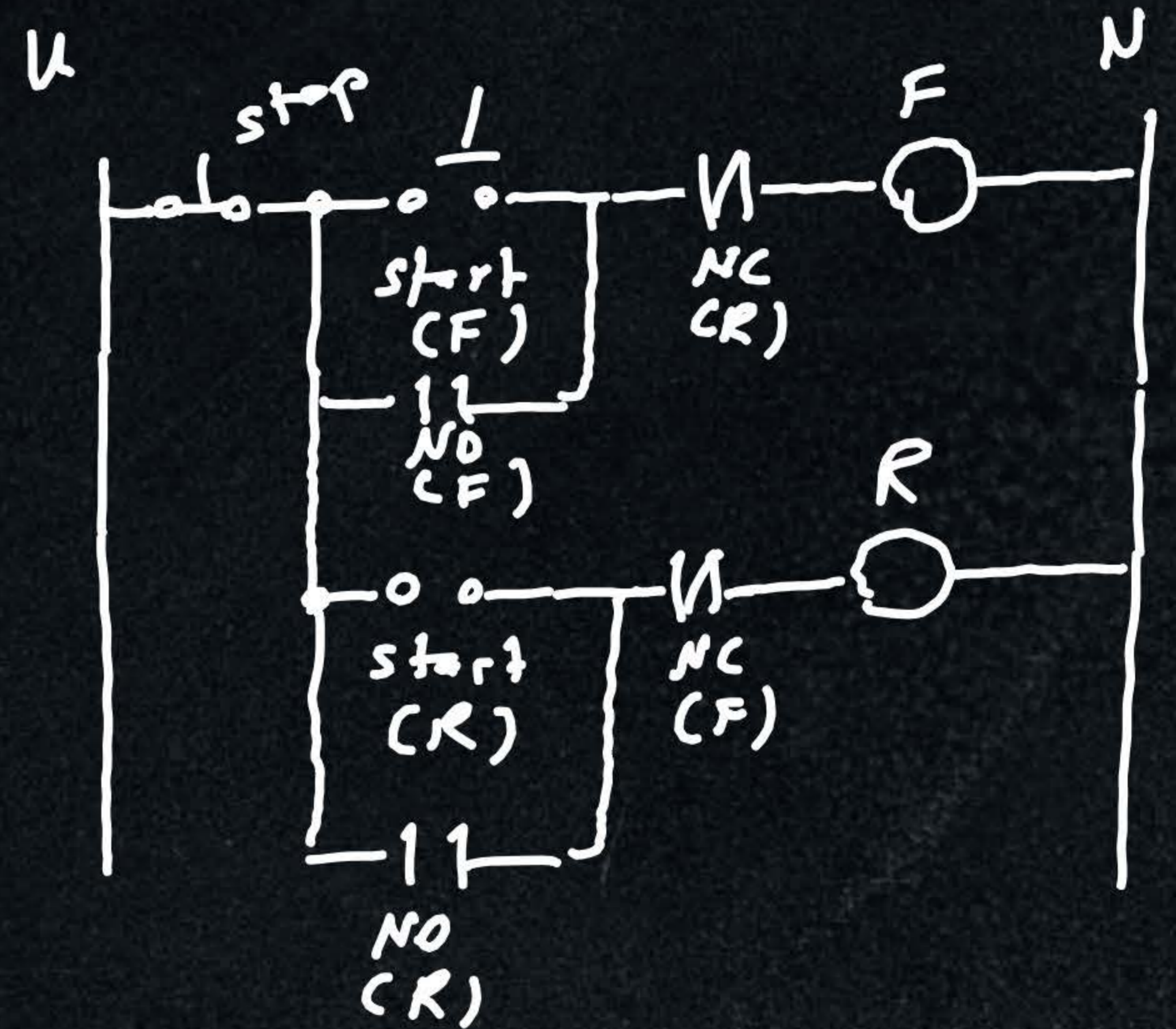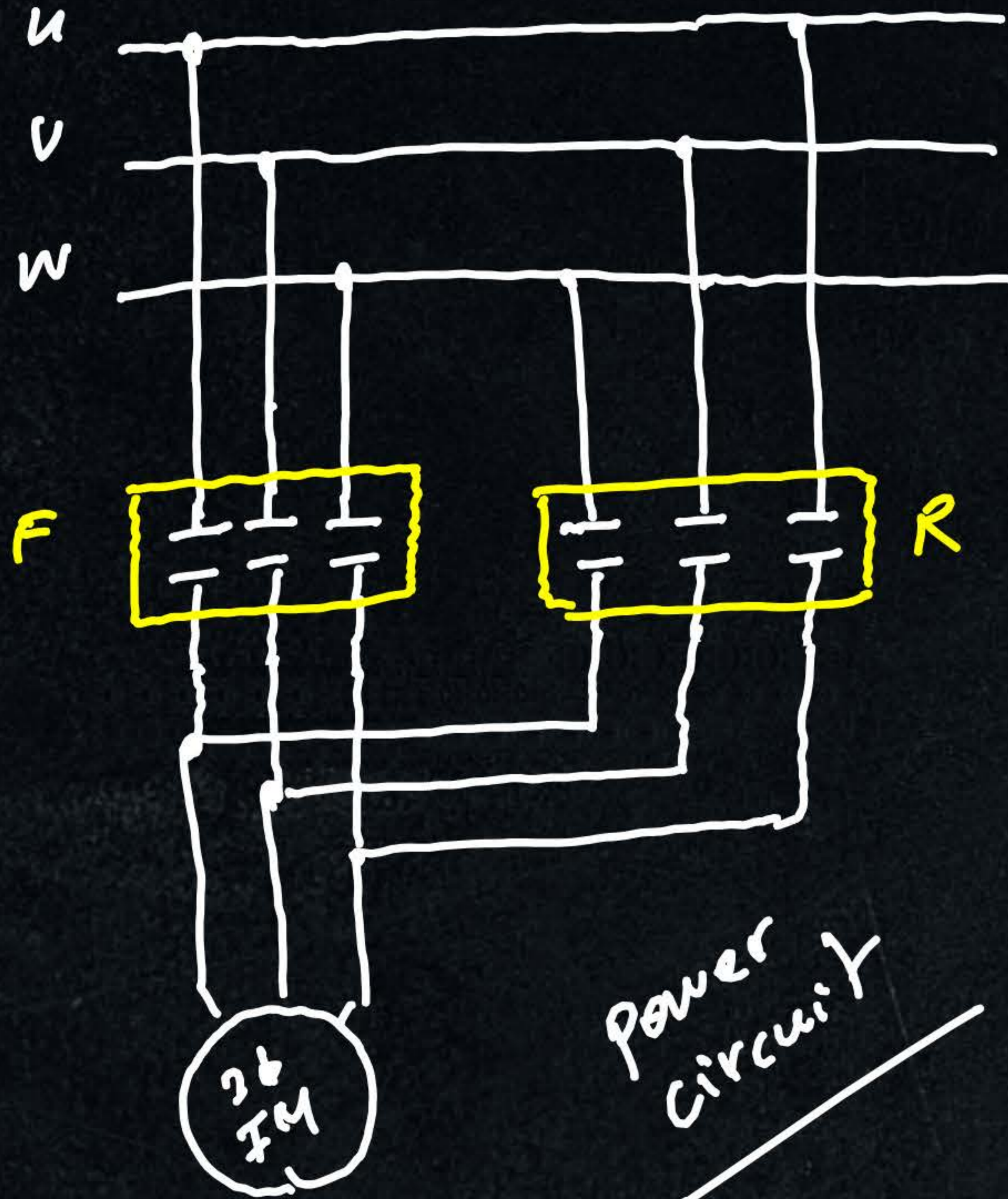6) Reversing the direction of 3 ϕ motor + start/stop




② PLC

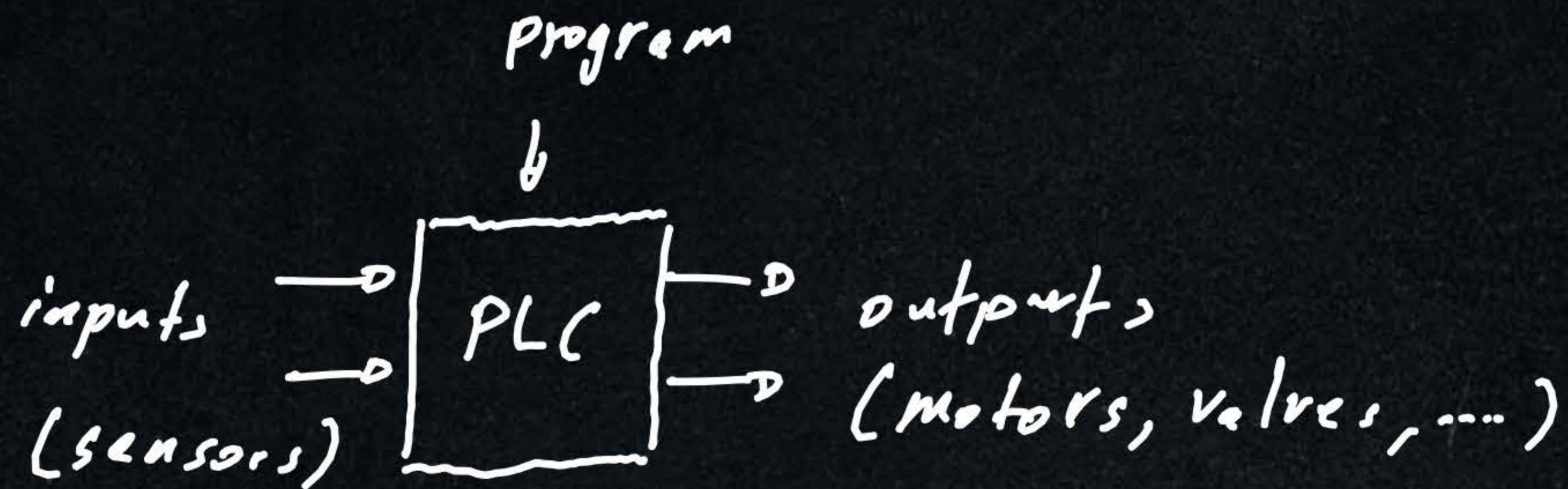- It is a special form of microprocessor-based controller that uses memory to store instructions and to implement functions such as logic, sequencing, counting, and arithmetic in order to control machines and processes.




- Advantages (compared to RLC)
 - 1) v can easily implemented changes "implemented in software"
 - 2) v more robust and reliable
 - 3) v more compact
 - 4) v require less maintenance
 - 5) v can operate faster

Block Diagram

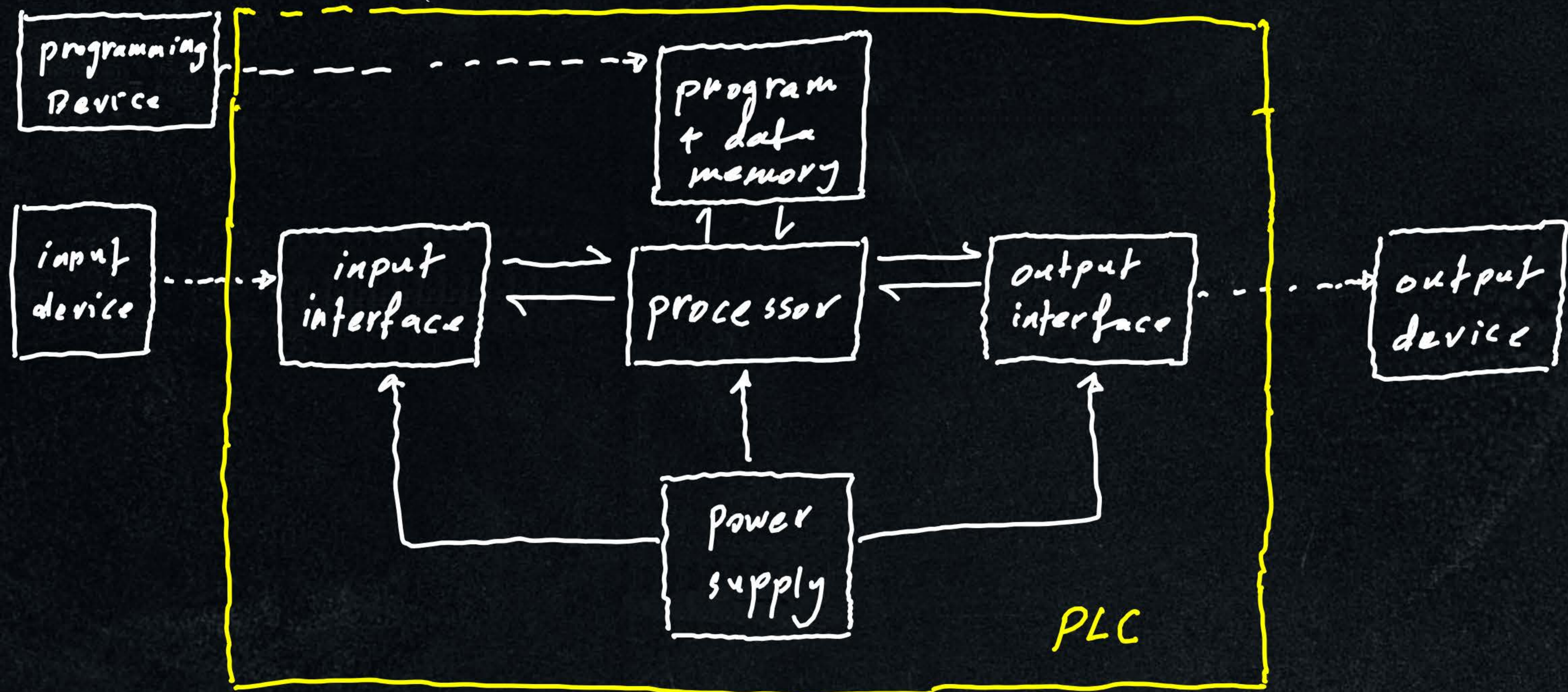

Input/output levels

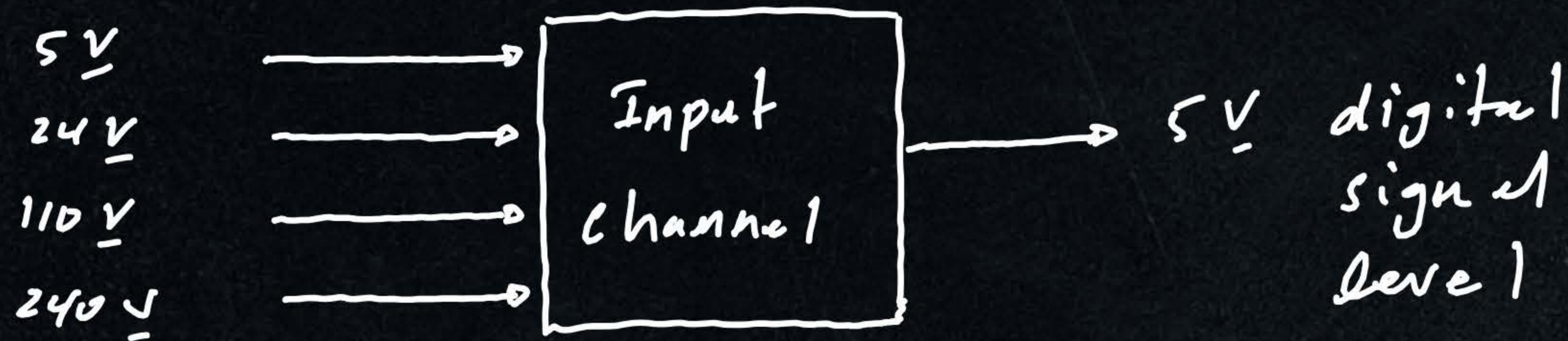

signal conditioning
with isolation



PLCs :

- * Mitsubishi
- * Siemens
- * Toshiba
- * Allen-Bradley
- * Schneider

Programming Languages :

- Ladder diagrams (LAD)
- Instruction lists (IL)
- Function block diagram (FBD)
- Sequential function charts (SFC)
- Structured text (ST)

I/O Addresses


- * The PLC has to be able to identify each input and output. It does this by allocating addresses to each input and output.
- * This is likely to be just a number prefixed by a letter to indicate whether it is an input or output.
- * Mitsubishi

24 inputs X400 - X427 in octal notation

16 outputs Y430 - Y447 in octal notation

* Siemens

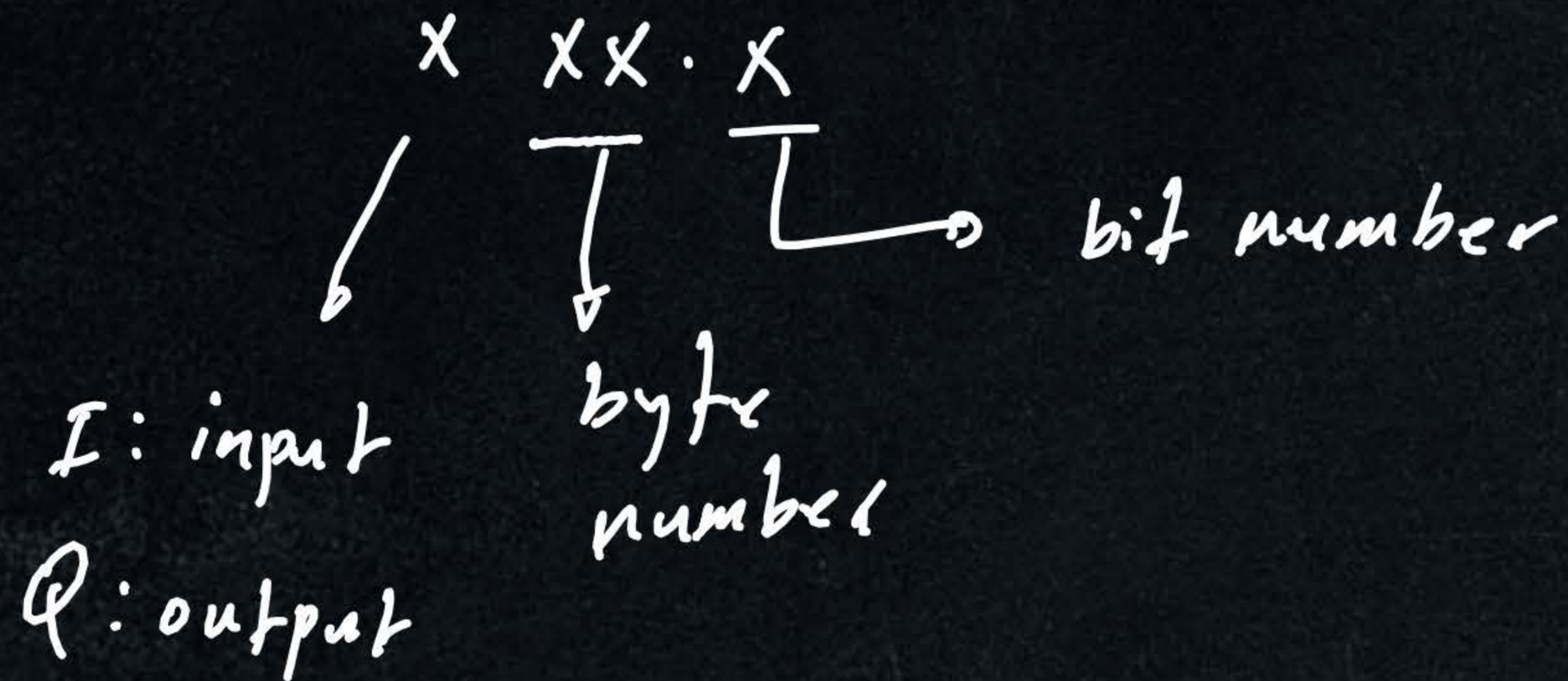The digital I/O is arranged into groups of 8 bits, called a byte. A signal is identified by its bit number (0-7) and its byte number (0-127).




EX: I 0.1 input at bit 1 in byte 0
 Q 2.0 output at bit 0 in byte 2

Logic Functions (LAD)


1) AND

<u>A</u>	<u>B</u>	<u>O</u>
0	0	0
0	1	0
1	0	0
1	1	1


$$O = A \cdot B$$

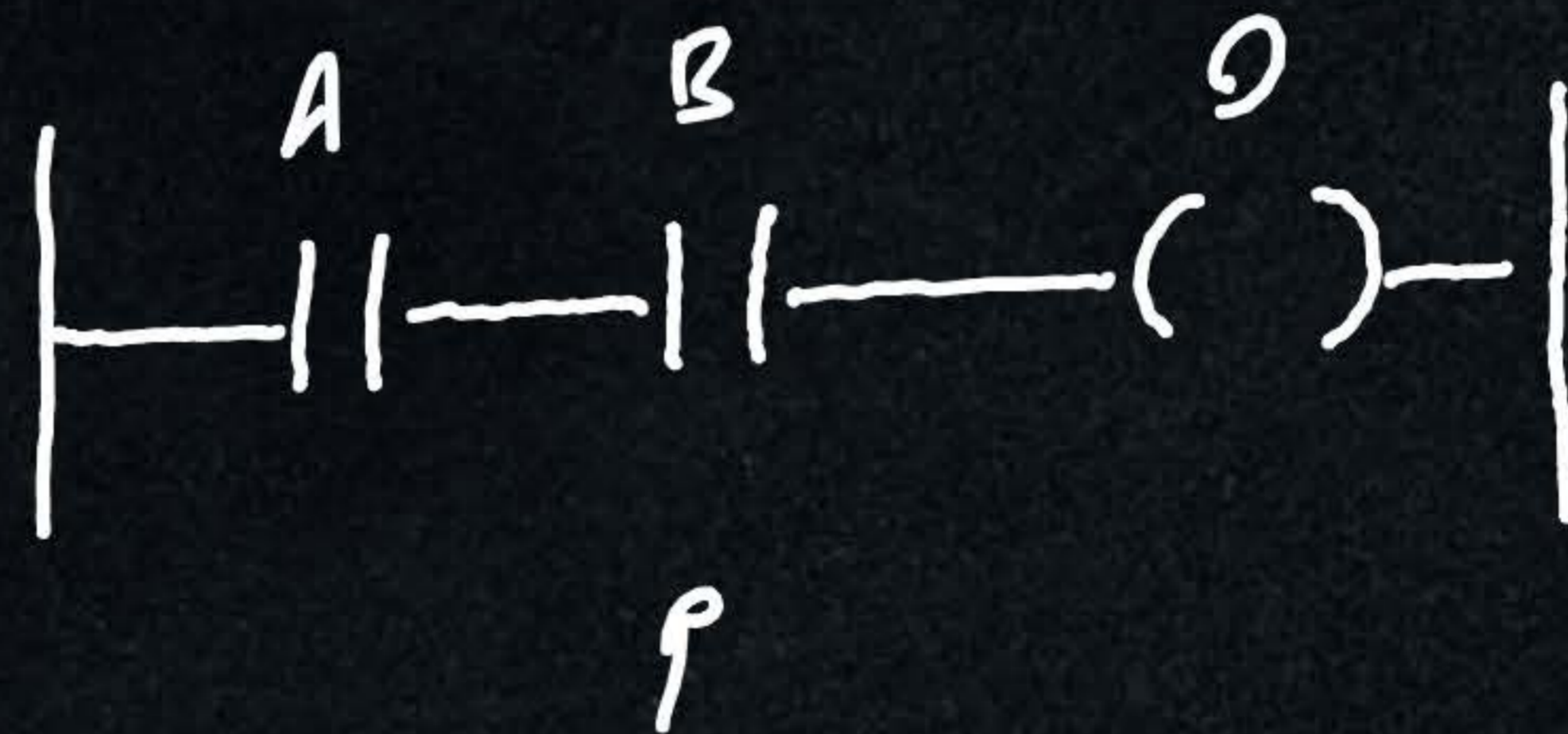

LAD

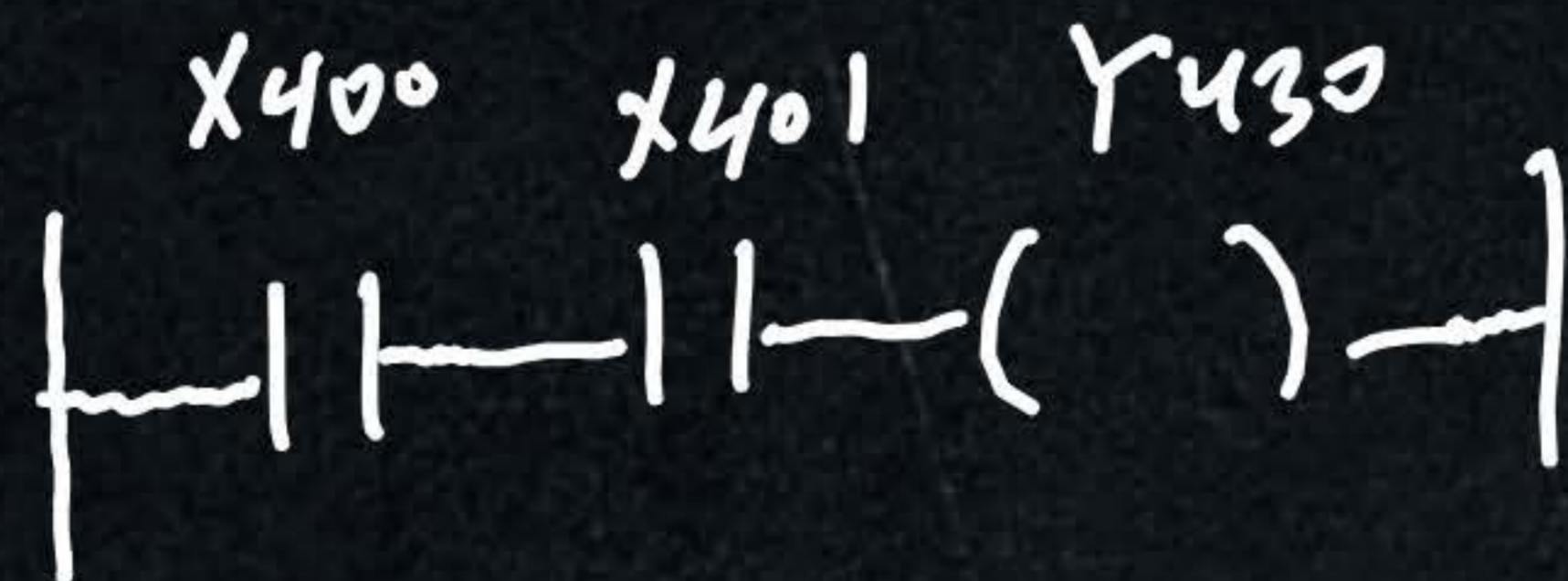


Mitsubishi

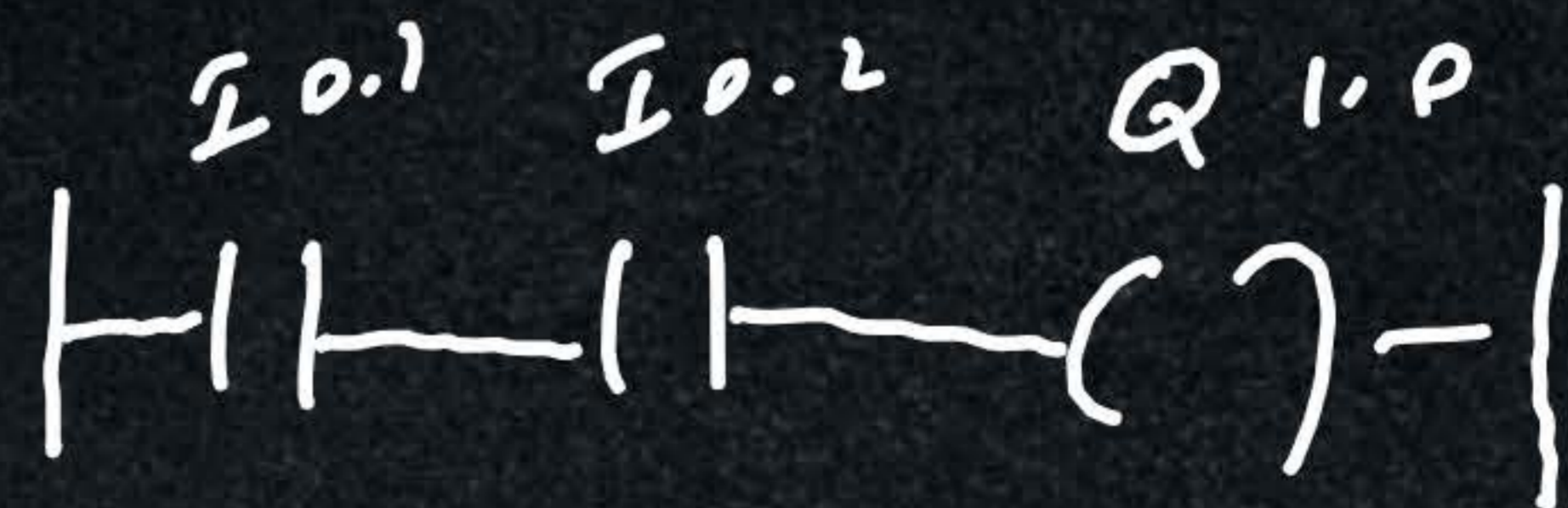


Siemens

2) OR


A	B	O
0	0	0
0	1	1
1	0	1
1	1	1

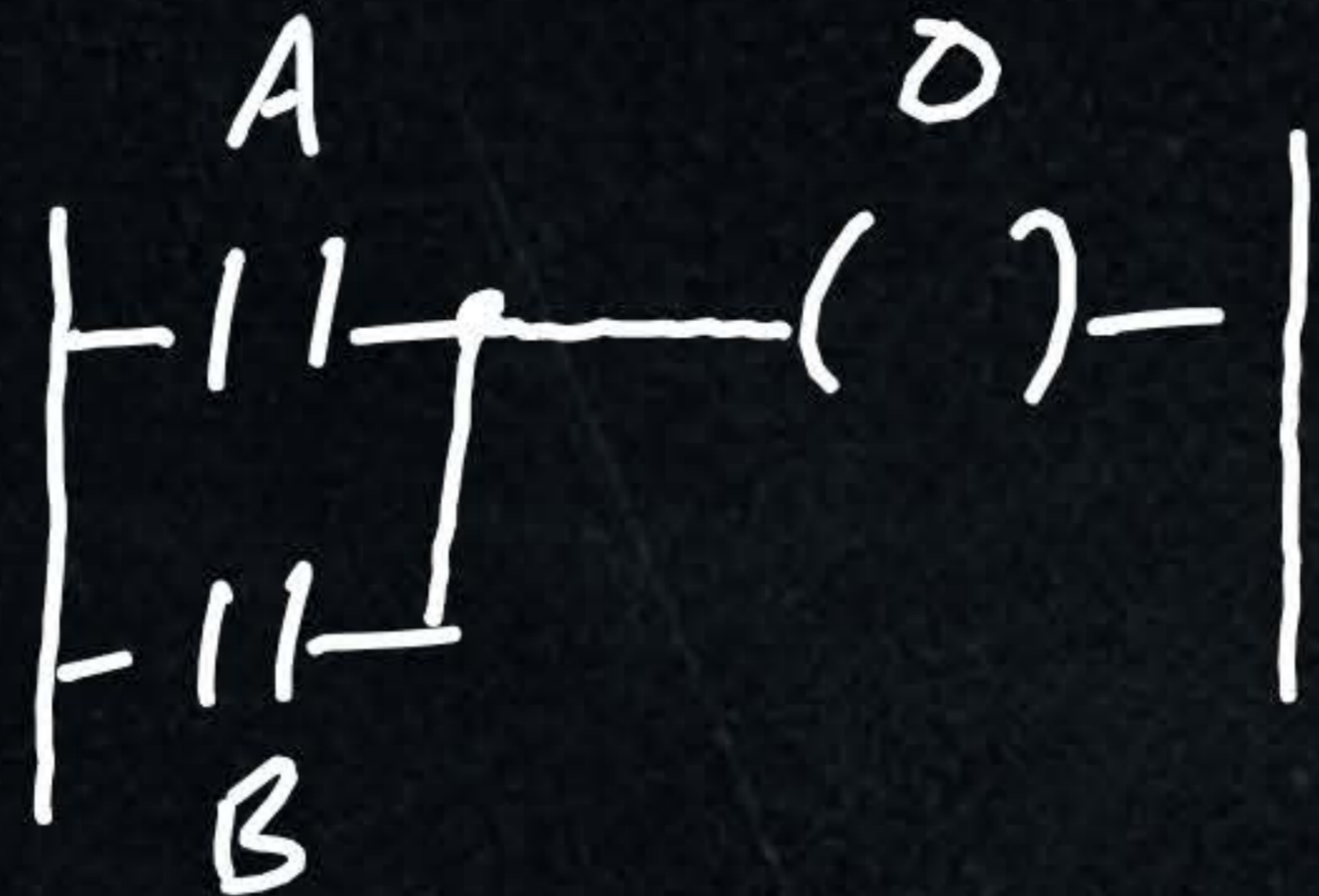

$$O = A + B$$

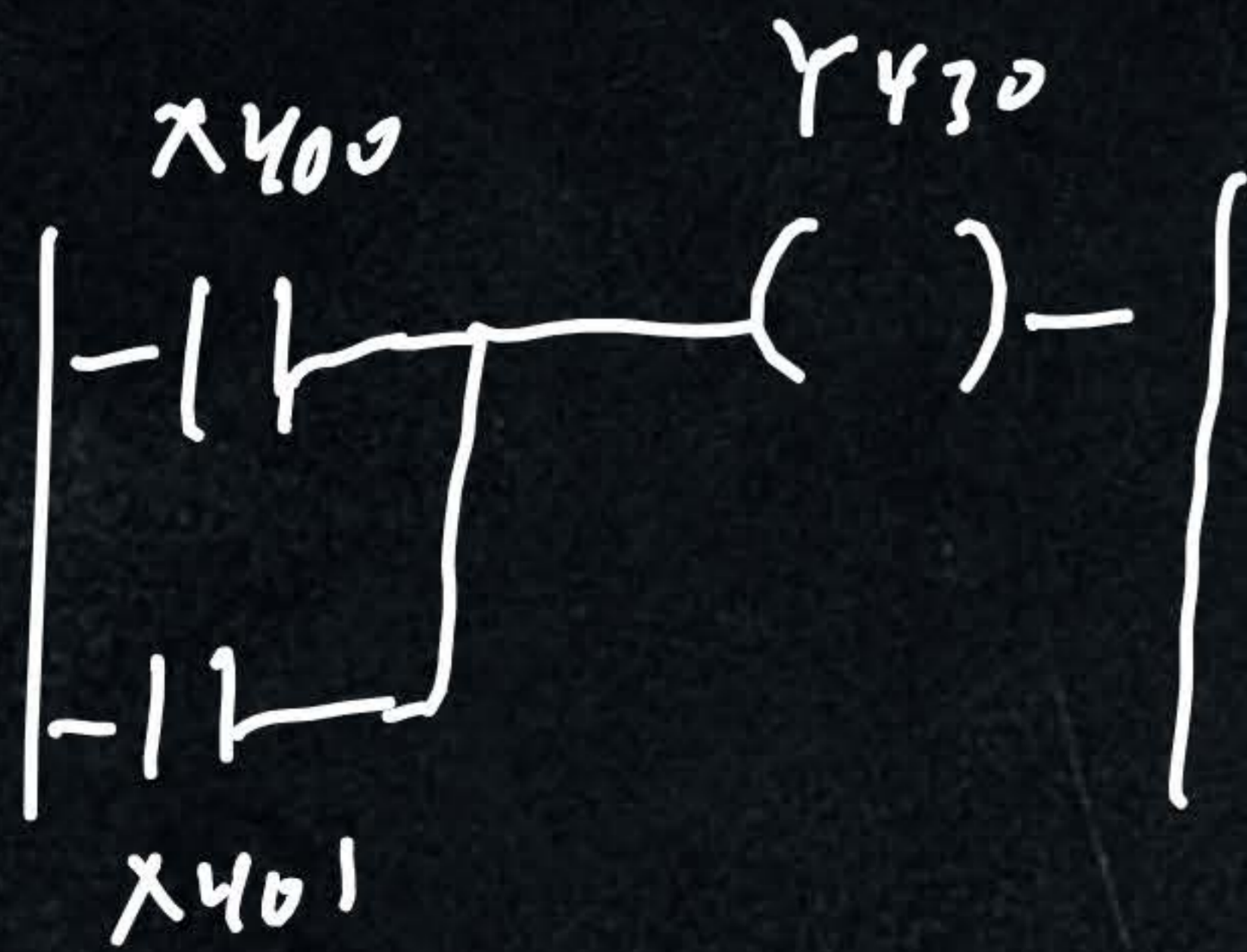

Mitsubishi:



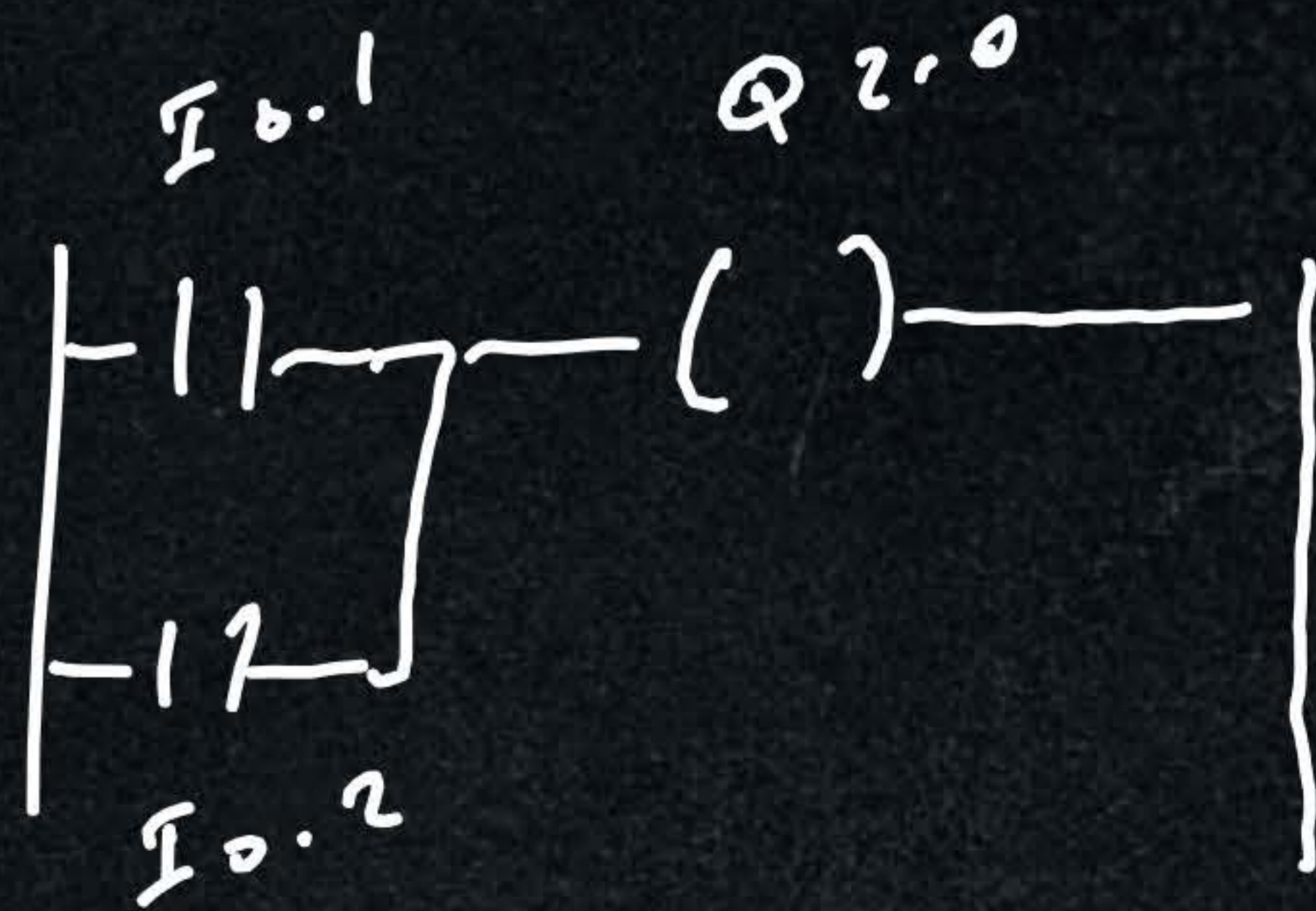


Siemens

3) NOT

A	O
0	1
1	0



$$O = A'$$

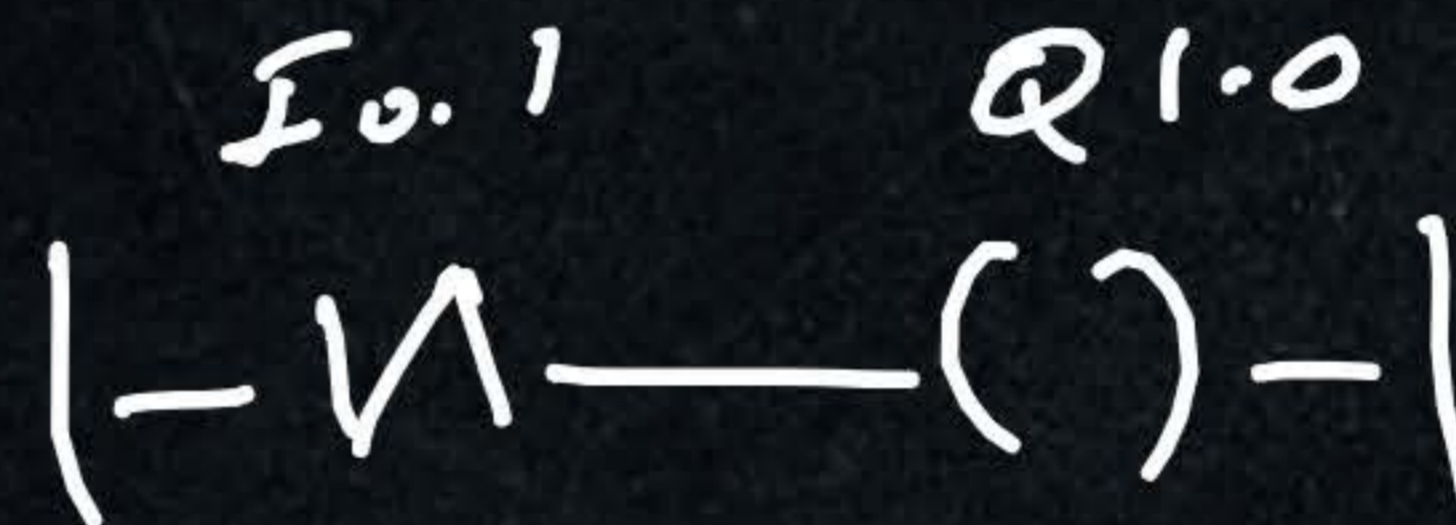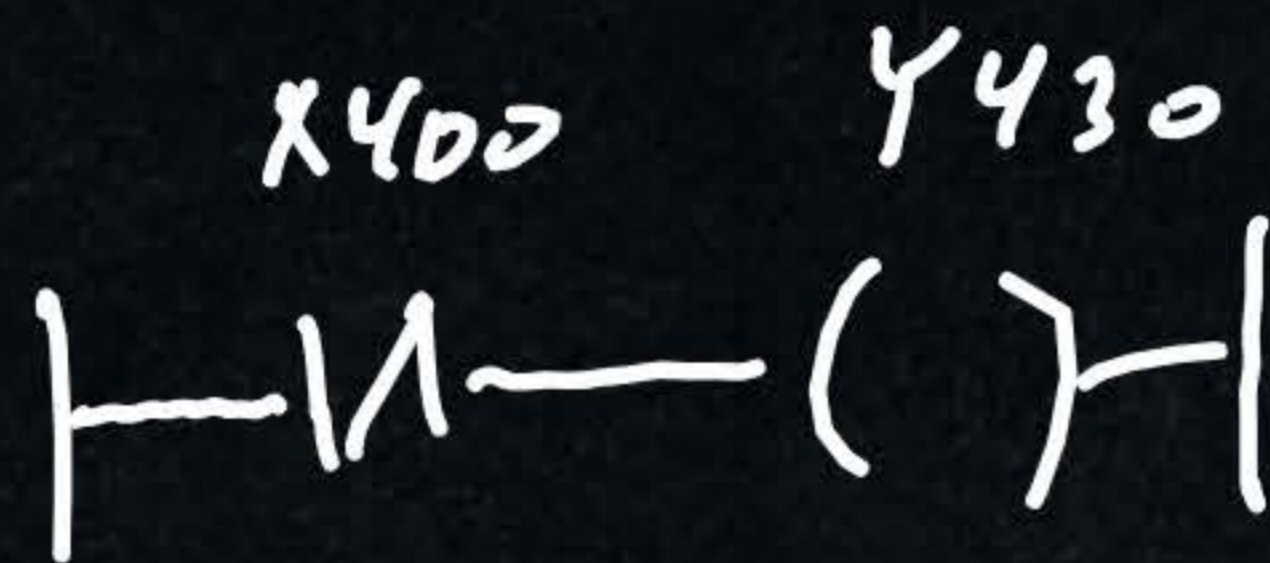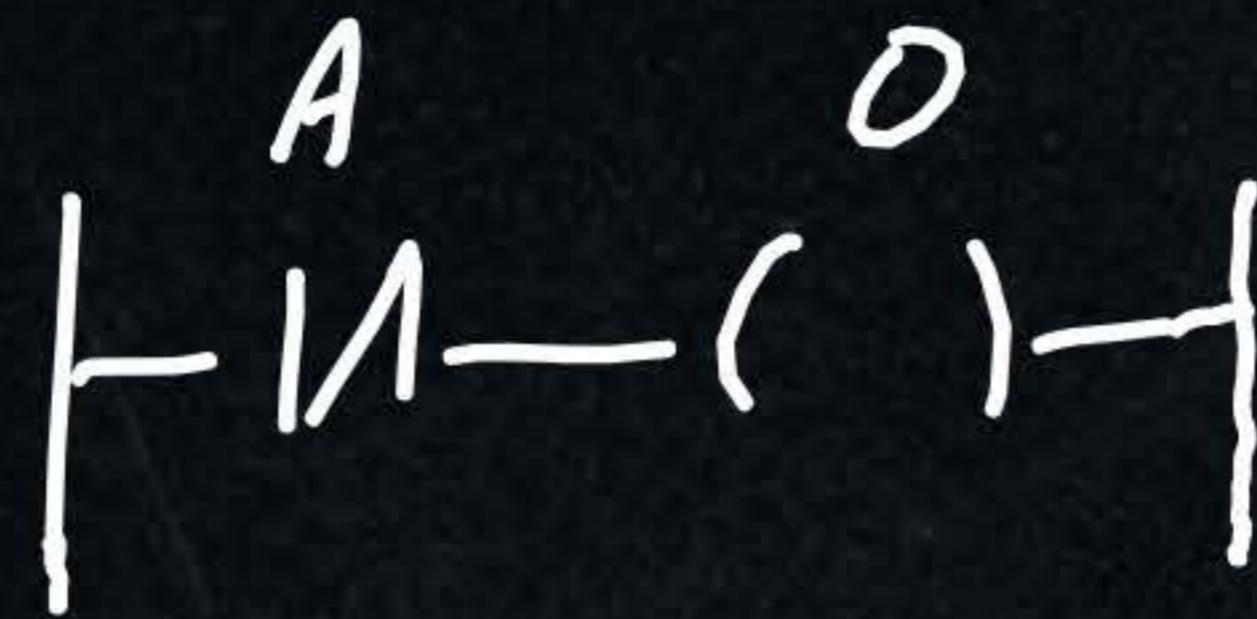

3) NAND

A	B	O
0	0	1
0	1	1
1	0	1
1	1	0




$$O = (AB) = A' + B'$$

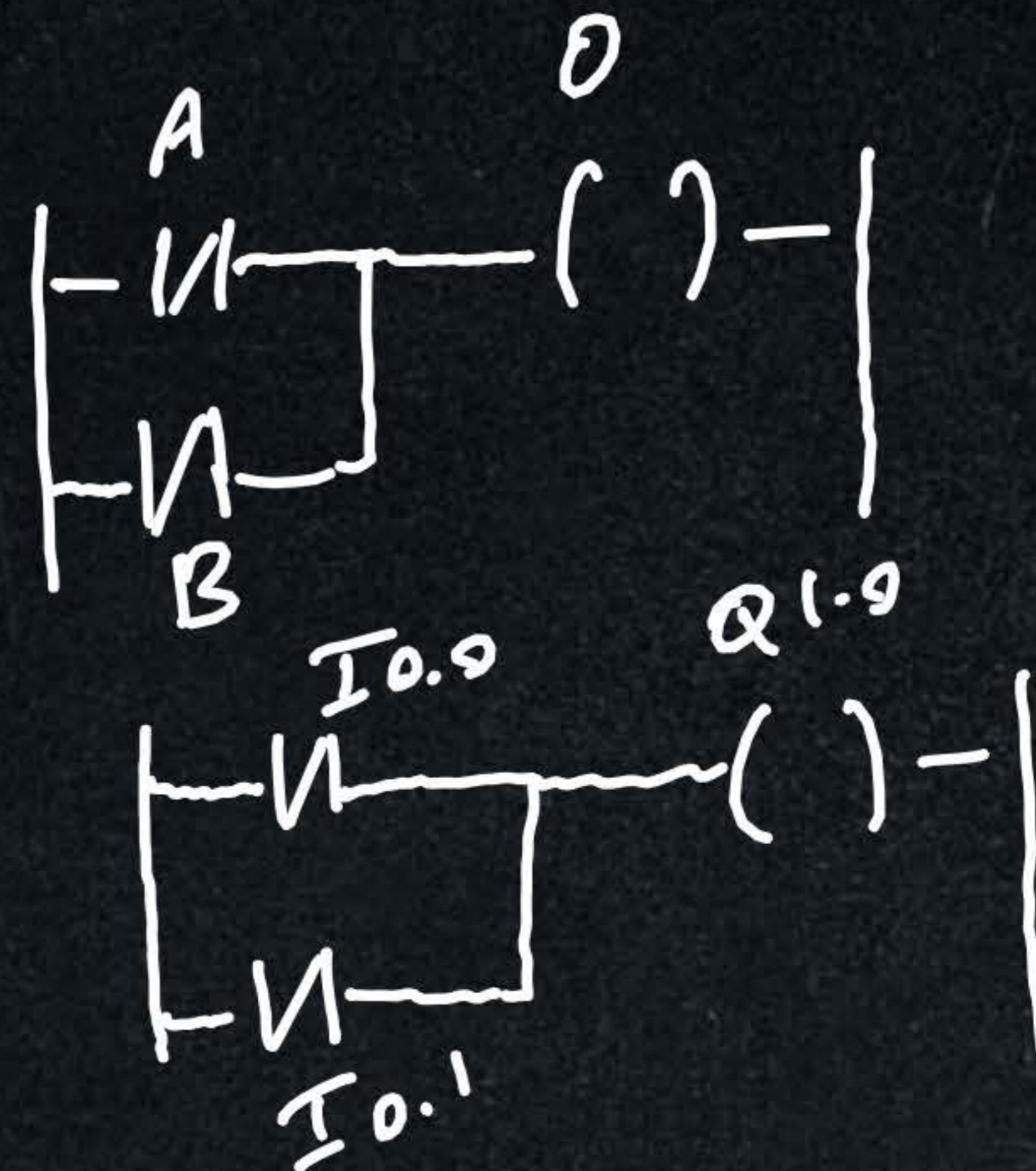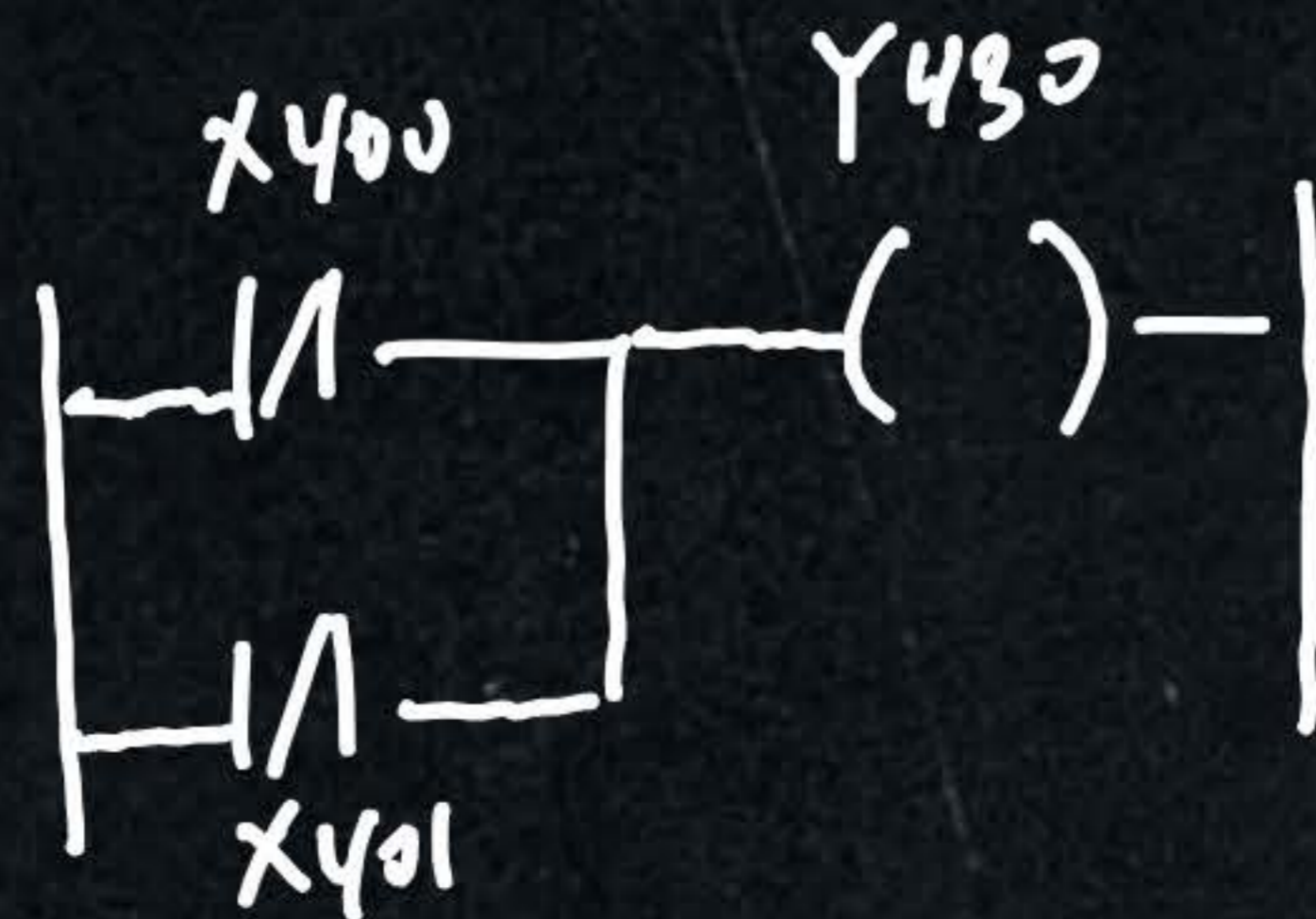

4) NOR

$$O = (A + B)' = A'B'$$



A	B	O
0	0	1
0	1	0
1	0	0
1	1	0

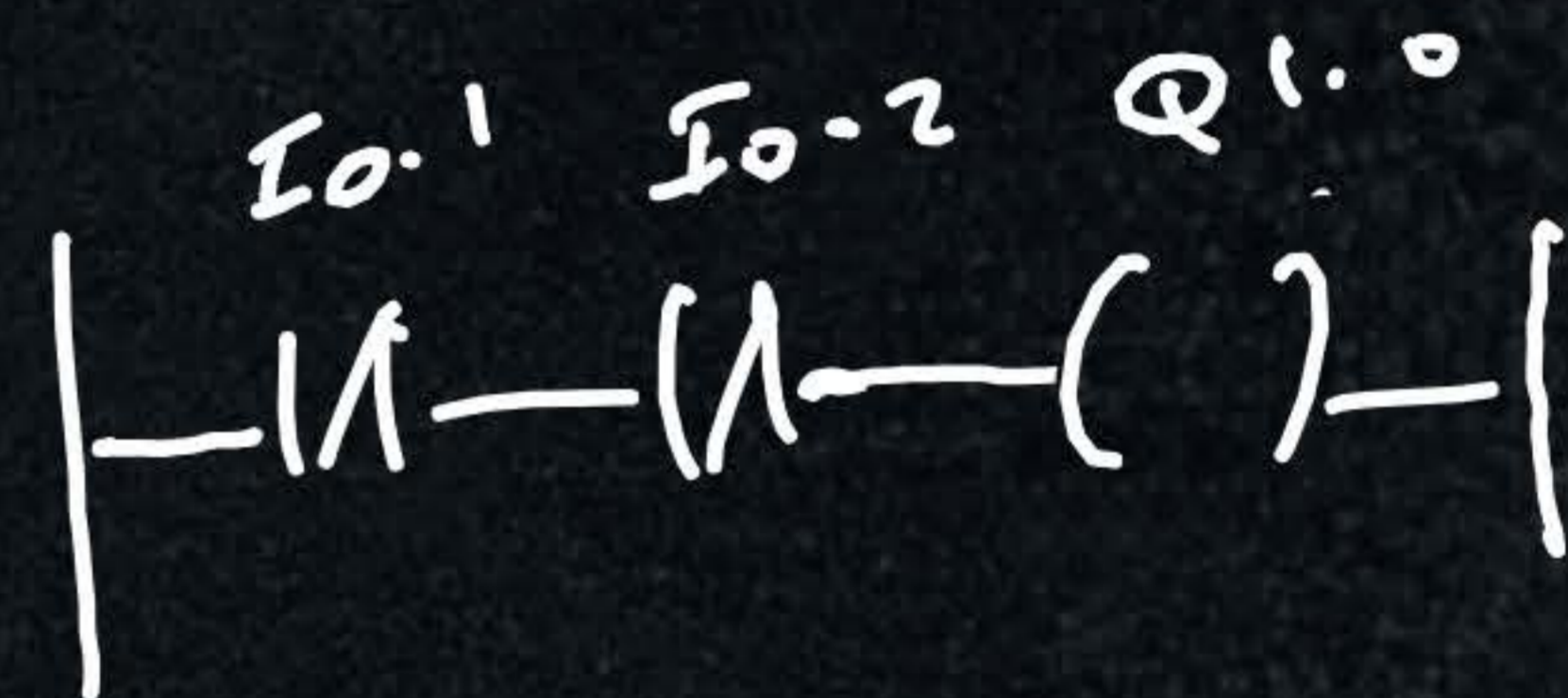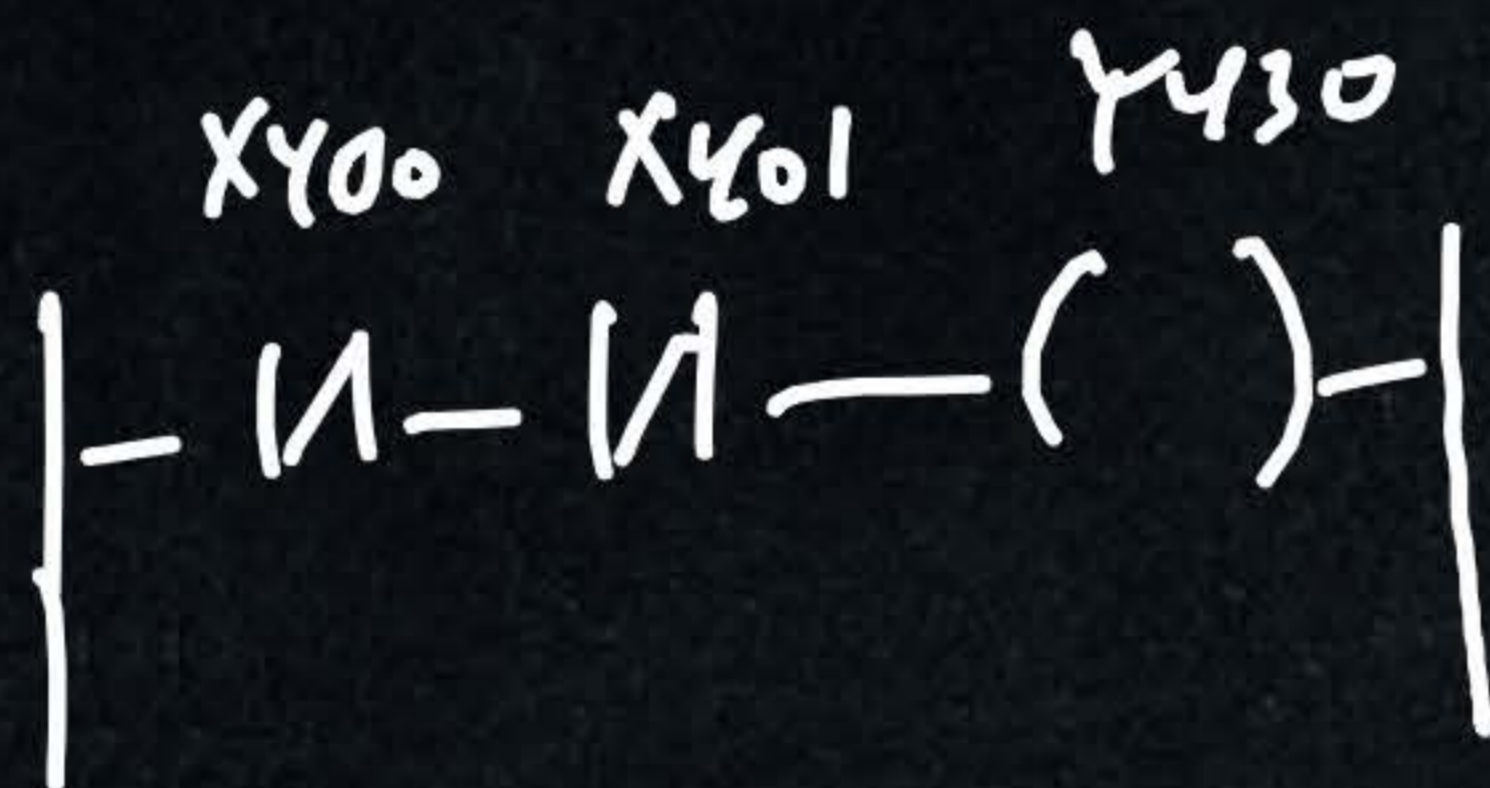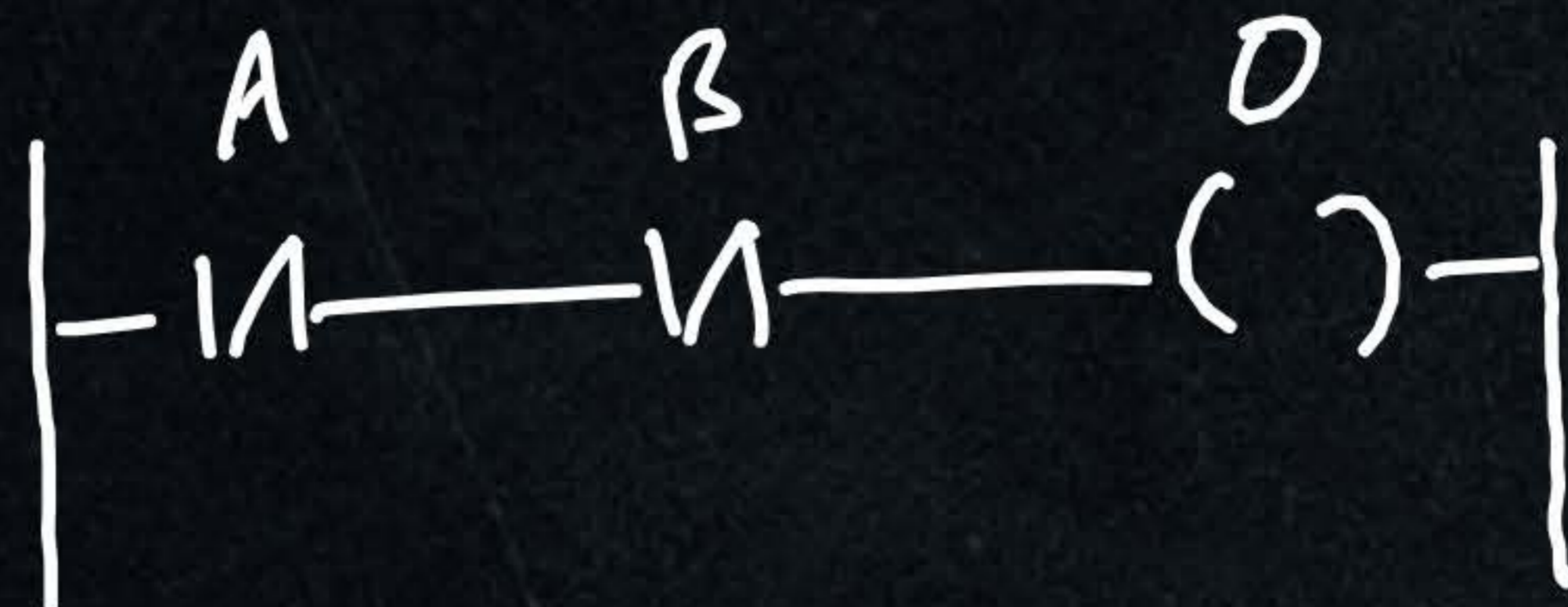





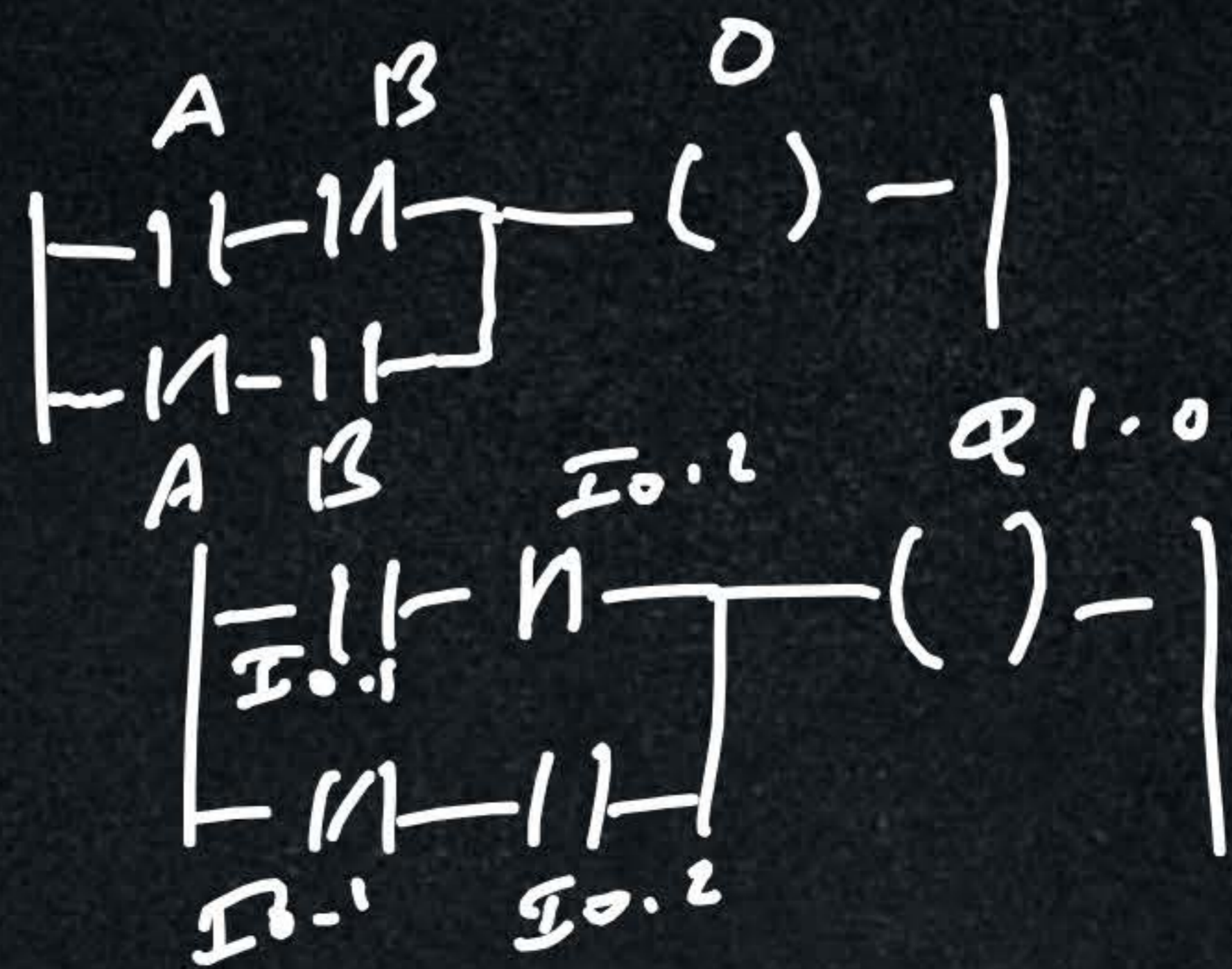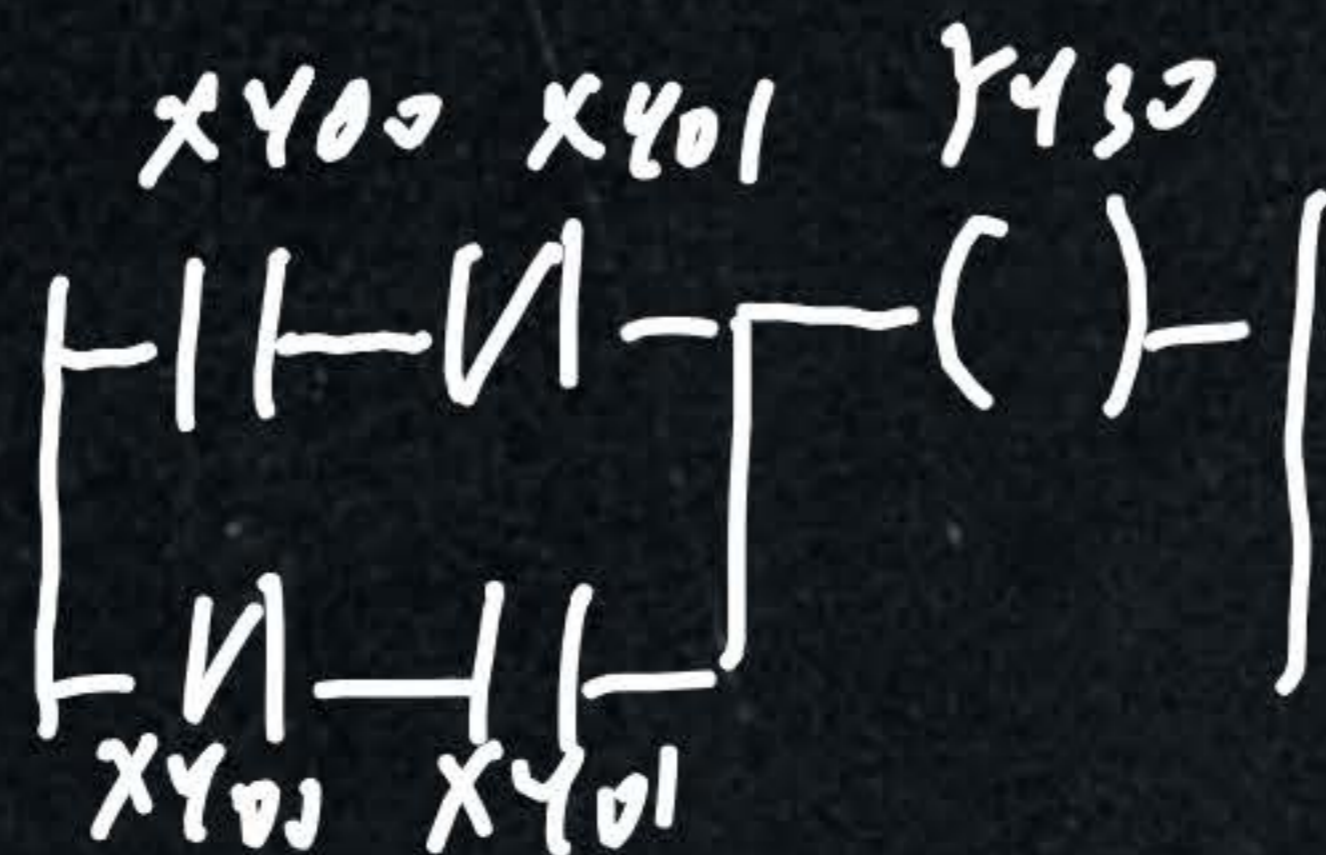

5) XOR

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

$$O = AB' + A'B$$



Logic Functions (FBD)


Function	FBD
AND	
OR	
NOT	
NAND	
NOR	
XOR	

IL Programming


<u>Mitsubishi</u>	<u>Siemens</u>	
LD	A	start a rung with open contacts
LDI	AN	" " " " closed "
AND	A	series element with open contacts
ANI	AN	" " " " closed "
OR	O	parallel element with open contacts
ORI	ON	" " " " closed "
OUT	=	An output

Logic Functions (IL)

1) OR

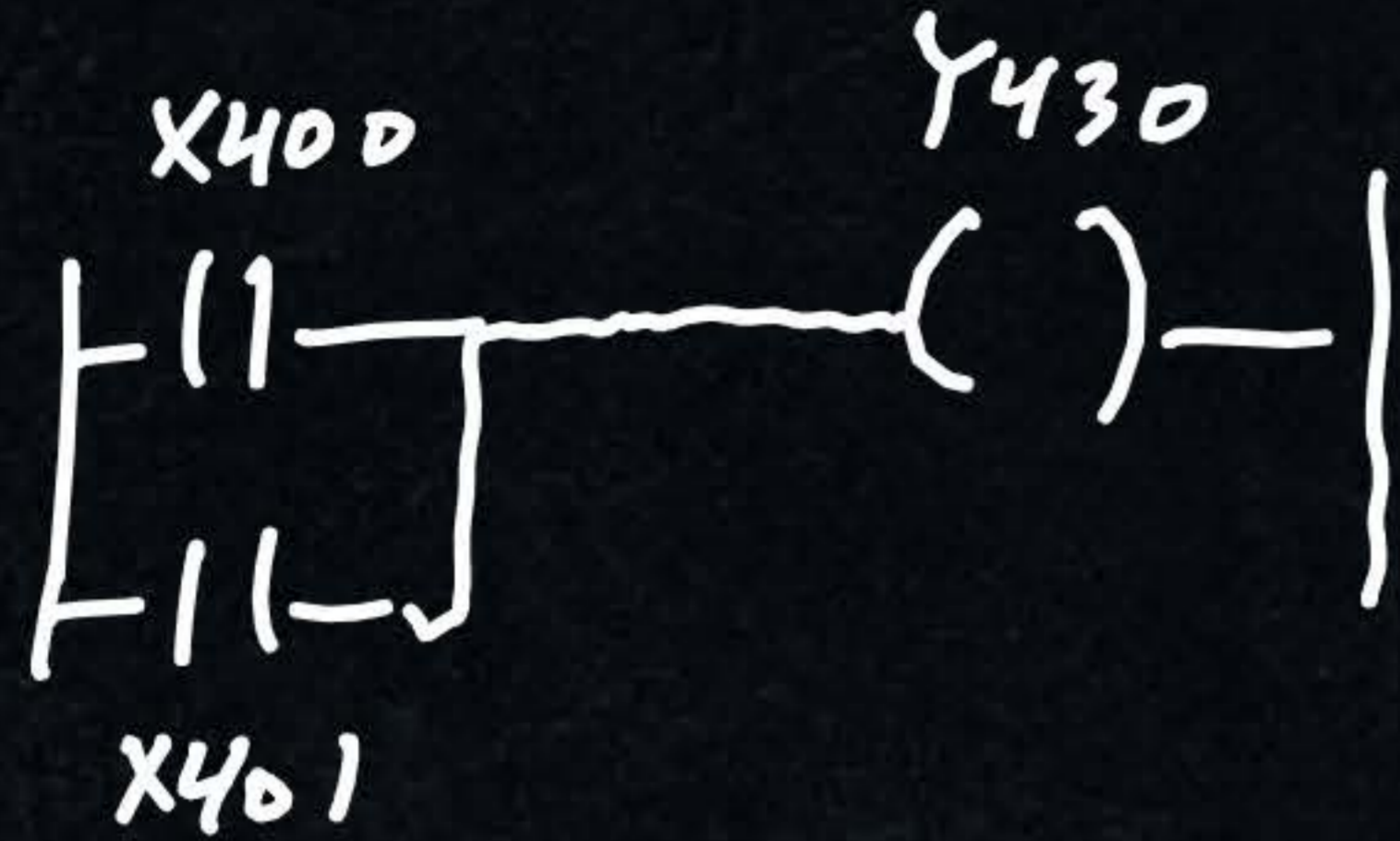


```
LD X 400  
OR X 401  
OUT Y 430
```

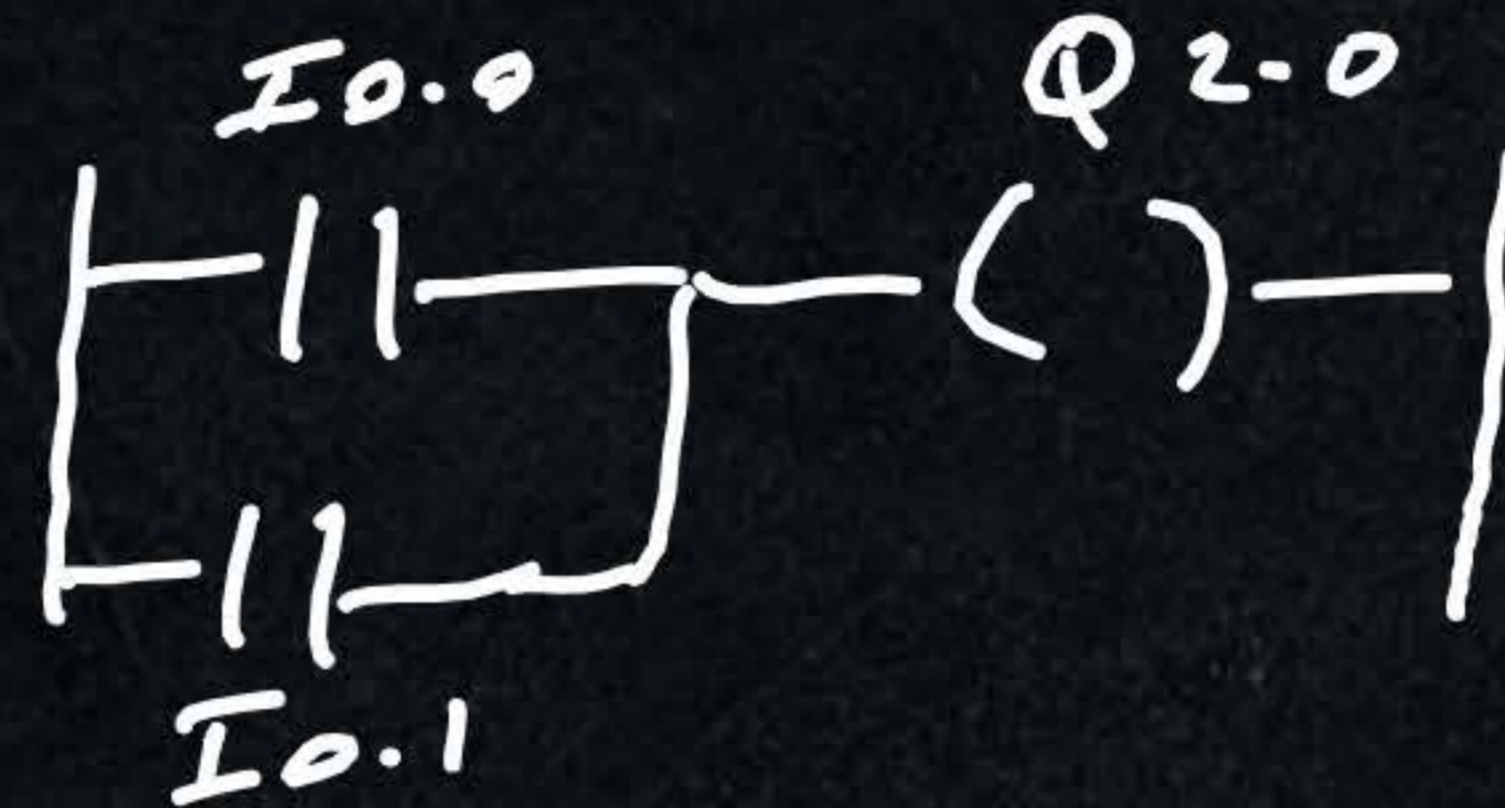


```
A I 0.0  
O I 0.2  
= Q 2.0
```

2) AND

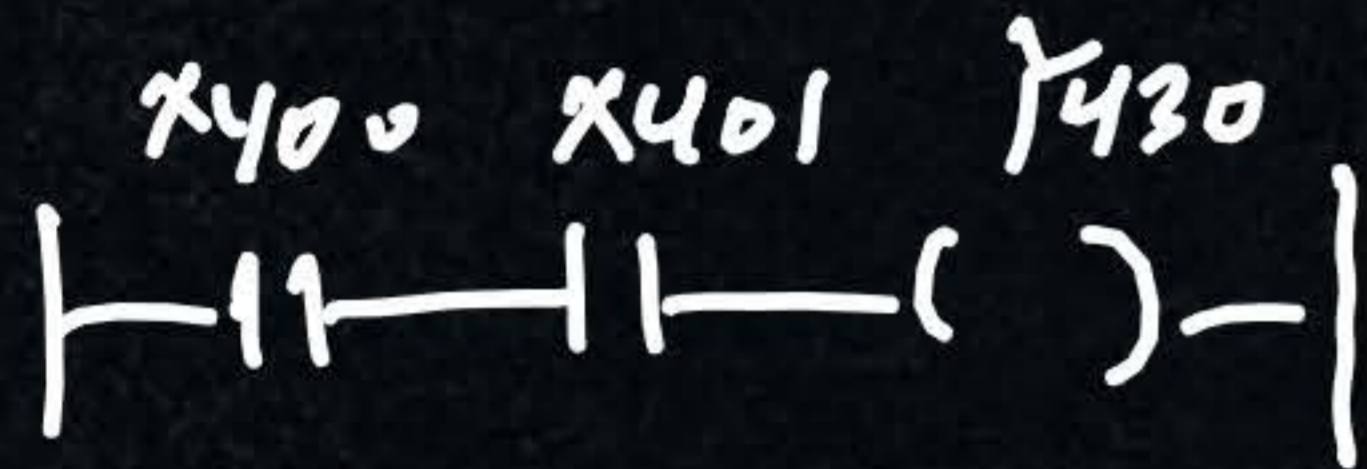


LD X400
AND X401
OUT Y430

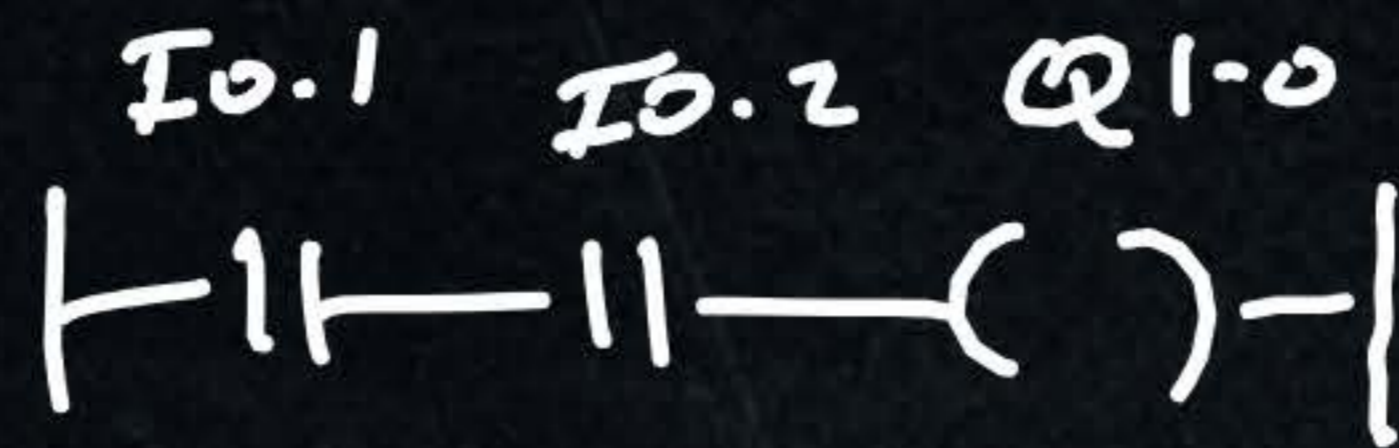


A I0.1
A I0.2
= Q1.0

3) NOR

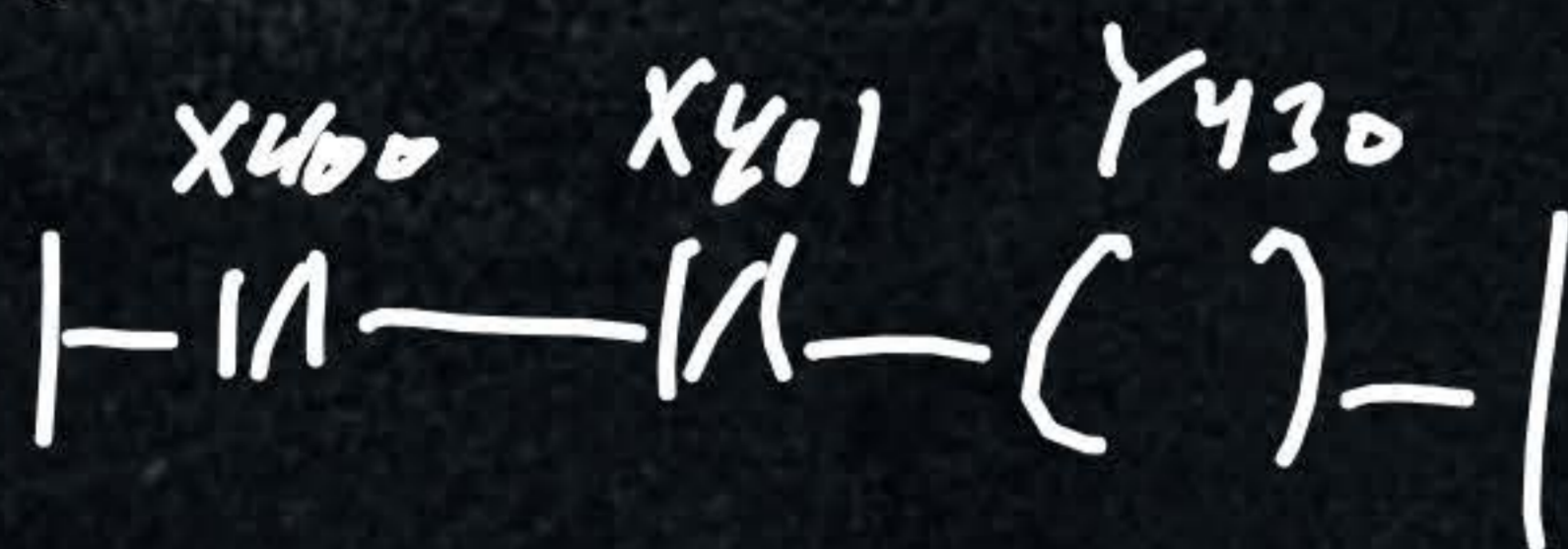


LDI X400
ANI X401
OUT Y430.

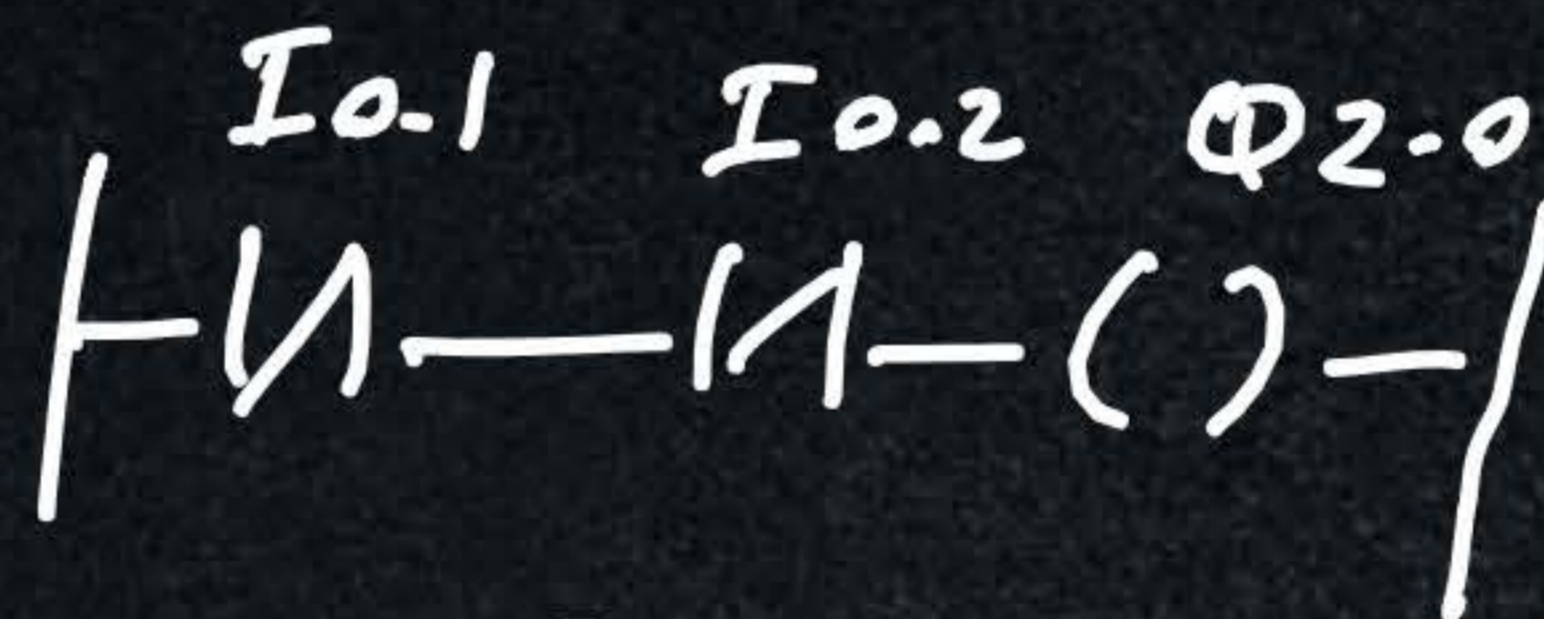


AN I0.1
AN I0.2
= Q2.0

4) NAND

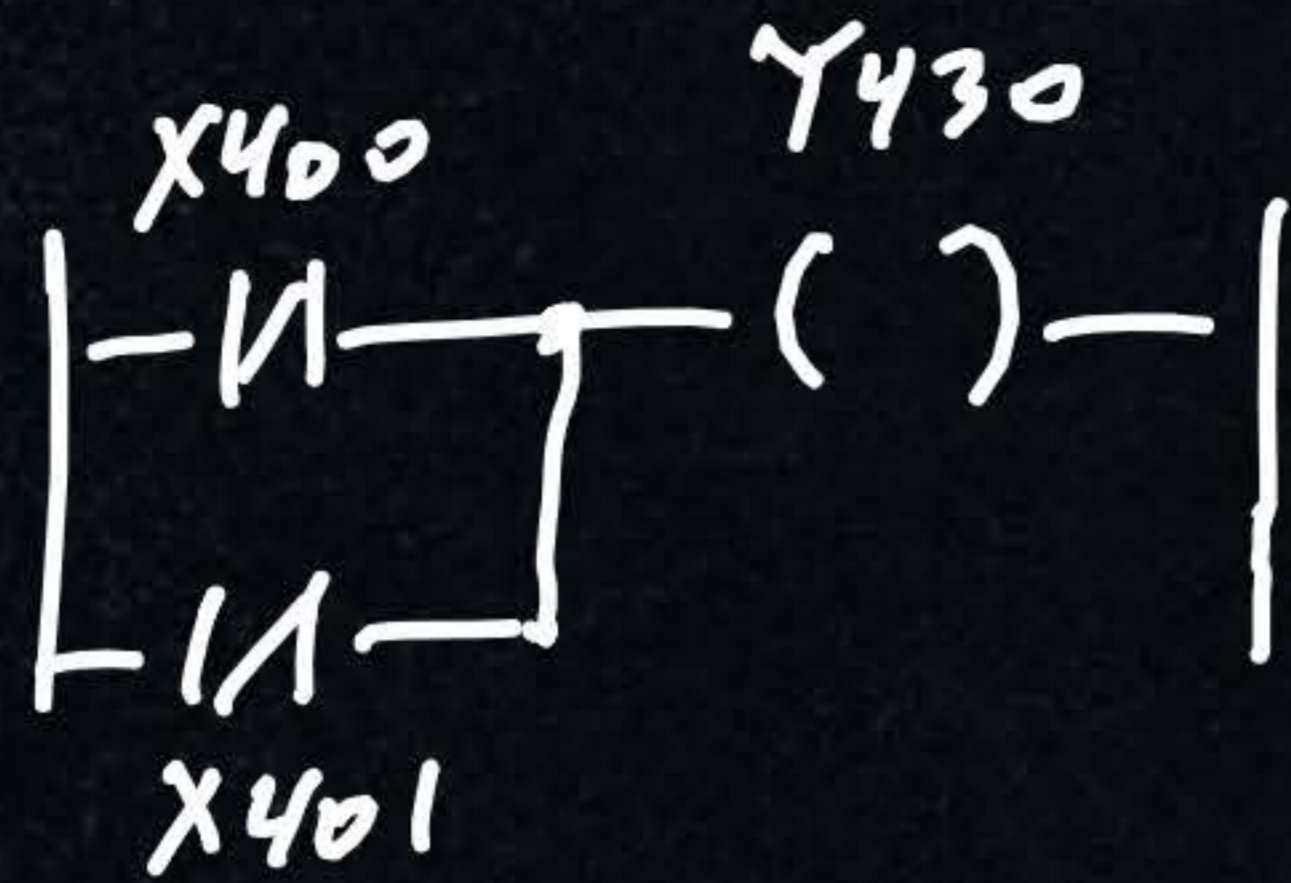


```
LDI X400  
ORI X401  
OUT Y430
```

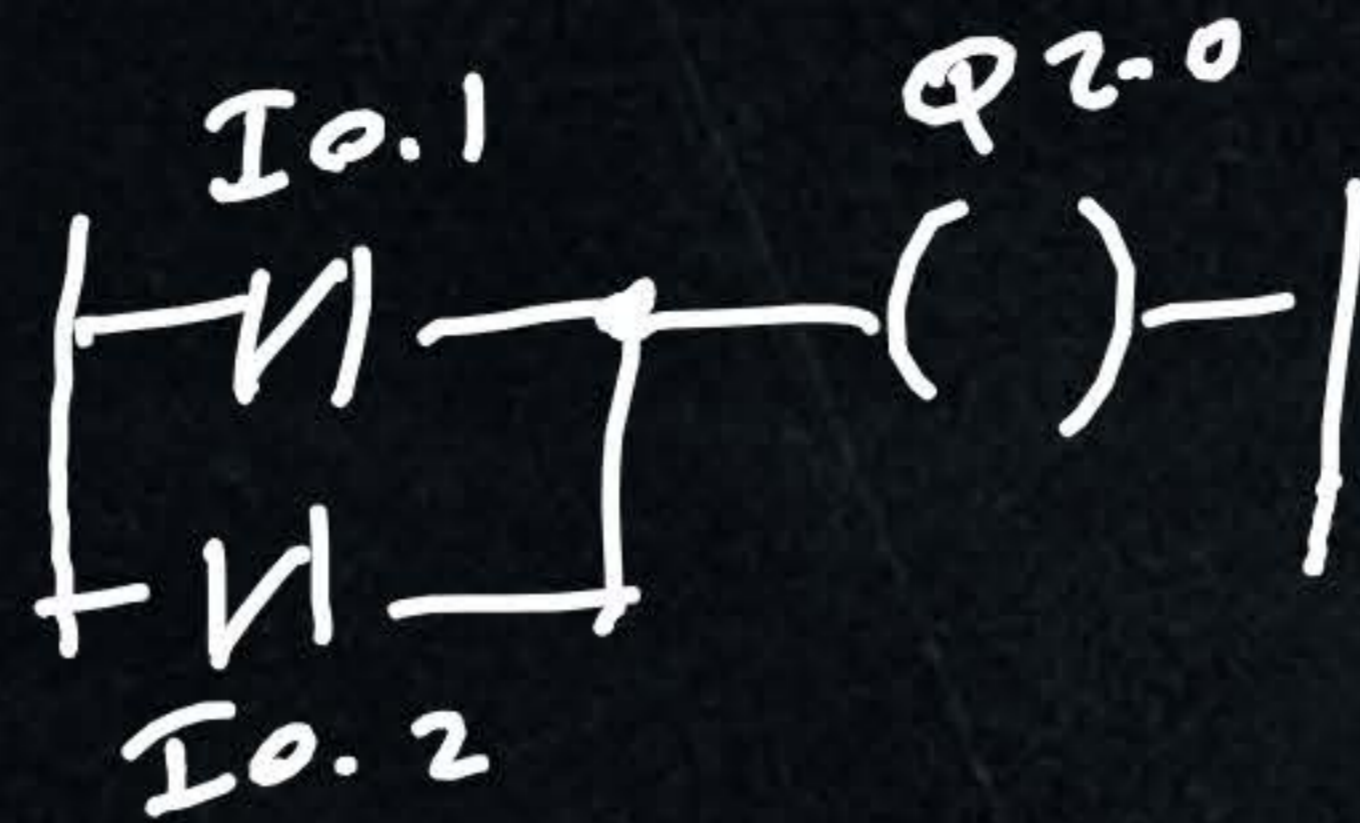


```
ANI I0.1  
ON I0.2  
= Q2.0
```

5) XOR

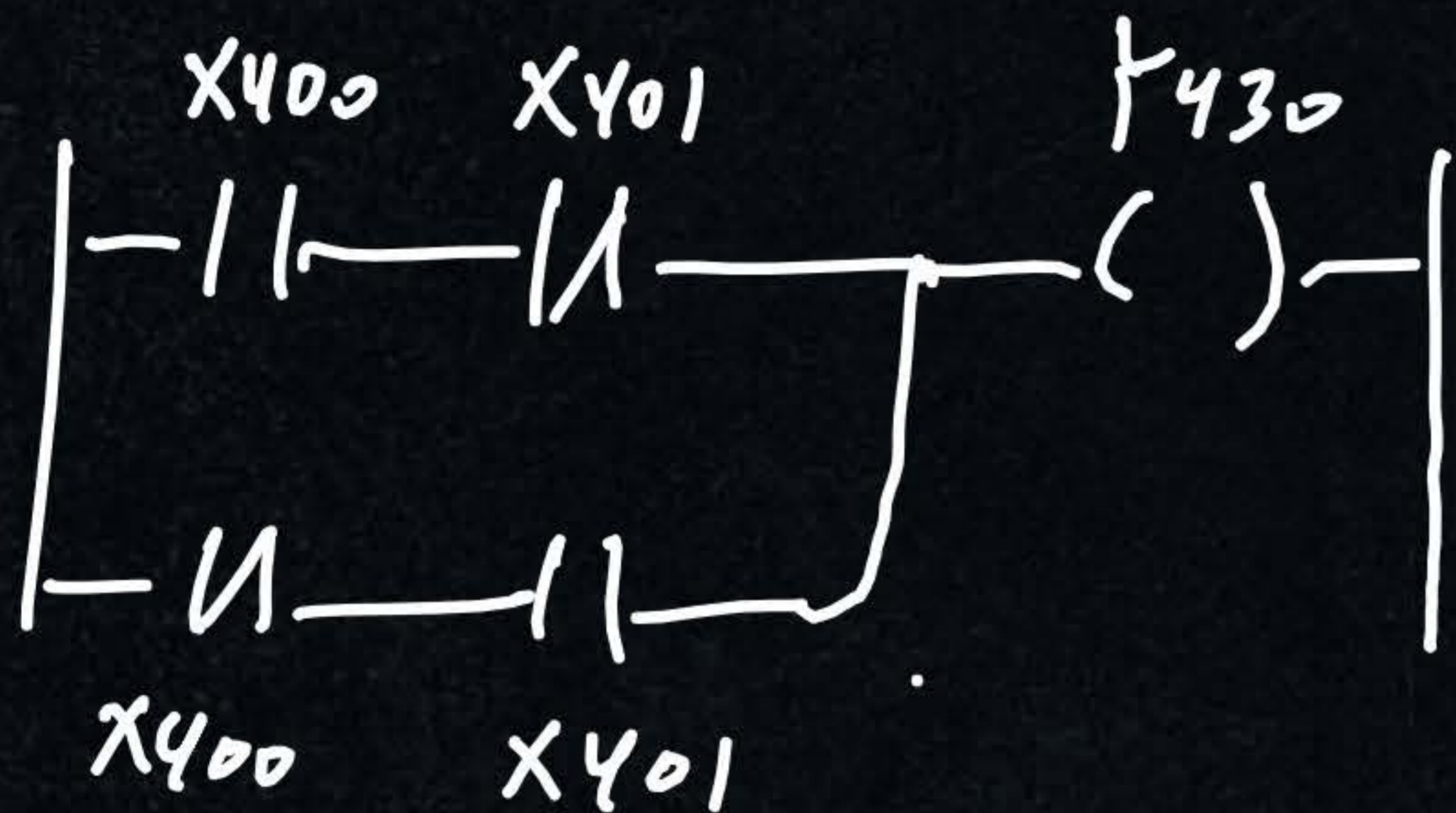
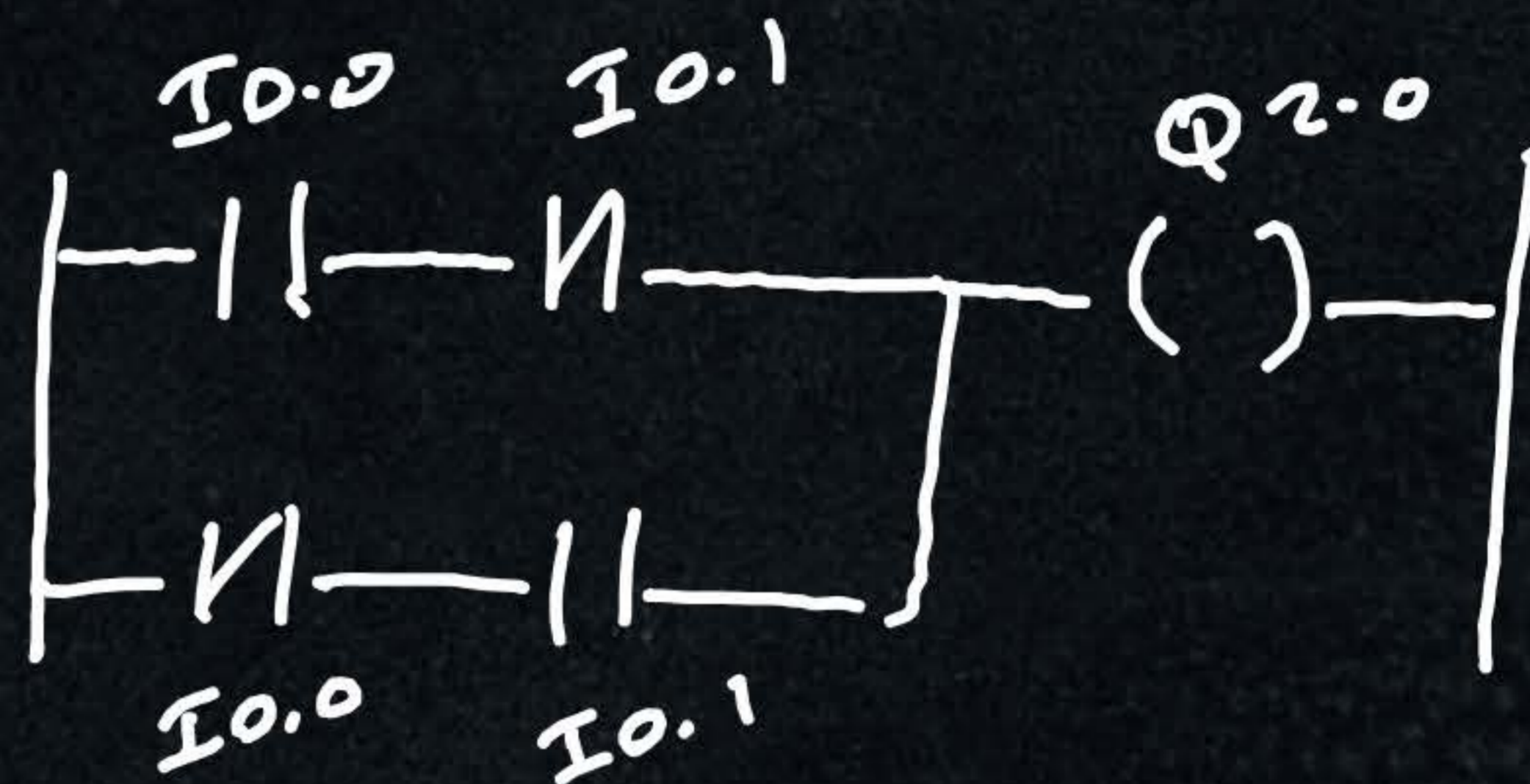
```
LD X400
ANI X401
LDI X400
AND X401
ORB
OUT Y430
```



```
A (
  A I0.0
  AN I0.1
)
O (
  AN I0.0
  A I0.1
)
=Q 2.0.
```


Example: γ - Δ starter of 3 ϕ IM using RLC

L-L
RMS voltage
supply
400V

$$I_Y = \frac{\text{phase voltage}}{R}$$


$$I_Y = \frac{V/\sqrt{3}}{R}$$

$$I_\Delta = \frac{\text{phase voltage}}{R}$$



$$I_\Delta = \frac{V}{R}$$



$$\frac{I_Y}{I_\Delta} = \frac{1}{\sqrt{3}} \Rightarrow I_Y = \frac{1}{\sqrt{3}} I_\Delta$$

$$T_{el,Y} = \frac{1}{3} T_{el,\Delta}$$

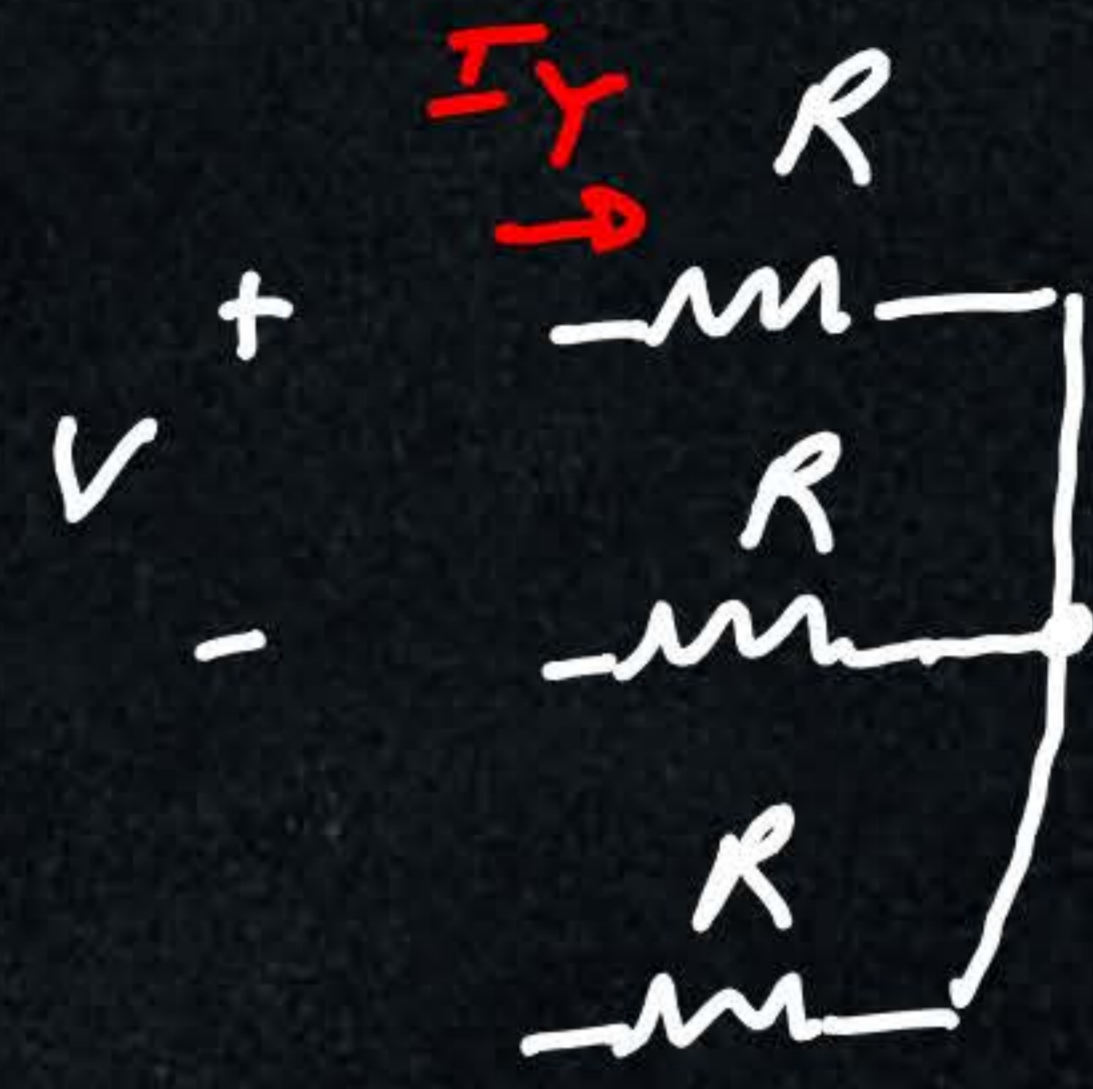


✓ 400/680 V
Y
✗ 230/400 V
Y

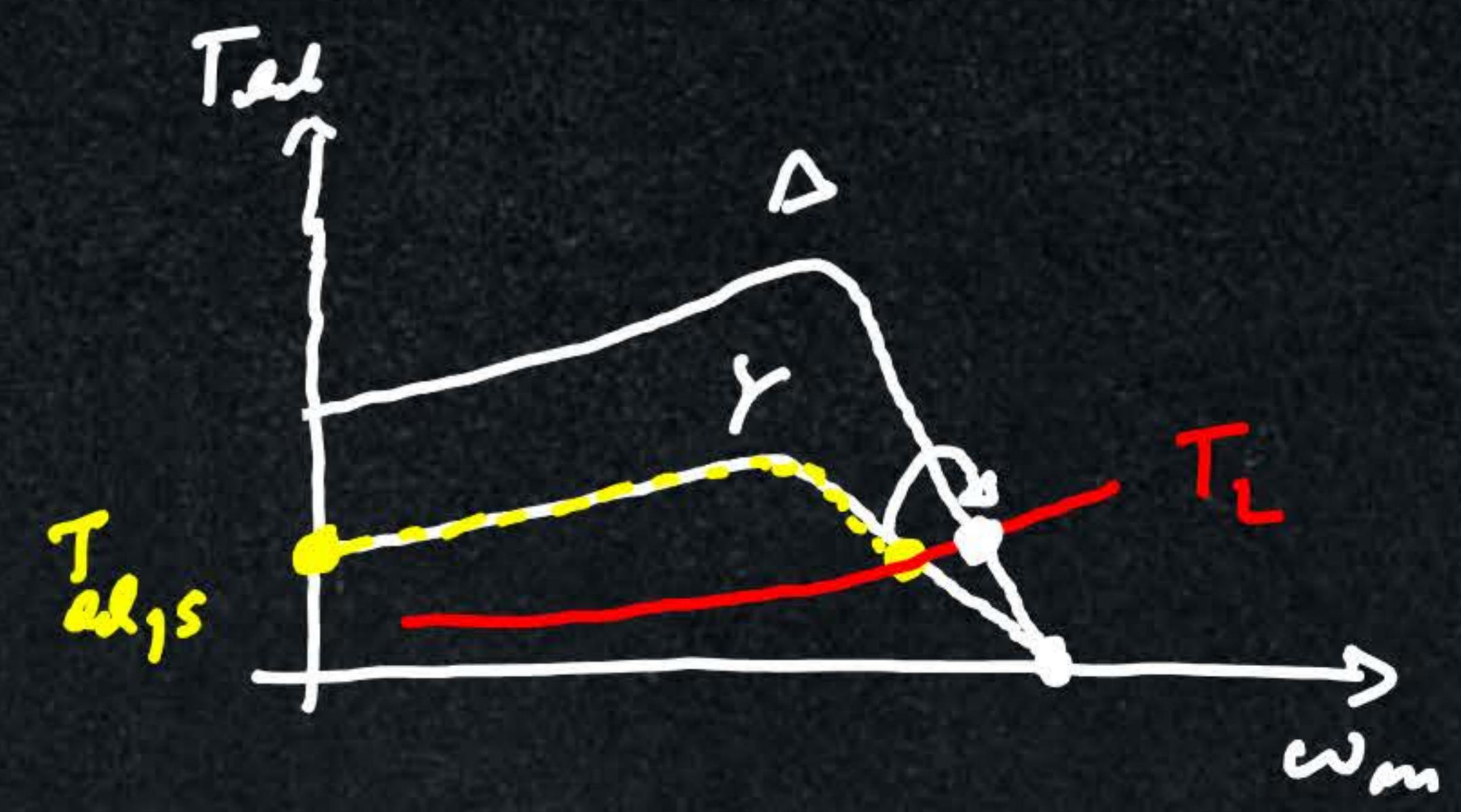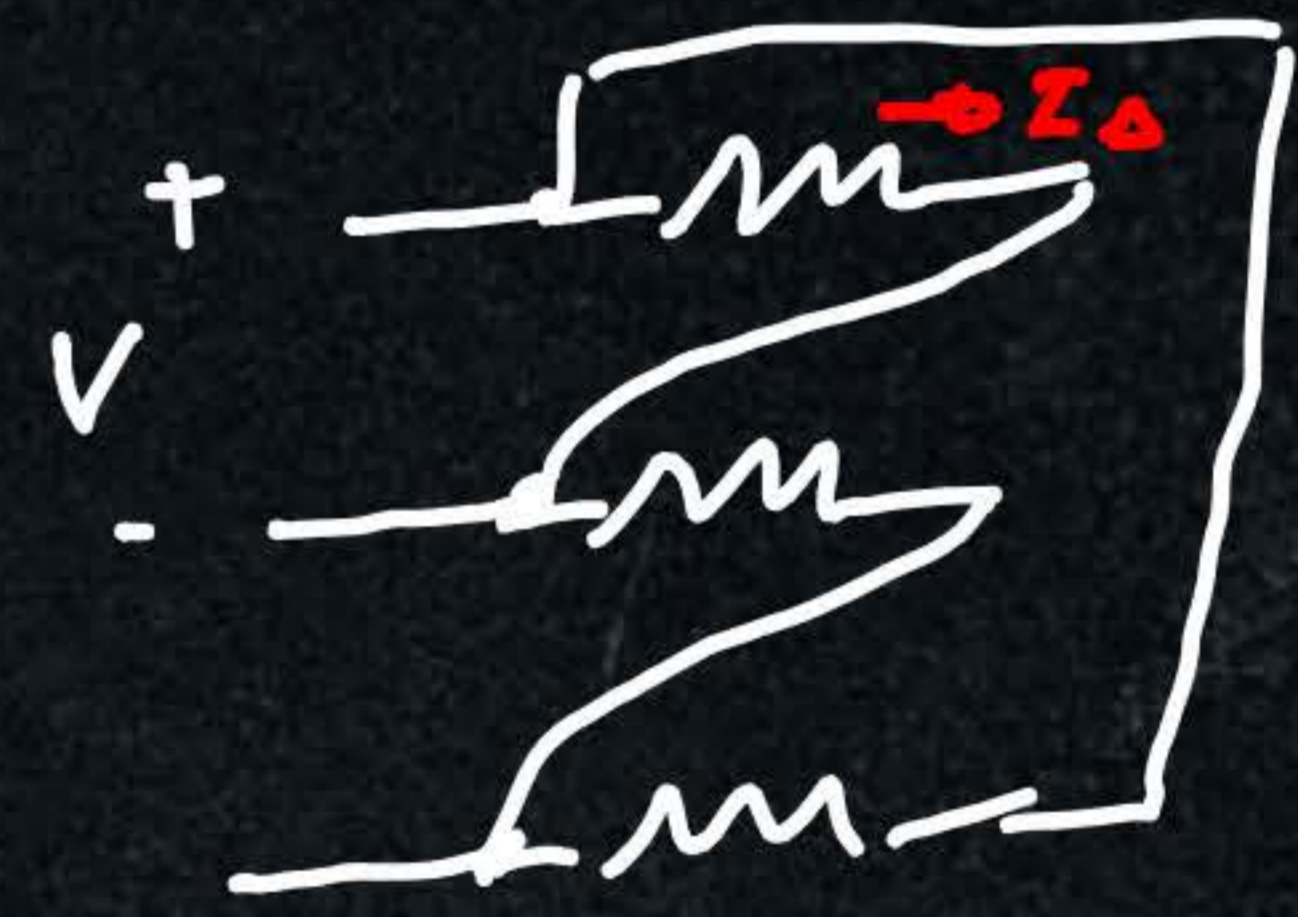

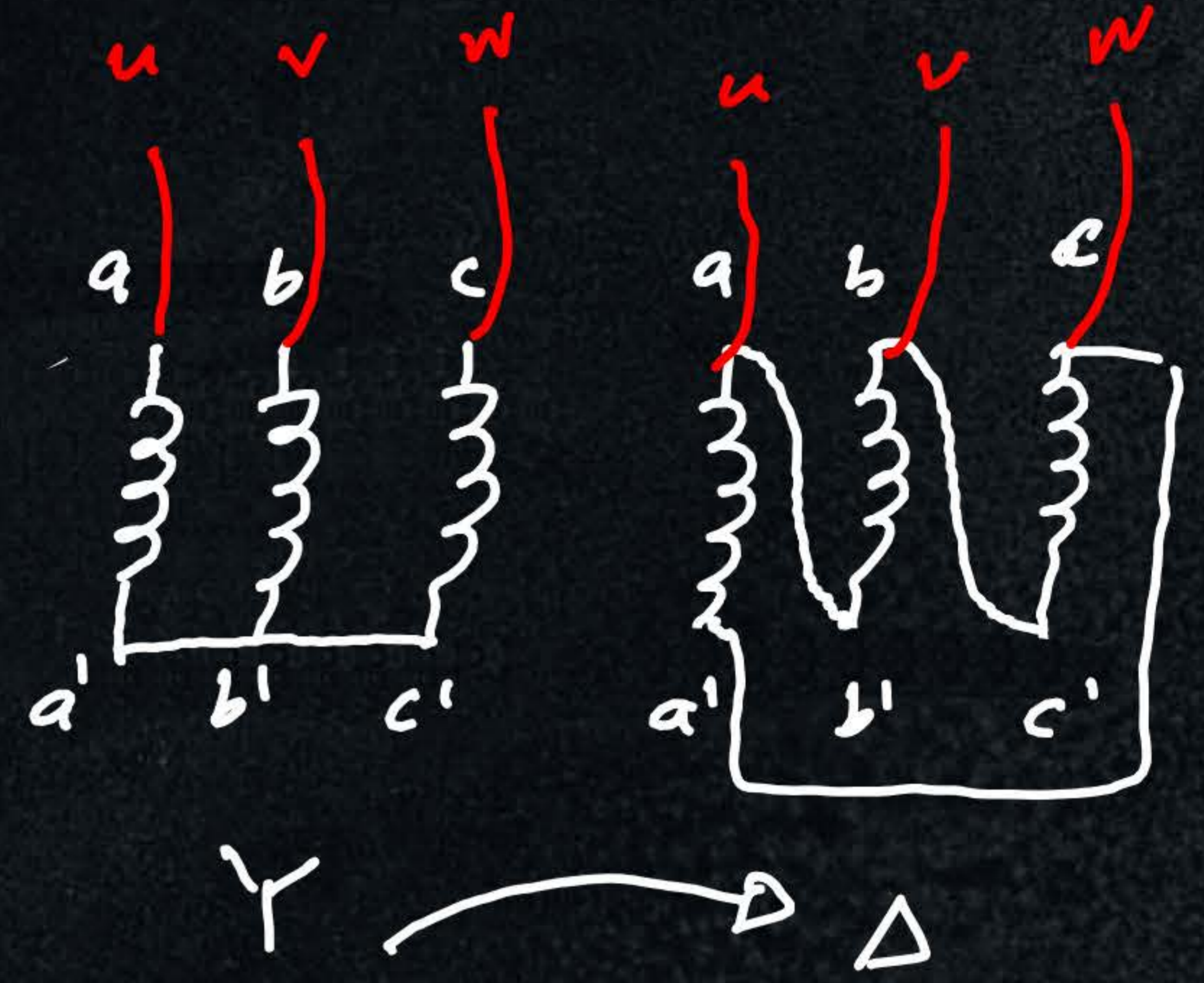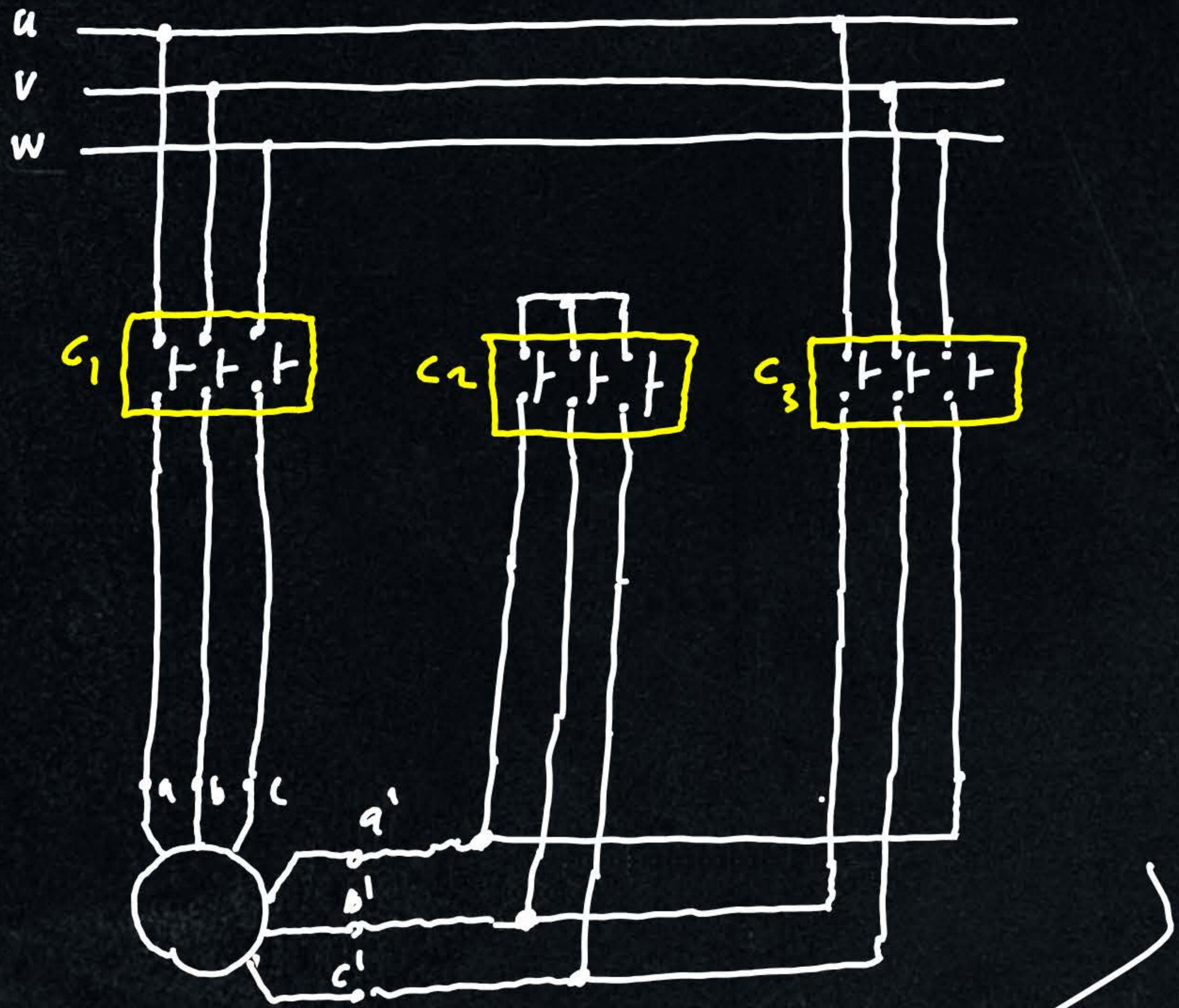

power circuit: 2



Control Circuit

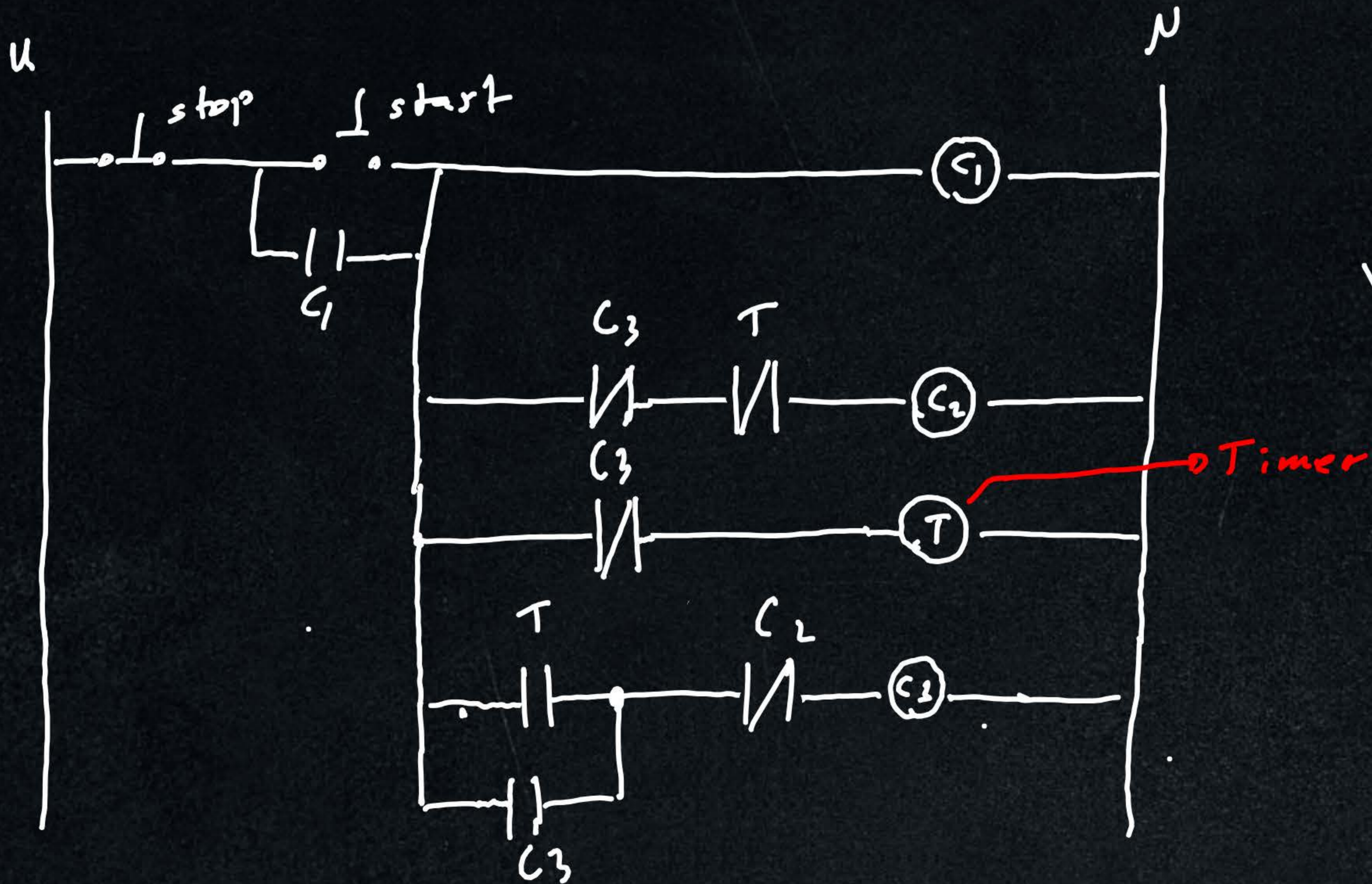


Internal Relay




Energizing coil activate the contacts

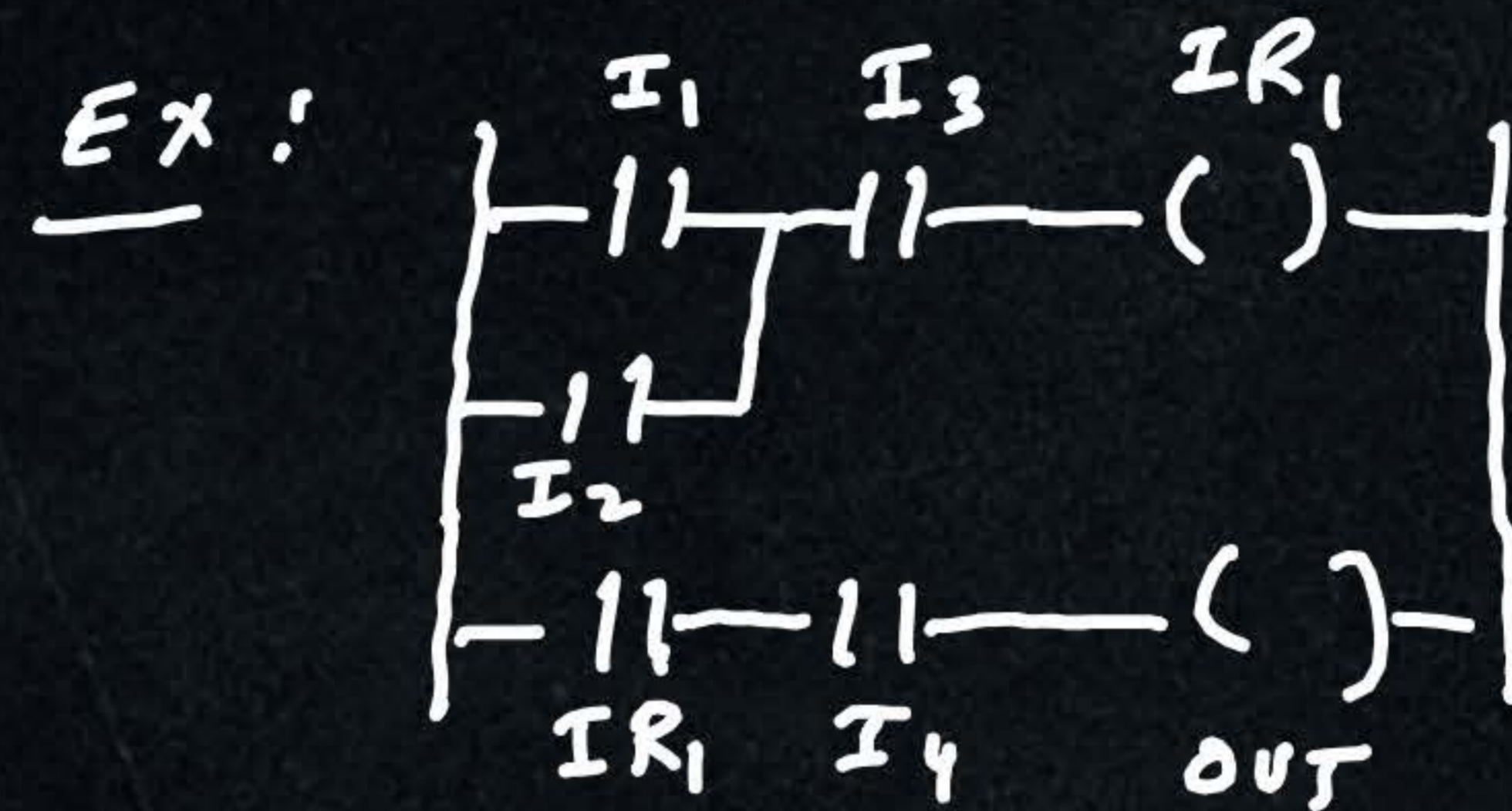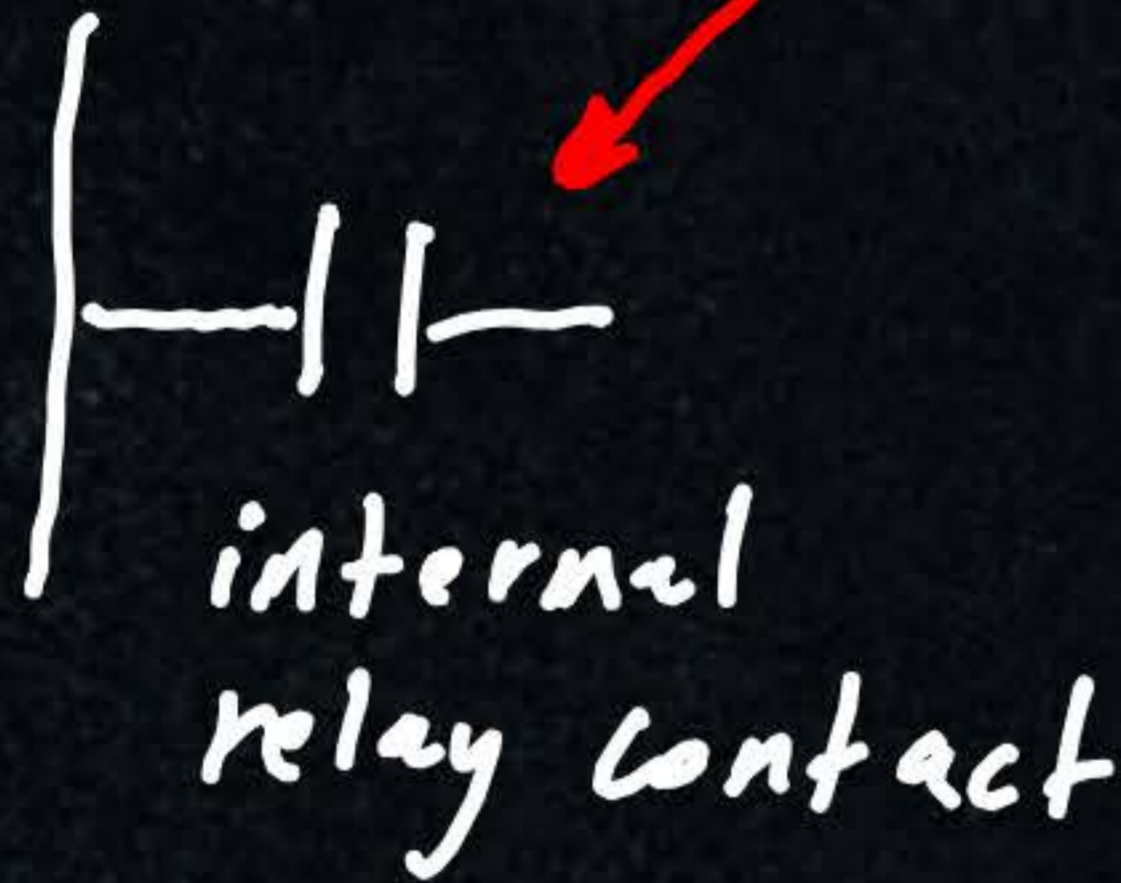

Mitsubishi:

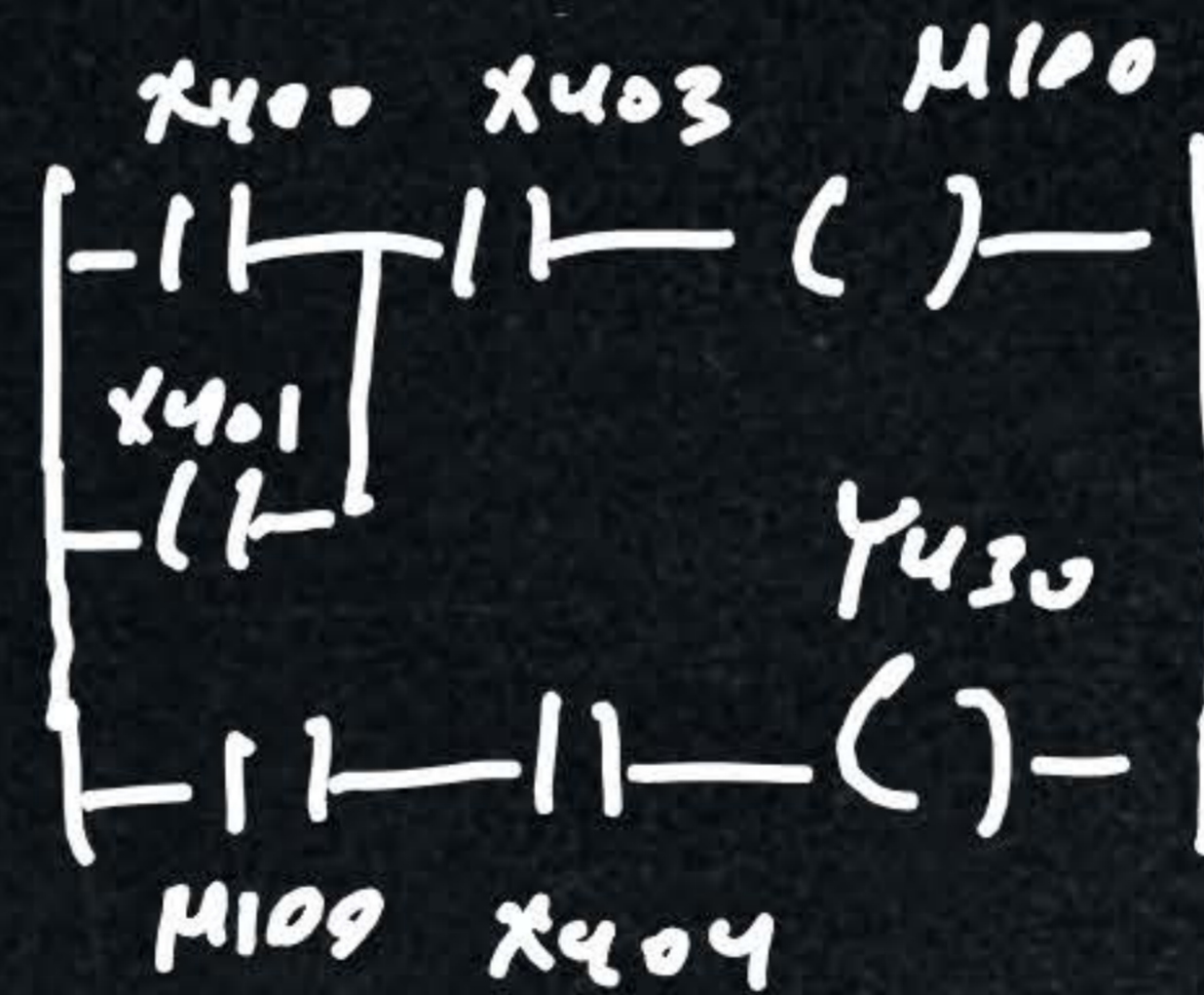

Siemens

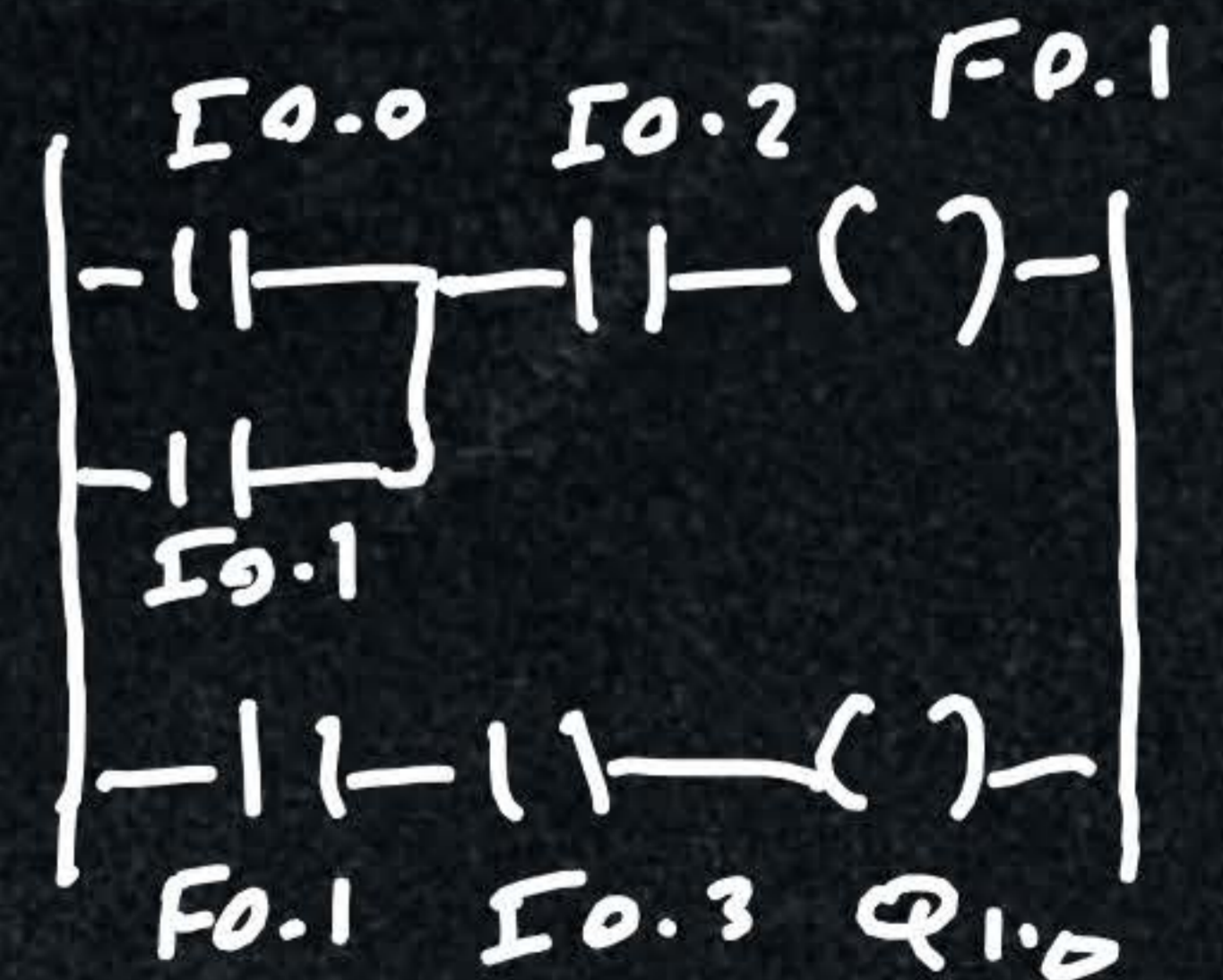

Addresses:-

Mitsubishi M100, M101, ...

Siemens F0.0, F0.1, ...

Toshiba R000, R001, ...

LD X400

OR X401

AND X403

OUT M100

LD M100

AND X404

OUT Y430

AI0.0

O I0.1

A I0.2

= F0.1



A F0.1

A I0.3


= Q1.0

Set and Reset


Mitsubishi

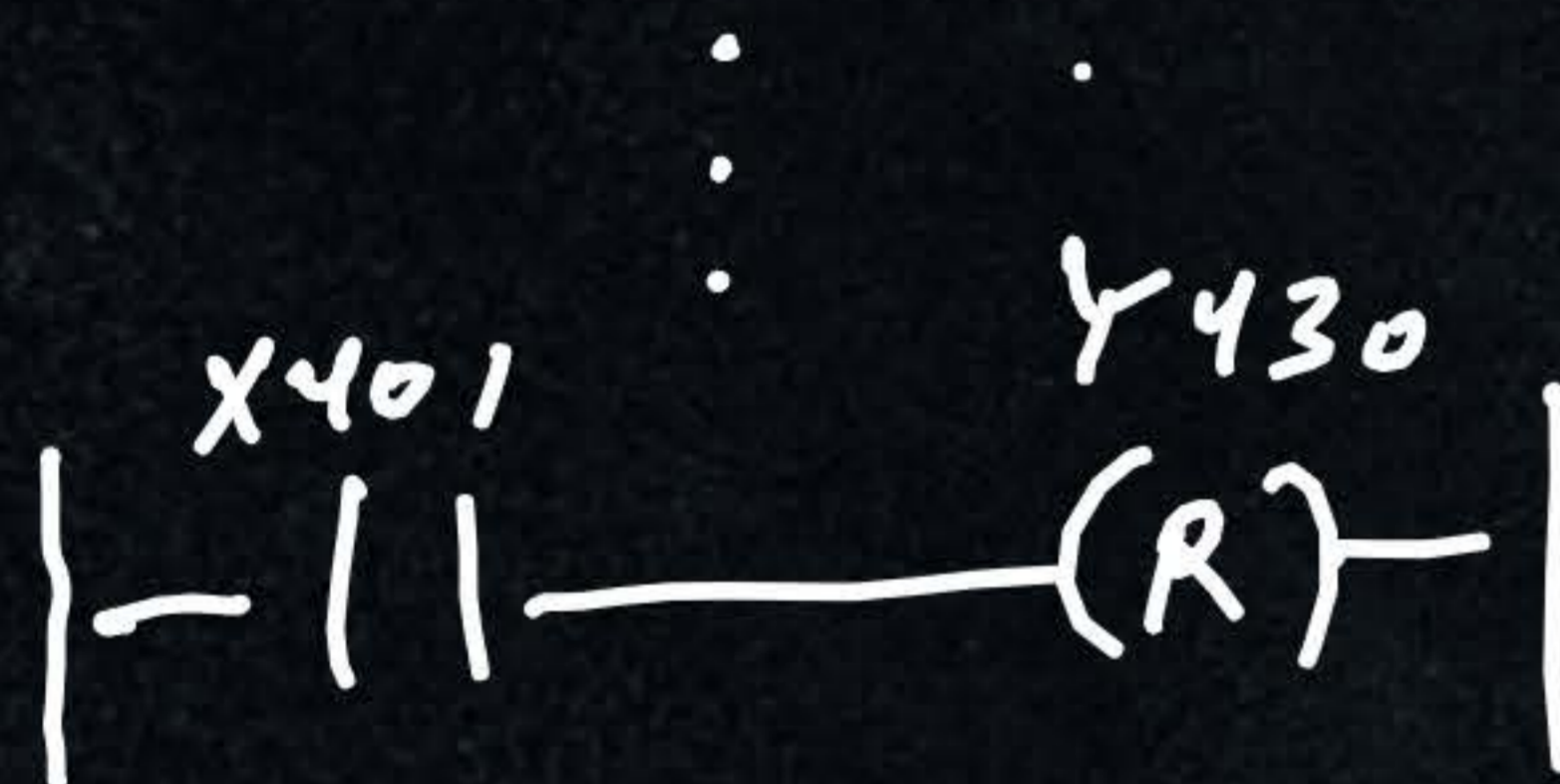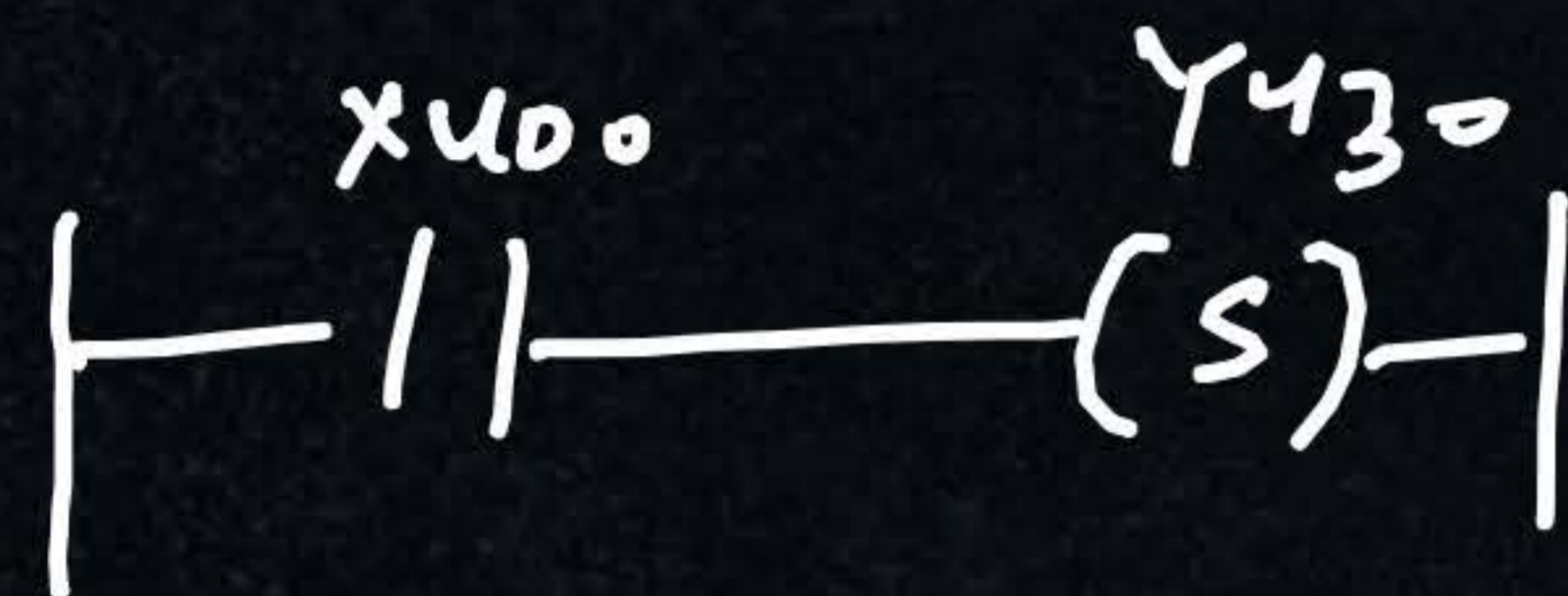
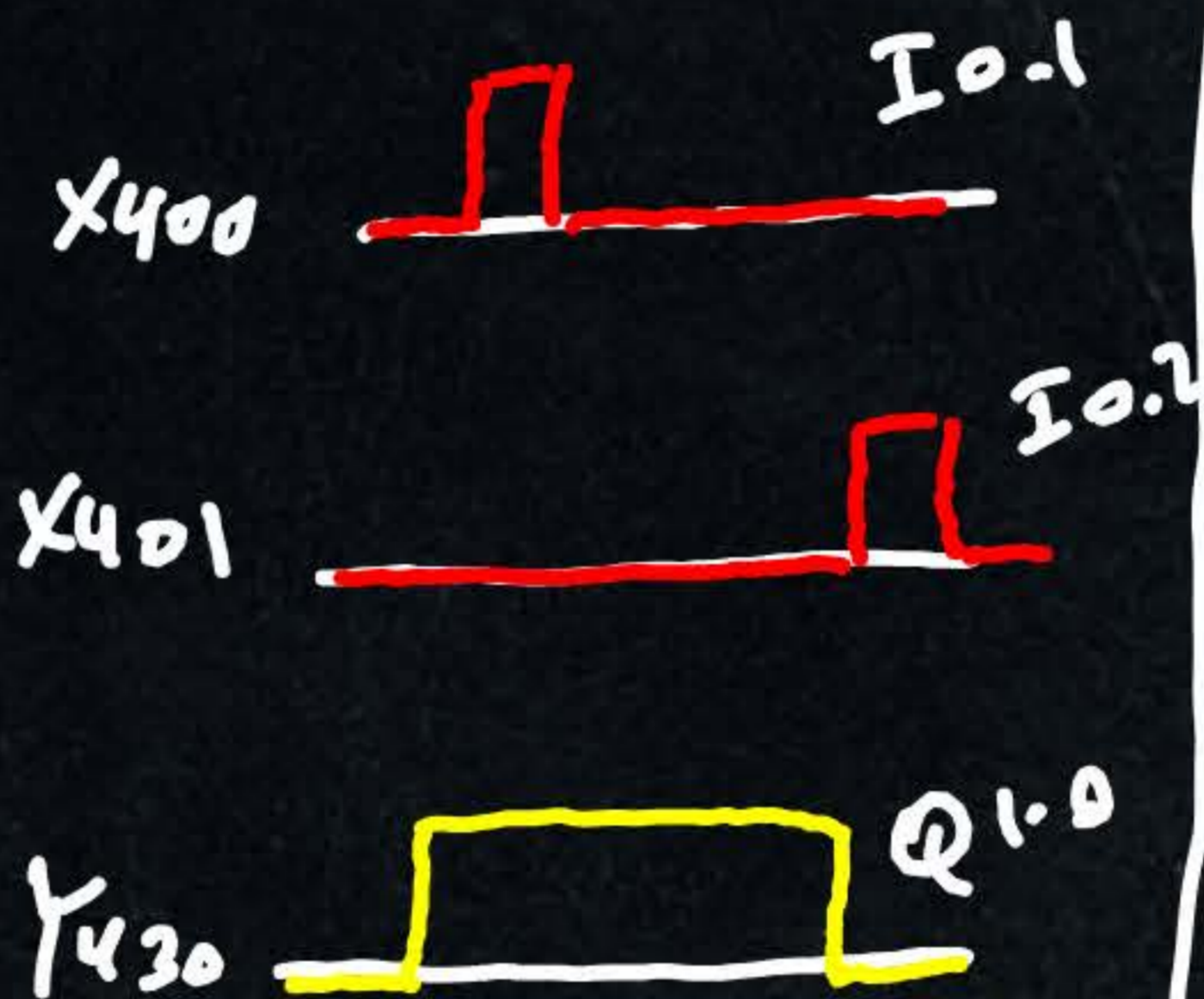
```
LD X 400
S Y 430
:
LD X 401
S Y 430
```



Siemens

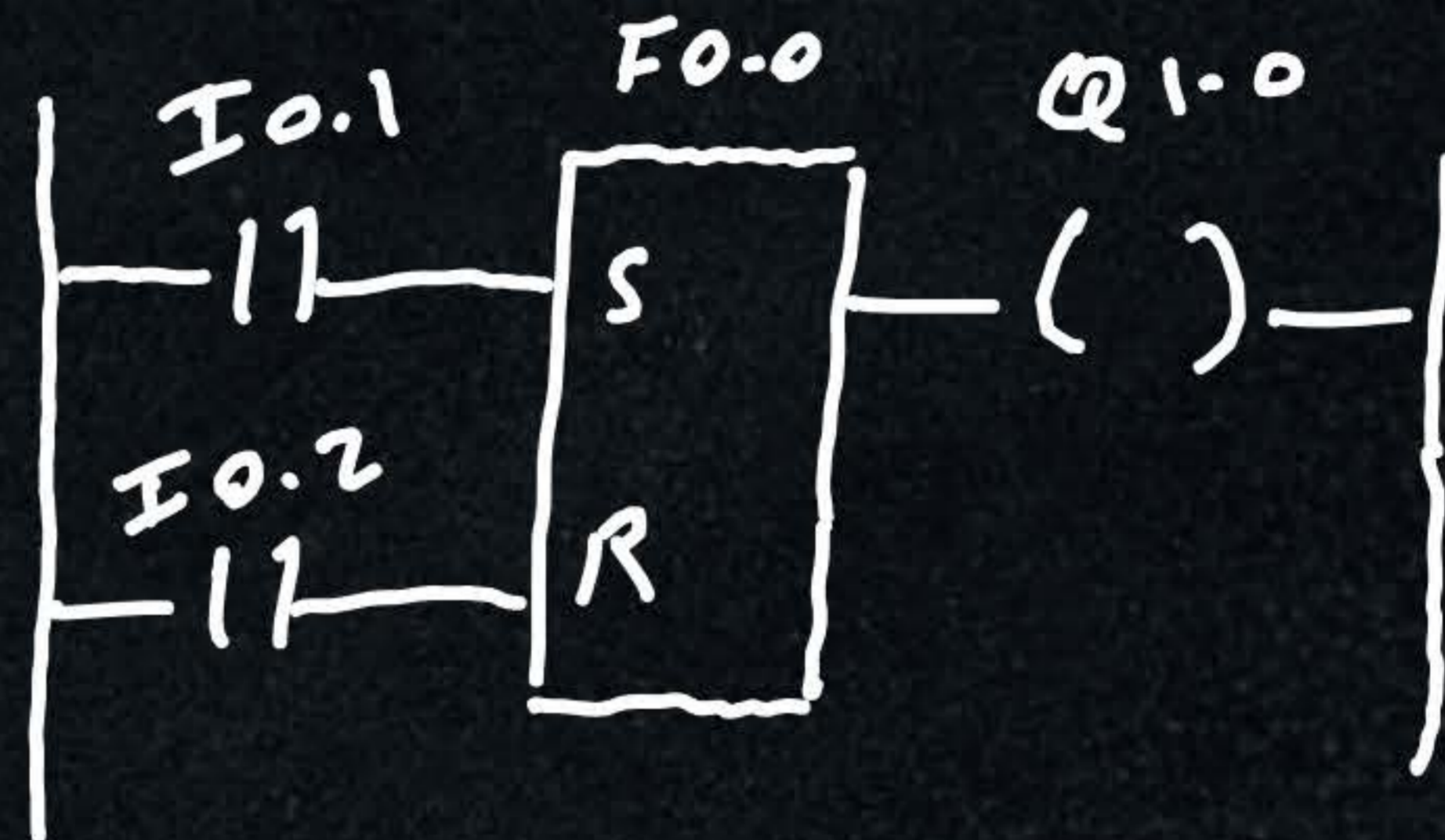


```
A I 0.1
S F 0.0
A I 0.2
R F 0.0
= Q 1.0
```


Timers

Types of timers


1) ON-delay timer

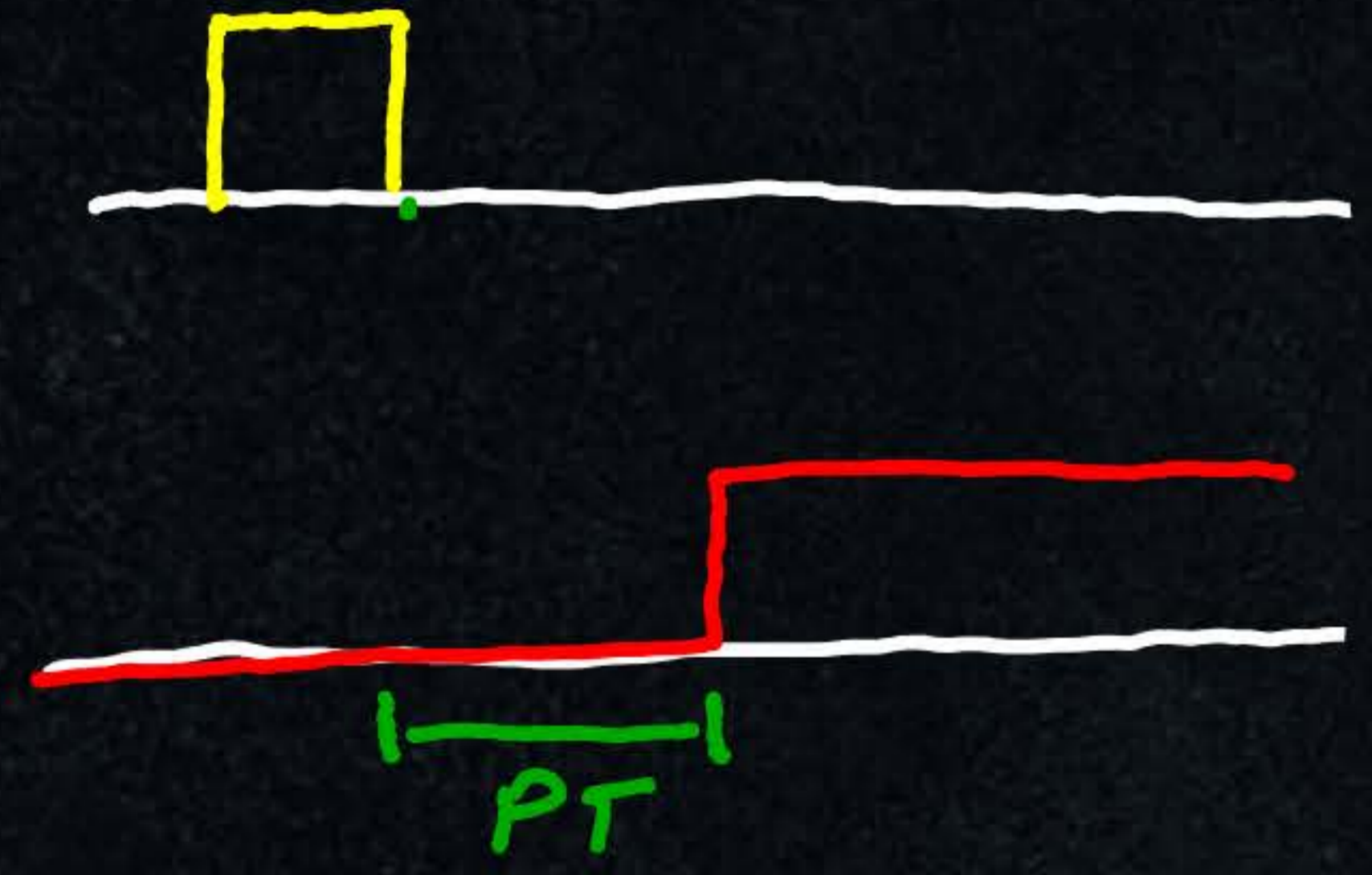

2) OFF-delay timer

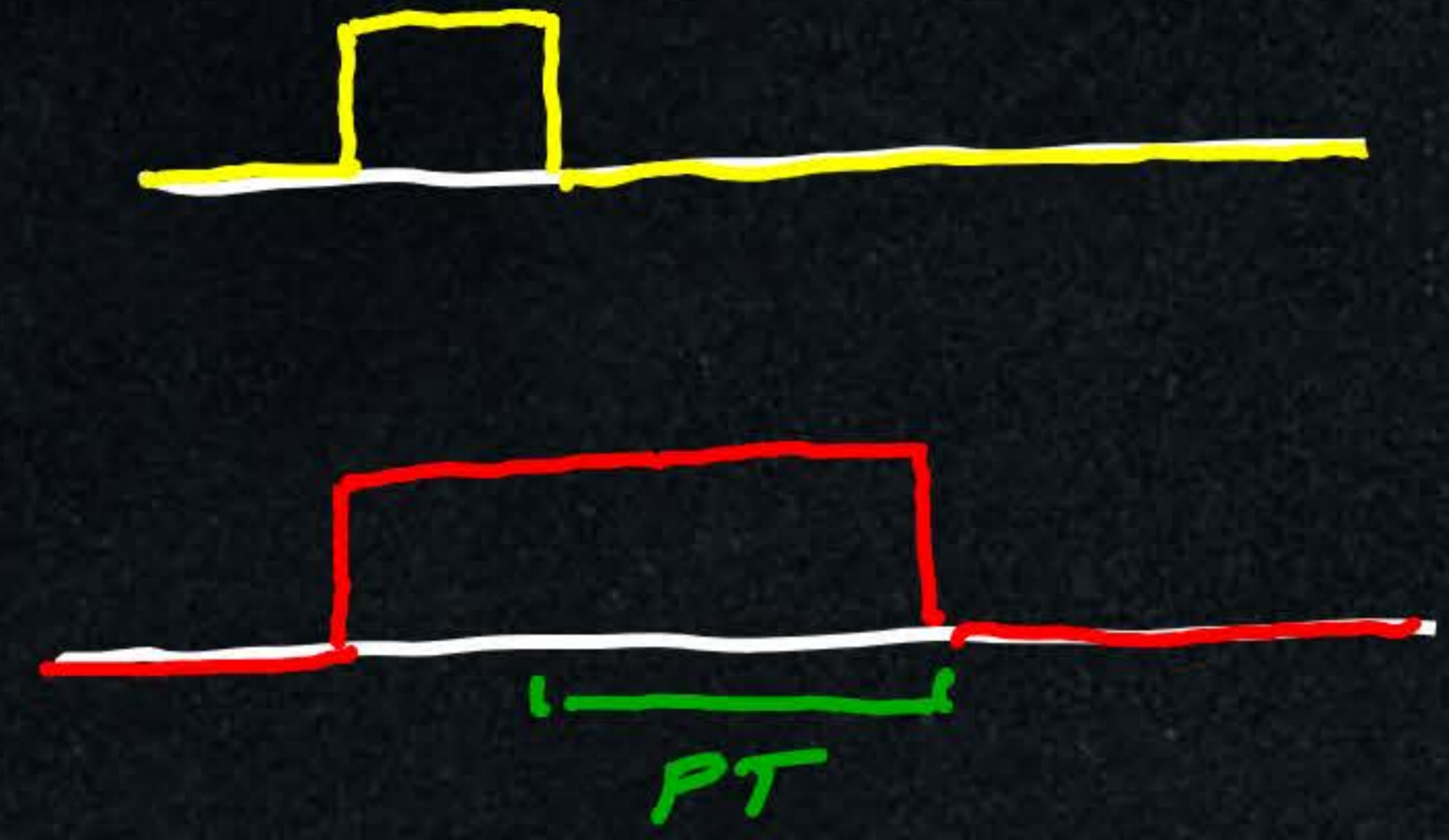

3) Pulse timer

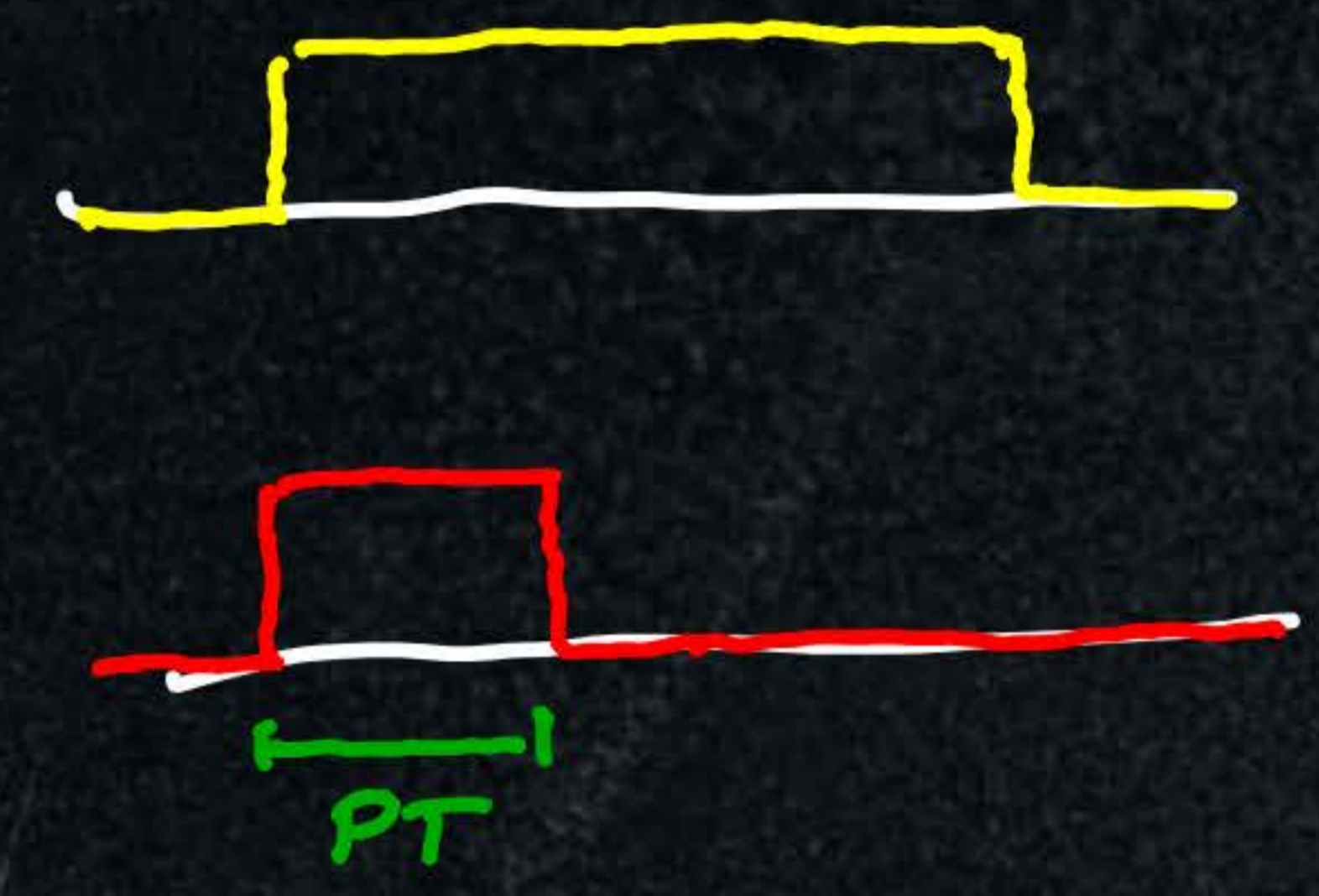

PT: preset time

Mitsubishi

PT: $n \times$ time base
where n is real integer

10ms, 100ms, 1sec,
10s, and 100s

Siemens

KT KXX.X
 000 0 → 10ms
 001 1 → 100ms
 002 2 → 1000ms
 ...
 ...

KT 5-2



PT = $5 \times 1000ms$
 = 5sec

Adresse


Mitsubishi: T450, T451, ...

Siemens: T0, T1, ...



Ex :- Resetting Latch

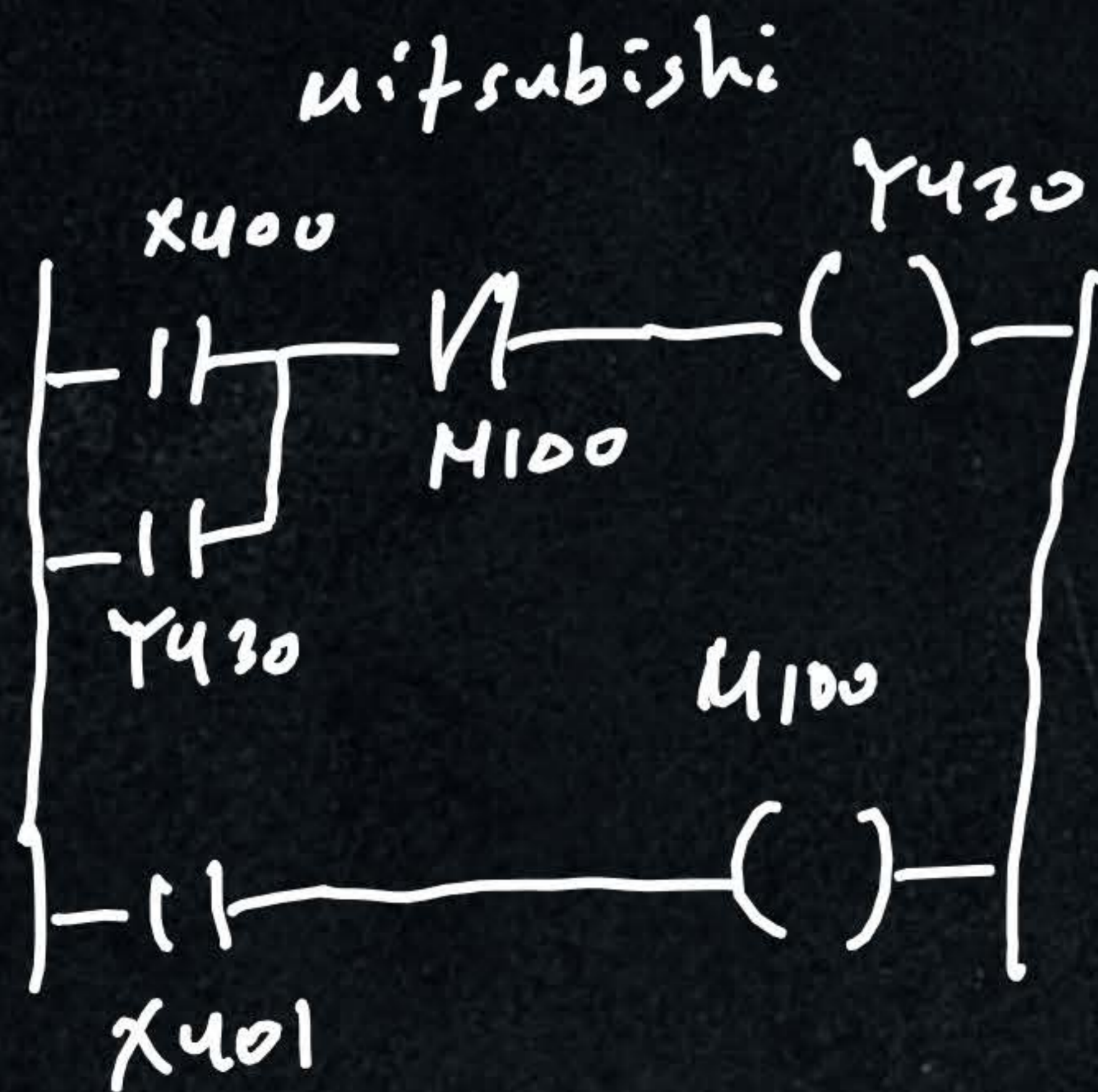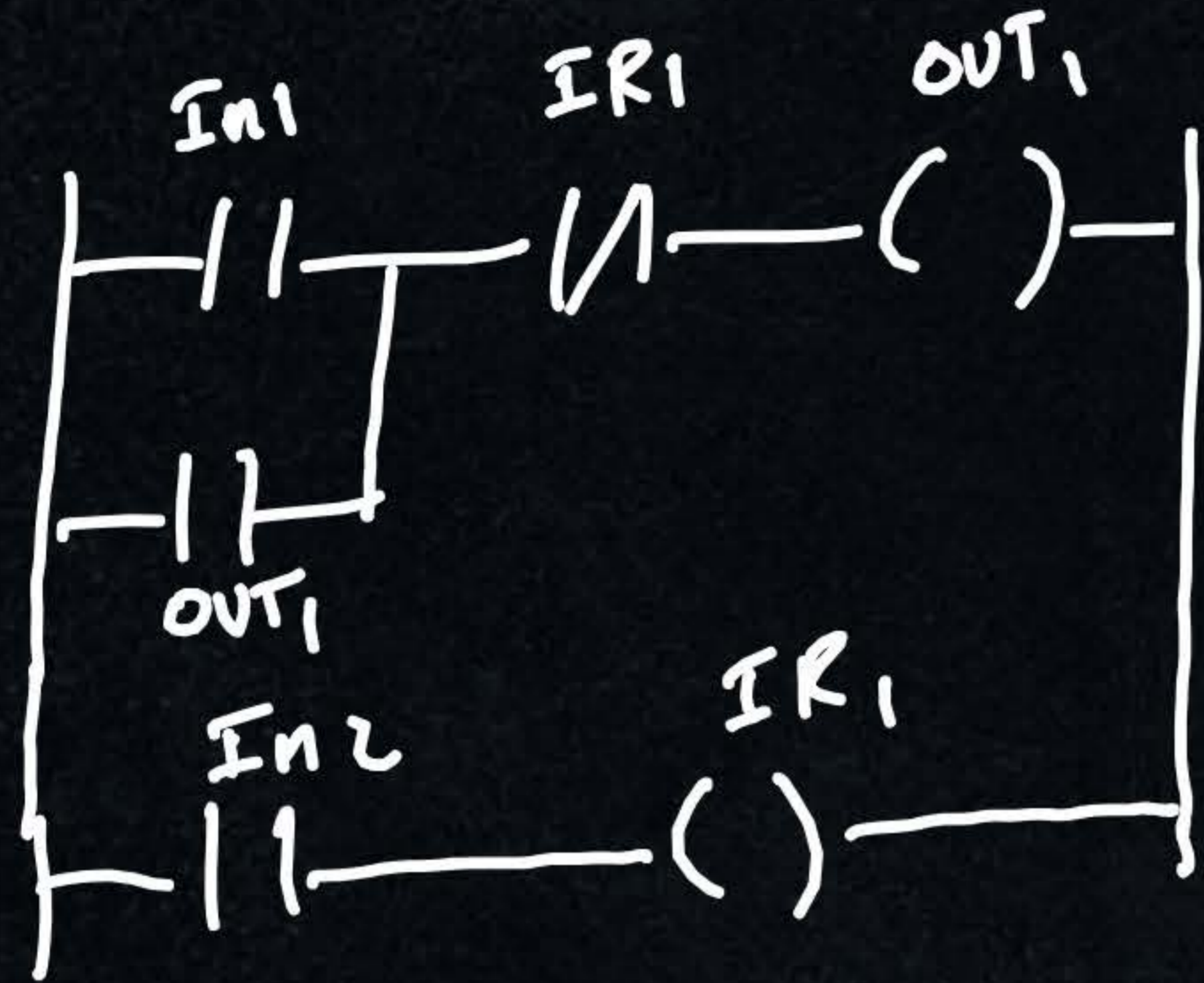

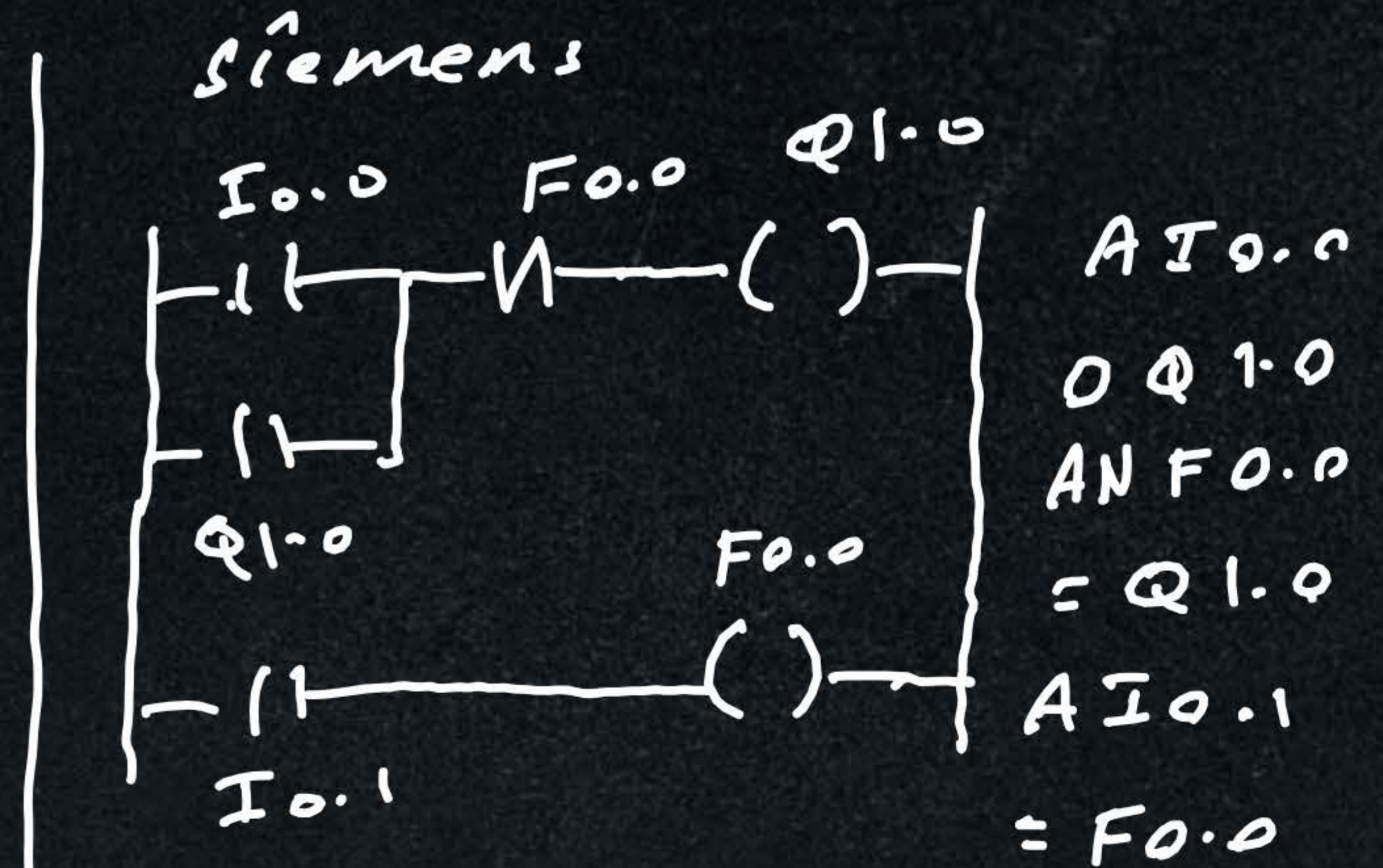
```
LD X400
OR Y430
ANI M100
OUT Y430
LD X401
OUT M100
```



Ex :- Resetting Latch

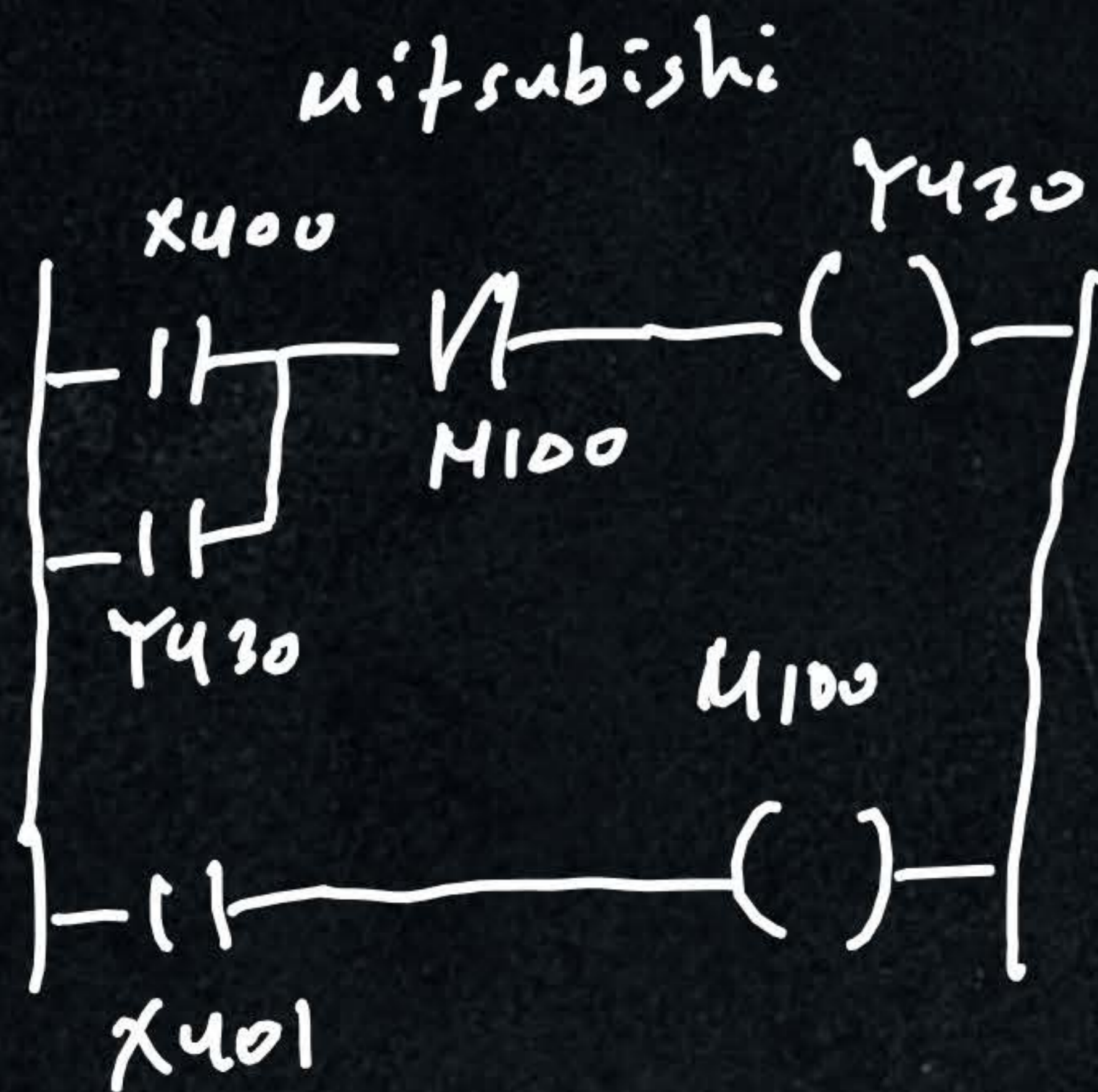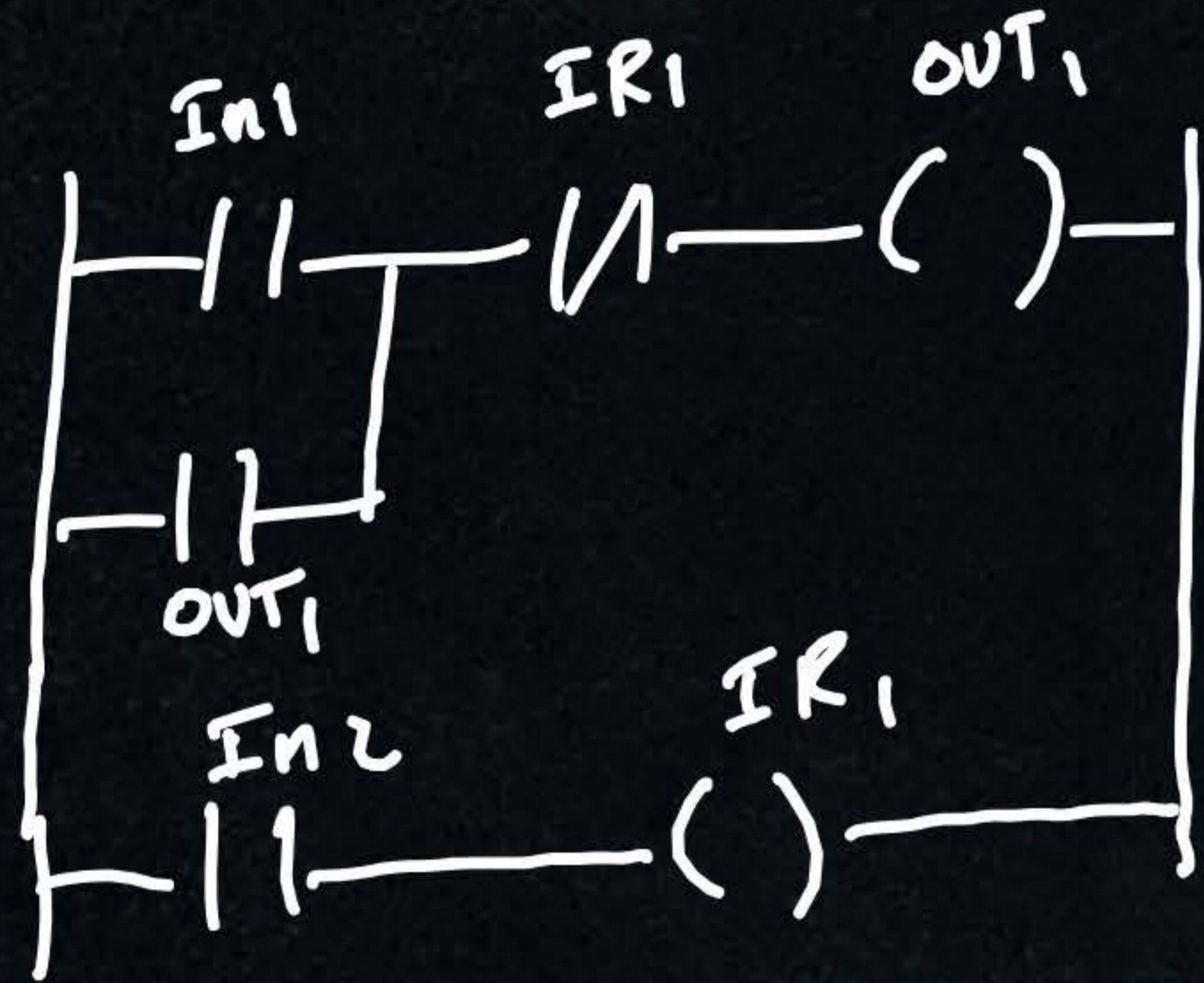

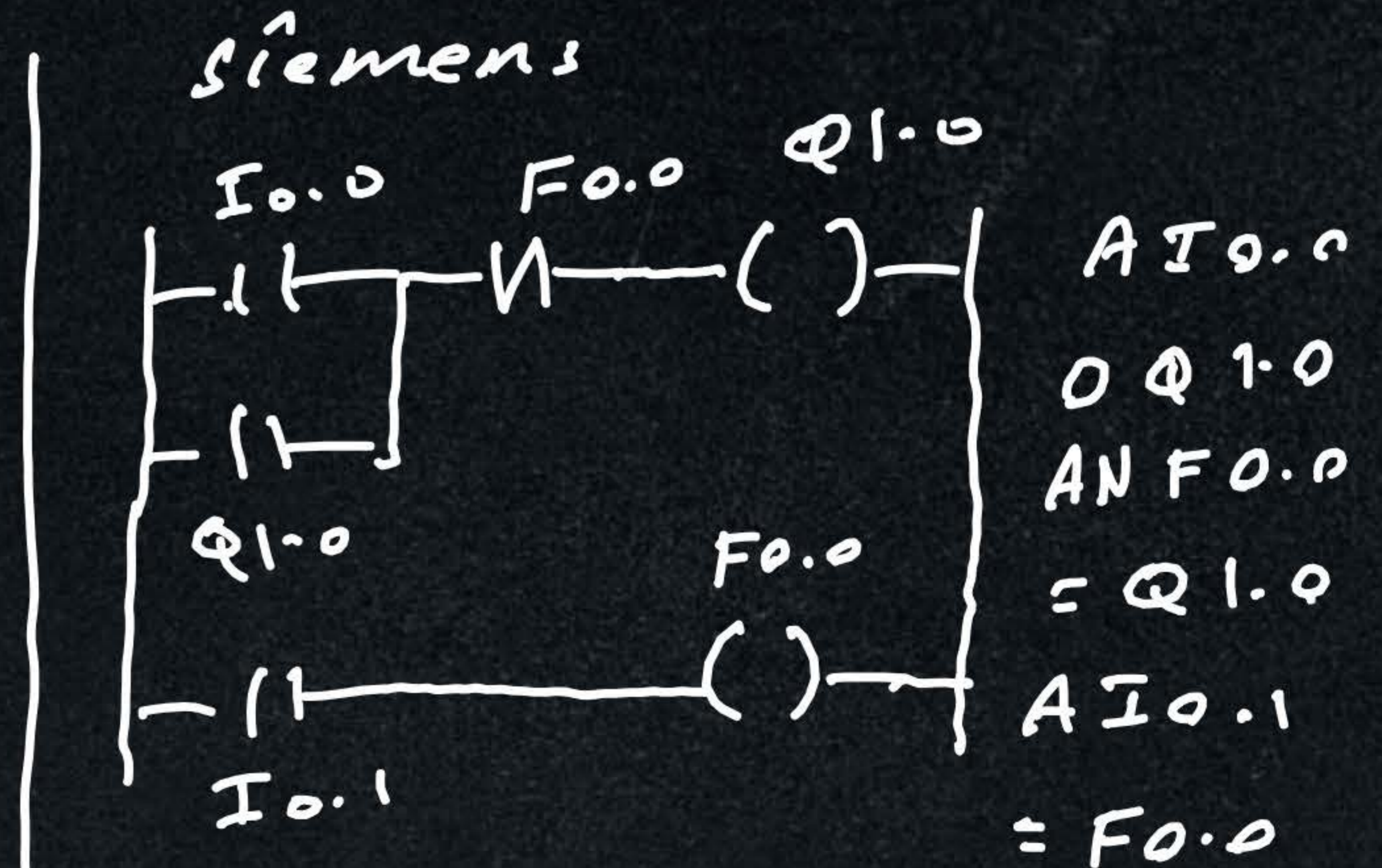
```
LD X400
OR Y430
ANI M100
OUT Y430
LD X401
OUT M100
```



```
AI0.0
OQ1.0
ANF0.0
= Q1.0
AI0.1
= F0.0
```


Ex Alarm system

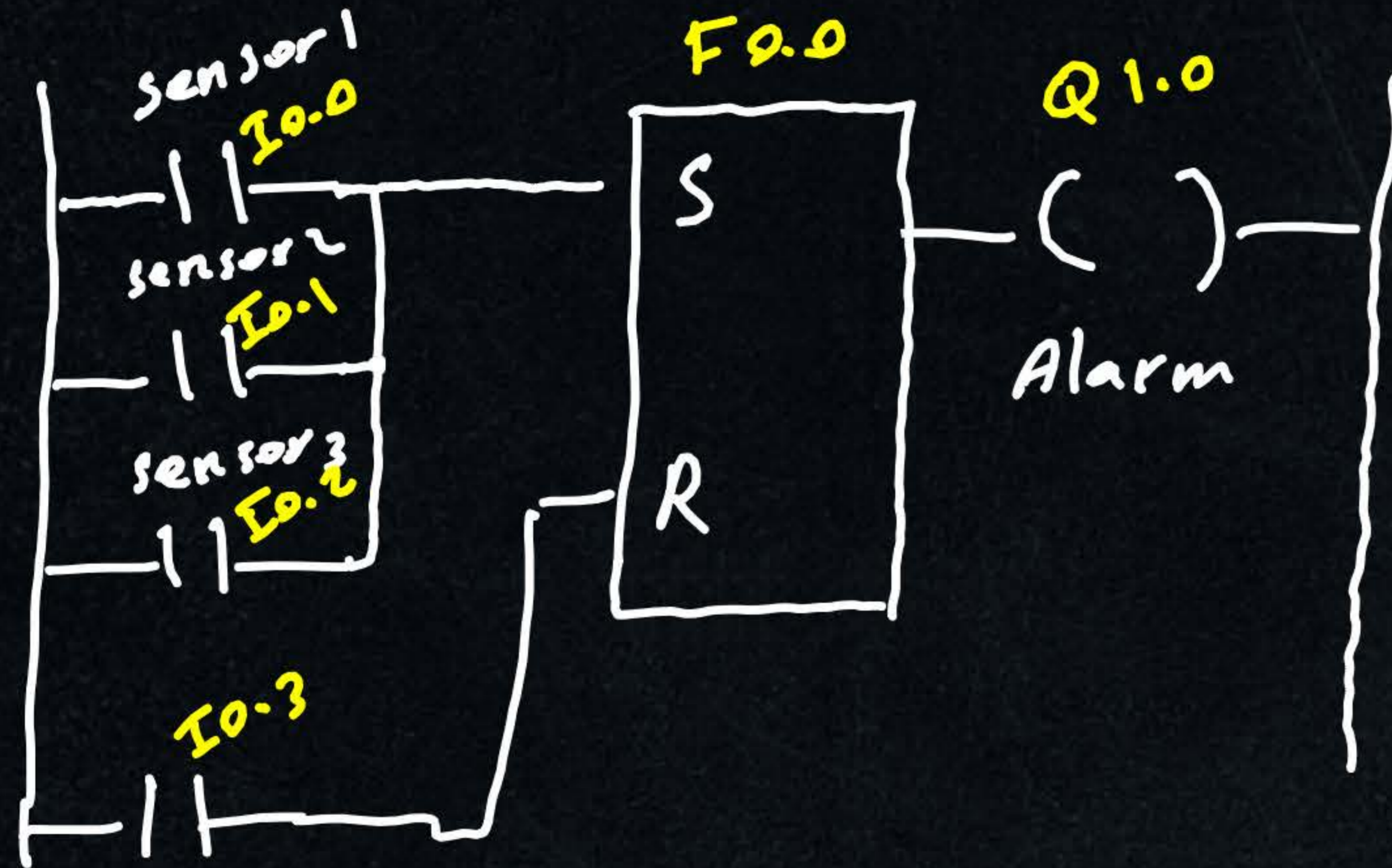

clear alarm switch



AI 0.0
 O I 0.1
 O I 0.2
 S F 0.0
 I 0.3
 R F 0.0
 A F 0.0
 = Q 1.0

Mitsubishi

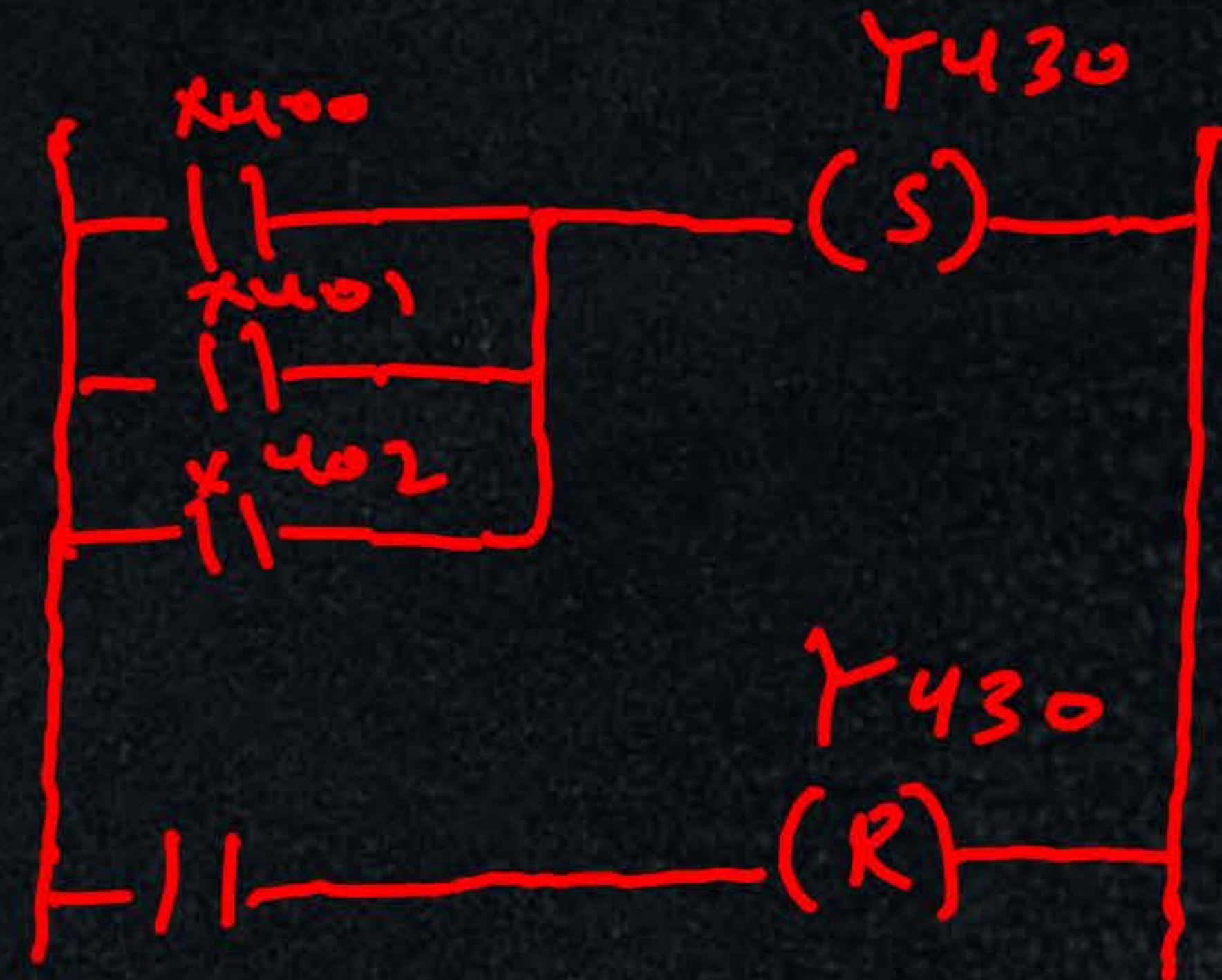

X403 1
 LD X400
 OR X401
 OR X402
 S Y430
 LD X403
 R Y430

Ex Starting of Multiple outputs

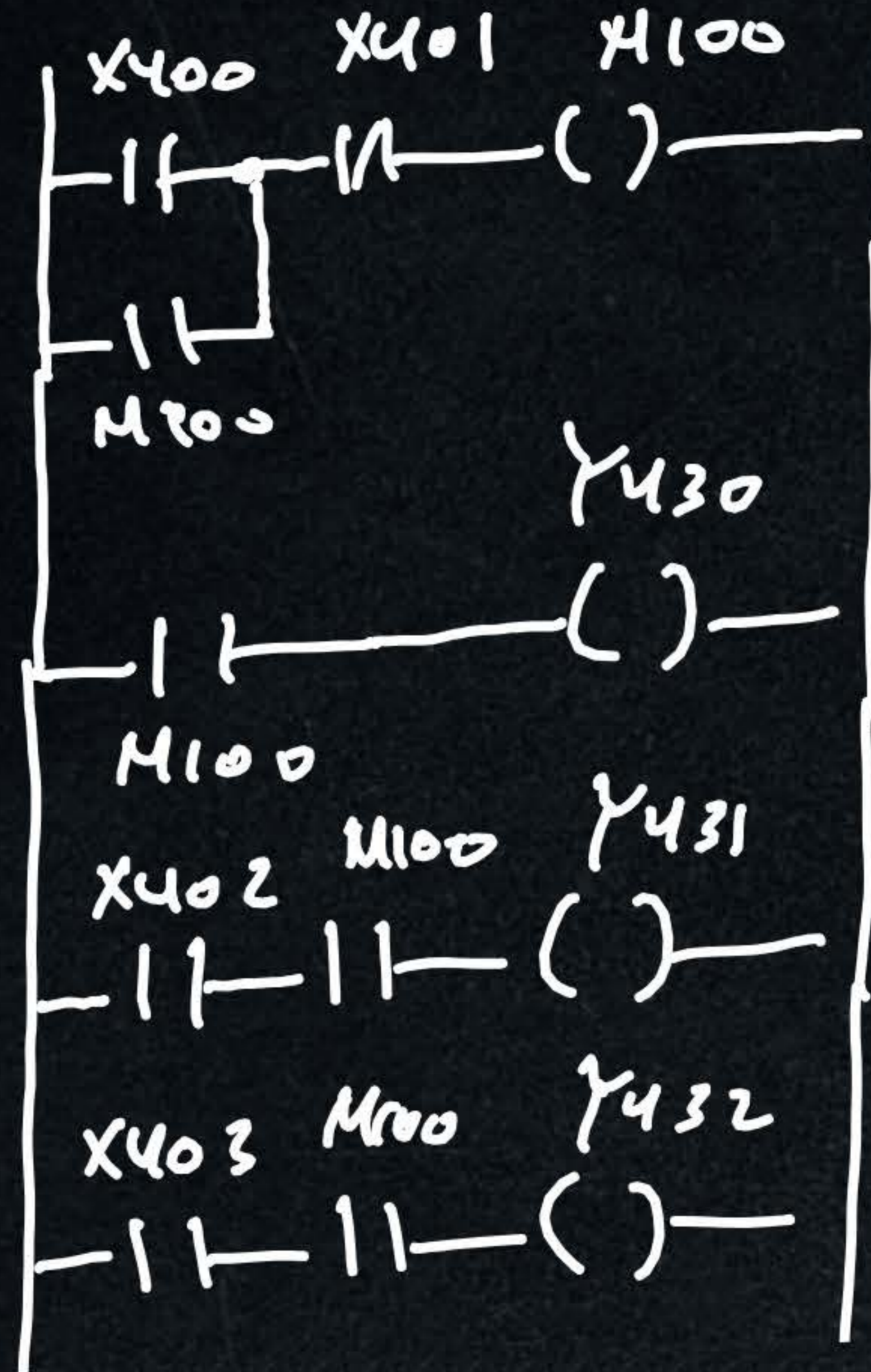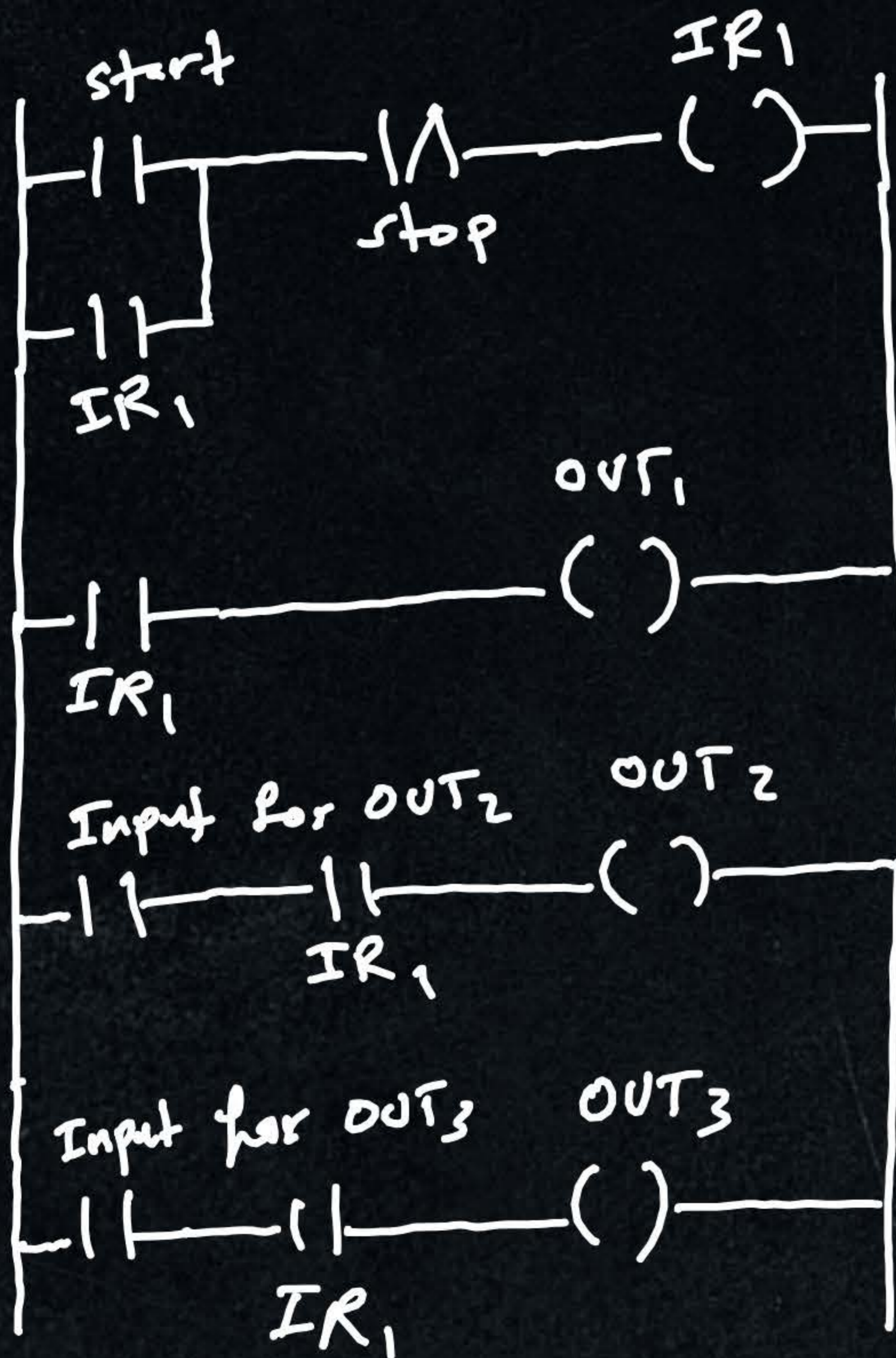


```

LD X400
OR M100
ANI X401
OUT M100
LD M100
OUT Y430
LD X402
AND M100
OUT Y431
LD X403
AND M100
OUT Y432
  
```

Timer

① on-delay timer


Mitsubishi:

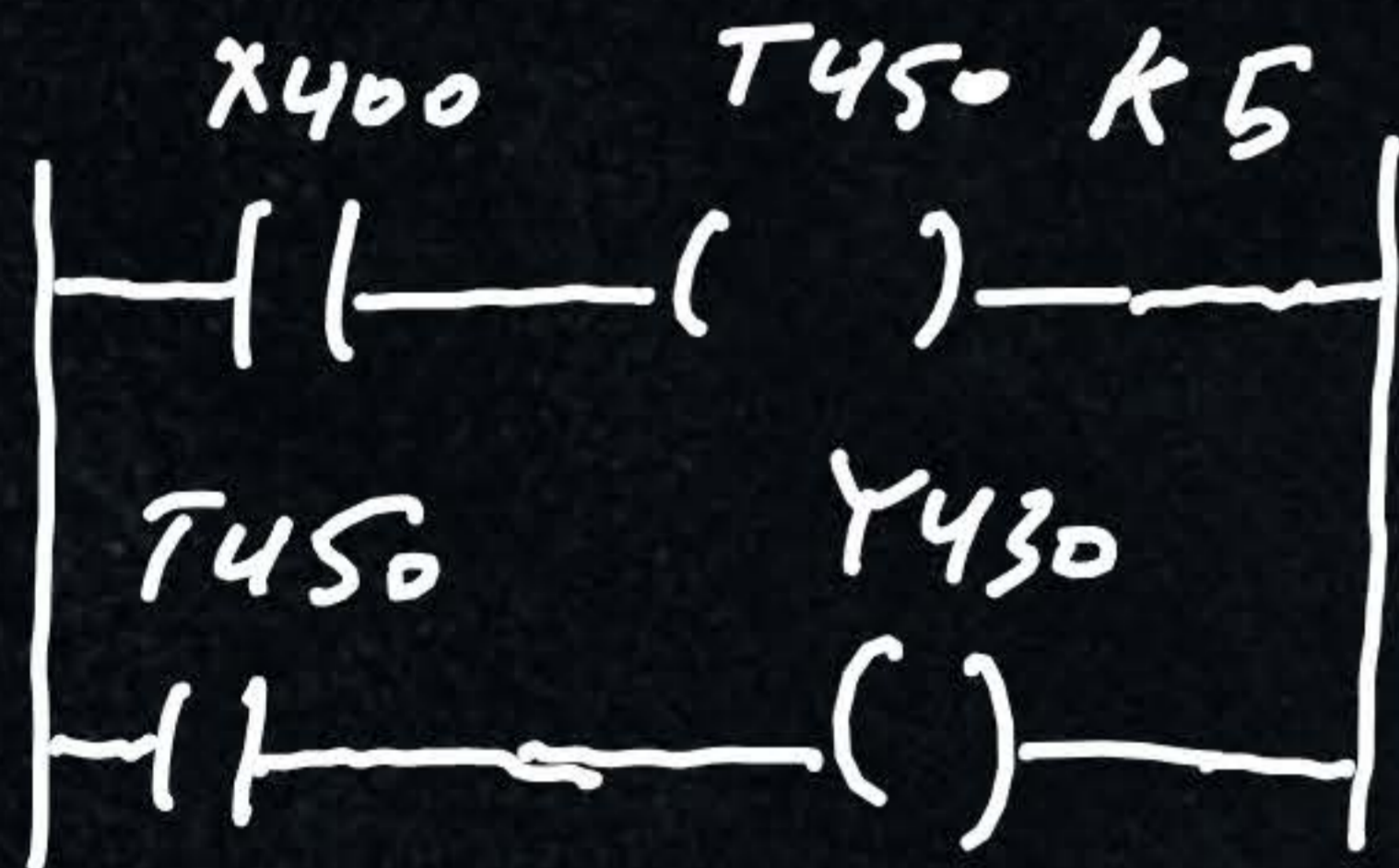

```
LD X400
OUT T450
K5
LD T450
OUT Y430
```






Siemens

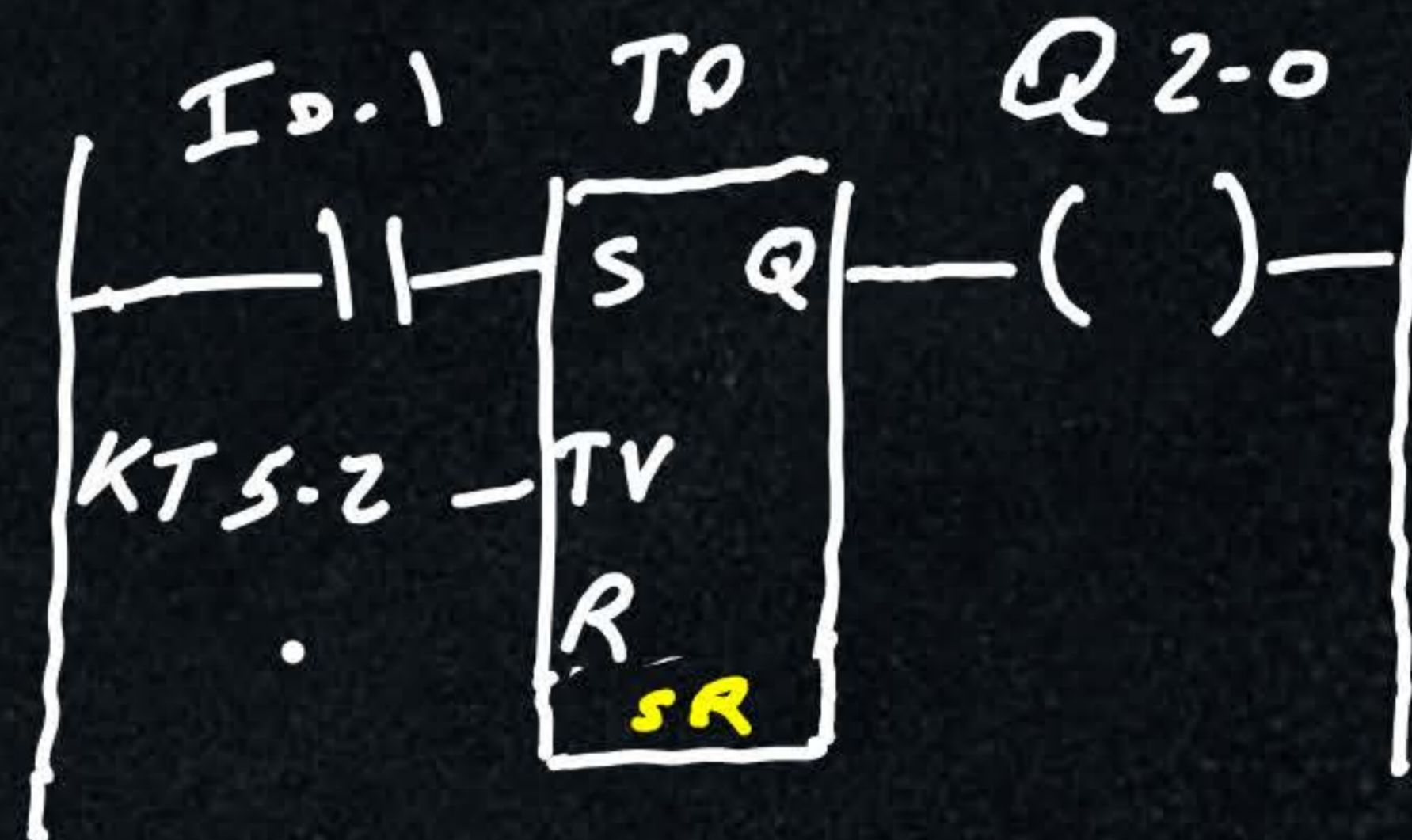

```
A I0.1
S R T0
LKT 5.2
ATO
= Q2.0
```

② OFF-delay timer

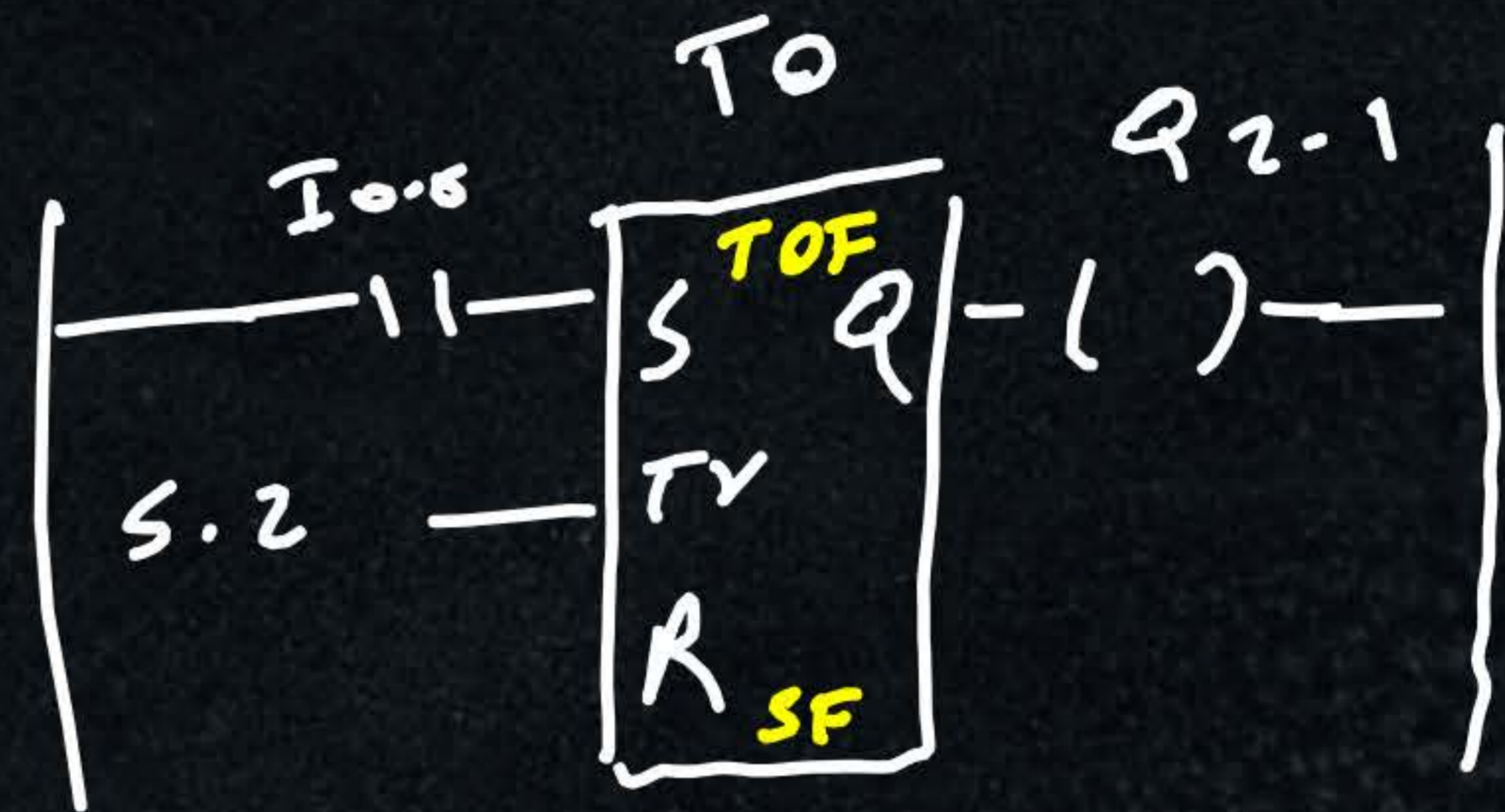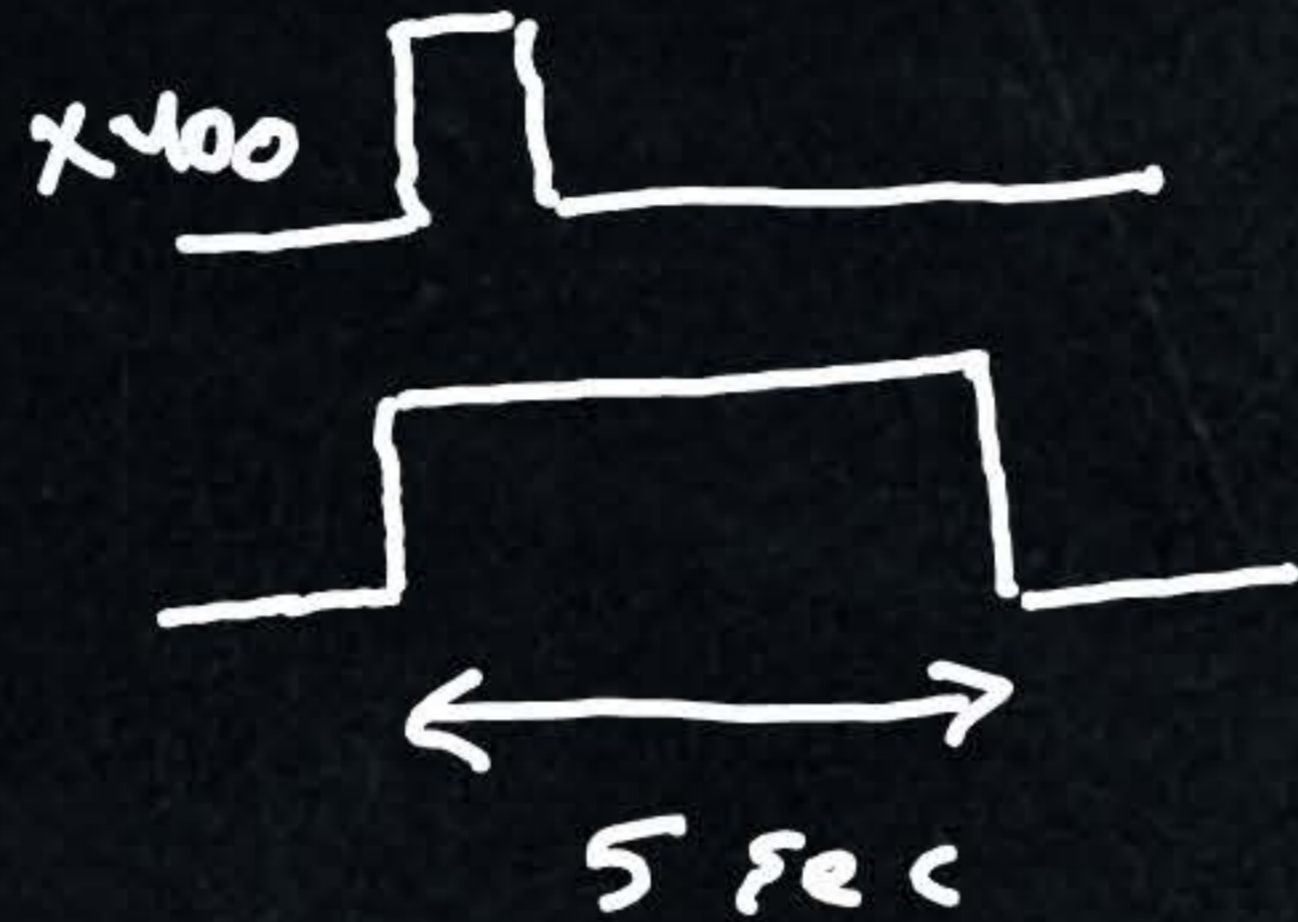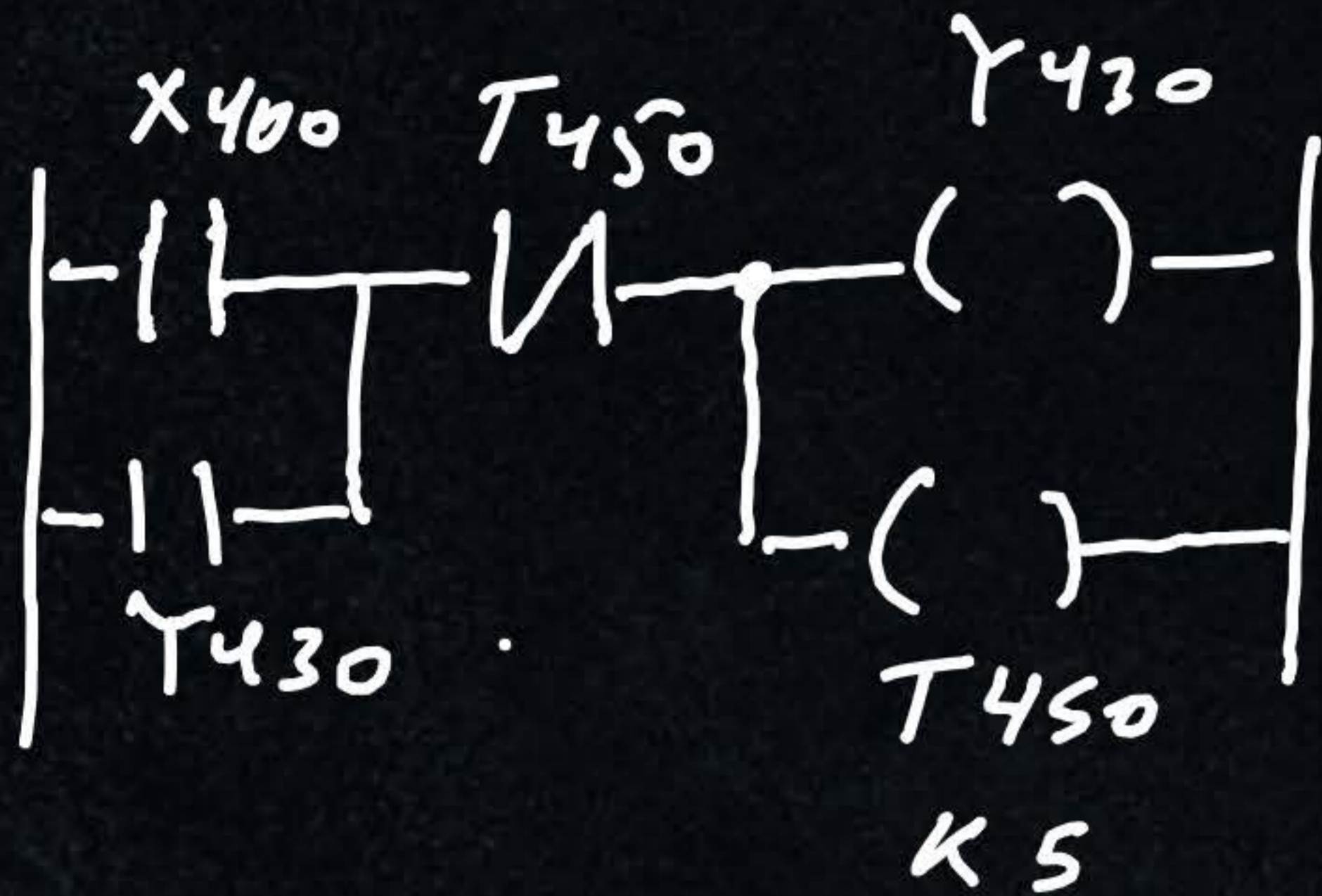

```

LD X400
OR Y430
ANI T450
OUT Y430

```

```

LD X400
OR Y430
ANI T450
OUT T450
K5


```

```

A I0.0
SF TO
LKT S.2
ATO
= Q2.0


```

EX: ON/OFF cycle

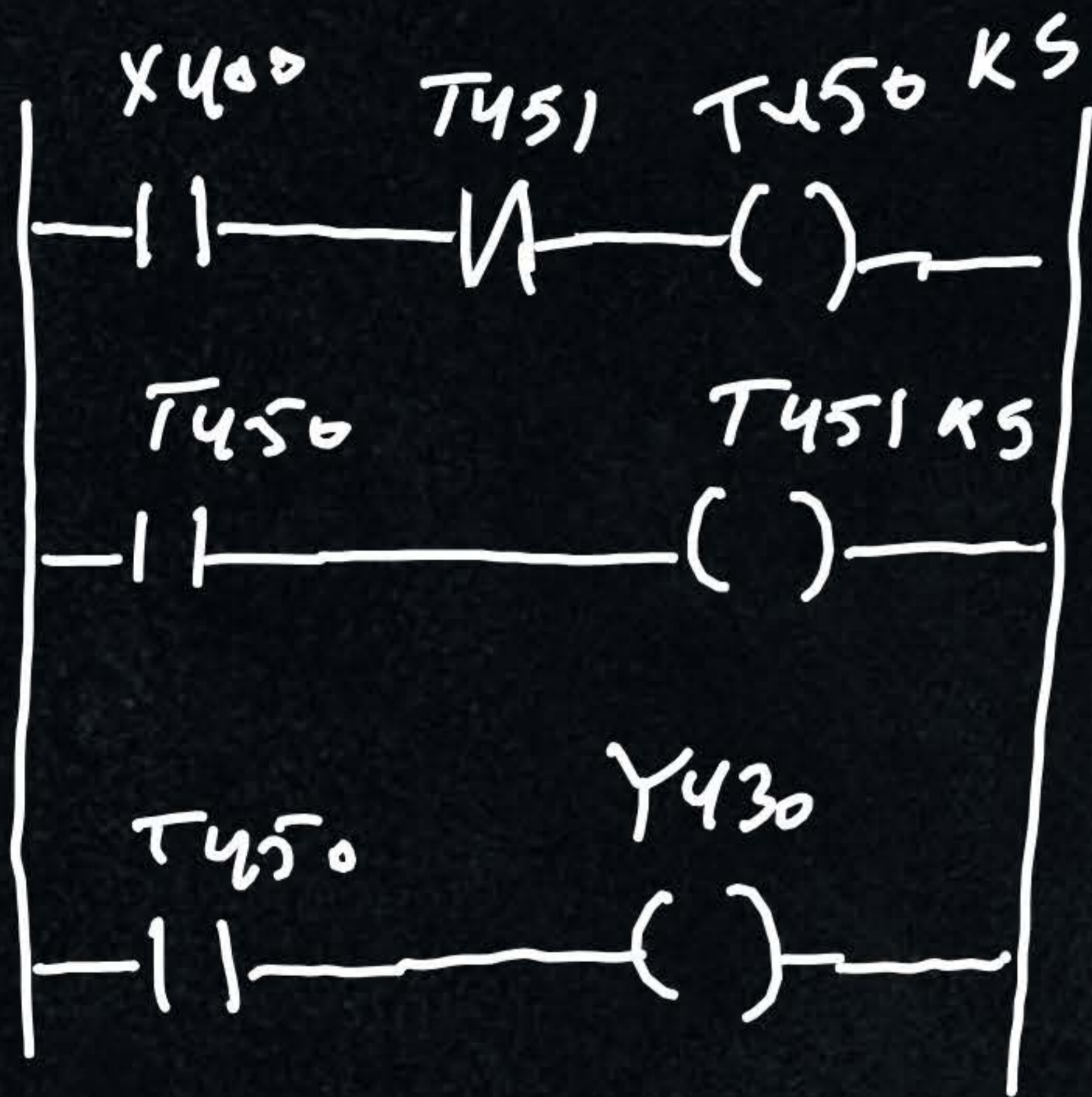


```
LD X400
ANI T451
OUT T450
  K5
LD T450
OUT T451
  K5
```

```
LD T450
OUT Y430
```

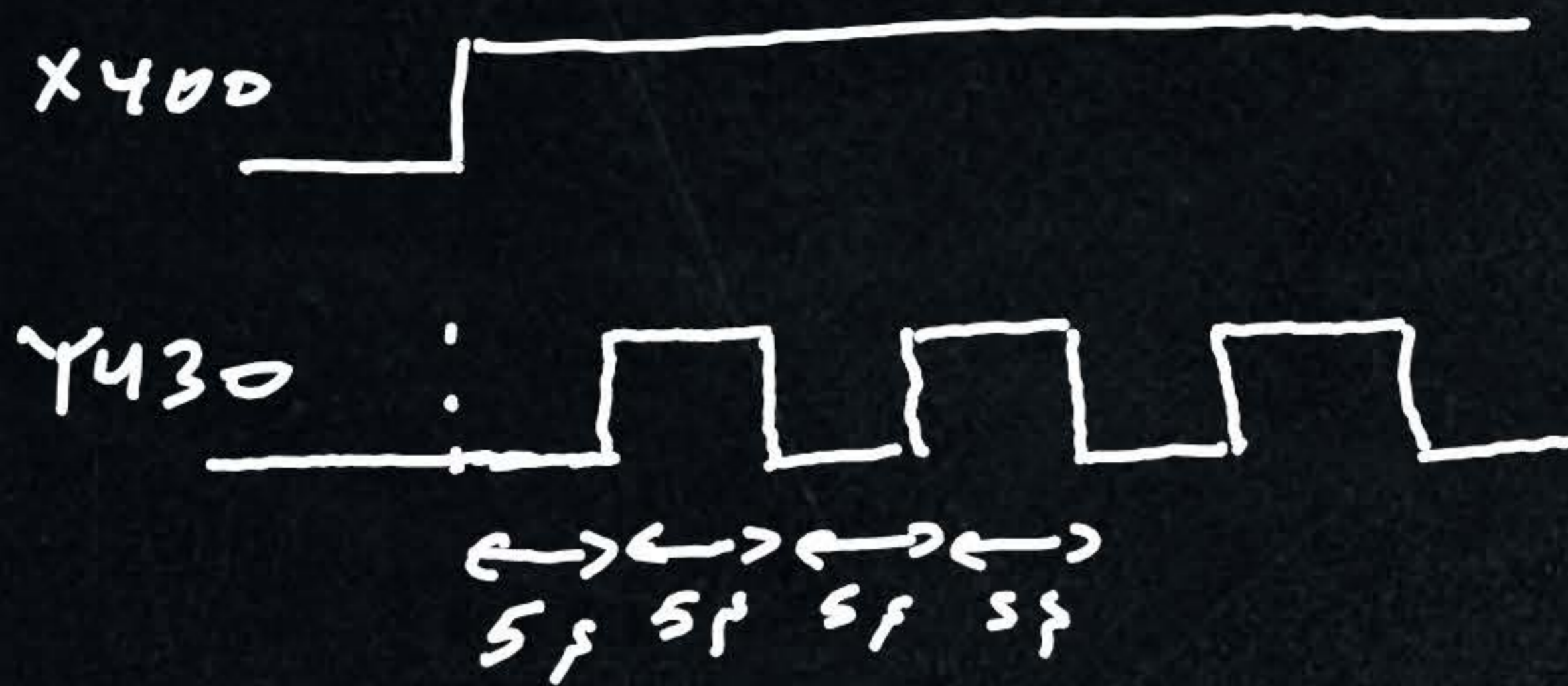

OFF 10 sec
ON 5 sec


mit subishi

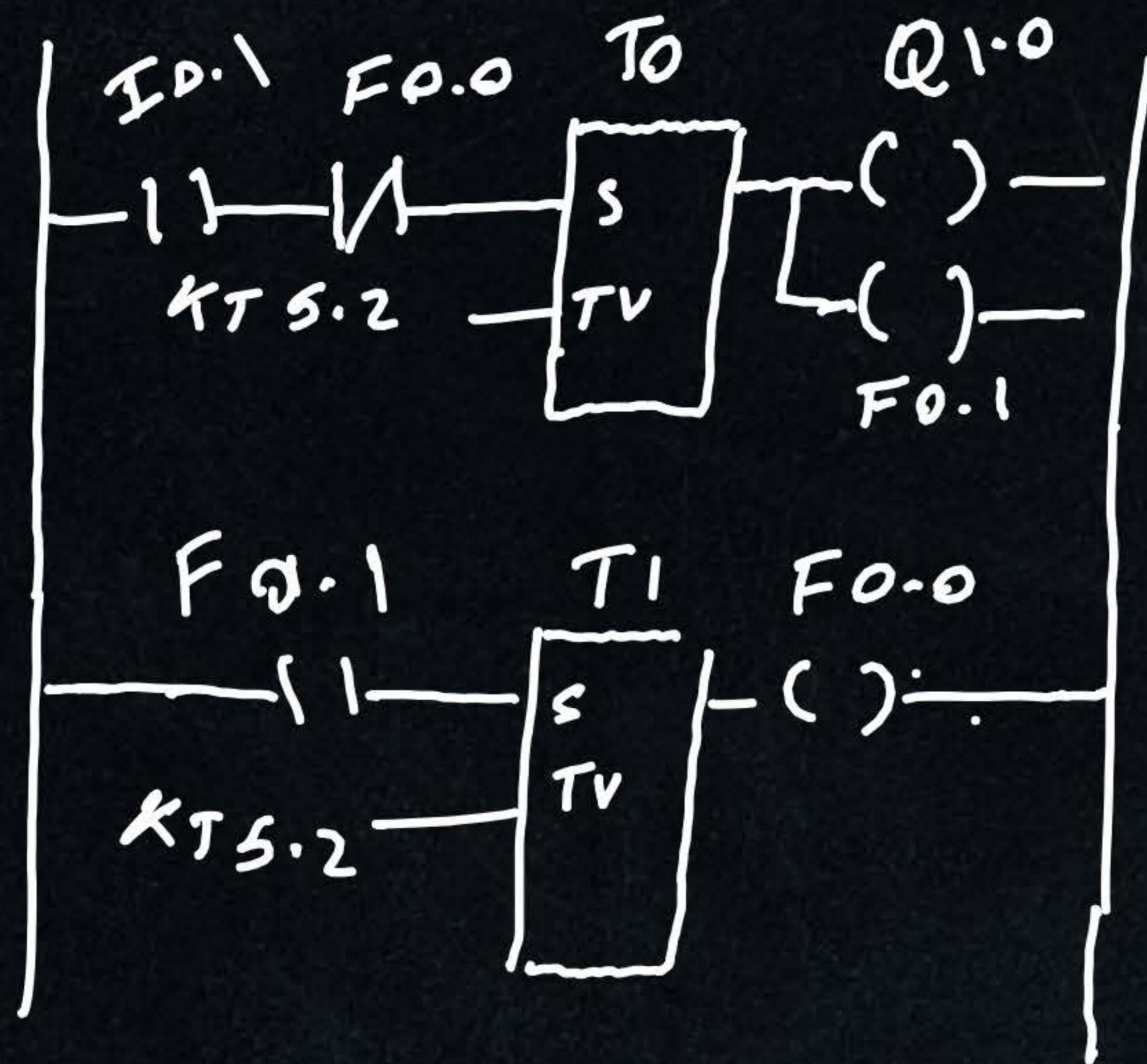



Counters

Up-counter → count from zero up to the preset value

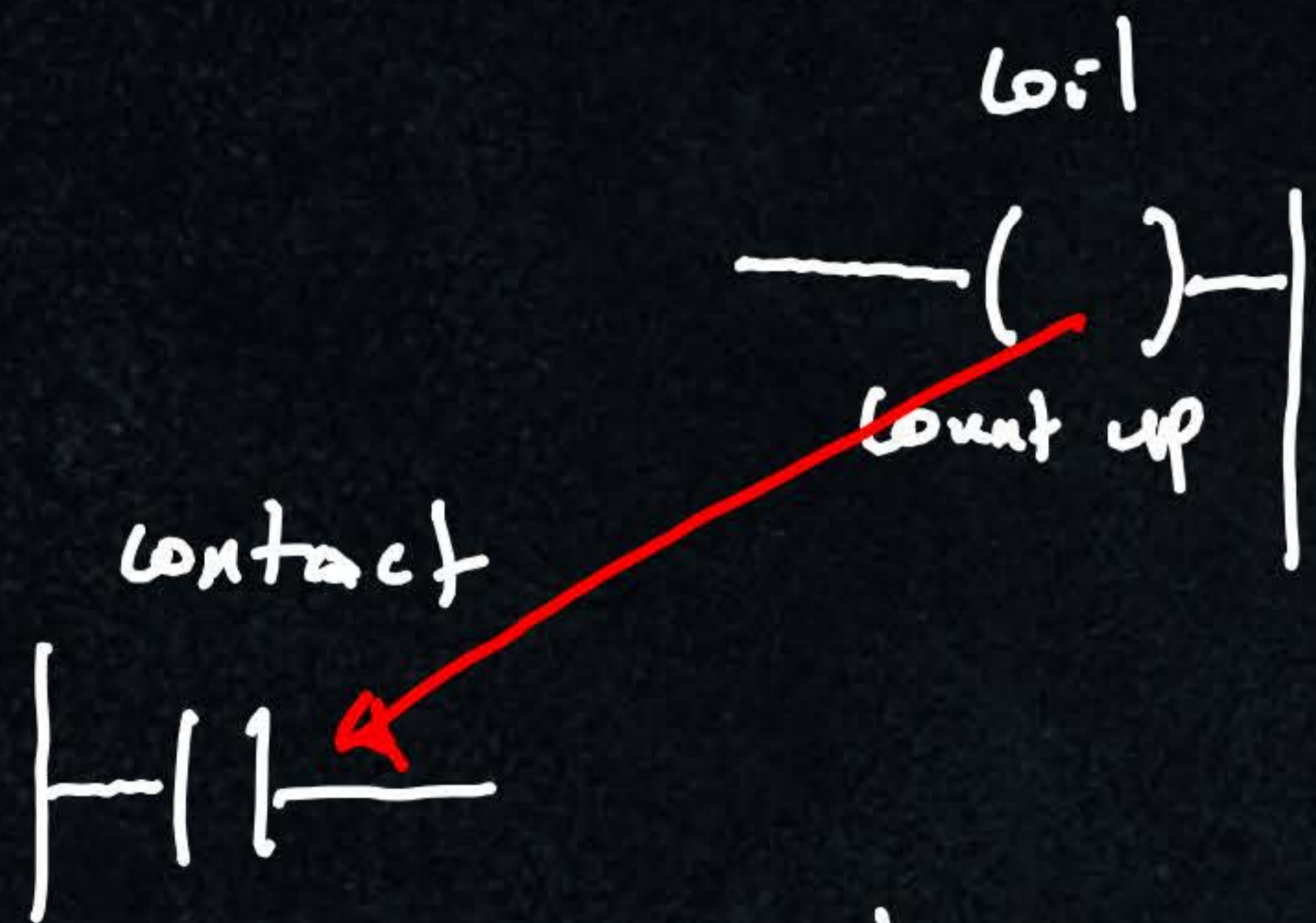Down-counter → count from present value to zero



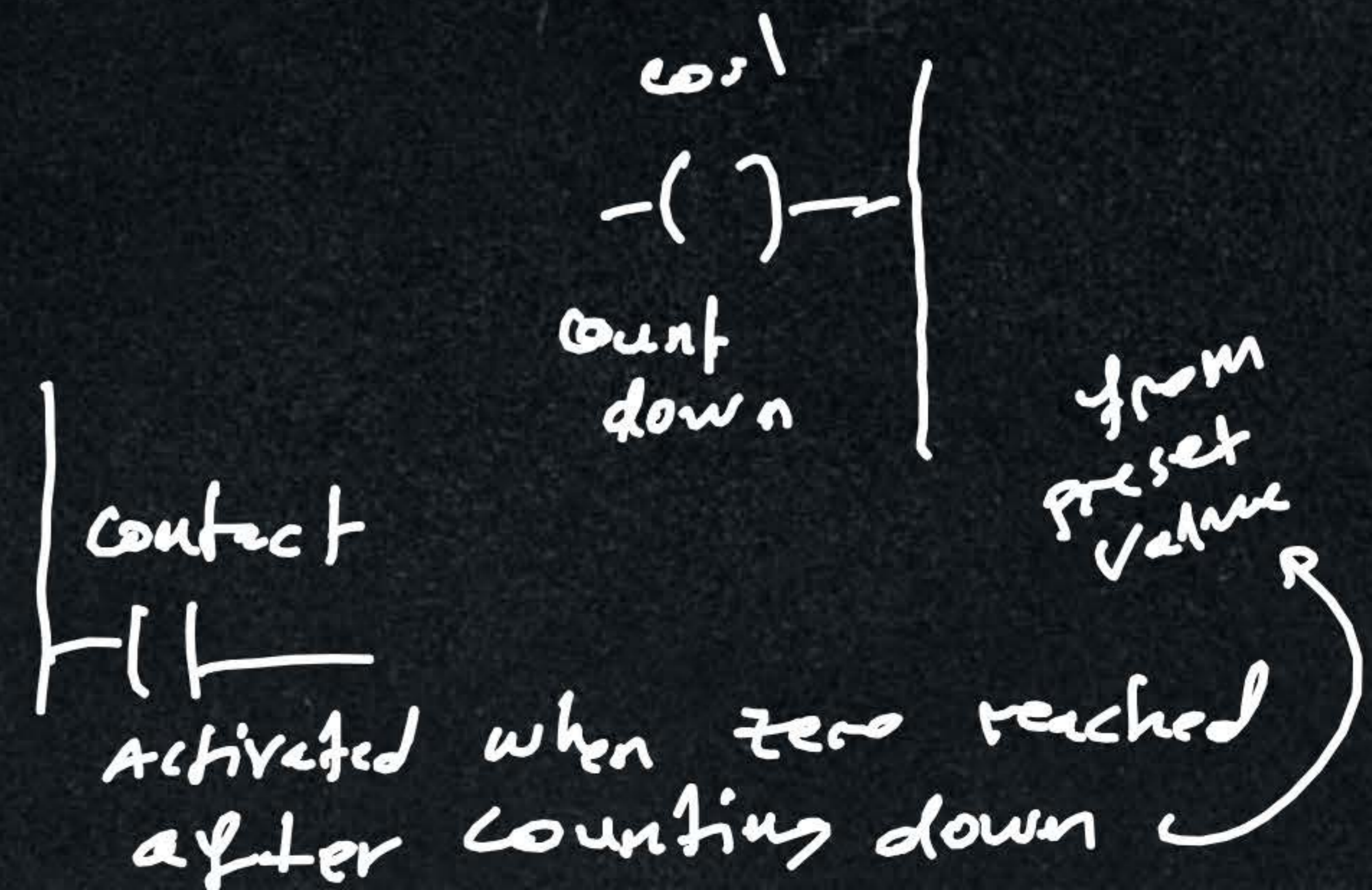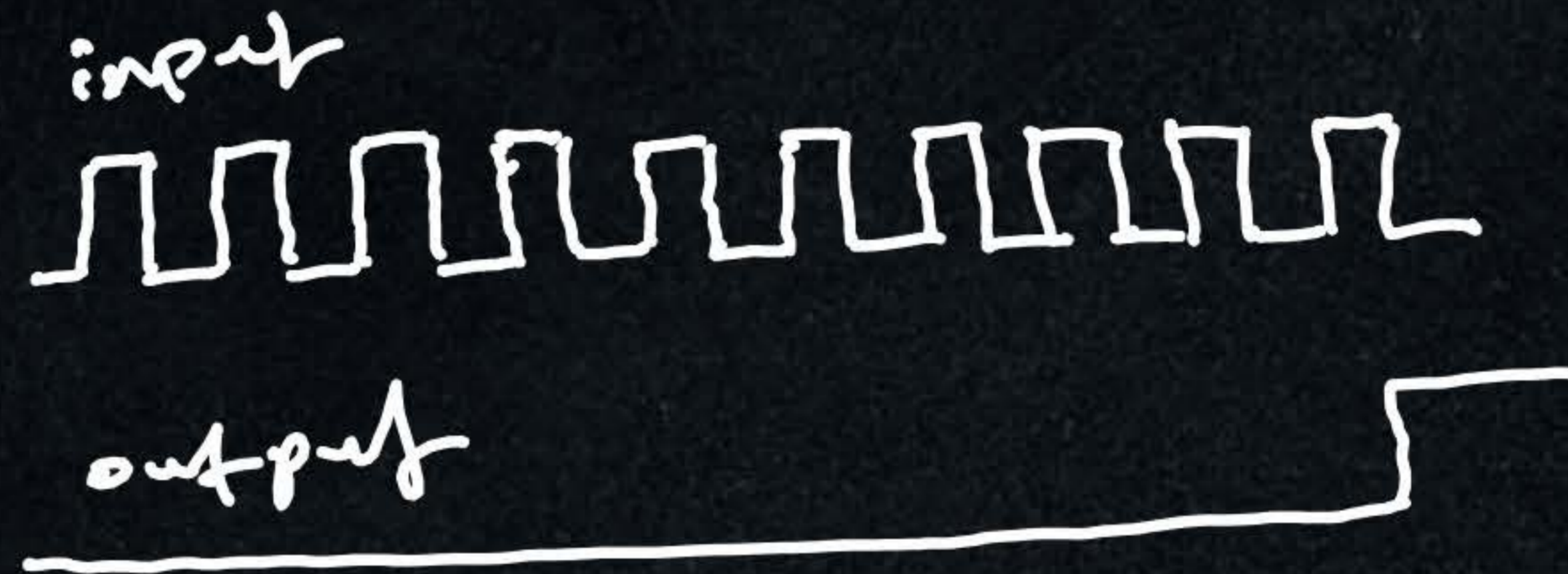Activated when set count reached after counting up from zero




Activated when zero reached after counting down

Addresses

Mitsubishi C460, C461, ---

Siemens C0, C1, ---

Mitsubishi

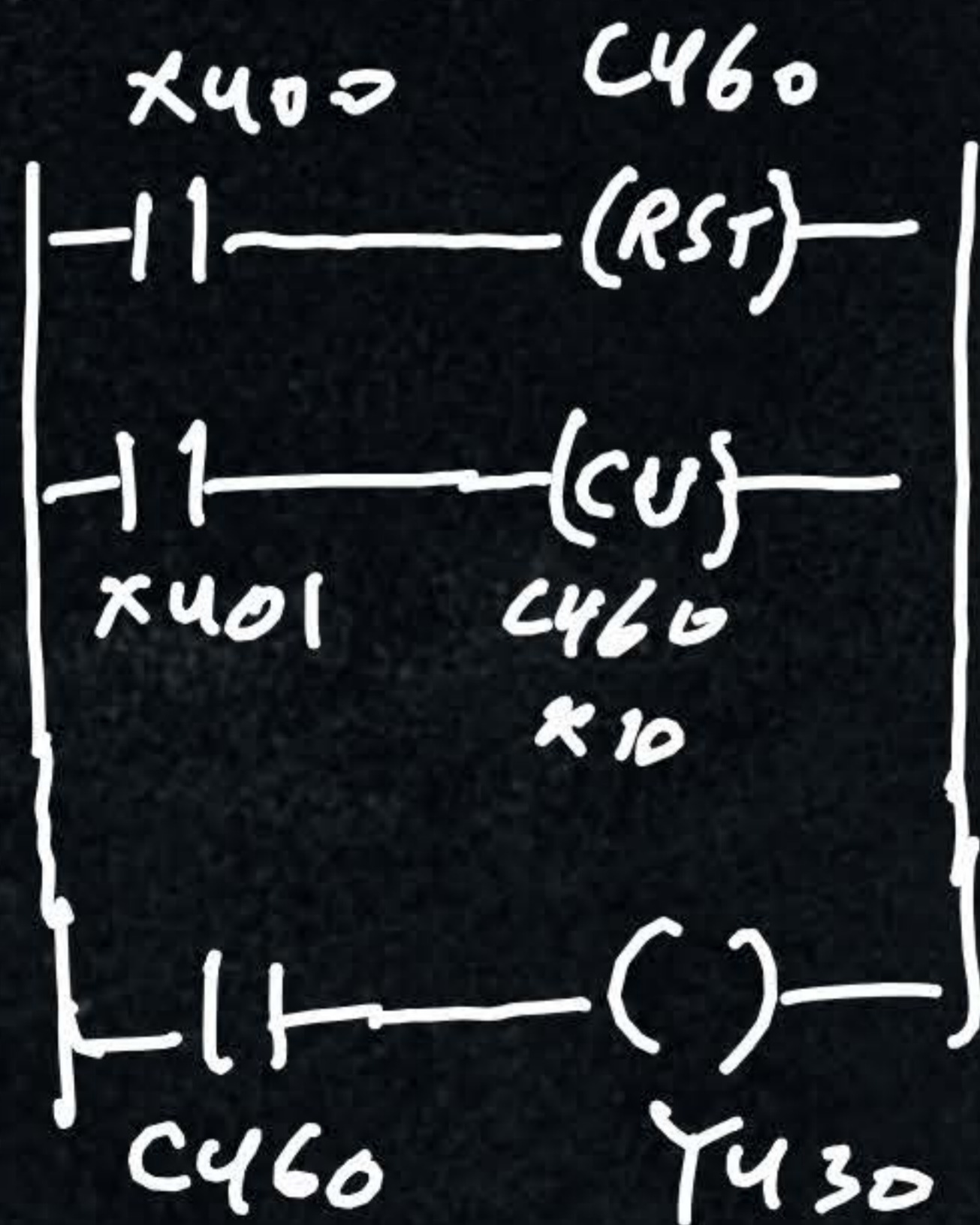


LD X400
RST C460

LD X401
CU C460 or OUT C460
X10

LD C460
OUT Y430

Siemens

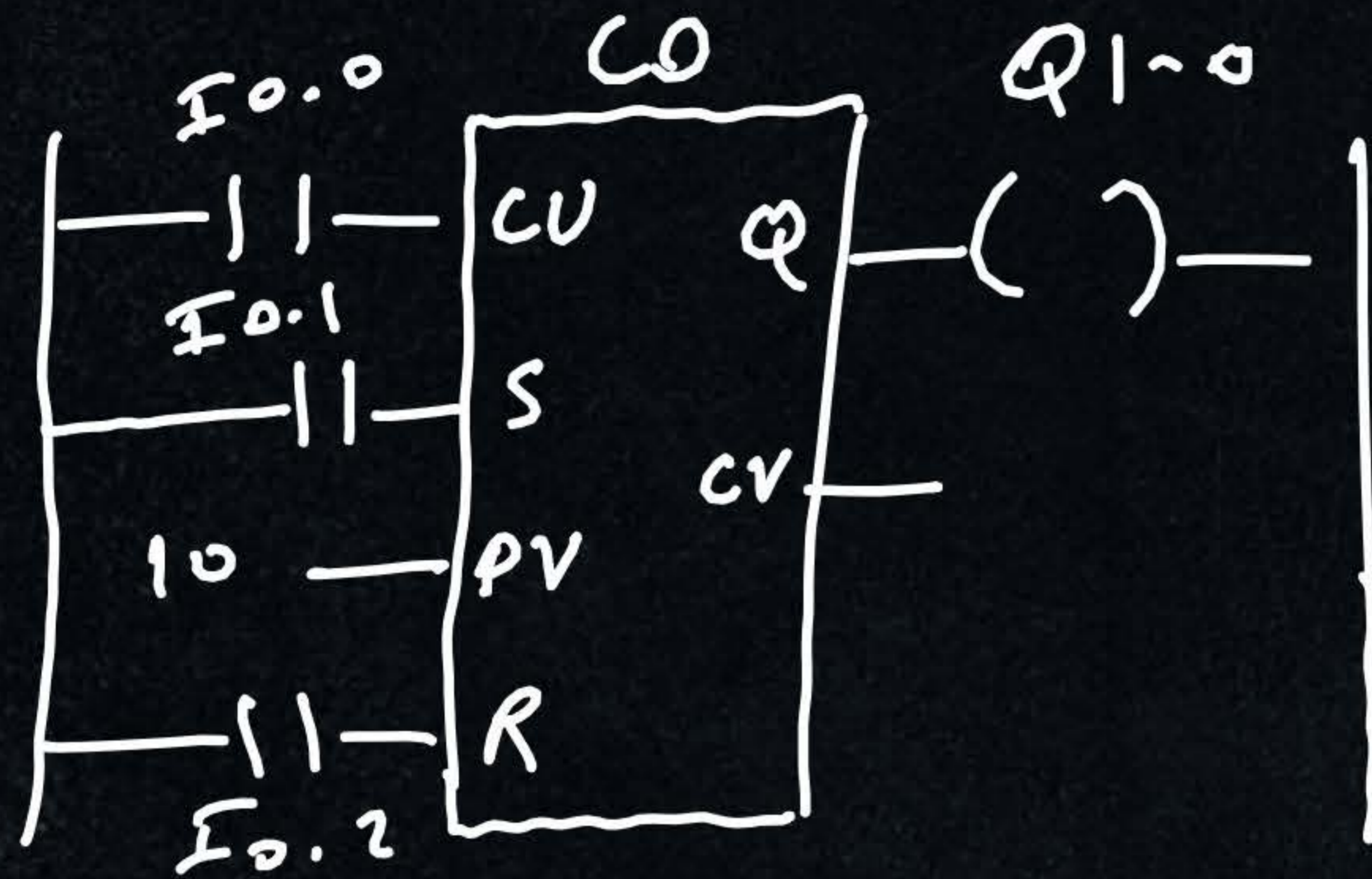

A I 0.0

A CO

CU CO

A I 0.1

= Q 1.0


S CO

LKC 10

A I 0.2

R CO

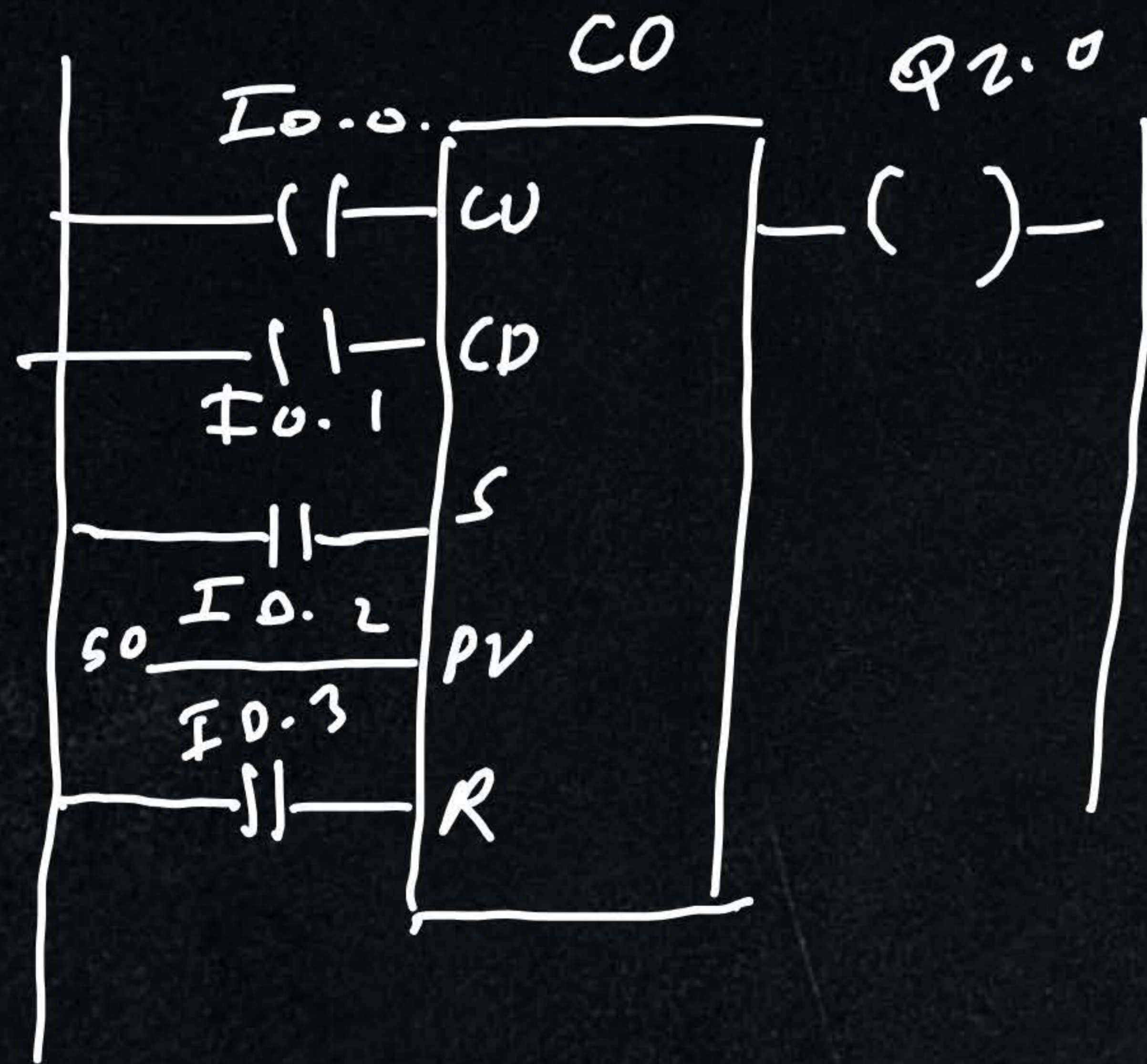EX: Design a counter that counts the cars entering a park or leaving it, and gives a message if the park is full.



```

A I 0.0
CU CO
A I 0.1
CD CO
A I 0.2
S CO
LKC 50
A I 0.3
R CO
ACD
= Q2.0

```

Special Machines

Applications:

- printers
- Disk drives
- Robotics
- Tape drives
- ⋮

⇒ Continuous energy conversion
is not required

Special Machines:

- stepper motors
- switched reluctance motors
- servo motors

Stepper Motors

- They rotate by a specific number of degrees in response to an electrical pulse.
- Typical step sizes are 1.8° , 2° , 2.5° , 5° , 7.5° , + 15° for each pulse.
- Stepper motors well-suited for open loop position control.
- Such motors develop torques ranging from $1 \mu\text{N.m}$ upto 40 N.m
 - ↓
tiny wrist watch motor
 - ↓
machine tool appli.
- Types of stepper motors
 - 1) Variable Reluctance (VR)
 - 2) permanent Magnet (PM)
 - 3) Hybrid.

① VR stepper motor

* It is constructed from ferromagnetic material with salient poles. The stator is made from a stack of steel laminations and has a number of equally spaced projecting poles (teeth) each wound with an exciting coil. The rotor has teeth of the same width as the stator poles.

- step angle = $\alpha = \frac{N_s - N_r}{N_s N_r} \times 360^\circ$

↓

angle, which the motor moves it per each pulse

N_s : stator poles

N_r : stator teeth

or $\alpha = \frac{360^\circ}{m_p N_r}$; where m_p is the number of stator phases.

- Resolution = Number of steps / revolution = $\frac{360^\circ}{\alpha}$

- If f is the stepping rate or stepping frequency or pulse rate in pulses per second (PPS), then the motor's speed is:

$$n = \frac{\alpha}{360^\circ} \times f \text{ [RPM]}$$

Drive circuit of VR stepper motor

